




# Computer Architecture

Hossein Asadi  
Department of Computer Engineering  
Sharif University of Technology  
[asadi@sharif.edu](mailto:asadi@sharif.edu)

# Today's Topics

- Register Transfer Language (RTL)

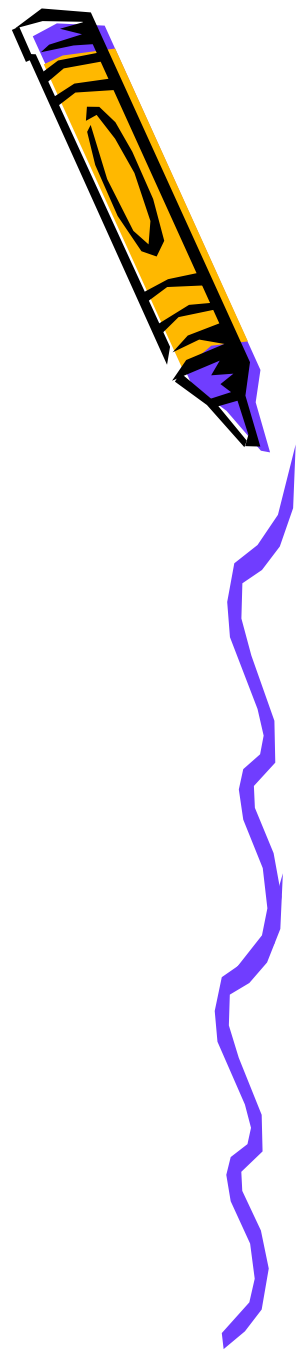


# Copyright Notice



- Parts (text & figures) of this lecture adopted from:
  - Computer Organization & Design, The Hardware/Software Interface, 3<sup>rd</sup> Edition, by D. Patterson and J. Hennessey, MK publishing, 2005.
  - "Intro to Computer Architecture" handouts, by Prof. Hoe, CMU, Spring 2009.
  - "Computer Architecture & Engineering" handouts, by Prof. Kubiawicz, UC Berkeley, Spring 2004.
  - "Intro to Computer Architecture" handouts, by Prof. Hoe, UWisc, Spring 2019.
  - "Computer Arch I" handouts, by Prof. Garzarán, UIUC, Spring 2009.



# Data Movements in Digital Systems

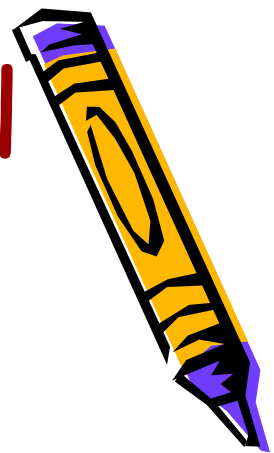

- Digital Systems Consists of
  - Combinational logic
    - AND gate, OR gate, NOT gate, etc
  - Sequential elements
    - FFs, latches
- Question:
  - How we can describe data movements in digital systems?
    - Gate-level?
      - Too much details and very complicated



# RTL & Micro-Operation




- Data Movement Characterized in terms of:
  - Registers
    - Set of flip-flops/latches
  - Operations done on registers
- Register Transfer Language (RTL)
  - Data movement at register level
  - A language to describe behavior of computers in register flow format
- Micro-operation (Micro-ops or uOps)
  - Functions performed on registers
    - Shift, clear, load, increment, etc.


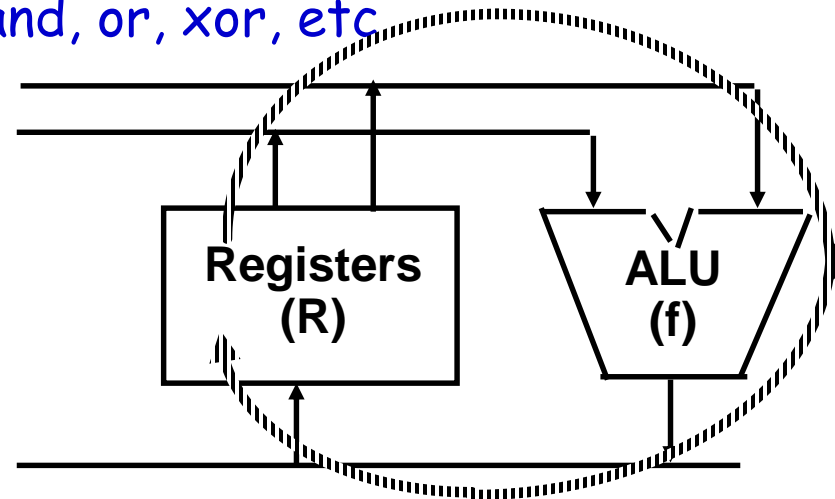
# Micro-Operation



- Definition:
  - An elementary operation performed on information stored in one or more registers
    - During one clock pulse
  - $R \leftarrow F(R, R)$ 
    - F: shift, load, clear, and, or, xor, etc



# High-Level Description of Computer uArch



- In Terms of RTL & uOps:
  - Set of registers and their functions
  - Microoperations set
    - Set of allowable uops provided by uArch
  - Control signals that initiate sequence of uOps to perform functions



# Register Transfer Language




- Our Focus in RTL
  - System's registers
  - Data transfers between them
  - Data transformations in them






# Designation of Registers

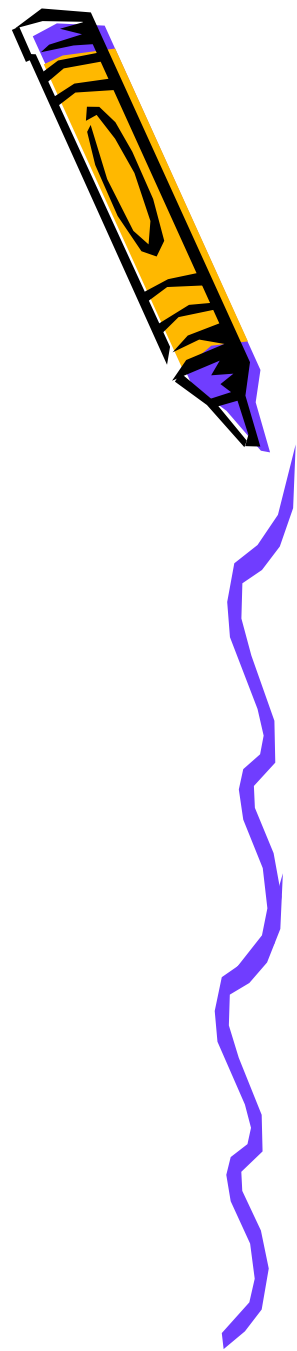

- How Registers Designated?
  - Using capital letters
  - Sometimes followed by numbers
    - e.g., A, R13, IR
- Often names indicate function:
  - PC
    - Program Counter
  - IR
    - Instruction Register
  - MAR
    - Memory Address Register



# Designation of Registers (cont.)

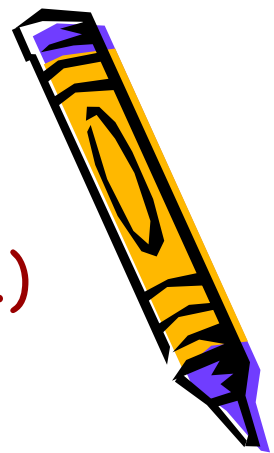


- How Registers Represented?
  - Registers and their contents can be viewed and represented in *various ways*
  - A register can be viewed as a single entity:



- Registers may also be represented showing bits of data they contain



# Designation of Registers (cont.)

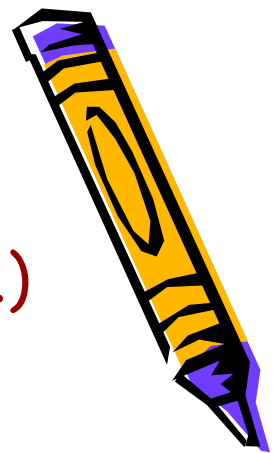

- How Registers Represented?
  - Common ways of drawing the block diagram of a register

Register



15 0



Numbering of bits

Showing individual bits




15 8 7 0



Subfields




# Data Transfer

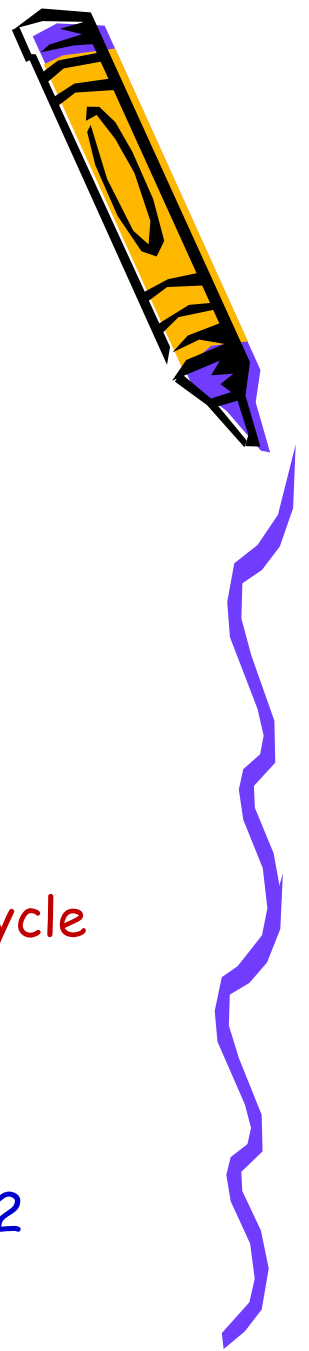

- Data Transfer:
  - Copying contents of one reg to another reg
- Example:
  - $R2 \leftarrow R1$
  - Contents of R1 copied (loaded) into R2
  - A **simultaneous** transfer from R1 to R2
    - All bits transferred at same time on **one clock cycle**
    - R1: source, R2: destination
    - Data lines from R1 to R2
  - This is a **non-destructive**
    - Contents of R1 not altered by copying them to R2
  - Control lines to perform action



# Data Transfer (cont.)

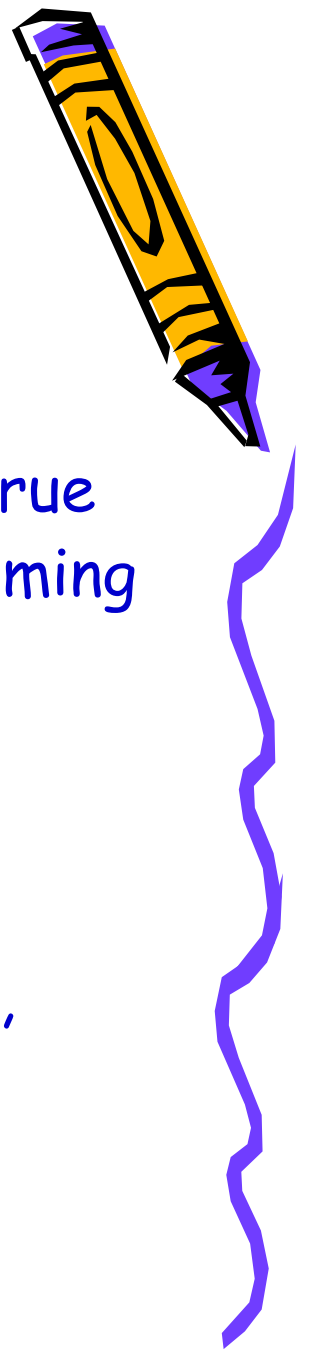

- Controlled (Conditional) Data Transfer
  - Actions will occur if a certain condition is true
  - Similar to an "if" statement in SW programming
  - Represented as:

P:  $R2 \leftarrow R1$

"if  $P = 1$ , then load contents of  $R1$  into  $R2$ ",  
i.e., if  $(P = 1)$  then  $(R2 \leftarrow R1)$




# Controlled Data Transfer


- HW Implementation

P:  $R2 \leftarrow R1$

Block diagram

 

Timing diagram

 

- Registers assumed to use *positive-edge-triggered* flip-flops

# Data Transfer (cont.)




- Simultaneous Micro-operations
  - If two or more operations are to occur simultaneously, they are separated with commas

P:  $R3 \leftarrow R5, MAR \leftarrow IR$

- Here, if control function  $P = 1 \rightarrow$ 
  - Load contents of R5 into R3
  - At same clock, load contents of IR into MAR



# Data Transfer (cont.)

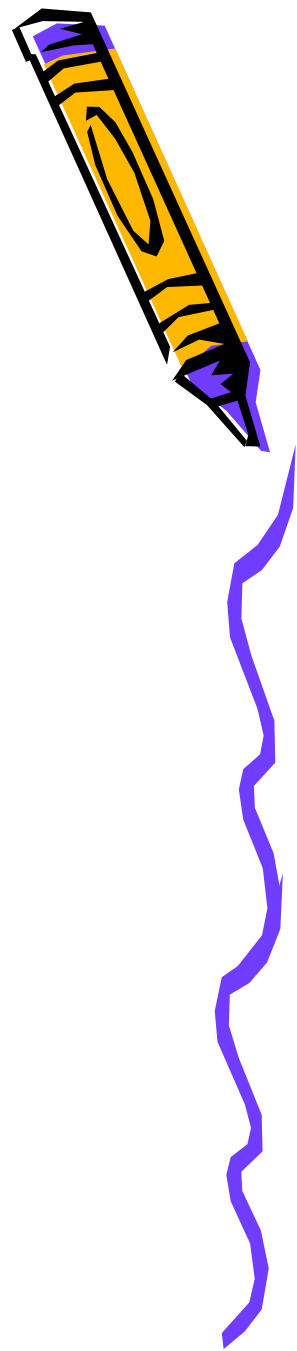

- Practice
  - Draw hardware implementation of following statement
  - P:  $R1 \leftarrow R2, R2 \leftarrow R1$






# Blocking and Non-Blocking Statements in RTL




- Non-Blocking Statements
  - Statement scheduled and executed together with other non-blocking assignments
  - Example in Verilog
    - $A \leq B$
    - $B \leq C$
- Blocking Statements
  - Statement executed sequentially
  - Example in Verilog
    - $A = B$
    - $B = C$



# Practice

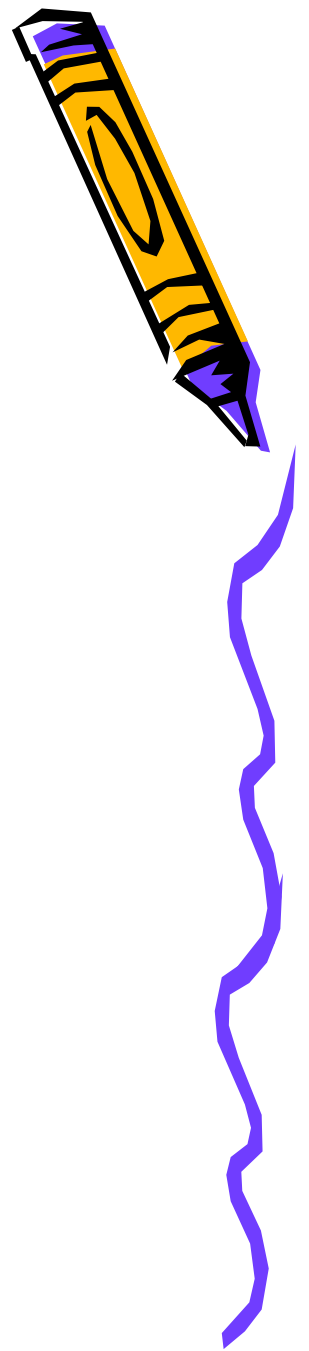

 - Code1
  - $R1 \leftarrow R2, R2 \leftarrow R1$
- Code2
  - $R1 \leftarrow R2$
  - $R2 \leftarrow R1$
- Code3
  - $R1 \leftarrow R2$
  - $R2 \leftarrow R1$
- Question:
  - New values of R1 and R2?



# Common Micro-Ops



- **Transfer** ( $R0 \leftarrow R1$ )
  - Transfers data from a reg to another reg
- **Arithmetic** ( $R0 \leftarrow R1 + R2$ )
  - Performs arithmetic on data in registers
- **Logic/Bit Manipulation**
  - Performs bit (Boolean) operations on data  
 $R0 \leftarrow R1 \& R2$  ; or  $R0 \leftarrow R1 | R2$
- **Shift**
  - Shift data in regs by n bits positions  
 $R0 \leftarrow R1 \ll 3$  ; or  $R0 \leftarrow R2 \gg 2$



# RTL & MIPS Assembly



MIPS Code	RTL Code
add \$t0, \$s2, \$s4	$\$t0 \leftarrow \$s2 + \$s4$
and r1, r2, r3	$r1 \leftarrow r2 \wedge r3$
lw \$s1, 100(\$s2)	$\$s1 \leftarrow \text{Mem}[\$s2 + 100]$
sw \$s1, 100(\$s2)	$\text{Mem}[\$s2 + 100] \leftarrow \$s1$



# Summary of Reg Transfer & Micro-Ops



$A \leftarrow B$

$AR \leftarrow DR(AD)$

$A \leftarrow \text{constant}$

$ABUS \leftarrow R1,$

$R2 \leftarrow ABUS$

AR

DR

$M[R]$

M

$DR \leftarrow M$

$M \leftarrow DR$

Transfer content of reg. B into reg. A

Transfer content of AD portion of reg. DR into reg. AR

Transfer a binary constant into reg. A

Transfer content of R1 into bus A and, at the same time,

Transfer content of bus A into R2

Address register

Data register

Memory word specified by reg. R

Equivalent to  $M[AR]$

Memory *read* operation: transfers content of memory word specified by AR into DR

Memory *write* operation: transfers content of DR into memory word specified by AR



# Summary of Reg Transfer & Micro-Ops (cont.)




- $GPR[rs]$ 
  - General Purpose Registers
  - A register from Register File indicated by index  $rs$
- $RF[rs]$ 
  - Register File


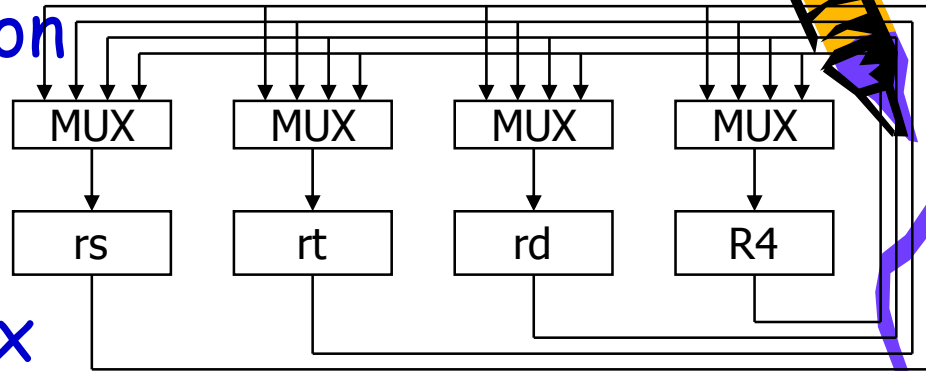
# Register Transfers: Interconnect


- Point-to-Point Connection

- Dedicated wires
- Muxes on inputs of each register




- Common Input from mux

 - Load enables for each register
- Control signals for multiplexer



- Common Bus with Output Enables

 
- Output enables and load enables for each register


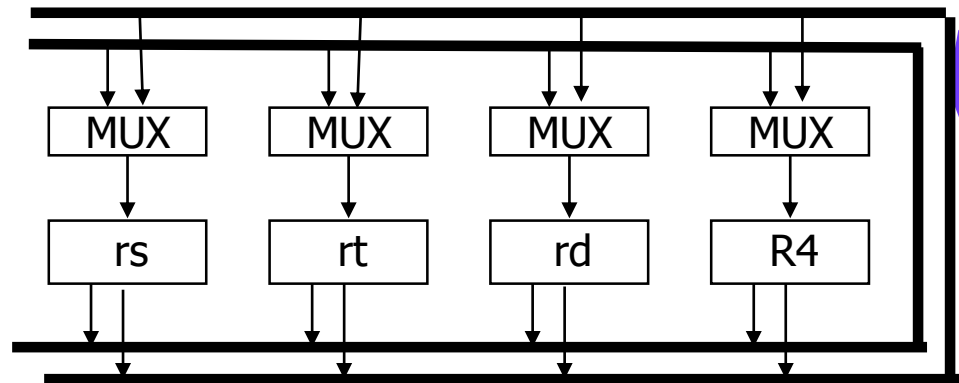
# Register Transfer: Multiple Busses




- One transfer per bus
- Each set of wires can carry one value
- State Elements
  - Registers
  - Register files
  - Memory
- Combinational Elements
  - Busses
  - ALUs
  - Memory (read)





# Connecting Registers

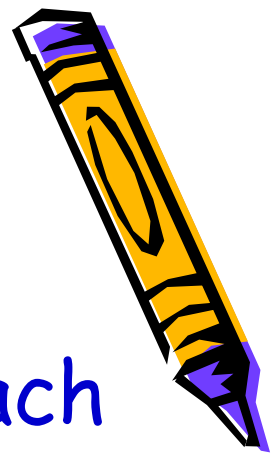


- How to Connect 32 Registers to each other?
  - Impractical to have data and control lines to directly allow each register to be loaded with contents of every possible other registers
- To completely connect  $n$  registers
  - $\rightarrow n(n-1)$  lines
  - $O(n^2)$  cost
  - Not a realistic approach to use in a large system



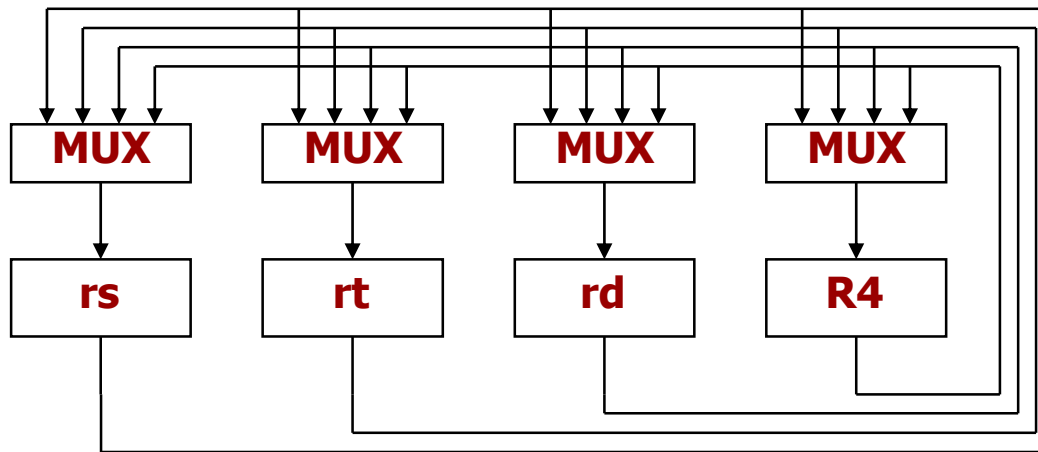
# Connecting Registers

- Point-to-Point Connection
  - Dedicated wires
  - Muxes on inputs of each register



# Connecting Registers (cont.)


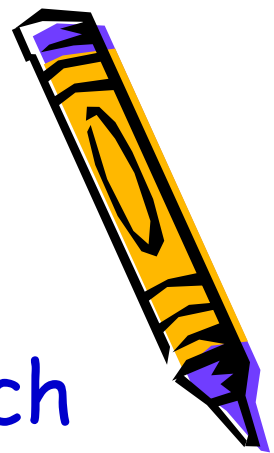


- Instead, Take a Different Approach
  - One centralized set of circuits for data transfer, called **bus**
  - Have control circuits to select:
    - Which reg as source
    - Which reg as destination
- Bus Definition:
  - A path (of a group of wires) over which information is transferred, from any of several sources to any of several destinations
  - A group of wires with multiple drivers



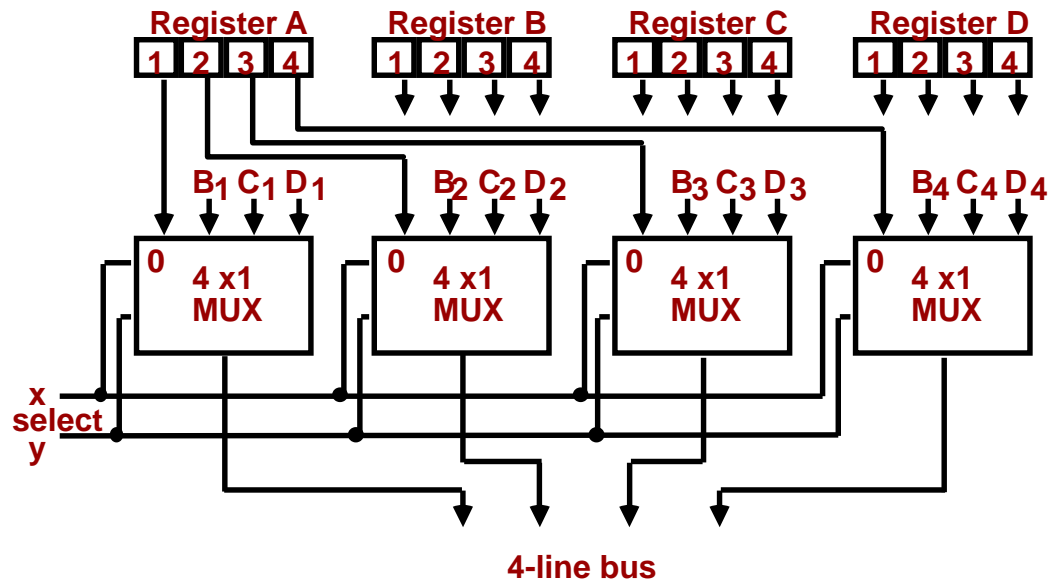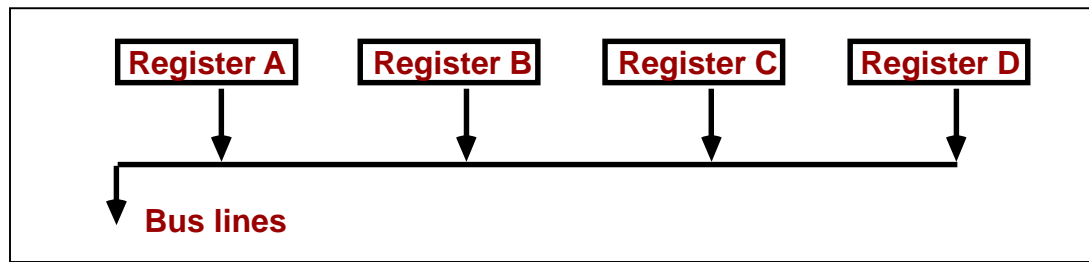
# Bus Transfer



- From a register to bus:  $BUS \leftarrow R$



# Bus Transfer: Bus to Destination Reg

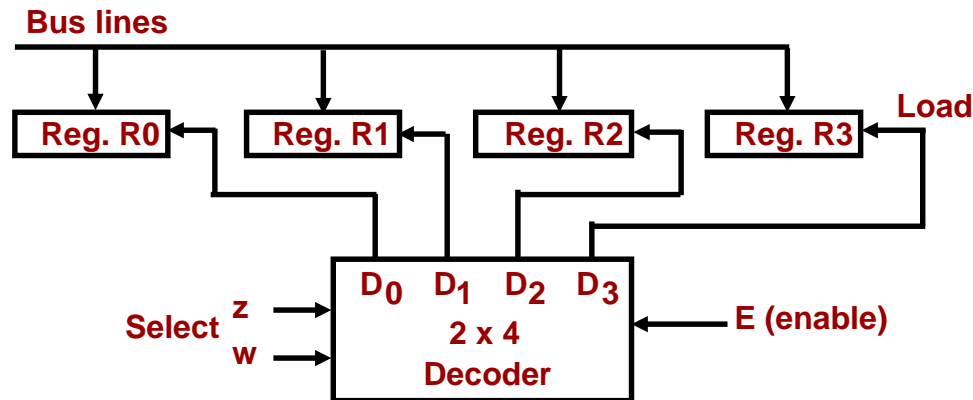

## Three-State Bus Buffers

 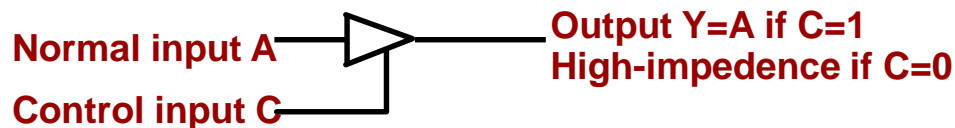


## 3-State Buf vs Mux implementation

Pros: area efficient & more scalable

Cons: probably more power consumption (leakage current in high-Z)



# Bus vs. Point-To-Point

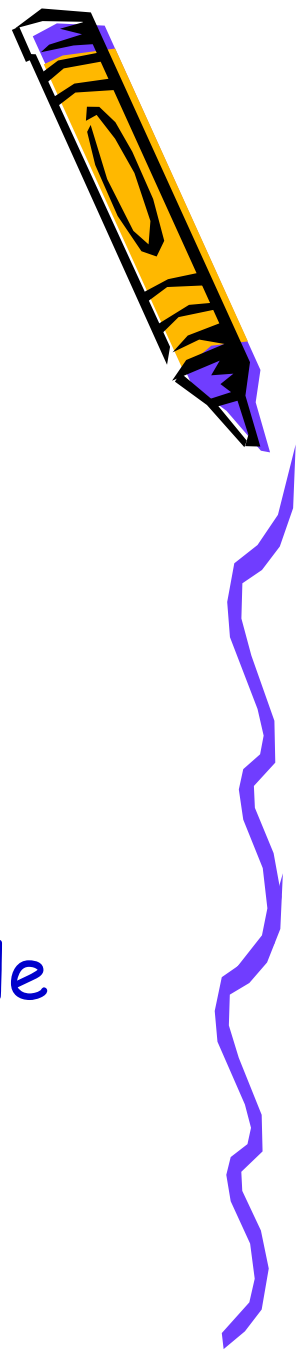


- Pros (Advantages)
  - Much less routing
  - Less area
  - Easy to scale
- Cons (Disadvantages)
  - Only one data transfer per clock cycle


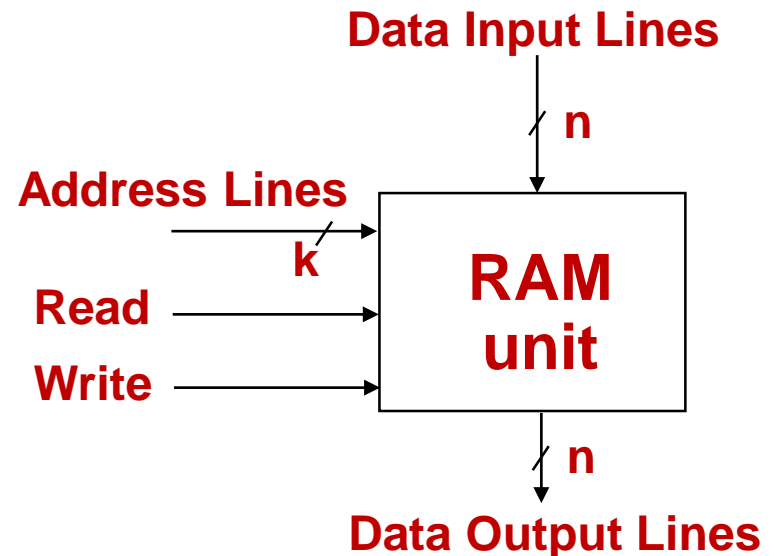
# Memory & Memory Transfer




- Memory (RAM)
  - Can be thought as a sequential circuit containing some number of registers
- Assume RAM with  $r = 2^k$  Words
  - $n$  data input lines
  - $n$  data output lines
  - $k$  address lines
  - A read control line
  - A write control line


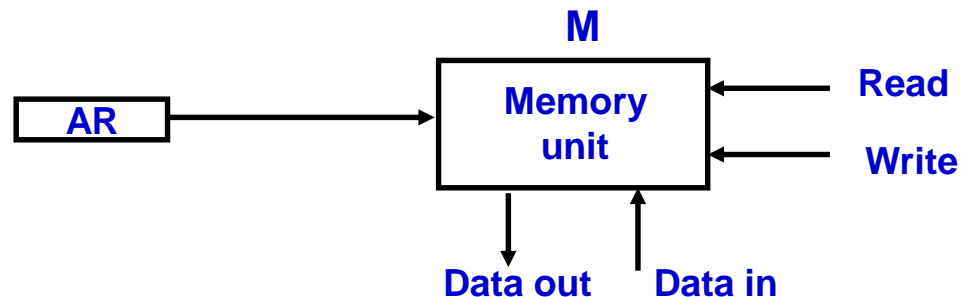
# Memory & Memory Transfer (cont.)



- Memory Transfer
  - Memory viewed at register level as a device (M)
  - Should specify which address in memory
    - Since it contains multiple locations
- Memory Accesses
  - Provide target address in a special register
    - Memory Address Register (MAR, or AR)
  - Contents of MAR sent to memory address lines





# Memory & Memory Transfer (cont.)



- Memory Read
  - To read a value from a location in memory and load it into a register
  - RTL notation looks like this:

**MAR  $\leftarrow$  Address**

**R1  $\leftarrow$  M[MAR]**



# Memory & Memory Transfer (cont.)



- Memory Write

- To write a value from a reg to a location in memory
- RTL notation looks like this:

**MAR  $\leftarrow$  address**

**M[MAR]  $\leftarrow$  R1**



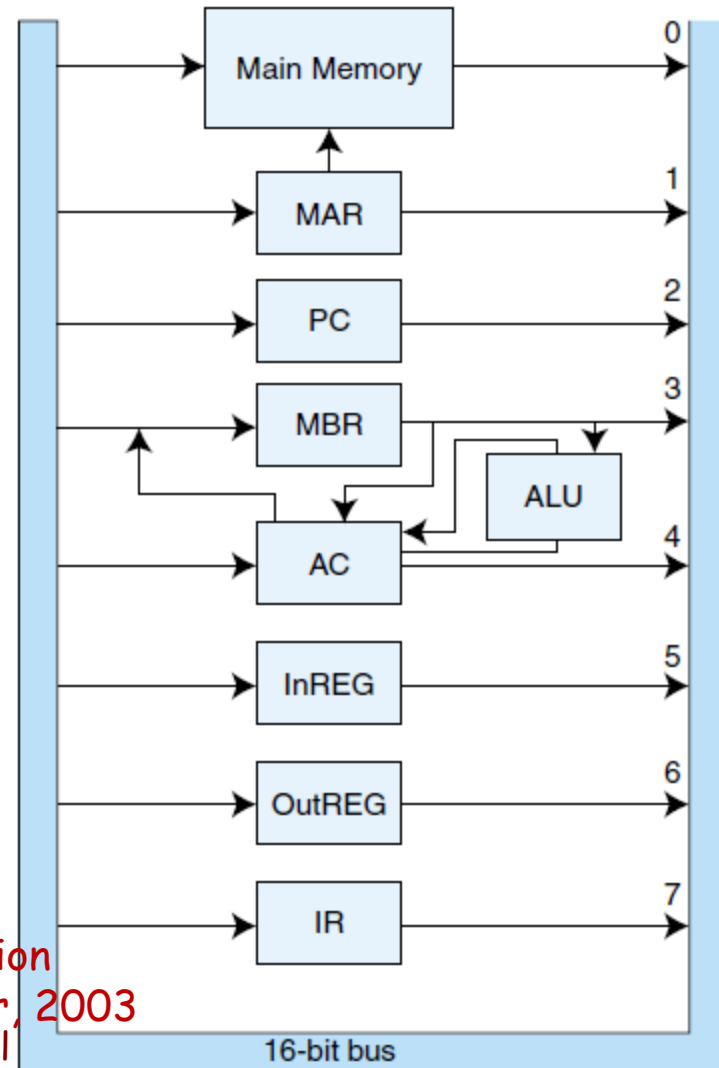
# RTL Example




- Memory Buffer Register
  - MBR
- Accumulator
  - AC
- Program Counter
  - PC
- Memory Address Register
  - MAR
- Instruction Register
  - IR


The Essentials of Computer Organization  
& Architecture, by L. Null and J. Lobur, 2003  
Lecture 3 Sharif University of Technol



# RTL Example (cont.)

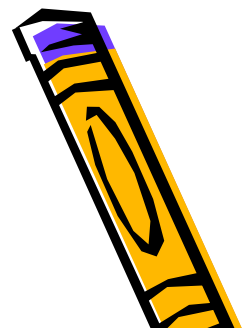


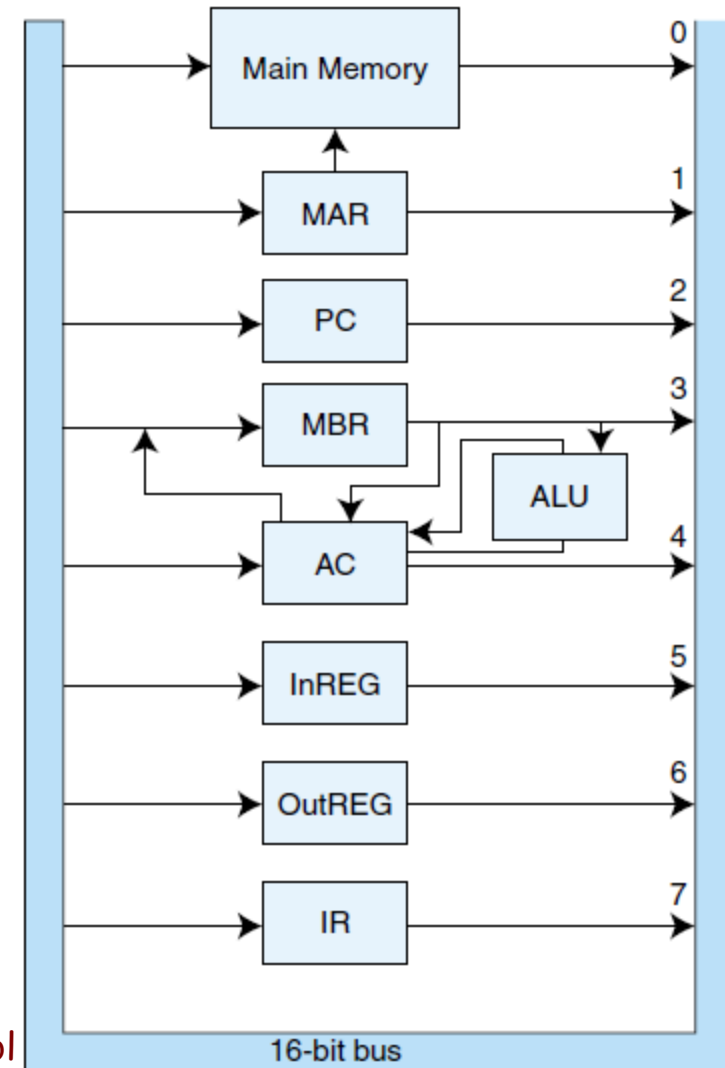- Store X
  - $MAR \leftarrow X, MBR \leftarrow AC$
  - $M[MAR] \leftarrow MBR$
- Add X
  - $MAR \leftarrow X$
  - $MBR \leftarrow M[MAR]$
  - $AC \leftarrow AC + MBR$


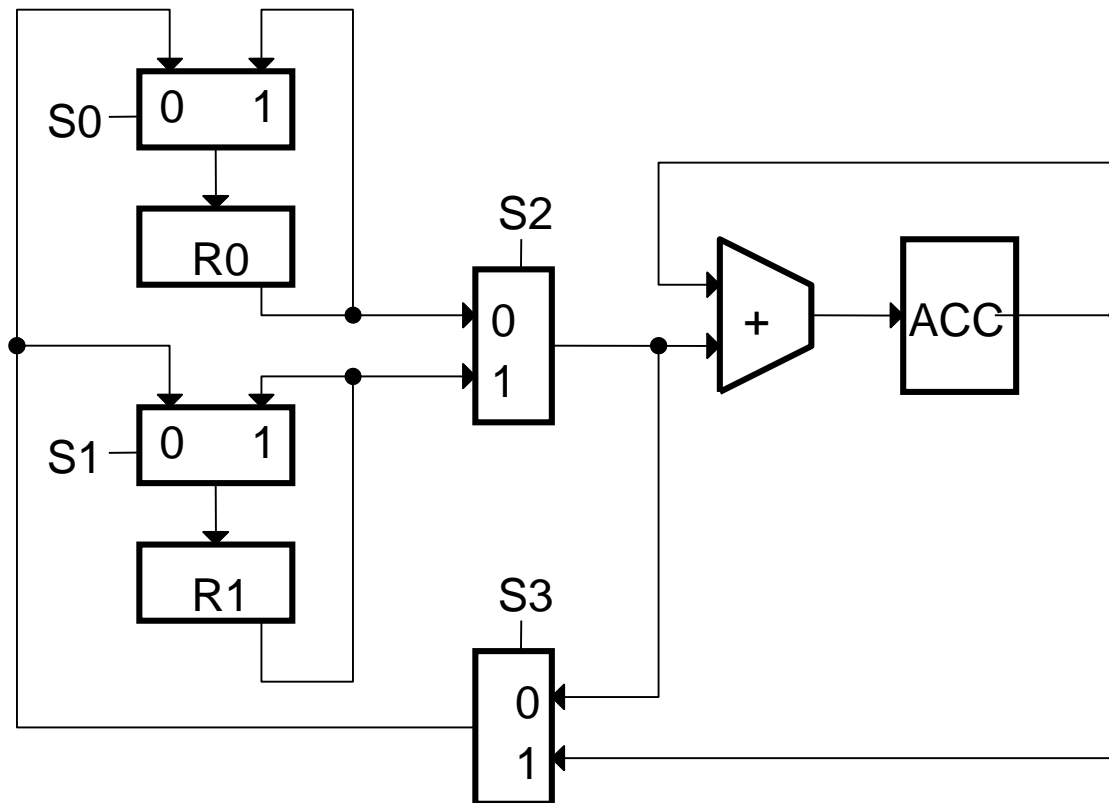
# Practice


- What is RTL description of this circuit?


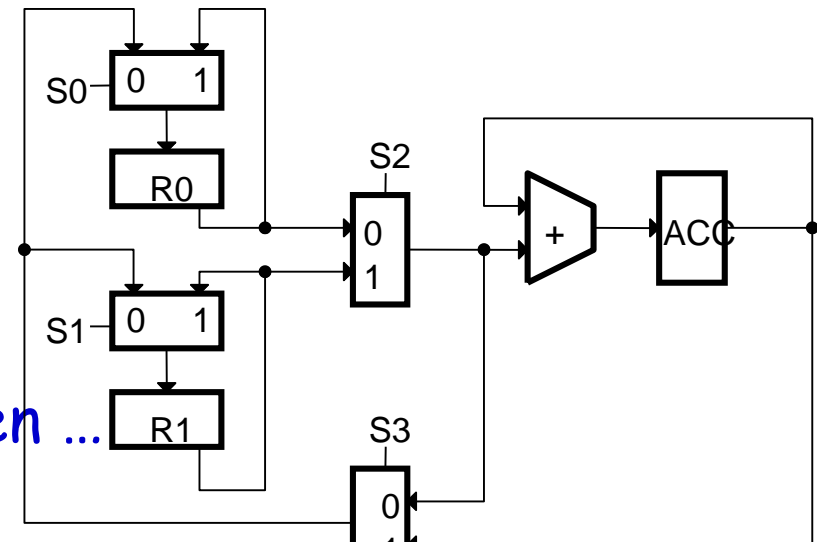
# Practice (cont.)



- In Each Clock Cycle:
  - $\sim S3.\sim S2.\sim S1: R1 \leftarrow R0$
  - $\sim S3.S2.\sim S0: R0 \leftarrow R1$
  - $S3.\sim S2.\sim S1: ACC \leftarrow R0 + ACC$
  - $S3.S2.\sim S0: ACC \leftarrow R1 + ACC$
  - What else?
    - $R1 \leftarrow ACC$
    - ...
- Or use "if-then-else"
  - If ( $S3=1$  and  $S1=0$ ) then ...



# Backup

