

Computer Architecture

Hossein Asadi
Department of Computer Engineering
Sharif University of Technology
asadi@sharif.edu



Lecture 7

What Learned So Far?

- Lecture 1
 - Review
 - ISA, computer organization, & addressing modes
 - uArchictecure
 - uArch basic blocks



- · Lecture 2
 - Performance metrics
 - · Latency, throughput, MIPS, & MFLOPS
 - CPU time
 - · CPI, IC, & clock cycle time
 - Performance evaluation
 - Standard benchmarks
 - Speedup
 - Amdahl law



- Lecture 3
 - Register level transfer language (RTL)
 - Micro-operations
 - Bus transfer & bus implementation



- · Lecture 4
 - Arithmetic Implementations
 - Ripple Carry (RC) Adder
 - Carry Select Adder (CSA)
 - Carry Look-Ahead (CLA) Adder
 - Combinational Multiplier
 - Sequential Multiplier
 - Booth Multiplier



- Lecture 5
 - Single-cycle datapath design
 - Datapath elements
 - PC, I-Mem, D-Mem, ALU, GPR, address bus, & data bus
 - Combining datapaths
 - Datapath for reg-reg operations
 - Datapath for load/store operations
 - Datapath for branch operations



- · Lecture 6
 - Control logic design for single-cycle CPU
 - ALU control design
 - Processor main control unit design
 - Implementing unconditional branch



Today's Topics

- · Efficiency of Single-Cycle Datapath
- · Multi-Cycle Datapath Design



Copyright Notice

- Parts (text & figures) of this lecture adopted from:
 - Computer Organization & Design, The Hardware/Software Interface, 3rd Edition, by D. Patterson and J. Hennessey, Morgan Kaufmann publishing, 2005.
 - "Intro to Computer Architecture" handouts, by Prof. Hoe, CMU, Spring 2009.
 - "Computer Architecture & Engineering" handouts, by Prof. Kubiatowicz, UC Berkeley, Spring 2004.
 - "Intro to Computer Architecture" handouts, by Prof. Hoe, UWisc, Fall 2009.
 - "Computer Arch I" handouts, by Prof. Garzarán, UIUC, Spring 2009. Lecture 7



Performance of Single-Cycle uArch


- · Simple but Inefficient Performance
- · Why?
 - Clock cycle determined by longest possible path
 - Clock cycles of all instructions same length
 - CPI = 1
- Longest Possible Path?
 - Load datapath



Single-Cycle CPU Clock Cycle Time

با توجه به اسلاید قبل الان طول هر clock cycle برابر ۴.۷ می شود

	I-cache	Decode, R-Read	ALU	PC update	D-cache	R-Write	Total
R-type	1	1	.9	-	-	.8	3.7
Load	1	1	.9	-	1	.8	4.7
Store	1	1	.9	-	1	-	/ 3.9
beq	1	1	.9	.1	-	- /	3.0

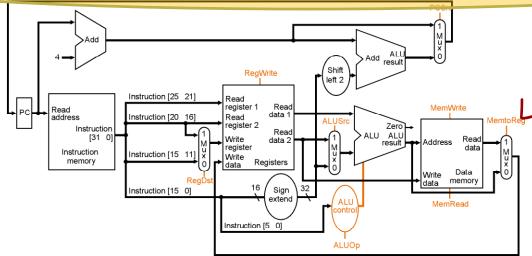

Clock cycle time

= 4.7 + setup + hold

Load on critical path

Setup time?

Hold time?


Critical path?

Lecture 7

Sharif University of Technology, Spring 2019

Definition

· Setup & Hold Time

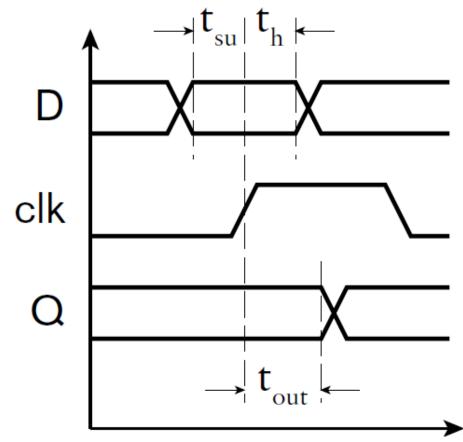




Sharif University of Technology, Spring 2019

Definition

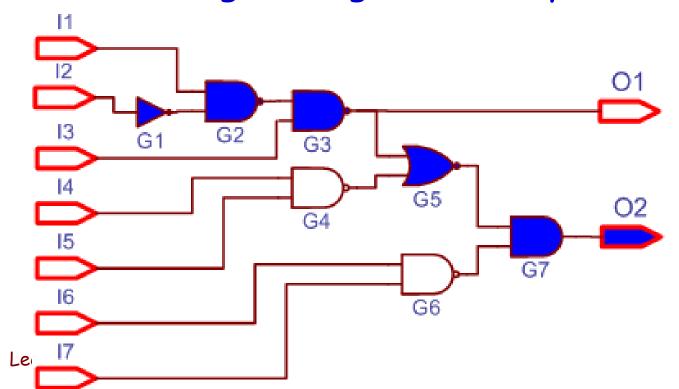- Critical Path
 - A path through combinational circuit that takes as long or longer than any other





Multicycle Implementation

Goal: Balance amount of work done each cycle

	I cache	Decode, R-Read	ALU	PC update	D cache	R- Write	Total
R-type	1	1	.9	-	-	.8	3.7
Load	1	1	.9	-	1	.8	4.7
Store	1	1	.9	-	1	-	3.9
beq	1	1	.9	.1	-	-	3.0

- Load needs 5 cycles
- Store and R-type need 4
- beq needs 3



Will Multi-Cycle Design be Faster?


	I cache	Decode, R-read	ALU	PC update	D cache	R-write	Total
R-type	1	1	.9	-	-	.8	3.7
Load	1	1	.9	-	1	.8	4.7
Store	1	1	.9	-	1	-	3.9
beq	1	1	.9	.1	-	-	3.0

Let's assume setup + hold time = 100ps = 0.1 ns

Single Cycle Design:

Clock cycle time = 4.7 + 0.1 = 4.8 ns time/inst = 1 cycle/inst * 4.8 ns/cycle = 4.8 ns/inst

Multicycle Design:

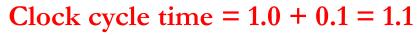



Will Multi-Cycle Design be Faster? (cont.)

	Cycles needed	Instruction frequency
R-type	4	60%
Load	5	20%
Store	4	10%
beq	3	10%

What is **CPI** assuming this instruction mix?

$$CPI = 4* 0.6 + 5*0.2$$


+ $4*0.1 + 3*0.1 = 4.1$

Let's assume setup + hold time = 0.1 ns

Single Cycle Design:

Clock cycle time = 4.7 + 0.1 = 4.8 ns time/inst = 1 cycle/inst * 4.8 ns/cycle = 4.8 ns/inst

Multicycle Design:

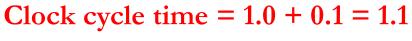


time/inst = CPI * 1.1 ns/cycle = 4.1 * 1.1 = 4.5



Will Multi-Cycle Design be Faster? (cont.)

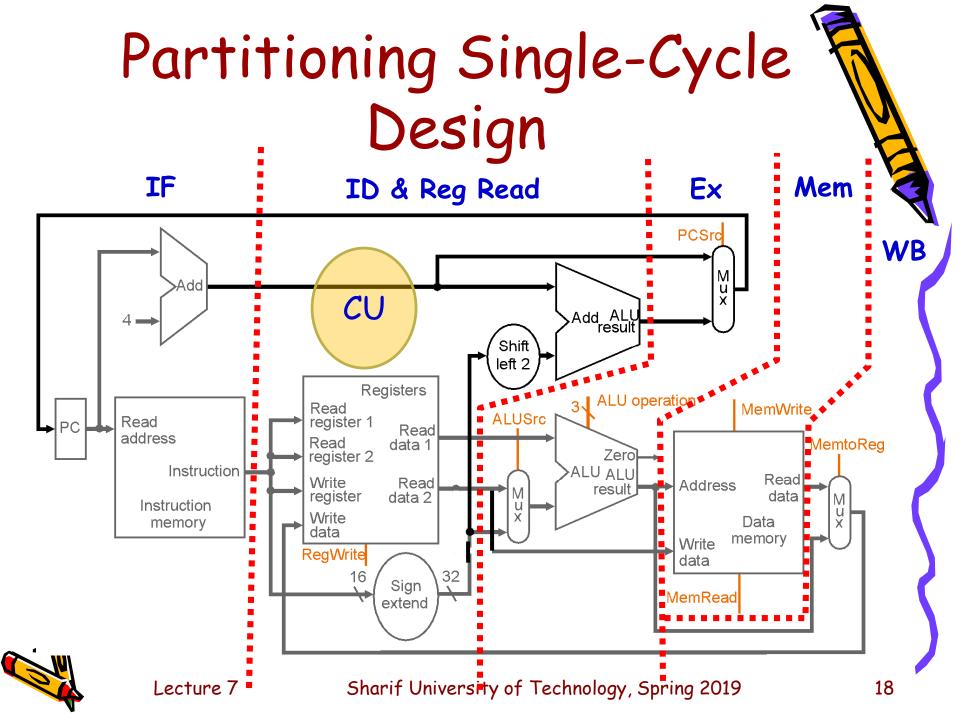- Much Smaller Clock Cycle Time
 - Compared to single-cycle datapath
- Possibly Faster Runtime
 - Compared to single-cycle datapath
 - Depends on:
 - How partitioning is performed
 - Frequency of instructions in benchmark programs





Where to Add Registers? IF Mem ID & Reg Read Ex **PCSrd** Μ Add CU Add ALU. result Shift left 2 Registers ALU operation **MemWrite** Read ALUSrc Read register 1

Read

Read

data 2

Sign

extend

data 1

Read

Write

Write

data

register

RegWrite

register 2

address

Instruction |

Lecture 7

Instruction

memory



Zero ALU ALU!

result J

-MemtoReg

Read

data

Data

memory


Address

Write

data


MemRead

Multicycle Datapath

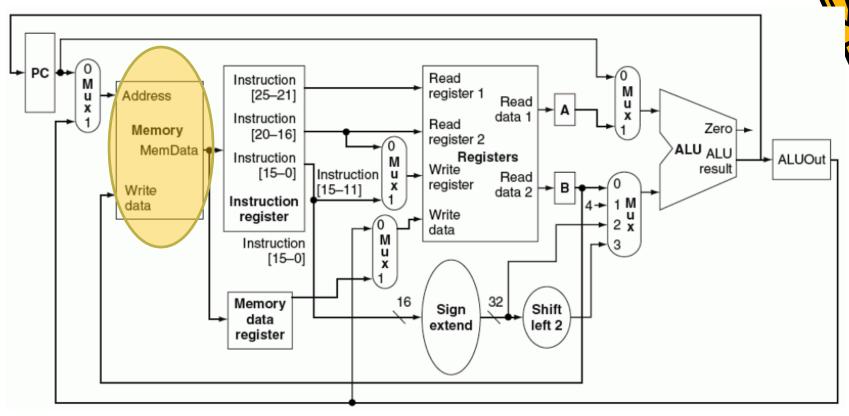

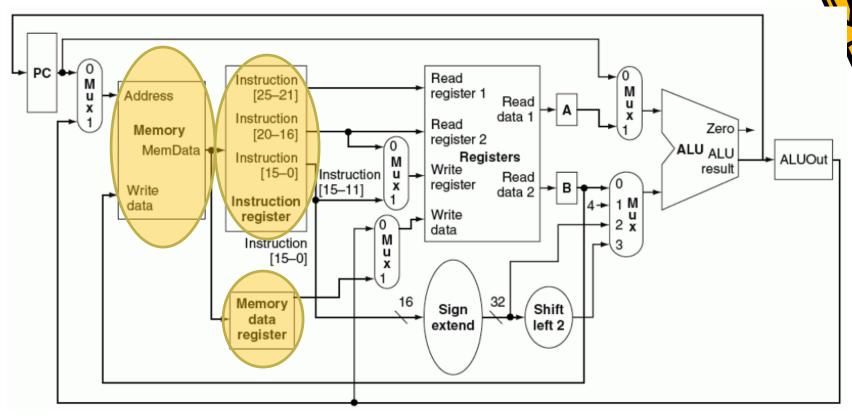
- Unified Memory
 - Used as both I-cache & D-cache
- Combines address busses of single-cycle datapath
 - Uses a MUX to select PC or ALU output





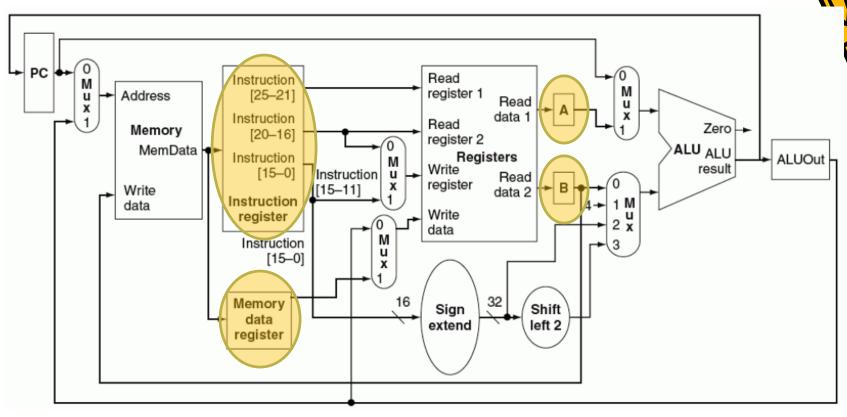
- •Instruction Register
 - \cdot IR \leftarrow Mem[PC]
- •Memory Data Register
 - •MDR ← Mem[ALUOut]





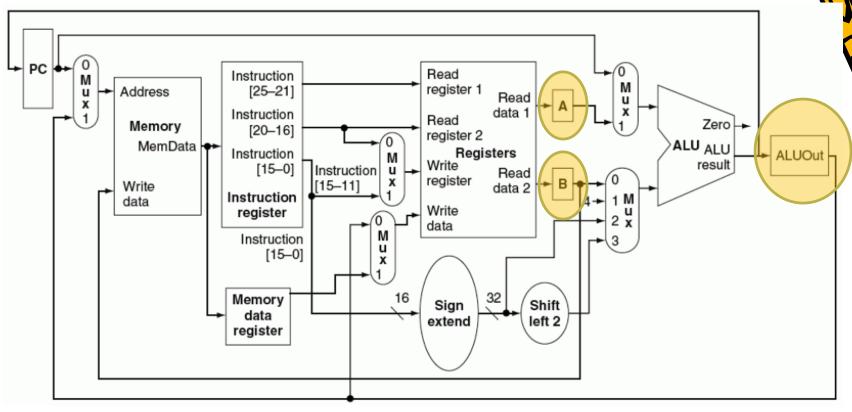- •Reg A & B
 - A **GPR**[IR[25:21]]
 - B **←** GPR[IR[20:16]]






- •ALUOut ← ALU result
- •ALUOut is then either
 - Written to GPR
 - Or used as an address for Memory



Multi-Cycle Datapath vs. Single-Cycle Datapath

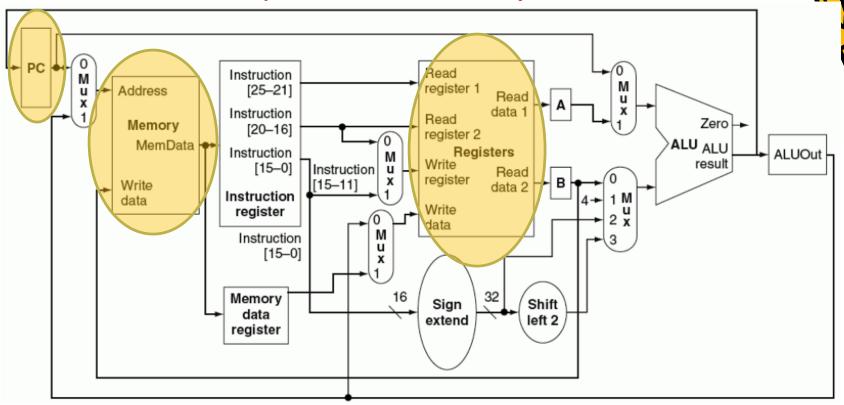- · Hardware Elements
 - Single memory unit
 - Used for both in instruction & data
 - Instruction & data must be accessed in different clock cycles
 - Single ALU unit
 - Rather than Using ALU and two adders
 - One or more registers added after every major functional unit






- ·User-Visible State Elements
 - PC

Lecture 7

- Memory
- Register file




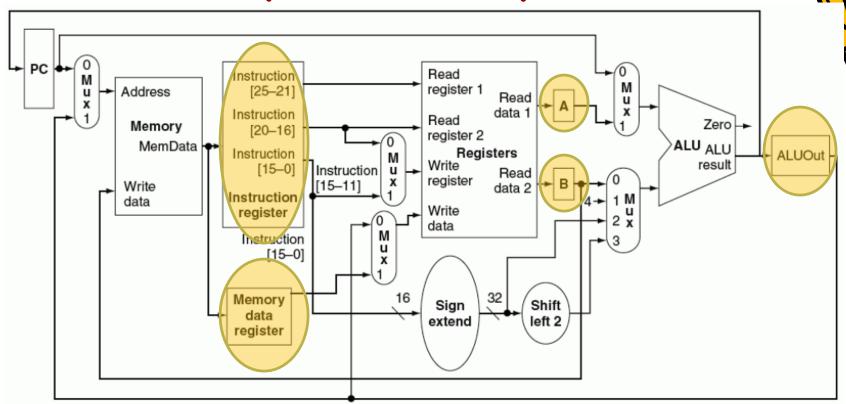


- ·Non-User-Visible State Elements
 - Instruction Register (IR)
 - Memory Data Register (MDR)
 - · Reg A & Reg B
 - ALUout

Lecture 7



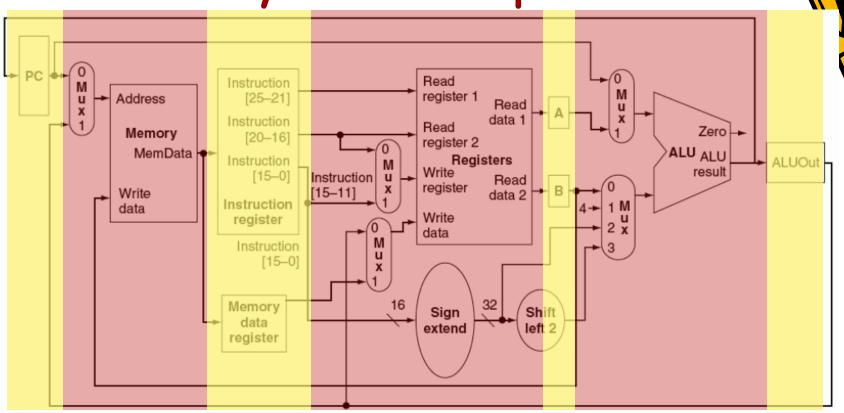

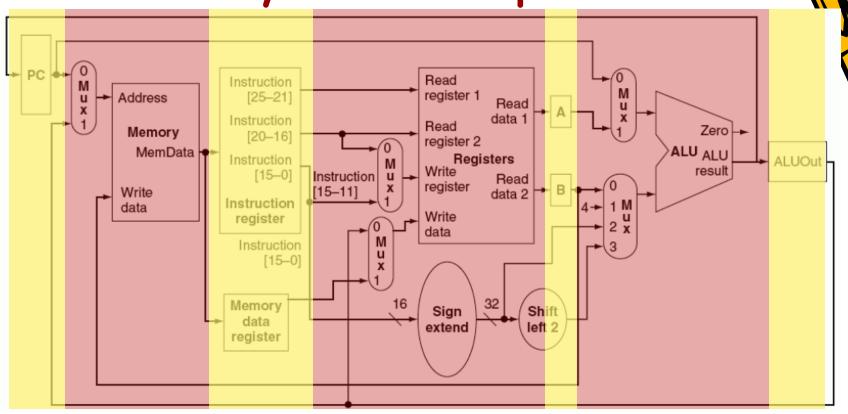- Note: registers hold data only between a pair of adjacent clock cycles
- Question: Do we need to have write or read control signals for registers, memory, & GPR?




- No WR/RD control signal for non-visible regs (MDR,A,B, ...
 - WR=1, RD=1
- But IR needs to hold instr. until end of exec. of that instr.
 - How about PC, memory, and GPR?
 - How about read signal?

Read & Write Control Signals

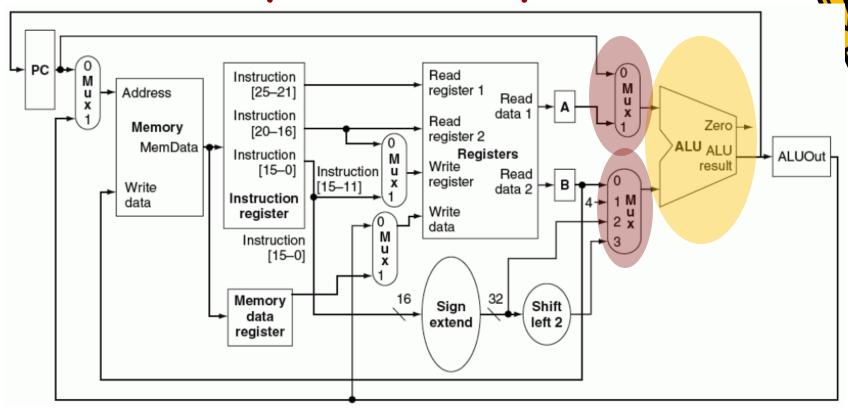- · Memory
 - Write signal required
 - Read signal required
 - · If simultaneous read and write not possible
 - Twice decode circuitry for simultaneous RD/WR
- PC
 - If write signal = 1 →
 - PC incremented by 4 in IF & ID cycles
 - · PC may capture wrong address in other cycles






- Three ALUs replaced by a single ALU
- ALU must accommodate all inputs
 - Which go to three ALUs in single-cycle datapath
 - A op B / PC+4 / PC+addr. / A+immediate



Cycle 1: Instruction Fetch

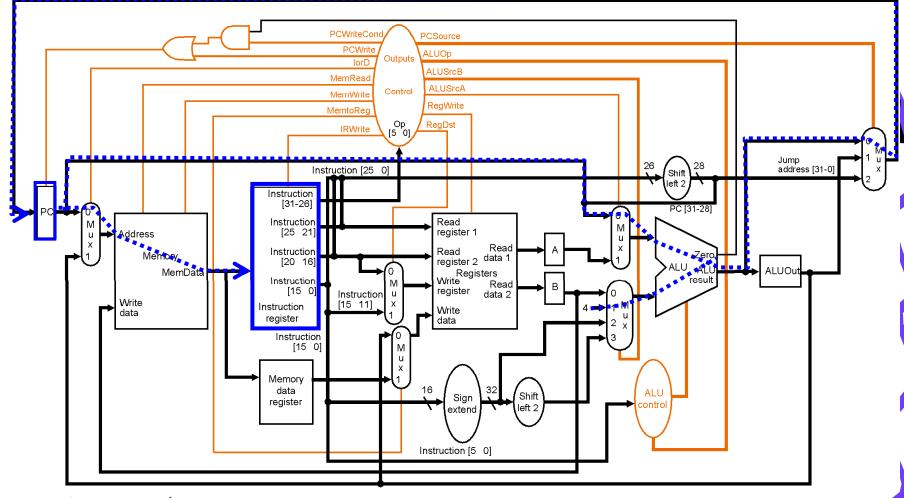


Datapath:

IR <= Mem[PC] PC <= PC + 4

Lecture 7

Cycle 1: Instruction Fetch

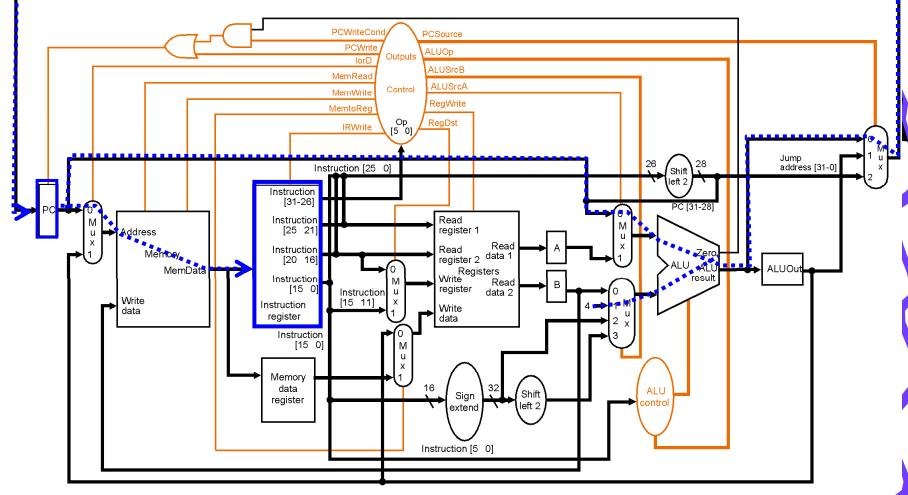

Control:



IorD=0, MemRead=1, MemWrite=0, IRwrite=1, ALUsrcA=0 ALUsrcB=01, PCWrite=1, ALUop=00, PCsource=00


Lecture 7

Control for IF Cycle

```
MemRead
ALUsrcA = 0
IorD = 0
IRwrite
ALUsrcB = 01
ALUop = 00
Pcwrite
PCsource = 00
```



Cycle 2: ID & RF Cycle

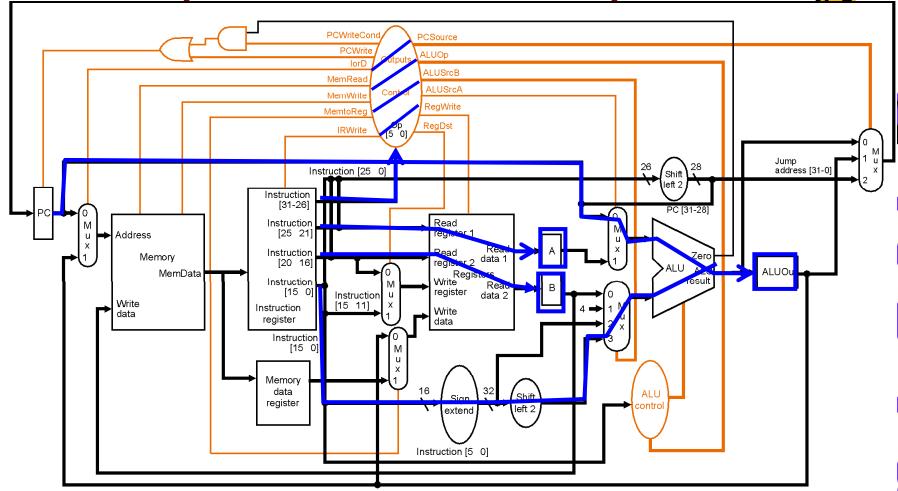



B <= GPR[IR[20-16]]

ALUout <= PC + (sign-extend (IR[15-0]) << 2)
Sharif University of Technology, Spring 2019



Lecture 7

Cycle 2: ID & RF Cycle

```
A <= GPR[IR[25-21]]
B <= GPR[IR[20-16]]
ALUout <= PC + (SignEx(IR[15-0]) << 2)
```

- Question 1:
 - We fetch A & B from GPR even though we don't know if they will be used.
 - Why?



Cycle 2: ID & RF Cycle

A <= GPR[IR[25-21]]
B <= GPR[IR[20-16]]
ALUout <= PC + (SignEx(IR[15-0]) << 2)

Question 2:

- We compute target address even though we don't know if it will be used.
 - Operation may not be branch
 - · Even if it is, branch may not be taken
- Why?



Cycle 2: ID & RF Cycle

A <= GPR[IR[25-21]]
B <= GPR[IR[20-16]]
ALUout <= PC + (SignEx(IR[15-0]) << 2)

Question 3:

- Control signals computed in Cycle 2. However, IorD signal used in Cycle 1. How this is possible?



Cycle 2: ID & RF Cycle


A <= GPR[IR[25-21]]
B <= GPR[IR[20-16]]
ALUout <= PC + (SignEx(IR[15-0]) << 2)

· Answer:

- Everything up to this point must be instruction-independent
 - · Because we haven't decoded instruction
- GPR and ALU are available in cycle 2 so we can use them up to fetch A & B and to calculate target branch address



Control for First Two Cycles

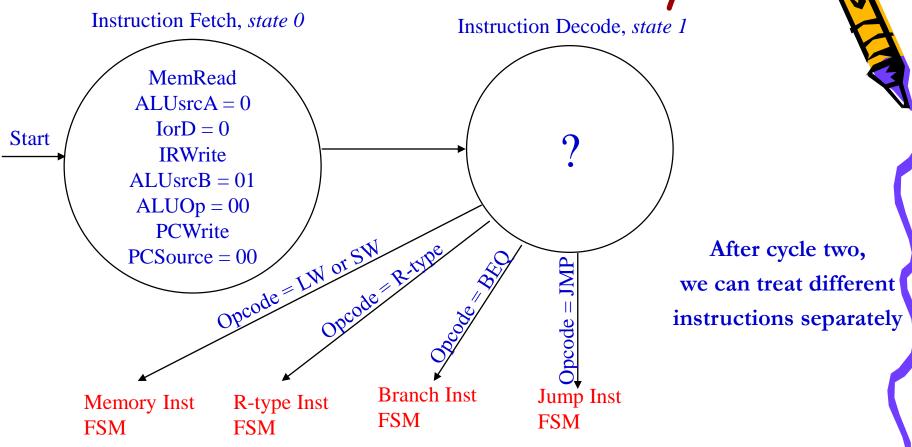


- Specification of Control
 - Using a <u>Finite State Machine (FSM)</u>



Cycle 2: ID & RF Cycle



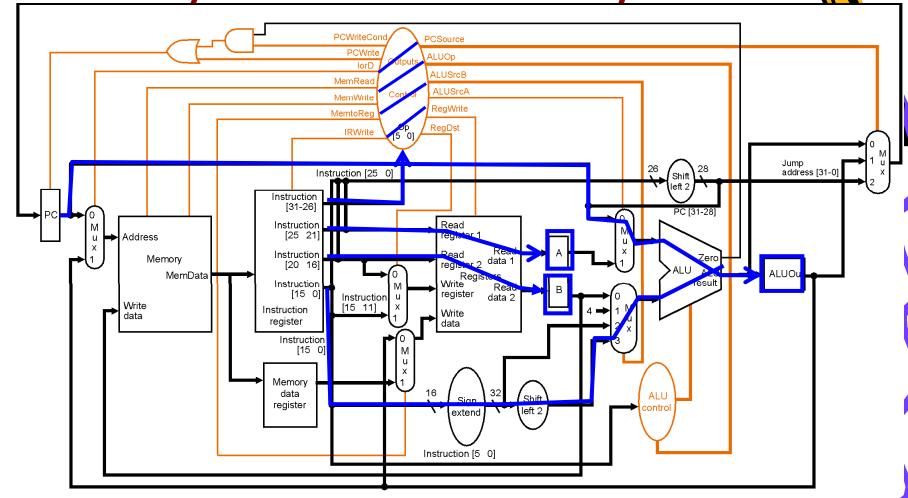

Control:


ALUSrcA=0, ALUSrcB=11, ALUOp=00

How about other signals? RegWrite, MemWrite, RegDest?

Lecture 7


Sharif University of Technology, Spring 2019

Cycle 3 for beg: Execute

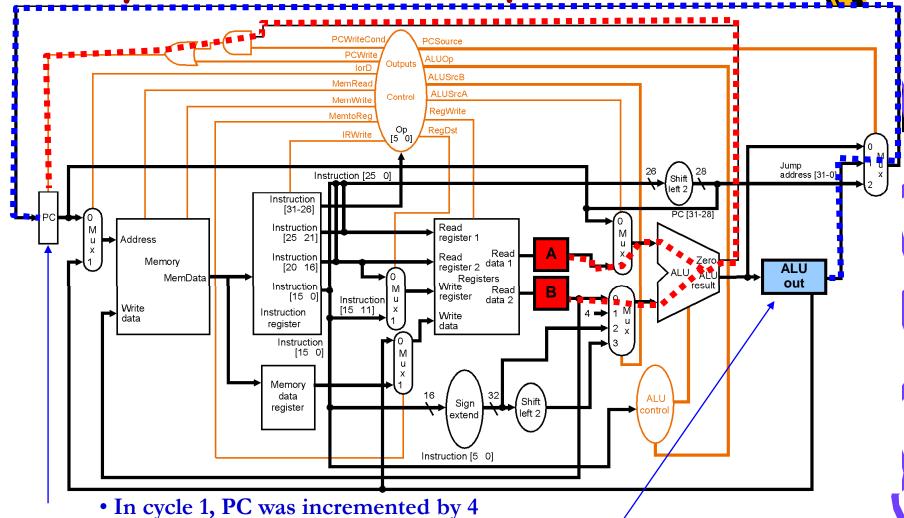

- In cycle 2, ALUout was set to branch target
- •This cycle, we conditionally update PC: if (A==B) PC=ALUout Lecture 7 Sharif University of Technology, Spring 2019

FSM State for Cycle 3 of beq

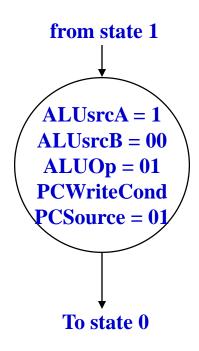



R-type Instructions

Cycle 3 (EXecute)


Cycle 4 (WriteBack)

$$GPR[IR[15-11]] = ALUout$$

R-type instruction is finished



R-Type Execution

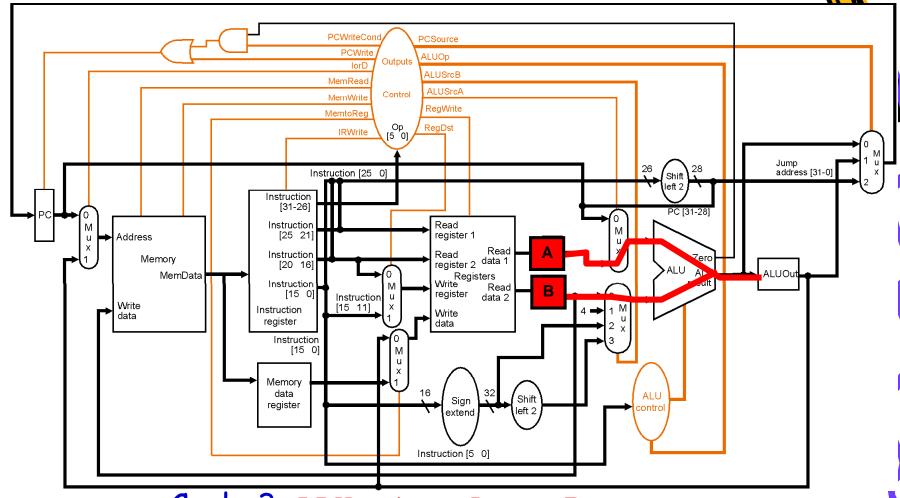


Cycle 3: ALUout = A op B

Cycle 4: GPR[IR[15-11]] = ALUout



R-Type Execution & WB

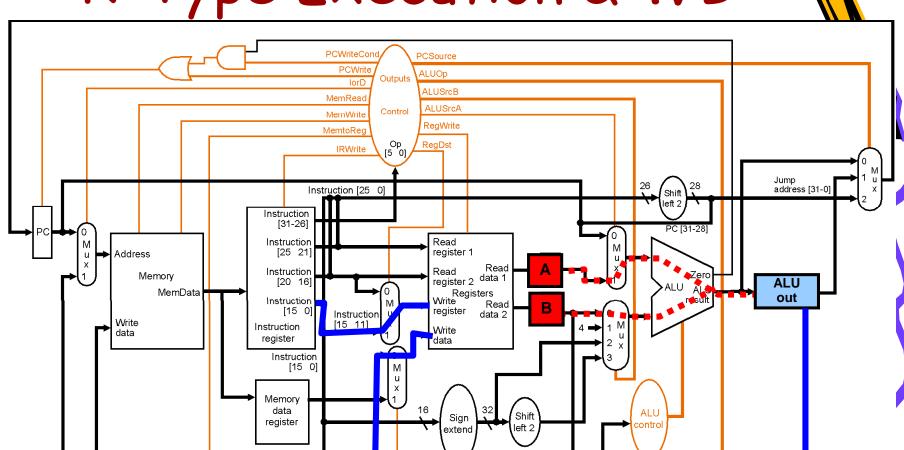


Cycle 3: ALUout = A op B

Cycle 4: GPR[IR[15-11]] = ALUout

Instruction [5 0]



FSM States for R-type Instructions

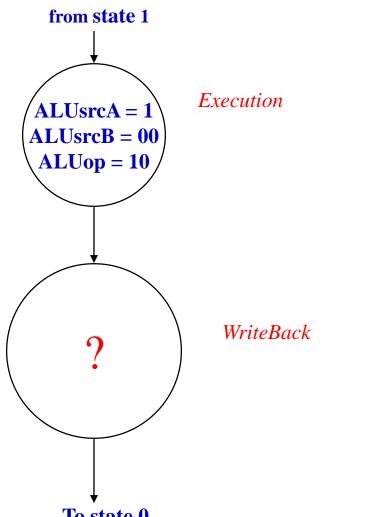



Load and Store

- EXecute (cycle 3):
 - Compute memory address

```
ALUout = A + sign-extend(IR[15-0])
```

- Mem (cycle 4):
 - Access memory (read or write)


```
Store: Mem[ALUout] = B (store finished)
```

- Load: MDR = Mem[ALUout]
- WB (cycle 5):
 - Write register (only for load))



GPR[IR[20-16]] = MDR


Cycle 3 for lw/sw: Address Computation'

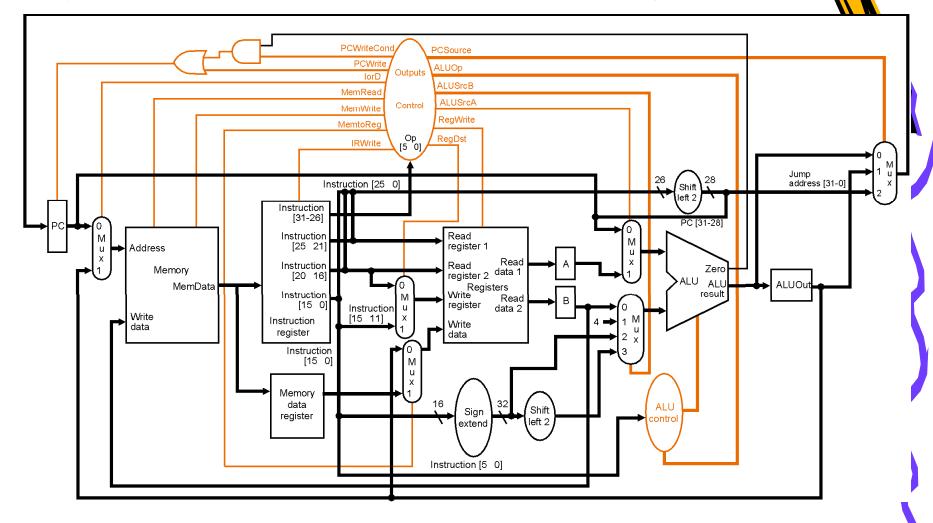




ALUout = A + sign-extend(IR[15-0])

Cycle 4 for Store: Memory Access

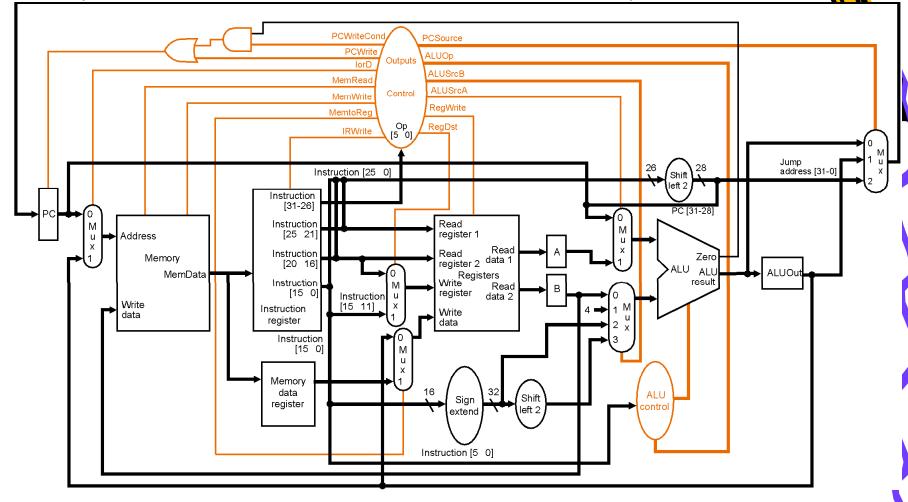




Cycle 4 for Load: Memory Access

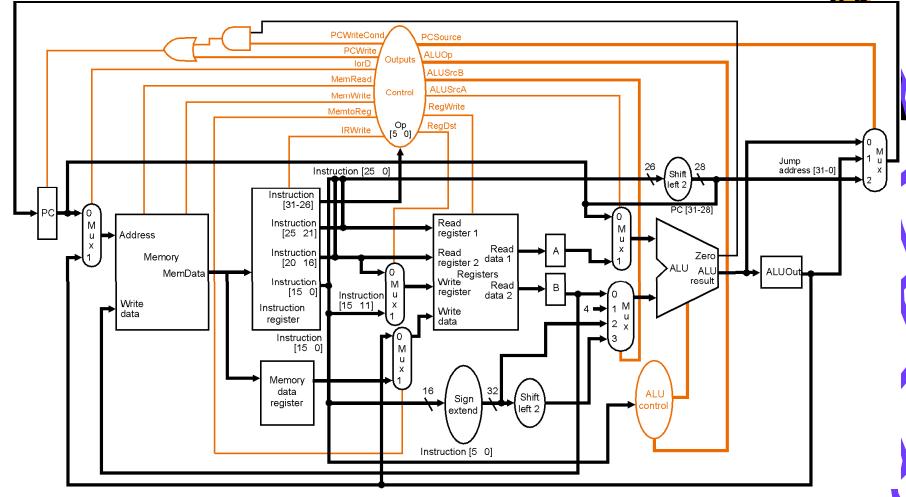



MDR = Memory[ALUout]


Cycle 5 for load: WriteBack

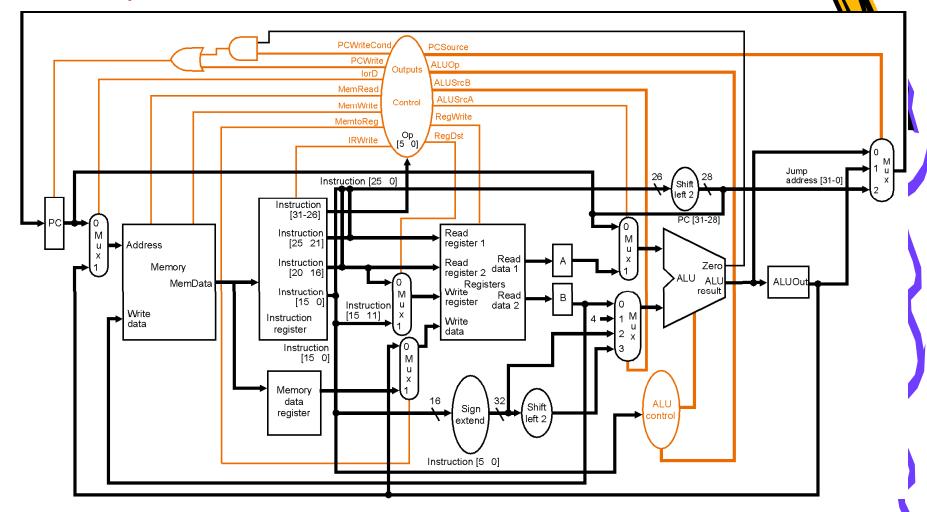




GPR[IR[20-16]] = MDR

Memory Instruction States from state 1

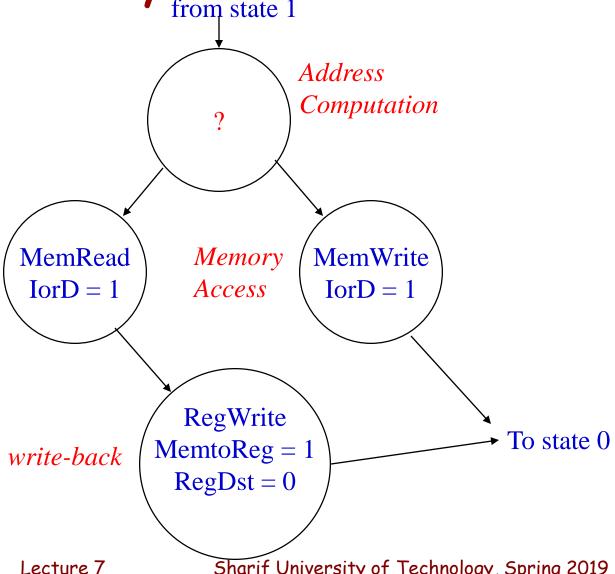




Cycle 3 for Jump

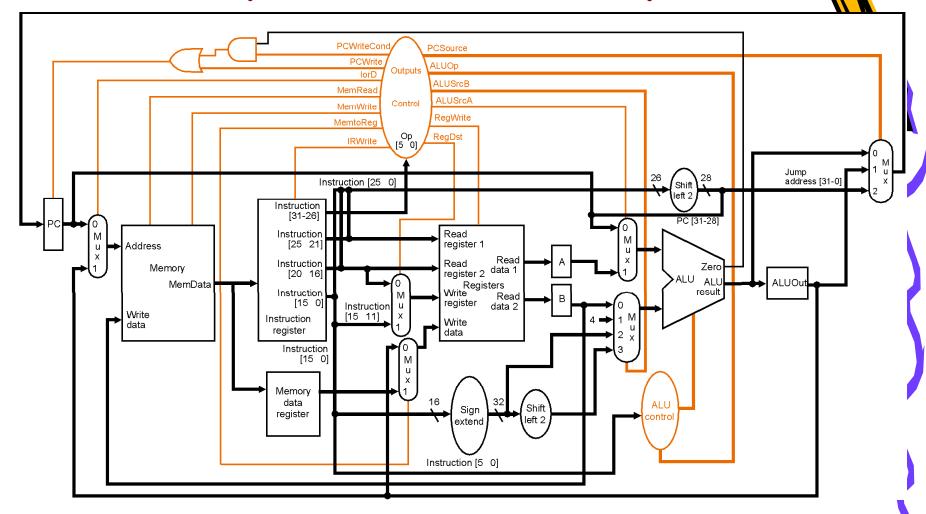




PC = PC[31-28] | (IR[25-0] << 2)

Cycle 3 Jump FSM state

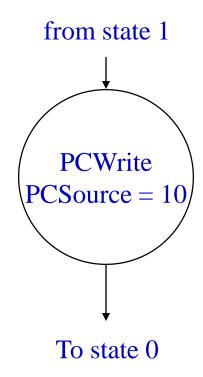




Complete FSM

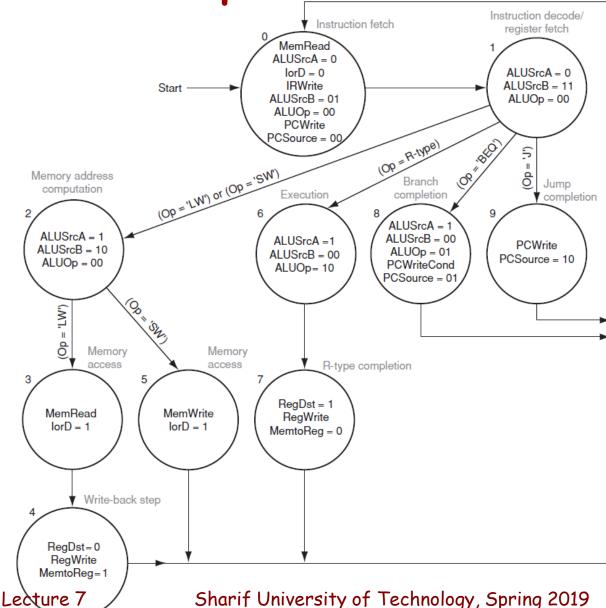



Single-Cycle Control Unit Implementation

- Unstructured LogicDesign
 - By Karnaugh Map
- · PLA/PAL

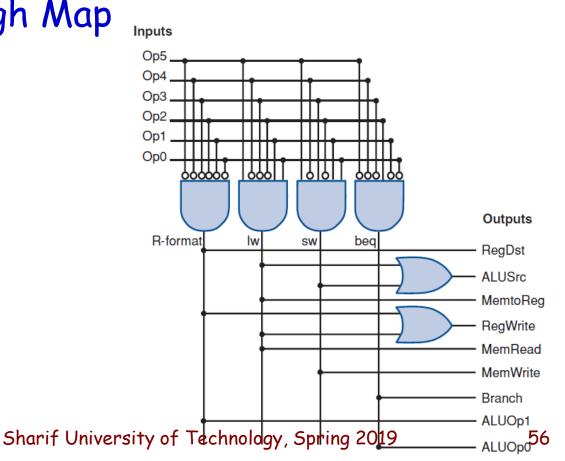





Lecture 7

PAL/PLA

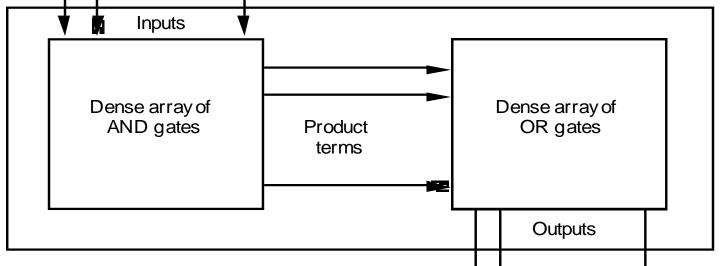- What is PAL/PLA?
 - Pre-fabricated building block of many AND/OR gates (or NOR/NAND)
 - Personalized by making or breaking connections among gates





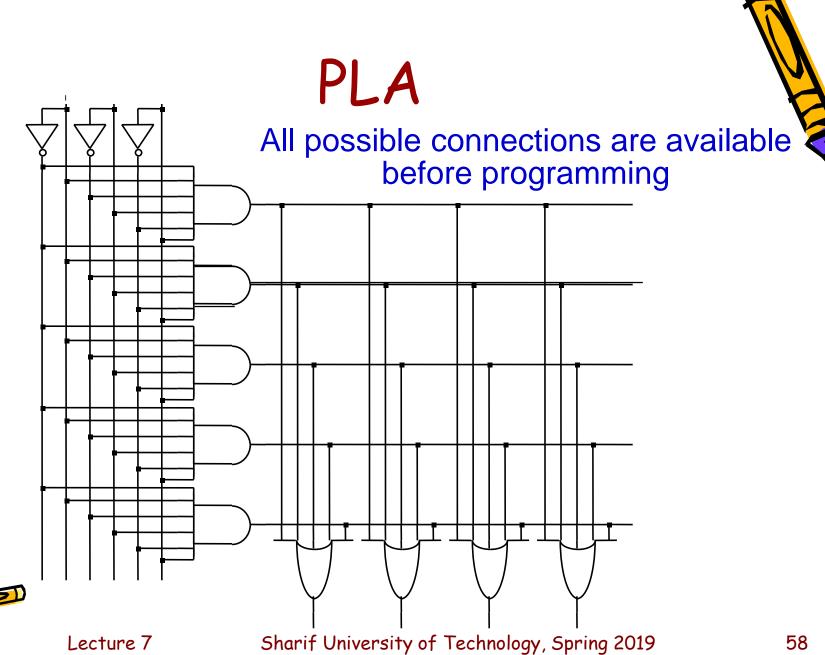

PLA Example

F1 = ABC


F2 = A + B + C

 $F3 = \overline{ABC}$

 $F4 = \overline{A + B + C}$


F5 = A xor B xor C

F6 = A xnor B xnor C

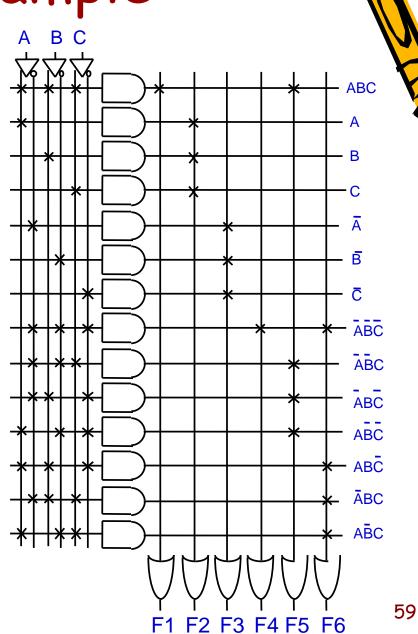



Multi-Cycle Control Unit Implementation

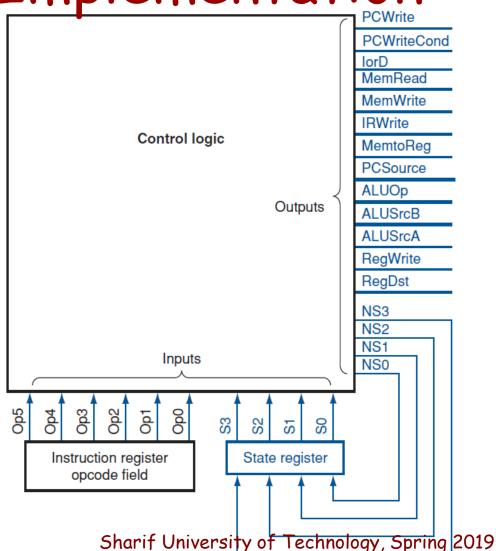



Lecture 7

Multi-Cycle Control Unit Implementation (cont.)

- State Register (53~50)
- · Control Logic
 - Combinational logic
 - Inputs?
 - Outputs?




Multi-Cycle Control Unit Implementation (cont.)

Control Logic Inputs

- Opcode bits: Op5~Op0

- 53~50

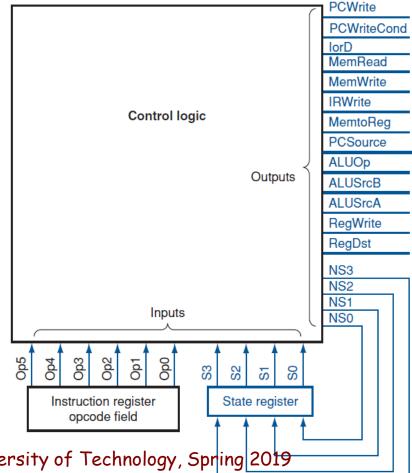




Sharif University of Technology, Spring 2019


Multi-Cycle Control Unit Implementation (cont.)

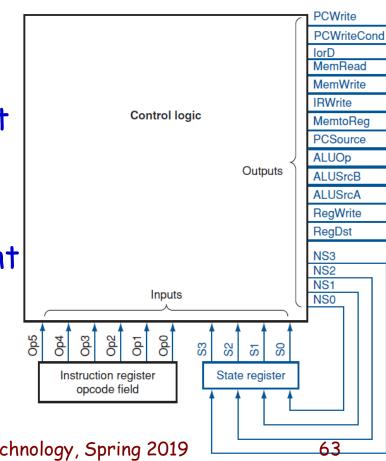- Control Logic Outputs
 - Control signals: PCWrite, IorD, ...
 - Depends only on current state
 - NS3~NS0
 - Depends on both current state & opcode bits





Multi-Cycle Control Unit Implementation in PLA

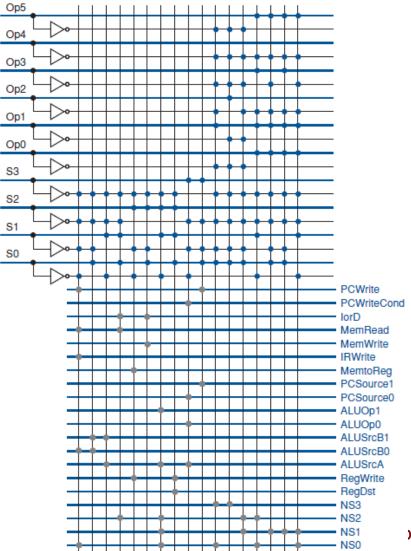



Lecture 7

oring 2019

Multi-Cycle Control Unit Implementation in ROM



- Can be used to implement control unit

- # of inputs: 10

- # of outputs: 20


- Use a ROM with:

Address width: 10

· Data width: 20

• ROM size: 20*210 = 20Kb

1024 entries

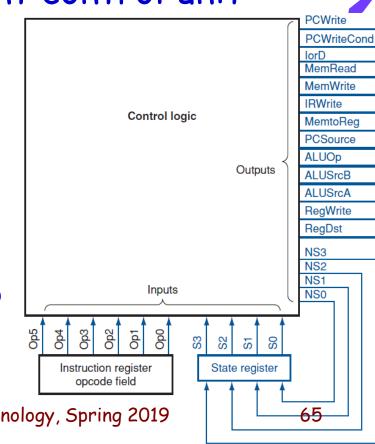



Multi-Cycle Control Unit Implementation in ROM (cont.)

· Question:

- Can we use smaller ROM(s) to implement control

unit?

Answer: 2 Separate ROMs

- First ROM: 16*24 = 256b

of inputs: 4


of outputs: 16

- Second ROM: 4*210 = 4Kb

• # of inputs: 10

of outputs: 4

- Total ROM size: 4.3Kb

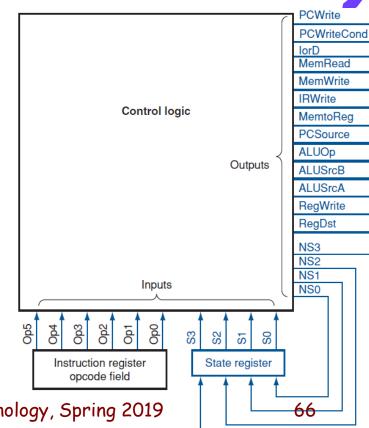




Implementing Multi-Cycle Control Using Micro-Program

- · Cons of ROM Implementation
 - 95% of ROM used to indicate next state
 - 4Kbits
 - What if we have more complex ISA?
 - · FP instructions which may take several cycles
- · Example:
 - Consider an FSM which requires 10 FFs
 - What would be size of ROM?




Implementing Multi-Cycle Control Using Micro-Program (cont.)

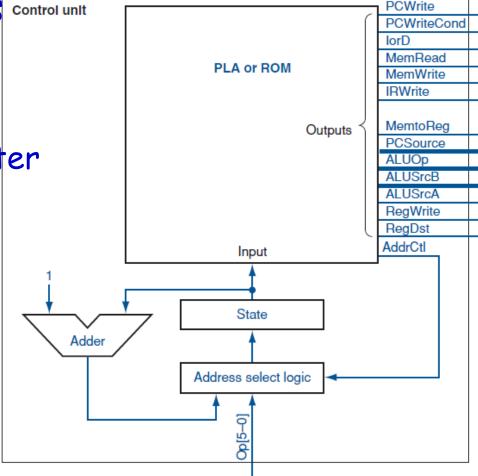- ROM Control Words Control unit
 - Micro-instructions
- State Register
 - Micro-program counter
 - Also called:
 - Microcode sequencer





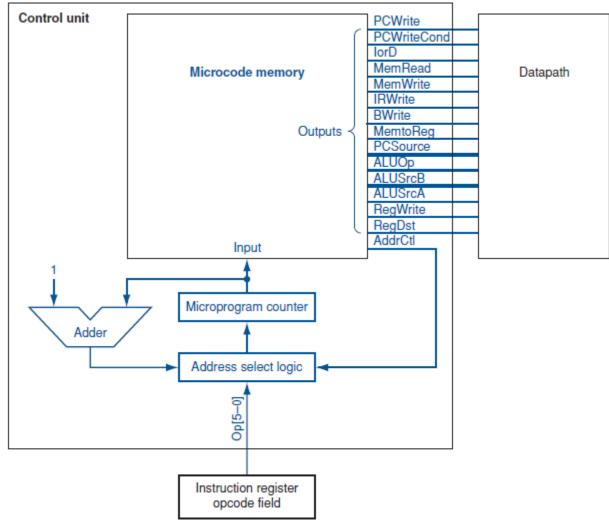Implementing Multi-Cycle Control Using Micro-Program (cont.)






Microprogramming (cont.)

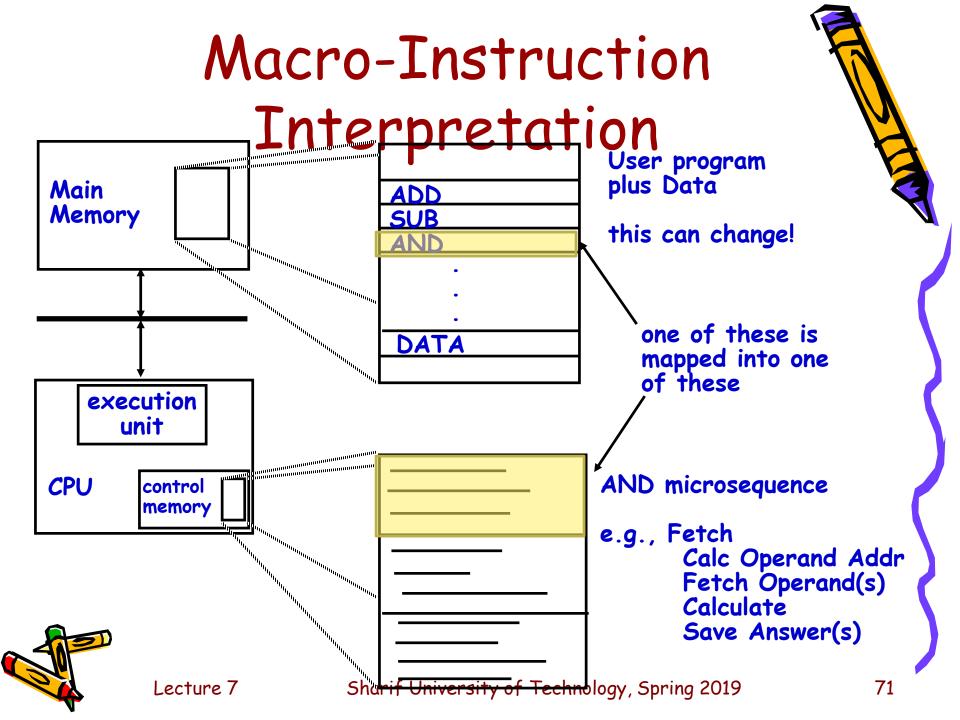- A Convenient Method to Implement structured control state diagrams
 - Random logic replaced by $\mu\text{-PC}$ sequencer and ROM
 - Each line of ROM called a μ -instruction
 - Limited state transitions:
 - Branch to zero, next sequential, branch to μ instruction address from displatch ROM





Microprogramming (cont.)

- 80x86 Instructions
 - -Instructions translate to 1 to 4 microoperations
- Complex 80x86 Instructions
 - -Executed by a conventional microprogram $(8K \times 72 \text{ bits})$ that issues long sequences of micro-operations



Hardwired vs. Micro-Programmed

- Micro-Programmed
 - Can change micro-operations without changing circuit (just by reprogramming ROM)
 - Easier design approach
 - More disciplined control logic
 - · Easier to debug
 - Enables more complex ISA
 - Enables family of machines with same ISA
- Hard-Wired
 - Area efficient
 - Probably less delay
 Lecture 7 Sharif University



Backup

