




Computer Architecture

Hossein Asadi
Department of Computer Engineering
Sharif University of Technology
asadi@sharif.edu

Today's Topics

- Data Path Design

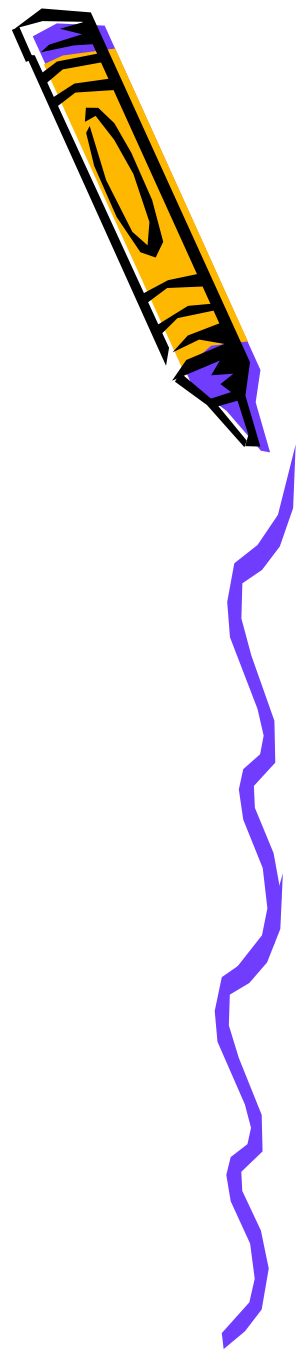

Copyright Notice



- Parts (text & figures) of this lecture adopted from:
 - Computer Organization & Design, The Hardware/Software Interface, 3rd Edition, by D. Patterson and J. Hennessey, MK publishing, 2005.
 - "Intro to Computer Architecture" handouts, by Prof. Hoe, CMU, Spring 2009.
 - "Computer Architecture & Engineering" handouts, by Prof. Kubiawicz, UC Berkeley, Spring 2004.
 - "Intro to Computer Architecture" handouts, by Prof. Hoe, UWisc, Fall 2009.
 - "Computer Arch I" handouts, by Prof. Garzarán, UIUC, Spring 2009.




Datapath






- Datapath?
 - A functional unit used to **operate** on or **hold** data within a processors
- Datapath Elements in MIPS
 - Instruction memory
 - Data memory
 - Register file
 - ALU
 - Adders
- Control Unit
 - Schedule data movements in datapath



Datapath (cont.)

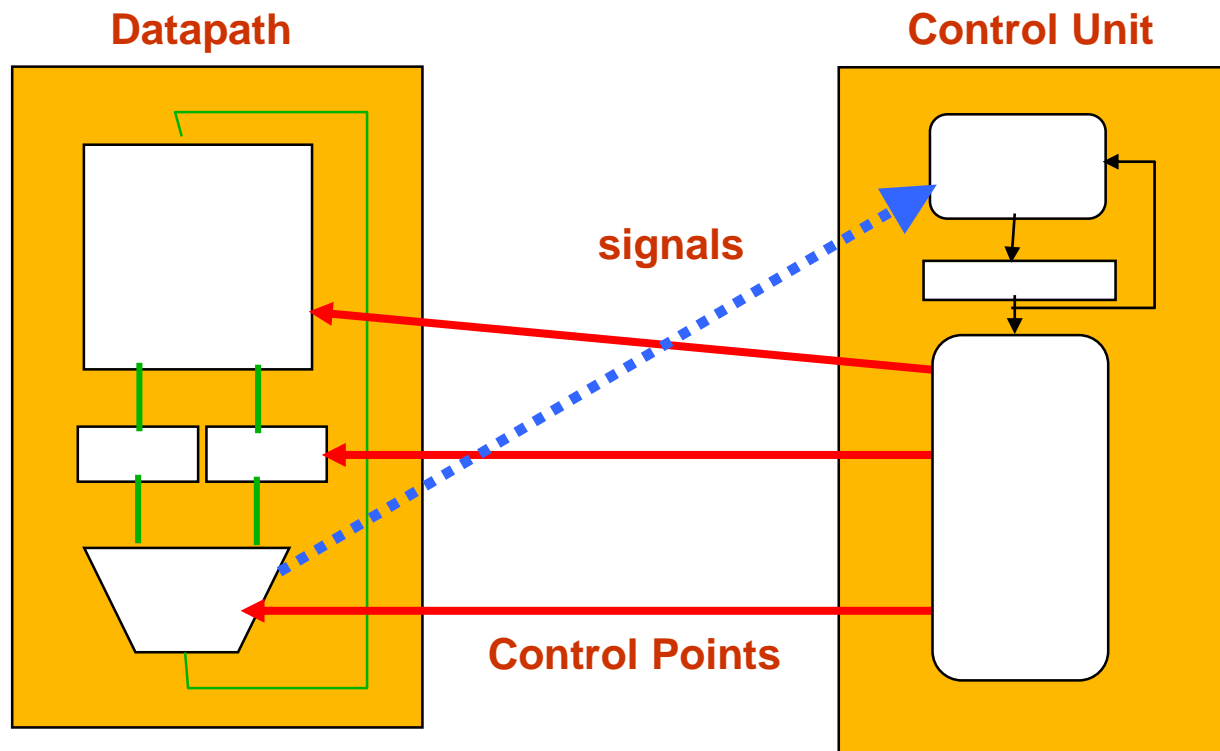


Abstract View of MIPS Implementation

 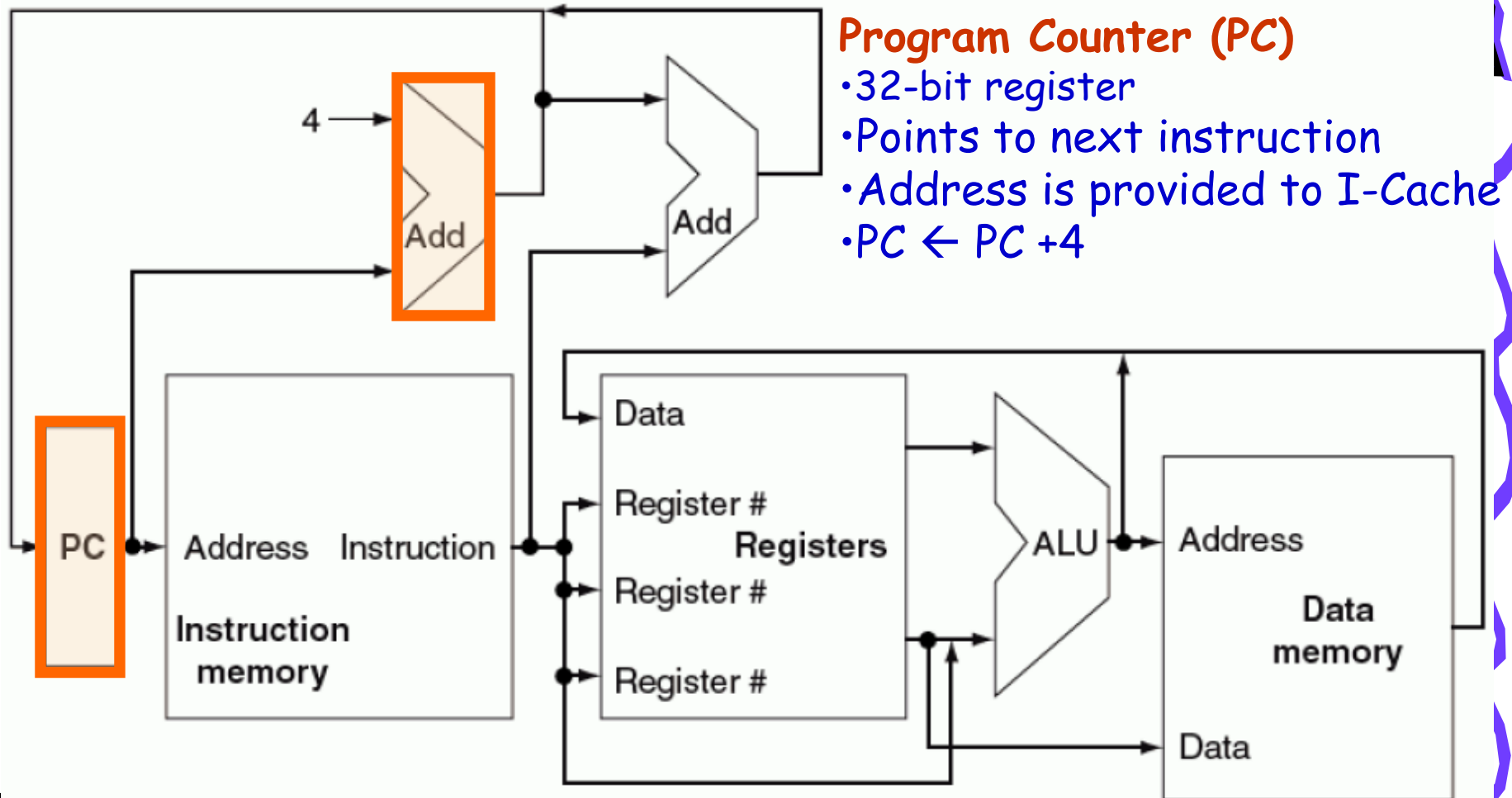 

Instruction Fetch

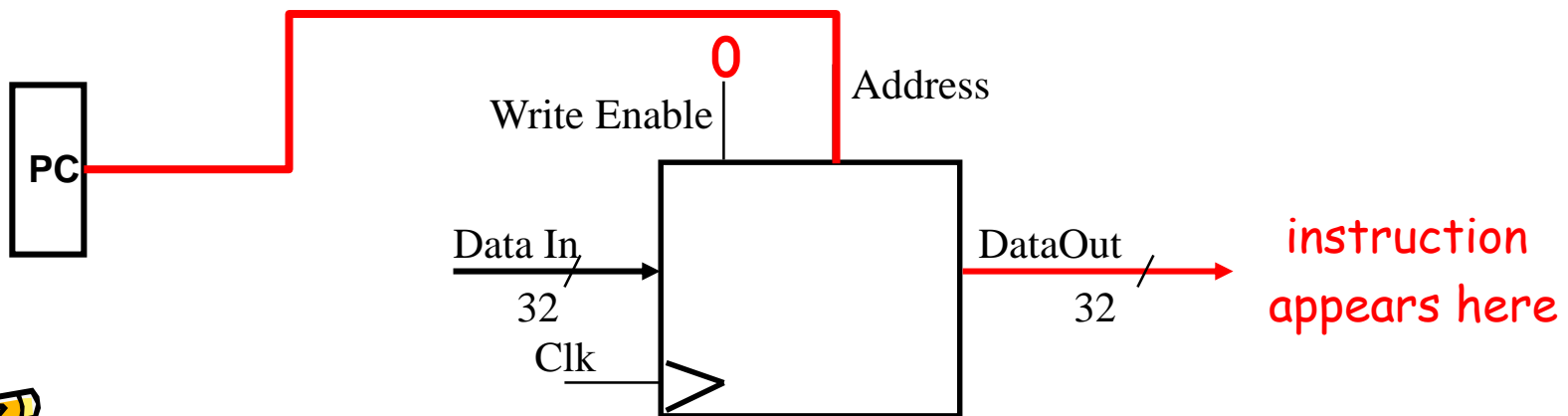- Program Counter (PC)
 - Supplies instruction address
 - Get instructions from memory




Instruction Memory (I-Cache)

چون داخل طراحی single cycle چیزی به عنوان IR نداریم

The output of the IR is available to control circuits

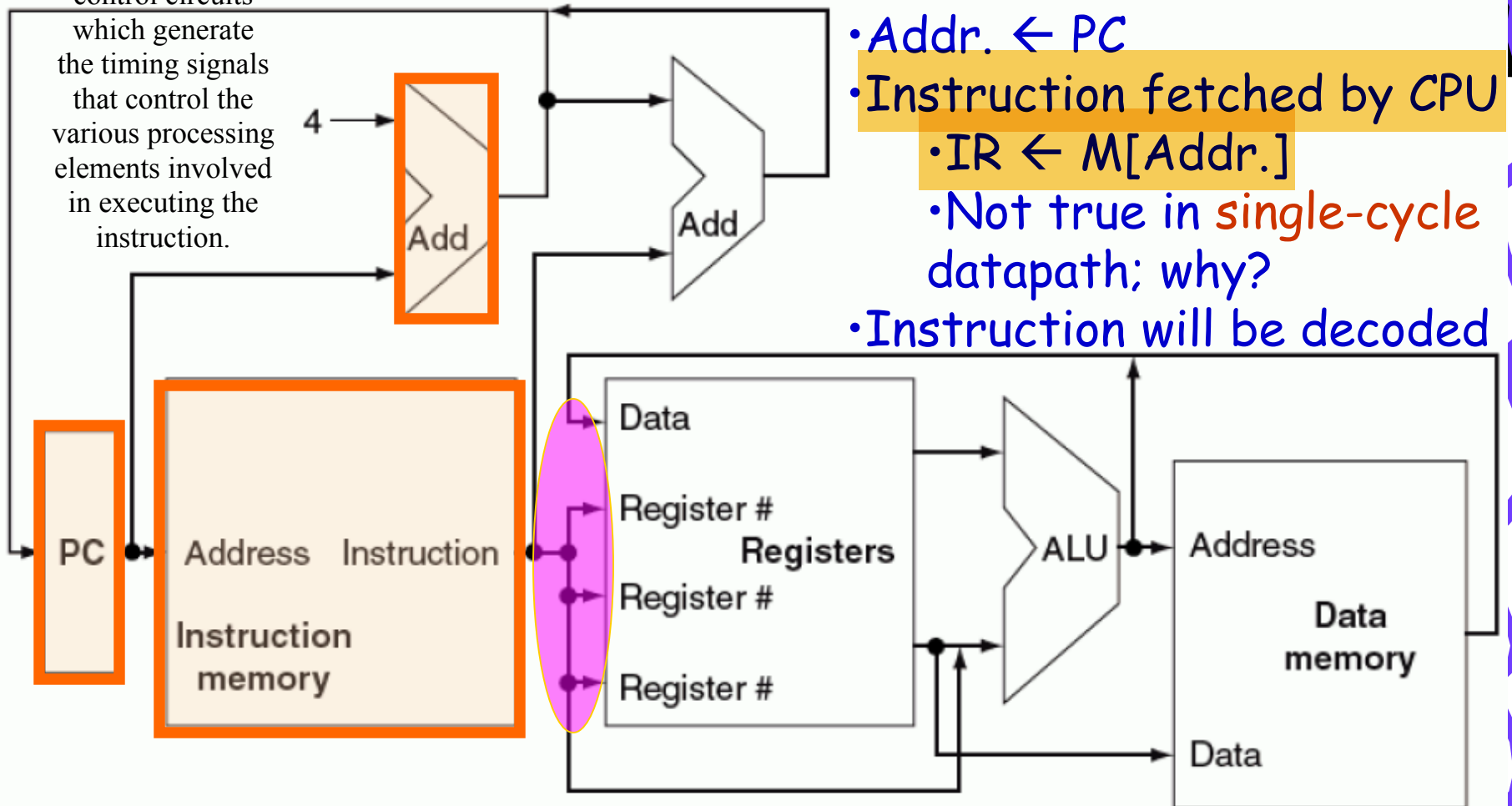
which generate the timing signals that control the various processing elements involved in executing the instruction.



Instruction Fetch Unit



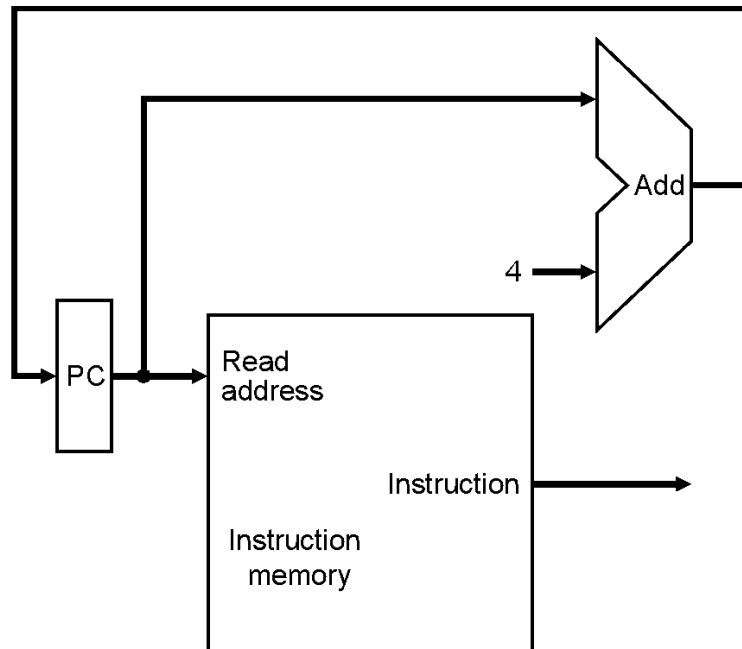- Updating PC for Next Instruction
 - Sequential Code: $PC \leftarrow PC + 4$
 - Branch and Jump: $PC \leftarrow \text{New Address}$
 - we'll worry about this later



Instruction Encoding



- MIPS Instruction Format

	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
r format	OP	rs	rt	rd	sa	funct
i format	OP	rs	rt	immediate		
j format	OP	target				

- OP: opcode
- rs: first register source operand
- rt: second register source operand
- rd: register destination operand
- sa: shift amount
- funct: function code




Instruction Encoding (cont.)




- R-TYPE

- *add rd, rs, rt*
- *sub, and, or, slt*

 


- LOAD / STORE

- *lw rt, rs, imm*
- *sw rt, rs, imm*

 


- BRANCH

- *beq rs, rt, imm*

 

R-Type Encoding

 


add \$4, \$3, \$2

rd

rt


rs

 

0 0 0 0 0 0 0 0 0 1 1 0 0 0 1 0 0 0 1 0 0 0 0 0 0 0 0 1 0 0 0 0 0

Encoding = 0x00622020


Register File

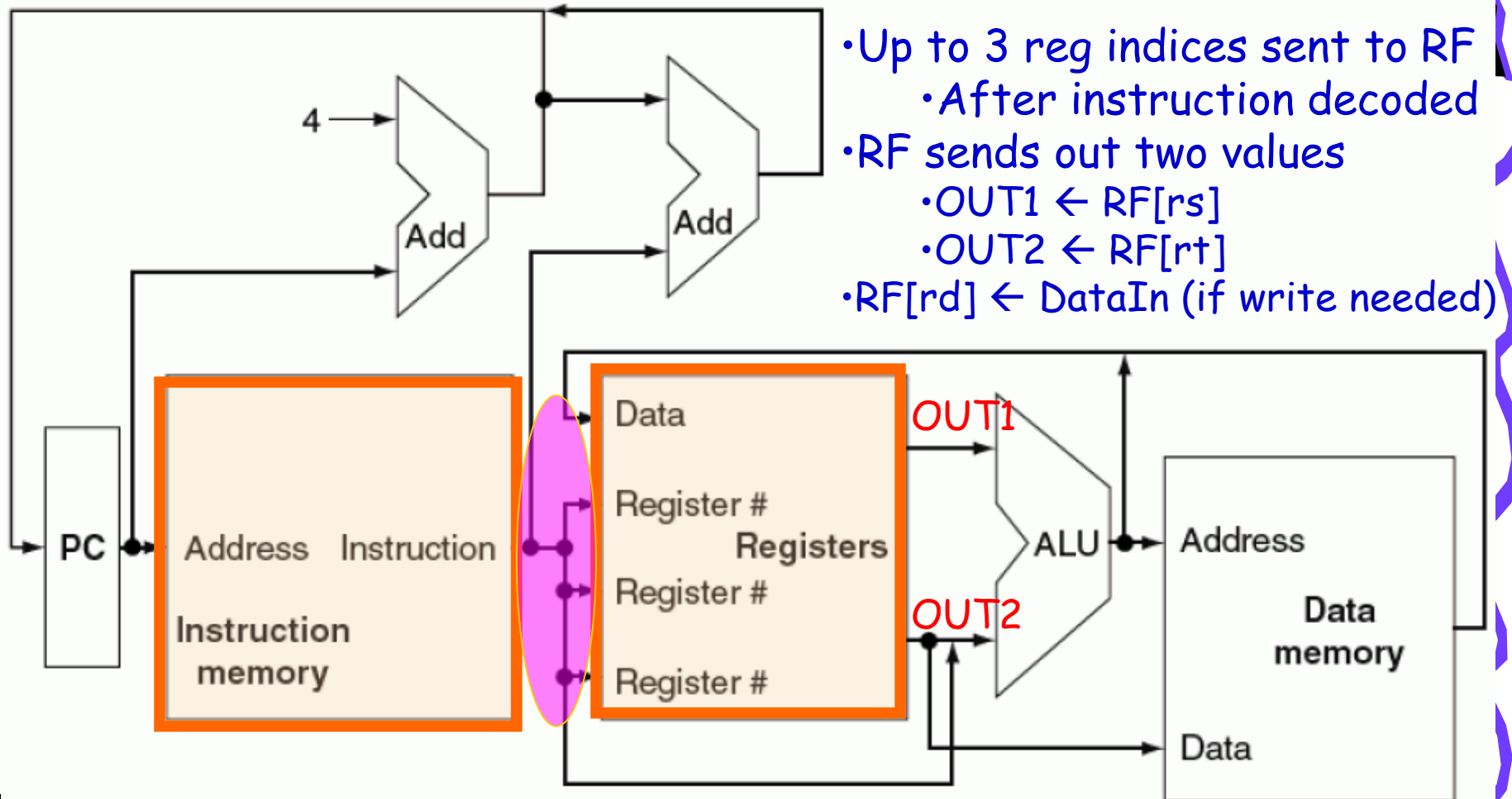

Datapath Elements



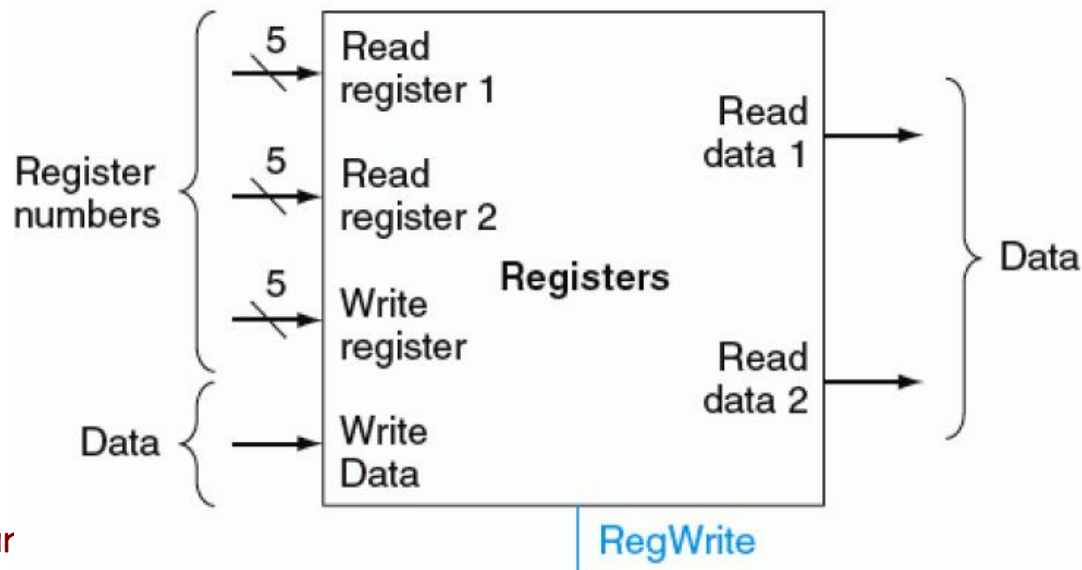
- Register File (RF)
 - Also called, General Purpose Registers (GPR)
 - Up to three indices as inputs
 - 32-bit write input data
 - Two 32-bit outputs



Datapath Elements (cont.)



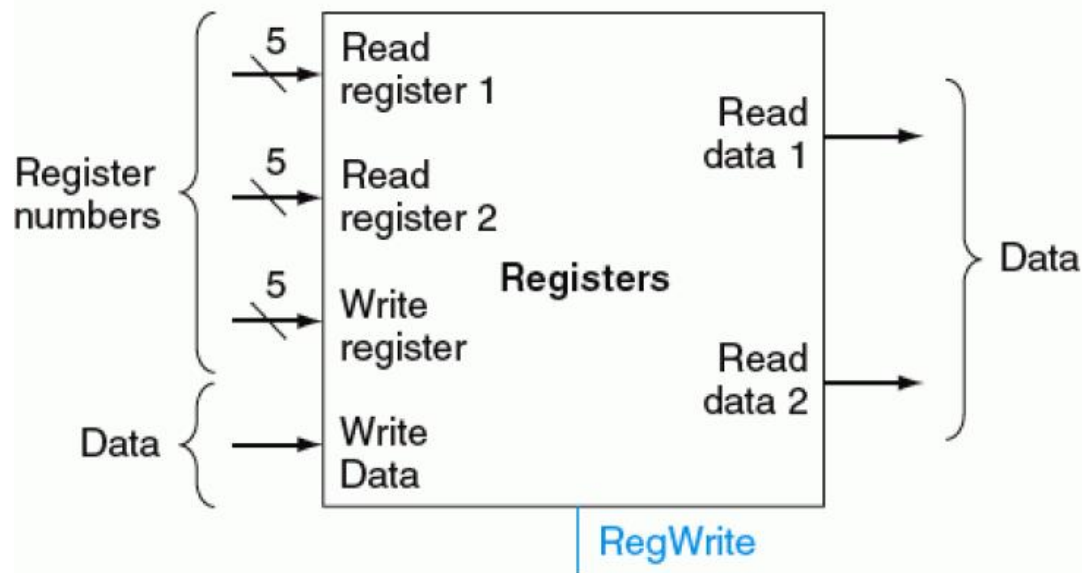- Question 1:
 - How read & write can be accomplished in one clock cycle without data contention?




Datapath Elements (cont.)



 
- Question 2:
 - How two simultaneous read operations possible?

به ازای هر ورودی Read Register یک mux قرار دارد که سیگنال select آن برای خواندن از هر رجیستر از ورودی های Read Register می آید



Most temporaries (except IR) are updated every cycle, so no write control is required (always write)
این موضوع برای multi cycle data path درست است.

ALU

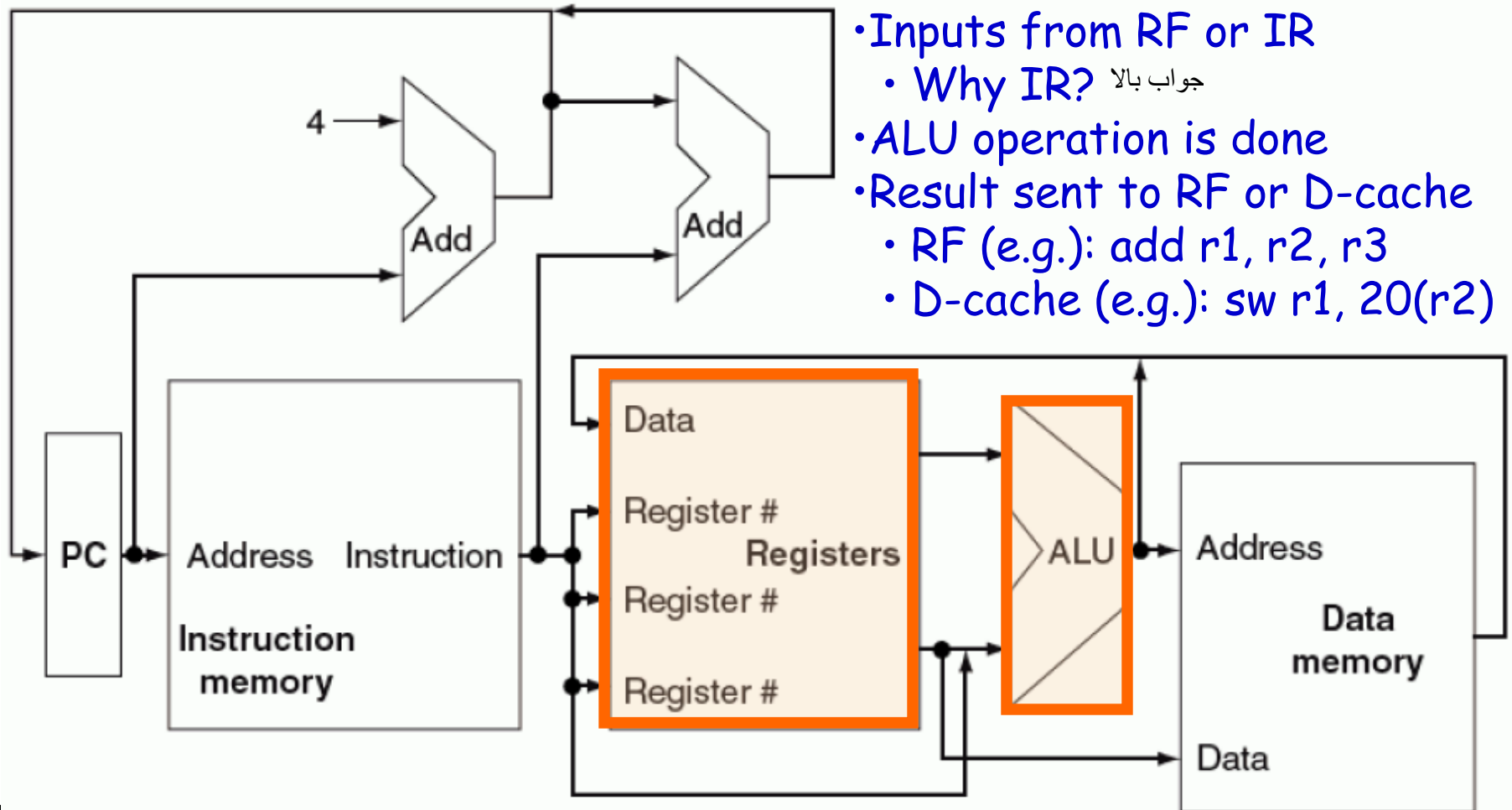


Reminder: Addressing Modes





Operand is constant

1. Immediate addressing


 


Operand is in register

2. Register addressing

 
 


3. Base addressing

  




lb \$t0, 48(\$s0)

4. PC-relative addressing

  

bne \$4, \$5, Label
(label will be assembled into
a distance)

5. Pseudodirect addressing

   

j Label



Datapath Elements (cont.)


از خروجی zero برای دستورات beq و bne استفاده می شود :

Zero = 0 \Rightarrow \$r1 \neq \$r2



Zero = 1 \Rightarrow \$r1 = \$r2

- ALU

 - Two 32-bit inputs
- One 32-bit output
- 4-bit operation selector
- Zero?



Data Memory (D-Cache)

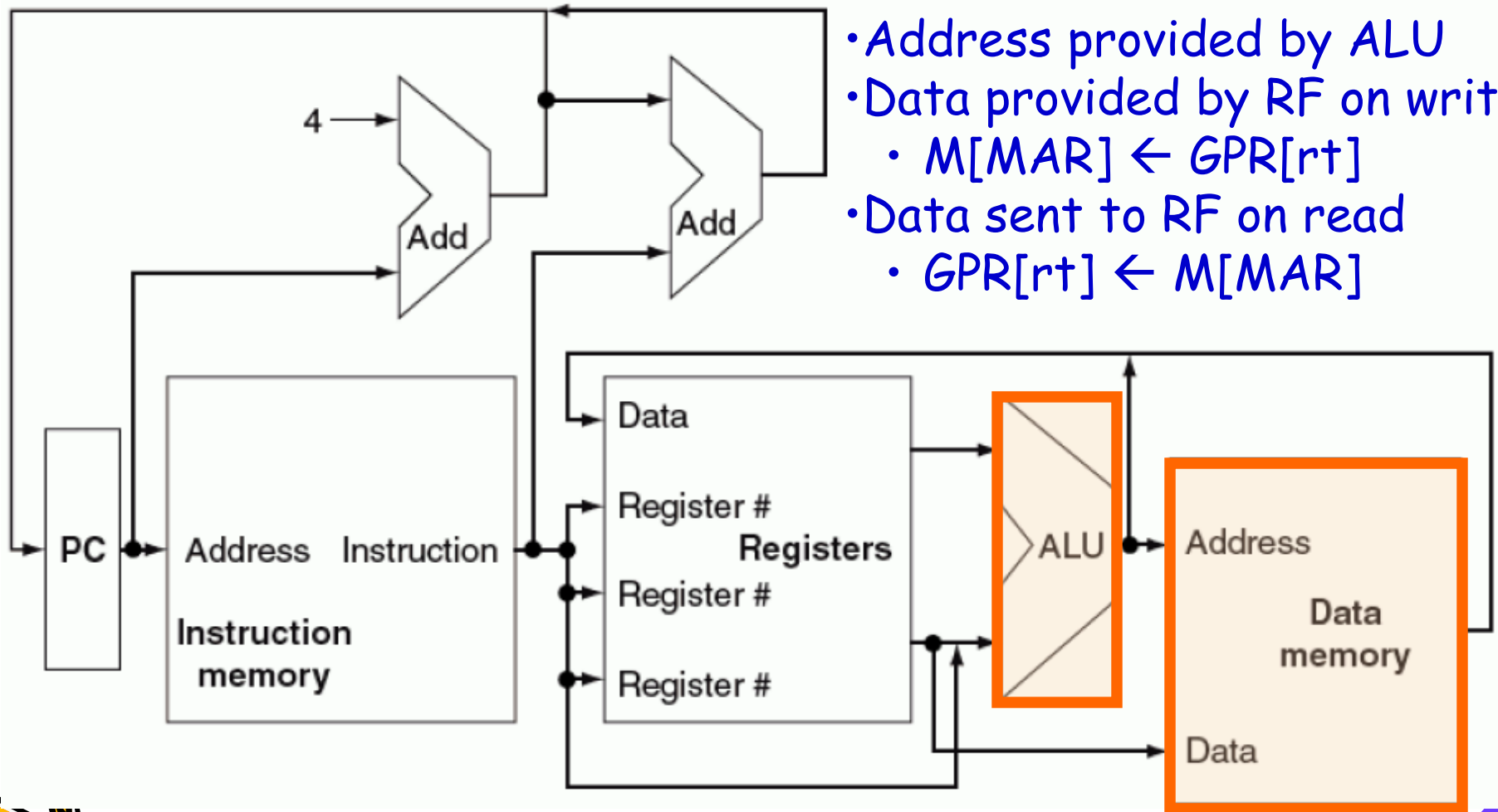 


- Address provided by ALU
- Data provided by RF on write
 - $M[MAR] \leftarrow GPR[rt]$
- Data sent to RF on read
 - $GPR[rt] \leftarrow M[MAR]$



Datapath Elements (cont.)



 - Data Memory Unit
 - Address
 - Loads/store: $MAR = GPR[rs] + imm16$
 - 32-bit write data
 - Write data $\leftarrow GPR[rt]$
 - 32-bit read data
 - $GPR[rt] \leftarrow$ Read data
 - MemRead signal
 - MemWrite signal





Discussion



- Compare **MemRead** and **MemWrite** Activation Process in Following Cases
 - Case A: separate I-cache & D-cache with separate data bus
 - Case B: separate I-cache & D-cache with common data bus
 - Case C: unified I-cache & D-cache




Abstract View of MIPS Implementation

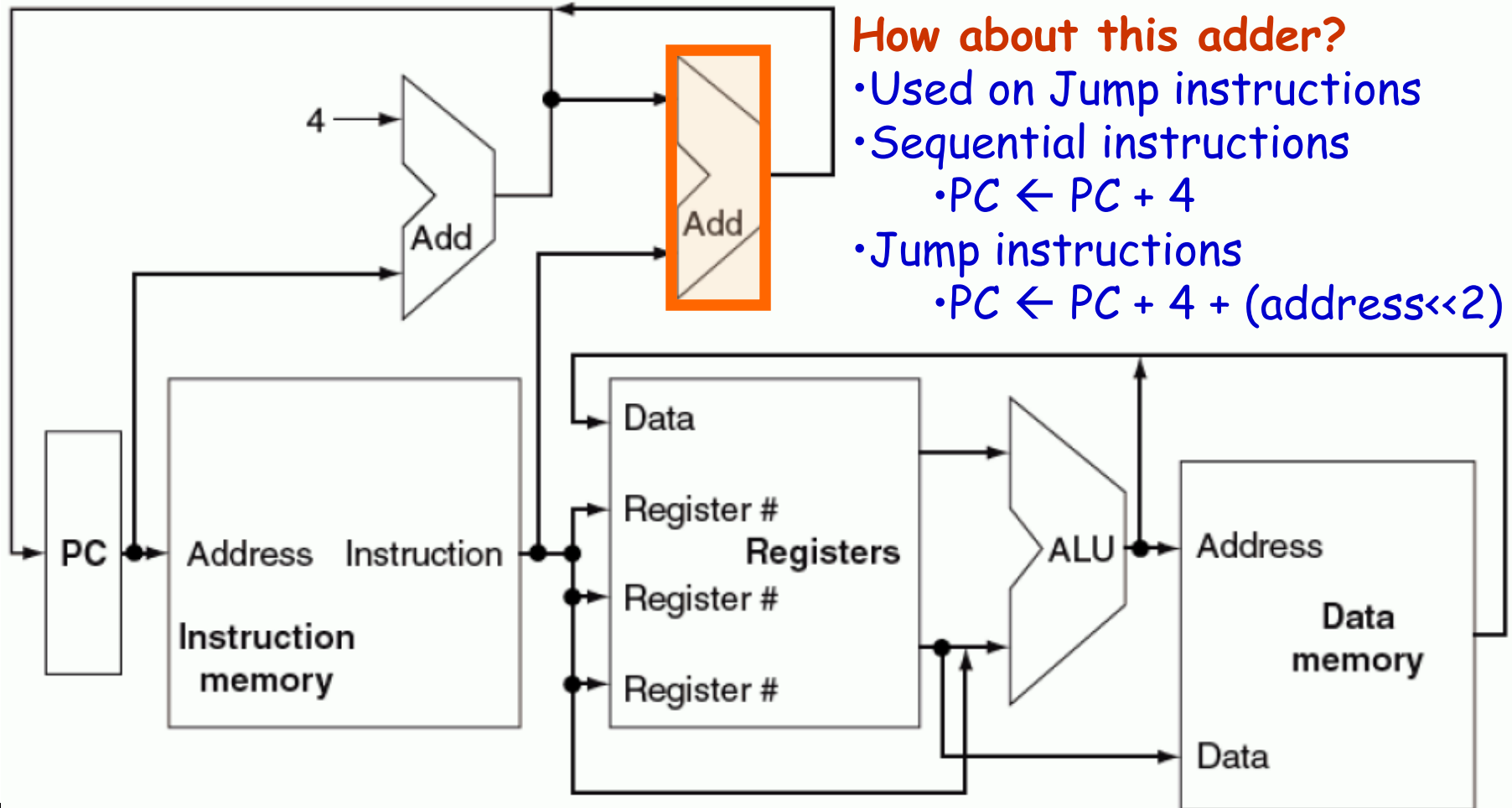 

Datapath Elements (cont.)




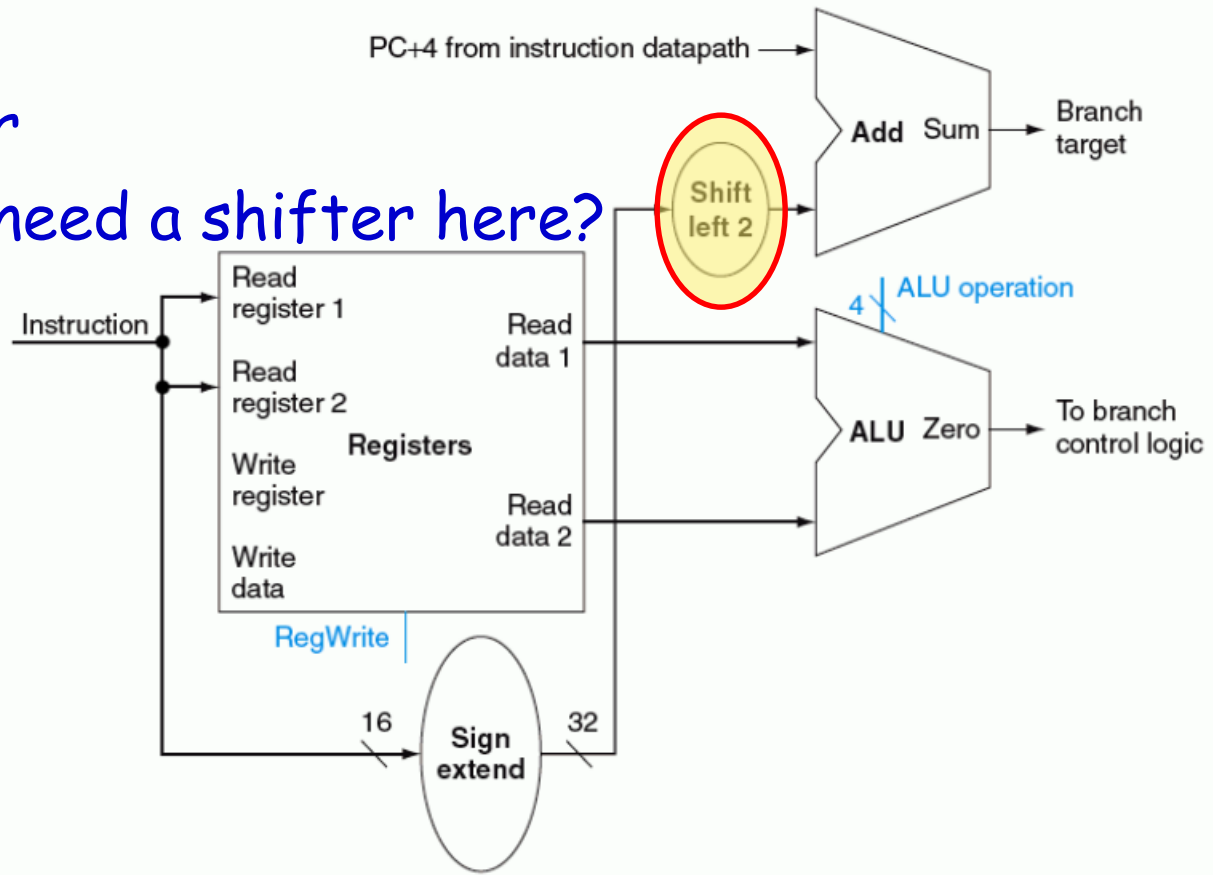- Branch Unit
 - Sign extend unit
 - Adder
 - Shifter
 - Do we need a shifter here?




Practice

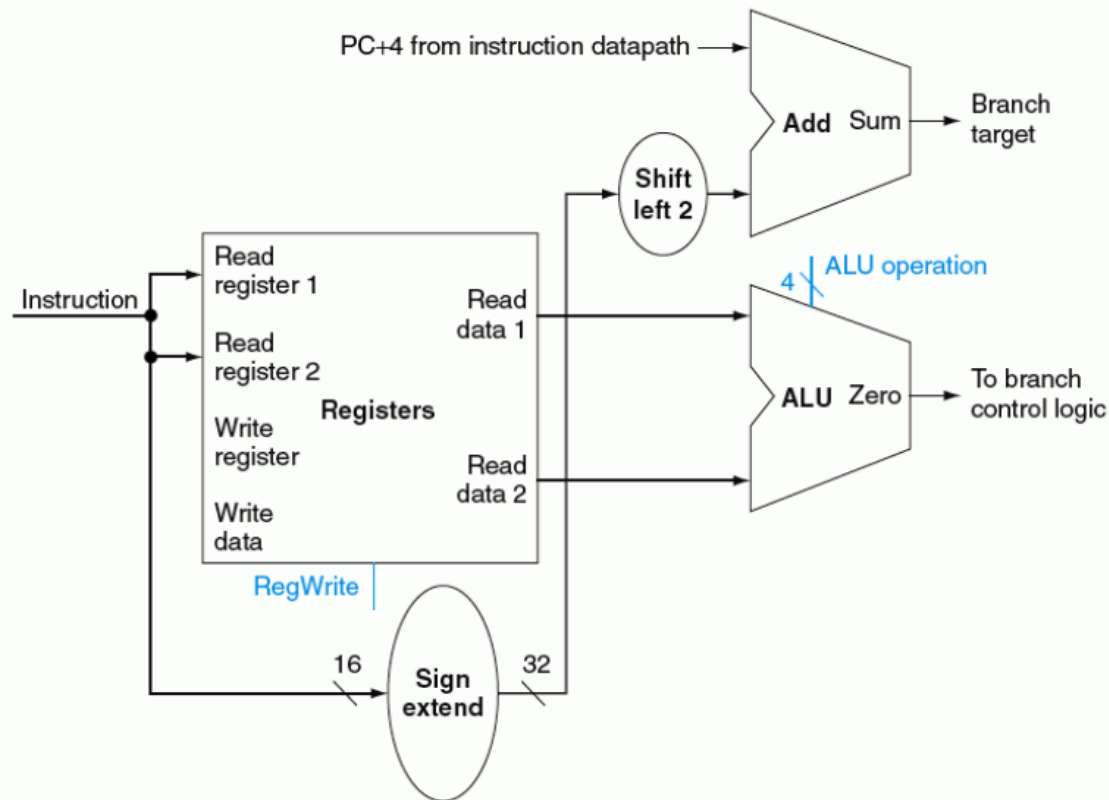
- In Following Circuit:
 - Draw sign-extend & shift logic



Address Bus & Data Bus

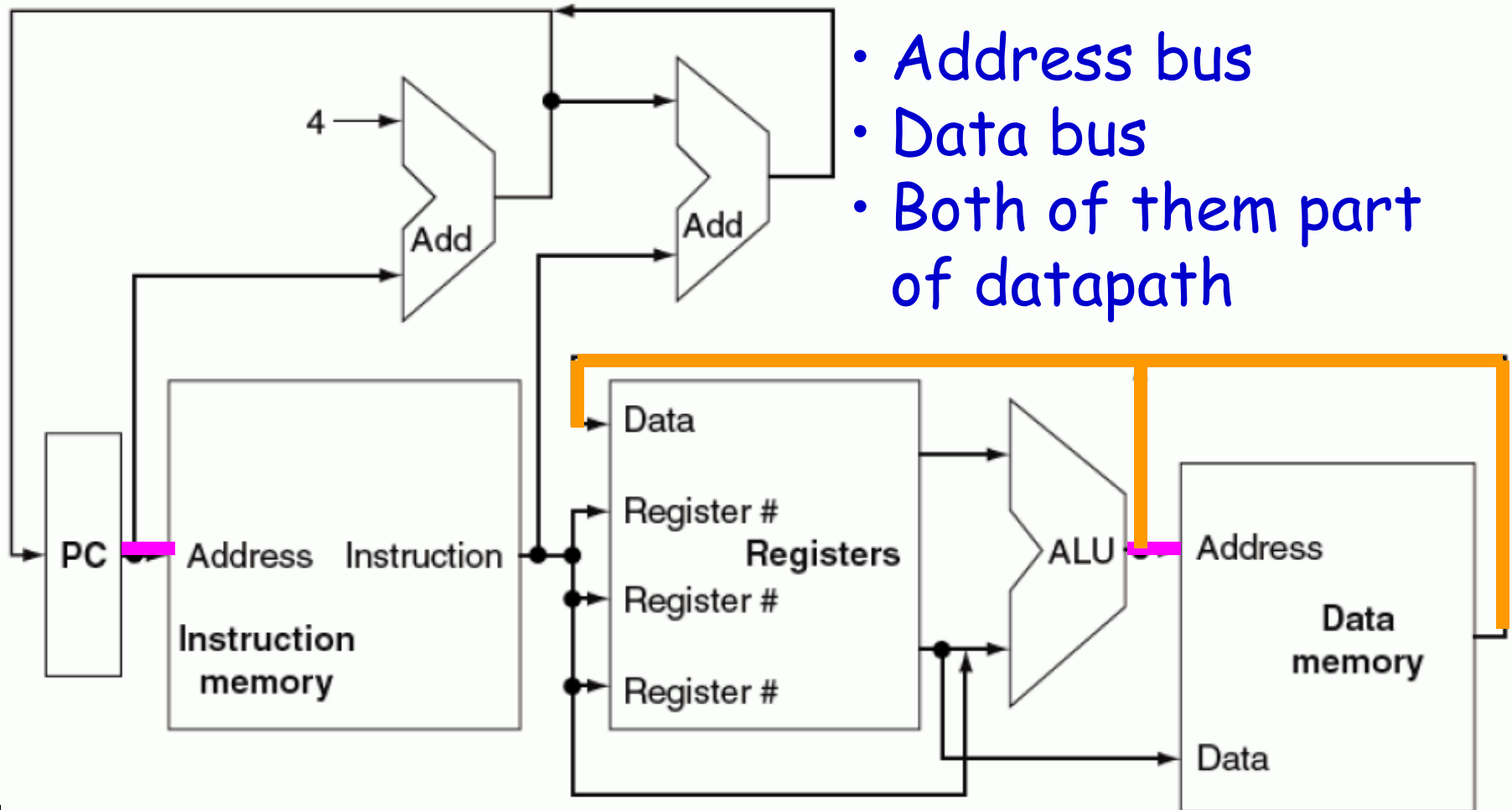


Combining Datapaths

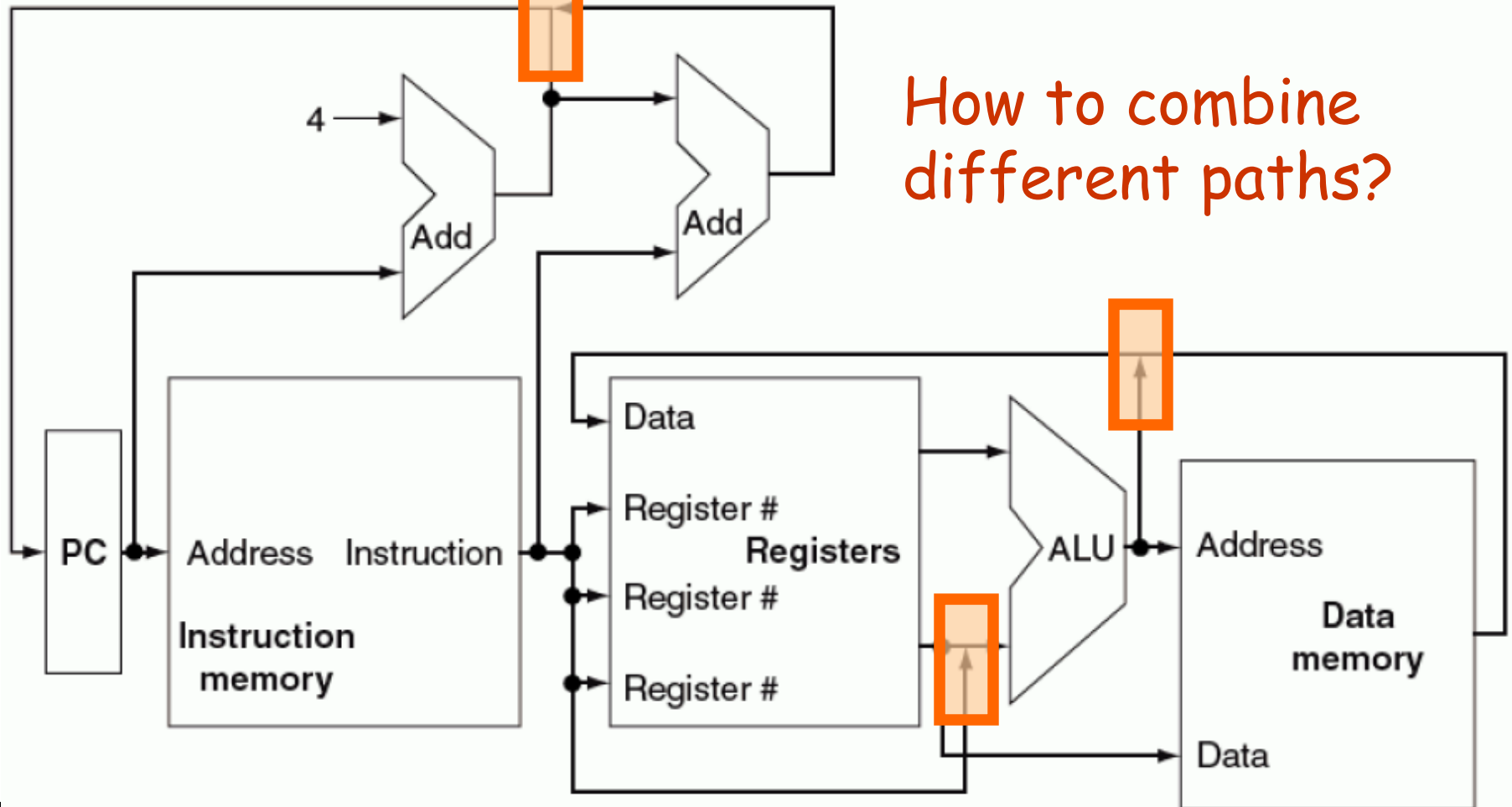


Combining Datapaths (cont.)



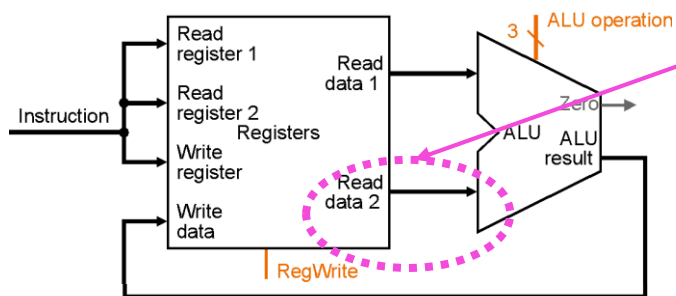- How to have different datapaths for different instruction?



R-type

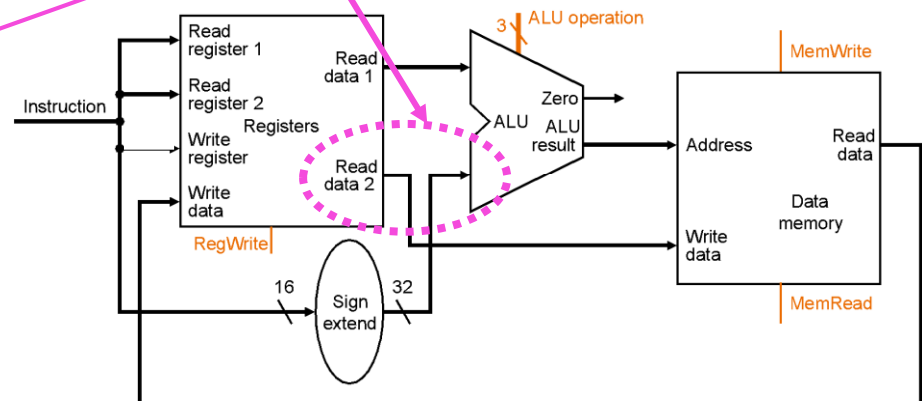



Store




Combining Datapaths (cont.)



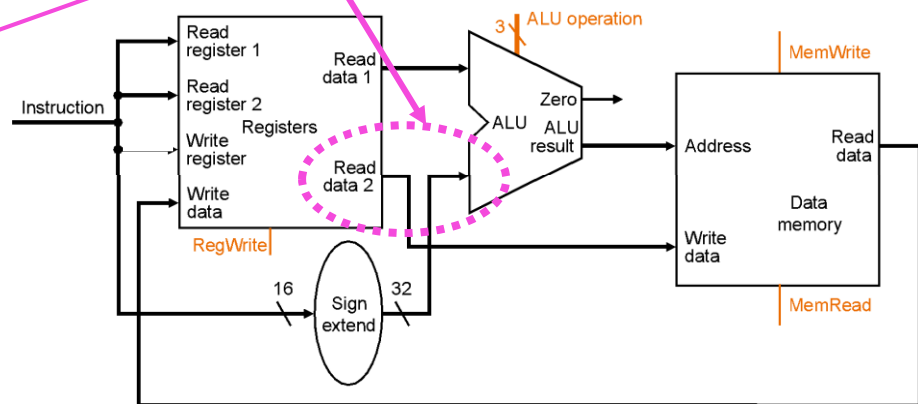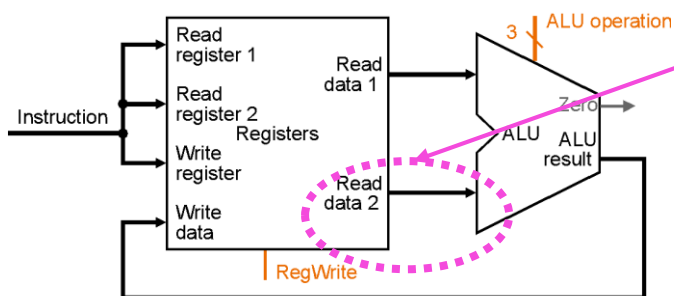- How to have different datapaths for different instruction?




- Use a multiplexer

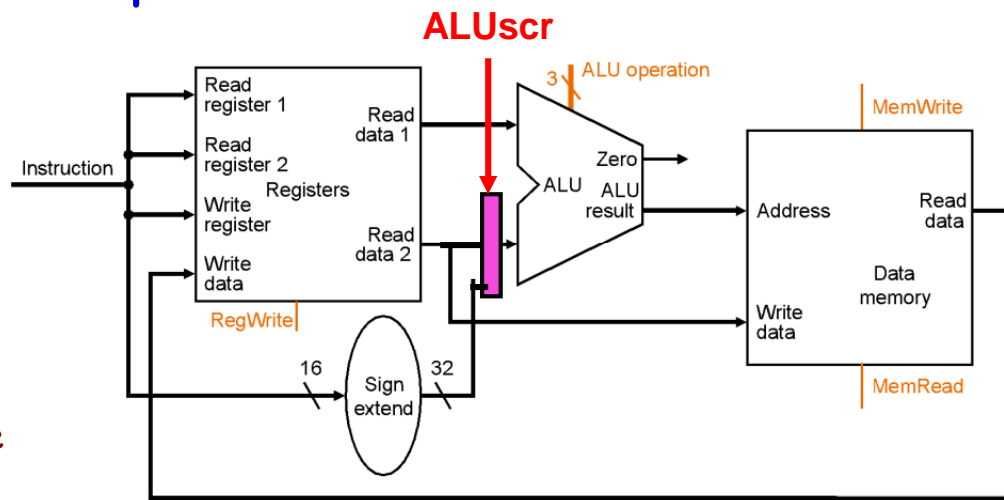

Combining Datapaths (cont.)



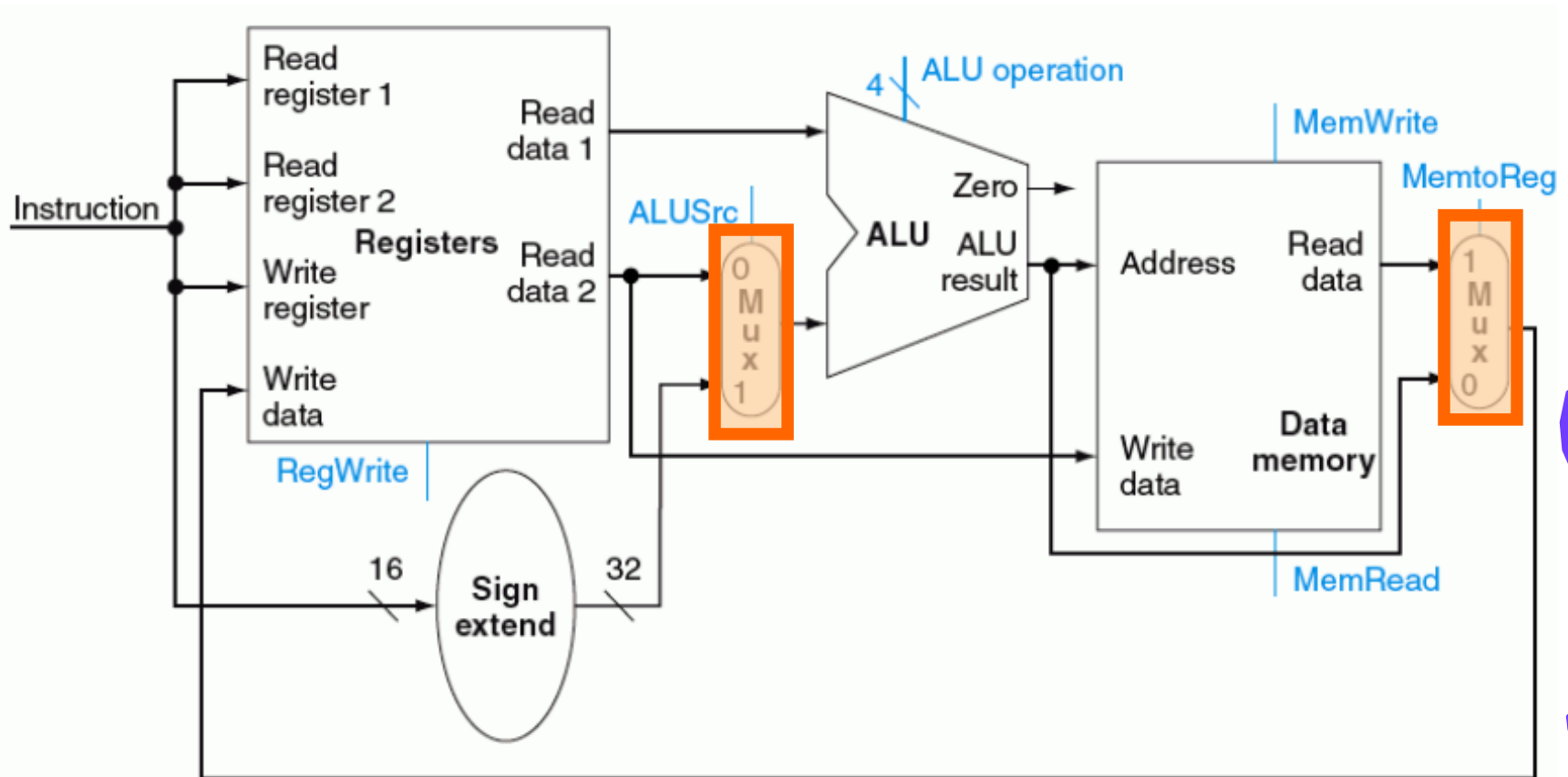- Merging R-type datapath with load/store datapath using multiplexer






Practice



- Question:
 - Could we swap rs, rt, & rd bits to have easier datapath design?
 - In other words, can we remove RegDst MUX?



Practice: Answer

 

- R-type
 - rs & rt: read index bits
 - rd: write index bits
- lw:
 - rs: read index bits
 - rt: write index bits
- sw:
 - rs & rt: read index bits




Reminder: Instruction Encoding




- R-TYPE

- *add rd, rs, rt*
- *sub, and, or, slt*

 


- LOAD / STORE

- *lw rt, rs, imm*
- *sw rt, rs, imm*

 


- BRANCH

- *beq rs, rt, imm*

 



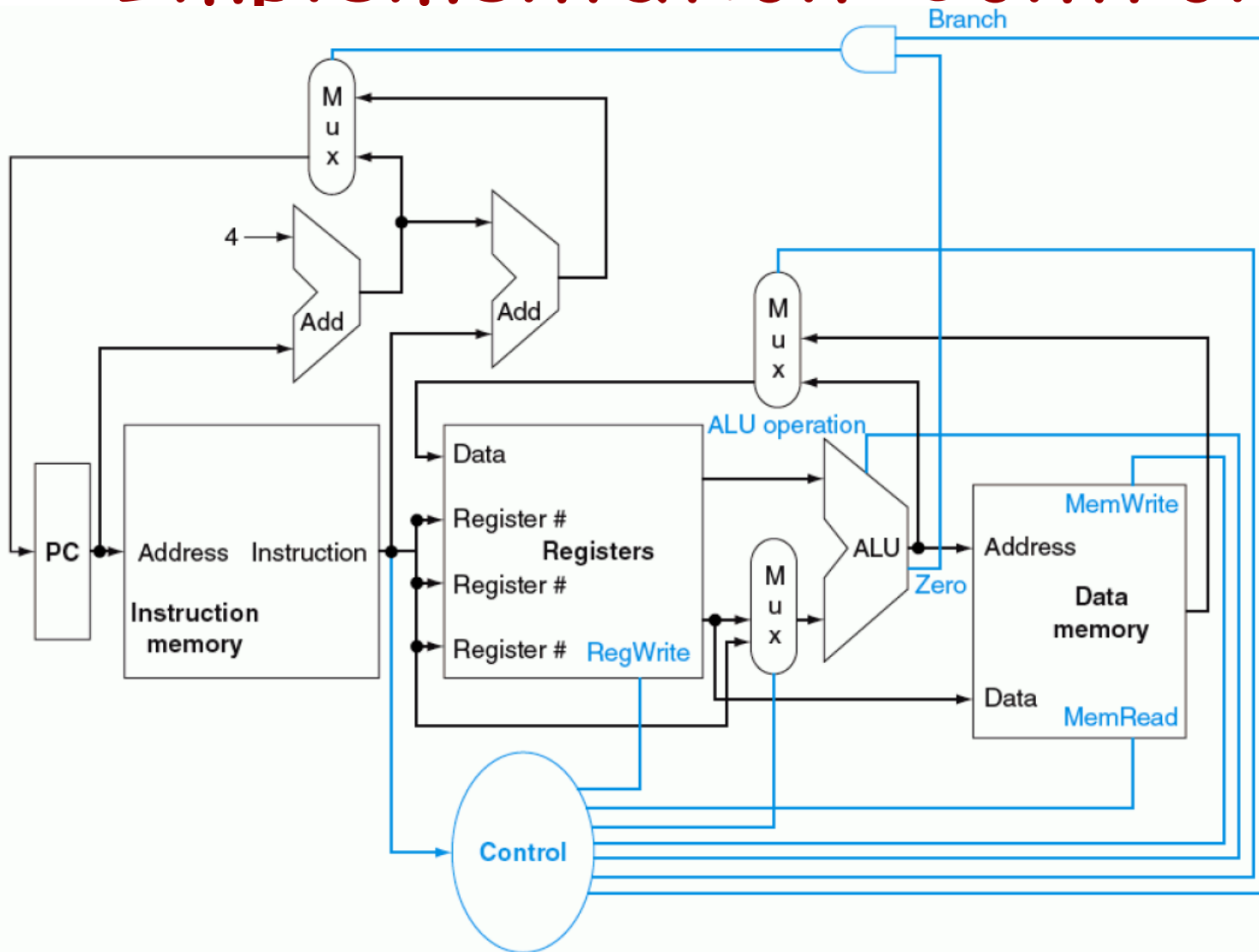
Abstract View of MIPS Implementation: Control



Datapath for Reg-Reg Operations



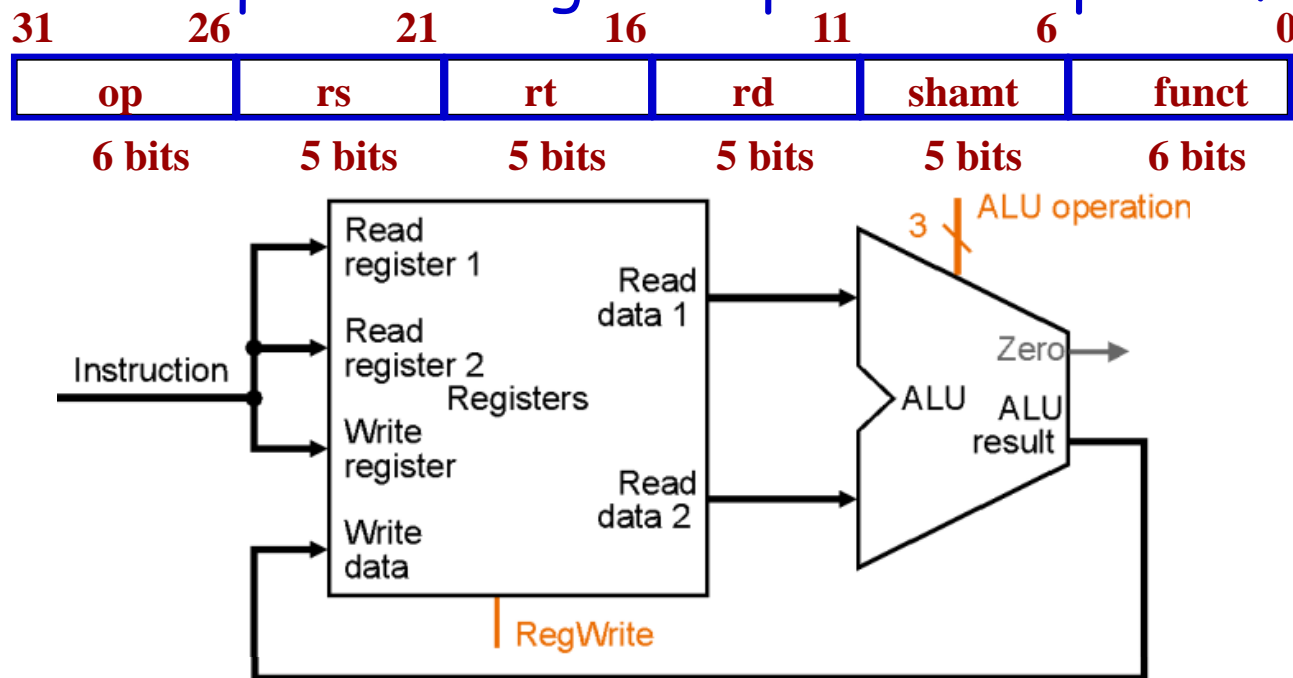- $GPR[rd] \leftarrow GPR[rs] \text{ op } GPR[rt]$
 - Example: *add rd, rs, rt*
 - ALU operation signal depends on op and funct




ALU operation and **RegWrite**: control logic after decoding instruction



Datapath for Load Operations



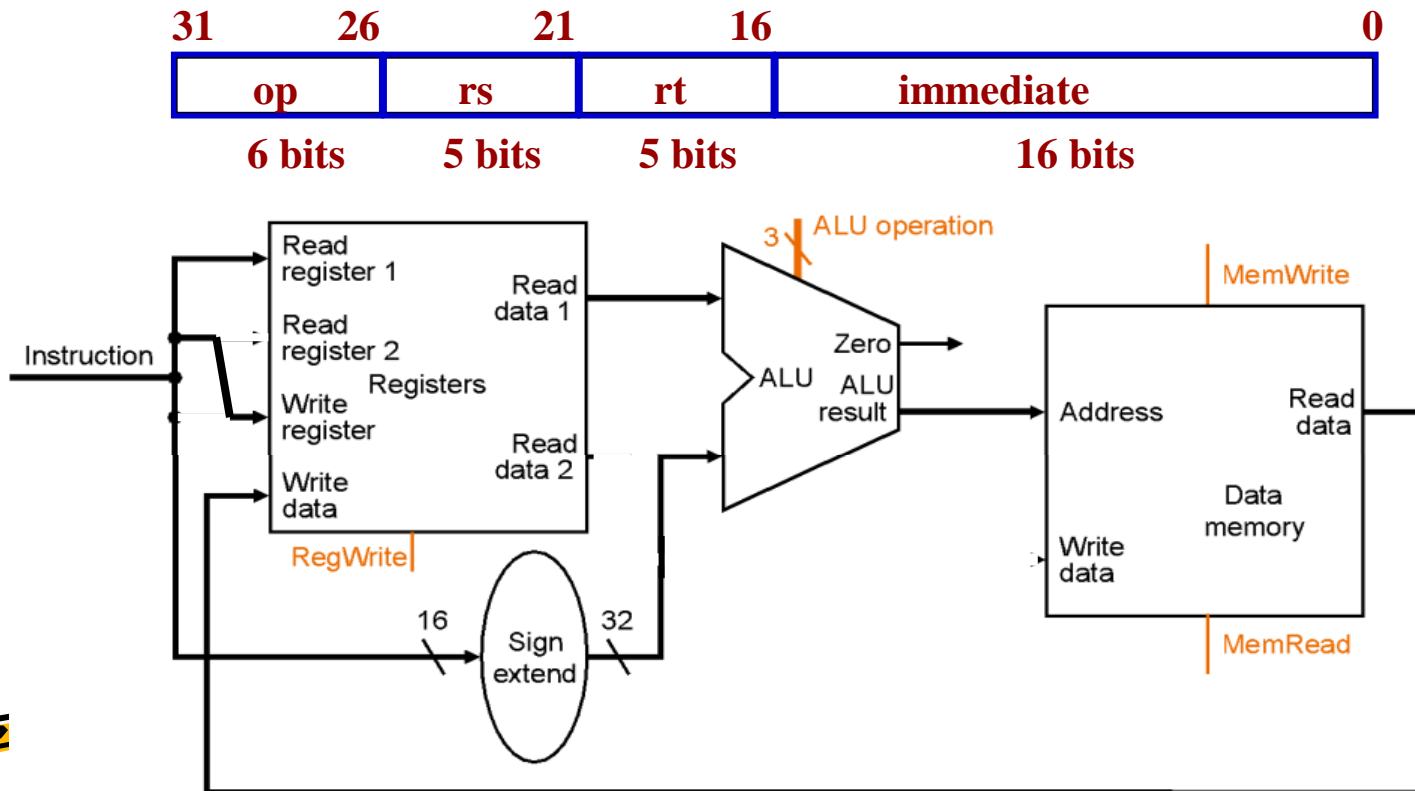
- $GPR[rt] \leftarrow Mem[GPR[rs] + SignExt[imm16]]$
 - Example: *lw rt, rs, imm16*



Datapath for Store Operations




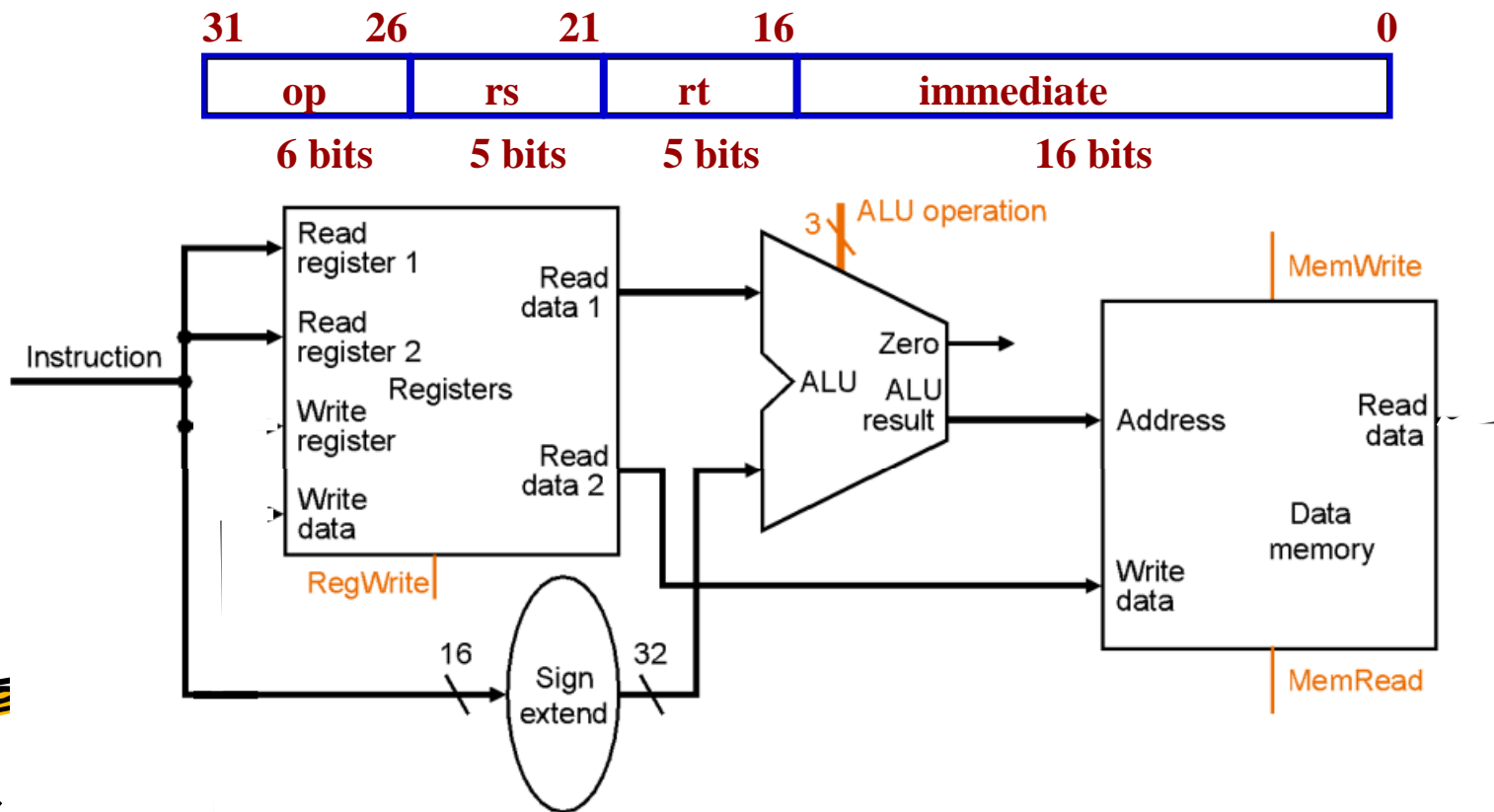
- $\text{Mem}[\text{GPR}[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow \text{GPR}[\text{rt}]$
 - Example: *sw rt, rs, imm16*



Datapath for Branch Operations



- beq rs, rt, imm16*

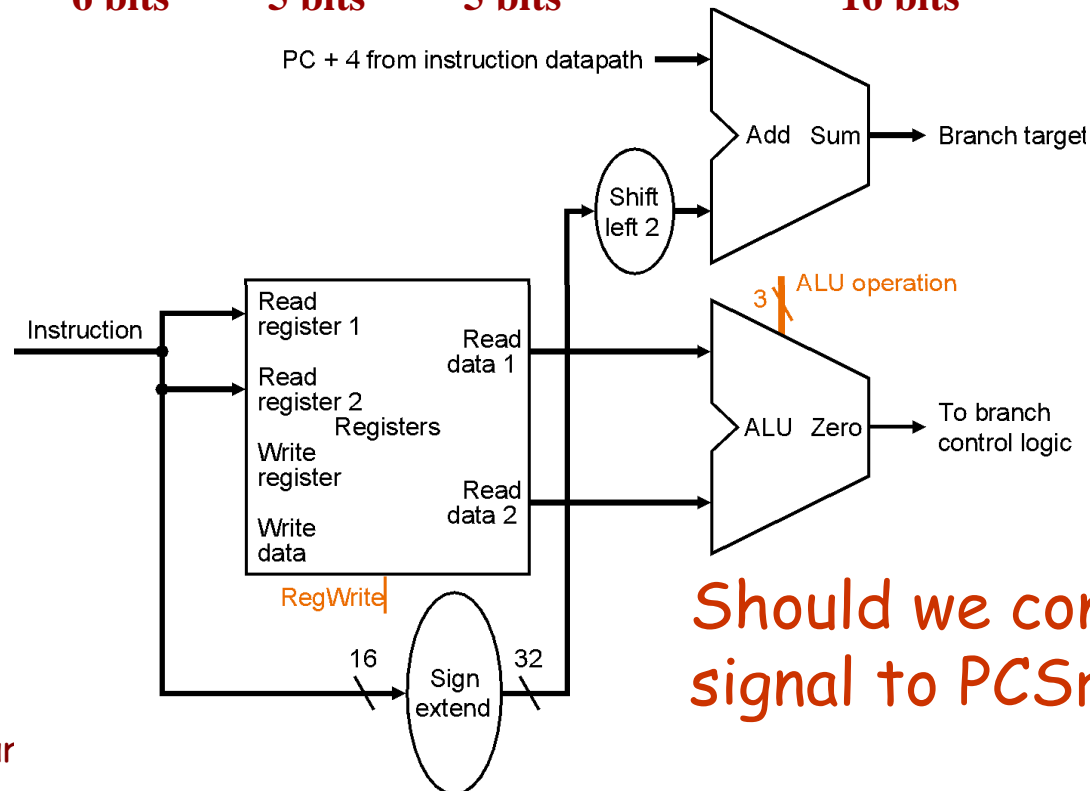 


Should we connect "Zero" signal to PCSrc selector?



A stylized illustration of a yellow pencil with a purple eraser and a purple band near the tip. The pencil is oriented diagonally, pointing towards the bottom right corner of the page. It has a thick black outline and a simple, graphic design.




Load Datapath

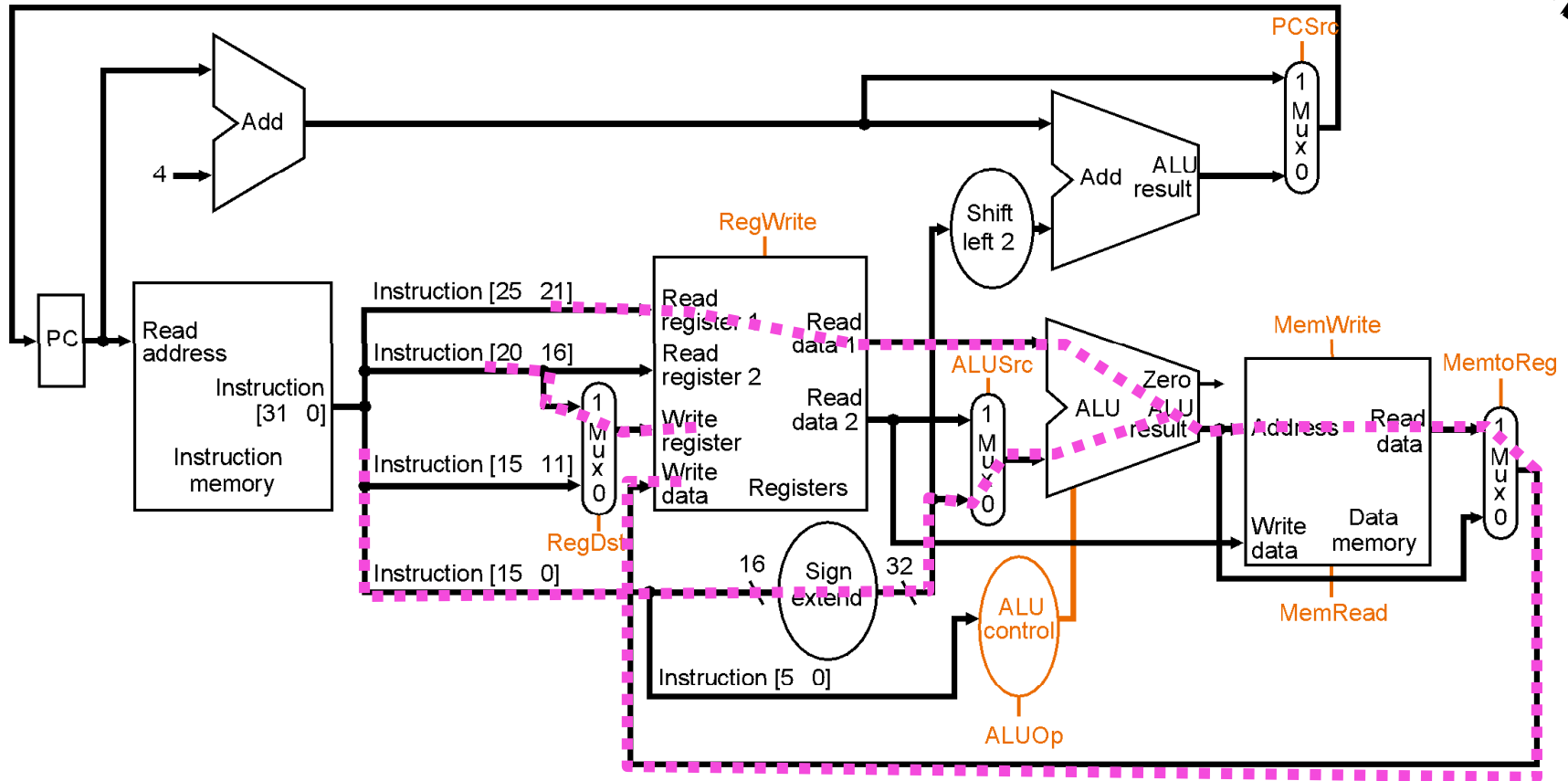

What control signals do we need for load??


Store Datapath

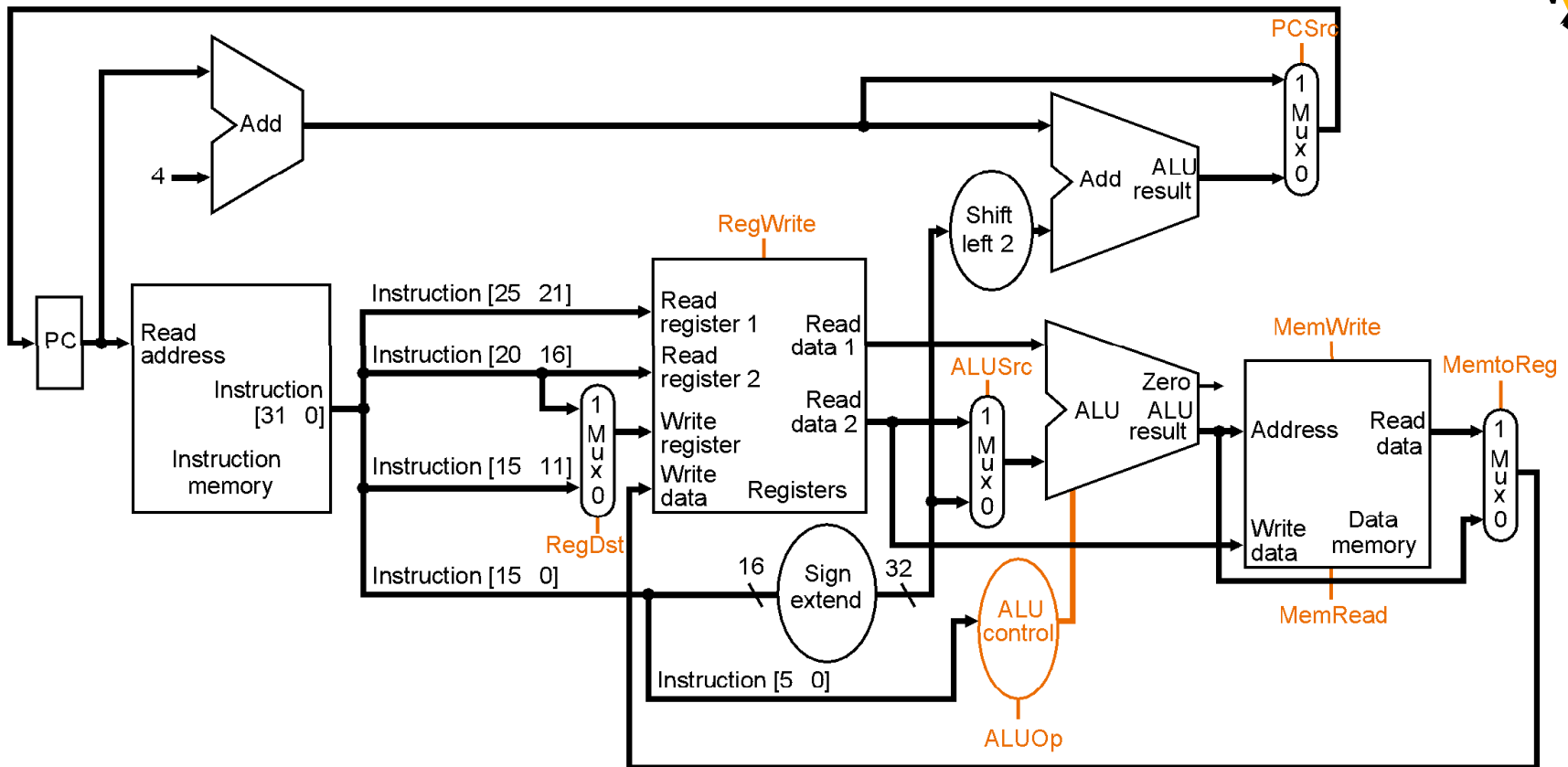

A stylized illustration of a yellow pencil with a purple eraser and a purple sharpened lead tip. The pencil is oriented diagonally from the top-left towards the bottom-right. It features black outlines and decorative black lines along its length.



Putting it All Together

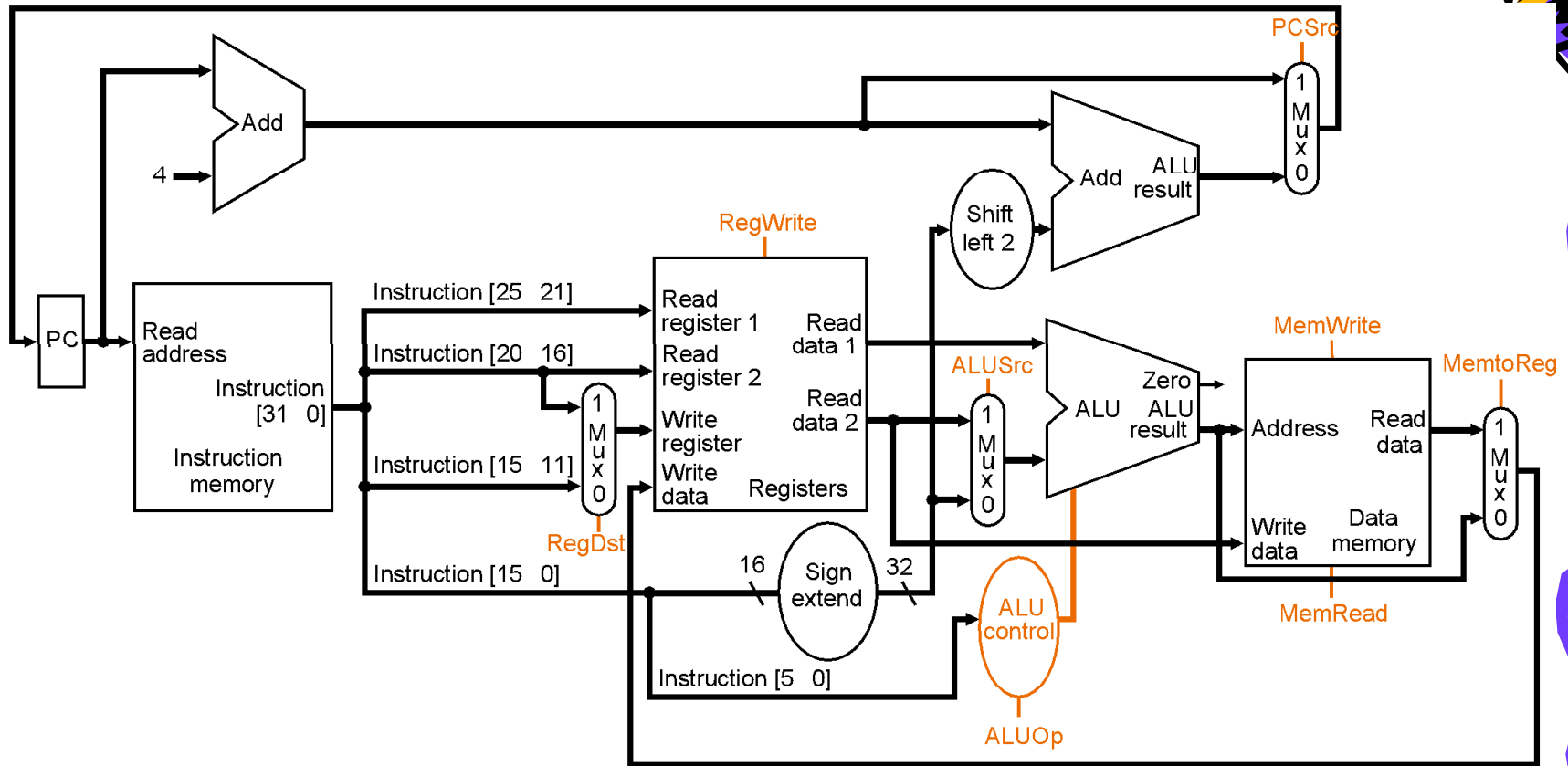

We have everything except details for generating control signals

Backup

