

# شريف جزوه



@sharifjozve96

INTERNATIONAL SIXTH EDITION

# SEDRA/SMITH

INSTRUCTOR'S SOLUTIONS MANUAL FOR  
MICROELECTRONIC CIRCUITS

This version of the text has been adapted and customized. Not for distribution in the U.S.A. or Canada.

This Instructor's Solutions Manual contains complete solutions for the 1000+ end-of-chapter problems created specifically for the International Sixth Edition of Sedra/Smith's *Microelectronic Circuits*.

Oxford University Press, Inc., publishes works that further Oxford University's objective of excellence in research, scholarship, and education.

Oxford New York  
Auckland Cape Town Dar es Salaam Hong Kong Karachi  
Kuala Lumpur Madrid Melbourne Mexico City Nairobi  
New Delhi Shanghai Taipei Toronto

With offices in  
Argentina Austria Brazil Chile Czech Republic France Greece  
Guatemala Hungary Italy Japan Poland Portugal Singapore  
South Korea Switzerland Thailand Turkey Ukraine Vietnam

Copyright © 2011 by Oxford University Press, Inc.

Published by Oxford University Press, Inc.  
198 Madison Avenue, New York, New York 10016  
<http://www.oup.com>

Oxford is a registered trademark of Oxford University Press

All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior permission of Oxford University Press.

**ISBN: 978-0-19-976570-6**

Printing number: 9 8 7 6 5 4 3 2 1

Printed in the United States of America  
on acid-free paper

## Contents

**Exercise Solutions** (Chapters 1 – 16)

**Problem Solutions** (Chapters 1 – 16)

## Preface

This manual contains complete solutions for all exercises and end-of-chapter problems included in the book *Microelectronic Circuits, International Sixth Edition*, by Adel S. Sedra and Kenneth C. Smith.

We are grateful to Mandana Amiri, Shahriar Mirabbasi, Roberto Rosales, Alok Berry, Norman Cox, John Wilson, Clark Kinnaird, Roger King, Marc Cahay, Kathleen Muhonen, Angela Rasmussen, Mike Green, John Davis, Dan Moore, and Bob Krueger, who assisted in the preparation of this manual. We also acknowledge the contribution of Ralph Duncan and Brian Silveira to previous editions of this manual.

Communications concerning detected errors should be sent to the attention of the Engineering Editor, mail to Oxford University Press, 198 Madison Avenue, New York, New York, USA 10016 or e-mail to [higher.education.us@oup.com](mailto:higher.education.us@oup.com). Needless to say, they would be greatly appreciated.

A website for the book is available at [www.oup.com/sedra-xse](http://www.oup.com/sedra-xse)

**Ex: 1.1 When output terminals are open circuited**

$$\text{For circuit a. } v_{OC} = v_s(t)$$

$$\text{For circuit b. } v_{OC} = i_s(t) \times R_s$$

**When output terminals are short-circuited**

$$\text{For circuit a. } i_{sc} = \frac{v_s(t)}{R_s}$$

$$\text{For circuit b. } i_{sc} = i_s(t)$$

**For equivalency**

$$R_s i_s(t) = v_s(t)$$

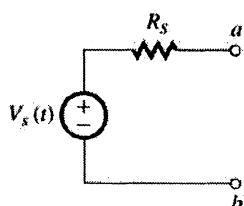


Figure 1.1a


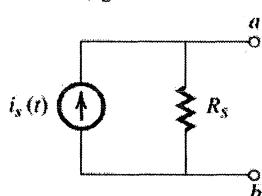


Figure 1.1b

**Ex: 1.2**

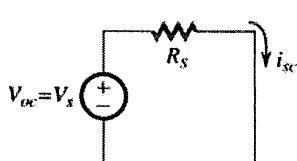


$$V_{OC} = V_s$$

$$i_{SC} = 10 \mu\text{A}$$

$$R = \frac{V}{i} = \frac{10 \text{ mV}}{10 \mu\text{A}} = 1 \text{ k}\Omega$$

**Ex: 1.3 Using voltage divider**

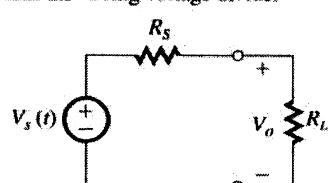

$$v_o(t) = v_s(t) \times \frac{R_L}{R_s + R_L}$$

$$\text{Given } v_s(t) = 10 \text{ mV and } R_s = 1 \text{ k}\Omega$$

$$\text{If } R_L = 100 \text{ k}\Omega$$

$$v_o = 10 \text{ mV} \times \frac{100}{100 + 1} = 9.9 \text{ mV}$$

$$\text{If } R_L = 10 \text{ k}\Omega$$

$$v_o = 10 \text{ mV} \times \frac{10}{10 + 1} \approx 9.1 \text{ mV}$$

$$\text{If } R_L = 1 \text{ k}\Omega$$

$$v_o = 10 \text{ mV} \times \frac{1}{1 + 1} = 5 \text{ mV}$$

$$\text{If } R_L = 100 \Omega$$


$$v_o = 10 \text{ mV} \times \frac{100}{100 + 1 \text{ K}} \approx 0.91 \text{ V}$$

$$80\% \text{ of source voltage} = 10 \text{ mV} \times \frac{80}{100} = 8 \text{ mV}$$

If  $R_L$  gives 8 mV when  $R_s = 1 \text{ k}\Omega$ , then

$$8 = 10 \times \frac{R_L}{1 + R_L} \Rightarrow R_L = 4 \text{ k}\Omega$$

**Ex: 1.4 Using current divider**

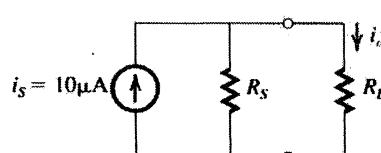

$$i_o = i_s \times \frac{R_s}{R_s + R_L}$$

$$\text{Given } i_s = 10 \mu\text{A}, R_s = 100 \text{ k}\Omega$$

For

$$R_L = 1 \text{ k}\Omega, i_o = 10 \mu\text{A} \times \frac{100}{100 + 1} = 9.9 \mu\text{A}$$

$$\text{For } R_L = 10 \text{ k}\Omega, i_o = 10 \mu\text{A} \times \frac{100}{100 + 10} \approx 9.1 \mu\text{A}$$

For

$$R_L = 100 \text{ k}\Omega, i_o = 10 \mu\text{A} \times \frac{100}{100 + 100} = 5 \mu\text{A}$$

For

$$R_L = 1 \text{ M}\Omega, i_o = 10 \mu\text{A} \times \frac{100 \text{ K}}{100 \text{ K} + 1 \text{ M}} \approx 0.9 \mu\text{A}$$

$$80\% \text{ of source current} = 10 \times \frac{80}{100} = 8 \mu\text{A}$$

If a load  $R_L$  gives 80% of the source current, then

$$8 \mu\text{A} = 10 \mu\text{A} \times \frac{100}{100 + R_L}$$

$$\Rightarrow R_L = 25 \text{ k}\Omega$$

**Ex: 1.5**  $f = \frac{1}{T} = \frac{1}{10^{-3}} = 1000 \text{ Hz}$

$$\omega = 2\pi f = 2\pi \times 10^3 \text{ rad/s}$$

**Ex: 1.6 (a)**  $T = \frac{1}{f} = \frac{1}{60} \text{ s} = 16.7 \text{ ms}$

(b)  $T = \frac{1}{f} = \frac{1}{10^{-3}} = 1000 \text{ s}$

(c)  $T = \frac{1}{f} = \frac{1}{10^6} \text{ s} = 1 \mu\text{s}$

**Ex: 1.7** If 6 MHz is allocated for each channel, then 470 MHz to 806 MHz will accommodate

$$\frac{806 - 470}{6} = 56 \text{ channels}$$

Since it starts with channel 14, it will go from channel 14 to channel 69

**Ex: 1.8**  $P = \frac{1}{T} \int_{0}^{T} \frac{v^2}{R} dt$

$$= \frac{1}{T} \times \frac{V^2}{R} \times T = \frac{V^2}{R}$$

Alternatively,

$$P = P_1 + P_3 + P_5 + \dots$$

$$= \left( \frac{4V}{\sqrt{2}\pi} \right)^2 \frac{1}{R} + \left( \frac{4V}{3\sqrt{2}\pi} \right)^2 \frac{1}{R} + \left( \frac{4V}{5\sqrt{2}\pi} \right)^2 \frac{1}{R} + \dots$$

$$= \frac{V^2}{R} \times \frac{8}{\pi^2} \times \left( 1 + \frac{1}{9} + \frac{1}{25} + \frac{1}{49} + \dots \right)$$

It can be shown by direct calculation that the infinite series in the parentheses has a sum that approaches  $\pi^2/8$ ; thus  $P$  becomes  $V^2/R$  as found from direct calculation.

Fraction of energy in fundamental

$$= 8/\pi^2 \approx 0.81$$

Fraction of energy in first five harmonics

$$= \frac{8}{\pi^2} \left( 1 + \frac{1}{9} + \frac{1}{25} \right) \approx 0.93$$

Fraction of energy in first seven harmonics

$$= \frac{8}{\pi^2} \left( 1 + \frac{1}{9} + \frac{1}{25} + \frac{1}{49} \right) \approx 0.95$$

Fraction of energy in first nine harmonics

$$= \frac{8}{\pi^2} \left( 1 + \frac{1}{9} + \frac{1}{25} + \frac{1}{49} + \frac{1}{81} \right) \approx 0.96$$

Note that 90% of the energy of the square wave is in the first three harmonics; that is, in the fundamental and the third harmonic.

**Ex: 1.9** (a)  $D$  can represent 15 distinct values between 0 and +15 V. Thus,

$$v_A = 0 \text{ V} \Rightarrow D = 0000$$

$$v_A = 1 \text{ V} \Rightarrow D = 0001$$

$$v_A = 2 \text{ V} \Rightarrow D = 0010$$

$$v_A = 15 \text{ V} \Rightarrow D = 1111$$

$$(b) \text{(i)} +1 \text{ V} \text{ (ii)} +2 \text{ V} \text{ (iii)} +4 \text{ V} \text{ (iv)} +8 \text{ V}$$

(c) The closest discrete value represented by  $D$  is 5 V; thus  $D = 0101$ . The error is  $-0.2 \text{ V}$  or  $-0.2/5.2 \times 100 = -4\%$

**Ex: 1.10** Voltage gain =  $20 \log 100 = 40 \text{ dB}$

Current gain =  $20 \log 1000 = 60 \text{ dB}$

$$\begin{aligned} \text{Power gain} &= 10 \log A_p = 10 \log (A_v A_i) \\ &= 10 \log 10^5 = 50 \text{ dB} \end{aligned}$$

**Ex: 1.11**  $P_{dc} = 15 \times 8 = 120 \text{ mW}$

$$P_L = \frac{(6/\sqrt{2})^2}{1} = 18 \text{ mW}$$

$$P_{\text{dissipated}} = 120 - 18 = 102 \text{ mW}$$

$$\eta = \frac{P_L}{P_{dc}} \times 100 = \frac{18}{120} \times 100 = 15\%$$

**Ex: 1.12**

$$v_o = 1 \times \frac{10}{10^6 + 10} \approx 10^{-5} \text{ V} = 10 \mu\text{V}$$

$$P_L = v_o^2 / R_L = \frac{(10 \times 10^{-6})^2}{10} = 10^{-11} \text{ W}$$

With the buffer amplifier:

$$\begin{aligned} v_o &= 1 \times \frac{R_i}{R_i + R_S} \times A_{\infty} \times \frac{R_L}{R_L + R_o} \\ &= 1 \times \frac{1}{1+1} \times 1 \times \frac{10}{10+10} = 0.25 \text{ V} \end{aligned}$$

$$P_L = \frac{v_o^2}{R_L} = \frac{0.25^2}{10} = 6.25 \text{ mW}$$

$$\begin{aligned} \text{Voltage gain} &= \frac{v_o}{v_s} = \frac{0.25 \text{ V}}{1 \text{ V}} = 0.25 \text{ V/V} \\ &\approx -12 \text{ dB} \end{aligned}$$

$$\text{Power gain } (A_p) = \frac{P_L}{P_i}$$

where  $P_L = 6.25 \text{ mW}$  and  $P_i = v_i i_i$ ,

$$v_i = 0.5 \text{ V} \text{ and}$$

$$i_i = \frac{1 \text{ V}}{1 \text{ M}\Omega + 1 \text{ M}\Omega} = 0.5 \mu\text{A}$$

Thus,


$$P_i = 0.5 \times 0.5 = 0.25 \mu\text{W}$$

and,

$$A_p = \frac{6.25 \times 10^{-3}}{0.25 \times 10^{-6}} = 25 \times 10^3$$

$$10 \log A_p = 44 \text{ dB}$$

This figure belongs to Exercise 1.15

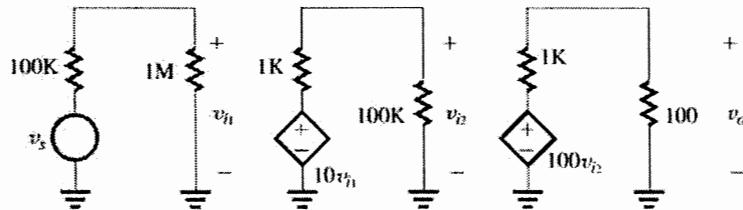

**Ex: 1.13** Open-circuit (no load) output voltage =

$$A_{v_o} v_i$$

Output voltage with load connected

$$= A_{v_o} v_i \frac{R_L}{R_L + R_o}$$

$$0.8 = \frac{1}{R_o + 1} \Rightarrow R_o = 0.25 \text{ k}\Omega = 250 \Omega$$

**Ex: 1.14**  $A_{v_o} = 40 \text{ dB} = 100 \text{ V/V}$

$$P_L = \frac{v_o^2}{R_L} = \left( A_{v_o} v_i \frac{R_L}{R_L + R_o} \right)^2 / R_L \\ = v_i^2 \times \left( 100 \times \frac{1}{1+1} \right)^2 / 1000 = 2.5 v_i^2$$

$$P_i = \frac{v_i^2}{R_i} = \frac{v_i^2}{10,000}$$

$$A_p = \frac{P_L}{P_i} = \frac{2.5 v_i^2}{10^{-4} v_i^2} = 2.5 \times 10^4 \text{ W/W}$$

$$10 \log A_p \approx 44 \text{ dB}$$

**Ex: 1.15** Without stage 3 (see figure above)

$$\frac{v_o}{v_s} = \left( \frac{1 \text{ M}}{100 \text{ K} + 1 \text{ M}} \right) (10) \left( \frac{100 \text{ K}}{100 \text{ K} + 1 \text{ K}} \right) \\ \times (100) \left( \frac{100}{100 + 1 \text{ K}} \right)$$

$$\frac{v_o}{v_s} = (0.909)(10)(0.9901)(100)(0.0909) = 81.8 \text{ V}$$

**Ex: 1.16** Given  $v_s = 1 \text{ mV}$

$$\frac{v_i}{v_s} = 0.909 \text{ So}$$

$$v_{i1} = 0.909 v_s = 0.909 \times 1 = 0.909 \text{ mV}$$

$$\frac{v_{i2}}{v_s} = \frac{v_{i2}}{V_{i1}} \times \frac{v_{i1}}{V_s} = 9.9 \times 0.909 = 9 \text{ V/V}$$

$$\text{For } v_s = 1 \text{ mV}$$

$$v_{i2} = 9 \times v_s = 9 \times 1 = 9 \text{ mV}$$

$$\frac{v_{i3}}{v_s} = \frac{v_{i3}}{v_{i2}} \times \frac{v_{i2}}{v_{i1}} \times \frac{v_{i1}}{v_s} = 90.9 \times 9.9 \times 0.909$$

$$= 818 \text{ V/V}$$

$$\text{For } v_s = 1 \text{ mV}$$


$$v_{i3} = 818 v_s = 818 \times 1 = 818 \text{ mV}$$

$$\frac{v_{iL}}{v_s} = \frac{v_{iL}}{v_{i3}} \times \frac{v_{i3}}{v_{i2}} \times \frac{v_{i2}}{v_{i1}} \times \frac{v_{i1}}{v_s} \\ = 0.909 \times 90.9 \times 9.9 \times 0.909 \approx 744$$

$$\text{For } V_s = 1 \text{ mV}$$

$$V_{iL} = 744 \times 1 \text{ mV} = 744 \text{ mV}$$

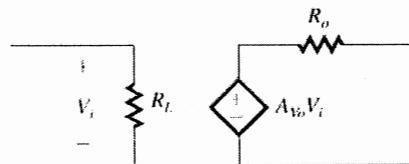**Ex: 1.17** Using voltage amplifier model, it can be represented as



$$R_i = 1 \text{ M}\Omega$$

$$R_o = 10 \Omega$$

$$A_{vo} = A_{v1} \times A_{v2} = 9.9 \times 90.9 = 900 \text{ V/V}$$

The overall voltage gain

$$\frac{V_o}{V_s} = \frac{R_o}{R_i + R_s} \times A_{vo} \times \frac{R_L}{R_L + R_o}$$

$$\text{For } R_L = 10 \Omega$$

Overall voltage gain

$$= \frac{1 \text{ M}}{1 \text{ M} + 100 \text{ K}} \times 900 \times \frac{10}{10 + 10} = 409 \text{ V/V}$$


$$\text{For } R_i = 1000 \Omega$$

Overall voltage gain

$$= \frac{1 \text{ M}}{1 \text{ M} + 100 \text{ K}} \times 900 \times \frac{1000}{1000 + 10} = 810 \text{ V/V}$$

∴ Range of voltage gain is from 409 to 810 V/V

**Ex: 1.18**

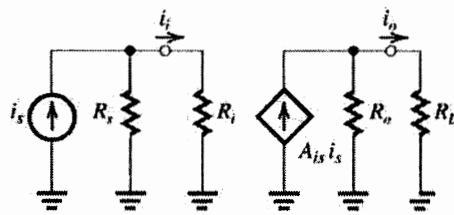


$$i_i = i_s \frac{R_s}{R_s + R_i}$$

$$i_o = A_{is} i_i \frac{R_o}{R_o + R_L} = A_{is} i_s \frac{R_s}{R_s + R_i} \frac{R_o}{R_o + R_L}$$

Thus,

$$\frac{i_o}{i_s} = A_{is} \frac{R_s}{R_s + R_i} \frac{R_o}{R_o + R_L}$$

**Ex: 1.19**

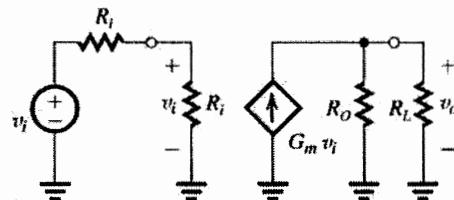

$$v_i = v_s \frac{R_i}{R_i + R_s}$$


$$v_s = G_m v_i (R_o \parallel R_L)$$

$$= G_m v_s \frac{R_i}{R_i + R_s} (R_o \parallel R_L)$$

Thus,

$$\frac{v_o}{v_s} = G_m \frac{R_i}{R_i + R_s} (R_o \parallel R_L)$$

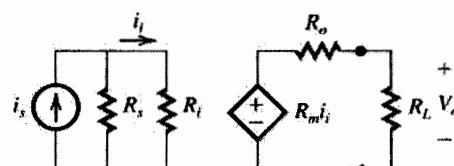**Ex: 1.20** Using transresistance circuit model the circuit will be



$$\frac{i_i}{i_s} = \frac{R_s}{R_i + R_s}$$


$$V_o = R_m i_i \times \frac{R_L}{R_L + R_o}$$

$$\frac{V_o}{i_i} = R_m \frac{R_L}{R_L + R_o}$$

$$\text{Now } \frac{V_o}{i_s} = \frac{V_o}{i_i} \times \frac{i_i}{i_s} = R_m \frac{R_L}{R_L + R_o} \times \frac{R_s}{R_i + R_s}$$

$$= R_m \frac{R_s}{R_s + R_i} \times \frac{R_L}{R_L + R_o}$$

**Ex: 1.21**

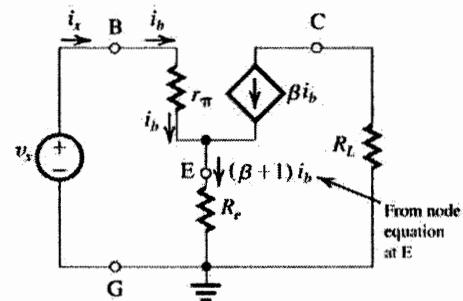

$$v_b = i_b r_\pi + (\beta + 1) i_b R_e$$


$$= i_b [r_\pi + (\beta + 1) R_e]$$

But  $v_b = v_x$  and  $i_b = i_x$ , thus


$$R_{in} = \frac{v_x}{i_x} = \frac{v_b}{i_b} = r_\pi + (\beta + 1) R_e$$

**Ex: 1.22**

f	Gain
10 Hz	60 dB
10 kHz	40 dB
100 kHz	20 dB
1 MHz	0 dB

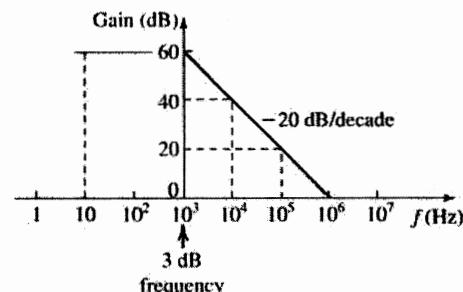

**Ex: 1.23**

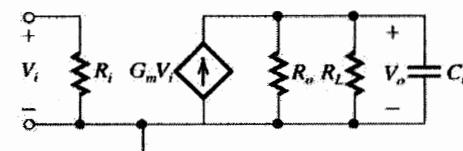

$$V_o = G_m V_i [R_o \parallel R_L \parallel C_L]$$

$$= \frac{G_m V_i}{\frac{1}{R_o} + \frac{1}{R_L} + s C_L}$$

$$\text{Thus, } \frac{V_o}{V_i} = \frac{G_m}{\frac{1}{R_o} + \frac{1}{R_L}} \frac{1}{1 + \frac{s C_L}{\frac{1}{R_o} + \frac{1}{R_L}}}$$

which is of the STC LP type.

$$\text{DC gain} = \frac{G_m}{\frac{1}{R_o} + \frac{1}{R_L}} \geq 100$$

$$\frac{1}{R_o} + \frac{1}{R_L} \leq \frac{G_m}{100} = \frac{10}{100} = 0.1 \text{ mA/V}$$

$$\frac{1}{R_L} \leq 0.1 - \frac{1}{50} = 0.08 \text{ mA/V}$$

$$R_L \geq \frac{1}{0.08} \text{ k}\Omega = 12.5 \text{ k}\Omega$$

$$\omega_o = \frac{1}{C_L(R_o + R_L)} \geq 2\pi \times 100 \text{ kHz}$$

$$C_L \leq \frac{\left( \frac{1}{50 \times 10^3} + \frac{1}{12.5 \times 10^3} \right)}{2\pi \times 10^5} = 159.2 \text{ pF}$$

**Ex: 1.24** Refer to Fig. E1.23

$$\frac{V_2}{V_s} = \frac{R_i}{R_s + \frac{1}{sC} + R_i} = \frac{R_i}{R_s + R_i s + \frac{1}{C(R_s + R_i)}}$$

which is a HP STC function.

$$f_{3\text{dB}} = \frac{1}{2\pi C(R_s + R_i)} \leq 100 \text{ Hz}$$

$$C \geq \frac{1}{2\pi(1+9)10^3 \times 100} = 0.16 \mu\text{F}$$

**Ex: 1.25**

T = 50 K

$$n_i = BT^{3/2} e^{-E_g/(2kT)}$$

$$= 7.3 \times 10^{15} (50)^{3/2} e^{-1.12/2 \times 8.62 \times 10^{-5} \times 50}$$

$$\approx 9.6 \times 10^{15} / \text{cm}^3$$

T = 350 K

$$n_i = BT^{3/2} e^{-E_g/(2kT)}$$

$$= 7.3 \times 10^{15} (350)^{3/2} e^{-1.12/2 \times 8.62 \times 10^{-5} \times 350}$$

$$= 4.15 \times 10^{11} / \text{cm}^3$$

**Ex: 1.26**

$$N_D = 10^{17} / \text{cm}^3$$

From Exercise 3.1  $n_i$  at

$$T = 350 \text{ K} = 4.15 \times 10^{11} / \text{cm}^3$$

$$n_n = N_D = 10^{17} / \text{cm}^3$$

$$p_n = \frac{n_i^2}{N_D}$$

$$= \frac{(4.15 \times 10^{11})^2}{10^{17}}$$

$$= 1.72 \times 10^6 / \text{cm}^3$$

**Ex: 1.27**

$$\text{At } 300 \text{ K}, n_i = 1.5 \times 10^{10} / \text{cm}^3$$

$$p_p = N_A$$

Want electron concentration

$$= n_p = \frac{1.5 \times 10^{10}}{10^6} = 1.5 \times 10^4 / \text{cm}^3$$

$$\therefore N_A = p_p = \frac{n_i^2}{n_p}$$

$$= \frac{(1.5 \times 10^{10})^2}{1.5 \times 10^4}$$

$$= 1.5 \times 10^{16} / \text{cm}^3$$

**Ex: 1.28**

$$\text{a. } v_{\text{d}} = -\mu_n E$$

Here negative sign indicates that electrons move in a direction opposite to E

We use

$$v_{\text{d}} = -\mu_n E$$

$$= 1350 \times \frac{1}{2 \times 10^{-4}} \because 1 \mu\text{m} = 10^{-4} \text{ cm}$$

$$= 6.75 \times 10^6 \text{ cm/s} = 6.75 \times 10^4 \text{ m/s}$$

b. Time taken to cross 2 μm

$$\text{length} = \frac{2 \times 10^6}{6.75 \times 10^4} \approx 30 \text{ ps}$$

c. In n+ drift current density  $J_n$  in

$$J_n = q n \mu_n E$$

$$= 1.6 \times 10^{-19} \times 10^{16} \times 1350 \times \frac{1 \text{ V}}{2 \times 10^{-4}}$$

$$= 1.08 \times 10^4 \text{ A/cm}^2$$

d. Drift current  $I_n = A q n v_{\text{d}}$ -drift

$$= A q n \mu_n E$$

$$= 0.25 \times 10^{-8} \times 1.08 \times 10^4$$

$$= 27 \mu\text{A}$$

$$\text{Note } 0.25 \mu\text{m}^2 = 0.25 \times 10^{-8} \text{ cm}^2$$

$$\text{Ex: 1.29 } J_n = q D_n \frac{dn(x)}{dx}$$

From Figure E1.29

$$n_o = 10^{17} / \text{cm}^3 = 10^5 / (\mu\text{m})^3$$

$$D_n = 35 \text{ cm}^2/\text{s} = 35 \times (10^4)^2 (\mu\text{m})^2/\text{s}$$

$$= 35 \times 10^8 (\mu\text{m})^2/\text{s}$$

$$\frac{dn}{dx} = \frac{10^5 - 0}{1} = 10^5 \mu\text{m}^{-2}$$

$$J_n = q D_n \frac{dn(x)}{dx}$$

$$= 1.6 \times 10^{-19} \times 35 \times 10^8 \times 10^5$$

$$= 56 \times 10^{-6} \text{ A}/(\mu\text{m})^2$$

$$= 56 \mu\text{A}/(\mu\text{m})^2$$

For  $I_n = 1 \text{ mA} = J_n \times A$

$$\Rightarrow A = \frac{1 \text{ mA}}{J_n} = \frac{10^3 \mu\text{A}}{56 \mu\text{A}/(\mu\text{m})^2} \approx 18 \mu\text{m}^2$$

**Ex: 1.30**

Using equation 1.45

$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T$$

$$D_n = \mu_n V_T = 1350 \times 25.9 \times 10^{-3}$$

$$\approx 35 \text{ cm}^2/\text{s}$$

$$D_p = \mu_p V_T = 480 \times 25.9 \times 10^{-3}$$

$$\approx 12.4 \text{ cm}^2/\text{s}$$

**Ex: 1.31**

Equation 3.50

$$W = \sqrt{\frac{2e_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) V_o}$$

$$= \sqrt{\frac{2\epsilon_s}{q} \left( \frac{N_A + N_D}{N_A N_D} \right) V_o}$$

$$W^2 = \frac{2\epsilon_s}{q} \left( \frac{N_A + N_D}{N_A N_D} \right) V_o$$

$$V_o = \frac{1}{2} \left( \frac{q}{\epsilon_s} \right) = \left( \frac{N_A N_D}{N_A + N_D} \right) W^2$$

Ex: 1 . 32

In a p+ n diode  $N_A \gg N_D$

$$\text{Equation 1.50 } W = \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) V_o}$$

We can neglect the term  $\frac{1}{N_A}$  as Compared to  $\frac{1}{N_D}$  since  $N_A \gg N_D$

$$\approx \sqrt{\frac{2\epsilon_s}{q N_D} \cdot V_o}$$

$$\text{Equation 1.51 } X_n = W \frac{N_A}{N_A + N_D}$$

$$\approx W \frac{N_D}{N_D}$$

$$= W$$

$$\text{Equation 1.52 } X_p = W \frac{N_A}{N_A + N_D}$$

since  $N_A \gg N_D$

$$\approx W \frac{N_D}{N_A} = W \left( \frac{N_A}{N_D} \right)$$

$$\text{Equation 1.53 } Q_J = Aq \left( \frac{N_A N_D}{N_A + N_D} \right)$$

$$W \approx Aq \frac{N_A N_D}{N_A} \cdot W \text{ since } N_A \gg N_D$$

$$\approx Aq N_D W$$

$$\text{Equation 1.54 } Q_J = A \sqrt{2\epsilon_s q \left( \frac{N_A N_D}{N_A + N_D} \right) V_o}$$

$$\approx A \sqrt{2\epsilon_s q \left( \frac{N_A N_D}{N_A} \right) V_o} \text{ since } N_A \gg N_D$$

$$= A \sqrt{2\epsilon_s q N_D V_o}$$

Ex: 1 . 33

In example 1.29  $N_A = 10^{18}/\text{cm}^3$  and

$$N_D = 10^{16}/\text{cm}^3$$

In the n-region of this pn junction diode

$$n_n = N_D = 10^{16}/\text{cm}^3$$

$$p_n = \frac{n_i^2}{n_n} = \frac{(1.5 \times 10^{10})^2}{10^{16}} = 2.25 \times 10^4/\text{cm}^3$$

As one can see from above equation, to increase minority carrier-concentration ( $p_n$ ) by a factor of 2, one must lower  $N_D (= n_n)$  by a factor of 2.

Ex: 1 . 34

$$\text{Equation 1.38 } I_S = Aq n_i^2 \left( \frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$

since  $\frac{D_p}{L_p}$  and  $\frac{D_n}{L_n}$  here approximately

similar values, if  $N_A \gg N_D$ , then the term  $\frac{D_n}{L_n N_A}$

can be neglected as compared to  $\frac{D_p}{L_p N_D}$

$$\therefore I_S \approx Aq n_i^2 \frac{D_p}{L_p N_D}$$

Ex: 1 . 35

$$I_S = Aq n_i^2 \left( \frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$

$$= 10^{-4} \times 1.6 \times 10^{-19} \times (1.5 \times 10^1)^2$$

$$\times \left( \frac{10}{5 \times 10^{-4} \times \frac{10^{16}}{2}} + \frac{10}{10 \times 10^{-4} \times 10^{18}} \right)$$

$$= 1.45 \times 10^{-14} \text{ A}$$

$$I = I_S (e^{V/V_T} - 1)$$

$$\approx I_S e^{V/V_T} = 1.45 \times 10^{-14} e^{0.605/25.9 \times 10^{-3}}$$

$$= 0.2 \text{ mA}$$

Ex: 1 . 36

$$W = \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) (V_o - V_F)}$$

$$= \sqrt{\frac{2 \times 1.04 \times 10^{-12}}{1.6 \times 10^{-19}} \left( \frac{1}{10^{18}} + \frac{1}{10^{16}} \right) (0.814 - 0.605)}$$

$$= 1.66 \times 10^{-5} \text{ cm} = 0.166 \mu\text{m}$$

Ex: 1 . 37

$$W = \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) (V_o + V_R)}$$

$$= \sqrt{\frac{2 \times 1.04 \times 10^{-12}}{1.6 \times 10^{-19}} \left( \frac{1}{10^{18}} + \frac{1}{10^{16}} \right) (0.814 + 2)}$$

$$= 6.08 \times 10^{-5} \text{ cm} = 0.608 \mu\text{m}$$

Using equation 1.53

$$Q_J = Aq \left( \frac{N_A N_D}{N_A + N_D} \right) W$$

$$= 10^{-4} \times 1.6 \times 10^{-19} \left( \frac{10^{18} \times 10^{16}}{10^{18} + 10^{16}} \right) \times 6.08 \times 10^{-5} \text{ cm}$$

$$= 9.63 \text{ pC}$$

**Ex: 1.40**

Equation 1.74

$$\tau_p = \frac{L_p^2}{D_p}$$

$$= \frac{(5 \times 10^{-4})^2}{5}$$

$$= 25 \text{ ns}$$

Equation 1.81

$$C_d = \left( \frac{\tau_T}{V_T} \right) I$$

In example 1.30  $N_A = 10^{18}/\text{cm}^3$ ,

$$N_D = 10^{16}/\text{cm}^3$$

Assuming  $N_A \gg N_D$

$$\tau_T \approx \tau_p = 25 \text{ ns}$$

$$\therefore C_d = \left( \frac{25 \times 10^{-9}}{25.9 \times 10^{-3}} \right) 0.1 \times 10^{-3}$$

$$= 96.5 \text{ pF}$$

**Ex: 1.38**

Equation 1.72

$$C_{jo} = A \sqrt{\left( \frac{\epsilon_s q}{2} \right) \left( \frac{N_A N_D}{N_A + N_D} \right) \left( \frac{1}{V_o} \right)}$$

$$= 10^{-4} \sqrt{\left( \frac{1.04 \times 10^{-12} \times 1.6 \times 10^{-19}}{2} \right)}$$

$$= \sqrt{\left( \frac{10^{18} \times 10^{16}}{10^{18} + 10^{16}} \right) \left( \frac{1}{0.814} \right)}$$

$$= 3.2 \text{ pF}$$

Equation 1.71

$$C_j = \frac{C_{jo}}{\sqrt{1 + \frac{V_R}{V_o}}}$$

$$= \frac{3.2 \times 10^{-12}}{\sqrt{1 + \frac{2}{0.814}}}$$

$$= 1.72 \text{ pF}$$

**Ex: 1.39**

$$C_d = \frac{dQ}{dV} = \frac{d}{dV} (\tau_T I)$$

$$= \frac{d}{dV} [\tau_T \times I_s (e^{V/V_T} - 1)]$$

$$= \tau_T I_s \frac{d}{dV} (e^{V/V_T} - 1)$$

$$= \tau_T I_s \frac{1}{V_T} e^{V/V_T}$$

$$= \frac{\tau_T}{V_T} \times I_s e^{V/V_T}$$

$$= \left( \frac{\tau_T}{V_T} \right) I$$

**Ex: 2.1**

The minimum number of terminals required by a single op amp is five: two input terminals, one output terminal, one terminal for positive power supply and one terminal for negative power supply.

The minimum number of terminals required by a quad op amp is 14: each op amp requires two input terminals and one output terminal (accounting for 12 terminals for the four op amps). In addition, the four op amp can all share one terminal for positive power supply and one terminal for negative power supply.

**Ex: 2.2**

Equation are  $v_3 = A(v_2 - v_1)$ ;

$$v_{id} = v_2 - v_1, \quad v_{icm} = \frac{1}{2}(v_1 + v_2)$$

a)

$$v_1 = v_2 - \frac{v_3}{A} = 0 - \frac{2}{10^3} = -0.002 \text{ V} = -2 \text{ mV}$$

$$v_{id} = v_2 - v_1 = 0 - (-0.002) = +0.002 \text{ V} \\ = 2 \text{ mV}$$

$$v_{icm} = \frac{1}{2}(-2 \text{ mV} + 0) = -1 \text{ mV}$$

b)  $-10 = 10^3(5 - v_1) \Rightarrow v_1 = 5.01 \text{ V}$

$$v_{id} = v_2 - v_1 = 5 - 5.01 = 0.01 \text{ V} = 10 \text{ mV}$$

$$v_{icm} = \frac{1}{2}(v_1 + v_2) = \frac{1}{2}(5.01 + 5) = 5.005 \text{ V}$$

$$\approx 5 \text{ V}$$

c)

$$v_3 = A(v_2 - v_1) = 10^3(0.998 - 1.002) = -4 \text{ V}$$

$$v_{id} = v_2 - v_1 = 0.998 - 1.002 = -4 \text{ mV}$$

$$v_{icm} = \frac{1}{2}(v_1 + v_2) = \frac{1}{2}(1.002 + 0.998) = 1 \text{ V}$$

d)

$$-3.6 = 10^3[v_2 - (-3.6)] = 10^3(v_2 + 3.6)$$

$$\Rightarrow \sqrt{2} = -3.6036 \text{ V}$$

$$v_{id} = v_2 - v_1 = -3.6036 - (-3.6)$$

$$= -0.0036 \text{ V} = -3.6 \text{ mV}$$

$$v_{icm} = \frac{1}{2}(v_1 + v_2) = \frac{1}{2}[-3.6 + (-3.6)]$$

$$= -3.6 \text{ V}$$

**Ex: 2.3**

From Figure E2.3 we have:  $V_3 = \mu V_d$  and

$$V_d = (G_m V_2 - G_m V_1)R = G_m R(V_2 - V_1)$$

Therefore:

$$V_3 = \mu G_m R(V_2 - V_1)$$

That is the open-loop gain of the op amp

$$is A = \mu G_m R. For G_m = 10 \text{ mA/V} and$$

$$\mu = 100 we have:$$

$$A = 100 \times 10 \times 10 = 10^4 \text{ V/V Or equivalently } 80 \text{ dB}$$

**Ex: 2.4**

The gain and input resistance of the inverting amplifier circuit shown in Figure 2.5 are

$$-\frac{R_2}{R_1} \text{ and } R_1 \text{ respectively. Therefore, we have:}$$


$$R_1 = 100 \text{ k}\Omega \text{ and}$$

$$-\frac{R_2}{R_1} = -10 \Rightarrow R_2 = 10 R_1$$

Thus:

$$R_2 = 10 \times 100 \text{ k}\Omega = 1 \text{ M}\Omega$$

**Ex: 2.5**

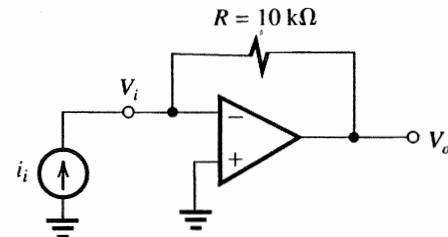

$$1.1$$

From Table we have:

$$R_m = \left. \frac{V_o}{i_i} \right|_{i_o = 0}, \text{ i.e., output is open circuit}$$

The negative input terminal of the op amp, i.e.,  $V_i$  is a virtual ground, thus  $V_i = 0$


$$V_o = V_i - Ri_i = 0 - Ri_i = -Ri_i$$

$$R_m = \left. \frac{V_o}{i_i} \right|_{i_o = 0} = -\frac{Ri_i}{i_i} = -R \Rightarrow R_m = -R \\ = -10 \text{ k}\Omega$$


$$R_i = \frac{V_i}{V_o} \text{ and } V_i \text{ is a virtual ground } (V_i = 0),$$

$$\text{thus } R_i = \frac{0}{i_i} = 0 \Rightarrow R_i = 0 \text{ }\Omega$$

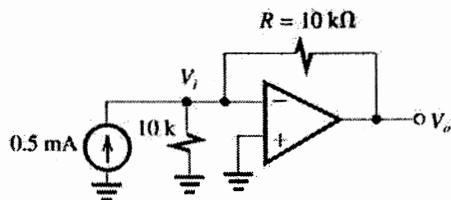Since we are assuming that the op amp in this transresistance amplifier is ideal, the op amp has zero output resistance and therefore the output resistance of this transresistance amplifier is also zero. That is  $R_o = 0 \text{ }\Omega$ .




Ex: 2.7

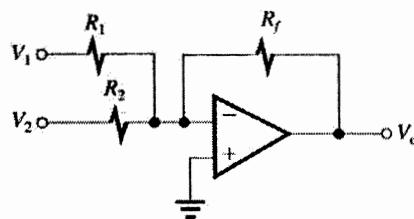

Connecting the signal source shown in Figure E2.5 to the input of this amplifier we have:  
 $V_i$  is a virtual ground that is  $V_i = 0$ , thus the current flowing through the  $10\text{ k}\Omega$  resistor connected between  $V_i$  and ground is zero. Therefore  
 $V_o = V_i - R \times 0.5\text{ mA} = 0 - 10\text{ k}\Omega \times 0.5\text{ mA}$   
 $= -5\text{ V}$

Ex: 2.6

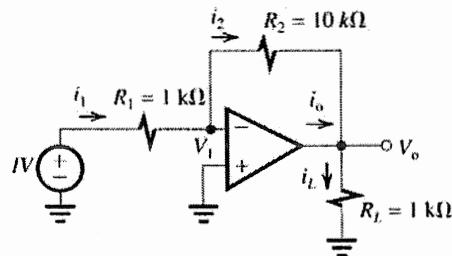

$V_i$  is a virtual ground, thus  $V_i = 0\text{ V}$

$$i_1 = \frac{1\text{ V} - V_i}{R_1} = \frac{1 - 0}{1\text{ k}\Omega} = 1\text{ mA}$$

Assuming an ideal op amp, the current flowing into the negative input terminal of the op amp is zero. Therefore,  $i_2 = i_1 \Rightarrow i_2 = 1\text{ mA}$

$$V_o = V_i - i_2 R_2 = 0 - 1\text{ mA} \times 10\text{ k}\Omega$$
 $= -10\text{ V}$

$$i_L = \frac{V_o}{R_L} = \frac{-10\text{ V}}{1\text{ k}\Omega} = -10\text{ mA}$$

$$i_o = i_L - i_2 = -10\text{ mA} - 1\text{ mA} = -11\text{ mA}$$

$$\text{Voltage gain} = \frac{V_o}{V_i} = \frac{-10\text{ V}}{1\text{ V}} = -10\text{ V/V}$$

or 20 dB

$$\text{Current gain} = \frac{i_L}{i_1} = \frac{-10\text{ mA}}{1\text{ mA}} = -10\text{ A/A}$$

or 20 dB

$$\text{Power gain} = \frac{P_L}{P_i} = \frac{-10(-10\text{ mA})}{1\text{ V} \times 1\text{ mA}} = 100\text{ W/W}$$

or 20 dB

Note that power gain in dB is  $10 \log_{10} \left| \frac{P_o}{P_i} \right|$ .

For the circuit shown above we have:

$$V_o = \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right)$$

Since it is required that  $V_o = -(V_1 + 5V_2)$ .

We want to have:

$$\frac{R_f}{R_1} = 1 \text{ and } \frac{R_f}{R_2} = 5$$

It is also desired that for a maximum output voltage of 10 V the current in the feedback resistor does not exceed 1 mA.


Therefore

$$\frac{10\text{ V}}{R_f} \leq 1\text{ mA} \Rightarrow R_f \geq \frac{10\text{ V}}{1\text{ mA}} \Rightarrow R_f \geq 10\text{ k}\Omega$$

Let us choose  $R_f$  to be  $10\text{ k}\Omega$ , then

$$R_1 = R_f = 10\text{ k}\Omega \text{ and } R_2 = \frac{R_f}{5} = 2\text{ k}\Omega$$

Ex: 2.8

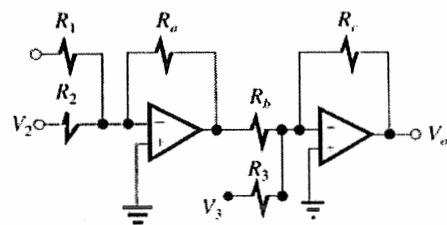

$$V_o = \left( \frac{R_a}{R_1} \right) \left( \frac{R_c}{R_b} \right) V_1 + \left( \frac{R_a}{R_2} \right) \left( \frac{R_c}{R_b} \right) V_2 - \left( \frac{R_c}{R_3} \right) V_3$$

We want to design the circuit such that

$$V_o = 2V_1 + V_2 - 4V_3$$

Thus we need to have

$$\left( \frac{R_a}{R_1} \right) \left( \frac{R_c}{R_b} \right) = 2, \quad \left( \frac{R_a}{R_2} \right) \left( \frac{R_c}{R_b} \right) = 1 \text{ and } \frac{R_c}{R_3} = 4$$

From the above three equations, we have to find six unknown resistors, therefore, we can arbitrarily choose three of these resistors. Let us choose:

Then we have


$$R_3 = \frac{R_C}{4} = \frac{10}{4} = 2.5 \text{ k}\Omega$$

$$\left(\frac{R_a}{R_1}\right)\left(\frac{R_c}{R_b}\right) = 2, \Rightarrow \frac{10}{R_1} \times \frac{10}{10} = 2 \Rightarrow R_1 = 5 \text{ k}\Omega$$

$$\left(\frac{R_a}{R_2}\right)\left(\frac{R_c}{R_b}\right) = 1 \Rightarrow \frac{10}{R_2} \times \frac{10}{10} = 1 \Rightarrow R_2 = 10 \text{ k}\Omega$$
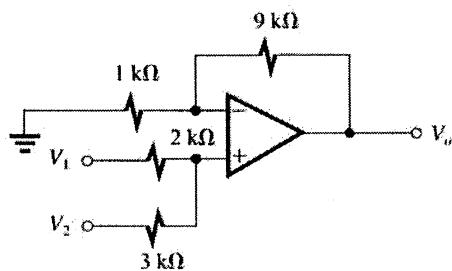
#### Ex: 2.9

Using the super position principle, to find the contribution of  $v_1$  to the output voltage  $v_o$ , we set  $v_2 = 0$



The  $V_+$  (the voltage at the positive input of the op amp is:  $V_+ = \frac{3}{2+3}V_1 = 0.6V_1$

Thus

$$V_o = \left(1 + \frac{9 \text{ k}\Omega}{1 \text{ k}\Omega}\right)V_+ = 10 \times 0.6V_1 = 6V_1$$

To find the contribution of  $V_2$  to the output voltage  $V_o$  we set  $V_1 = 0$ .

$$\text{Then } V_+ = \frac{2}{2+3}V_2 = 0.4V_2$$


Hence

$$V_o = \left(1 + \frac{9 \text{ k}\Omega}{1 \text{ k}\Omega}\right)V_+ = 10 \times 0.4V_2 = 4V_2$$

Combining the contributions of  $v_1$  and  $v_2$

$$\text{To } V_o \text{ we have } V_o = 6V_1 + 4V_2$$

#### Ex: 2.10

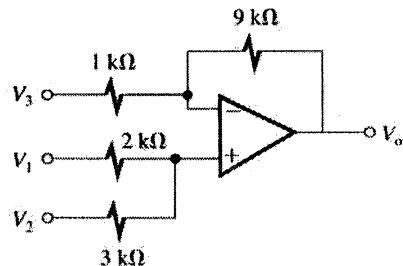

Using the super position principle, to find the contribution of  $V_1$  to  $V_o$  we set  $V_2 = V_3 = 0$ . Then

we have (refer to the solution of exercise 2.9):

$$V_o = 6V_1$$

To find the contribution of  $V_2$  to  $V_o$  we set

$$V_1 = V_3 = 0, \text{ then: } V_o = 4V_2$$


To find the contribution of  $V_3$  to  $V_o$  we set

$$V_1 = V_2 = 0, \text{ then}$$

$$V_o = -\frac{9 \text{ k}\Omega}{1 \text{ k}\Omega}V_3 = -9V_3$$

Combining the contributions of  $V_1, V_2$  and  $V_3$  to  $V_o$  we have:  $V_o = 6V_1 + 4V_2 - 9V_3$

#### Ex: 2.11

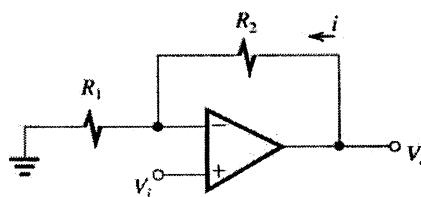

$$\frac{V_o}{V_i} = 1 + \frac{R_2}{R_1} = 2 \Rightarrow \frac{R_2}{R_1} = 1 \Rightarrow R_1 = R_2$$

If  $V_o = 10 \text{ V}$  then it is desired that

$$i = 10 \mu\text{A}$$

Thus,


$$i = \frac{10 \text{ V}}{R_1 + R_2} = 10 \mu\text{A} \Rightarrow R_1 + R_2 = \frac{10 \text{ V}}{10 \mu\text{A}}$$

$R_1 + R_2 = 1 \text{ M}\Omega$  and

$$R_1 = R_2 \Rightarrow R_1 = R_2 = 0.5 \text{ M}\Omega$$

#### Ex: 2.12

a)

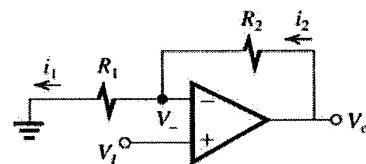

$$V_o = A(V_i - V_-) \Rightarrow V_- = V_i - \frac{V_o}{A}$$

$$i_2 = i_1 \Rightarrow \frac{V_o - V_-}{R_2} = \frac{V_-}{R_1} \Rightarrow \frac{V_o}{R_2} = \left(\frac{1}{R_2} + \frac{1}{R_1}\right)V_-$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right)V_- = \left(1 + \frac{R_2}{R_1}\right)\left(V_i - \frac{V_o}{A}\right) \Rightarrow$$

$$V_o + \frac{1 + R_2/R_1}{A}V_o = (1 + R_2/R_1)V_i$$

$$\frac{V_o}{V_i} = \frac{1 + R_2/R_1}{1 + \frac{1 + R_2/R_1}{A}} \Rightarrow G = \frac{1 + R_2/R_1}{1 + \frac{1 + R_2/R_1}{A}}$$

(b) For  $R_1 = 1 \text{ k}\Omega$  and  $R_2 = 9 \text{ k}\Omega$  the ideal value for the closed-loop gain is  $1 + \frac{9}{1}$ , that is

$$10. \text{ The actual closed-loop gain is } G = \frac{10}{1 + \frac{10}{A}}$$

If  $A = 10^3$  then  $G = 9.901$  and

$$\epsilon = \frac{G - 10}{10} \times 100 = -0.99\% \approx -1\%$$

For  $V_I = 1 \text{ V}$ ,  $V_O = G \times V_I = 9.901 \text{ V}$  and

$$V_O = A(V_+ - V_-) \Rightarrow V_+ - V_- = \frac{V_O}{A} = \frac{9.901}{1000} \approx 9.9 \text{ mV}$$

If  $A = 10^4$  then  $G = 9.99$  and  $\epsilon = -0.1\%$

For  $V_I = 1 \text{ V}$ ,  $V_O = G \times V_I = 9.99 \text{ V}$ , therefore,

$$V_+ - V_- = \frac{V_O}{A} = \frac{9.99}{10^4} = 0.999 \text{ mV} \pm 1 \text{ mV}$$

If  $A = 10^5$  then  $G = 9.999$  and

$$\epsilon = -0.01\%$$

For  $V_I = 1 \text{ V}$ ,  $V_O = G \times V_I = 9.999$  thus,

$$V_+ - V_- = \frac{V_O}{A} = \frac{9.999}{10^5} = 0.09999 \text{ mV}$$


$\approx 0.1 \text{ mV}$

### Ex: 2.13

$$i_I = OA, V_I = V_T = 1 \text{ V},$$

$$i_1 = \frac{V_I}{1 \text{ k}\Omega} = \frac{1 \text{ V}}{1 \text{ k}\Omega} = 1 \text{ mA}$$

$$i_2 = i_1 = 1 \text{ mA},$$

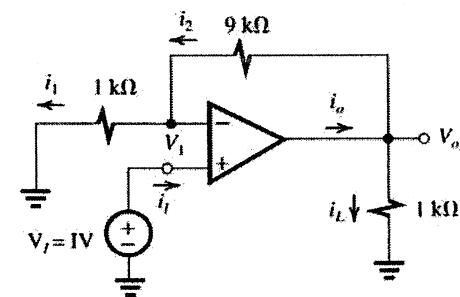

$$V_O = V_I + i_2 \times 9 \text{ k}\Omega = 1 + 1 \times 9 = 10 \text{ V}$$

$$i_L = \frac{V_O}{1 \text{ k}\Omega} = \frac{10 \text{ V}}{1 \text{ k}\Omega} = 10 \text{ mA},$$

$$i_O = i_L + i_2 = 11 \text{ mA}$$

$$\frac{V_O}{V_I} = \frac{10 \text{ V}}{1 \text{ V}} = 10 \frac{\text{V}}{\text{V}} \text{ or } 20 \text{ dB}$$

$$\frac{i_L}{i_s} = \frac{10 \text{ mA}}{0} = \infty$$

$$\frac{P_L}{P_I} = \frac{V_O \times i_L}{V_I \times I_s} = \frac{10 \times 10}{1 \times 10} = \infty$$


### Ex: 2.14

(a) load voltage

$$= \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 1 \text{ M}\Omega} \times 1 \text{ V} \approx 1 \text{ mV}$$

(b) load voltage = 1V

### Ex: 2.15

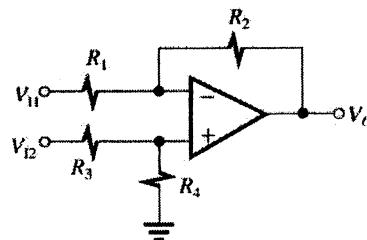

$$(a) R_1 = R_3 = 2 \text{ k}\Omega, R_2 = R_4 = 200 \text{ k}\Omega$$

Since  $R_4/R_3 = R_2/R_1$  we have:

$$A_d = \frac{V_O}{V_{I2} - V_{I1}} = \frac{R_2}{R_1} = \frac{200}{2} = 100 \text{ V/V}$$

$$(b) R_{id} = 2R_1 = 2 \times 2 \text{ k}\Omega = 4 \text{ k}\Omega$$

Since we are assuming the op amp is ideal

$$R_o = 0 \text{ }\Omega$$

$$(c) A_{cm} = \frac{V_O}{V_{ICM}} = \left( \frac{R_4}{R_4 + R_3} \right) \left( 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right)$$

$$= \left( \frac{1}{1 + \frac{R_3}{R_4}} \right) \left( 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right)$$

$$= \frac{\frac{R_4}{R_3} - \frac{R_2}{R_1}}{\frac{R_4}{R_3} + 1}$$

The worst case common-mode gain  $A_{cm}$  happens when  $|A_{cm}|$  has its maximum value.

If the resistors have 1% tolerance, we

$$\text{have } \frac{R_{3nom}(1 - 0.01)}{R_{3nom}(1 + 0.01)} \leq \frac{R_4}{R_3} \leq \frac{R_{4nom}(1 + 0.01)}{R_{3nom}(1 - 0.01)}$$

where  $R_{3nom}$  and  $R_{4nom}$  are nominal values for  $R_3$  and  $R_4$  respectively. We have :

$$R_{3nom} = 2 \text{ k}\Omega \text{ and } R_{4nom} = 200 \text{ k}\Omega, \text{ thus,}$$

$$\frac{200 \times 0.99}{2 \times 1.01} \leq \frac{R_4}{R_3} \leq \frac{200 \times 1.01}{2 \times 0.99}$$

$$98.02 \leq \frac{R_4}{R_3} \leq 102.02$$

Similarly, we can show that

$$98.02 \leq \frac{R_2}{R_1} \leq 102.02$$

$$\text{Hence, } -102.02 \leq -\frac{R_2}{R_1} \leq -98.02$$

Therefore,

$$-4 \leq \frac{R_4}{R_3} - \frac{R_2}{R_1} \leq 4 \Rightarrow \left| \frac{R_4}{R_3} - \frac{R_2}{R_1} \right| \leq 4$$

In the worst case

$$\frac{\left| \frac{R_4}{R_3} - \frac{R_2}{R_1} \right|}{1 + \frac{R_4}{R_3}} \leq \frac{4}{1 + 98.02} \Rightarrow |A_{cm}| \leq 0.04$$

Note that the worst case  $A_{cm}$  happens when

$$\frac{R_4}{R_3} = 98.02 \text{ and } \frac{R_2}{R_1} = 102.02$$

The differential gain  $A_d$  of the amplifier

$$\text{is } A_d = \frac{R_2}{R_1}, \text{ therefore, the corresponding value of}$$

CMRR for the worst case  $A_{cm}$  is :

$$\text{CMRR} = 20 \log \frac{|A_d|}{|A_{cm}|} = 20 \log \frac{102.02}{0.04} \Rightarrow$$

$$\text{CMRR} = 20 \log(2550.5) \approx 68 \text{ dB}$$

### Ex: 2.16

We choose  $R_3 = R_1$  and  $R_4 = R_2$ . Then for the circuit to behave as a difference amplifier with a gain of 10 and an input resistance of  $20 \text{ k}\Omega$  we require

$$A_d = \frac{R_2}{R_1} = 10 \text{ and}$$

$$R_{id} = 2R_1 = 20 \text{ k}\Omega \Rightarrow R_1 = 10 \text{ k}\Omega \text{ and}$$

$$R_2 = A_d R_1 = 10 \times 10 \text{ k}\Omega = 100 \text{ k}\Omega$$

Therefore,  $R_1 = R_3 = 10 \text{ k}\Omega$  and

$$R_2 = R_4 = 100 \text{ k}\Omega$$

### Ex: 2.17

Given  $V_{icm} = +5 \text{ V}$

$V_{id} = 10 \sin \omega t \text{ mV}$

$$2R_1 = 1 \text{ k}\Omega, R_2 = 0.5 \text{ M}\Omega$$

$$R_3 = R_4 = 10 \text{ k}\Omega$$

$$v_{o-} = v_{i-} - \frac{1}{2}v_{id} = 5 - \frac{1}{2} \times 0.01 \sin \omega t \\ = 5 - 0.005 \sin \omega t \text{ V}$$

$$v_{i2} = v_{icm} + \frac{1}{2}v_{id}$$

$$= 5 + 0.005 \sin \omega t \text{ V}$$

$$v_{-(\text{Op Amp A}_1)} = V_{i1} = 5 - 0.005 \sin \omega t \text{ V}$$

$$v_{-(\text{Op Amp A}_2)} = V_{i2} = 5 + 0.005 \sin \omega t \text{ V}$$

$$v_{id} = v_{i2} - v_{i1} = 0.01 \sin \omega t$$

$v_{o1}$  - The to voltage at the output of op amp A.

$$v_{o1} = V_{i1} - R_2 \times \frac{V_{id}}{2R_1} \\ = 5 - 0.005 \sin \omega t - 500 \text{ k} \times \frac{0.01 \sin \omega t}{1 \text{ k}\Omega} \\ = (5 - 5.005 \sin \omega t) \text{ V}$$

$v_{o2}$  - The voltage at the output of op amp A2

$$V_{o2} = v_{i2} + R_2 \times \frac{v_{id}}{2R_1} \\ = (5 + 5.005 \sin \omega t) \text{ V}$$


$$v_{+(\text{Op Amp A}_3)} = v_{o2} \times \frac{R_4}{R_3 + R_4} = v_{o2} \frac{10}{10 + 10} \\ \because R_3 = R_4 = 10 \text{ k}\Omega \\ = \frac{1}{2}v_{o2} = \frac{1}{2}(5 + 5.005 \sin \omega t) \\ = (2.5 + 2.5025 \sin \omega t) \text{ V}$$

$$v_{-(\text{Op Amp A}_3)} = V_{+}(\text{Op Amp A}_3) \\ = (2.5 + 2.5025 \sin \omega t) \text{ V}$$


$$v_o = \frac{R_4}{R_3} \left( 1 + \frac{R_2}{R_1} \right) v_{id}$$

$$\frac{10 \text{ k}}{10 \text{ k}} \left( 1 + \frac{0.5 \text{ M}\Omega}{0.5 \text{ M}\Omega} \right) \times 0.01 \sin \omega t \\ = 1(1 + 1000) \times 0.01 \sin \omega t \\ = 10.01 \sin \omega t \text{ V}$$


### Ex: 2.18

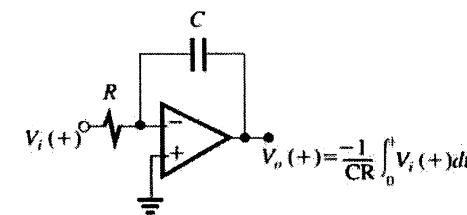

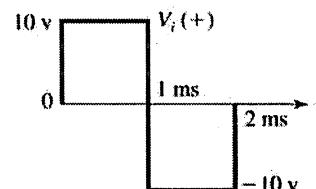The waveforms for one period of the input and the output signals are shown below:



**Ex: 2.20**

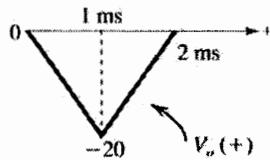


We have

$$\begin{aligned} -20 &= \frac{-1}{CR} \int_0^{1 \text{ ms}} 10 \, dt \\ \Rightarrow -20 &= \frac{-1}{CR} \times 10 \times 1 \text{ ms} \end{aligned}$$

$$CR = \frac{10}{20} \times 1 \text{ ms} \times 0.5 \text{ ms}$$

**Ex: 2.19**

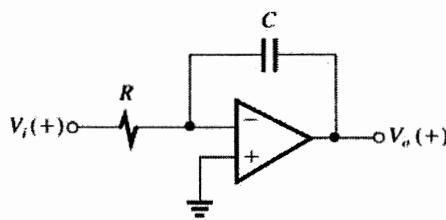

The input resistance of this inverting integrator is  $R_1$ , therefore,  $R = 10 \text{ k}\Omega$

Since the desired integration time constant is  $10^{-3} \text{ s}$ , we have:  $CR = 10^{-3} \text{ s} \Rightarrow$

$$C = \frac{10^{-3} \text{ s}}{10 \text{ k}\Omega} = 0.1 \mu\text{F}$$

From equation (2.50) the transfer function of this integrator is:

$$\frac{V_o(jw)}{V_i(jw)} = -\frac{1}{jwCR}$$

For  $w = 10 \text{ rad/s}$  the integrator transfer function has magnitude

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{10 \times 10^{-3}} = 100 \text{ V/V} \text{ and phase}$$

$$\phi = 90^\circ$$


For  $w = 1 \text{ rad/s}$  the integrator transfer function has magnitude

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{10 \times 10^{-3}} = 1000 \text{ V/V} \text{ and phase}$$

$$\phi = 90^\circ$$

Using equation (2.53) the frequency at which the integrator gain magnitude is unity is
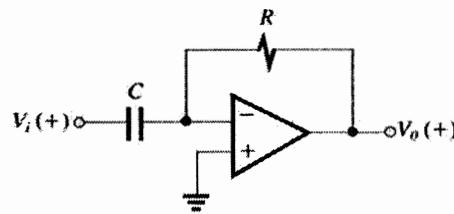
$$w_{\text{int}} = \frac{1}{CR} = \frac{1}{10^{-3}} = 1000 \text{ rad/s}$$



$C = 0.01 \mu\text{F}$  is the input capacitance of this differentiator. We want  $CR = 10^{-2} \text{ s}$  (the time constant of the differentiator), thus,

$$R = \frac{10^{-2}}{0.01 \mu\text{F}} = 1 \text{ M}\Omega$$

From equation (2.57), we know that the transfer function of the differentiator is of the form

$$\frac{V_o(jw)}{V_i(jw)} = -jwCR$$

Thus, for  $w = 10 \text{ rad/s}$  the differentiator transfer function has magnitude

$$\left| \frac{V_o}{V_i} \right| = 10 \times 10^{-2} = 0.1 \text{ V/V} \text{ and phase}$$


$$\phi = -90^\circ$$

For  $w = 10^3 \text{ rad/s}$  the differentiator transfer function has magnitude

$$\left| \frac{V_o}{V_i} \right| = 10^3 \times 10^{-2} = 10 \text{ V/V} \text{ and phase}$$

$$\phi = -90^\circ$$

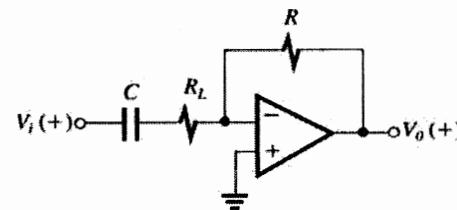
If we add a resistor in series with the capacitor to limit the high frequency gain of the differentiator to 100, the circuit would be:



At high frequencies the capacitor C acts like a short circuit. Therefore, the high-frequency gain of this circuit is:  $\frac{R}{R_L}$ . To limit the magnitude of this high-frequency gain to 100, we should have:

$$\frac{R}{R_L} = 100 \Rightarrow R_L = \frac{R}{100} = \frac{1 \text{ M}\Omega}{100} = 10 \text{ k}\Omega$$

Ex: 2.21

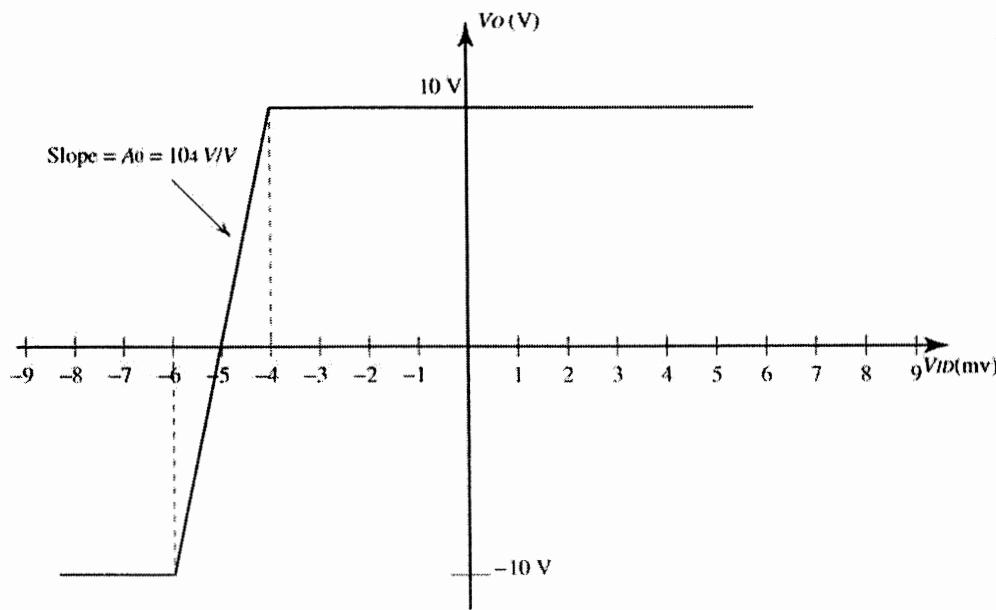

$$V_O = V_3$$


$$V_{ID} = V_2 - V_1$$

$$V_{ID} = V_+ - V_{OS} - V_-$$

when  $V_+ = V_- = 0$  then

$V_{ID} = 0 - 5 \text{ mV} = -5 \text{ mV}$ . This input offset voltage causes an offset in the voltage transfer characteristic. Rather than passing through the origin, it is now shifted to the left by  $V_{OS}$

Ex: 2.23

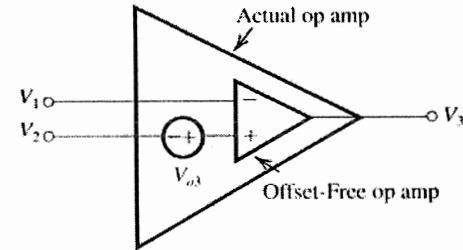

Ex: 2.22

From equation (2.41) we have:

$$f_M = \frac{SR}{2\pi V_{O \max}} = 15.915 \text{ kHz} \geq 15.9 \text{ kHz}$$

Using equation (2.42), for an input sinusoid with frequency  $f = 5 f_M$ , the maximum possible amplitude that can be accommodated at the output without incurring SR distortion is:

$$V_O = V_{O \max} \left( \frac{f_M}{5 f_M} \right) = 10 \times \frac{1}{5} = 2 \text{ V(peak)}$$

$$V_O \approx V_3$$


$$V_{ID} = V_2 - V_1$$

$$V_{ID} = V_+ - V_{OS} - V_-$$

In order to have zero differential input for the offset-free op amp (i.e.,  $V_+ - V_- = 0$ ) we need

$$V_{ID} = V_+ - V_- - V_{OS} = 0 - 5 \text{ mV} = -5 \text{ mV}$$

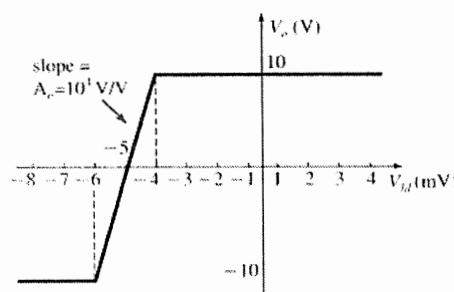Thus, the transfer characteristic  $V_O$  versus  $V_{ID}$  is:



**Ex: 2.24**

From equation(2.44) we have:

$$V_o = I_{B1}R_2 \approx I_B R_2$$

$$= 100 \text{ nA} \times 1 \text{ M}\Omega = 0.1 \text{ V}$$

From equation (2.46) the value of resistor  $R_3$

(placed in series with positive input to minimize the output offset voltage) is:

$$R_3 = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \text{ k}\Omega \times 1 \text{ M}\Omega}{10 \text{ k}\Omega + 1 \text{ M}\Omega} = 9.9 \text{ k}\Omega$$

$$R_3 = 9.9 \text{ k}\Omega \approx 10 \text{ k}\Omega$$

With this value of  $R_3$  the new value of the output dc voltage (using equation (2.47)) is:


$$V_o = I_{os}R_2 = 10 \text{ nA} \times 10 \text{ k}\Omega \approx 0.01 \text{ V}$$

**Ex: 2.25**

Using equation (2.54) we have:

$$V_o = V_{os} + \frac{V_{os}}{CR}t \Rightarrow 12 = 2 \text{ mV} + \frac{2 \text{ mV}}{1 \text{ ms}}t$$
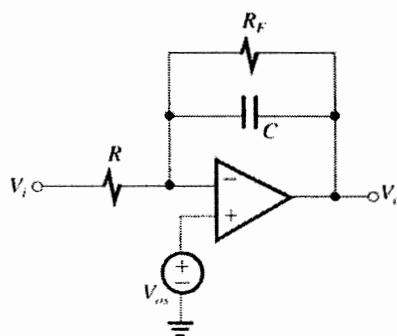
$$\Rightarrow t = \frac{12 \text{ V} - 2 \text{ mV}}{2 \text{ mV}} \times 1 \text{ ms} \approx 6 \text{ ms} \Rightarrow t = 6 \text{ D}$$



With the feedback resistor  $R_f$  to have at least

+ 10 V of output signal swing available, we have to make sure that the output voltage due to  $V_{os}$  has a magnitude of at most 2 V. From equation (2.43), we know that the output dc voltage due to  $V_{os}$  is

$$V_o = V_{os} \left( 1 + \frac{R_f}{R} \right) \Rightarrow 2 \text{ V} = 2 \text{ mV} \left( 1 + \frac{R_f}{10 \text{ k}\Omega} \right)$$

$$1 + \frac{R_f}{10 \text{ k}\Omega} \approx 1000 \Rightarrow R_f \approx 10 \text{ M}\Omega$$

The corner frequency of the resulting STC

$$\text{network is } w = \frac{1}{CR_f}$$

We know  $RC = 1 \text{ ms}$  and

$$R = 10 \text{ k}\Omega \Rightarrow C = 0.1 \mu\text{F}$$

$$\text{Thus } w = \frac{1}{0.1 \mu\text{F} \times 10 \text{ M}\Omega} = 1 \text{ rad/s}$$

$$f = \frac{w}{2\pi} = \frac{1}{2\pi} = 0.16 \text{ Hz}$$

**Ex: 2.26**

From equation (2.28) we have:

$$w_t = A_O w_b \Rightarrow f_t = A_O f_b \Rightarrow f_b = \frac{f_t}{A_O}, \text{ and}$$

we know

$$20 \log A_O = 106 \text{ and } f_t = 3 \text{ MHz, therefore } f_b \approx 15 \text{ Hz}$$

By definition the open-loop gain (in dB) at  $f_b$  is:

$$A_O(\text{in dB}) - 3 = 106 - 3 = 103 \text{ dB}$$

To find the open-loop gain at frequency  $f$  we can use equation (2.31) (especially when  $f \gg f_b$  which is the case in this exercise) and write:

$$\text{Open-loop gain at } f \approx 20 \log \left( \frac{f_t}{f} \right)$$

Therefore:

$$\text{Open-loop gain at } 300 \text{ Hz} =$$

$$20 \log \frac{3 \text{ MHz}}{300} = 80 \text{ dB}$$

$$\text{Open-loop gain at } 3 \text{ kHz} =$$

$$20 \log \frac{3 \text{ MHz}}{3 \text{ kHz}} = 60 \text{ dB}$$


$$\text{Open-loop gain at } 12 \text{ kHz} =$$

$$20 \log \frac{3 \text{ MHz}}{12 \text{ kHz}} = 48 \text{ dB}$$


$$\text{Open-loop gain at } 60 \text{ kHz} =$$


$$20 \log \frac{3 \text{ MHz}}{60 \text{ kHz}} = 34 \text{ dB}$$

**Ex: 2.27**

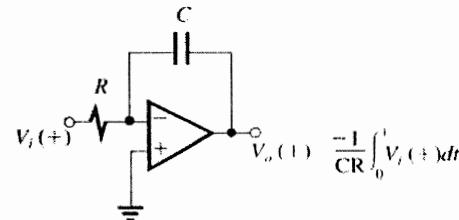

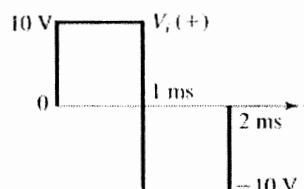The waveforms for one period of the input and the output signals are shown below:



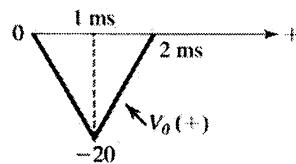

We have

$$\begin{aligned} -20 &= \frac{-1}{CR} \int_0^{1 \text{ ms}} 10 \, dt \\ \Rightarrow -20 &= \frac{-1}{CR} \times 10 \times 1 \text{ ms} \\ CR &= \frac{10}{20} \times 1 \text{ ms} = 0.5 \text{ ms} \end{aligned}$$

### Ex: 2.28

Since dc gain of the op amp is much larger than the de gain of the designed non-inverting amplifier, we can use equation(2.35). Therefore:

$$f_{3\text{db}} = \frac{f_t}{1 + \frac{R_2}{R_1}} \quad \text{and} \quad 1 + \frac{R_2}{R_1} = 100 \quad \text{and}$$

$$f_t = 2 \text{ MHz}$$

$$\text{Hence } f_{3\text{db}} = \frac{2 \text{ MHz}}{100} = 20 \text{ kHz}$$

### Ex: 2.29

For the input voltage step of magnitude V the output waveform will still be given by the exponential waveform of equation(2.40)

If  $w_t V \leq SR$

$$\text{That is } V \leq \frac{SR}{w_t} \Rightarrow V \leq \frac{SR}{2\pi f_t}$$


$V \leq 0.16 \text{ V}$ , thus, the largest possible input voltage step is 0.16 V.

From Appendix F we know that the 10% to 90% rise time of the output waveform of the form of

$$\text{equation (2.40) is } t_r \approx 2.2 \frac{1}{w_t}$$

Thus,  $t_r \approx 0.35 \mu\text{s}$

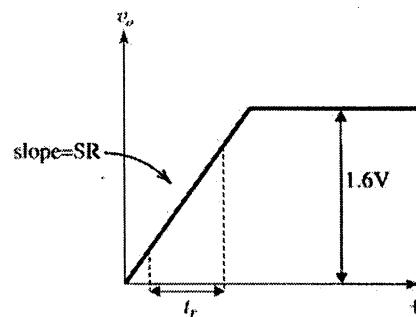If an input step of amplitude 1.6 V (10 times as large compared to the previous case) is applied, the the output is slew-rate limited and is linearly rising with a slope equal to the slew-rate, as shown in the following figure.



$$\begin{aligned} t_r &= \frac{0.9 \times 1.6 - 0.1 \times 1.6}{1 \text{ V}/\mu\text{s}} \\ \Rightarrow t_r &= 1.28 \mu\text{s} \end{aligned}$$

### Ex: 2.30

From equation (2.41) we have:

$$f_M = \frac{SR}{2\pi V_{o \text{ max}}} = 15.915 \text{ kHz} \approx 15.9 \text{ kHz}$$

Using equation (2.42), for an input sinusoid with frequency  $f = 5 f_M$ , the maximum possible amplitude that can be accommodated at the output without incurring SR distortion is:

$$V_o = V_{o \text{ max}} \left( \frac{f_M}{5 f_M} \right) = 10 \times \frac{1}{5} = 2 \text{ V (peak)}$$

**Ex: 3 . 1**

Refer to Fig3 . 3(a). for  $V_I \geq 0$ , the diode conducts and presents a zero voltage drop. Thus  $V_O = V_I$ . For  $V_I < 0$ , the diode is cut-off, zero current flows through R and  $V_O = 0$ . The results is the transfer characteristic in Fig E3 . 1 .

**Ex: 3 . 2**

see Figure3 . 3a and 3 . 3b

During the positive half of the sinusoid, the diode is forward biased, so it conducts resulting in  $v_o = 0$ . During the negative half of the input signal  $v_i$ , the diode is reverse biased. The diode does not conduct resulting in no current flowing in the circuit. So  $v_o = 0$  and  $v_d = v_i - v_o = v_i$ . This results in the waveform shown in Figure E3 . 2

**Ex: 3 . 3**


$$\hat{I}_D = \frac{\hat{v}_i}{R} = \frac{10 \text{ V}}{1 \text{ k}\Omega} = 10 \text{ mA}$$

$$\text{dc component of } v_o = \frac{1}{\pi} \hat{v}_o$$


$$= \frac{1}{\pi} \hat{v}_i = \frac{10}{\pi} \\ = 3.18 \text{ V}$$

**Ex: 3 . 4**


(a)

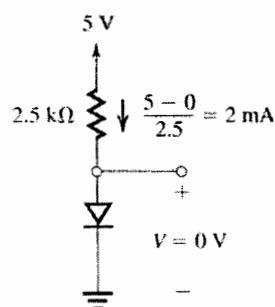


(b)

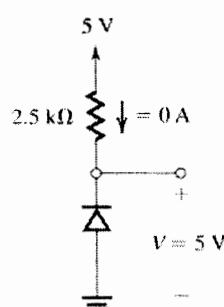


**(c)**

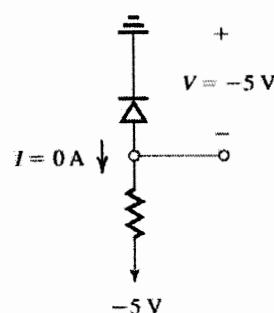


**(d)**

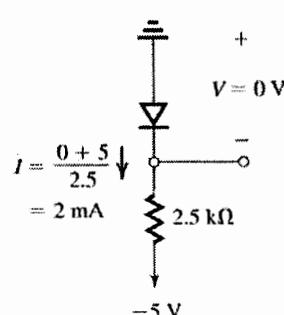

**(e)**

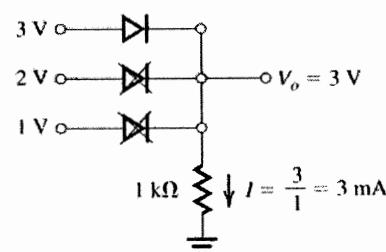

**(f)**

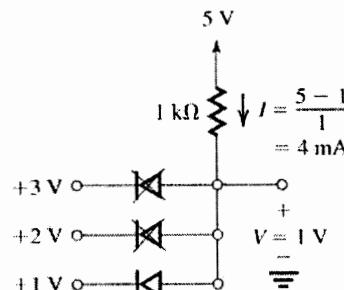

**Ex: 3 . 5**

$$V_{avg} = \frac{10}{\pi}$$

$$50 + R = \frac{\frac{10}{\pi} - 0}{\frac{1}{1 \text{ mA}}} = \frac{10}{\pi} \text{ k}\Omega$$

$$\therefore R = 3.133 \text{ k}\Omega$$

For an output voltage of 2.4 V, the voltage drop across each diode =  $\frac{2.4}{3} = 0.8 \text{ V}$


Now  $I$ , the current through each diode is

$$I = I_s e^{\frac{V}{V_T}} = 6.91 \times 10^{-16} e^{0.8(25 \times 10^{-3})} \\ = 54.6 \text{ mA}$$


$$R = \frac{10 - 2.4}{54.6 \times 10^{-3}} \\ = 139 \Omega$$

Ex: 3.12


(a)

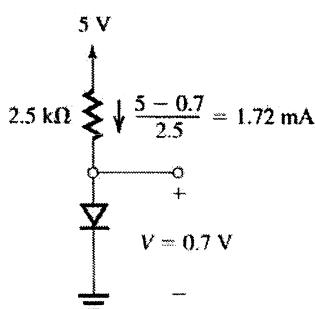


(b)

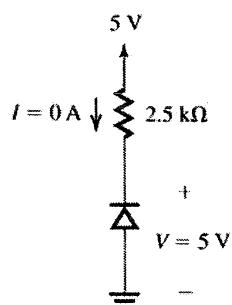


(c)

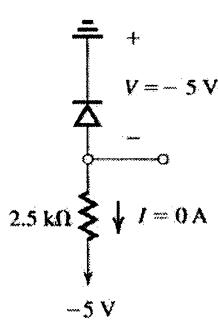


(d)

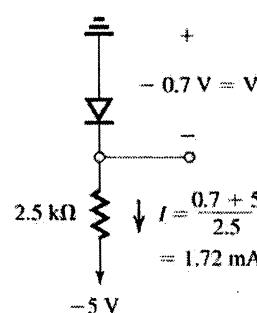

(e)

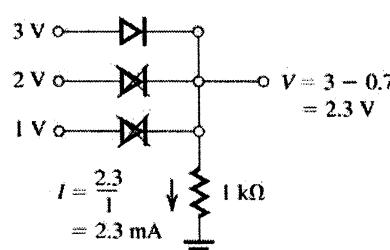

(f)

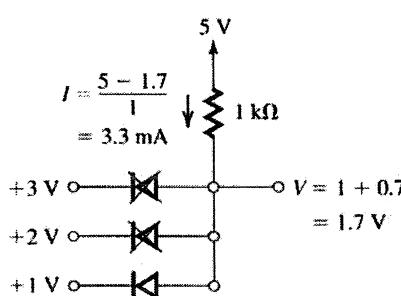

Ex: 3.13

$$r_d = \frac{V_T}{I_D}$$

$$I_D = 0.1 \text{ mA} \quad r_d = \frac{25 \times 10^{-3}}{0.1 \times 10^{-3}} = 250 \Omega$$

$$I_D = 1 \text{ mA} \quad r_d = \frac{25 \times 10^{-3}}{1 \times 10^{-3}} = 25 \Omega$$

$$I_D = 10 \text{ mA} \quad r_d = \frac{25 \times 10^{-3}}{10 \times 10^{-3}} = 2.5 \Omega$$

Ex: 3.14

For small signal model, using equation 3.15

$$i_D = I_D + \frac{I_D}{V_T} \cdot v_d$$

$$\Delta i_D = \frac{I_D}{V_T} \cdot \Delta v_d \quad (1)$$

For exponential model

$$i_D = I_S e^{\frac{V_D}{V_T}}$$

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{V_2 - V_1}{V_T}} = e^{\frac{\Delta V}{V_T}}$$

$$\begin{aligned} \Delta i_D &= i_{D2} - i_{D1} = i_{D1} e^{\frac{\Delta V}{V_T}} - i_{D1} \\ &= i_{D1}(e^{\frac{\Delta V}{V_T}} - 1) \end{aligned} \quad (2)$$


In this problem  $i_{D1} = I_D = 1 \text{ mA}$

Using equations (1) and (2) results and using

$$V_T = 25 \text{ mV}$$

	$\Delta V(\text{mV})$	$\Delta i_D(\text{mA})$ small signal	$\Delta i_D(\text{mA})$ expo. model
a	-10	-0.4	-0.33
b	-5	-0.2	-0.18
c	+5	+0.2	+0.22
d	+10	+0.4	+0.49

Ex: 3.15

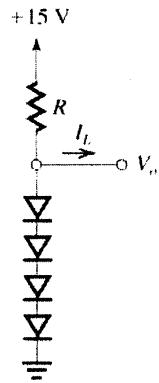

$$\text{a. In this problem } \frac{\Delta V_O}{\Delta I_L} = \frac{20 \text{ mV}}{1 \text{ mA}} = 20 \Omega$$

i. Total small signal resistance of the four diodes  
 $= 20 \Omega$

$$\text{i. For each diode } r_d = \frac{20}{4} = 5 \Omega$$

$$\text{But } r_d = \frac{V_T}{I_D} \Rightarrow 5 = \frac{25 \text{ mV}}{I_D}$$

$$\therefore I_D = 5 \text{ mA}$$

$$\text{and } R = \frac{15 - 3}{5 \text{ mA}} = 2.4 \text{ k}\Omega$$

b. For  $V_O = 3 \text{ V}$ , voltage drop across each

$$\text{diode} = \frac{3}{4} = 0.75 \text{ V}$$

$$i_D = I_S e^{\frac{V_D}{V_T}}$$

$$I_S = \frac{i_D}{e^{\frac{V_D}{V_T}}} = \frac{5}{e^{0.75/25 \times 10^{-3}}} = 4.7 \times 10^{-16} \text{ A}$$

$$\text{c. If } i_D = 5 - i_L = 5 - 1 = 4 \text{ mA}$$

Across each diode the voltage drop is

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

$$= 25 \times 10^{-3} \times \ln\left(\frac{4 \times 10^{-3}}{4.7 \times 10^{-16}}\right)$$

$$= 0.7443 \text{ V}$$

Voltage drop across 4 diodes

$$= 4 \times 0.7443 = 2.977 \text{ V}$$

so change in  $V_O = 3 - 2.977 = 23 \text{ mV}$

Ex: 3.16

For a zener diode

$$V_O = V_{zo} + I_Z r_Z$$


$$10 = V_{zo} + 0.01 \times 50$$

$$V_{zo} = 9.5 \text{ V}$$

For  $I_Z = 5 \text{ mA}$

$$V_O = 9.5 + 0.005 \times 50 = 9.75 \text{ V}$$

Ex: 3.17

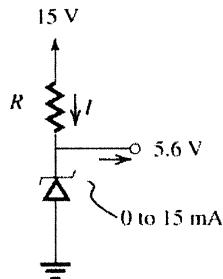

The minimum zener current should be

$$5 \times I_{ZK} = 5 \times 1 = 5 \text{ mA.}$$


Since the load current can be as large as 15 mA, we should select R so that with  $I_L = 15 \text{ mA}$ , a zener current of 5 mA is available. Thus the current should be 20 mA. Leading to

$$R = \frac{15 - 5.6}{20 \text{ mA}} = 470 \Omega$$


Maximum power dissipated in the diode occurs when  $I_L = 0$  is

$$P_{max} = 20 \times 10^{-3} \times 5.6 = 112 \text{ mW}$$

Ex: 3.18

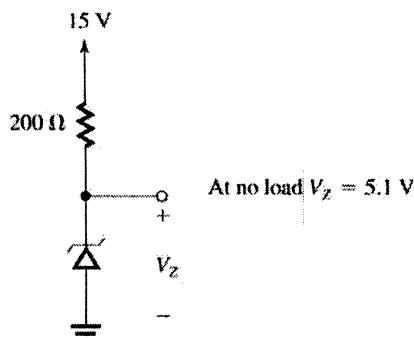


FOR LINE REGULATION

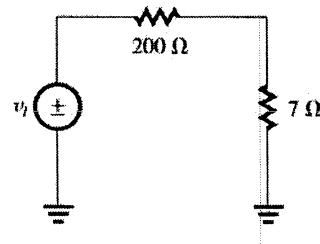


$$\text{Line Regulation} = \frac{v_o}{v_i} = \frac{7}{200 + 7} = 33.8 \text{ mV/V}$$

For Load Regulation:

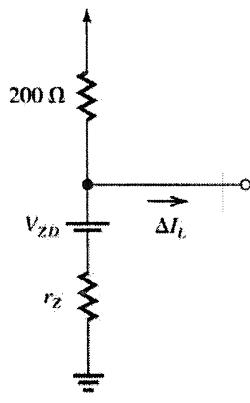

$$\begin{aligned}\frac{\Delta V_o}{\Delta I_i} &= \frac{-\Delta I_L r_Z}{1 \text{ mA}} \\ &= -7 \text{ mV/mA}\end{aligned}$$

Ex: 3.19

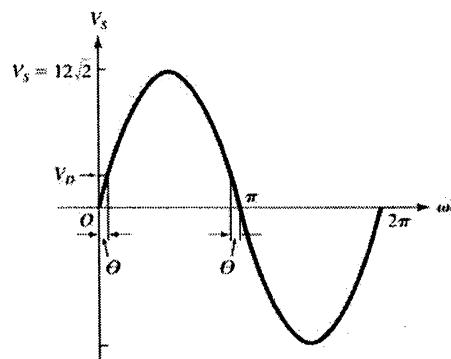

a. The diode starts conduction at

$$v_s = V_D = 0.7 \text{ V}$$

$$v_s = V_s \sin \omega t, \text{ here } V_s = 12\sqrt{2}$$

At  $\omega t = 0$

$$v_s = V_s \sin \theta = V_D = 0.7 \text{ V}$$

$$12\sqrt{2} \sin \theta = 0.7$$

$$\theta = \sin^{-1}\left(\frac{0.7}{12\sqrt{2}}\right) \approx 2.4^\circ$$

\* Conduction starts at  $\theta$  and stops at  $180 - \theta$ .

∴ Total conduction angle =  $180 - 2\theta$

$$= 175.2^\circ$$

$$\text{b. } v_{o,\text{avg}} = \frac{1}{2\pi} \int_0^{\pi} (V_s \sin \phi - V_D) d\phi$$

$$= \frac{1}{2\pi} [-V_s \cos \phi - V_D \phi]_0^{\pi - \theta}$$

$$= \frac{1}{2\pi} [V_s \cos \theta - V_s \cos(\pi - \theta) - V_D(\pi - 2\theta)]$$

But  $\cos \theta \geq 1$ ,  $\cos(\pi - \theta) \leq -1$  and

$$\pi - 2\theta \leq \pi$$

$$v_{o,\text{avg}} = \frac{2V_s}{2\pi} - \frac{V_D}{2}$$

$$= \frac{V_s}{\pi} - \frac{V_D}{2}$$

For  $V_s = 12\sqrt{2}$  and  $V_D = 0.7 \text{ V}$


$$v_{o,\text{avg}} = \frac{12\sqrt{2}}{\pi} - \frac{0.7}{2} = 5.05 \text{ V}$$

c. The peak diode current occurs at the peak diode voltage

$$\therefore \hat{i}_D = \frac{V_S - V_D}{R} = \frac{12\sqrt{2} - 0.7}{100} \\ = 163 \text{ mA}$$

$$\text{PIV} = +V_S = 12\sqrt{2} \\ \approx 17 \text{ V}$$

Ex: 3.20

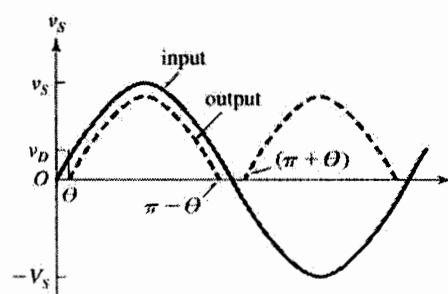

a. As shown in the diagram the output is zero between  $(\pi - \theta)$  to  $(\pi + \theta)$

$$= 2\theta$$

Here  $\theta$  is the angle at which the input signal reaches  $V_D$

$$\therefore V_S \sin \theta = V_D$$

$$\theta = \sin^{-1}\left(\frac{V_D}{V_S}\right)$$

$$2\theta = 2 \sin^{-1}\left(\frac{V_D}{V_S}\right)$$

b. Average value of the output signal is given by

$$V_{O,\text{avg}} = \frac{1}{2\pi} \left[ 2 \times \int_{-\theta}^{\pi - \theta} (V_S \sin \phi - V_D) d\phi \right] \\ = \frac{1}{\pi} [-V_S \cos \phi - V_D \phi]_{\phi=-\theta}^{\pi-\theta} \\ = 2 \frac{V_S}{\pi} - V_D$$

c. Peak current occurs when  $\phi = \frac{\pi}{2}$

Peak Current

$$= \frac{V_S \sin(\pi/2) - V_D}{R} = \frac{V_S - V_D}{R}$$

If  $V_S$  is 12 V(rms)

$$\text{then } V_S = \sqrt{2} \times 12 = 12\sqrt{2}$$

$$\text{Peak current} = \frac{12\sqrt{2} - 0.7}{100} \approx 163 \text{ mA}$$

Non zero output occurs for angle  $= 2(\pi - 2\theta)$

The fraction of the cycle for which  $v_o > 0$  is

$$= \frac{2(\pi - 2\theta)}{2\pi} \times 100 \\ = \frac{2\left[\pi - 2\sin^{-1}\left(\frac{0.7}{12\sqrt{2}}\right)\right]}{2\pi} \times 100$$

$$\approx 97.4\%$$

Average output voltage  $V_o$  is

$$V_o = 2 \frac{V_S}{\pi} - V_D = \frac{2 \times 12\sqrt{2}}{\pi} - 0.7 = 10.1 \text{ V}$$

Peak diode current  $\hat{i}_D$  is


$$\hat{i}_D = \frac{V_S - V_D}{R} = \frac{12\sqrt{2} - 0.7}{100} \\ = 163 \text{ mA}$$

$$\text{PIV} = V_S - V_D + V_S$$

$$= 12\sqrt{2} - 0.7 + 12\sqrt{2}$$

$$= 33.2 \text{ V}$$

Ex: 3.21

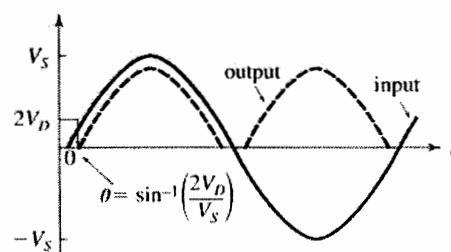

$$V_{O,\text{avg}} = \frac{1}{2\pi} \int (V_S \sin \phi - 2V_D) d\phi \\ = \frac{2}{2\pi} [-V_S \cos \phi - 2V_D \phi]_{\phi=0}^{\pi-2\theta} \\ = \frac{1}{\pi} [2V_S - 2V_D(\pi - 2\theta)]$$

But  $\cos 0 = 1$

$\cos(\pi - 2\theta) \approx -1$

$\pi - 2\theta \approx \pi$

$$\Rightarrow V_{O,\text{avg}} = \frac{2V_S}{\pi} - 2V_D$$

$$= \frac{2 \times 12\sqrt{2}}{\pi} = -1.4 = 9.4 \text{ V}$$

$$(b) \text{ Peak diode current} = \frac{\text{Peak Voltage}}{R}$$



$$= \frac{V_s - 2V_D}{R} = \frac{12\sqrt{2} - 1.4}{100}$$

$$= 156 \text{ mA}$$

$$\text{PIV} = V_s - V_D = 12\sqrt{2} - 0.7 = 16.3 \text{ V}$$

Ex: 3.22

Full wave peak Rectifier:

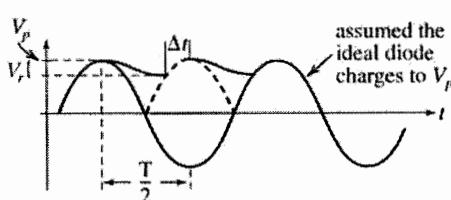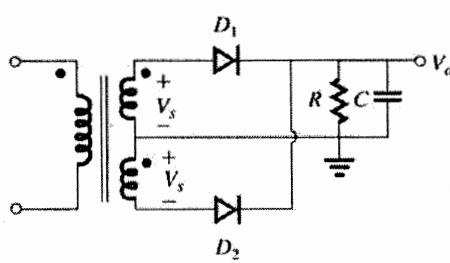

The ripple voltage is the amount of discharge that occurs when the diodes are not conducting. The output voltage is given by:

$$v_o = V_p e^{-t/RC}$$

$$V_p - V_r = V_p e^{-T/2RC} \leftarrow \text{discharge is only half the period.}$$

$$V_r = V_p \left( 1 - e^{-T/2RC} \right)$$

$$e^{-T/2RC} \approx 1 - \frac{T/2}{RC}$$

for  $CR \gg T/2$

$$\approx V_p \left( 1 - 1 + \frac{T/2}{RC} \right)$$

$$= \frac{V_p}{2fRC} \quad (a)$$

To find the average current, note that the charge supplied during conduction is equivalent to the charge lost during discharge.

$$Q_{\text{SUPPLIED}} = Q_{\text{LOST}}$$

$$i_{\text{can}} \Delta t = CV_r \quad \text{SUB (a)}$$

$$(i_{D,\text{av}} - I_L) \Delta t = t \frac{V_p}{2fRt} = \frac{V_p}{2fR}$$

$$= \frac{V_p \pi}{\omega R}$$

$$i_{D,\text{av}} = \frac{V_p \pi}{\omega \Delta t R} + I_L$$

where  $\omega \Delta t$  is the conduction angle.

Note the conduction angle is the same expression as for the half wave rectifier and is given in

EQ3.30

$$\omega \Delta t = \sqrt{\frac{2V_r}{V_p}} \quad (b)$$

Substituting for  $\omega \Delta t$  we get:

$$\Rightarrow i_{D,\text{av}} = \frac{\pi V_p}{\sqrt{\frac{2V_r}{V_p} \cdot R}} + I_L$$

Since the output is approximately held at  $V_p$ ,

$$\frac{V_p}{R} \approx I_L. \text{ Thus:}$$

$$\Rightarrow i_{D,\text{av}} \cong \pi I_L \sqrt{\frac{V_p}{2V_r}} + I_L \\ = I_L \left[ 1 + \pi \sqrt{\frac{V_p}{2V_r}} \right] \text{ Q.E.D}$$

If  $t = 0$  is at the peak, the maximum diode current occurs at the onset of conduction or at  $t = \omega \Delta t$ .

During conduction, the diode current is given by:

$$i_D = i_C + i_L$$

$$i_{D,\text{max}} = C \frac{dV_s}{dt} + i_L$$

$$\begin{aligned} \text{assuming } i_L \text{ is const. } i_L &\approx \frac{V_p}{R} = I_L \\ &= C \frac{d}{dt} (V_p \cos \omega t) + I_L \\ &= -C \sin \omega t \times \omega V_p + I_L \\ &= -C \sin(-\omega \Delta t) \times \omega V_p + I_L \end{aligned}$$

for a small conduction angle

$$\sin(-\omega \Delta t) \approx -\omega \Delta t. \text{ Thus:}$$

$$\Rightarrow i_{D,\text{max}} = C \omega \Delta t \times \omega V_p + I_L$$

Sub (b) to get:

$$i_{D,\text{max}} = C \sqrt{\frac{V_r^2}{V_p}} \omega V_p + I_L$$

SUB  $\omega = 2\pi f$  sub (a) for  $f$


$$= 2\pi \frac{V_p}{2V_r RC}$$

$$\Rightarrow i_{D,\text{max}} = \sqrt{\frac{2V_r}{V_p} \frac{2\pi V_p^2}{2V_r R C}} + I_L$$

$$= \pi \frac{V_p}{V_r} I_L \sqrt{\frac{2V_r}{V_p}} + I_L$$

$$\begin{aligned}
 &= I_L \left[ 1 + \frac{\pi V_p}{V_r} \sqrt{\frac{2V_r}{V_p}} \right] \\
 &= I_L \left[ 1 + \pi \sqrt{\frac{2V_p}{V_r}} \right] \\
 &= I_L \left[ 1 + 2\pi \sqrt{\frac{V_p}{2V_r}} \right] \text{ Q.E.D.}
 \end{aligned}$$

Ex: 3.23

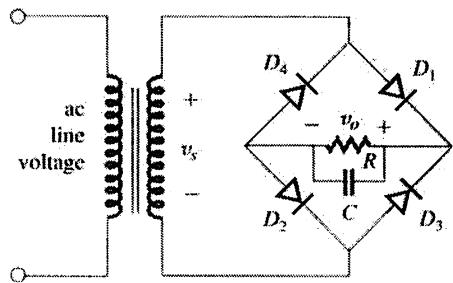

The output voltage,  $v_o$ , can be expressed as

$$v_o = (V_p - 2V_{DO})e^{-tRC}$$

At the end of the discharge interval

$$v_o = (V_p - 2V_{DO} - V_r)$$

The discharge occurs almost over half of the time period  $\approx T/2$

For time constant  $RC \gg \frac{T}{2}$

$$e^{-tRC} \approx 1 - \frac{T}{2} \times \frac{1}{RC}$$

$$\therefore V_p - 2V_{DO} - V_r = (V_p - 2V_{DO}) \left( 1 - \frac{T}{2} \times \frac{1}{RC} \right)$$

$$\Rightarrow V_r = (V_p - 2V_{DO}) \times \frac{T}{2RC}$$

Here  $V_p = 12\sqrt{2}$  and  $V_r = 1$  V

$$V_{DO} = 0.8$$
 V

$$T = \frac{1}{f} = \frac{1}{60} \text{ s}$$

$$T = (12\sqrt{2} - 2 \times 0.8) \times \frac{1}{2 \times 60 \times 100 \times C}$$

$$C = \frac{(12\sqrt{2} - 1.6)}{2 \times 60 \times 100} = 1281 \mu\text{F}$$

Without considering the ripple voltage the dc output voltage

$$= 12\sqrt{2} - 2 \times 0.8 = 15.4$$
 V

If ripple voltage is included the output voltage is

$$= 12\sqrt{2} - 2 \times 0.8 - \frac{V_r}{2} = 14.9$$
 V

Diode current without taking ripple voltage into consideration  $= \frac{12\sqrt{2} - 2 \times 0.8}{100 \Omega} \approx 0.15$  A

The conduction angle  $\omega\Delta t$  can be obtained using equation 4.30

$$\omega\Delta t = \sqrt{\frac{2V_r}{V_p}} = \sqrt{\frac{2 \times 1}{12\sqrt{2} - 2 \times 0.8}} = 0.36$$

rad  $= 20.7^\circ$

The average and peak diode currents can be calculated using equations 3.34 and 3.35

$$i_{D\text{ ave}} = I_L \left( 1 + \pi \sqrt{\frac{V_r}{2V_p}} \right) \text{ Here } I_L = \frac{14.9}{100} \text{ V,}$$

and  $V_p = 12\sqrt{2} - 2 \times 0.8$ ,  $V_r = 1$  V

$$i_{D\text{ base}} = 1.45$$
 A


$$\begin{aligned}
 i_{D\text{ peak}} &= I \left( 1 + 2\pi \sqrt{\frac{V_r}{2V_p}} \right) \\
 &= 2.74 \text{ A}
 \end{aligned}$$

PIV of the diodes

$$= V_S - V_{DO} = 12\sqrt{2} - 0.8 = 16.2$$
 V

To keep the safety margin, select a diode capable of a peak current of 3.5 to 4A and having a PIV rating of 20 V.

Ex: 3.24

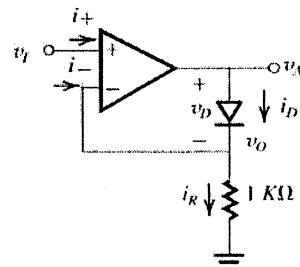

The diode has 0.7 V drop at 1 mA current.

$$i_D = I_S e^{v_D/V_T}$$

$$\frac{i_D}{1 \text{ mA}} = e^{\frac{v_D - 0.7}{V_T}}$$

$$\Rightarrow v_D = V_T \ln\left(\frac{i_D}{1 \text{ mA}}\right) + 0.7 \text{ V}$$

For  $v_I = 10$  mV,  $v_O = v_I = 10$  mV

It is ideal op amp, so  $i_+ = i_- = 0$

$$\therefore i_D = i_R = \frac{10 \text{ mV}}{1 \text{ k}\Omega} = 10 \mu\text{A}$$

$$v_D = 25 \times 10^{-3} \ln\left(\frac{10 \text{ mA}}{1 \text{ mA}}\right) + 0.7 = 0.58 \text{ V}$$

$$V_A = v_D + 10 \text{ mV}$$

$$= 0.58 + 0.01$$

$$= 0.59 \text{ V}$$

For  $v_I = 1$  V

$$v_O = v_I = 1 \text{ V}$$

$$i_D = \frac{v_o}{1 \text{ k}\Omega} = \frac{1}{1 \text{ k}\Omega} = 1 \text{ mA}$$

$$v_D = 0.7 \text{ V}$$

$$V_A = 0.7 \text{ V} + 1 \text{ k}\Omega \times 1 \text{ mA}$$


$$= 1.7 \text{ V}$$

For  $v_I = -1 \text{ V}$ , the diode is cutoff

$$\therefore v_O = 0 \text{ V}$$

$V_A = -12 \text{ V}$  because it is ideal amplifier.

Ex: 3.25

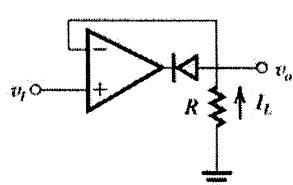


$v_I > 0 \sim$  diode is cutoff

$$v_O = 0 \text{ V}$$

$v_I < 0 \sim$  diode conducts and opamp sinks load current.

$$v_O = v_I$$

Ex: 3.26

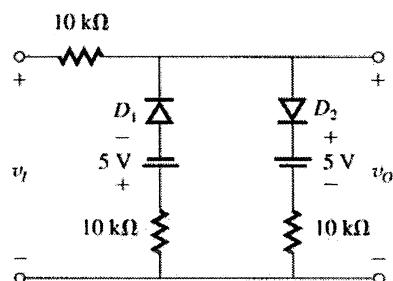

Both diodes are cut-off

for  $-5 \leq v_I \leq +5$

$$\text{and } v_O = v_I$$

For  $v_I \leq -5 \text{ V}$

Diode  $D_1$  conducts and

$$v_O = -5 + \frac{1}{2}(+v_I + 5)$$

$$= \left( -2.5 - \frac{v_I}{2} \right) \text{ V}$$

For  $v_I \geq 5 \text{ V}$


Diode  $D_2$  conducts and

$$v_O = +5 + \frac{1}{2}(v_I - 5)$$

$$= \left( 2.5 + \frac{v_I}{2} \right) \text{ V}$$

Ex: 3.27

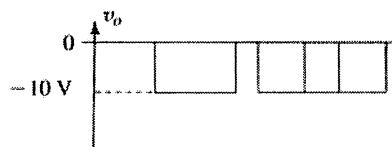Reversing the diode results in the peak output voltage being clamped at 0 V:



Here the dc component of  $v_O = V_O = -5 \text{ V}$

**Ex: 4 . 1**

$$\therefore I_C = I_S e^{v_{BE}/V_T}$$

$$v_{BE2} - v_{BE1} = V_T \ln \left[ \frac{I_C2}{I_C1} \right]$$

$$v_{BE2} = 700 + 25 \ln \left[ \frac{0.1}{1} \right] \\ = 642 \text{ mV}$$

$$v_{BE2} = 700 + 25 \ln \left[ \frac{10}{1} \right] \\ = 758 \text{ mV}$$

$$I_{SB} = \frac{I_{SC}}{\beta} = \frac{10^{-16}}{100} = 10^{-18} \text{ A}$$

$$I_{SE} = I_{SC} \left[ 1 + \frac{1}{\beta} \right] = 10^{-16} \times \frac{101}{100} \\ = 1.01 \times 10^{-16} \text{ A}$$

$$V_{BE} = V_T \ln \left[ \frac{I_C}{I_S} \right] = 25 \ln \left[ \frac{1 \text{ mA}}{10^{-16}} \right] \\ = 25 \times 29.9336 \\ = 743 \text{ mV}$$

**Ex: 4 . 6**

**Ex: 4 . 2**

$$\therefore \alpha = \frac{\beta}{\beta + 1}$$

$$\frac{50}{50+1} < \alpha < \frac{150}{150+1}$$

$$0.98 < \alpha < 0.993$$

**Ex: 4 . 3**

$$I_C = I_E - I_B \\ = 1.460 \text{ mA} - 0.01446 \text{ mA} \\ = 1.446 \text{ mA}$$

$$\alpha = \frac{I_C}{I_E} = \frac{1.446}{1.460} = 0.99$$

$$\beta = \frac{I_C}{I_B} = \frac{1.446}{0.01446} = 100$$

$$I_C = I_S e^{v_{BE}/V_T}$$

$$I_S = \frac{I_C}{e^{v_{BE}/V_T}} = \frac{1.446}{e^{700/25}} \\ = \frac{1.446}{e^{28}} \text{ A} = 10^{-15} \text{ A}$$

**Ex: 4 . 4**

$$\beta = \frac{\alpha}{1-\alpha} \text{ and } I_C = 10 \text{ mA}$$

$$\text{For } \alpha = 0.99 \quad \beta = \frac{0.99}{1-0.99} = 99$$

$$I_B = \frac{I_C}{\beta} = \frac{10}{99} = 0.1 \text{ mA}$$

$$\text{For } \alpha = 0.98 \quad \beta = \frac{0.98}{1-0.98} = 49$$


$$I_B = \frac{I_C}{\beta} = \frac{10}{49} = 0.2 \text{ mA}$$

**Ex: 4 . 5**

Given:

$$I_S = 10^{-16} \text{ A}, \beta = 100, I_C = 1 \text{ mA}$$
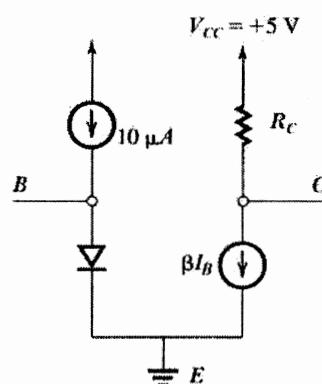
$$I_{SE} = I_{SC} + I_{SB} = I_{SC} \left[ 1 + \frac{1}{\beta} \right]$$



$$v_{BE} = 690 \text{ mV}$$

$$I_C = 1 \text{ mA}$$

For active range  $V_C \geq V_B$

$$R_c(\max) = \frac{V_{CC} - 0.690}{I_C} \\ = \frac{5 - 0.69}{1} \\ = 4.31 \text{ kΩ}$$

**Ex: 4 . 7**

$$I_S = 10^{-15} \text{ A}$$

$$\text{Area}_C = 100 \times \text{Area}_E$$

$$I_{SC} = 100 \times I_S = 10^{-13} \text{ A}$$

**Ex: 4 . 8**

$$i_C = I_S e^{v_{BE}/V_T} - I_{SC} e^{v_{BC}/V_T}$$

for  $i_C = 0$

$$I_S e^{v_{BE}/V_T} = I_{SC} e^{v_{BC}/V_T}$$

$$\frac{I_{SC}}{I_S} = \frac{e^{v_{BE}/V_T}}{e^{v_{BC}/V_T}} \\ = e^{(v_{BE} - v_{BC})/V_T}$$

$$\therefore V_{CE} = V_{BE} - V_{BC} = V_T \ln \left[ \frac{I_C}{I_S} \right]$$

For collector Area = 100 × Emitter Area

$$V_{CE} = 25 \ln \left[ \frac{100}{1} \right] = 115 \text{ mV}$$

Ex: 4.9

$$i_C = I_S e^{\frac{V_{BE}}{V_T}} + I_{SC} e^{\frac{V_{BC}}{V_T}}$$

$$i_B = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T}} + I_{SC} e^{\frac{V_{BC}}{V_T}}$$

$$\beta_{\text{forced}} = \left. \frac{i_C}{i_B} \right|_{\text{sat}} < \beta$$

$$= \beta \frac{I_S e^{\frac{V_{BE}}{V_T}} + I_{SC} e^{\frac{V_{BC}}{V_T}}}{I_S e^{\frac{V_{BE}}{V_T}} + \beta I_{SC} e^{\frac{V_{BC}}{V_T}}}$$

$$= \beta \frac{I_S e^{(V_{BE} - V_{BC})/V_T} + I_{SC}}{I_S e^{(V_{BE} - V_{BC})/V_T} + \beta I_{SC}}$$

$$= \beta \frac{e^{V_{CE\text{sat}}/V_T} + I_{SC}/I_S}{e^{V_{CE\text{sat}}/V_T} + \beta I_{SC}/I_S}$$

$$\beta_{\text{forced}} = 100 \frac{e^{200/25} - 100}{e^{200/25} + 100 \times 100} = 100 \times 0.2219 \approx 22.2$$

Ex: 4.10

$$I_E = \frac{I_S e^{\frac{V_{BE}}{V_T}}}{\alpha}$$

$$2 \text{ mA} = \frac{51}{50} 10^{-14} e^{\frac{V_{BE}}{V_T}}$$

$$V_{BE} = 25 \ln \left[ \frac{2}{10^3} \times \frac{50}{51} \times 10^{14} \right]$$

$$= 650 \text{ mV}$$

$$I_C = \frac{\beta}{\beta + 1} I_E = \frac{50}{51} \times 2$$

$$= 1.96 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{1.96}{50} \Rightarrow 39.2 \mu\text{A}$$

Ex: 4.11

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} = 1.5 \text{ A}$$

$$\therefore V_{BE} = V_T \ln [1.5 \times 10^{-11}]$$

$$= 25 \times 25.734$$

$$= 643 \text{ mV}$$

Ex: 4.12

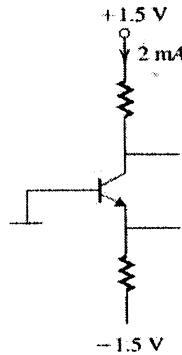


Fig 6.12

$$\beta = 100, V_{BE} = 0.8 \text{ V at } I_C = 1 \text{ mA}$$

$$V_{RE2} - V_{RE1} = V_T \ln [I_{C2}/I_{C1}]$$

$$= 25 \times 0.693 = 0.01733$$

$$\therefore V_{BE2} = 0.817 \text{ V}$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{1.5 - 0.5}{2} \text{ k}\Omega$$

$$= 500 \Omega$$

$$R_E = \frac{V_{EE} - V_{BE}}{I_C} \frac{\beta}{(\beta + 1)}$$

$$= \frac{1.5 - 0.817}{2} \times \frac{100}{101} \text{ k}\Omega$$

$$= 338 \Omega$$

Ex: 4.13

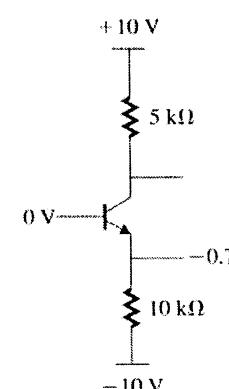


Fig 6.13

$$\beta = 50, V_{BE} = 0.7 \text{ V}$$

$$V_E = V_B - 0.7 \text{ V}$$

$$= 0 - 0.7 = -0.7 \text{ V}$$

$$I_E = \frac{-0.7 + 10}{10 \text{ K}}$$

$$= 0.93 \text{ mA}$$

$$I_C = \frac{50}{51} I_E = 0.91 \text{ mA}$$


$$V_C = 10 - 0.91 \times 5$$

$$= 5.45 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.91}{50}$$

$$= 0.0182 \mu\text{A}$$

Ex: 4.14

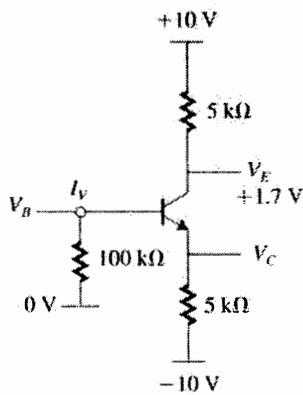

$$I_E = \frac{V_{EE} - V_E}{R_E}$$

$$\approx \frac{10 - 1.7}{5}$$

$$= 1.66 \text{ mA}$$

$$I_B = \frac{V_B - 0}{100 \text{ k}\Omega}$$

$$= 0.01 \text{ mA}$$

$$I_C = I_E - I_B$$

$$= 1.65 \text{ mA}$$


$$\alpha = \frac{I_C}{I_E} = \frac{1.65}{1.66} = 0.99$$

$$\beta = \frac{I_C}{I_B} = \frac{1.65}{0.01} = 165$$

$$V_C = V_{CC} + I_C R_C$$

$$= -10 + 1.65 \times 5 = -1.75 \text{ V}$$

Ex: 4.15

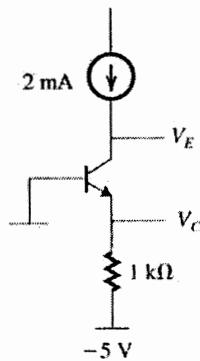

$V_{BE}$  decreases approx 2 mV/°C rise  
for 30°C rise

$$\Delta V_{BE} = -2 \times 30$$

$$= -60 \text{ mV}$$


$$\Delta V_E = -60 \text{ mV}$$

Since  $I_E$  is constant

$I_C$  is constant

$$\therefore \Delta V_C = 0 \text{ V}$$

Ex: 4.16

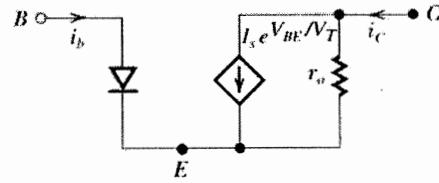

$$A + C, \quad i_C = I_S e^{\frac{V_{BE}}{V_T}} + \frac{v_{CE}}{r_O}$$

$$\text{and } r_O = \frac{V_A}{I}$$

$$\therefore i_C = I_S e^{\frac{V_{BE}}{V_T}} + \frac{V_{CE} \cdot I_S e^{\frac{V_{BE}}{V_T}}}{V_A}$$

$$= I_S e^{\frac{V_{BE}}{V_T}} \left[ 1 + \frac{v_{CE}}{V_A} \right]$$

QED

$$i_C = I_S e^{\frac{V_{BE}}{V_T}} + \frac{v_{CE}}{r_O} \text{ in Fig (a)}$$

$$i_B = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T}}$$

$$\therefore i_C = \beta i_B + \frac{v_{CE}}{r_O} \text{ as in Fig (b)}$$

QED

Ex: 4 . 17

$$r_o = \frac{V_A}{I_C} \quad (\text{V})$$

$I_C(\text{mA})$	0.1	1.0	10
$r_o$	$\frac{100}{0.0001}$	$\frac{100}{0.001}$	$\frac{100}{0.010}$
$r_o$	$10^6 \Omega$	$10^5 \Omega$	$10^4 \Omega$
$r_o$	1 MΩ	100 kΩ	10 kΩ

Ex: 4 . 18

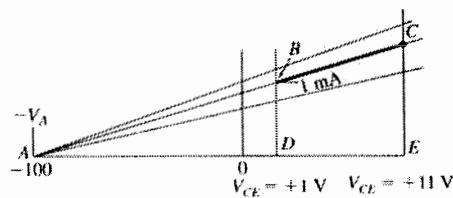


Fig 4 . 18

By similar triangles ABD v ACE


$$\frac{1}{r_o} = \frac{\Delta I_C}{\Delta V_{CE}}$$

$$\frac{BD}{CE} = \frac{AD}{AE} \quad \text{or} \quad \frac{1 \text{ mA}}{x} = \frac{100 + 1}{100 + 11}$$

$$\Rightarrow x = \frac{1 \times 111}{101} = 1.099 \text{ mA}$$

$$I_C \approx 1.1 \text{ mA}$$

Ex: 4 . 19

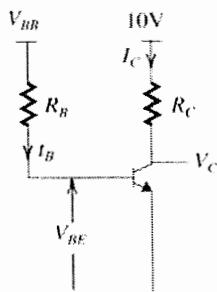

$$R_C = 10 \text{ k}\Omega, \beta = 50$$

$$(a) \text{ active } V_C \approx 5 \text{ V}$$

$$I_C = \frac{V_{CC} - V_C}{R_C}$$

$$= \frac{10 - 5}{10}$$

$$\approx 0.5 \text{ mA}$$

$$V_{BB} = V_{BE} + I_B R_B$$

$$= 0.7 + 10 \times 0.01$$

$$= 0.8 \text{ V}$$

$$(b) \text{ edge of saturation } V_{CE} = 0.3 \text{ V}$$

$$I_C = \frac{10 - 0.3}{10 \text{ K}} = \frac{9.7}{10} = 0.97 \text{ mA}$$

$$I_C = I_C / \beta = 0.97 / 50 = 0.0194 \text{ mA}$$

$$V_{BB} = 0.7 + 0.0194 \times 10 = 0.894 \text{ V}$$

$$(c) \text{ saturated } V_{CE} = 0.2 \text{ V}$$

$$I_C = (10 - 0.2) / 10 = 0.98 \text{ mA}$$

$$I_B = I_C / \beta F = 0.98 / 10 = 0.098 \text{ mA}$$

$$V_B = 0.7 + 0.098 \times 10 = 1.68 \text{ V}$$

Ex: 4 . 20

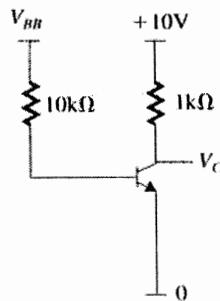


Fig 6.20

For  $V_{BB} = 0$

$$I_B = 0$$

Transistor is OFF


$$\therefore I_C = 0$$

$$V_C = V_{CC} - I_C R_C$$

$$= +10 - 0$$

$$= +10 \text{ V}$$

Ex: 4.21

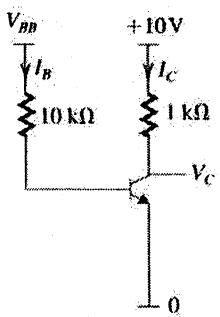

For  $V_{BB} = 1.7 \text{ V}$

$$I_B = \frac{1.7 - 0.7}{10} = 0.1 \text{ mA}$$

$$I_C = \beta I_B \\ = 50 \times 0.1 = 5 \text{ mA}$$

$$V_C = 10 - 5 \times 1 \text{ k}\Omega \\ = +5 \text{ V} > V_{BE} \text{ (so Active)}$$

$$(a) \text{ edge of saturation } V_{CE} = 0.3 \text{ V}$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{10 - 0.3}{5} = 1.94 \text{ k}\Omega$$

$$(b) \text{ deep saturation } v_{CE} = 0.2 \text{ V}$$

$$I_B = 0.1 \text{ mA (unchanged)}$$

$$I_C = \beta_{\text{forced}} I_B = 10 \times 0.1 = 1 \text{ mA}$$

$$R_C = \frac{10 - 0.2}{1 \text{ mA}} = 9.8 \text{ k}\Omega$$

Ex: 4.22

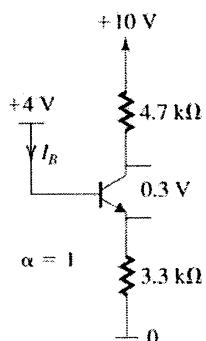


Fig 4.22

At edge of saturation  $v_{CE} = 0.3 \text{ V}$

$$V_{CC} = I_C R_C + 0.3 + I_E R_E$$


$$\approx I_E [R_C + R_E] + 0.3$$

$$I_E = \frac{10 - 0.2}{4.7 + 3.3} = 1.225 \text{ mA}$$

$$V_{BB} = I_E R_E + 0.7$$

$$= 1.225 \times 3.3 + 0.7 \\ = 4.7 \text{ V}$$

Ex: 4.23

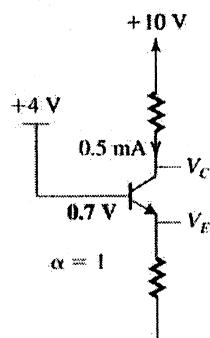

$$V_E = V_B - 0.7$$


$$= 4 - 0.7 = 3.3 \text{ V}$$

$$R_E = \frac{3.3 \text{ V}}{0.5 \text{ mA}} = 6.6 \text{ k}\Omega$$

$$V_C = V_B + 2 \text{ V} \\ = 4 + 2 = +6 \text{ V}$$

$$R_C = \frac{V_{CC} - V_C}{I_C} \\ = \frac{10 - 6}{0.5} = 8 \text{ k}\Omega$$

Ex: 4.24

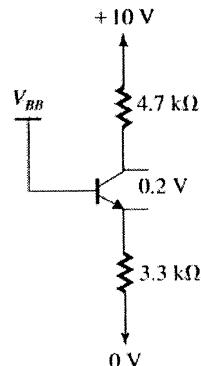

$$\beta_{\text{forced}} = 5$$

$$\text{Then } I_C = 5 I_B$$

$$I_E = 6 I_B$$


$$I_B = \frac{10 - 0.2}{5 \times 4.7 + 6 \times 3.3} \\ \approx 0.226 \text{ mA}$$

$$V_E = 6 I_B \times 3.3 \\ = 4.48 \text{ V}$$

$$V_{BB} = V_E + 0.7$$

$$= 5.18 \text{ V}$$

Ex: 4.25

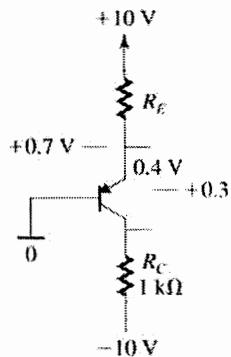

$$V_b = 0$$

$$V_c = +0.7 \text{ V}$$


$$I_e = \frac{10 - 0.7}{2} = 4.65 \text{ mA}$$

$$I_c = 0.99 I_e$$

$$R_c = \frac{10 - 0.4 + 0.7}{0.99 \times 4.65} = 2.2 \text{ k}\Omega$$

$$[V_c(\max) = 0 + 0.7 - 0.4 = +0.3 \text{ V}]$$

Ex: 4.26

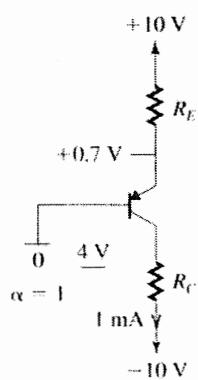


$$I_e = I_c$$

$$R_E = \frac{10 - 0.7}{1} = 9.3 \text{ k}\Omega$$

$$V_c = V_b - 4 \\ = -4 \text{ V}$$

$$R_C = \frac{10 - 4}{1} = 6 \text{ k}\Omega$$

Ex: 4.27

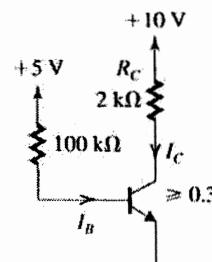

$$50 \leq \beta \leq 150$$

In active range

$$I_B = \frac{5 - 0.7}{100 \text{ k}\Omega} = 0.043 \text{ mA}$$

$V_c$  lowest for largest  $\beta$

$$I_c = \beta I_B = 150 \times 0.043 \text{ A}$$

$$R_C = \frac{V_{CC} - 0.3}{150 \times 0.043} = 1.5 \text{ k}\Omega$$


For  $\beta = 50$

$$V_c = 10 - 50 \times 0.043 = 6.78 \text{ V}$$

For  $\beta = 150$

$$V_c = 0.3 \text{ V}$$

Ex: 4.28

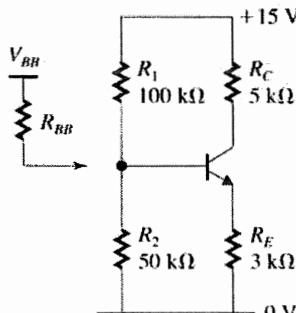

$$\beta = 50$$

$$V_{BB} = \frac{15 \times 50}{150} = 5 \text{ V}$$

$$R_{BB} = 50 \parallel 100 \\ = 100/3 \text{ k}\Omega$$


$$I_E = \frac{V_{BB} - V_{BE}}{R_E + [R_{BB}/(\beta + 1)]} \\ = \frac{4.3}{3 + \frac{100}{3} \cdot \frac{1}{51}} \\ = 1.18 \text{ mA}$$

$$I_C = I_E \frac{50}{51} = 1.15 \text{ mA}$$

$$\% \text{ change} = \frac{1.28 - 1.15}{1.28}$$


$\Rightarrow -9.8\%$

Ex: 4.29

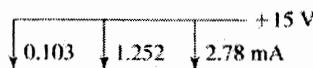

$$\begin{aligned} \text{Total current drawn} &= 0.103 + 1.252 + 2.75 \text{ mA} \\ &= 4.135 \text{ mA} \\ \text{Power Consumed} &= V \times I \\ &= 15 \times 4.135 \\ &= 62 \text{ mW} \end{aligned}$$

Ex: 4.30

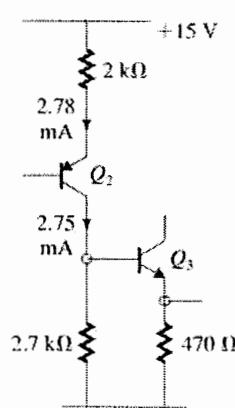

$$\beta = 100$$

$I_{E2}$  unchanged

$I_{C2}$  unchanged

$$V_{E3} = V_{C2} - 0.7 \text{ V}$$

$$IE_3 = \frac{VC_2 - 0.7}{0.470}$$

$$= 101 I_{B3}$$

$$= 101 \left[ 2.75 - \frac{V_{C2}}{2.7} \right]$$

Hence


$$VC_2 \left[ \frac{1}{(\beta+1)0.47} + \frac{1}{2.7 \text{ k}} \right] = 2.75 + \frac{0.7}{(\beta+1)0.47}$$

$$\Rightarrow VC_2 = 7.06 \text{ V}$$

$$VE3 = VC_2 - 0.7 = 6.36 \text{ V}$$


$$IC3 = \frac{VE3}{0.47} \times \frac{100}{101} = 13.4 \text{ mA}$$

Ex: 4.31

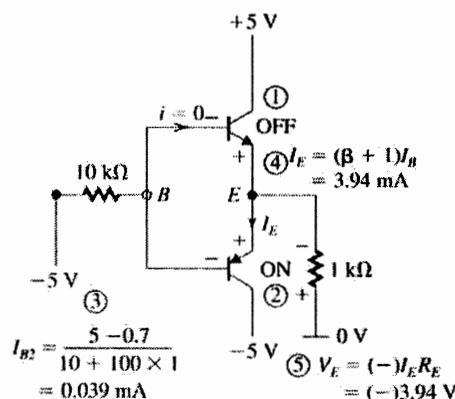

$$\text{Ans: } V_E = -3.94 \text{ V}$$

Ex: 4.32

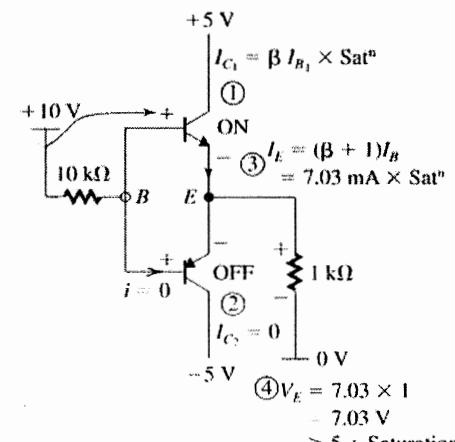

$$\textcircled{5} V_B = V_E + 0.7 \quad V_E \Rightarrow \frac{V_{CC} - 0.2}{1}$$

$$= 5.5 \text{ V} \quad = 4.8 \text{ V}$$

$$I_B = \frac{10 - 5.5}{10} \quad I_E \Rightarrow 4.8 \text{ mA}$$

$$\approx 0.45 \text{ mA}$$

$$\textcircled{6} I_{C(\text{sat})} = I_E - I_B \quad V_F \Rightarrow \frac{V_{CC} - 0.2}{1}$$

$$= 4.8 - 0.45 \quad = 4.8 \text{ V}$$

$$= 4.35 \text{ mA} \quad I_F \Rightarrow 4.8 \text{ mA}$$

$$\textcircled{7} \beta_{\text{forced}} = \frac{I_C}{I_B}$$

$$= \frac{4.35}{0.45} = 9.6 \ll 30$$

**Ex: 4 . 33**

$$A_V = -\frac{V_{CC} - V_{CE}}{V_T} = \frac{10 - V_{CE}}{0.025} = -320 \text{ V/V}$$

$$\Rightarrow V_{CE} = 10 - 8 = 2.0 \text{ V}$$

$$R_C = \frac{10 - V_{CE}}{1 \text{ mA}} = \frac{10 - 2}{1} = 8 \text{ k}\Omega$$

$$V_{CE \text{ Swing}} = 2.0 - 0.3 = 1.7 \text{ V}$$

$$A_V = \frac{\Delta V_{CE}}{\Delta V_{BE}} = -320 = \frac{1.7}{\Delta V_{BE}}$$

$$\Rightarrow |\Delta V_{BE}| = \frac{1.7}{320} = 5.3 \text{ mV}$$

**Ex: 4 . 34**

$$\text{Given: } g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{I_C = I_C}$$

$$\text{But } I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\text{thus } \frac{\partial I_C}{\partial V_{BE}} = \frac{I_S e^{\frac{V_{BE}}{V_T}}}{V_T}$$

$$= \frac{I_C}{V_T}$$

**Ex: 4 . 35**

$$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V}$$

**Ex: 4 . 36**

$$I_C = 0.5 \text{ mA (constant)}$$

$$\beta = 50 \quad \beta = 200$$

$$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V} \quad = 20 \text{ mA/V}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.5}{50} = \frac{0.5}{200} \approx 10 \mu\text{A} \quad \approx 2.5 \text{ mA}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{50}{20} = \frac{200}{20} = 2.5 \text{ k}\Omega \quad = 10 \text{ k}\Omega$$

**Ex: 4 . 37**


$$\beta = 100 \quad I_C = 1 \text{ mA}$$

$$g_m = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40} = 2.5 \text{ k}\Omega$$

$$r_c = \frac{r_\pi}{\beta + 1} = 25 \text{ }\Omega$$

**Ex: 4 . 38**

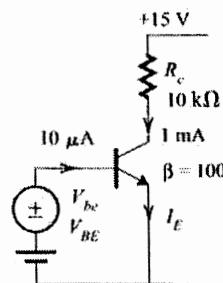

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mA/V}$$

$$A_V = \frac{v_{re}}{v_{be}} = -g_m R_C$$

$$= -40 \times 10$$

$$= -400 \text{ V/V}$$

$$V_C = V_{CC} - I_C R_C$$

$$= 15 - 1 \times 10 = 5 \text{ V}$$

$$N_C(t) = V_C + N_C(t)$$

$$= (V_{CC} - I_C R_C) + A_V v_{be}(t)$$


$$= (15 - 10) - 400 \times 0.005 \sin \omega t$$

$$= 5 - 2 \sin \omega t (t)$$

$$i_b(t) = I_B + v_{be}(t)$$

$$= 10 + 2 \sin \omega t (\mu\text{A})$$

**Ex: 4 . 39**

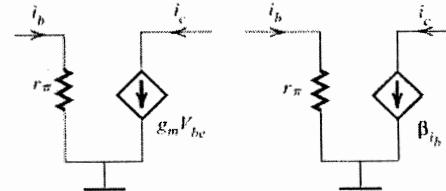


$$\text{Note: } g_m = \frac{I_C}{V_T} \text{ and } r_\pi = \frac{\beta}{g_m}$$

$$\text{given } i_C = \beta i_b = (g_m r_\pi) i_b$$

$$= r_\pi g_m \left( \frac{v_{be}}{r_\pi} \right)$$

$$= g_m v_{be}$$

**Ex: 4 . 40**

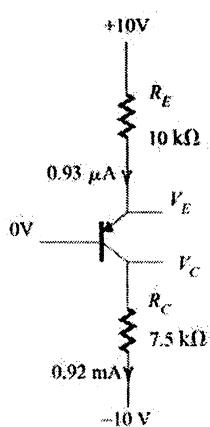

Change  $R_C$  to  $7.5 \text{ k}\Omega$


$$V_C = -10 + 0.92 \times 7.5 \\ \approx -3.1 \text{ V}$$

$$A_V = \frac{v_o}{v_i} = g_m R_C \\ = 36.8 \times 7.5 \\ = 276 \text{ V/V}$$

$$\hat{v}_o = A_V v_i$$

$$\approx 276 \times 10 \text{ mV} \\ \approx 2.76 \text{ V}$$

**Ex: 4 . 41**

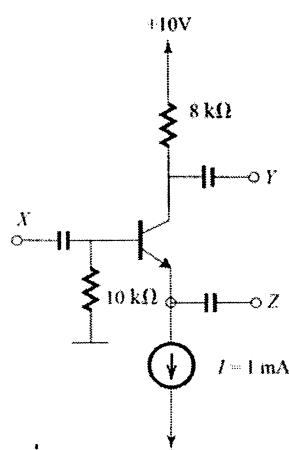

$$I_E = 1 \text{ mA}$$

$$I_C = \frac{100}{101} = 0.99 \text{ mA}$$

$$I_B = \frac{1}{101} = 0.0099 \text{ mA}$$

$$V_C = 10 - 8 \times 0.99 = 2.18 \text{ V}$$


$$V_B = -10 \times 0.0099 = -0.099 \approx -0.1 \text{ V}$$

$$V_E = -0.1 - 0.7 = -0.8 \text{ V}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.99}{0.025} = 39.6 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{39.6} = 2.53 \text{ k}\Omega$$
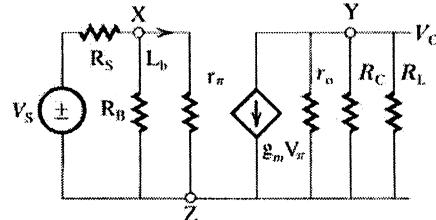
$$r_O = \frac{V_A}{I_C} = \frac{100}{0.99} = 101 \approx 100 \text{ k}\Omega$$



$$\frac{v_o}{v_s} = \frac{r_\pi \parallel R_B}{R_B + r_\pi \parallel R_B} \cdot (-)g_m(r_o \parallel R_C \parallel R_L) \\ = \frac{2}{2+2} (-) 39.6 (3.85) = -76.2 \text{ V/V}$$


$$\frac{r_o \parallel R_C \parallel R_L}{R_C \parallel R_L} = \frac{3.85}{4.00}$$

thus effect of  $r_o$  is  $\approx 3.9\%$

**Ex (2) 4 . 41**

$$A_{VO} = -g_m(r_o \parallel R_C)$$

$$R_O = (r_o \parallel R_C)$$

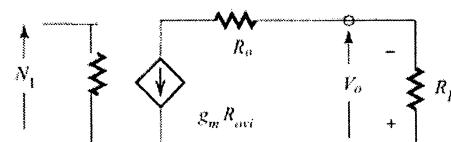

$$A_V = -\frac{g_m R_O V_1}{V_1} \times \frac{R_L}{R_O + R_L} \\ = -g_m \times \frac{R_O R_L}{R_O + R_L} \\ = -g_m \times \frac{(r_o \parallel R_C) R_L}{(r_o \parallel R_C) + R_L} \\ = -g_m (r_o \parallel R_C \parallel R_L)$$

**Ex: 4 . 42**

For  $I_C = 1 \text{ mA}$

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{0.025} = 40 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40} = 2.5 \text{ k}\Omega$$

$$r_O = \frac{V_A}{I_C} = \frac{100}{1} = 100 \text{ k}\Omega$$

$$R_{IN} = r_\pi = 2.5 \text{ k}\Omega$$

$$A_{VO} = -g_m(r_o \parallel R_C) = -40(5 \parallel 100) \\ = -97.6 \text{ V/V}$$

(cont.)

$$\frac{v_1}{v_s} = \frac{R_{IN}}{R_S + R_{IN}} = \frac{2.5}{5 + 2.5} = \frac{1}{3}$$

$$\frac{v_O}{v_S} = \frac{v_1}{v_s} \cdot \frac{r_o}{r_\pi} = -\frac{1}{3} \times 97.6 = -32.5 \text{ V/V}$$

$$|v_O| = A_{VO} v_s = 32.5 \times \frac{15}{1000} = 0.49 \text{ V}$$

For  $I_C = 0.5 \text{ mA}$  and  $R_C = 10 \text{ k}\Omega$

$$g_m = \frac{0.5}{0.025} = 20 \text{ mA/V}$$

$$r_\pi = \frac{100}{20} = 5.0 \text{ k}\Omega$$

$$r_o = \frac{100}{0.5} = 200 \text{ k}\Omega$$

$$R_{IN} = r_\pi = 5 \text{ k}\Omega$$

$$A_{VO} = -20(200 \text{ k} \parallel 10 \text{ k}) \\ = -190.5 \text{ V/V}$$

$$R_O = R_C \parallel r_o$$

$$= 10 \text{ k} \parallel 200 \text{ k}$$

$$= 9.5 \text{ k}$$


$$A_V = \frac{-190.5 \times 5}{5 + 9.5} \\ = -65.6 \text{ V/V}$$

$$G_V = \frac{v_O}{v_s} = \frac{1}{2} \times 65.6 = -32.8 \text{ V/V}$$

$$\frac{v_1}{v_s} = \frac{5}{5 + 5} = \frac{1}{2} \Rightarrow \hat{v}_{sig} = 10 \text{ mV}$$

$$|v_O| = 32.8 \times 10 \text{ m} = 0.33 \text{ V}$$

Ex: 4 . 43

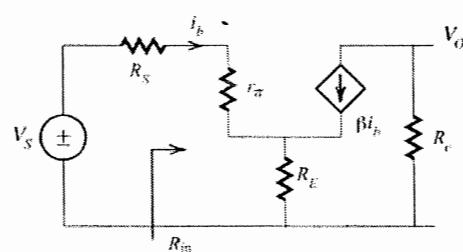

$$R_{IN} = \frac{v_1}{i_b} = r_\pi + (\beta + 1)R_E$$

$$\frac{V_S}{V_\pi} = \frac{R_S + r_\pi + (\beta + 1)R_E}{r_\pi}$$

$$= 1 + \frac{R_S}{r_\pi} + \frac{R_E}{r_\pi / (\beta + 1)}$$

$$= 1 + \frac{R_S}{r_\pi} + \frac{R_E}{r_e} \text{ Q E D}$$

$$\frac{v_S}{v_\pi} = \frac{100}{10} = 1 + 10 \text{ K} + \frac{R_E}{5/101}$$

$$\Rightarrow R_E = \frac{7 \times 5}{101} = \frac{5}{101} \approx 0.35 \text{ k}\Omega = 350 \text{ }\Omega$$

$$R_{IN} = 5 \text{ k} + (\beta + 1)0.35 \approx 40.4 \text{ k}\Omega$$

$$G_V = \frac{\beta(r_o \parallel R_C \parallel R_L)}{R_{sig} + R_{IN}} = \frac{100 \times 10}{10 + 40.4} \\ = -19.8 \text{ V/V}$$

Ex: 4 . 44

$$g_m = \frac{I_C}{V_T} = \frac{1}{0.025} = 40 \text{ ms}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{r_\pi}{\beta + 1} \approx 25 \text{ }\Omega$$

$$R_{IN} = r_\pi = 25 \text{ }\Omega$$

$$A_{VO} = g_m(r_o \parallel R_C) \approx g_m R_C \\ = 40 \times 5 = 200 \text{ V/V}$$

$$A_V = A_{VO} \times \frac{5}{5 + 5} = 100 \text{ V/V}$$

$$G_V = \frac{R_{IN}}{R_S + R_{IN}} \cdot A_V = \frac{25}{5000 + 25} \times 100 \\ = 0.5 \text{ V/V}$$

Ex: 4 . 45

$$R_S = 50 \text{ }\Omega$$

$$R_{IN} = r_\pi = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{I_E} = 50$$

$$\Rightarrow I_E = 25 / 50 = 0.5 \text{ mA}$$


$$A_{VO} = +g_m R_C = 20 \times 5 = 100 \text{ V/V}$$

$$G_V = \frac{1}{2} \times A_V = 40 \text{ V/V}$$

$$\Rightarrow A_V = 80 = g_m R_C$$

$$\therefore R_C = 80 / 20 = 4 \text{ k}\Omega$$

Ex: 4 . 46

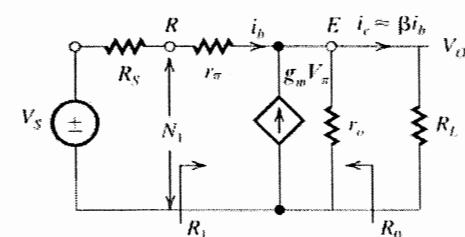

P Insert 30

$$i_b = \frac{v_1 - v_O}{r_\pi} \text{ and } v_O = +g_m V_\pi R_L$$

$$i_b = \frac{v_1 - (g_m V_\pi + i_b) R_L}{r_\pi}$$

$$\Rightarrow R_1 = \frac{v_1}{i_b} = r_\pi + (\beta + 1)R_L$$

$$= 0.5 + 101 \times 1 = 101.5 \text{ k}\Omega$$

$G_{VO} = 1$  [ $R_L$  moved,  $r_O = \infty$ ]

$$R_O = \frac{r_\pi + R_S}{\beta + 1} = \frac{0.5 + 10}{101} \Rightarrow 104 \text{ }\Omega$$

$$G_V = \frac{v_o}{v_s} = \frac{R_L}{R_O + R_S} = \frac{1}{0.104 + 1} = 0.91 \text{ V/V}$$


$$I_E = \frac{3.3}{\frac{2.6}{151} + 3.3} = 0.995 \text{ mA}$$

$$\% = \frac{0.995 - 0.984}{1} \times 100$$

= 1.1 %

Ex: 4.48

Ex: 4.47

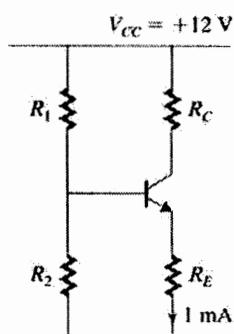

Design 1

$\beta = 100$

$R_E = 3 \text{ k}\Omega$

$$R_{BB} = \frac{80 \times 40}{80 + 40} = 26.7 \text{ k}\Omega$$

$$V_{BB} = \frac{12 \times 40}{80 + 40} = 4 \text{ V}$$

$$I_E = \frac{4 - 0.7}{26.7 + 3} = 1.01 \text{ mA}$$

$\beta = 50$

$$I_E = \frac{3.3}{26.7 + 3} = 1.04 \text{ mA}$$

$$\% \text{ change} = \frac{1.04 - 0.937}{1} \times 100 = 10.3 \%$$

Design 2

$\beta = 100$

$R_E = 3.3 \text{ k}\Omega$

$$R_{BB} = \frac{8 \times 40}{8 + 4} = 2.67 \text{ k}\Omega$$

$$V_{BB} = \frac{12 \times 4}{8 + 4} = 4 \text{ V}$$


$$I_{EE} = \frac{4 - 0.7}{2.67 + 3.3} = 0.99 \text{ mA}$$

$\beta = 150$

$$I_E = \frac{3.3}{2.6 + 3.3} = 0.984 \text{ mA}$$

$\beta = 150$

Ex: 4.48

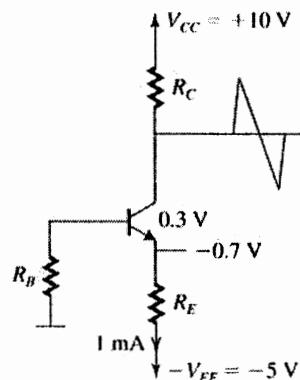

$$A_V = \frac{I_C R_C}{V_T} I_E \text{ given } \therefore \text{maximize } R_C$$

$$V_C = I_C R_C + 2 + 0.3 + I_E R_E$$

$$I_E = \frac{V_{EE} - 0.7}{R_E + R_B / (\beta + 1)} = \frac{4.3}{R_E + R_B / (\beta + 1)} = 1 \text{ mA}$$

$$\Rightarrow R_E + R_B / (\beta + 1) = 4.3 \text{ k}\Omega$$

For independence from  $\beta$ , set  $R_B = 0$  (OK for  $C_B$ )


$$\Rightarrow R_E = 4.3 \text{ k}\Omega$$

$$V_C(\min) = V_E + 0.3 \text{ V} = -0.3 \text{ V}$$

$$VCQ = V_C(\min) + 2 \text{ V} = +10 \text{ V}$$

$$R_C = \frac{V_{CC} - V_{CQ}}{I_C} = \frac{10 - 0.9}{0.9} = 8.48 \text{ k}\Omega$$

Ex: 4.49

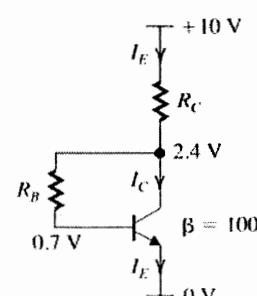

$$V_C = V_E + 0.4 + 2$$

$$= +2.4 \text{ V}$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{10 - 2.4}{2} = \frac{7.6}{1} = 7.6 \text{ k}\Omega$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{1}{101} \text{ mA}$$

(cont.)

$$R_B = \frac{V_C - V_B}{I_B} = 101(2.4 - 0.7) = 171.7 \text{ k}\Omega$$

Using 5% resistors:

$$R_C = 7.5 \text{ k}\Omega \quad R_B = 180 \text{ k}\Omega$$

$$0.7 + I_B R_B + I_E R_C - V_{CC} = 0$$

$$I_B = \frac{10 - 0.7}{180 + 7.5(\beta + 1)}$$

$$I_B = 9.92 \mu\text{A}$$


$$I_E = 101 \times I_B$$

$$= 1.002 \text{ mA}$$

$$V_C = 10 - 7.5(1.002)$$

$$= 2.5 \text{ V}$$

Ex. 4.50

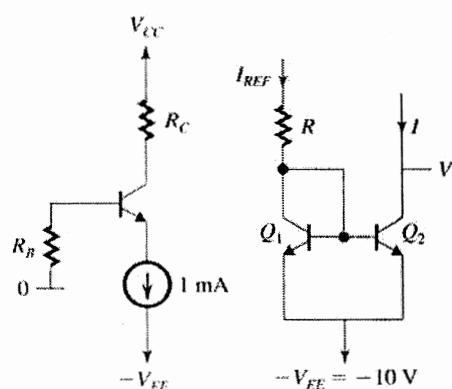

$$\beta = 100 \quad R_o = 100 \text{ k}\Omega$$

$$R_c = 7.5 \text{ k}\Omega$$

$$I_B = I_E / (\beta + 1) \approx I_E / 100$$

$$= 0.01 \text{ mA}$$

$$V_B = 0 - I_B R_B = -1 \text{ V}$$

$$V_E = V_B - 0.7 \text{ V} = -1.7 \text{ V}$$

$$V_C = V_{CC} - \frac{\beta}{\beta + 1} \times 1 \times 7.5 = +2.57 \text{ V}$$

$$R = \frac{V_{CC} - 0.7 + V_{EE}}{I_{REF}} = \frac{19.3}{1} = 19.3 \text{ k}\Omega$$

Ex. 4.51

Refer to Fig. E4.51

$$I_C = \alpha(1 \text{ m}) = 1 \text{ mA}$$

$$I_B = 0.01 \text{ mA}$$

$$V_E = 10 - 8 \text{ k}(1 \text{ m}) = +2 \text{ V}$$

$$V_B = 100 \text{ k} \times (-0.01 \text{ m}) = -1 \text{ V}$$

$$V_E = -1 - 0.7 = -1.7 \text{ V}$$

$$\beta = 100; \text{ upper limit} \Rightarrow V_{CC} - V_C = 8 \text{ V}$$

lower value  $\Rightarrow V_B - V_C = 0.4 \text{ V}$  (where

$$V_C = -1.4 \text{ V})$$

Swing:  $-1.4 - 2 = -3.4 \text{ V}$

$\beta = 50$ : upper still 8 V, lower

$$\Rightarrow I_B = 0.0196 \text{ mA} \text{ so } V_B = -1.96 \text{ V}$$

$$-1.96 \text{ V} - 0.4 - 2 = -4.4 \text{ V}$$

$\beta = 200$ : upper still 8 V,

$$\text{lower} \Rightarrow I_B = 0.005 \text{ mA} \text{ so } V_B = -0.5 \text{ V}$$

$$-0.5 - 0.4 - 2 = -2.9 \text{ V}$$

$$V_A = 100 \text{ V}$$

$$r_o = \frac{100}{1 \text{ m}} = 100 \text{ k}\Omega$$


$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ m}}{25 \text{ m}} = 40 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40 \text{ m}} = 2.5 \text{ k}\Omega$$


$$r_e = \frac{r_\pi}{(\beta + 1)} \approx 25 \text{ }\Omega$$

Ex: 4.52

Example 4.50

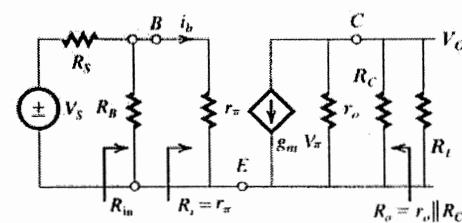

Ex: 4 . 53

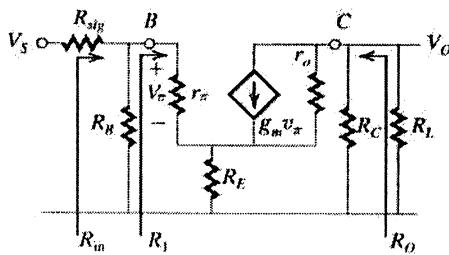

with  $R_E$ :

$$\frac{V_{\text{sig}}}{5 \text{ mV}} = \frac{5 + 20}{20} = \frac{5}{4} \Rightarrow V_{\text{sig}} = 6.25 \text{ mV}$$

w/o  $R_E$ :

$$\frac{V_{\text{sig}}}{5 \text{ mV}} = \frac{5 + (2.5 \parallel 100)}{(2.5 \parallel 100)} = \frac{3}{1} \Rightarrow V_s = 15 \text{ mV}$$

$$|V_o| = |V_s| \times A_V = 512.4 = 62 \text{ mV}$$

Ex: 4 . 54

$$g_m = 40 \text{ mA/V} \quad V_A = 100$$

$$r_p = 100 \text{ k}\Omega \quad \beta = 100$$

$$r_\pi = 2.5 \text{ k}\Omega \quad \alpha = 0.99$$

$$r_i = 25 \text{ }\Omega \quad I_e = 1 \text{ mA}$$

$$R_{\text{in}} = r_e = 25 \text{ }\Omega$$

$$A_{\text{vo}} = +g_m(R_C \parallel r_o)$$

$$= 40 \times 10^{-3} \times (8 \text{ k} \parallel 100 \text{ k}) \\ = -296 \text{ V/V}$$

$$R_{\text{out}} = R_C \parallel r_o = 7.4 \text{ k}\Omega$$

$$A_V = +g_m(R_C \parallel R_L \parallel r_o) \\ = 40 \times 3 = 120 \text{ V/V}$$

$$\frac{r_i}{r_{\text{sig}}} = \frac{r_e}{R_{\text{sig}} + r_e} = \frac{25}{5000 + 25} \\ = 0.005 \text{ V/V}$$

$$G_V = \frac{\alpha(R_C \parallel R_L)}{R_{\text{sig}} + (\beta + 1)(r_e + R_E)} \\ = 0.6 \text{ V/V}$$

$$R_{\text{sig}} = \frac{\alpha(R_C \parallel R_L)}{G_V}$$

$$R_{\text{sig}} = 54 \text{ }\Omega$$

Example 4 . 50

$$g_m = 40 \text{ mA/V} \quad r_\pi = 2.5 \text{ k}\Omega$$

$$r_o = 100 \text{ k}\Omega \quad V_A = 100 \text{ V} \quad R_g = 100 \text{ k}\Omega$$

$$R_{\text{sig}} = 5 \text{ k}\Omega \quad R_C = 8 \text{ k}\Omega \quad R_L = 5 \text{ k}\Omega$$

$$R_t = r_\pi + (\beta + 1)R_E$$

$$R_{\text{IN}} = R_g \parallel R_1 = 4 \times R_{\text{sig}} = 20 \text{ k}\Omega$$

$$\therefore R_E = \frac{25 - 2.5}{101} = 0.22 \text{ k}\Omega = 223 \text{ }\Omega$$

$$A_{\text{vo}} = \frac{-g_m R_C}{1 + g_m R_E} = \frac{-40(8)}{1 + 40(223)} = -32 \text{ V/V}$$


$$R_{\text{out}} = 8 \text{ k}\Omega$$

$$A_V = \frac{-R_C \parallel R_L}{r_e + R_E} = \frac{-8 \text{ k} \parallel 5 \text{ k}}{25 + 223} = -12.4 \text{ V/V}$$


$$G_V = \frac{-\beta(R_C \parallel R_L)}{R_{\text{sig}} + (\beta + 1)(r_e + R_E)} = -9.9 \text{ V/V}$$

$$\text{OR } G_V = \frac{R_{\text{IN}}}{R_{\text{sig}} + R_{\text{IN}}} \times A_V = \frac{20 \text{ k}}{25 \text{ k}} \times -12.4$$

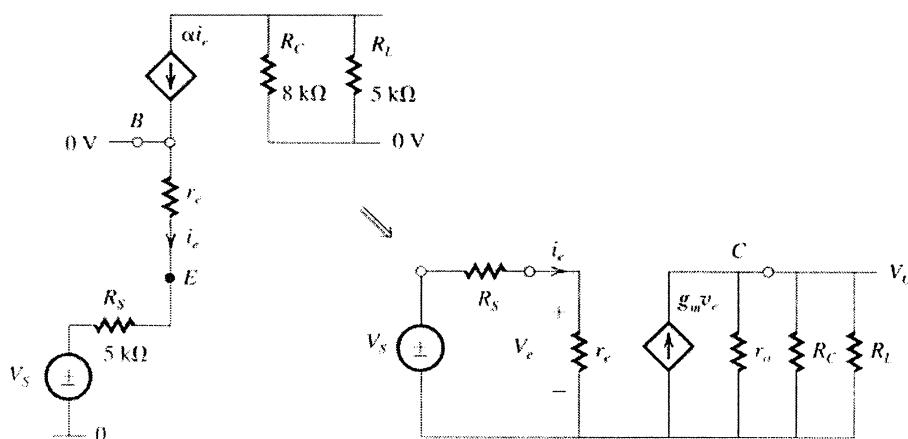Note: without  $R_E$ :  $A_V = -g_m(R_C \parallel R_L)$   
 $= -123 \text{ V/V}$



Ex: 4.55

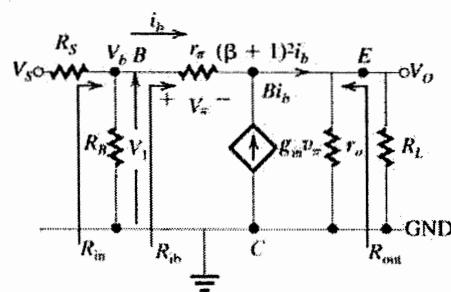

$$I_c = 5 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_c}$$

$$r_\pi = \frac{100(25 \text{ m})}{5 \text{ m}} = 500 \Omega$$

$$r_o = \frac{V_A}{I_c} = \frac{100}{5 \text{ m}} = 20 \text{ k}\Omega$$

$$i_b = \frac{V_b - V_o}{r_\pi} \text{ and } V_o = (\beta + 1)i_b(r_o \parallel R_L)$$

$$\therefore i_b = \frac{V_b - i_b(\beta + 1)(r_o \parallel R_L)}{r_\pi}$$

Ex 4.56 blank

$$\begin{aligned} \therefore R_{ib} &= \frac{V_b}{i_b} = r_\pi + (\beta + 1)(r_o \parallel R_L) \\ &= 0.5 + (101)(20 \parallel 1) \\ &= 96.7 \text{ k}\Omega \\ R_{IN} &= R_B \parallel R_{ib} = 40 \parallel 96.7 = 28.3 \text{ k}\Omega \\ G_V &= \frac{V_o}{V_S} = \frac{V_1}{V_S} \times \frac{V_o}{V_1} \\ &= -\frac{R_{IN}}{R_S + R_{IN}} \times \frac{(\beta + 1)(r_o \parallel R_L)}{(R_S \parallel R_B) + (\beta + 1)(r_e + (r_o \parallel R_L))} \\ &= 0.796 \text{ V/V} \end{aligned}$$

$$G_{vo} = \frac{40}{10 + 40} \times \frac{20 \text{ K}}{(10 \text{ K} \parallel 40 \text{ K})(5\text{E} + 5 + 20 \text{ K})}$$

$$G_{vo} = 0.8 \text{ V/V}$$

$$\begin{aligned} R_{out} &= r_o \parallel (r_e + [R_S \parallel R_B]) / (\beta + 1) \\ &= 20 \parallel [0.05 + 0.079] \text{ k}\Omega \\ &\approx 84 \Omega \end{aligned}$$

$$\hat{V}_o = \frac{\hat{V}_\pi \times (r_o \parallel r_e)}{r_e} = \frac{0.01 \times 0.95}{0.005} = 1.9 \text{ V}$$

$$\begin{array}{lll} \text{For } R_i(\text{k}\Omega) & 0.5 & 1.0 & 2.0 \\ G_V(\text{V/V}) & 0.68 & 0.735 & 0.765 \end{array}$$

**Ex: 5.1**

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{34.5 \text{ pF/m}}{4 \text{ nm}} = 8.625 \text{ fF}/(\mu\text{m})^2$$

$$\mu_n = 450 \text{ cm}^2/\text{VS}$$

$$k' = \mu_n C_{ox} = 388 \mu\text{A/V}^2$$

$$V_{ov} = (v_{gs} - v_t) = 0.5 \text{ V}.$$

$$g_{ds} = \frac{1}{1 \text{ k}\Omega} = k' \frac{W}{L} V_{ov} \Rightarrow \frac{W}{L} = 5.15$$

$L = 0.18 \mu\text{m}$ , so  $W = 0.93 \mu\text{m}$

**Ex: 5.2**

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{34.5 \text{ pF/m}}{4 \text{ nm}} = 2.30 \text{ fF}/\mu\text{m}^2$$

$$\mu_n = 550 \text{ cm}^2/\text{VS}$$

$$k' = \mu_n C_{ox} = 127 \mu\text{A/V}^2$$

$$I_D = \frac{1}{2} k' \frac{W}{L} V_{ov}^2 = 0.2 \text{ mA}, \frac{W}{L} = 20$$

$$\therefore V_{ov} = 0.40 \text{ V}.$$

$$V_{D_{\min}} = V_{ov} = 0.40 \text{ V}, \text{ for saturation}$$

$$\text{Ex: 5.3 } I_D = \frac{1}{2} k' \frac{W}{L} V_{ov}^2 \text{ in saturation}$$

Change in  $I_D$  is:

(a) double L, 0.5

(b) double W, 2

(c) double  $V_{ov}$ ,  $2^2 = 4$

(d) double  $V_{ds}$ , no change (ignoring length modulation)

(e) changes (a) - (d), 4

case (c) would cause leaving saturation if

$$V_{ds} < 2V_{ov}$$

**Ex: 5.4** In saturation  $v_{ds} \geq V_{ov}$ , so  $2V_{ov}$

$$I_D = \frac{1}{2} k' \frac{W}{L} V_{ov}^2, \text{ so } 4 I_D.$$

$$\text{Ex: 5.5 } V_{ov} = 0.5 \text{ V}$$

$$g_{ds} = k' \frac{W}{L} V_{ov} \times \frac{1}{1 \text{ k}\Omega}$$

$$\therefore k_n = k' \frac{W}{L} = 2 \text{ mA/V}^2$$

For  $v_{ds} = 0.5 \text{ V} \geq V_{ov}$

$$I_D = \frac{1}{2} k' \frac{W}{L} V_{ov}^2 = 0.25 \text{ mA}$$

for all  $v_{ds} \geq V_{ov} = 0.5 \text{ V}$ .

**Ex: 5.6**

$$V_A = V_A L = 50 \times 0.8 = 40 \text{ V},$$

$$\lambda = \frac{1}{V_A} = 0.025 \text{ V}^{-1}$$

$$V_{DS} = 1 \text{ V} > V_{ov} = 0.5 \text{ V}$$


$$\Rightarrow \text{Saturation: } I_D = \frac{1}{2} k' \frac{W}{L} V_{ov}^2 (1 + \lambda V_{DS})$$

$$I_D = \frac{1}{2} \times 200 \times \frac{16}{0.8} \times 0.5^2 (1 + 0.025 \times 1) \\ = 0.51 \text{ mA}$$

$$r_o = \frac{V_A}{I_D} = \frac{40}{0.51} = 78.4 \text{ k}\Omega \approx 80 \text{ k}\Omega$$

$$r_o = \frac{\Delta V_{DS}}{\Delta I_D} \Rightarrow \Delta I_D = \frac{2 \text{ V}}{80 \text{ K}} = 0.025 \text{ mA}$$

**Ex: 5.7**

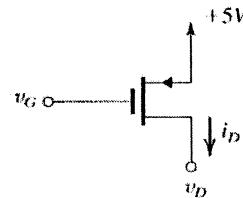

$$V_{tp} = -1 \text{ V}.$$

$$k_p = 60 \mu\text{A/V}^2$$

$$\frac{W}{L} = 10 \Rightarrow k_p = 600 \mu\text{A/V}^2$$

(a) Conduction occurs for  $v_{GS} \leq V_{tp} = -1 \text{ V}$ .

or  $v_G \leq V_{tp} + V_s = +4 \text{ V}$ .

(b) Triode region occurs for  $v_{GD} \leq V_{tp}$

or  $v_G - v_D \leq -1$

or  $v_D \geq v_G + 1$

(c) Conversely, for saturation

$$v_D \leq v_G + 1$$

(d) Given  $\lambda \equiv 0$

$$I_D = \frac{1}{2} k' \frac{W}{L} |V_{ov}|^2 = 75 \mu\text{A}$$

$$\therefore |V_{ov}| = 0.5 \text{ V} = -v_{GS} + V_{tp}$$

$$= -v_G + v_S + V_{tp} = 4 - v_G$$

$$\therefore v_G = +3.5 \text{ V.}$$

$$v_D \leq v_G + 1 = 4.5 \text{ V.}$$

(e) For  $\lambda = -0.02 \text{ V}^{-1}$  and  $|V_{ov}| = 0.5 \text{ V}$ ,

$$I_D = 75 \mu\text{A} \text{ and } r_o = \frac{1}{2|I_D|} = 667 \text{ k}\Omega$$

(f) At  $V_D = 3 \text{ V}$ ,

$$I_D = \frac{1}{2} k_n \frac{W}{L} |V_{ov}|^2 (1 + |\lambda| |v_{DS}|)$$

$$= 75 \mu\text{A} (1.04) = 78 \mu\text{A}$$

At  $V_D = 0 \text{ V}$ ,

$$I_D = 75 \mu\text{A} (1.10) = 82.5 \mu\text{A}$$

$$r_o = \frac{\Delta V_{DS}}{\Delta I_D} = \frac{3 \text{ V}}{4.5 \mu\text{A}} = 667 \text{ k}\Omega$$

Ex: 5.8

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 \Rightarrow 0.3 = \frac{1}{2} \times \frac{60}{1000}$$

$$\times \frac{120}{3} V_{ov}^2 \Rightarrow$$

$$V_{ov} = 0.5 \text{ V} \Rightarrow V_{GS} = V_{GV} + V_t = 0.5 + 1$$

$$= 1.5 \text{ V}$$


$$V_S = -1.5 \text{ V} \Rightarrow R_S = \frac{V_S - V_{SS}}{I_D}$$

$$= \frac{-1.5 - (-2.5)}{0.3} = 3.33 \text{ k}\Omega$$

$$R_S = 3.33 \text{ k}\Omega$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.4}{0.3} = 7 \text{ k}\Omega$$

Ex: 5.9

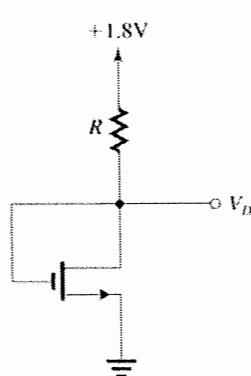

$$V_{in} = 0.5 \text{ V.}$$

$$\mu_n C_{ox} = 0.4 \text{ mA/V}^2$$

$$\frac{W}{L} = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}} = 4.0$$

$$\lambda = 0$$


saturation mode ( $v_{GD} = 0 < V_m$ )

$$V_D = 0.8 \text{ V.} = 1.8 - I_D R_D$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_D - V_m)^2 = 72 \mu\text{A}$$

$$\therefore R = \frac{1.8 - 0.8}{72 \mu\text{A}} = 13.9 \text{ k}\Omega$$

Ex: 5.10

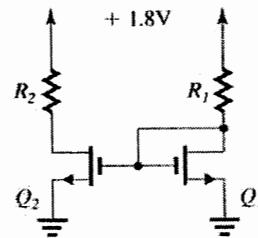

From Ex: 5.9,  $V_{GS} = 0.8 \text{ V}$ ,  $V_m = 0.5 \text{ V}$ ,

$$V_{ov} = 0.3 \text{ V.}$$

$$I_D = 72 \mu\text{A} \text{ (saturation)}$$

At the triode/saturation boundary

$$V_D = V_{ov} = 0.3 \text{ V}$$

$$\therefore R_2 = \frac{1.8 \text{ V} - 0.3 \text{ V}}{72 \mu\text{A}} = 20.8 \text{ k}\Omega$$

Ex: 5.11

$$R_D = 12.4 \times 2 = 24.8 \text{ k}\Omega$$

$V_{GS} = 5 \text{ V}$ , Assume triode region:

$$I_D = k_n \frac{W}{L} [(V_{GS} - V_t)V_{DS} - \frac{1}{2} V_{DS}^2] \quad \left. \begin{array}{l} \\ \end{array} \right\} \Rightarrow$$

$$I_D = \frac{V_{DD} - V_{DS}}{R} \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

$$\frac{5 - V_{DS}}{24.8} = 1 \times \left( (5 - 1)V_{DS} - \frac{V_{DS}^2}{2} \right)$$

$$\Rightarrow V_{DS}^2 - 8.08V_{DS} + 0.4 = 0$$

$$\Rightarrow V_{DS} = 0.05 \text{ V} < V_{ov} \Rightarrow \text{triode region}$$

$$I_D = \frac{5 - 0.05}{24.8} = 0.2 \text{ mA}$$

Ex: 5.12

As indicated in Example 3.5

$V_D \geq V_G - V_t$  for the transistor to be in saturation region.

$$V_{D_{\min}} = V_G - V_t = 5 - 1 = 4 \text{ V}$$

$$I_D = 0.5 \text{ mA} \Rightarrow R_{D_{\max}} = \frac{V_{DD} - V_{D_{\min}}}{I_D} = \frac{10 - 4}{0.5} = 12 \text{ k}\Omega$$

**Ex: 5.13**

$$I_D = 0.32 \text{ mA} = \frac{1}{2} k_s \frac{W}{L} V_{ov}^2 = \frac{1}{2} \times 1 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = 0.8 \text{ V}$$

$$V_{GS} = 0.8 + 1 = 1.8 \text{ V}$$

$$V_G = V_S + V_{GS} = 1.6 + 1.8 = 3.4 \text{ V}$$

$$R_{G2} = \frac{V_G}{I} = \frac{3.4}{1 \mu} = 3.4 \text{ M}\Omega,$$

$$R_{G1} = \frac{5 - 3.4}{1 \mu} = 1.6 \text{ M}\Omega$$


$$R_S = \frac{V_S}{0.32} = 5 \text{ k}\Omega$$

$$V_{DS} \geq V_{ov} \Rightarrow V_D \geq V_{ov} + V_S \Rightarrow V_D \geq 0.8 + 1.6 = 2.4 \text{ V}$$

Assume

$$V_D = 3.4 \text{ V}, \text{ then } R_D = \frac{5 - 3.4}{0.32} = 5 \text{ k}\Omega$$

**Ex: 5.14**

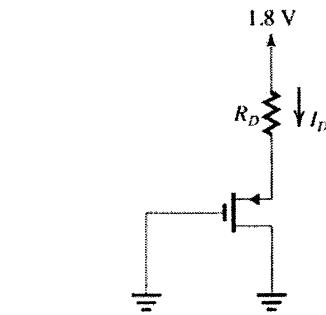

$$V_{ip} = -0.4 \text{ V.}$$

$$k_p = 0.1 \text{ mA/V}^2$$

$$\frac{W}{L} = \frac{10 \mu\text{m}}{0.18 \mu\text{m}} \Rightarrow k_p = 5.56 \text{ mA/V}^2$$

$$V_{GS} = -0.6 + V_{ip} = -1.0 \text{ V} \approx -1.8 + I_D R$$

$$I_D R = 0.8 \text{ V, for } V_{ov} = -0.6 \text{ V}$$

$$I_D = \frac{1}{2} k_p V_{ov}^2 = 0.1 \text{ mA}$$


$$\therefore R = 800 \Omega$$

**Ex: 5.15**

$V_t = 0$ : Since the circuit is perfectly symmetrical  $V_o = 0$  and therefore  $V_{GS} = 0$  which implies the transistors are turned off and  $I_{DN} = I_{DP} = 0$ .

$V_t = 2.5 \text{ V}$ : If we assume that the NMOS is turned on, then  $V_o$  would be less than 2.5 V and this implies that PMOS is off ( $V_{GSP} > 0$ )
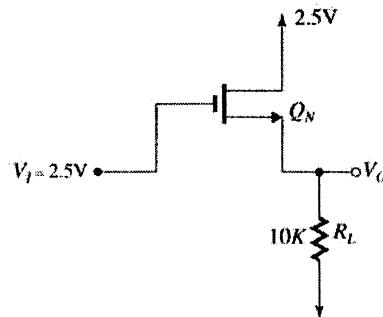
$$I_{DN} = \frac{1}{2} k_s \frac{W}{L} (V_{GS} - V_t)^2$$




$$I_{DN} = \frac{1}{2} \times 1 (2.5 - V_S - 1)^2$$

$$I_{DN} = 0.5(1.5 - V_S)^2$$

$$\text{Also: } V_S = R_L I_{DN} = 10 I_{DN}$$

$$I_{DN} = 0.5(1.5 - 10 I_{DN})^2$$

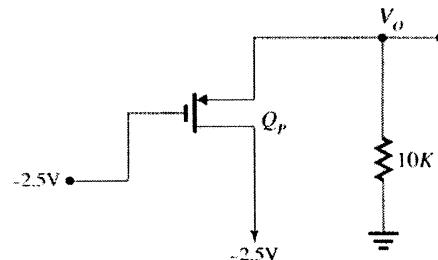

$$\Rightarrow 100 I_{DP}^2 = 32 I_{DP} + 2.25 = 0 \Rightarrow I_{DP} = 0.104 \text{ mA}$$

$$I_{DP} = 0, V_o = 10 \times 0.104 = 1.04 \text{ V}$$


$V_t = -2.5 \text{ V}$ : Again if we assume that  $Q_P$  is turned on, then  $V_o > -2.5 \text{ V}$  and  $V_{GS} < 0$  which implies the NMOS  $Q_N$  is turned off.

$$I_{DN} = 0$$

$$I_{DP} = \frac{1}{2} k_n \frac{W}{L} (V_{SG} - |V_t|)^2 = \frac{1}{2} \times 1 \\ \times (v_g + 2.5 - 1)^2$$

$$V_y = -10I_{DP} \Rightarrow 2I_{DP} = (-10I_{DP} + 1.5)^2 \\ \Rightarrow I_{DP} = 0.104 \text{ mA} \Rightarrow V_o = -10 \times 0.104 \\ = -1.04 \text{ V}$$

**Ex: 5.16**

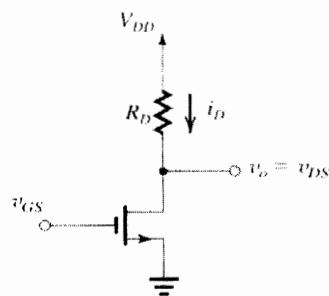

$$V_{DD} = 1.8 \text{ V}$$

$$R_D = 17.5 \text{ k}\Omega$$

$$V_t = 0.4 \text{ V.}$$

$$k_n = 4 \text{ mA/V}^2$$

$$\lambda = 0$$

(A) Cutoff/Saturation Boundary

$$v_{GS} = V_t - 0.4 \text{ V.}, v_o = v_{DS} = 1.8 \text{ V.}$$

(B) Saturation/Triode Boundary

$$v_{GD} = v_{GS} - v_o = V_t = 0.4 \text{ V.},$$

$$\Rightarrow v_{GS} = \left[ V_{DD} - \frac{1}{2} k_n (v_{GS} - V_t)^2 R_D \right] = 0.4$$

$$v_{GS} = [1.8 - 35(v_{GS}^2 - 0.8 v_{GS} + 0.16)] = 0.4$$

$$35v_{GS}^2 - 27v_{GS} + 3.4 = 0$$

$$v_{GS} = 0.613 \text{ V., } 0.1585$$

$$I_D = 90.7 \mu\text{A}$$

$$v_o = 0.213 \text{ V.}$$


(C) For  $v_{GS}|_C < V_{DD} = 1.8 \text{ V.}$ , triode,

$$V_{OV} = 1.4 \text{ V.}$$

$$r_{DS} = (k_n V_{ov})^{-1} = 179 \Omega$$

$$V_o|_C = V_{DS}|_C = V_{DD} \frac{r_{DS}}{R_D + r_{DS}} = 18 \text{ mV.}$$

**Ex: 5.17**

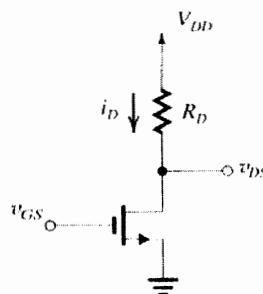

$$V_t = 0.4 \text{ V.}$$

$$V_{DD} = 1.8 \text{ V.}$$

$$V_{GS} = 0.6 \text{ V.}$$

$$k_n = 0.4 \text{ mA/V}^2$$

$$\frac{W}{L} = 10$$

$$R_D = 17.5 \text{ k}\Omega$$

(a)  $V_{OV} = 0.2 \text{ V.},$

$$g_m = k_n \frac{W}{L} V_{ov} = 800 \mu\text{A/V}$$

for  $A_V = -g_m R_D = -10$ , make

$$R_D = 12.5 \text{ k}\Omega$$

$$v_{GS} = 0.6 \text{ V.}, I_D = 0.08 \text{ mA.}$$

$$V_{DS} = 0.8 \text{ V.}$$

(b) keep  $R_D = 17.5 \text{ k}\Omega$

$$\therefore g_m R_D = -10 \Rightarrow g_m = 571 \mu\text{A/V}$$


$$= k_n \frac{W}{L} V_{ov}$$

$$\therefore V_{OV} = 0.143 \text{ V.}$$

$$v_{GS} = 0.54 \text{ V.}, I_D = 0.04 \text{ mA.}$$

$$v_{DS} = 1.1 \text{ V.}$$


**Ex: 5.18**

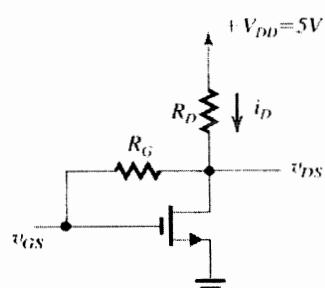

$$V_t = 0.7 \text{ V}, \\ k_n = 1 \text{ mA/V}^2$$

$$i_t = \frac{v_t}{r_o} + i = \frac{v_t}{r_o} + g_m v_t$$
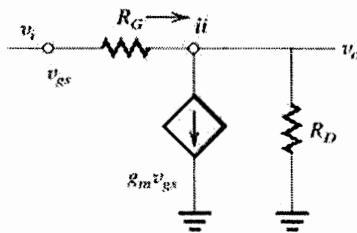
$$\therefore \text{Req} = \frac{v_t}{i_t} r_o \parallel \frac{1}{g_m}$$



$$\text{Design for } A_v = \frac{v_o}{v_i} = -25, R_{in} = 500 \text{ k}\Omega$$

$$\therefore g_m R_D = 25 = k_n V_{ov} R_D$$

$$R_{in} = \frac{v_i}{i_t} = \frac{v_i}{v_i - v_o} R_G$$

$$\Rightarrow R_G = 26 R_{in} = 13 \text{ M}\Omega$$

$$I_D R_D = \left( \frac{1}{2} k_n V_{ov}^2 \right) R_D$$

$$= \frac{1}{2} g_m R_D V_{ov} = 12.5 \text{ V}_{ov}$$

and

$$V_{ov} = V_{DD} - V_t - I_D R_D = 4.3 - 12.5 \text{ V}_{ov}$$

$$\therefore V_{ov} = 0.319 \text{ V.}$$

$$g_m = 319 \mu\text{A/V}$$


$$R_D = 78.5 \text{ k}\Omega$$

$$V_{DS} = V_{ov} + V_t$$


$$\hat{v}_{GD} = 0 + 26 \hat{v}_t \approx V_t$$

$$\therefore |\hat{v}_t| < \frac{V_t}{26} = 27 \text{ mV.}$$

Ex: 5.19

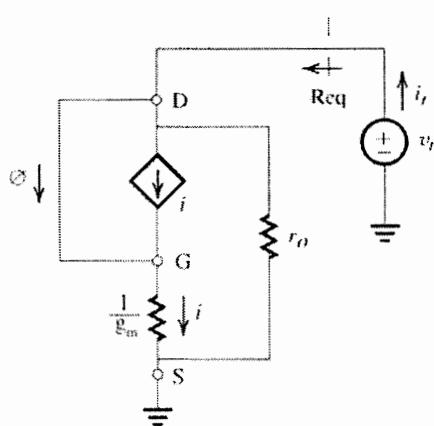

Ex: 5.20

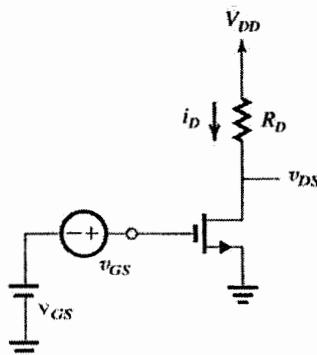

$$V_{DD} = 5 \text{ V.}$$

$$V_{GS} = 2 \text{ V.}$$

$$V_t = 1 \text{ V.}$$

$$\lambda = 0$$

$$k_n = 20 \mu\text{A/V}^2$$

$$R_D = 10 \text{ k}\Omega$$

$$\frac{W}{L} = 20$$

$$(a) V_{GS} = 2V \Rightarrow V_{ov} = 1 \text{ V.}$$

$$I_D = \frac{1}{2} k_n \frac{W}{L} V_{ov}^2 = 200 \mu\text{A}$$

$$V_{DS} = V_{DD} - I_D R_D = +3 \text{ V}$$

$$(b) g_m = k_n \frac{W}{L} V_{ov} = 400 \mu\text{A/V}$$

$$(c) A_V = \frac{v_{DS}}{v_{GS}} = -g_m R_D = -4$$

$$(d) v_{gs} = 0.2 \sin \omega t \text{ V.}$$

$$v_{ds} = -0.8 \sin \omega t \text{ V.}$$

$$v_{DS} = V_{DS} + v_{ds} \Rightarrow 2.2 \leq v_{DS} \leq 3.8 \text{ V.}$$

$$(e) \text{ Using (5.43)}$$

$$i_D = \frac{1}{2} k_n (V_{GS} - V_t)^2$$

$$+ k_n (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n v_{gs}^2$$

$$i_D = 200 \mu\text{A} + (80 \mu\text{A}) \sin \omega t$$

$$+ (8 \mu\text{A}) \sin^2 \omega t$$

$$= [200 + 80 \sin \omega t + (4 - 4 \cos \omega t)] \mu\text{A}$$

$I_D$  shifts by 4  $\mu\text{A}$

$$2\text{HD} = \frac{\dot{i}_{2\omega}}{\dot{i}_\omega} = \frac{4 \mu\text{A}}{80 \mu\text{A}} = 0.05 \text{ (5%)}$$

**Ex: 5.21**

$$\text{a) } g_m = \frac{2I_D}{V_{OV}} I_D = \frac{1}{2} \times k_n \frac{W}{L} V_{OV}^2 = \frac{1}{2} \times 60 \times 40 \times (1.5 - 1)^2$$

$$I_D = 300 \mu\text{A} = 0.3 \text{ mA}, V_{OV} = 0.5 \text{ V}$$

$$g_m = \frac{2 \times 0.3}{0.5} = 1.2 \text{ mA/V},$$

$$r_o = \frac{V_A}{I_D} = \frac{15}{0.3} = 50 \text{ k}\Omega$$

$$I_D = 0.5 \text{ mA} \Rightarrow g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

$$= \sqrt{2 \times 60 \times 40 \times 0.5 \times 10^3}$$

$$g_m = 1.55 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{15}{0.5} = 30 \text{ k}\Omega$$

**Ex: 5.22**

$$I_D = 0.1 \text{ mA}, g_m = 1 \text{ mA/V}, k_n = 50 \mu\text{A/V}^2$$

$$g_m = \frac{2I_D}{V_{OV}} \Rightarrow V_{OV} = \frac{2 \times 0.1}{1} = 0.2 \text{ V}$$

$$I_D = \frac{1}{2} k_n \frac{W}{L} V_{OV}^2 \Rightarrow \frac{W}{L} = \frac{2I_D}{k_n V_{OV}^2}$$

$$= \frac{2 \times 0.1}{50 \times 0.2^2} = 100$$

**Ex: 5.23**

$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV}$  Same bias conditions, so same  $V_{OV}$  and also same  $L$  and  $g_m$  for both PMOS and NMOS.

$$\mu_n C_{ox} W_n = \mu_p C_{ox} W_p \Rightarrow \frac{\mu_p}{\mu_n} = 0.4 = \frac{W_n}{W_p}$$

$$\Rightarrow \frac{W_p}{W_n} = 2.5$$

**Ex: 5.24**

$$I_D = \frac{1}{2} k_n \frac{W}{L} (V_{SG} - |V_t|)^2$$

$$= \frac{1}{2} \times 60 \times \frac{16}{0.8} \times (1.6 - 1)^2$$

$$I_D = 216 \mu\text{A}$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 216}{1.6 - 1} = 720 \mu\text{A/V}$$

$$= 0.72 \text{ mA/V}$$

$$\lambda = 0.04 \Rightarrow V_A = \frac{1}{\lambda} = \frac{1}{0.04} = 25 \text{ V}/\mu\text{m}$$

$$r_o = \frac{V_A \times L}{I_D} = \frac{25 \times 0.8}{0.216} = 92.6 \text{ k}\Omega$$

**Ex: 5.25**

$$g_m r_o = \frac{2I_D}{V_{OV}} \times \frac{V_A}{I_D} = \frac{2V_A}{V_{OV}} = A_o$$

$$V_A \times L = V_A$$


$$L = 0.8 \text{ }\mu\text{m} \Rightarrow A_o = \frac{2 \times 12.5 \times 0.8}{0.2}$$

$$= 100 \text{ V/V}$$

**Ex: 5.26**

$$(5.70) A_{vo} = -g_m (R_o \parallel r_o)$$

$$(5.72) R_o = R_D \parallel r_o$$

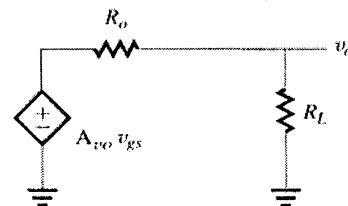


$$A_v = \frac{v_o}{v_{GS}} = A_{vo} \frac{R_L}{R_o + R_L}$$

$$= -g_m R_o \frac{R_L}{R_o + R_L}$$

$$\therefore A_v = -g_m (R_o \parallel R_L) = -g_m (R_D \parallel r_o \parallel R_L)$$

same as (5.75)

**Ex: 5.27**

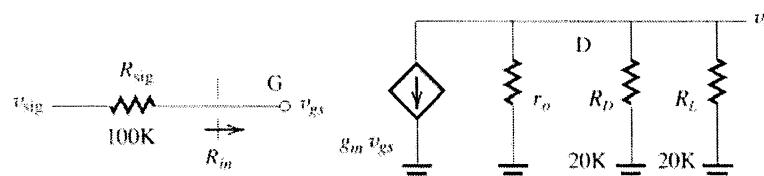

$$I_D = 0.25 \text{ mA}, V_{OV} = 0.25 \text{ V},$$

$$V_A = 50 \text{ V}$$

$$r_o = \frac{V_A}{I_D} = 200 \text{ k}\Omega$$

$$g_m = \frac{2I_D}{V_{OV}} = 2 \text{ mS}$$

$$R_{in} = \infty$$

$$A_{vD} = -g_m(R_D \parallel r_o) \approx -g_m R_D = -4$$

$$R_O = R_D \parallel r_o \approx R_D = 20 \text{ k}\Omega$$


$$A_v = G_V = -g_m(R_D \parallel r_o \parallel R_L) \approx$$

$$-g_m(R_D \parallel R_L) = -20 \text{ V/V}$$

for  $\hat{v}_{gs} = (10\%) 2V_{OV} = 0.05 \text{ V}$ ,

$$\hat{v}_o = |A_v \hat{v}_{gs}| = 1 \text{ V.}$$

**Ex: 5.28**

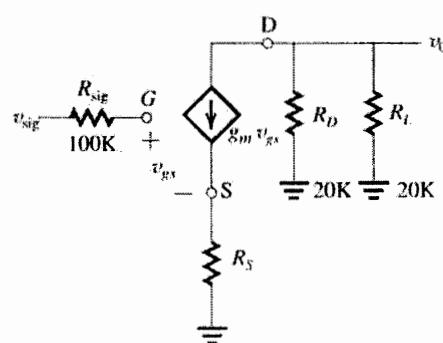

Assuming  $V_A \rightarrow \infty$

From Ex 5.27

$$g_m = 2 \text{ mS}$$


$$\frac{v_{gs}}{V_{Dsig}} = \frac{1}{1 + g_m R_S} = \frac{50 \text{ mV}}{200 \text{ mV}} \Rightarrow g_m R_S = 3$$

$$\therefore R_S = 1.5 \text{ k}\Omega$$

$$G_V = A_V = \frac{-g_m(R_D \parallel R_L)}{1 + g_m R_S} = \frac{-20}{4} = -5$$

$$\hat{v}_o = |G_V \hat{v}_{sig}| = 1 \text{ V.}$$

**Ex: 5.29**

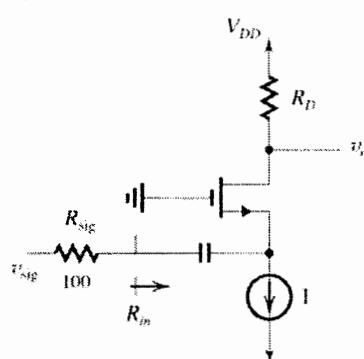

$$R_{in} = \frac{1}{g_m} = R_{sig} = 100 \text{ }\Omega$$

$$\Rightarrow g_m = 10 \text{ mA/V}$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2I_D}{0.25 \text{ V}} \Rightarrow I_D = 1 \text{ mA}$$

$$G_V = \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} g_m R_D$$

$$= \left(\frac{1}{2}\right)(10 \text{ mA/V})(2 \text{ k}\Omega)$$

$$= +10$$

**Ex: 5.30**

CD amplifier


$$R_{out} = \frac{1}{g_m} = 100 \text{ }\Omega \Rightarrow g_m = 10 \text{ mA/V}$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2I_D}{0.25 \text{ V}} \Rightarrow I_D = 1.25 \text{ mA}$$

$$\hat{v}_o = \hat{v}_{sig} \frac{g_m R_L}{1 + g_m R_L} = 0.91 \text{ V.}$$

$$\hat{v}_{gs} = \hat{v}_{sig} \frac{1}{1 + g_m R_L} = 91 \text{ mV.}$$

$$R_{out} = 100 \text{ }\Omega$$

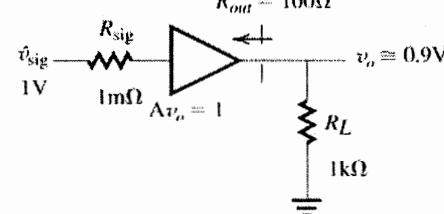

**Ex: 5.31**

CD (source follower)

$$R_{out} = 200 \text{ }\Omega = \frac{1}{g_m} \Rightarrow g_m = 5 \text{ mA/V}$$

$$g_m = k_a \frac{W}{L} V_{OV} = (0.4 \text{ mA/V}^2)$$

$$\left(\frac{W}{L}\right)(0.25 \text{ V}) \Rightarrow \frac{W}{L} = 50$$


$$I_D = \frac{1}{2} k_a \frac{W}{L} V_{OV}^2 = 0.625 \text{ mA}$$

$$G_V = \frac{g_m R_L}{1 + g_m R_L}$$

for  $K \leq R_L \leq 10 \text{ k}\Omega$

$$0.83 \leq G_V \leq 0.98$$

Ex: 5.32

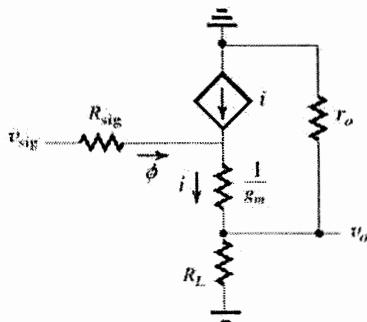

$$R_S = \frac{V_S - V_{SS}}{I_D} = \frac{-2 - (-5)}{0.5} = 6 \text{ k}\Omega$$

$$\rightarrow R_S = 6.2 \text{ k}\Omega$$

If we choose  $R_D = R_S = 6.2 \text{ k}\Omega$  then  $I_D$  will slightly change:

$$I_D = \frac{1}{2} \times 1 \times (V_{GS} - 1)^2. \text{ Also}$$

$$V_{GS} = -V_S = 5 - R_S I_D$$

$$2I_D = (4 - 6.2I_D)^2$$

$$\Rightarrow 38.44I_D^2 - 51.6I_D + 16 = 0$$

$$\Rightarrow I_D = 0.49 \text{ mA}, 0.86 \text{ mA}$$

$I_D = 0.86$  results in  $V_s > 0$  or  $V_s > V_G$  which is not acceptable, therefore  $I_D = 0.49 \text{ mA}$

$$V_s = -5 + 6.2 \times 0.49 = -1.96 \text{ V}$$

$$V_D = 5 - 6.2 \times 0.49 = +1.96 \text{ V}$$

$R_G$  should be selected in the range of  $1 \text{ M}\Omega$  to  $10 \text{ M}\Omega$  to have low current.

Ex: 5.35

$$I_D = 0.5 \text{ mA} = \frac{1}{2} k_n \frac{W}{L} V_{OV}^2 \Rightarrow V_{OV}^2$$

$$= \frac{0.5 \times 2}{1} = 1 \Rightarrow$$

$$V_{OV} = 1 \text{ V} \Rightarrow V_{GS} = 1 + 1 = 2 \text{ V}$$

$$= V_D \Rightarrow R_D = \frac{5 - 2}{0.5} = 6 \text{ k}\Omega$$

$\Rightarrow R_D = 6.2 \text{ k}\Omega$  standard value. For this  $R_D$  we have to recalculate  $I_D$ :

$$I_D = \frac{1}{2} \times 1 \times (V_{GS} - 1)^2$$

$$= \frac{1}{2} (V_{DD} - R_D I_D - 1)^2$$

$$(V_{GS} = V_D = V_{DD} - R_D I_D)$$

$$I_D = \frac{1}{2} (4 - 6.2I_D)^2 \Rightarrow I_D = 0.49 \text{ mA}$$

$$V_D = 5 - 6.2 \times 0.49 = -1.96 \text{ V}$$

Ex: 5.36

Using Eq. 3.53

$$I = I_{REF} \frac{(W/L)_2}{(W/L)_1} \Rightarrow I_{REF} = 0.5 \times \frac{1}{5}$$

$$\Rightarrow I_{REF} = 0.1 \text{ mA}$$

$$I_{REF} = 0.1 = \frac{1}{2} k_n \left( \frac{W}{L} \right)_1 V_{OV}^2 \Rightarrow V_{OV}$$

$$= \frac{0.1 \times 2}{0.8} = 0.25 \Rightarrow V_{OV} = 0.5 \text{ V}$$

$$V_{GS} = V_{OV} + V_t = 1.5 \text{ V}$$

$$\Rightarrow V_G = -5 + 1.5 = -3.5 \text{ V}$$

$$A_{VO} = A_V |_{R_L \rightarrow \infty} = \frac{g_m r_o}{1 + g_m r_o}$$

$$A_{VO} = \frac{r_o}{r_o + \frac{1}{g_m}}$$

$$A_{VO} = \frac{\left(\frac{V_A}{I_D}\right)}{\left(\frac{V_A}{I_D}\right) + \left(\frac{V_{OV}}{2I_D}\right)}$$

$$= \frac{2V_A}{2V_A + V_{OV}} = \left[ 1 + \frac{V_{OV}}{2V_A} \right]^{-1}$$

for  $V_A = 20 \text{ V}$ .

$$A_{VO} = 0.99 = \frac{1}{1 + \frac{V_{OV}}{4V_A}} \Rightarrow V_{OV} = 0.40 \text{ V}.$$

Ex: 5.33

$$I_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_t)^2 \Rightarrow 0.5 \text{ mA}$$

$$\approx \frac{1}{2} \times 1 \times (V_{GS} - 1)^2$$

$$V_{GS} = 2 \text{ V}.$$

IF  $V_t = 1.5 \text{ V}$  then:

$$I_D = \frac{1}{2} \times 1 \times (2 - 1.5)^2 = 0.125 \text{ mA}$$

$$\Rightarrow \frac{\Delta I_D}{I_D} = \frac{0.5 - 0.125}{0.5} = 0.75 = 75\%$$

Ex: 5.34

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{5 - 2}{0.5} = 6 \text{ k}\Omega$$

$$\Rightarrow R_D = 6.2 \text{ k}\Omega$$

$$I_D = \frac{1}{2} k_n \frac{W}{L} V_{OV}^2 \Rightarrow 0.5 = \frac{1}{2} \times 1 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 1 \text{ V}$$

$$\Rightarrow V_{GS} = V_{OV} + V_t = 1 + 1 = 2 \text{ V}$$

$$\Rightarrow V_S = -2 \text{ V}$$

$$R = \frac{V_{GS} - V_G}{I_{REF}} = \frac{5 - (-3.5)}{0.1} = 85 \text{ k}\Omega$$

$$V_{DS2} \geq V_{OV} \Rightarrow V_{DSmin} = V_{OV} = 0.5 \text{ V}$$

$$\Rightarrow V_{Dmin} = -4.5 \text{ V}$$


Ex: 5.37

$$V_t = 1.5 \text{ V}$$

$$k_n \frac{W}{L} = 1 \text{ mA/V}^2$$

$$V_A = 75 \text{ V.}$$
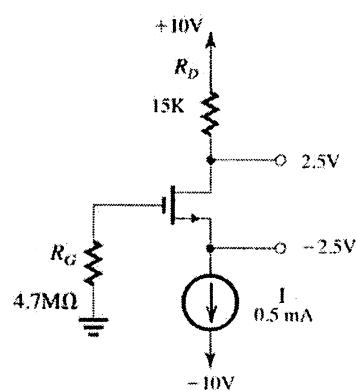
$$I_D = 0.5 \text{ mA} = \frac{1}{2} k_n \frac{W}{L} V_{ov}^2 \Rightarrow V_{ov} = 1.0 \text{ V.}$$



$$V_{GS} = V_t + V_{ov} = 2.5 \text{ V}$$

$$V_g = 0$$

$$V_s = -2.5 \text{ V.}$$

$$V_D = V_{DD} - I_D R_D = +2.5 \text{ V.}$$


$$g_m = k_n \frac{W}{L} V_{ov} = 1 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = 150 \text{ k}\Omega$$

$$V_{GD} = \hat{v}_{gd} = V_t$$

$$-\hat{v}_{gd} \cong \hat{v}_d = V_t - V_{GD} = 4.0 \text{ V.}$$

Ex: 5.38

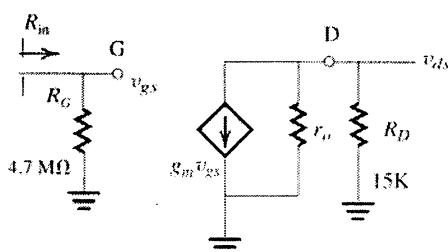

$$g_m = \sqrt{2k_n \frac{W}{L} I_D} = 1 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = 150 \text{ k}\Omega$$

For  $r_o \rightarrow \infty$

$$R_{in} = R_G = 4.7 \text{ M}\Omega$$

$$A_{vo} = -g_m R_D = -15$$

$$R_{out} = R_D = 15 \text{ k}\Omega$$

For  $r_o = 150 \text{ k}\Omega$ ,  $R_L = 15 \text{ k}\Omega$

$$R_{in} = 4.7 \text{ M}\Omega$$

$$A_{vo} = -g_m (R_D \parallel r_o) = -13.6$$

$$R_{out} = R_D \parallel r_o = 13.6 \text{ k}\Omega$$



$$G_V = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_L}{R_L + R_{out}} = -7.0$$

$$v_{DS} = v_O = V_{DS} + v_{ds}$$

$$= 2.5 \text{ V} + G_V(0.4 \text{ V}_p-p)$$

$v_O$  is a  $2.8 \text{ V}_p-p$  sinusoid superimposed upon a  $2.5 \text{ V}$   $d_c$  voltage.

Ex: 5.39

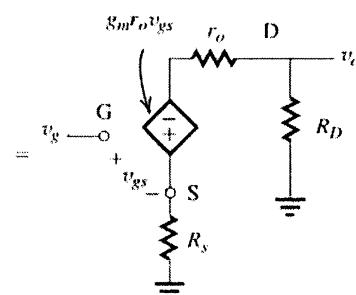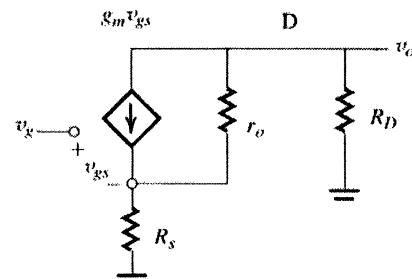

$$(1) v_o = v_{gs} \frac{-g_m r_o R_D}{R_D + r_o + R_s}$$

$$(2) v_{gs} = v_s \frac{R_D + r_o + R_s}{R_D + r_o + R_s (1 + g_m r_o)}$$

$$(3) v_o = V_s \frac{-g_m r_o R_D}{R_D + r_o + R_s (1 + g_m r_o)}$$

we want

$$\left. \frac{v_o}{v_g} \right|_{R_S} = \frac{1}{3} \left. \frac{v_o}{v_g} \right|_{R_S=0}$$

using (3)


$$\frac{-g_m r_o R_D}{(R_D + r_D) + R_S(1 + g_m r_o)} = \frac{1 - g_m r_o R_D}{3(R_D + r_o)}$$

$$R_S = \frac{2(R_D + r_o)}{1 + g_m r_o} = 2.185 \text{ k}\Omega$$

based on  $R_D = 15 \text{ K}$ ,  $r_o = 150 \text{ K}$ ,

$$g_m = 1 \text{ mS}$$

Ex: 5.40

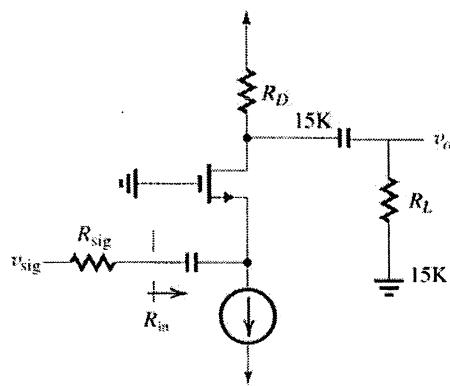

$$g_m = 1 \text{ mA/V}$$

For  $R_{sig} = 50 \Omega$

$$k_{in} = \frac{1}{g_m} = 1 \text{ k}\Omega$$

$$k_{out} = R_D = 15 \text{ k}\Omega$$

$$A_{vo} = +g_m R_D = +15$$


$$A_V = g_m (R_D \parallel R_L) = +7.5$$

$$G_V = \frac{R_{in}}{R_{sig} + R_{in}} A_V = 7.1$$

For other  $R_{sig}$

$R_{sig}$	$G_V$
1 k\Omega	3.75
10 k\Omega	0.68
100 k\Omega	0.07

Ex: 5.41

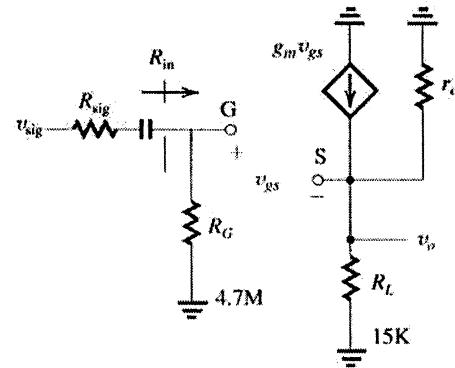

$$g_m = 1 \text{ mA/V}$$

$$r_o = 150 \text{ k}\Omega$$

$$R_{in} = R_G$$

$$A_{vo} = \frac{g_m r_o}{1 + g_m r_o}$$

$$A_V = \frac{g_m (r_o \parallel R_L)}{1 + g_m (r_o \parallel R_L)}$$

$$R_{out} = \frac{1}{g_m} \parallel r_o$$

(a)

	$r_o \rightarrow \infty$	$r_o = 150 \text{ k}\Omega$
$R_{in}$	4.7 M\Omega	4.7 M\Omega
$A_{vo}$	1.0	0.993
$A_V$	0.938	0.932
$R_{out}$	1 k\Omega	0.993 k\Omega

$$(b) G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_v = 0.768$$

Ex 5.42

See the next page

using eq. (5.107)

$$V_t = V_{to} + r\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}$$

$$V_t = 0.8 + 0.4[\sqrt{0.7 + 3} - \sqrt{.7}]$$

$$V_t = 1.23 \text{ V}$$

**Ex: 5.43**

$$V_{GS} = +1 \text{ V}, V_+ = -2 \text{ V}$$

$$V_{GS} - V_+ = 3 \text{ V}$$

TO OPERATE IN SATURATION REGION:

$$V_{DS \text{ min}} = V_{GS} - V_+ = 3 \text{ V}$$

$$i_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_+)^2$$

$$= \frac{1}{2} \times 2 \times 3^2 = 9 \text{ mA}$$

**Ex: 6.A.1** (a) The minimum value of  $I_n$  occurs when

$$V_{ov} = 0.2 \text{ V} \text{ and } \frac{W}{L} = 0.1, \text{ that is}$$

$$I_{n\min} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 \approx 0.8 \text{ }\mu\text{A}$$

The maximum value of  $I_n$  occurs when

$$V_{ov} = 0.4 \text{ V} \text{ and } \frac{W}{L} = 100, \text{ that is}$$

$$I_{n\max} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 \approx 3.1 \text{ mA}$$

(b) For a similar range of current in an npn transistor, we have

$$\begin{aligned} \frac{I_{n\max}}{I_{n\min}} &= \frac{3.1 \text{ mA}}{0.8 \text{ }\mu\text{A}} = \frac{I_S e^{V_{BE\max}/V_T}}{I_S e^{V_{BE\min}/V_T}} \\ &\Rightarrow e^{(V_{BE\max} - V_{BE\min})/V_T} = e^{\Delta V_{BE}/V_T} \\ &= \frac{3.1 \text{ mA}}{0.8 \text{ }\mu\text{A}} \end{aligned}$$

$$\Delta V_{BE} = V_T \ln\left(\frac{3.1 \text{ mA}}{0.8 \text{ }\mu\text{A}}\right) \text{ and } V_T = (25) \text{ mV}$$

$$\Rightarrow \Delta V_{BE} = 207 \text{ mV}$$

**Ex: 6.A.2** For an NMOS Fabricated in the 0.5  $\mu\text{m}$  process, with  $\frac{W}{L} = 10$ , we want to find the transconductance and the intrinsic gain obtained for the following drain currents: ( $L = 0.5 \mu\text{m}$ )

$$I_D = (10) \text{ }\mu\text{A}, g_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)} I_D.$$

$$\mu_n C_{ox} = (190) \frac{\mu\text{A}}{\text{V}^2}$$

$$g_m = \sqrt{2 \times 190 \times 10 \times 10} \approx 0.2 \frac{\text{mA}}{\text{V}}$$

$$r_o = \frac{V_A}{I_D} = \frac{V_A' L}{I_D} = \frac{20 \times 0.5}{10 \text{ }\mu\text{A}} = 1 \text{ M}\Omega$$

intrinsic gain

$$\approx g_m r_o = 0.2 \frac{\text{mA}}{\text{V}} \times 1 \text{ M}\Omega = 200 \frac{\text{V}}{\text{V}}$$

For  $I_D = 100 \mu\text{A}$  we have:

$$g_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)} I_D = \sqrt{2 \times 190 \times 10 \times 100}$$

$$g_m = 0.62 \frac{\text{mA}}{\text{V}} \approx 0.6 \frac{\text{mA}}{\text{V}}$$

$$r_o = \frac{V_A' L}{I_D} = \frac{20 \times 0.5}{100 \text{ }\mu\text{A}} = 100 \text{ k}\Omega$$

$$g_m r_o = 0.62 \frac{\text{mA}}{\text{V}} \times 100 \text{ k}\Omega = 62 \text{ V/V}$$

For  $I_D = 1 \text{ mA}$

$$\begin{aligned} g_m &= \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)} I_D \\ &= \sqrt{2 \times 190 \times 10 \times 1} \approx 2 \frac{\text{mA}}{\text{V}} \end{aligned}$$

$$\begin{aligned} r_o &= \frac{V_A' L}{I_D} = \frac{20 \times 0.5}{1 \text{ mA}} = 10 \text{ k}\Omega \\ g_m r_o &= 2 \frac{\text{mA}}{\text{V}} \times 10 \text{ k}\Omega = 20 \text{ V/V} \end{aligned}$$

**Ex: 6.A.3** For an NMOS fabricated in the 0.5  $\mu\text{m}$  CMOS technology specified in Table 7.A.1 with  $L = 0.5 \mu\text{m}$ ,  $W = 5 \mu\text{m}$ , and  $V_{ov} = 0.3 \text{ V}$

We have

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 = \frac{1}{2} 190 \frac{\mu\text{A}}{\text{V}^2} \times \frac{5}{0.5} \times 0.3^2$$

$$I_D = 85.5 \text{ }\mu\text{A}$$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 85.5 \text{ }\mu\text{A}}{0.3 \text{ V}} = 0.57 \text{ mA/V}$$

$$r_o = \frac{V_A' L}{I_D} = \frac{20 \times 0.5}{85.5 \text{ }\mu\text{A}} \approx 117 \text{ k}\Omega$$

$$A_o = g_m r_o = 66.7 \text{ V/V}$$

$$C_{gs} = \frac{2}{3} WLC_{ox} + C_{ov}$$

$$\approx \frac{2}{3} \times 5 \times 0.5 \times 3.8 + 0.4 \times 5$$

$$C_{gs} = 8.3 \text{ fF}, C_{gd} = C_{ov} W = 0.4 \times 5 = 2 \text{ fF}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} = \frac{0.57 \text{ mA}}{2\pi(8.3 + 2)}$$

$$f_T = 8.8 \text{ GHz}$$

**Ex: 6.1**

For this problem, use eq. 6.11

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)} \cdot \sqrt{I_D}$$

For  $I_D = 10 \mu\text{A}$ ,

$$g_m = \sqrt{2(387 \mu\text{A/V}^2)(10)(10 \mu\text{A})} = 0.28 \text{ mA/V}$$

using eq. 6.15

$$\begin{aligned} A_O &= V_A' \sqrt{\frac{2\mu_n C_{ox}(WL)}{I_D}} \\ &= 5 \text{ V/}\mu\text{m} \sqrt{\frac{2(387 \mu\text{A/V}^2)(10)(.36)^2}{10 \mu\text{A}}} \end{aligned}$$

$$A_O = 50 \text{ V/V}$$

Since  $g_m$  varies with  $\sqrt{I_D}$  and  $A_O$  with  $\frac{1}{\sqrt{I_D}}$

For

$$I_D = 100 \mu\text{A} \Rightarrow g_m = 0.28 \text{ mA} \left( \frac{100}{10} \right)^{\frac{1}{2}} = .89 \text{ mA/V}$$


$$A_O = 50 \left( \frac{100}{100} \right)^{\frac{1}{2}} = 158 \text{ V/V}$$

For  $I_D = 1 \text{ mA}$ :

$$g_m = .28 \text{ mA/V} \left( \frac{1}{.010} \right)^{\frac{1}{2}} = 2.8 \text{ mA/V}$$

$$A_O = 50 \left( \frac{.010}{1} \right)^{\frac{1}{2}} = 5 \text{ V/V}$$

Ex: 6.2

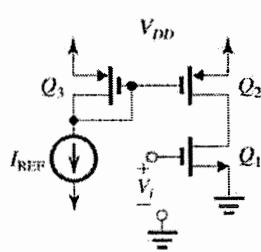

Since all transistors have the same

$$\frac{W}{L} = \frac{7.2 \mu\text{m}}{0.36 \mu\text{m}},$$

we have

$$I_{REF} = I_{D3} = I_{D2} = I_{D1} = 100 \mu\text{A}$$

$$g_m = \sqrt{2 \mu_n C_{ov} \left( \frac{W}{L} \right)} \sqrt{I_{D1}}$$

$$= \sqrt{2(387 \mu\text{A/V}^2) \left( \frac{7.2}{0.36} \right)} (100 \mu\text{A})$$

$$\approx 1.24 \text{ mA/V}$$

$$r_{o1} = \frac{V_A p L_1}{I_{D1}} = \frac{5 \text{ V}/\mu\text{m} (0.36 \mu\text{m})}{0.1 \text{ mA}} = 18 \text{ k}\Omega$$

$$r_{o2} = \frac{|V_{AP}| L_2}{I_{D2}} = \frac{6 \text{ V}/\mu\text{m} (0.36 \mu\text{m})}{0.1 \text{ mA}} = 21.6 \text{ k}\Omega$$


Voltage Gain is

$$A_V = -g_m (r_{o1} \parallel r_{o2})$$

$$A_V = -(1.24 \text{ mA/V}) (18 \text{ k}\Omega \parallel 21.6 \text{ k}\Omega)$$

$$= -12.2 \text{ V/V}$$

Ex: 6.3

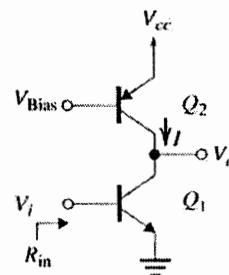

$$I_C = I = 100 \mu\text{A}$$

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.1 \mu\text{A}}{25 \text{ mV}} = 4 \text{ mA/V}$$

$$R_{in} = r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{100}{4 \text{ mA/V}} = 25 \text{ k}\Omega$$

$$r_{o1} = \frac{V_A}{I} = \frac{50 \text{ V}}{0.1 \text{ mA}} = 500 \text{ k}\Omega$$

$$r_{o2} = \frac{|V_A|}{I} = \frac{50 \text{ V}}{0.1 \text{ mA}} = 500 \text{ k}\Omega$$

$$A_O = g_{m1} r_{o1} = (4 \text{ mA/V}) (500 \text{ k}\Omega) = 2000 \text{ V/V}$$

$$A_V = -g_{m1} (r_{o1} \parallel r_{o2}) = -(4 \text{ mA/V})$$

$$(500 \text{ k}\Omega \parallel 500 \text{ k}\Omega) = -1000 \text{ V/V}$$

Ex: 6.4 If  $L$  is halved:  $L = \frac{0.55 \mu\text{m}}{2}$ , and

$$|V_A| = |V_A| \cdot L,$$

$$|V_A| = 5 \text{ V}/\mu\text{m} \frac{(0.55 \mu\text{m})}{2} = 1.375 \text{ V}$$

$$R_o = \frac{|V_A|}{|V_{ov}|/2} \cdot \frac{|V_A|}{I_D} = \frac{2 (1.375 \text{ V})^2}{(0.3 \text{ V}) (100 \mu\text{A})}$$


$$= 126 \text{ k}\Omega$$

$$\text{Since } I_D = \frac{1}{2} (\mu_n C_{ov}) \left( \frac{W}{L} \right) |V_{ov}|^2 \left( 1 + \frac{V_{SD}}{|V_A|} \right)$$

$$\frac{W}{L} = \frac{2 (100 \mu\text{A})}{90 \mu\text{A/V}^2 (0.3 \text{ V})^2 \left( 1 + \frac{0.3 \text{ V}}{1.375 \text{ V}} \right)}$$

$$\frac{W}{L} = 20.3$$

Ex: 6.5

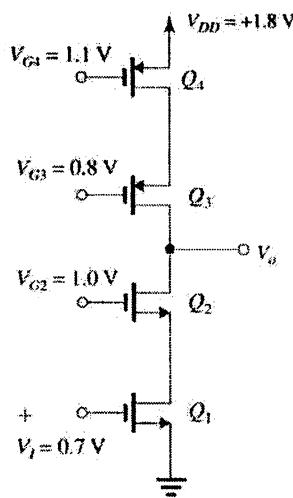

If all transistors are identical and the gate voltages are fixed,  $|V_{ov}| = 0.7 - 0.5 = 0.2 \text{ V}$

$$V_{D1} = V_{S2} = V_{G2} - V_{ov} = 0.2 \text{ V}$$

$$= 1.0 - 0.5 - 0.2 = 0.3 \text{ V}$$

the lowest  $V_{DS2}$  can go is  $|V_{ov}| = 0.2 \text{ V}$

$$\therefore V_{ov\min} = V_{DS1} + V_{DS2} = 0.3 + 0.2 = 0.5 \text{ V}$$

Similarly,  $V_{SG4} = V_{SG3} = 0.7 \text{ V}$

$$V_{D4} = V_{S3} = V_{G3} + |V_i| + |V_{ov}|$$

$$= 0.8 + 0.5 + 0.2 = 1.5 \text{ V}$$

$V_{SD3}$  can go as low as  $|V_{ov}|$ , so

$$V_{ov\max} = V_{D4} - V_{SD3\min} = 1.5 - 0.2 = 1.3 \text{ V}$$

Ex: 6.6  $g_{m1} = g_{m2} = g_{m3} = g_{m4} = g_m$

$$= \frac{I_D}{|V_{ov}|} = \frac{0.2 \text{ mA}}{0.2 \text{ V}/2} = 2 \text{ mA/V}$$

$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = r_o$$

$$= \frac{|V_A|}{I_D} = \frac{2 \text{ V}}{0.2 \text{ mA}} = 10 \text{ k}\Omega$$

$$R_{on} = (g_{m2}r_{o1})r_{o3} = (2 \text{ mA/V})(10 \text{ k}\Omega)^2$$

$$= 200 \text{ k}\Omega$$

$$R_{op} = (g_{m3}r_{o2})(r_{o4}) = (2 \text{ mA/V})(10 \text{ k}\Omega)^2$$

$$= 200 \text{ k}\Omega$$

$$R_o = R_{on} \parallel R_{op} = 100 \text{ k}\Omega$$

$$Av = -\frac{1}{2}(g_{m2}r_o)^2 = -\frac{1}{2}[(2 \text{ mA/V})(10 \text{ k}\Omega)]^2$$

$$Av = -200 \text{ V/V}$$

$$\text{Ex: 6.7 } g_m = \frac{I_D}{V_{ov}} = \frac{0.25 \text{ mA}}{0.25 \text{ V}/2}$$

$$= 2 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{5 \text{ V}}{0.25 \text{ mA}} = 20 \text{ k}\Omega$$

(a) From Fig. 6.13

$$R_{in} = \frac{1}{g_m} + \frac{R_L}{(g_m r_o)}$$

$$R_L = \infty:$$

$$R_{in} = \frac{1}{2 \text{ mA/V}} + \frac{R_L}{(2 \text{ mA/V})(20 \text{ k}\Omega)}$$

$$= 500 \text{ }\Omega + \frac{\infty}{40} \rightarrow \infty$$

$$R_L = 1 \text{ M}\Omega:$$

$$R_{in} = 500 \text{ }\Omega + \frac{1 \text{ M}\Omega}{40} = 25.5 \text{ k}\Omega$$

$$R_L = 100 \text{ k}\Omega:$$

$$R_{in} = 500 \text{ }\Omega + \frac{100 \text{ k}\Omega}{40} = 3 \text{ k}\Omega$$

$$R_L = 20 \text{ k}\Omega:$$

$$R_{in} = 500 \text{ }\Omega + \frac{20 \text{ k}\Omega}{40} = 1 \text{ k}\Omega$$

$$R_L = 0:$$

$$R_{in} = 500 \text{ }\Omega + \frac{0}{40} = 0.5 \text{ k}\Omega$$

(b) From Fig. 6.13

$$R_O = r_o + R_S + (g_m r_o)R_S$$

$$R_S = 0:$$

$$R_O = 20 \text{ k}\Omega + 0 + (40)(0) = 20 \text{ k}\Omega$$

$$R_S = 1 \text{ k}\Omega:$$

$$R_O = 20 \text{ k}\Omega + 1 \text{ k}\Omega + (40)(1 \text{ k}\Omega) = 61 \text{ k}\Omega$$

$$R_S = 10 \text{ k}\Omega:$$

$$R_O = 20 \text{ k}\Omega + 10 \text{ k}\Omega + (40)(10 \text{ k}\Omega) = 430 \text{ k}\Omega$$

$$R_S = 20 \text{ k}\Omega:$$

$$R_O = 20 \text{ k}\Omega + 20 \text{ k}\Omega + (40)(20 \text{ k}\Omega) = 840 \text{ k}\Omega$$

$$R_S = 100 \text{ k}\Omega:$$

$$R_O = 20 \text{ k}\Omega + 100 \text{ k}\Omega + (40)(100 \text{ k}\Omega) = 4.12 \text{ M}\Omega$$

Ex: 6.8  $g_{m1} = g_{m2} = g_m$

$$= \frac{I_D}{V_{ov}} = \frac{100 \mu\text{A}}{0.2 \text{ V}/2} = 1 \text{ mA/V}$$

$$r_{o1} = r_{o2} = r_o$$

$$= \frac{V_A}{I_D} = \frac{2 \text{ V}}{0.1 \text{ mA}} = 20 \text{ k}\Omega$$

so,  $(g_m r_o) = 1 \text{ mA/V}(20 \text{ k}\Omega) = 20$

(a) For  $R_L = 20 \text{ k}\Omega$ ,

$$R_{in2} = \frac{R_L + r_{o2}}{1 + g_m r_{o2}} = \frac{20 \text{ k}\Omega + 20 \text{ k}\Omega}{1 + 20} = 1.9 \text{ k}\Omega$$

$$\therefore A_{V1} = -g_m(r_{o1} \parallel R_{in2})$$

$$= -1 \text{ mA/V}(20 \text{ k}\Omega \parallel 1.9 \text{ k}\Omega) = -1.74 \text{ V/V}$$

or

If we use the approximation of eq. 6.35

$$R_{in2} \approx \frac{R_L}{g_m r_{o2}} + \frac{1}{g_m} = \frac{20 \text{ k}\Omega}{20} + \frac{1}{1 \text{ mA/V}} \\ = 2 \text{ k}\Omega$$

then,

$$A_{V1} = -1 \text{ mA/V}(20 \text{ k}\Omega \parallel 2 \text{ k}\Omega) = -1.82 \text{ V/V}$$

Either method is correct.

continuing, from eq. 6.31

$$A_V = -g_m [(g_m r_{o2} r_{o1}) \parallel R_L]$$

$$A_V = -1 \text{ mA/V} \{ [(20)(20 \text{ k}\Omega)] \parallel 20 \text{ k}\Omega \} \\ = -19.04 \text{ V/V}$$

$$A_{V2} = \frac{A_V}{A_{V1}} = \frac{-19.04}{-1.82} = 10.5 \text{ V/V}$$

(b) Now, for  $R_L = 400 \text{ k}\Omega$ ,


$$R_{in2} \approx \frac{R_L}{g_m r_{o2}} + \frac{1}{g_m} = \frac{400 \text{ k}\Omega}{20} + \frac{1}{1 \text{ mA/V}} \\ = 21 \text{ k}\Omega$$

$$A_{V1} = -1 \text{ mA/V}(20 \text{ k}\Omega \parallel 21 \text{ k}\Omega) = -10.2 \text{ V/V}$$

$$A_V = -1 \text{ mA/V} \{ [(20)(20 \text{ k}\Omega)] \parallel 400 \text{ k}\Omega \} \\ = -200 \text{ V/V}$$

$$A_{V2} = \frac{A_V}{A_{V1}} = \frac{-200}{-10.2} = 19.6 \text{ V/V}$$

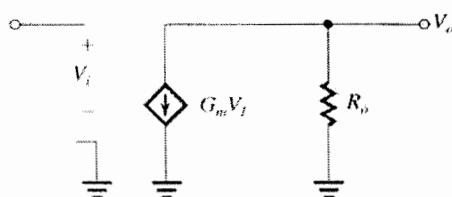**Ex: 6.9** The circuit of Fig. 6.14 can be modeled as



$$\text{Where } G_m = \frac{g_m}{1 + g_m R_s}$$

$$\text{and } R_o \approx (1 + g_m R_s) r_o$$

The open-circuit (no load) Voltage gain is

$$Av_o = -G_m R_o = \frac{g_m}{1 + g_m R_s} \cdot (1 + g_m R_s) r_o$$


$$= -g_m R_o$$

so, the gain remains the same

If  $R_L$  is connected to the output,

$$Av = \frac{-g_m}{1 + g_m R_s} [(1 + g_m R_s) r_o] \parallel R_L \\ = \frac{-g_m}{1 + g_m R_s} \cdot \frac{(1 + g_m R_s) r_o R_L}{(1 + g_m R_s) r_o + R_L} \\ = -\frac{R_L}{R_L + (1 + g_m R_s) r_o}$$

**Ex: 6.10**

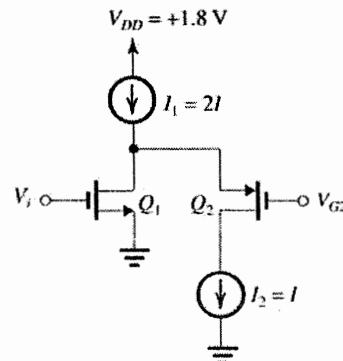

$$(a) I_m = I \text{ and } I_{o2} = I$$

Since  $V_{ov1} = V_{ov2} = 0.2 \text{ V}$  we have

$$\frac{I_{D2}}{I_{D1}} = \frac{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 V_{ov2}^2}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 V_{ov1}^2} = \frac{I}{I} = 1$$

and

$$\frac{k_p \left(\frac{W}{L}\right)_2}{k_n \left(\frac{W}{L}\right)_1} = 1 \Rightarrow \left(\frac{W}{L}\right)_2 = \frac{k_n}{k_p} \left(\frac{W}{L}\right)_1 = \frac{k_n}{k_p} \left(\frac{W}{L}\right)_1 = \frac{1}{4}$$

or

$$\left(\frac{W}{L}\right)_2 = 4 \left(\frac{W}{L}\right)_1$$

(b) The minimum voltage allowed across current source  $I_1$  would be  $|V_{ov1}| = 0.2 \text{ V}$  if made with a single transistor. If a 0.1  $V_{pp}$  signal swing is to be allowed at the drain of  $Q_1$ , the highest dc bias voltage would be

$$V_{DD} - |V_{ov1}| - \frac{0.1 \text{ V}_{pp}}{2} = 1.8 - 0.2 - \frac{1}{2} (0.1) \\ = 1.55 \text{ V}$$

$$(c) V_{SG2} = |V_{ov1}| + |V_{tp}| = 0.2 + 0.5 = 0.7 \text{ V}$$

$V_{GS2}$  can be set at  $1.55 - 0.7 = 0.85 \text{ V}$

(d) Since current source  $I_2$  is implemented with a cascaded current source similar to Fig.6.10, the minimum voltage required across it for proper operation is  $2V_{ov} = 2(0.2 \text{ V}) = 0.4 \text{ V}$

(e) From parts (c) and (d), the allowable range of signal swing at the output is from 0.4 V to 1.55 V  $\rightarrow V_{ov}$  or 1.35 V.

so,  $0.4 \text{ V} \leq V_o \leq 1.35 \text{ V}$

Ex:6.11 Referring to fig. 6.19,

$$R_{op} = (g_m r_{o3})(r_{o4} \parallel r_{\pi3}) \quad \text{and}$$

$$R_{on} = (g_m r_{o2})(r_{o3} \parallel r_{\pi2})$$

If  $Q_1$  and  $Q_4$  can be selected and biased so that  $r_{o1}$  and  $r_{o4}$  are very high and have insignificant effect ( $r_o \gg r_\pi$ ) then,

$$R_{on} = (g_m r_{o2})r_{\pi2}$$

$$R_{op} = (g_m r_{o3})r_{\pi3}$$

Since  $g_m r_\pi = \beta$ ,

$$R_{on} = \beta_2 r_{o2}$$

$$R_{op} = \beta_3 r_{o3}$$

Since  $A_v = -g_m(R_{on} \parallel R_{op})$ ,

$$|Av_{max}| = g_m(\beta_2 r_{o2} \parallel \beta_3 r_{o3})$$

Ex:6.12 For the npn transistors,

$$g_{m1} = g_{m2} = \frac{|I_C|}{V_T} = \frac{0.2 \text{ mA}}{25 \text{ mV}} = 8 \text{ mA/V}$$

$$r_{\pi1} = r_{\pi2} = \frac{\beta}{g_m} = \frac{100}{8 \text{ mA/V}} = 12.5 \text{ k}\Omega$$

$$r_{o1} = r_{o2} = \frac{|V_A|}{|I_C|} = \frac{5 \text{ V}}{0.2 \text{ mA}} = 25 \text{ k}\Omega$$

From Fig. 6.19,

$$R_{on} = (g_m r_{o2})(r_{o1} \parallel r_{\pi2}) \\ = (8 \text{ mA/V})(25 \text{ k}\Omega)(25 \text{ k}\Omega \parallel 12.5 \text{ k}\Omega)$$

$$R_{on} = 1.67 \text{ M}\Omega$$

For the pnp transistors,

$$g_{m3} = g_{m4} = \frac{|I_C|}{V_T} = \frac{0.2 \text{ mA}}{25 \text{ mV}} = 8 \text{ mA/V}$$

$$r_{\pi3} = r_{\pi4} = \frac{\beta}{g_m} = \frac{50}{8 \text{ mA/V}} = 6.25 \text{ k}\Omega$$

$$r_{o3} = r_{o4} = \frac{|V_A|}{|I_C|} = \frac{4 \text{ V}}{0.2 \text{ mA}} = 20 \text{ k}\Omega$$

$$R_{op} = (g_{m3} r_{o3})(r_{o4} \parallel r_{\pi3}) \\ = (8 \text{ mA/V})(20 \text{ k}\Omega)(20 \text{ k}\Omega \parallel 6.25 \text{ k}\Omega)$$

$$R_{op} = 762 \text{ k}\Omega$$

$$A_v = -g_{m1}(R_{on} \parallel R_{op}) \\ = -(8 \text{ mA/V})(1.67 \text{ M}\Omega \parallel 0.762 \text{ M}\Omega)$$

$$A_v = -4.186 \text{ V/V}$$

$Av_{max}$  occurs when  $Q_1$  and  $Q_4$  are selected and bias so that  $r_{o1}$  and  $r_{o4}$  are  $\gg r_\pi$

$$\text{Then, } R_{on} = (g_{m2} r_{o2})r_{\pi2} = \beta_2 r_{o2}$$

$$R_{on} = 100(25 \text{ k}\Omega) = 2.5 \text{ M}\Omega$$

$$R_{op} = (g_{m3} r_{o3})r_{\pi3} = \beta_3 r_{o3}$$

$$R_{op} = 50(20 \text{ k}\Omega) = 1 \text{ M}\Omega$$

Finally,

$$A_{vmax} = -(8 \text{ mA/V})(2.5 \text{ M}\Omega \parallel 1.0 \text{ M}\Omega)$$

$$A_{vmax} = -5714 \text{ V/V}$$

Ex:6.13  $g_m = \frac{|I_C|}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mA/V}$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40 \text{ mA/V}} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{10 \text{ V}}{1 \text{ mA}} = 10 \text{ k}\Omega$$

Referring to Fig. 6.20,

$$R_o \approx r_o[1 + g_m(R_e \parallel r_\pi)]$$

$$R_o \approx 10 \text{ k}\Omega \left[ 1 + 40 \frac{\text{mA}}{\text{V}} (0.5 \text{ k}\Omega \parallel 2.5 \text{ k}\Omega) \right]$$

$$R_o \approx 176.7 \text{ k}\Omega$$

without  $R_e$  (that is,  $R_e = 0$ ).

$$R_o = r_o = 10 \text{ k}\Omega$$

Ex:6.14 Fig.6.21(a)

$$r_{o1} = r_{o2} = r_o = \frac{V_A}{I} = \frac{5 \text{ V}}{0.1 \text{ mA}} = 50 \text{ k}\Omega$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} (W/L) I_D}$$

$$g_{m1} = \sqrt{2(200 \text{ }\mu\text{A/V}^2)(25)(100 \text{ }\mu\text{A})}$$

$$g_{m1} = \frac{1 \text{ mA}}{V} \text{, } G_m = g_{m1} = 1 \text{ mA/V}$$

$$g_{m2} = \frac{|I_C|}{V_T} = \frac{0.1 \text{ mA}}{25 \text{ mV}} = 4 \text{ mA/V}$$

$$r_{\pi2} = \frac{\beta}{g_{m2}} = \frac{100}{4 \text{ mA/V}} = 25 \text{ k}\Omega$$

Assuming an ideal current source,


$$R_o = (g_{m2} r_{o2})(r_{o1} \parallel r_{\pi2})$$

$$R_o = (4 \text{ mA/V})(50 \text{ k}\Omega)(50 \text{ k}\Omega \parallel 25 \text{ k}\Omega) = 3.33 \text{ M}\Omega$$

$$A_{vO} = -G_m R_o = -(1 \text{ mA/V})(3.33 \text{ M})$$

$$= -3.33 \times 10^3 \text{ V/V}$$

Fig. 7.21 (b)

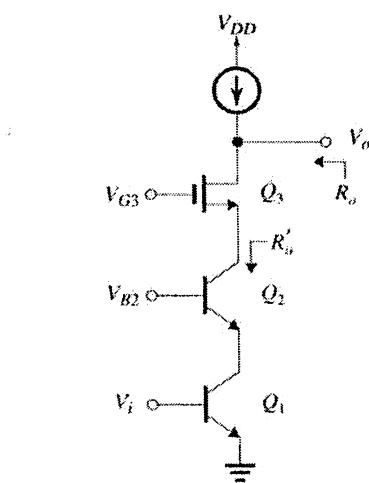

From part (a),

$$g_{m3} = 1 \text{ mA/V}$$

$$g_{m4} = g_{m2} = 4 \text{ mA/V}$$

$$r_{o3} = r_{o2} = r_{o1} = r_o = 50 \text{ k}\Omega$$

$$r_{\pi1} = r_{\pi2} = r_\pi = 25 \text{ k}\Omega$$

$$G_m \approx g_{m1} = 4 \text{ mA/V}$$

From Fig. 6.19  $R'_o = (g_{m2}r_{o2})(r_{o1} \parallel r_{\pi2})$

$$R_o = (g_{m3}r_{o3})R'_o \text{ so,}$$

$$R_o = (1 \text{ mA/V})(50 \text{ k}\Omega)(4 \text{ mA/V})(50 \text{ k}\Omega)$$

$$(50 \text{ k}\Omega \parallel 25 \text{ k}\Omega)$$

$$R_o = 167 \text{ M}\Omega$$

$$A_{vo} = -g_{m1}R_o = -4 \text{ mA/V}(167 \text{ M}\Omega)$$

$$\approx -668 \times 10^3 \text{ V/V}$$

**Ex:6.15** In the current source of Example 6.15 we have  $I_O = 100 \mu\text{A}$  and we want to reduce the change in output current,  $\Delta I_O$ , corresponding to a 1 V change in output voltage,  $\Delta V_O$ , to 1% of  $I_O$ .

$$\text{That is } \Delta I_O = \frac{\Delta V_O}{r_{o2}} = 0.01I_O \Rightarrow \frac{1 \text{ V}}{r_{o2}}$$

$$= 0.01 \times 100 \mu\text{A}$$

$$r_{o2} = \frac{1 \text{ V}}{1 \mu\text{A}} = 1 \text{ M}\Omega$$

$$r_{o2} = \frac{V_A \times L}{I_O} \Rightarrow 1 \text{ M}\Omega = \frac{20 \times L}{100 \mu\text{A}}$$

$$\Rightarrow L = \frac{100 \text{ V}}{20 \text{ V}/\mu\text{m}} = 5 \text{ }\mu\text{m}$$

To keep  $V_{OV}$  of the matched transistors the same as that of Example 6.15  $\frac{W}{L}$  of the transistor should remain the same. Therefore

$$\frac{W}{5 \mu\text{m}} = \frac{10 \mu\text{m}}{1 \mu\text{m}} \Rightarrow W = 50 \mu\text{m}$$

So the dimensions of the matched transistors  $Q_1$  and  $Q_2$  should be changed to:

$$W = 50 \mu\text{m} \text{ and } L = 5 \mu\text{m}$$

**Ex:6.16** For the circuit Figure 4.7 we have:

$$I_2 = I_{REF} \frac{(W/L)_2}{(W/L)_1}, I_3 = I_{REF} \frac{(W/L)_3}{(W/L)_1}$$

$$\text{and } I_5 = I_4 \frac{(W/L)_5}{(W/L)_4}$$

Since all channel lengths are equal

$$L_1 = L_2 = \dots = L_5 = 1 \mu\text{m}$$

and

$$I_{REF} = 10 \mu\text{A}, I_2 = 60 \mu\text{A}, I_3 = 20 \mu\text{A},$$

$$I_4 = I_5 = 20 \mu\text{A} \text{ and } I_5 = 80 \mu\text{A},$$

we have:

$$I_2 = I_{REF} \frac{W_2}{W_1} \Rightarrow \frac{W_2}{W_1} = \frac{I_2}{I_{REF}} = \frac{60}{10} = 6$$

$$I_3 = I_{REF} \frac{W_3}{W_1} \Rightarrow \frac{W_3}{W_1} = \frac{I_3}{I_{REF}} = \frac{20}{10} = 2$$

$$I_5 = I_4 \frac{W_5}{W_4} \Rightarrow \frac{W_5}{W_4} = \frac{I_5}{I_4} = \frac{80}{10} = 4$$

In order to allow the voltage at the drain of  $Q_2$  to go down to within 0.2 V of the negative supply voltage we need  $V_{OV2} = 0.2 \text{ V}$

$$I_2 = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 V^2_{OV2} = \frac{1}{2} k_n \left( \frac{W}{L} \right)_2 V^2_{OV2}$$

$$60 \mu\text{A} = \frac{1}{2} 200 \frac{\mu\text{A}}{\text{V}^2} \left( \frac{W}{L} \right)_2 (0.2)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_2 = \frac{120}{200 \times (0.2)^2} = 15 \Rightarrow W_2 = 15 \times L_2$$

$$W_2 = 15 \mu\text{m}, \frac{W_2}{W_1} = 6 \Rightarrow W_1 = \frac{W_2}{6} = 2.5 \mu\text{m}$$

$$\frac{W_3}{W_1} = 2 \Rightarrow W_3 = 2 \times W_1 = 5 \mu\text{m}$$

In order to allow the voltage at the drain of  $Q_5$  to go up to within 0.2 V of positive supply we need

$$V_{OV5} I_5 = \frac{1}{2} k_p \left( \frac{W}{L} \right)_5 V^2_{OV2} \Rightarrow V^2_{OV2}$$

$$80 \mu\text{A} = \frac{1}{2} 80 \frac{\mu\text{A}}{\text{V}^2} \left( \frac{W}{L} \right)_5 (0.2)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_5 = \frac{2 \times 80}{80 \times (0.2)^2} = 50 \Rightarrow W_5 = 50 L_5$$

$$W_5 = 50 \mu\text{m}$$

$$\frac{W_5}{W_4} = 4 \Rightarrow W_4 = \frac{50 \mu\text{m}}{4} = 12.5 \mu\text{m}$$

Thus:

$$W_1 = 2.5 \mu\text{m}, W_2 = 15 \mu\text{m}, W_3 = 5 \mu\text{m}$$

$$W_4 = 12.5 \mu\text{m} \text{ and } W_5 = 50 \mu\text{m}$$

**Ex: 6.19**

See next page:

**Ex:6 .17** From equation 6 .72 we have:


$$I_o = I_{\text{REF}} \left( \frac{m}{1 + \frac{m+1}{\beta}} \right) \left( 1 + \frac{V_o - V_{BE}}{V_A} \right)$$

$$I_o = 1 \text{ mA} \left( \frac{1}{1 + \frac{1+1}{100}} \right) \left( 1 + \frac{5 - 0.7}{100} \right) = 1.02 \text{ mA}$$

$$I_o = 1.02 \text{ mA}$$

$$R_O = r_{O2} = \frac{V_A}{I_o} = \frac{100 \text{ V}}{1.02 \text{ mA}} = 98 \text{ k}\Omega \approx 100 \text{ k}\Omega$$

**Ex:6 .18**

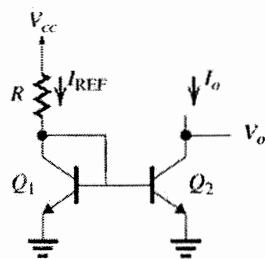

From equation 6 .74 we have:

$$I_o = \frac{I_{\text{REF}}}{1 + (2/\beta)} \left( 1 + \frac{V_o - V_{BE}}{V_A} \right) \Rightarrow$$

$$0.5 \text{ mA} = \frac{I_{\text{REF}}}{1 + (2/100)} \left( 1 + \frac{2 - 0.7}{50} \right) \Rightarrow$$

$$I_{\text{REF}} = 0.5 \text{ mA} \frac{1.02}{1.026 \text{ mA}} = 0.497 \text{ mA}$$

$$I_{\text{REF}} = \frac{V_{CC} - V_{BE}}{R} \Rightarrow R = \frac{V_{CC} - V_{BE}}{I_{\text{REF}}}$$


$$R = \frac{5 - 0.7}{0.497 \text{ mA}} = \frac{4.3}{0.497} 8.65 \text{ k}\Omega$$

$$V_{O\min} = V_{CESAT} \approx 0.3 \text{ V}$$

For  $V_o = 5 \text{ V}$ , From equation 6 .74 we have:

$$I_o = \frac{I_{\text{REF}}}{1 + (2/\beta)} \left( 1 + \frac{V_o - V_{BE}}{V_A} \right)$$
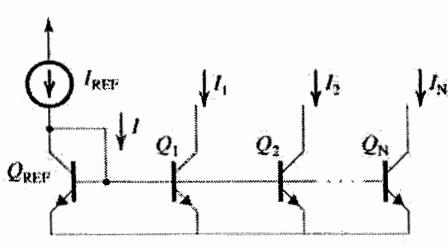
$$I_o = \frac{0.497}{1 + (2/100)} \left( 1 + \frac{5 - 0.7}{50} \right) = 0.53 \text{ mA}$$



$$I_{\text{REF}} = I_{CQ_{\text{REF}}} + I_{CQ_{\text{REF}}} \frac{N+1}{\beta}$$

$$\Rightarrow I_{CQ_{\text{REF}}} = \frac{I_{\text{REF}}}{1 + \frac{N+1}{\beta}}$$

Thus:

$$I_1 = I_2 = \dots = I_N = \frac{I_{\text{REF}}}{1 + \frac{N+1}{\beta}}$$

For an error not exceeding 10% we need:

$$\frac{I_{\text{REF}}}{1 + \frac{N+1}{\beta}} \geq I_{\text{REF}}(1 - 0.1)$$

$$\frac{I_{\text{REF}}}{1 + \frac{N+1}{\beta}} \geq 0.9 I_{\text{REF}} \Rightarrow \frac{1}{1 + \frac{N+1}{\beta}} \geq 0.9$$

$$\Rightarrow 1 + \frac{N+1}{\beta} \leq \frac{1}{0.9} \Rightarrow 1 + \frac{N+1}{\beta} \leq 1.11$$

$$\frac{N+1}{\beta} \leq 0.11 \Rightarrow N+1 \leq 0.11 \beta \Rightarrow$$

$$N+1 \leq 11 \Rightarrow N \leq 10$$

The maximum number of outputs for an error not exceeding to be less than 10% then we need  $N < 10$ .

In this case the maximum number of outputs for an error of less than 10% is  $N = 9$ .

**Ex: 6.20** Referring to Fig. 6.3.2

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_{REF} = 100 \mu A$$

$$\text{Since } I_D = \frac{1}{2} \mu_n C_{ov} \left( \frac{W}{L} \right) V_{ov}^2$$

$$V_{ov} = \sqrt{\frac{2I_D}{\mu_n C_{ov} \left( \frac{W}{L} \right)}} = \sqrt{\frac{2(100 \mu A)}{(387 \mu A/V^2) \left( \frac{3.6}{0.36} \right)}}$$

$$= 0.23 V$$

The minimum output voltage is

$$V_{kn} + 2V_{op} = 0.5 V + 2(0.23 V) = 0.96 V$$

To obtain the output resistance,  $R_O$ , we need  $g_{m3}$ .

$$g_{m3} = \frac{I_{D3}}{V_{ov}/2} = \frac{2(0.1 mA)}{0.23 V} = 0.87 mA/V$$

$$r_{o3} = r_{o2} = \frac{V_A(L)}{I_D} = \frac{(5V/\mu m)(0.36 \mu m)}{0.1 mA} = 18 k\Omega$$

From eq. 6.77

$$R_o \approx g_{m3} r_{o3} r_{o2} = (0.87 mA/V)(18 k\Omega)^2$$

$$= 282 k\Omega$$

**Ex:** For the Wilson mirror from the equation

6.80 we have :

$$\frac{I_o}{I_{REF}} = \frac{1}{1 + \frac{2}{\beta(\beta + 2)}} = 0.9998$$

$$\text{Thus } \frac{|I_o - I_{REF}|}{I_{REF}} \times 100 = 0.02\%$$

whereas for the simple mirror from equation 6.69 we have :

$$\frac{I_o}{I_{REF}} = \frac{1}{1 + \frac{2}{\beta}} = 0.98$$

$$\text{Hence } \frac{|I_o - I_{REF}|}{I_{REF}} \times 100 = 2\%$$

For the Wilson current mirror we have

$$R_o = \frac{\beta r_o}{2} = \frac{100 \times 100 k\Omega}{2} = 5 M\Omega \text{ and for}$$

the simple mirror  $R_o = r_o = 100 k\Omega$

**Ex: 6.22** For the two current sources designed in Example 6.6 we have :

$$g_m = \frac{I_C}{V_T} = \frac{10 \mu A}{25 mV} = 0.4 mA/V \text{ and}$$

$$r_o = \frac{V_A}{I_C} = \frac{100 V}{10 \mu A} = 10 M\Omega, r_n = \frac{\beta}{g_m} = 250 k\Omega$$

For the current source in Fig. 6.37a we have

$$R_o = r_{o2} = r_o = 10 M\Omega$$

For the current source in Fig. 6.37b from equation 6.98 we have:

$$R_o \approx [1 + g_m(R_E \parallel r_n)]r_o$$

In Example 6.6  $R_E = R_3 = 11.5 k\Omega$ , therefore,

$$R_o \approx [1 + 0.4 \frac{mA}{V} (11.5 k\Omega \parallel 250 k\Omega)] 10 M\Omega \\ \Rightarrow R_o = 54 M\Omega$$

**Ex: 7 . 1**

Referring to Fig 7 . 3

If  $R_D$  is doubled to 5 K,

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D$$

$$= 1.5 - \frac{0.4 \text{ mA}}{2} (5 \text{ K}) = 0.5 \text{ V}$$

$$V_{CM_{max}} = V_i + V_D = 0.5 + 0.5 = + 1.0 \text{ V}$$

Since the currents  $I_{D1}$  and  $I_{D2}$  are still 0.2 mA each,

$$V_{GS} = 0.82 \text{ V}$$

$$\text{So, } V_{CM_{min}} = V_{SS} + V_{GS} + V_{DS}$$

$$= -1.5 \text{ V} + 0.4 \text{ V} + 0.82 \text{ V} = -0.28 \text{ V}$$

So, the common-mode range is  
 $-0.28 \text{ V}$  to  $1.0 \text{ V}$

**Ex: 7 . 2**

(a) The value of  $v_{id}$  that causes  $Q_1$  to conduct the entire current is  $\sqrt{2} V_{OV}$

$$\rightarrow \sqrt{2} \times 0.316 = 0.45 \text{ V}$$

$$\text{then, } V_{D1} = V_{DD} - I \times R_D \\ = 1.5 - 0.4 \times 2.5 = 0.5 \text{ V}$$

$$V_{D2} = V_{DD} = + 1.5 \text{ V}$$

(b) For  $Q_2$  to conduct the entire current:

$$v_{id} = -\sqrt{2} V_{OV} = -0.45 \text{ V}$$

then,

$$V_{D1} = V_{DD} = + 1.5 \text{ V}$$

$$V_{D2} = 1.5 - 0.4 \times 2.5 = 0.5 \text{ V}$$

(c) Thus the differential output range is:

$$V_{D2} - V_{D1}: \text{from } 1.5 - 0.5 = + 1 \text{ V} \\ \text{to } 0.5 - 1.5 = - 1 \text{ V}$$

**Ex: 7 . 3**

Refer to answer table for Exercise 7 . 3 where values were obtained in the following way:

$$V_{OV} = \sqrt{I/KW/L} \rightarrow \frac{W}{L} = \frac{I}{KV_{OV}^2}$$


$$g_m = \frac{I}{V_{OV}}$$

$$\left(\frac{v_{id}/2}{V_{OV}}\right)^2 = 0.1 \rightarrow v_{id} = 2 V_{OV} \sqrt{0.1}$$

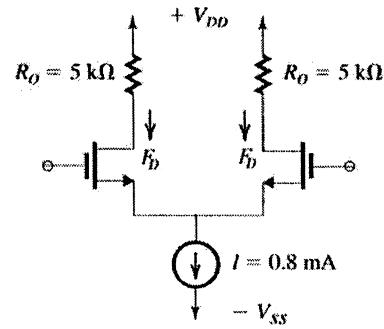**Ex: 7 . 4**

$$I_D = \frac{I}{2} = \frac{0.8 \text{ mA}}{2} = 0.4 \text{ mA}$$

$$I_D = \frac{1}{2} k_n \left( \frac{W}{L} \right) (V_{OV})^2 \text{ So that}$$



$$V_{OV} = \sqrt{\frac{2 I_D}{k_n \left( \frac{W}{L} \right)}} = \sqrt{\frac{2(0.4 \text{ mA})}{0.2(\text{mA/V}^2)(100)}} = 0.2 \text{ V}$$

$$g_m = \frac{I_D}{V_{OV}/2} = \frac{0.4 \text{ mA}}{0.2 \text{ V}} = 4 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{20 \text{ V}}{0.4 \text{ mA}} = 50 \text{ kΩ}$$

$$A_d = g_m (R_D \parallel r_o)$$

$$A_D = (4 \text{ mA/V})(5 \text{ K} \parallel 50 \text{ K}) = 18.2 \text{ V/V}$$

**Ex: 7 . 5**

With  $I = 200 \mu\text{A}$ , for all transistors,

$$I_D = \frac{I}{2} = \frac{200 \mu\text{A}}{2} = 100 \mu\text{A}$$

$$L = 2(0.18 \mu\text{m}) = 0.36 \mu\text{m}$$

$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = \frac{|V_A| L}{I_D} \\ = \frac{(10 \text{ V/μm})(0.36 \mu\text{m})}{0.1 \text{ mA}} = 36 \text{ kΩ}$$

$$\text{Since } I_{D1} = I_{D2} = \frac{1}{2} \mu\text{A} C_{ov} \left( \frac{W}{L} \right) V_{OV}^2,$$

$$\left( \frac{W}{L} \right)_1 = \left( \frac{W}{L} \right)_2 = \frac{2 I_D}{\mu_A C_{ov} (V_{OV})^2} \\ = \frac{2(100 \mu\text{A})}{(400 \mu\text{A/V}^2)(0.2 \text{ V})^2} = 12.5$$

$$\left( \frac{W}{L} \right)_3 = \left( \frac{W}{L} \right)_4 = \frac{2 I_D}{\mu_A C_{ov} (V_{OV})^2} \\ = \frac{2(100 \mu\text{A})}{(100 \mu\text{A/V}^2)(0.2 \text{ V})^2} = 50$$

$$g_m = \frac{I_D}{|V_{OV}|/2} = \frac{(100 \mu\text{A})(2)}{0.2 \text{ V}} = 1 \text{ mA/V},$$

so,

$$A_D = g_m (r_{o1} \parallel r_{o3}) = 1 (\text{mA/V})(36 \text{ K} \parallel 36 \text{ K}) \\ = 18 \text{ V/V}$$

**Ex 7.6**

$$L = 2(0.18 \mu\text{m}) = 0.36 \mu\text{m}$$

$$\text{All } r_O = \frac{|V_A| \cdot L}{|I_D|}$$

The drain current for all transistors is

$$I_D = \frac{I}{2} = \frac{200 \mu\text{A}}{2} = 100 \mu\text{A}$$

$$r_O = \frac{(10 \text{ V}/\mu\text{m})(0.36 \mu\text{m})}{0.1 \text{ mA}} = 36 \text{ k}\Omega$$

Referring to Fig 7.12(a).

Since  $I_D = \frac{1}{2} \mu_A C_{ox} \left(\frac{W}{L}\right) (V_{ov})^2$  for all NMOS transistors

$$\begin{aligned} \left(\frac{W}{L}\right)_1 &= \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 \\ &= \frac{2 I_D}{\mu_n C_{ox} (V_{ov})^2} = \frac{2(100 \mu\text{A})}{400 \mu\text{A/V}^2 (0.2 \text{ V})^2} = 12.5 \\ \left(\frac{W}{L}\right)_5 &= \left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_8 \\ &= \frac{2 I_D}{\mu_p C_{ox} (V_{ov})^2} = \frac{2(100 \mu\text{A})}{100 \mu\text{A/V}^2 (0.2 \text{ V})^2} = 50 \end{aligned}$$

For all transistors,

$$g_m = \frac{|I_D|}{|V_{ov}|/2} = \frac{(0.1 \text{ mA})(2)}{(0.2 \text{ V})} = 1 \text{ mA/V}$$

From Fig 7.12(b),

$$\begin{aligned} R_{on} &= (g_m r_{o3}) r_{o1} = (1 \text{ mA/V})(36 \text{ k})^2 \\ &= 1.296 \text{ M}\Omega \end{aligned}$$

$$\begin{aligned} R_{op} &= (g_m r_{o5}) r_{o7} = (1 \text{ mA/V})(36 \text{ k})^2 \\ &= 1.296 \text{ M}\Omega \end{aligned}$$

Using eq 7.38

$$\begin{aligned} A_d &= g_m (R_{on} \parallel R_{op}) \\ &= (1 \text{ mA/V}) 1.296 (\text{M}\Omega \parallel \text{M}\Omega) \\ &= 648 \text{ V/V} \end{aligned}$$

**Ex: 7.7**

The transconductance for each transistor is

$$g_m = \sqrt{2 \mu_n C_{ox} (W/L) I_D}$$

$$I_D = \frac{I}{2} = \frac{0.8 \text{ mA}}{2} = 0.4 \text{ mA}$$

from eq 7.35 the differential gain for matched

$$R_D \text{ values is } A_d = \frac{V_{o2} - V_{o1}}{V_{id}} = g_m R_D$$

If we ignore the 1% here,

$$A_d = g_m R_D \approx (4 \text{ mA/V})(5 \text{ K}) = 20 \text{ V/V}$$

From eq. 7.49

$$A_{CM} = \frac{V_{od}}{V_{icm}} = \pm \frac{\Delta R_D}{2 R_{SS}} = \frac{(0.01)(5 \text{ K})}{2(25 \text{ K})} = 0.001 \text{ V/V}$$

$$\begin{aligned} CMRR(\text{dB}) &= 20 \log_{10} \frac{|A_d|}{|A_{CM}|} = 20 \log_{10} \left( \frac{20}{0.001} \right) \\ &= 86 \text{ dB} \end{aligned}$$

**Ex: 7.8**

From Exercise 7.7

$$W/L = 100, \mu_n C_{ox} (0.2 \text{ mA/V}^2),$$

$$I_D = \frac{I}{2} = \frac{0.8 \text{ mA}}{2} = 0.4 \text{ mA}$$

$$\begin{aligned} g_m &= \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \\ &= \sqrt{2(0.2 \text{ mA/V}^2)(100)(0.4 \text{ mA})} \end{aligned}$$


$$g_m = 4 \text{ mA/V}$$

using eq. 7.64 and the fact that  $R_{SS} = 25 \text{ k}\Omega$


$$CMRR = \frac{(2 g_m R_{SS})}{\left(\frac{\Delta g_m}{g_m}\right)} = \frac{2(4 \text{ mA/V})(25 \text{ K})}{0.01} = 20,000$$

$$CMRR(\text{dB}) = 20 \log_{10}(20,000) = 86 \text{ dB}$$

**Ex: 7.9**

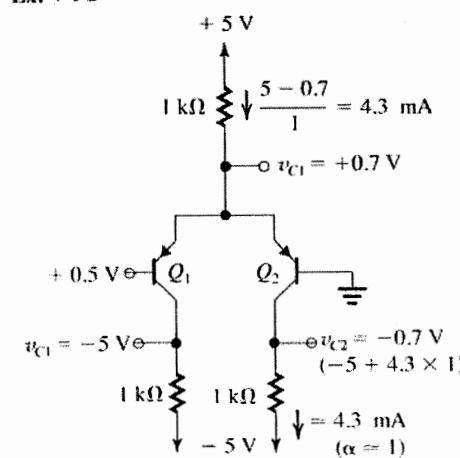

**Ex: 7.10**

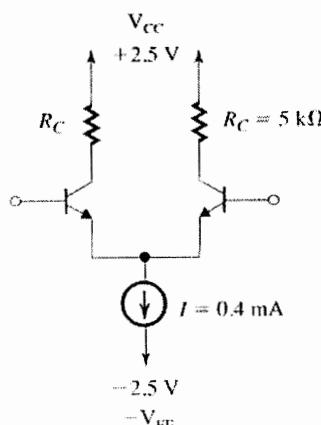

$$I_{C1} = I_{C2} = I_{E1} = I_{E2} = \frac{I}{2} = \frac{0.4 \text{ mA}}{2}$$

$$= 0.2 \text{ mA}$$

From eq. 7.66

$$V_{CM\max} \approx V_C + 0.4 \text{ V}$$

$$= V_{CC} - I_C R_C + 0.4 \text{ V}$$

$$= 2.5 - 0.2 \text{ mA}(5 \text{ K}) + 0.4 \text{ V} = + 1.9 \text{ V}$$

From eq. 7.67

$$V_{CM\min} = -V_{EE} + V_{CS} + V_{BE}$$

$$V_{CM\min} = -2.5 \text{ V} + 0.3 \text{ V} + 0.7 \text{ V} = -1.5 \text{ V}$$

Input range is  $-1.5 \text{ V}$  to  $+1.9 \text{ V}$

**Ex: 7.11**

Substituting  $i_{E1} + i_{E2} \approx I$  in Eqn. 7.70 yields

$$i_{E1} = \frac{I}{1 + e^{(v_{B2} - v_{B1})/V_T}}$$

$$0.99 I = \frac{I}{1 + e^{(v_{B2} - v_{B1})/V_T}}$$

$$v_{B1} - v_{B2} = -V_T \ln\left(\frac{1}{0.99} - 1\right)$$

$$= -25 \ln(1/99)$$

$$= 25 \ln(99) = 115 \text{ mV}$$

**Ex: 7.12**

(a) The DC current in each transistor is 0.5 mA.  
Thus  $V_{BE}$  for each will be

$$V_{BE} = 0.7 + 0.025 \ln\left(\frac{0.5}{1}\right)$$

$$= 0.683 \text{ V}$$

$$\Rightarrow vE = 5 - 0.683 = +4.317 \text{ V}$$

$$(b) g_m = \frac{IC}{VT} = \frac{0.5}{0.025} = 20 \frac{\text{mA}}{\text{V}}$$

$$(c) i_{C1} = 0.5 + g_{m1} \Delta v_{BE1}$$

$$= 0.5 + 20 \times 0.005 \sin(2\pi \times 1000t) \text{ mA}$$

$$i_{C2} = 0.5 - 0.1 \sin(2\pi \times 1000t) \text{ mA}$$

(d)

$$v_{C1} = (V_{CC} - I_C R_C) - 0.1 \times R_C \sin(2\pi \times 1000t)$$

$$= (15 - 0.5 \times 10) - 0.1 \times 10 \sin(2\pi \times 1000t) \text{ V}$$


$$v_{C2} = 10 + 1 \sin(2\pi \times 1000t) \text{ V}$$

$$(e) v_{C2} - v_{C1} = 2 \cdot \sin(2\pi \times 1000t) \text{ V}$$

$$(f) \text{Voltage gain} = \frac{v_{C2} - v_{C1}}{v_{B1} - v_{B2}}$$

$$= \frac{2 \text{ V}}{0.1 \text{ V}} \text{ Peak} = 200 \text{ V/V}$$

**Ex: 7.13**

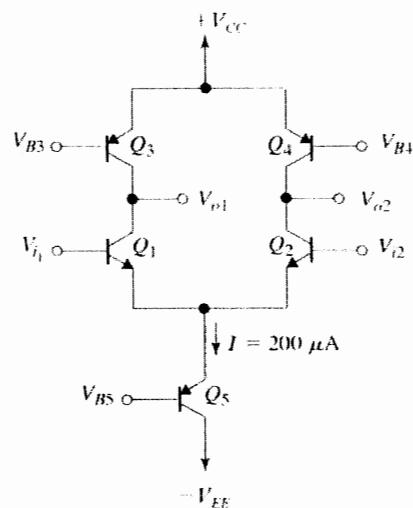

$$I = 200 \mu\text{A}$$

Since  $\beta \gg 1$ ,

$$I_{C1} = I_{C2} \approx \frac{I}{2} = \frac{200 \mu\text{A}}{2} = 100 \mu\text{A}$$

$$g_{m1} = g_{m2} = g_m = \frac{|I_C|}{V_T} = \frac{100 \mu\text{A}}{25 \text{ mV}} = 4 \text{ mA/V}$$

$$R_{C1} = R_{C2} = R_C = r_o = \frac{|V_A|}{I_C}$$

$$= \frac{10 \text{ V}}{100 \mu\text{A}} = 100 \text{ k}\Omega$$

$$R_{EE} = \frac{V_A}{I} = \frac{10 \text{ V}}{200 \mu\text{A}} = 50 \text{ k}\Omega$$

$$r_{e1} = r_{e2} = r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.1 \text{ mA}} = 0.25 \text{ k}\Omega$$

Since  $R_O \gg r_e$ ,

$$|A_d| \approx$$

$$\frac{R_C \parallel r_o}{r_e} = \frac{100 \text{ k}\Omega \parallel 100 \text{ k}\Omega}{0.25 \text{ k}\Omega} = 200 \text{ V/V}$$

$$R_{id} = 2r_a = r_a = \frac{\beta}{g_m} = \frac{100}{4 \text{ mA/V}} = 25 \text{ k}\Omega$$

$$R_{id} = 2(25 \text{ k}\Omega) = 50 \text{ k}\Omega$$

If the total load resistance is assumed to be mismatched by 1%,

$$|A_{em}| = \frac{\Delta R_C}{2R_{EE}} = \frac{(0.01)(100 \text{ k}\Omega)}{2(50 \text{ k}\Omega)} = 0.01$$

$$\text{CMRR(dB)} = 20 \log_{10} \left| \frac{A_d}{A_{em}} \right| = 20 \log_{10} \left| \frac{200}{0.01} \right|$$

$$= 86 \text{ dB}$$

Note: If only the load transistors are mismatched, and since  $\alpha \geq 1$ ,

$$V_{O1} = -\frac{R_C \parallel V_O}{2R_{EE} + r_o} V_{icm} = -\frac{(100 \text{ K} \parallel 100 \text{ K}) V_{icm}}{2(50 \text{ K}) + 0.25 \text{ K}}$$

$$= -0.499 V_{icm}$$

$$V_{O2} \approx \frac{-(R_C + \Delta R_C) \parallel r_O V_{icm}}{2R_{EE} + r_o}$$

$$\approx -\frac{[(1.01)100 \text{ K}] \parallel 100 \text{ K}}{2(50 \text{ K}) + 0.25 \text{ K}} \cdot V_{icm} = 0.501 V_{icm}$$

$$\text{CMRR} = \frac{|A_d|}{|A_{icm}|} = \frac{200}{0.501 - 0.499}$$

= 100,000 → 100 dB

Using eq. 7.103

$$R_{icm} = \beta R_{EE} \cdot \frac{1 + \frac{R_C}{\beta r_O}}{1 + \frac{R_C + 2R_{EE}}{r_O}} = (100)(50 \text{ K})$$

$$\cdot \frac{1 + \frac{100 \text{ K}}{100(100 \text{ K})}}{1 + \frac{100 \text{ K} + 2(50 \text{ K})}{100 \text{ K}}}$$

$$R_{icm} \approx 1.68 \text{ M}\Omega$$

**Ex: 7.14**

From Exercise 7.4

$$V_{ov} = 0.2 \text{ V}$$

Using Eqn. 7.108 we obtain  $V_{os}$  due to  $\Delta R_D / R_D$  as:

$$V_{os} = \left(\frac{V_{ov}}{2}\right) \cdot \left(\frac{\Delta R_D}{R_D}\right)$$

$$= \frac{0.2}{2} \times 0.02 = 0.002 \text{ V i.e } 2 \text{ mV}$$

To obtain  $V_{os}$  due to  $\frac{\Delta W/L}{W/L}$

Use Eqn. 7.113

$$V_{os} = \left(\frac{V_{ov}}{2}\right) \left(\frac{\Delta W/L}{W/L}\right)$$

$$\rightarrow V_{os} = \left(\frac{0.2}{2}\right) \times 0.02 = 0.002$$

$$\rightarrow 2 \text{ mV}$$

The offset voltage arising from  $\Delta V_t$  is obtained from Eqn. 7.116

$$V_{ov} = \Delta V_t = 2 \text{ mV}$$

Finally, from Eqn. 7.117 the total input offset is:

$$V_{os} = \left[ \left( \frac{V_{ov}}{2} \frac{\Delta R_D}{R_D} \right)^2 + \left( \frac{V_{ov}}{2} \frac{\Delta W/L}{W/L} \right)^2 + (\Delta V_t)^2 \right]^{1/2}$$

$$= \sqrt{(2 \times 10^{-3})^2 + (2 \times 10^{-3})^2 + (2 \times 10^{-3})^2}$$

$$= \sqrt{3 \times (2 \times 10^{-3})^2}$$

$$= 3.46 \text{ mV}$$

**Ex: 7.15**

From Eqn. 7.127

$$V_{os} = V_T \sqrt{\left(\frac{\Delta R_C}{R_C}\right)^2 + \left(\frac{\Delta I_S}{I_S}\right)^2}$$

$$= 25 \sqrt{(0.02)^2 + (0.1)^2}$$

$$= 2.5 \text{ mV}$$

$$I_B = \frac{100}{2(\beta + 1)} = \frac{100}{2 \times 101} = 0.5 \mu\text{A}$$

$$I_{os} = I_B \left(\frac{\Delta \beta}{\beta}\right)$$

$$= 0.5 \times 0.1 \mu\text{A} = 50 \text{ nA}$$

**Ex: 7.16**

$$(W/L)_a \times \mu_n C_{ox} = 0.2 \text{ m} \times 100 = 20 \text{ m} \frac{\text{A}}{\text{V}}$$

$$(W/L)_p \times \mu_p C_{ox} = 0.1 \text{ m} \times 200 = 20 \text{ m} \frac{\text{A}}{\text{V}}$$

Since all transistors have the same drain current ( $I/2$ ) and the name product  $W/L \times \mu C_{ox}$ , then all transconductances  $g_m$  are identical.

$$|V_{ov}| = \sqrt{\frac{I_D}{20 \text{ mA/V}}} = \sqrt{0.8 \text{ mA}} = 0.2 \text{ V}$$

thus,

$$g_m = \frac{I_D}{V_{ov}} = \frac{(0.8 \text{ mA}/2)}{0.2 \text{ V}} = 4 \text{ mA/V}$$

From Eqn. 7.138

$$G_m = g_m = 4 \text{ mA/V}$$

$$R_O = r_{o2} \parallel r_{o4}$$

$$r_{o2} = \frac{V_{AO}}{I_{D2}} = \frac{20}{(0.8 \text{ mA}/2)} = 50 \text{ k}\Omega$$

$$r_{o4} = \frac{V_{AO}}{I_{D4}} = \frac{20}{(0.8 \text{ mA}/2)} = 50 \text{ k}\Omega$$

thus,

$$R_O = 50 \parallel 50 = 25 \text{ k}\Omega$$

From Eqn. 7.141

$$A_d = G_m R_O = 4 \frac{\text{mA}}{\text{V}} \times 25 \text{ k}\Omega = 100 \frac{\text{V}}{\text{V}}$$

From Eqn. 7.148a

$$A_{in} = \frac{1}{2g_m R_{SS}} = \frac{1}{2 \times 4 \times 25} = 0.005 \text{ V/V}$$

$$\text{CMRR} = \frac{|A_d|}{|A_{in}|} = \frac{100}{0.005} = 20,000$$

$$\rightarrow 86 \text{ dB}$$

**Ex: 7.17**

From Eqn. 7.156  $G_m = g_m$

$$g_m = \frac{I/2}{V_T} = \frac{(0.8 \text{ mA}/2)}{25 \text{ mV}} = 16 \frac{\text{mA}}{\text{V}}$$

From Eqn. 7.159

$$R_O = r_{o2} \parallel r_{o4}$$

$$= \frac{V_A}{I_{C2}} \parallel \frac{V_A}{I_{C4}} \approx \frac{1}{2} \frac{V_A}{I/2}$$

$$= \frac{100 \text{ V}}{0.8 \text{ mA}} = 125 \text{ k}\Omega$$

$$A_d = G_m \times R_D = 16 \times 125 = 2000 \frac{\text{V}}{\text{V}}$$

From Eqn. 7.162

$$R_{id} = 2 \times r_\pi$$

$$\approx 2 \times \frac{V_T}{(I/2)} \beta_\pi = \frac{2 \times 25 \text{ m} \times 160}{(0.8 \text{ mA}/2)}$$

$$= 20 \text{ k}\Omega$$

For a simple current mirror the output resistance (thus  $R_{oe}$ ) is  $r_o$

$$\rightarrow R_{EE} = \frac{V_A}{I} = \frac{100 \text{ V}}{0.8 \text{ mA}} = 125 \text{ k}\Omega$$

From Eqn. 7.167

$$A_{cm} = \frac{-r_{o4}}{\beta_3 R_{EE}}$$

$$A_{cm} = \frac{-2 \times 125 \text{ K}}{160 \times 125 \text{ K}}$$

$$A_{cm} = -0.0125 \frac{\text{V}}{\text{V}}$$

$$C_{MRR} = \left| \frac{2000}{0.0125} \right|$$

$$C_{MRR} = 160,000$$

$$20 \log_{10}(160,000) = 104 \text{ dB}$$

Ex: 7.18

$$G_m = gm_{12} = \frac{I/2}{V_T} = \frac{1 \text{ mA}/2}{25 \text{ m}} = 20 \text{ mA/V}$$

$$r_{o4} = r_{o5} = \frac{V_A}{I/2} = \frac{100 \text{ V}}{0.5 \text{ mA}} = 200 \text{ k}\Omega$$

$$\rightarrow R_{o4} = \beta_4 r_{o4} = 50 \times 200 \text{ K} = 10 \text{ M}\Omega$$

$$R_{o5} = \beta_5 \frac{r_{o5}}{2} = 100 \times \frac{200 \text{ K}}{2} = 10 \text{ M}\Omega$$

From Eqn. 7.174

$$R_O = \left[ \beta_4 r_{o4} \parallel \beta_5 \frac{r_{o5}}{2} \right]$$

$$= (10 \parallel 10) \text{ M}\Omega = 5 \text{ M}\Omega$$

$$A_d = g_m \times R_o = 20 \times 5000 = 10^5 \text{ V/V}$$

i.e. 100 dB

Ex: 7.19

Refer to Fig 7.41

(a) Using Eqn. 7.178

$$I_6 = \frac{(W/L)_6}{(W/L)_4} (I/2)$$

$$\Rightarrow 100 = \frac{(W/L)_6}{100} \times 50$$

thus,  $(W/L)_6 = 200$

Using Eqn. 7.179

$$I_7 = \frac{(W/L)_7}{(W/L)_5} (I)$$

$$\Rightarrow 100 = \frac{(W/L)_7}{200} \times 100$$

thus,  $(W/L)_7 = 200$

(b) For  $Q_1$ ,

$$I = \frac{1}{2} \mu_p C_{ov} \left( \frac{W}{L} \right)_1 V_{ov1}^2$$

$$\Rightarrow V_{ov1} = \sqrt{\frac{50}{\frac{1}{2} \times 30 \times 200}} = 0.129 \text{ V}$$

Similarly for  $Q_2$ ,  $V_{ov2} = 0.129 \text{ V}$

For  $Q_6$ ,

$$100 = \frac{1}{2} \times 90 \times 200 V_{ov6}^2$$

$$\Rightarrow V_{ov6} = 0.105 \text{ V}$$

$$(c) g_m = \frac{2I_D}{V_{ov}}$$

	$I_D$	$V_{ov}$	$g_m$
$Q_1$	50 $\mu\text{A}$	0.129 V	0.775 mA/V
$Q_2$	50 $\mu\text{A}$	0.129 V	0.775 mA/V
$Q_6$	100 $\mu\text{A}$	0.105 V	1.90 mA/V

$$(d) r_{oa} = 10 / 0.05 = 200 \text{ k}\Omega$$

$$r_a = 10 / 0.05 = 200 \text{ k}\Omega$$

$$r_b = 10 / 0.1 = 100 \text{ k}\Omega$$

$$r_o = 10 / 0.1 = 100 \text{ k}\Omega$$

(e) Eqn. 7.176

$$A_1 = -g_m (r_{o2} \parallel r_{o4})$$

$$= -0.775 (200 \parallel 200) = -77.5 \frac{\text{V}}{\text{V}}$$

Eqn. 7.177

$$A_2 = -g_m (r_{o6} \parallel r_{o7})$$

$$= -95 \frac{\text{V}}{\text{V}}$$

Overall voltage gain is:

$$A_1 \times A_2 = 77.5 \times 95 = 7363 \text{ V/V}$$

Ex: 7.20

Referring to Fig. 7.42 all  $I_D$  values are the same.

so,  $V_{GSB} = V_{DD} + I_D R_E$

Using the equation developed in the text,

$$R_E = \frac{2}{\sqrt{2\mu_n C_{ox} \left( \frac{W}{L} \right)_{12} I_B}} \cdot \left( \sqrt{\frac{\left( \frac{W}{L} \right)_{12}}{\left( \frac{W}{L} \right)_{13}}} - 1 \right)$$

$$R_E = \frac{2}{\sqrt{2(90 \mu\text{A/V}^2)(80)(10 \mu\text{A})}} \cdot \left( \sqrt{\frac{80}{20}} - 1 \right)$$

$$= 5.27 \text{ k}\Omega$$

$$g_{m12} = \frac{2}{R_B} \left( \sqrt{\frac{(W/L)_{12}}{2}} - 1 \right)$$

$$g_{m12} = \frac{2}{5.27 \text{ K}} \cdot \left( \sqrt{\frac{80}{20}} - 1 \right) = 0.38 \text{ mA/V}$$

### Ex 7.21

$$I_o = 90 \mu\text{A}$$

$$\mu_n C_{ox} = 160 \mu\text{A/V}^2$$

$$\mu_p C_{ox} = 40 \mu\text{A/V}^2$$

$$\text{For } Q_8 \text{ and } Q_9 : W/L = 40/0.8$$

(as given in Example 7.5)

$$|V_{ov1}| = \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}}$$

$$\rightarrow |V_{ov1}|_{8,9} = \sqrt{\frac{2 \times 90 \mu}{40 \mu \times \frac{40}{0.8}}} = 0.3 \text{ V}$$

then,

$$g_{m8,9} = \frac{2I_D}{|V_{ov1}|} = \frac{2 \times 90 \mu\text{A}}{0.3 \text{ V}} = 0.6 \text{ mA/V}$$

Since  $g_m$  of  $Q_{10}$ ,  $Q_{11}$  and  $Q_{13}$  are identical to  $g_m$  of  $Q_8$  and  $Q_9$  then:

$$V_{ov11} = 0.3 \text{ V}$$

Thus, for  $Q_{13}$ ,

$$(0.3)^2 = \frac{2 \times 90 \mu}{160 \mu \cdot (W/L)_{13}}$$

$$\rightarrow (W/L)_{13} = 12.5$$

i.e.  $(10/0.8)$

Since  $Q_{12}$  is 4 times as wide as  $Q_{13}$ , then

$$\left(\frac{W}{L}\right)_{12} = \frac{4 \times 10}{0.8} = \frac{40}{0.8}$$

$$R_B = \frac{2}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_{12} I_B}} \cdot \left( \sqrt{\frac{(W/L)_{12}}{2}} - 1 \right)$$

$$= \frac{2}{\sqrt{2 \times 160 \mu \times \frac{40}{0.8} \times 90 \mu}} \cdot \left( \sqrt{\frac{40/0.8}{2}} - 1 \right)$$

$$\rightarrow R_B = 1.67 \text{ k}\Omega$$

The voltage drop on  $R_o$  is:

$$1.67 \text{ k}\Omega \times 90 \mu\text{A} = 150 \text{ mV}$$

$$V_{ov12} = \sqrt{\frac{2 \times 90 \mu}{160 \mu \times \frac{40}{0.8}}} = 0.15 \text{ V}$$

$$V_{ov12} = V_{gs12} - V_{o}$$

$$V_{gs12} = 0.15 + 0.7 = 0.85 \text{ V}$$

$$\text{thus, } V_{gs12} = V_{gs12} + I_B R_o - V_{ss}$$

$$= 0.85 + 0.15 - 2.5$$

$$= -1.5 \text{ V}$$

$$V_{ov11} = |V_{ov1}| = 0.3 \text{ V}$$

$$\rightarrow V_{gs11} = 0.3 + 0.7 = 1 \text{ V}$$

$$V_{G11} = -1.5 + 1 = -0.5 \text{ V}$$

Finally,

$$V_{gs} = V_{bp} - V_{gs1} = +2.5 + (-0.3 - 0.8)$$

$$= +1.4 \text{ V}$$

### Ex: 7.22

$$R_o = 20.2 \text{ k}\Omega$$

$$A_V = 8513 \text{ V/V}$$

$$R_o = 152 \Omega$$

With  $R_s = 10 \text{ k}\Omega$  and  $R_t = 1 \text{ k}\Omega$

$$A_V = \frac{20.2}{20.2 + 10} \times 8513 \times \frac{1}{(1 + 0.152)} = 4943 \text{ V/V}$$

### Ex 7.23

$$\frac{i_{e8}}{i_{b8}} = \beta_8 + 1 = 101$$

$$\frac{i_{b8}}{i_{c7}} = \frac{R_5}{R_5 + R_{14}} = \frac{15.7}{15.7 + 303.5} = 0.0492$$

$$\frac{i_{c7}}{i_{b7}} = \beta_7 = 100$$

$$\frac{i_{b7}}{i_{c5}} = \frac{R_3}{R_3 + R_{13}} = \frac{3}{3 + 234.8} = 0.0126$$

$$\frac{i_{c5}}{i_{b5}} = \beta_5 = 100$$

$$\frac{i_{b5}}{i_{c2}} = \frac{R_1 + R_2}{R_1 + R_2 + R_{12}} = \frac{40}{40 + 5.05} = 0.8879$$

$$\frac{i_{c2}}{i_1} = \beta_2 = 100$$

Thus the overall current gain is:

$$\frac{i_{e8}}{i_1} = 101 \times 0.0492 \times 100 \times 0.0126 \times 100..$$

$$\times 0.8879 \times 100$$

$$= 55993 \text{ A/A}$$

and the overall voltage gain is

$$\frac{V_o}{V_{id}} = \frac{R_6}{R_{11}} \cdot \frac{i_{e8}}{i_1}$$

$$= \frac{3}{20.2} \times 55993 = 8256 \text{ V/V}$$

**Ex: 8 . 1**

$$A_M = \frac{-R_G}{R_G + R_{sig}} \times g_m(R_L \parallel R_D)$$

$$= -\frac{10}{10 + 0.1} \times 2 \times \frac{10 \text{ K}}{2}$$

$$A_u = -9.9 \text{ V/V}$$

$$f_{p1} = \frac{1}{2\pi C_{C1}(R_G + R_{sig})}$$

$$= \frac{1}{2\pi \times 1 \mu \times (10 + 0.1 \text{ M})} = 0.016 \text{ Hz}$$

$$f_{p2} = \frac{1}{2\pi C_S / g_m} = \frac{1}{2\pi \times 1 \mu / 2 \text{ m}} = 318 \text{ Hz}$$

$$f_{p3} = \frac{1}{2\pi C_{C2}(R_L + R_D)} = \frac{1}{2\pi 1 \mu \times (10 + 10)}$$

$$= 8 \text{ Hz}$$

$$f_L \approx f_{p2} = 318 \text{ Hz}$$

**Ex: 8 . 2**

$$C_{CI} = C_E = C_{C2} = 1 \mu\text{F}$$

$$g_m = 40 \frac{\text{mA}}{\text{V}} \rightarrow I_C = 40 \text{ mA} \times 25 \text{ m} = 1 \text{ mA}$$

$$r_\pi = 2.5 \text{ k}\Omega = \frac{\beta}{g_m} \Rightarrow \beta = 100$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

$$f_{p1} = \frac{1}{2\pi C_{C1}[R_B \parallel r_\pi + R_{sig}]}$$

$$= \frac{1}{2\pi 1 \mu [100 \text{ K} \parallel 2.5 \text{ K} + 5 \text{ K}]}$$

$$f_{p1} = 21.4 \text{ Hz}$$

$$f_{p2} = \frac{1}{2\pi \cdot C_E [r_e + \frac{R_B \parallel R_{sig}}{\beta + 1}]}$$

$$f_{p2} = \frac{1}{2\pi \cdot 1 \mu [25 + \frac{100 \text{ K} \parallel 5 \text{ K}}{101}]}$$

$$f_{p2} = 2.2 \text{ KHz}$$

$$f_{p3} = \frac{1}{2\pi \cdot C_{C2} \cdot (R_C + R_L)}$$

$$= \frac{1}{2\pi \cdot 1 \mu (8 \text{ K} + 5 \text{ K})}$$

$$f_{p3} = 12.2 \text{ Hz}$$

**Ex: 8 . 3**

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{10 \times 10^{-9}}$$

$$= 3.45 \times 10^{-3} \text{ F/m}^2 = 3.45 \text{ fF}/\mu\text{m}^2$$

$$C_{ov} = WL_{ov}C_{ov} = 10 \times 0.05 \times 3.45$$

$$= 172 \text{ fF}$$

$$C_{gs} = \frac{2}{3} WLC_{ox} + C_{ov}$$

$$= \frac{2}{3} \times 10 \times 1 \times 3.45 + 1.72 = 24.72 \text{ fF}$$

$$C_{gd} = C_{ov} = 1.72 \text{ fF}$$

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}} = \frac{10}{\sqrt{1 + \frac{1}{0.6}}} = 6.1 \text{ fF}$$

$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DB}}{V_o}}} = \frac{10}{\sqrt{1 + \frac{2 + 1}{0.6}}} = 4.1 \text{ fF}$$

**Ex: 8 . 4**

Peak current occurs At  $V_I = V_{th} = 5 \text{ V}$

$$\text{i Peak} = \frac{1}{2} K_n \left( \frac{W}{L} \right)_n (V_{th} - V_m)^2$$

$$= \frac{1}{2} \times 20 \times 20 (5 - 2)^2 = 1800$$

**Ex: 8 . 5**

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \frac{\text{mA}}{\text{V}}$$

$$C_{de} = \tau_F \cdot g_m = 20 \times 10^{-12} \times 40 \times 10^{-3}$$

$$= 0.8 \text{ pF}$$

$$C_{je} = 2 C_{geo} = 2 \times 20 = 40 \text{ fF}$$

$$C_\pi = C_{de} + C_{je} = 0.84 \text{ pF}$$

$$C\mu = \frac{C_{\mu o}}{\left(1 + \frac{V_{CB}}{V_{oc}}\right)^{m_{CB}}}$$

$$= \frac{20 \text{ fF}}{\left(1 + \frac{2}{0.5}\right)^{0.33}} = 12 \text{ fF}$$

$$f_T = \frac{g_m}{2\pi(C\pi + C\mu)}$$

$$= \frac{40 \times 10^{-3}}{2\pi(0.84 + 0.012) \times 10^{-12}} = 7.47 \text{ GHz}$$

**Ex: 8 . 6**

$$|h_{fe}| \approx \frac{f_T}{f} \rightarrow 10 = \frac{f_T}{50}$$

$$\Rightarrow f_T = 500 \text{ MHz}$$

$$f_T = \frac{g_m}{2\pi(C\pi + C\mu)}$$

$$C\pi + C\mu = \frac{40 \times 10^{-3}}{2\pi \times 500 \times 10^6} = 12.7 \text{ pF}$$

$$C\pi = 12.7 - C\mu = 12.7 - 2 = 10.7 \text{ pF}$$

**Ex: 8 . 7** Diffusion component of  $C\pi$  at  $I_c$  of 1 mA  
 $= 10.7 - 2 = 8.7 \text{ pF}$

Since  $C_{de}$  is proportional to  $I_C$ , then:

$$C_{de} (I_C = 0.1 \text{ mA}) = 0.87 \text{ pF}$$

$$C\pi (I_C = 0.1 \text{ mA}) = 2.87 \text{ pF}$$

$$\begin{aligned} f_T (I_C = 0.1 \text{ mA}) &= \frac{g_m}{2\pi(C\pi + C\mu)} \\ &= \frac{4 \times 10^{-3}}{2\pi(2.87 + 2) \times 10^{-12}} \\ &= 130.7 \text{ MHz} \end{aligned}$$

**Ex: 8 . 8**

$$A_M = -\frac{R_G}{R_G + R_{sig}} g_m R_L$$

$$R_L = 7.14 \text{ k}\Omega, g_m = 1 \text{ mA/V}$$

$$R_{sig} = 10 \text{ k}\Omega$$

$$\begin{aligned} A_M &= \frac{-4.7 \text{ M}\Omega}{(4.7 + 0.01) \text{ M}\Omega} \times 1 \times 7.14 \\ &= -7.12 \text{ V/V} \end{aligned}$$

$$f_H = \frac{1}{2\pi C_{in}(R_{sig} || R_G)} C_{in} = 4.26 \text{ pF}$$

$$f_H = \frac{1}{2\pi \times 4.26(10 \text{ K} \parallel 4.7 \text{ M})} = 3.7 \text{ MHz}$$

**Ex: 8 . 9**

$$C_{gs} = 1 \text{ pF}$$

$$C_{eq} = (1 + g_m R_L) C_{gd} = (1 + 1 \times 7.14)$$

$$C_{gd} = 8.14 C_{gs}$$

$$f_T \geq 1 \text{ MHz} \Rightarrow \frac{1}{2\pi C_{in}(R_{sig} || R_G)} \geq 1 \text{ MHz}$$

$$C_{in} = C_{gs} + C_{eq} = 1 \text{ pF} + 8.14 C_{gd} \text{ pF}$$

$$\frac{1}{2\pi(1 + 8.14 C_{gd}) \text{ pF} (100 \text{ K} \parallel 4.7 \text{ M})} \geq 1 \text{ MHz}$$

$$\Rightarrow 1.63 \geq 1 + 8.14 C_{gd}$$

$$C_{gd} \leq 0.077 \text{ pF} \text{ or } C_{gd} \leq 77 \text{ fF}$$

**Ex: 8 . 10**

$$\textcircled{1} A_v = -39/2 = -19.5 \text{ V/V}$$

$$A_M = \frac{-R_B}{R_B + R_{sig}} \cdot \frac{r_\pi + g_m \cdot R_L}{r_\pi + r_X + (R_B + R_{sig})}$$

$$\begin{aligned} A_M &= \frac{-100}{100 + 5} \cdot \frac{2.5 \times 40 \cdot 10^{-3} \times R_L}{2.5 + 0.05 + (100 \parallel 5)} \\ &= -0.013 \times R_L \end{aligned}$$

$$\Rightarrow R_L = 1.5 \text{ k}\Omega = r_o \parallel R_C \parallel R_L$$

$$1.5 \text{ k}\Omega = (100 \parallel 8 \parallel R_L) \text{ k}\Omega$$

$$= 7.4 \text{ k} \parallel R_L$$

$$\rightarrow R_L = 1.9 \text{ k}\Omega$$

$$\textcircled{2} f_H = \frac{1}{2\pi C_{in} \cdot R_{sig}} R_{sig} = 1.65 \text{ kHz}$$

$$C_{in} = C\pi + C\mu(1 + g_m R_L)$$

$$C_{in} = 7 + 1 (1 + 40 \times 10^{-3} + 1.5 + 10^3)$$

$$= 68 \text{ pF}$$

$$\Rightarrow f_H = \frac{1}{2\pi \cdot 68 \text{ p} \cdot 1.65 \text{ K}} = 1.42 \text{ MHz}$$

**Ex: 8 . 11** Using equations 8 . 61 and 8 . 63 we can write the general form of the transfer function of a direct-coupled amplifier as:

$$A(s) = \frac{A_{DC}}{1 + \frac{s}{2\pi f_{3dB}}} \text{ where } A_{DC} \text{ is the DC gain}$$

of the amplifier and  $f_{3dB}$  is the upper 3dB frequency of the amplifier.

In this case we have  $A_{DC} = 1000$  and

$$f_{3dB} = 100 \text{ KHz} = 10^5 \text{ Hz}$$

$$\text{Therefore } A(s) = \frac{1000}{1 + \frac{s}{2\pi \times 10^5}}$$

**Ex: 8 . 12**

For this amplifier we have:

$$H(s) = \frac{A_M}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$

By definition at  $\omega = \omega_n$  we have

$$|H(j\omega_H)|^2 = \frac{A_M^2}{2} \Rightarrow$$

$$\frac{A_M^2}{\left(1 + \left(\frac{\omega_H}{\omega_{p1}}\right)^2\right)\left(1 + \left(\frac{\omega_H}{\omega_{p2}}\right)^2\right)} = \frac{A_M^2}{2} \Rightarrow$$

$$\left[1 + \left(\frac{\omega_H}{\omega_{p1}}\right)^2\right] \left[1 + \left(\frac{\omega_H}{\omega_{p2}}\right)^2\right] = 2$$

$$\text{If } \omega_{p2} = K\omega_{p1} \text{ and } \omega_H = 0.9\omega_{p1}, \text{ then}$$

$$\left[1 + \left(\frac{0.9\omega_{p1}}{\omega_{p1}}\right)^2\right] \left[1 + \left(\frac{0.9\omega_{p1}}{K\omega_{p1}}\right)^2\right] = 2$$

$$(1 + 0.9^2) \left(1 + \left(\frac{0.9}{K}\right)^2\right) = 2$$

$$1 + \left(\frac{0.9}{K}\right)^2 = 1.1 \Rightarrow \left(\frac{0.9}{K}\right)^2 = 0.1 \Rightarrow K = 2.78$$

If  $\omega_H = 0.99\omega_{p1}$ , then :

$$\left[1 + \left(\frac{0.99\omega_{p1}}{\omega_{p1}}\right)^2\right] \left[1 + \left(\frac{0.99\omega_{p1}}{K\omega_{p1}}\right)^2\right] = 2$$

$$(1 + 0.99^2) \left(1 + \left(\frac{0.99}{K}\right)^2\right) = 2 \Rightarrow$$

$$1 + \left(\frac{0.99}{K}\right)^2 = 1.01 \Rightarrow \left(\frac{0.99}{K}\right)^2 = 0.01 \Rightarrow$$

$$K = 9.88$$

**Ex: 8 . 13**

From Exercise 8 . 12 we have:

$$\left[1 + \left(\frac{\omega_H}{\omega_{p1}}\right)^2\right] \left[1 + \left(\frac{\omega_H}{\omega_{p2}}\right)^2\right] = 2 \text{ and}$$

$$\omega_{p2} = K\omega_{p1}$$

$$K = 1 \Rightarrow \left[1 + \left(\frac{\omega_H}{\omega_{p1}}\right)^2\right] \left[1 + \left(\frac{\omega_H}{\omega_{p2}}\right)^2\right] = 2$$

$$1 + \left(\frac{\omega_H}{\omega_{p1}}\right)^2 = \sqrt{2} \Rightarrow \left(\frac{\omega_H}{\omega_{p1}}\right)^2 = \sqrt{2} - 1$$

$$\omega_H = \sqrt{\sqrt{2} - 1} \quad \omega_{p1} = 0.64 \omega_{p1} \text{ (exact value)}$$

(note that in this case the zeros are at  $S = \infty$ ) we have :

$$\omega_H = 1 / \sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2}} = 1 / \sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{K^2 \omega_{p1}^2}}$$

$$\omega_H = \omega_{p1} / \sqrt{1 + \frac{1}{K^2}}$$

$$\text{For } K = 1 \Rightarrow \omega_H = \frac{1}{\sqrt{2}} \omega_{p1} = 0.71 \omega_{p1}$$

For the case of  $K = 2$ , the exact value of  $\omega_H$  can be found from the following equation:

$$\left[1 + \left(\frac{\omega_H}{\omega_{p1}}\right)^2\right] \left[1 + \left(\frac{\omega_H}{K\omega_{p1}}\right)^2\right] = 2$$

Assuming  $\frac{\omega_H}{\omega_{p1}} = X$  we have

$$(1 + X^2) \left(1 + \frac{X^2}{K^2}\right) = 2 \Rightarrow$$

$$\frac{1}{K^2} X^4 + \left(1 + \frac{1}{K^2}\right) X^2 + 1 = 2 \Rightarrow$$

$$X^4 + (K^2 + 1)X^2 - K^2 = 0 \Rightarrow$$

$$X^2 = \frac{-(K^2 + 1) + \sqrt{(K^2 + 1)^2 + 4K^2}}{2}$$

$$\frac{\omega_H}{\omega_{p1}} = \sqrt{\frac{-(K^2 + 1) + \sqrt{(K^2 + 1)^2 + 4K^2}}{2}} \quad (*)$$

$$\text{For } K = 2 \Rightarrow \frac{\omega_H}{\omega_{p1}} = 0.84 \Rightarrow \omega_H = 0.84 \omega_{p1}$$

In this case, the approximate value of  $\omega_H$  is:

$$\omega_H = \omega_{p1} / \sqrt{1 + \frac{1}{K^2}} = 0.89 \omega_{p1}$$

For  $K = 4$ , using equation (\*), the exact value of  $\omega_H$  is:

$$\omega_H = 0.95 \omega_{p1}$$

In this case, the approximate value of  $\omega_H$  is :

$$\omega_H = \omega_{p1} / \sqrt{1 + \frac{1}{K^2}} = 0.97 \omega_{p1}$$

**Ex: 8 . 14**

We have  $A_M =$

-10.8 V/V and  $f_H \geq 128.3$  KHz, therefore, the gain-bandwidth product is:

$$10.8 \times 128.3 = 1.3856 \text{ MHz} \geq 1.39 \text{ MHz}$$

Now we want to find the value of  $R_L'$  that will result in  $f_H = 180$  KHz. We have:

$$\tau_{gs} + \tau_{gd} = \frac{1}{\omega_H} = \frac{1}{2\pi f_H}$$

$$\tau_{gs} + \tau_{gd} = \frac{1}{2\pi \times 180 \text{ KHz}} = 884.2 \text{ nsec}$$

$$\tau_{gs} = 80.8 \text{ nsec} \Rightarrow \tau_{gd} = 884.2 - 80.8$$

$$\tau_{gd} = 803.4 \text{ nsec}$$

$$\tau_{gd}' = R_{gd} C_{gd} = (R' + R_L' + g_m R_L' R') C_{gd}$$

$$R' = R_{in} \parallel R_{sig} = 80.8 \text{ k}\Omega, g_m = 4 \frac{\text{mA}}{\text{V}},$$

$$C_{gd} = 1 \text{ pF}$$

Thus

$$803.4 \text{ nsec} = (80.8 \text{ k}\Omega + R_L' + 323.2 R_L') + 1 \text{ pF}$$

$$\Rightarrow 324.2 R_L' = \frac{803.4 \text{ nsec}}{1 \text{ pF}} - 80.8 \text{ k}\Omega$$

$$\Rightarrow R_L' = \frac{722.6 \text{ k}\Omega}{324.2} = 2.23 \text{ k}\Omega$$

$$\Rightarrow R_L' = 2.23 \text{ k}\Omega$$

For this value of  $R_L'$  we have


$$A_M = -\frac{R_{in}}{R_{in} + R_{sig}} (g_m R_L')$$

$$A_M = -\frac{420}{420 \times 100} \times 4 \times 2.23 = -7.2 \text{ V/V}$$

Therefore, the gain-bandwidth product is:

$$7.2 \times 180 \text{ KHz} = 1.296 \text{ MHz} \geq 1.3 \text{ MHz}$$

**Ex: 8 . 15**

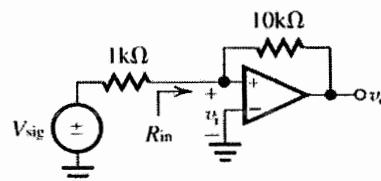

Using Miller's theorem we have

$$R_{in} = \frac{10 \text{ k}\Omega}{A + 1}, V_i = \frac{R_{in}}{R_{in} + 1 \text{ k}\Omega} V_{sig} \text{ and}$$

$$V_o = -AV_i$$

Assuming  $V_{sig} = 1 \text{ V}$  we have

A(V/V)	$R_{in}(\Omega)$	$V_i(\text{mV})$	$V_o(\text{V})$	$\frac{V_o}{V_{sig}}$ ( $\frac{\text{V}}{\text{V}}$ )
10	909	476	4.76	4.76
100	99	90	-9	-9
1000	9.99	9.9	-9.9	-9.9
10000	1	0.999	-9.99	-9.99

**Ex: 8.16** Referring to the solution of Example 8.10 the value of  $f_u$  determined by the exact analysis is:

$$f_u = f_r = 143.4 \text{ MHz}$$

Also,

$$A_M = -g_m \cdot R'_L = -1.25 \times 10 = -12.5 \text{ V/V}$$

Therefore the gain-bandwidth product ( $f_T$ ) is:

$$f_T = 143.4 \times 12.5 = 1.79 \text{ GHz}$$

Since  $f_r$  is less than  $f_{T2} = 2.44 \text{ GHz}$  and  $f_r = 40 \text{ GHz}$ , therefore it is a good approximation of the unity gain frequency.

**Ex:** Referring to the solution of Example 8.10 if a load resistor is connected at the output halving the value of  $R'_L$ , then we have

$$R'_L = \frac{r_{o1} \| r_{o2}}{2} \text{ and therefore}$$

$$|A_M| = g_m \cdot \frac{r_{o1} \| r_{o2}}{2} = 1.25 \times \frac{10}{2} = 6.25 \text{ V/V}$$

Using equation 8.92 and assuming  $f_u \approx f_r$ , we have:

$$f_u \approx$$

$$f_u \approx \frac{1}{2\pi \cdot [(C_{gs} + C_{gd}(1 + g_m R'_L)) \cdot R'_{sig} + (C_L + C_{gd}) R'_L]} \cdot 10 \text{ K}$$

$$+ (25f + 5f) \times 5 \text{ K}$$

$$f_u \approx 223 \text{ MHz}$$

$$f_T = |A_M| \cdot f_u = 6.25 \times 223 = 1.4 \text{ GHz}$$

**Ex: 8.18** Referring to the solution of Example 8.10

$$g_{m1} = \frac{2I_{D1}}{V_{OV1}} \text{ is } I_{D1} \text{ is increased by 4 and } V_{ov} \text{ by 2}$$

then :

$$g_m = \frac{2(4I_{D1})}{(2V_{OV1})} = 2g_{m1} = 2 \times 1.25 \text{ mA} \\ = 2.50 \text{ mA}$$

To calculate  $R'_L$

If  $R'_{L1} = r_{OQ1} \| r_{OQ2} = 10 \text{ k}\Omega$  in example 9.10

Since  $r_O = \frac{V_A}{I_D} \rightarrow$  increasing  $I_D$  by 4 reduces

both  $r_{OQ1}$  and  $r_{OQ2}$  by 4

Thus :

$$r_{OQ1} \| r_{OQ2} = 10 \text{ k}\Omega \rightarrow \frac{r_{OQ1}}{4} \| \frac{r_{OQ2}}{4} = \frac{1}{4}$$

$$(r_{OQ1} \| r_{OQ2})$$

$$R'_L = \frac{1}{4} \times 10 \text{ K} = 2.5 \text{ k}\Omega$$

$$|A_M| = g_m \cdot R'_L = 2.5 \times 2.5 \\ = 6.25 \text{ A/A}$$

Using equation 8.93 and assuming  $f_u \approx f_r$  we have:

$$f_u =$$

$$\frac{1}{2\pi \{ [C_{gs} + C_{gd}(1 + g_m R'_L)] R'_{sig} + (C_L + C_{gd}) R'_L \}} \\ f_H =$$

$$\frac{1}{2\pi \{ [20f + 5f(1 + 6.25)] 10 \text{ K} + (25 + 5) f \times 2.5 \text{ K} \}} \\ f_H = 250 \text{ MHz} \Rightarrow f_r \approx f_H = 250 \text{ MHz}$$

$$f_u \approx |A_M| \cdot f_H = 6.25 \times 250 = 1.56 \text{ GHz}$$

**Ex: 8.19**

$$r_{open} = \frac{V_{Au}}{I} = \frac{130 \text{ V}}{1 \text{ mA}} = 130 \text{ k}\Omega$$

$$r_{open} = \left| \frac{V_{Ap}}{I} \right| = \frac{50 \text{ V}}{1 \text{ mA}} = 50 \text{ k}\Omega$$

$$R'_L = r_{open} \| r_{open} = 130 \text{ k}\Omega \| 50 \text{ k}\Omega$$

$$R'_L = 36 \text{ k}\Omega$$

$$g_m = \frac{I}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{200}{40 \text{ mA/V}} = 5 \text{ k}\Omega$$

(a) From equation 8.97 we have:

$$A_M = -\frac{r_n}{R_{sig} + r_x + r_\pi} (g_m R'_L) \\ = -\frac{5}{36 + 0.2 + 5} (40 \times 36 \text{ k}\Omega) \approx -175 \text{ V/V}$$

$$A_M = -175 \frac{\text{V}}{\text{V}}$$

(b) Using Miller's theorem we have:

$$C_{in} = C_n + C_\mu (1 + g_m R'_L) \\ = 16 \text{ pF} + 0.3 \text{ pF} (1 + 40 \times 36) = 448 \text{ pF}$$

$$C_{in} = 448 \text{ pF}$$

$$f_H \approx \frac{1}{2\pi C_{in} R'_{sig}} = \frac{1}{2\pi C_{in} [r_\pi \| (R_{sig} + r_x)]}$$

$$f_H = \frac{1}{2\pi \times 448 \text{ pF} \underbrace{[5 \| (36 + 0.2)]}_{\approx 4.3 \text{ k}\Omega}} \approx 82.6 \text{ kHz}$$

(c) Using the method of open-circuit time constants, from equation 8.100 we have:

$$\tau_H = C_\pi R'_{sig} + C_\mu [(1 + g_m R'_L) R'_{sig} + R'_L] + C_L R'_L$$

We have  $R'_{sig} = r_\pi \| (R_{sig} + r_x) \approx 4.3 \text{ k}\Omega$

$$R'_L = r_{open} \| r_{open} = 36 \text{ k}\Omega$$

Thus:

$$\begin{aligned}\tau_H &= 16 \times 4.3 + 0.3[(1 + 40 \times 36)4.3 + 36] \\ &+ 5 \times 36 \\ \tau_H &= 2.12 \text{ nsec}\end{aligned}$$

$$f_H = \frac{1}{2\pi\tau_H} \approx 75.1 \text{ kHz}$$

(d) Using equations 8.102, 8.103 and 8.104 we have:

$$f_Z = \frac{1}{2\pi C_\mu} = \frac{1}{2\pi \frac{40 \text{ mA}}{0.3 \text{ pF}}} = 21.2 \text{ GHz}$$

$f_{p1} \approx$

$$\frac{1}{2\pi [C_\pi + C_\mu(1 + g_m R_L)] R_{sig}} + (C_L + C_\mu) R_L' \\ \Rightarrow f_{p1} = 75.1 \text{ kHz}$$

$f_{p2} \approx$

$$\frac{1}{2\pi} \frac{[C_\pi + C_\mu(1 + g_m R_L)] R_{sig} + (C_L + C_\mu) R_L'}{[C_\pi(C_L + C_\mu) + C_L C_\mu] R_{sig} R_L}$$

$$f_{p2} = 25.2 \text{ MHz}$$

Since  $f_{p1} \ll f_z$  and  $f_{p1} \ll f_{p2}$ , thus  $f_H \approx f_{p1} = 75.1 \text{ kHz}$   
(e)  $f_i \leq |A_M| f_H = 175 \times 75.1 \text{ kHz} = 13.1 \text{ MHz}$   
 $f_i = 13.1 \text{ MHz}$

Ex: 8.20 Referring to the solution of Example 8.11 we have  $f_T = |A_M| \cdot f_H$ , since  $|A_M|$  remains the same as that of the example, to place  $f_t$  at 2 GHz we need

$$\begin{aligned}2 \text{ GHz} = f_T &= |A_M| \cdot f_H = \frac{|A_M|}{2\pi(C_L + C_{gd})R_L'} \\ \Rightarrow C_L &= \frac{|A_M|}{2\pi R_L' \cdot f_T} - C_{gd} \\ &= \frac{12.5}{2\pi \times 10 \text{ k}\Omega \times 2 \text{ GHz}} - 5 \times \text{fF} \\ \Rightarrow C_L &= 94.5 \text{ fF}\end{aligned}$$

Ex: 8.21 For a CS amplifier fed with  $R_{sig} = 0$  we know that:

$$f_t = \frac{g_m}{2\pi(C_L + C_{gd})}$$

$$\text{and } f_z = \frac{g_m}{2\pi C_{gd}}$$

Therefore,

$$\frac{f_z}{f_t} = \frac{g_m / (2\pi C_{gd})}{g_m / [2\pi(C_L + C_{gd})]} = \frac{C_L + C_{gd}}{C_{gd}}$$

$$\frac{f_z}{f_t} = \frac{C_L}{C_{gd}} + 1 \Rightarrow \frac{f_z}{f_t} = 1 + \frac{C_L}{C_{gd}}$$

Ex: 8.22  $R_L = 500 \text{ k}\Omega$ , and from

Example 8.12

$$g_m = 1.25 \text{ mA/V}, r_o = 20 \text{ k}\Omega,$$

$$C_{gs} = 20 \text{ fF}, C_{gd} = 5 \text{ fF}, C_L = 15 \text{ fF},$$

$$R_{sig} = 10 \text{ k}\Omega, R_L = 20 \text{ k}\Omega.$$

$$\begin{aligned}R_{in} &= \frac{1}{g_m} + \frac{R_L}{g_m r_o} = \frac{1}{1.25 \text{ mA}} + \frac{500 \text{ k}\Omega}{1.25 \times 20} \\ &= 20.8 \text{ k}\Omega\end{aligned}$$

$$G_V = \frac{R_L}{R_{sig} + R_{in}} = \frac{500}{10 + 20.8} = 16.2 \text{ V/V}$$

To obtain  $f_H$ :

$$R_{gs} = R_{sig} \parallel R_{in} = 10 \text{ k}\Omega \parallel 20.8 \text{ k}\Omega = 6.75 \text{ k}\Omega$$

$$R_{gd} = R_L \parallel R_O$$

$$R_O = r_o + R_{sig} + (g_m r_o) \cdot R_{sig} = 280 \text{ k}\Omega$$

(same as in Eq. 8.12)

$$R_{gd} = 500 \text{ k}\Omega \parallel 280 \text{ k}\Omega = 179.5 \text{ k}\Omega$$

$$\tau_H = C_{gs} \cdot R_{gs} + (C_{gd} + C_L) \cdot R_{gd}$$

$$= 20 \text{ f} \times 6.75 \text{ k}\Omega + (5 \text{ f} + 15 \text{ f}) \times 179.5 \text{ k}\Omega$$

$$\tau_H = 0.135 \text{ ns} + 3.59 \text{ ns} = 3.72 \text{ ns}$$

$$\text{Thus, } f_H = \frac{1}{2\pi\tau_H} = 42.7 \text{ MHz}$$

Ex: 8.23 a) Low-frequency gain

$$A_V; g_m r_o 40; R_L = r_o$$

$$\text{CS - Amplifier: } A_V = -g_m(R_L \parallel r_o)$$

$$\text{Since } R_L = r_o \rightarrow$$

$$A_V = -\frac{1}{2}(g_m r_o) = -\frac{1}{2} \times 40 = -20 \text{ V/V}$$

CASCODE Amplifier:

$$A_V = -g_m(R_O \parallel R_L) = -g_m(R_O \parallel r_o)$$

$$\text{where } R_O = r_{o2} + r_{o1} + (g_{m2} r_{o2}) r_{o1}$$

$$\text{since } r_{o2} = r_{o1} = r_o \text{ and } g_{m2} = g_{m1} = g_m$$

$$\begin{aligned}R_O &= 2r_o + (g_m r_o) \cdot r_o = r_o(2 + g_m r_o) \\ &= 42r_o\end{aligned}$$

$$\begin{aligned}\Rightarrow A_V &= -g_m(42r_o \parallel r_o) \approx -g_m \cdot r_o \\ &= -40 \text{ V/V}\end{aligned}$$

$$\frac{A_{V \text{ CASCODE}}}{A_{V \text{ CS}}} = \frac{-40}{-20} = 2$$

b)  $f_H$ : Neglect components of  $\tau_H$  that do not

include  $R_{sig}$ ; also  $C_{gd} = 0.25 C_{gs}$

CS - Amplifier:

$$\begin{aligned}\tau_H &= C_{gs} \cdot R_{sig} + C_{gd}[(1 + g_m \cdot R_L) R_{sig} + R_L] \\ &+ (C_L + C_{ds}) R_L\end{aligned}$$

$$\text{where: } R_L' = r_o \parallel r_L = \frac{r_o}{2}$$

$$\Rightarrow \tau_H = C_{gs} \cdot R_{sig} + C_{gd} \left[ \left( 1 + \frac{g_m r_o}{2} \right) R_{sig} \right]$$

$$\text{since } C_{gd} = 0.25 C_{gs} \text{ and } g_m r_o = 40$$

$$\Rightarrow \tau_H = C_{gs} \cdot R_{sig} + 0.25 \times C_{gs} \times 21 \times R_{sig}$$

$$= R_{sig} \times C_{gs} \times 6.25$$

CASCODE - Amplifier:

Using Eq 8.118 and neglecting the terms that do not include  $R_{sig}$ :

$$\tau_H = R_{sig} [C_{gs} + C_{gd}(1 + g_m R_{d1})]$$

$$R_{d1} = r_o \parallel \left( \frac{r_o + R_L}{g_m r_o} \right) = r_o \parallel \frac{2r_o}{g_m r_o}$$

$$= r_o \parallel \frac{r_o}{20} \approx \frac{r_o}{20}$$

$$\Rightarrow \tau_H = R_{sig} \left[ C_{gs} + 0.25 \times C_{gs} \left( 1 + \frac{g_m r_o}{20} \right) \right]$$

$$= R_{sig} \cdot C_{gs} \times 1.75$$

$$\frac{f_H \text{ CASCODE}}{f_H \text{ CS}} = \frac{\tau_{cs}}{\tau_{\text{CASCODE}}}$$

$$= \frac{R_{sig} \cdot C_{gs} \times 6.25}{R_{sig} \cdot C_{gs} \times 1.75} = 3.6$$

c)  $f_T = |A_V| \cdot f_H$

$$\frac{f_T \text{ CASCODE}}{f_T \text{ CS}} = \left( \frac{|A_V| \text{ CASCODE}}{|A_V| \text{ CS}} \right) \times \left( \frac{f_H \text{ CASCODE}}{f_H \text{ CS}} \right)$$

$$= 2 \times 3.6$$

$$= 7.2$$

Ex: 8.24 Referring to the solution of Exercise 8.19 we have:

$$g_m = 40 \frac{\text{mA}}{\text{V}} \text{ and } r_\pi = 5 \text{ k}\Omega$$

Note that for the cascode amplifier considered in this exercise:

$$r_{\pi 1} = r_{\pi 2} = r_\pi = 5 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = g_m = 40 \frac{\text{mA}}{\text{V}}$$

$$R_{in} = r_{\pi 1} + r_x = 5 \text{ k}\Omega + 0.2 \text{ k}\Omega = 5.2 \text{ k}\Omega$$

$$A_o = g_m \cdot r_o = 40 \times 130 = 5200 \text{ V/V}$$

$$R_{o1} = r_{o1} = r_o = 130 \text{ k}\Omega$$

$$R_{in2} \approx r_{e2} \parallel \frac{r_{o2} + R_L}{r_{o2} + \frac{R_L}{\beta + 1}} = \frac{5 \text{ K}}{200 + 1}$$

$$\times \frac{130 + 50}{130 + \frac{50}{201}} = 35 \text{ }\Omega$$

$$R_{in2} \approx 35 \text{ }\Omega$$

$$R_o \approx \beta_2 r_{o2} = 200 \times 130 \text{ k}\Omega = 26 \text{ M}\Omega$$

$$A_M = \frac{-r_\pi}{r_\pi + r_x + R_{sig}} \cdot g_m (\beta r_o \parallel R_L)$$

$$A_M \approx -242 \frac{\text{V}}{\text{V}}$$

To calculate  $f_H$  we use the method of open-circuit time constants. From Figure 8.30 we have:

$$R'_{sig} = r_{\pi 1} \parallel (r_{x1} + R_{sig}) = 5 \text{ K} \parallel (0.2 + 36)$$

$$R'_{sig} = 4.4 \text{ k}\Omega$$

$$R_{\pi 1} = R'_{sig} = 4.4 \text{ k}\Omega$$

$$R_{o1} = r_{o1} \parallel R_{in2} = r_o \parallel \left[ r_{e2} \left( \frac{r_{o2} + R_L}{r_{o2} + \frac{R_L}{\beta_2 + 1}} \right) \right]$$

$$R_{o1} = 130 \text{ K} \parallel 35 \text{ }\Omega \approx 35 \text{ }\Omega$$

$$R_{\mu 1} = R'_{sig} (1 + g_{m1} R_{o1}) + R_{o1}$$

$$R_{\mu 1} = 10.6 \text{ k}\Omega$$

$$\tau_H = C_{\pi 1} \cdot R_{\pi 1} + C_{\mu 1} \cdot R_{\mu 1} + (C_{ex1} + C_{\pi 2})$$

$$R_{o1} + (C_L + C_{ex2} + C_{\mu 2}) \cdot (R_L \parallel R_o)$$

$$\tau_H = 16 \text{ p} \times 4.4 \text{ K} + 0.3 \text{ p} \times 10.6 \text{ K} + (0 + 16 \text{ p})$$

$$\times 35 + (5 \text{ p} + 0 + 0.3 \text{ p}) (50 \text{ K} \parallel 26 \text{ M})$$

$$\tau_H = 339 \text{ ns}$$

$$f_H = \frac{1}{2\pi\tau_H} = \frac{1}{2\pi \times 339 \text{ ns}} \approx 469 \text{ KHz}$$

$$f_T \approx |A_M| \cdot f_H = 242 \times 469 \text{ KHz}$$

$$\approx 113.5 \text{ MHz}$$

Compared to the CE amplifier in Exercise 8.19

$|A_M|$  has increased from 175 V/V to

242 V/V,  $f_H$  has increased from 75.1 KHz to 469 KHz and  $f_T$  has increased from 13.1 MHz to 113.5 MHz

To increase  $f_H$  to 1 MHz we need:

$$\tau_H = \frac{1}{2\pi f_H} = 159 \text{ ns}, \text{ thus}$$

$$16 \text{ p} \times 4.4 \text{ K} + 0.3 \text{ p} \times 10.6 \text{ K} + 16 \text{ p} \times 35$$

$$+ (C_L + 0.3 \text{ p}) \cdot (50 \text{ K} \parallel 26 \text{ M}) = 159 \text{ ns}$$

$$\Rightarrow C_L = 1.4 \text{ pF}$$

$$\text{Ex: 8.25 } R'_L = R_L \parallel r_o = 20 \text{ K} \parallel 20 \text{ K}$$

$$= 10 \text{ K}$$

From Eq 8.121 we have:

$$A_M = \frac{g_m R'_L}{1 + g_m R'_L} = \frac{1.25 \times 10}{1 + 1.25 \times 10} = 0.93 \frac{\text{V}}{\text{V}}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} = \frac{1}{2\pi} \times \frac{1.25 \text{ m}}{(20 \text{ f} + 5 \text{ f})} = 8 \text{ GHz}$$

$$f_z = \frac{1}{2\pi} \cdot \frac{g_m}{C_{gs}} = \frac{1}{2\pi} \cdot \frac{1.25 \text{ m}}{20 \text{ f}} \approx 10 \text{ GHz}$$

$$R_{gd} = R_{sig} = 10 \text{ K}$$

$$R_{gs} = \frac{R_{sig} + R'_L}{1 + g_m \cdot R'_L} = \frac{10 \text{ K} + 10 \text{ K}}{1 + 1.25 \times 10} = 1.48 \text{ k}\Omega$$

**Ex:8 . 28**

$$f_Z = \frac{1}{2\pi \cdot C_{ss} \cdot R_{ss}} \\ = \frac{1}{2\pi \cdot (0.4 \text{ p}) 25 \text{ K}} = 15.9 \text{ MHz}$$

**Ex:8 . 29** For a loaded bipolar differential amplifier:

$$A_d = \frac{1}{2} g_m \cdot r_o$$

where,

$$g_m = \frac{I/2}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V}$$

$$r_o = \frac{V_A}{I/2} = \frac{100 \text{ V}}{0.5 \text{ mA}} = 200 \text{ k}\Omega \\ \Rightarrow A_d = \frac{1}{2} \times 20 \frac{\text{mA}}{\text{V}} \times 200 \text{ k}\Omega \\ = 2000 \text{ V/V}$$

The dominant pole is set by the output load capacitance

$$f_z = \frac{1}{2\pi \cdot C_L(r_{o2} \parallel r_{o4})} \\ = \frac{1}{2\pi \times 2 \text{ pF} \times (200 \text{ K} \parallel 200 \text{ K}) \Omega} \\ = 0.796 \text{ MHz} \approx 0.8 \text{ MHz}$$

**Ex:8 . 30 (a)**

$$A_M = -g_m \times R'_L = -g_m(R_L \parallel r_o)$$

$$A_M = -2 \frac{\text{mA}}{\text{V}} \times (20 \text{ k}\Omega \parallel 20 \text{ k}\Omega) = -20 \frac{\text{V}}{\text{V}}$$

To calculate  $\tau_H$  using the method of open-circuit time-constants we can employ Eq (8 . 84)

$$\tau_H = C_{gs} \cdot R_{sig} + C_{gd}[R_{sig}(1 + g_m R'_L) + R'_L] \\ + C_L \cdot R'_L$$

$$\tau_H = 20 \text{ f} \times 20 \text{ K} + 5 \text{ f}[20 \text{ K}(1 + 20) + 10 \text{ K}] \\ + 5 \text{ f} \times 10 \text{ K}$$

$$\tau_H = 2.6 \text{ ns} \Rightarrow f_H = \frac{1}{2\pi\tau_H} = 61.2 \text{ MHz}$$

The gain-bandwidth product is:

$$\text{GBP} = 20 \times 61.2 \text{ M} = 1.22 \text{ GHz}$$

$$(b) \text{ With source degeneration of } R_s = \frac{2}{g_m}$$

$$R_O = r_o[1 + g_m R_s] = 3r_o$$

$$R_O = 3 \times 20 \text{ k}\Omega = 60 \text{ k}\Omega$$

$$A_M = -g_m r_o \times \frac{R_L}{R_L + R_O} = -2 \times 20 \\ \times \frac{20}{20 + 60} = -10 \frac{\text{V}}{\text{V}}$$

$$G_m = \frac{g_m}{1 + g_m R_s} = \frac{g_m}{1 + 2} = \frac{g_m}{3} = \frac{2}{3} \frac{\text{mA}}{\text{V}}$$

Using Eq 8 . 153 to 8 . 157 we have:

$$R'_L = R_L \parallel R_O = 20 \text{ K} \parallel 60 \text{ K} = 15 \text{ k}\Omega \\ R_{gd} = R_{sig}(1 + G_m R'_L) + R'_L = 235 \text{ k}\Omega \\ R_{gs} = \frac{R_{sig} + R_S}{1 + g_m R_S \times \frac{r_o}{r_o + R_L}} = \frac{R_{sig} + R_S}{1 + 2 \times \frac{20}{20 + 20}} \\ = \frac{R_{sig} + R_S}{2} \\ R_S = \frac{2}{g_m} = 1 \text{ k}\Omega \Rightarrow R_{gs} = \frac{20 + 1}{2} = 10.5 \text{ k}\Omega \\ \tau_H = C_{gs} R_{gs} + C_{gd} \cdot R_{gd} + C_L R'_L \\ = 20 \text{ f}(10.5 \text{ K} + 5 \text{ f} \times 235 \text{ K} + 5 \text{ f} \times 15 \text{ K}) \\ \tau_H = 1.46 \text{ ns} \Rightarrow f_H = \frac{1}{2\pi\tau_H} = 109 \text{ MHz} \\ \text{GBP} = 10 \times 109 \text{ MHz} \approx 1.1 \text{ GHz}$$

**Ex:8 . 31**

$$R_{in} = (\beta_1 + 1)(r_{e1} + r_{e2})$$

Since in this case  $r_{e1} = r_{e2} = r_e$  and

$\beta_1 = \beta_2 = \beta$  we have

$$R_{in} = r_\pi + r_\pi = 2r_\pi = \frac{2\beta V_T}{I_C} \approx 10 \text{ k}\Omega$$

we have:

$$\frac{V_O}{V_{Sig}} = \frac{1}{2} \left( \frac{R_{in}}{R_{in} + R_{Sig}} \right) g_m R_L \\ \frac{V_O}{V_{Sig}} = \frac{1}{2} \left( \frac{10}{10 + 10} \right) \frac{V_T}{I_C} R_L = 50 \frac{\text{V}}{\text{V}}$$

we have:

$$f_{p1} = \frac{1}{2\pi \left( \frac{C_\pi}{2} + C_\mu \right) (R_{sig} \parallel 2r_\pi)}$$

$$f_{p1} = \frac{1}{2\pi \left( \frac{6 \text{ pF}}{2} + 2 \text{ pF} \right) (10 \text{ K} \parallel 10 \text{ K})} \\ \approx 6.4 \text{ MHz}$$

we have:

$$f_{p2} = \frac{1}{2\pi C_\mu R_L} = \frac{1}{2\pi \times 2 \text{ pF} \times 10 \text{ K}} \\ \approx 8 \text{ MHz}$$

Therefore, the transfer function of this CC-CB amplifier is:

$$A(s) = \frac{A_M}{\left( 1 + \frac{s}{2\pi f_{p1}} \right) \left( 1 + \frac{s}{2\pi f_{p2}} \right)}$$

$$|A(s)|_{s=j\omega_H} = \frac{|A_M|}{\sqrt{2}} \text{ or } |A(s)|_{s=j\omega_H}^2 = \frac{A_M^2}{2}$$

Thus:

$$\frac{A_M^2}{\left(1 + \frac{(2\pi f_M)^2}{(2\pi f_{p1})^2}\right)\left(1 + \frac{(2\pi f_M)^2}{(2\pi f_{p2})^2}\right)} = \frac{A_M^2}{2}$$

$$\left(1 + \frac{f_M^2}{f_{p1}^2}\right)\left(1 + \frac{f_M^2}{f_{p2}^2}\right) = 2$$

Solving this equation for  $f_H$  we have:

$$f_H \approx 4.6 \text{ MHz}$$

Using the approximate formula, we have:

$$f_H \approx \frac{1}{\sqrt{\frac{1}{f_{p1}^2} + \frac{1}{f_{p2}^2}}} \approx 5 \text{ MHz}$$

**Ex:8 . 32** From Eq 8 . 178

$$\omega_i = \frac{G_{m1}}{C_C} \text{ from Example 7 . 4}$$

$$G_{m1} = G_{m1,z} = 0.3 \text{ mA/V}$$

thus, for  $f_T = 10 \text{ MHz}$ :

$$C_C = \frac{0.3 \text{ mA/V}}{2\pi \times 10 \times 10^6} = 4.8 \text{ pF}$$

From Eqn. 8 . 173

$$f_Z = \frac{G_{m2}}{2\pi \cdot C_C} \quad G_{m2} = g_{m6} = 0.6 \text{ mA/V}$$

$$\Rightarrow f_Z = \frac{0.6 \text{ mA/V}}{2\pi \times 4.8 \text{ pF}} = 20 \text{ MHz}$$

From Eqn. 8 . 177

$$f_{p2} = \frac{G_{m2}}{2\pi \cdot C_2} = \frac{0.6 \text{ mA/V}}{2\pi \times 2 \text{ pF}} = 48 \text{ MHz}$$

**Ex:8 . 33** To obtain Req:

$$\text{Req} = R_2 \parallel r_{o2} \parallel r_{\pi5}$$

$$R_2 = 20 \text{ k}\Omega$$

$$r_{o2} = \frac{V_A}{I_{C2}} \approx \frac{100 \text{ V}}{0.25 \text{ mA}} = 400 \text{ k}\Omega$$

$$r_{\pi5} = (\beta + 1) \frac{V_T}{I_S} = 101 \times \frac{25 \text{ mV}}{1 \text{ mA}}$$

$$= 2525 \text{ }\Omega$$

Thus,

$$\text{Req} = 20 \text{ K} \parallel 400 \text{ K} \parallel 2525 = 2.2 \text{ k}\Omega$$

To obtain Ceq :

$$C_{eq} = C_{\mu2} + C_{\pi5} + C_{\mu5}(1 + g_{m5}R_{L5})$$

$$C_{\mu2} = C_{\pi5} = 2 \text{ pF}$$

$$R_{L5} \approx R_3 = 3 \text{ k}\Omega$$

$$g_{m5} = \frac{I_S}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \frac{\text{mA}}{\text{V}}$$

$$C_{\pi5} + C_{\mu5} = \frac{g_{m5}}{2\pi f_T}$$

$$\Rightarrow C_{\pi5} = \frac{40 \text{ m}}{2\pi \times 400 \text{ m}} = 2 \text{ p} = 14 \text{ pF}$$

thus,

$$C_{eq} = 2 \text{ pF} + 14 \text{ pF} + 2 \text{ pF}(1 + 40 \times 3)$$

$$= 258 \text{ pF}$$

Finally,

$$f_P = \frac{1}{2\pi \cdot \text{Req} \cdot C_{eq}}$$

$$= \frac{1}{2\pi \times 2.2 \text{ K} \times 258 \text{ p}}$$

$$= 280 \text{ KHz}$$

Ex:9 . 1 (c)  $A = 100 \text{ V/V}$  and  $A_f = 10 \text{ V/V}$

$$A_f = \frac{A}{1 + \beta A} \Rightarrow \beta = \frac{1}{A_f} - \frac{1}{A} = \frac{1}{10} - \frac{1}{100} = 0.09$$

$$\beta = 0.09$$

$$\text{since: } 1 + \frac{R_2}{R_1} = \frac{1}{\beta}$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{1}{0.09} - 1 = 10.11$$

(d) The amount of feed-back is:

$$1 + A\beta = 1 + 100 \times 0.09 = 10 \text{ which is } 20 \text{ dB}$$

(e) For  $V_S = 1 \text{ V}$ ;  $V_O = A_f V_S = 10 \times 1 = 10 \text{ V}$

$$V_f = \beta \cdot V_O = 0.09 \times 10 = 0.9 \text{ V}$$

$$V_i = \frac{V_O}{A} = \frac{10}{100} = 0.1 \text{ V}$$

(f) If  $A$  decreases by 20%:

$$A = 0.8 \times 100 = 80 \text{ V/V}$$

$$A_f = \frac{80}{1 + 80 \times 0.09} = 9.7561$$

$$\Delta A_f = 10 - 9.7561 \rightarrow 2.44\% \text{ of } A_f = 10$$

Ex:9 . 2 (c)  $A = 10^4 \text{ V/V}$  and  $A_f = 10^3$

$$A_f = \frac{A}{1 + \beta A} \Rightarrow \beta = \frac{1}{A_f} - \frac{1}{A} = \frac{1}{10^3} - \frac{1}{10^4} = 9 \times 10^{-4}$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{1}{\beta} - 1 = 110.1$$

(d) The amount of feed-back is:

$$1 + A\beta = 1 + 10^4 \times 9 \times 10^{-4} = 10 \text{ which is } 20 \text{ dB}$$

(e) For  $V_S = 0.01 \text{ V}$ :

$$V_O = A_f \cdot V_S = 10^3 \times 0.01 = 10 \text{ V}$$

$$V_f = \beta \cdot V_O = 9 \times 10^{-4} \times 10 = 0.009 \text{ V}$$

$$V_i = \frac{V_O}{A} = \frac{10}{10^4} = 0.001 \text{ V}$$

Ex:9 . 3  $\frac{dA_f}{A_f} = 0.1\%$  and  $\frac{dA}{A} = 10\%$

$$\frac{dA_f}{A_f} = \left( \frac{1}{1 + A\beta} \right) \cdot \frac{dA}{A} \Rightarrow 0.01 = \frac{1}{1 + A\beta}$$

$A_f = \frac{A}{1 + A\beta}$  and the largest close-loop gain possible occurs when  $A = 1000 \text{ V/V}$

$$\Rightarrow A_f = 0.01 \times 1000 = 10 \text{ V/V}$$

If three of these amplifiers are cascaded:

$$A_{\text{TOT}} = A_{f1} \times A_{f2} \times A_{f3} = 1000 \text{ V/V} \text{ and the total variability is:}$$

$$\frac{dA_1}{A_1} + \frac{dA_2}{A_2} + \frac{dA_3}{A_3} = 0.3\% \text{ maximum}$$

Ex:9 . 4 For Example 7 . 1

$$A_O \approx 6000, \beta = 10^{-3}$$

$$(1 + A\beta) = (1 + (6 \times 10^3) \times 10^{-3}) = 7$$

$$\therefore f_{hf} = f_H(1 + A\beta) = 1 \times 7 = 7 \text{ kHz}$$

Ex:9 . 5

$$V_o = V_s \frac{A_1 A_2}{1 + A_1 A_2 \beta} + V_u \frac{A_1}{1 + A_1 A_2 \beta} = V_{sf} + V_{nf}$$


$$= \frac{(1 \times 100) \times V_s}{1 + (100 \times 1) \times 1} + \frac{1 \times V_u}{1 + (100 \times 1) \times 1} = 0.99 + 0.0099$$

Thus,  $V_M \approx 1 \text{ V}$  and  $V_{nf} \approx 0.01 \text{ V}$

New S/N ratio  $\approx 100 / 1$

an improvement of  $20 \log(100 / 1) = 40 \text{ dB}$

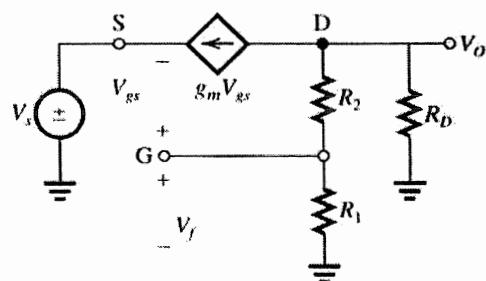Ex:9 . 6 Replacing the amplifier by its small signal model



Open-loop gain: without  $R_2$  and  $R_1$  and the gate grounded:

$$V_O = -g_m V_{gs} \times R_D$$

$$V_{gs} = -V_S \Rightarrow A = g_m R_D$$

Feed-back factor:

$$\beta = \frac{V_f}{V_O} \Rightarrow V_f = \frac{R_1}{R_1 + R_2} \cdot V_O \Rightarrow \beta = \frac{R_1}{R_1 + R_2}$$

Closed-loop gain  $A_f$

$$A_f = \frac{V_O}{V_S}$$

$$V_O = -g_m V_{gs} \times \{(R_1 + R_2) \parallel R_D\}$$

$$= -g_m V_{gs} \cdot \frac{(R_2 + R_1) R_D}{R_2 + R_1 + R_D}$$

but  $R_2 + R_1 \gg R_D \quad R_2 + R_1 + R_D \approx R_2 + R_1$

$$\rightarrow V_O = \left( -g_m V_{gs} \cdot \frac{(R_2 + R_1) R_D}{R_2 + R_1} \right) \\ \approx -g_m V_{gs} \cdot R_D$$

$$-V_{gs} = V_S - V_f = V_S - \frac{R_1 V_O}{R_1 + R_2}$$

$$\Rightarrow V_o = g_m R_D \left\{ V_s - \frac{R_1 V_o}{R_1 + R_2} \right\}$$

$$\Rightarrow V_o \left\{ 1 + \frac{g_m R_D R_1}{R_1 + R_2} \right\} = g_m R_D V_s$$

Thus:

$$A_f = \frac{V_o}{V_s} = \frac{g_m R_D}{1 + g_m R_D R_1 / (R_1 + R_2)}$$

if  $A \cdot \beta \gg 1 \Rightarrow (g_m R_D) \cdot R_1 / (R_1 + R_2) \gg 1$

$$A_f = \frac{g_m R_D}{g_m R_D R_1 / (R_1 + R_2)} = \frac{R_1 + R_2}{R_1}$$

$$= 1 + \frac{R_2}{R_1}$$

Ex: 9.7 From Example 9.2 we know that:


$$A_f = \frac{-g_{m2} R_D}{1 + \frac{g_{m2} R_D}{1 + \frac{R_F}{R_M}}} \text{ where } -g_{m2} R_D \text{ is the open-loop gain}$$

loop gain

$$\text{if loop-gain } A\beta \gg 1 \Rightarrow \frac{g_{m2} R_D}{1 + \frac{R_F}{R_M}} \gg 1$$

$$\text{thus: } A_f = \frac{-g_{m2} R_D}{\frac{g_{m2} R_D}{\left(1 + \frac{R_F}{R_M}\right)}} = -\left(1 + \frac{R_F}{R_M}\right)$$

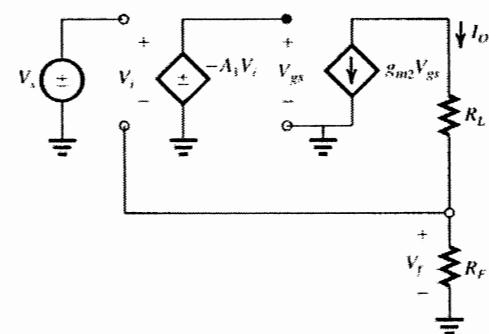Ex: 9.8 The equivalent small-signal model for Fig 9.10 b) is:



Open-loop gain:  $V_s \equiv V_i$

$$I_o = -g_{m2} V_{gs}, \text{ and } V_{gs} = -A_1 V_i$$

$$\Rightarrow I_o = g_{m2}(A_1 V_i) \rightarrow A = \frac{I_o}{V_i} = A_1 g_{m2}$$

$$\beta = \frac{V_f}{I_o}$$

$$V_f = I_o \cdot R_f \rightarrow \frac{V_f}{I_o} = R_f \Rightarrow \beta = R_f$$

$$\text{Closed-loop gain: } A_f = \frac{I_o}{V_s}$$

$$I_o = A_1 g_{m2} V_i \text{ and } V_i = V_s - V_f$$

$$I_o = A_1 g_{m2} \{V_s - V_f\} = A_1 g_{m2} \{V_s - I_o R_f\} \\ \Rightarrow I_o (1 + R_f A_1 g_{m2}) = A_1 g_{m2} \cdot V_s$$

$$A_f = \frac{I_o}{V_s} = \frac{A_1 g_{m2}}{1 + R_f A_1 g_{m2}} \text{ which is the same}$$


$$\text{as } A_f = \frac{A}{1 + \beta A}$$

$$\text{If } A\beta \gg 1 \Rightarrow R_f A_1 g_{m2} \gg 1 \text{ and}$$

$$A_f \approx \frac{A_1 g_{m2}}{R_f A_1 g_{m2}}$$

$$\rightarrow A_f \approx \frac{1}{R_f}$$

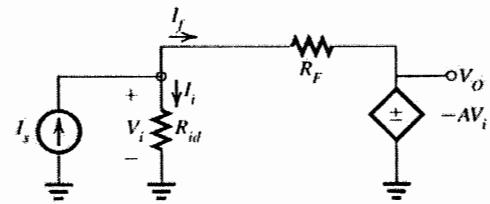Ex: 9.9 The equivalent small-signal circuit for Fig 9.11 b)



$$V_o = -AV_i \rightarrow V_i = \frac{-V_o}{A}$$

$$I_S = I_i + I_f \quad I_i = \frac{V_i}{R_{id}} = \frac{-V_o}{AR_{id}} \quad (1)$$

$$I_f = \frac{V_i - V_o}{R_F} = \frac{-V_o}{AR_F} - \frac{V_o}{R_F} \\ = -V_o \left( \frac{1}{AR_F} + \frac{1}{R_F} \right) \quad (2)$$

$$(1) + (2): I_S = -V_o \left\{ \frac{1}{AR_{id}} + \frac{1}{AR_F} + \frac{1}{R_F} \right\}$$

$$= \frac{-V_o}{R_F} \left\{ \frac{1}{AR_{id}} + \frac{1}{A} + 1 \right\}$$

$$\Rightarrow \frac{V_o}{I_S} = \frac{-R_F}{\left(1 + \frac{1}{A} + \frac{R_F}{AR_{id}}\right)}$$

if  $A \gg 1$  and  $AR_{id} \gg R_F$

$$\Rightarrow 1 + \frac{1}{A} + \frac{R_F}{AR_{id}} \approx 1 \text{ and } A_f \approx -R_F$$

**Ex: 9 . 1 . 0**

From Example 7 . 1

$$A_0 \approx 6000, \beta = 10^{-3}$$

$$(1 + A\beta) = (1 + (6 \times 10^3) \times 10^{-3}) = 7$$

$$\therefore f_{HF} = f_H(1 + A\beta) = 1 \times 7 = 7 \text{ kHz}$$

**Ex: 9 . 1 . 1**

$$I_{E1} = I_{E2} = 0.5 \text{ mA}$$


$$V_{C2} = 10.7 - 0.5 \times 20 = +0.7 \text{ V}$$

$$V_o = 0.7 - V_{BE3} = 0$$

$$I_{E3} = 5 \text{ mA}$$

$$r_{e1} = r_{e2} = V_A/I = 50 \Omega, r_{e3} = 5 \Omega$$

A-Circuit:

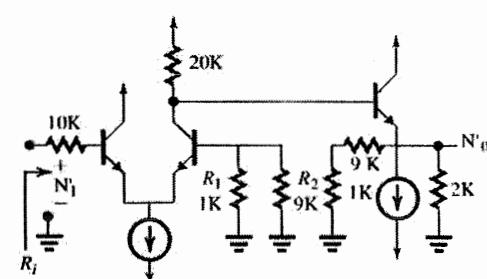


$$A = \frac{V_o}{V_i} = \frac{[20 \parallel (\beta_2 + 1)(r_{e3} + 2 \parallel 10)]}{r_{e1} + r_{e2} + \frac{10}{\beta_1 + 1} + \frac{1}{\beta_2 + 1}} \times \frac{(2 \parallel 10)}{r_{e3} + (2 \parallel 10)} = 85.7 \text{ V/V}$$

$$R_i = R_S + (\beta + 1)(r_{e1} + r_{e2}) + R_E \parallel R_4$$

$$= 10 + 101(50 + 50) + (1 \parallel 9) = 21 \text{ k}\Omega$$

$$R_o = 2 \parallel 10 \parallel \left[ r_{e3} + \frac{20}{\beta_2 + 1} \right] = 181 \text{ }\Omega$$

B-Circuit:

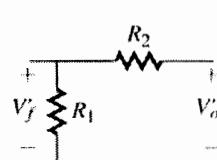

$$\beta = V_f' / V_o'$$

$$= \frac{1}{9 + 1} = 0.1 \text{ V/V}$$

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + A\beta} = \frac{85.7}{1 + 85.7 \times 0.1} = 8.96 \text{ V/V}$$

$$R_{if} = R_i(1 + A\beta) = 21 \times 9.57 = 201 \text{ k}\Omega$$

$$R_{in} = R_{if} - R_S = 201 - 10 = 191 \text{ k}\Omega$$

$$R_{out} = (R_{out} \parallel R_L) = \frac{R_o}{1 + A\beta} = \frac{181}{9.57} = 18.8 \text{ }\Omega$$


$$\Rightarrow R_{out} = 18.8 \text{ }\Omega$$

**Ex: 9 . 1 . 2** The feed-back network is composed of the voltage-driver resistors  $R_1$  and  $R_2$

a) The loading effect of the feed-back network at the input is:  $R_1 \parallel R_2$

b) The loading effect of the feed-back network at the output is:  $R_1 + R_2$


The A circuit is:

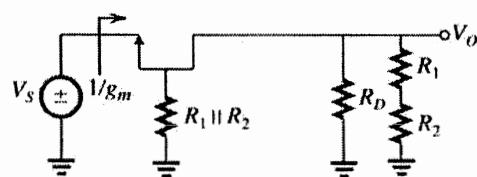

For the CG amplifier:

$$A = g_m [R_D \parallel (R_1 + R_2)]$$

To obtain  $\beta$ :

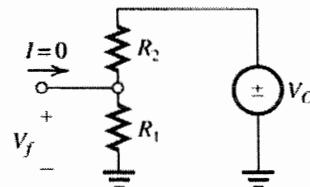

$$\beta = \frac{V_F}{V_o} = \frac{R_1}{R_1 + R_2}$$

$$A_f = \frac{A}{1 + A\beta} \text{ Substituting:}$$

$$A_f = \frac{g_m R_D}{1 + \frac{R_D(1 + g_m R_1)}{R_1 + R_2}}$$

if  $R_1 + R_2 \gg R_D$  we obtain the same result as in Exercise 10.6

From the A circuit:

$$R_i = 1/g_m \Rightarrow R_{in} = \frac{1}{g_m}(1 + A\beta)$$

$$R_D = R_D \parallel (R_1 + R_2) \Rightarrow R_{out} = \frac{(R_D \parallel R_1 + R_2)}{1 + A\beta}$$

(c)  $R_i = R_S \parallel R_F$

Following the procedure used in Example 9.7

$$R_{if} = \frac{R_i}{1 + A\beta} \Rightarrow \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{A\beta}{R_i}$$

$$\frac{1}{R_{if}} = \frac{1}{R_i} + \frac{(R_S \parallel R_F)g_m(r_o \parallel R_F)}{(R_S \parallel R_F) \cdot R_F} \text{ if we call}$$

$$\mu = g_m(r_o \parallel R_F)$$

$$\Rightarrow \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{\mu}{R_F} \text{ or } R_{if} = R_i \parallel \frac{R_F}{\mu}$$

Substituting for  $R_i = R_S \parallel R_F$ :

$$\begin{aligned} R_{if} &= R_S \parallel R_F \parallel \frac{R_F}{\mu} \\ &= R_S \parallel \frac{R_F}{(1 + \mu)} \end{aligned}$$

Since

$$\begin{aligned} R_{if} &= R_S \parallel R_{in} \rightarrow R_{in} = \frac{R_F}{1 + \mu} \\ &= \frac{R_F}{1 + g_m(r_o \parallel R_F)} \end{aligned}$$

(d)  $R_o = r_o \parallel R_F$

Following the procedure used in Example 9.7

$$R_{of} = \frac{R_o}{1 + A\beta} \Rightarrow \frac{1}{R_{of}} = \frac{1}{R_o} + \frac{A\beta}{R_o}$$

$$\frac{1}{R_{of}} = \frac{1}{R_o} + \frac{(R_S \parallel R_F)g_m(r_o \parallel R_F)}{R_F \cdot (r_o \parallel R_F)} \text{ if we call}$$

$$\mu = g_m(R_S \parallel R_F)$$

$$R_{of} = R_o \parallel \frac{R_F}{\mu}$$

Substituting for

$$R_o = r_o \parallel R_F; R_{of} = r_o \parallel R_F \parallel \frac{R_F}{\mu}$$

$$R_{of} = r_o \parallel \frac{R_F}{1 + \mu}$$

Since:  $R_{of} = R_{out} \parallel R_L$  and  $R_L = \infty$

$$\Rightarrow R_{out} = r_o \parallel \frac{R_F}{1 + g_m(R_S \parallel R_F)}$$

(e) For  $g_m = 5 \frac{\text{mA}}{\text{V}}$   $r_o = 20 \text{ k}\Omega$

$$R_f = 10 \text{ k}\Omega$$

$$R_S = 1 \text{ k}\Omega$$

$$\begin{aligned} A &= -(1 \parallel 10 \text{ k}\Omega) \cdot 5 \text{ m}(20 \text{ k}\Omega \parallel 10 \text{ k}\Omega) \\ &\approx -30.3 \text{ k}\Omega \end{aligned}$$

$$\beta = -1/R_F = -1/10 \text{ K} = -0.1 \text{ mA/V}$$

$$A\beta = -30.3 \times -0.1 = 3.03$$

$$A_f = \frac{A}{1 + A\beta} = \frac{-3.03 \text{ K}}{1 + 3.03} = -7.52 \text{ k}\Omega$$

$$R_i = R_S \parallel R_F = 1 \parallel 10 = 909 \text{ }\Omega$$

$$R_o = r_o \parallel R_F = 20 \parallel 10 = 6.67 \text{ k}\Omega$$

$$R_{in} = \frac{10 \text{ K}}{1 + 5 \text{ m}(20 \text{ k}\Omega \parallel 10 \text{ k}\Omega)} = 291 \text{ }\Omega$$

$$R_{if} = \frac{R_i}{1 + A\beta} = \frac{909}{4.03} = 225.6 \text{ }\Omega$$

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{6.67 \text{ K}}{4.03} = 1.66 \text{ k}\Omega$$

$$R_{out} = 20 \text{ k}\Omega \parallel \frac{10 \text{ K}}{1 + 5 \text{ m}(1 \text{ K} \parallel 10 \text{ k}\Omega)} = 1.66 \text{ k}\Omega$$

Ex: 9.16  $\mu = 100$

$$R_S = \infty \quad r_{o1} = 1 \text{ k}\Omega \quad R_1 = 10 \text{ k}\Omega$$

$$R_2 = 90 \text{ k}\Omega \quad g_m = 5 \text{ mA/V}$$

$$r_o = 20 \text{ k}\Omega$$

Refer to Example 9.8

$$R_i = 100 \text{ K}, \text{ unchanged}$$

$$\begin{aligned} A &= -\mu \cdot \frac{R_i}{R_1 \parallel R_2} = -100 \cdot \frac{100}{10 \parallel 90} \\ &= -1.11 \times 10^3 \text{ A/A} \end{aligned}$$

$$\beta = -0.1 \text{ A/A, unchanged}$$

$$A\beta = 111$$

$$A_f = \frac{-1.11 \times 10^3}{1 + 111} = -9.91 \text{ A/A}$$

$$R_{in} = \frac{90 \text{ K}}{100} = 900 \text{ }\Omega$$

$$R_o = 900 \text{ k}\Omega, \text{ unchanged}$$

$$R_{out} = (1 + 111) \cdot 900 \text{ K} = 100 \text{ M}\Omega$$

Ex: 9.17 If  $R_1 = 0 \Rightarrow \beta = \frac{R_1}{R_1 + R_2} = -1$

All of  $I_O$  is fed-back.

$\Rightarrow$  if  $A\beta \gg 1 \rightarrow$  ideal

$$A_f = -\frac{1}{\beta} = 1 \text{ A/A}$$

$$R_i = R_S \parallel R_{id} \parallel R_1 = \infty \parallel \infty \parallel R_1 = R_1$$

$$R_o = r_{o2} + (R_1 \parallel 0) + g_m r_{o2} (R_1 \parallel 0) = r_{o2}$$

Replacing  $R_2$  for 0 in Eq 9.69

$$A = \frac{-\mu R_i r_{o2}}{\frac{1}{g_m} + r_{o2}} = -\mu g_m R_i = -\mu g_m R_1$$

$$A_f = \frac{A}{1 + A\beta} = \frac{-\mu \cdot g_m \cdot R_1}{1 + \mu g_m \cdot R_1}$$

From Eq 9.77

$$R_{out} = \mu \cdot \frac{R_1}{R_1} \cdot g_m r_{o2} \cdot R_1 = \mu g_m r_{o2} \cdot R_1$$

To obtain  $R_{in}$ :

$$R_{in} = \frac{R_i}{1 + A\beta} = \frac{R_1}{1 + \mu g_m R_1}$$

$$R_{in} = \frac{1}{\frac{1}{R_{in}} - \frac{1}{R_s}}$$

$$R_s = \infty \Rightarrow R_{in} = \frac{R_1}{1 + \mu g_m R_1} = \frac{1}{\frac{1}{R_1} + \mu g_m}$$

$$\text{Since } \mu g_m \gg \frac{1}{R_1} \Rightarrow R_{in} = 1/\mu g_m$$

**Ex:9.18** Small-signal equivalent circuit:


$$\frac{-V_r}{V_t} = \frac{g_{m2} \cdot R_{D2}}{R_{D2} + R_2 + R_1 \parallel 1/g_{m1}}.$$

$$\left( \frac{R_1}{R_1 + 1/g_{m1}} \right) \cdot R_{D1}$$

$$A\beta = \frac{4 \text{ m} \times 10 \text{ K}}{(10 \text{ K} + 9 \text{ K} + 1 \text{ K} \parallel 1/4 \text{ m})}.$$

$$\left( \frac{1 \text{ K}}{1 \text{ K} \parallel 1/4 \text{ m}} \right) \cdot 10 \text{ K} = 16.66$$

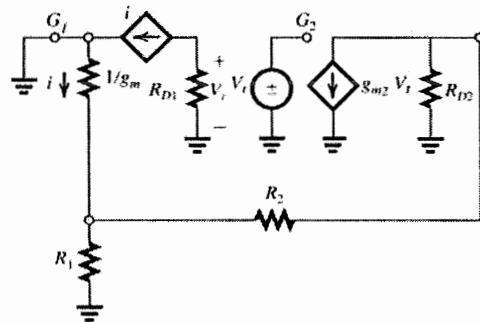Compared to 17.39 obtained in Example 9.4




$$\text{Ex 9.19 } V_x = \frac{-g_m r_o}{r_o + R_F + R_S} \cdot R_S \cdot V_t$$

$$\frac{-V_x}{V_t} = A\beta = \frac{g_m r_o}{r_o + R_F + R_S} \cdot R_S$$

$$A\beta = \frac{5 \text{ m} \times 20 \text{ K} \times 1 \text{ K}}{20 \text{ K} + 10 \text{ K} + 1 \text{ K}} = 3.22$$

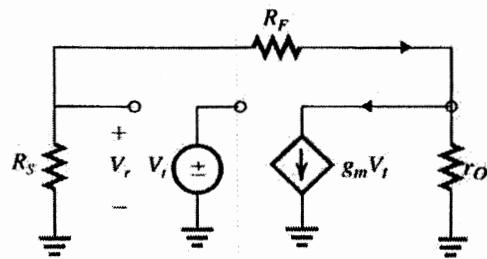as compared to 3.03 obtained in Exercise 9.15



$$\text{Ex 9.20 } A(j\omega) = \left( \frac{10}{1 + j\omega/10^4} \right)^3$$

$$\text{Thus } \phi = -3 \tan^{-1}(\omega/10^4)$$

$$\text{At } \omega_{180^\circ}, \phi = 180^\circ \Rightarrow \tan^{-1}(\omega_{180}/10^4) = 60^\circ$$

$$(\omega_{180}/10^4) = \sqrt{3} \Rightarrow \omega_{180} = \sqrt{3} \times 10^4 \text{ rad/s}$$

Amplifier stable if  $|A\beta| < 1$  at  $\omega_{180}$

$$\text{When } |A\beta| = 1: \beta_{cr} = \frac{1}{|A(j\omega_{180})|}$$

$$\therefore \beta_{cr} = \frac{1}{1000 / (1 + (\sqrt{3})^{3/2})} = 0.008$$

**Ex 9.21** Pole is shifted by factor  $(1 + A_o\beta)$

$$= 1 + 10^5 \times 0.01 = 1001$$

$$f_{pf} = f_p(1 + A_o\beta) = 100 \times 1001 = 100.1 \text{ kHz}$$

For closed loop gain = 1,  $\beta = 1$

$$f'_{pf} = f_p(1 + A_o\beta) = 10^5(1001) = 10^7 \text{ Hz}$$

**Ex 9.22** From Eq. 9.92 Poles will coincide when

$$(\omega_{p1} + \omega_{p2})^2 - 4(1 + A_o\beta) \cdot \omega_{p1}\omega_{p2} = 0$$

Using

$$A_o = 100, \omega_{p1} = 10^4, \omega_{p2} = 10^6 \text{ rad/s}$$

$$(10^4 + 10^6)^2 - 4(1 + 100\beta) \times 10^{10} = 0$$

$$1 + 100\beta = (1.01)^2 \times 100/4$$

$$\Rightarrow \beta = 0.245$$

Corresponding  $Q = 0.5$

For maximally flat response  $Q = 0.707$  and

$$\frac{1}{\sqrt{2}} = \frac{\sqrt{(1 + 100\beta) \times 10^{10}}}{10^4 + 10^6} \Rightarrow \beta = 0.5$$

Corresponding gain is

$$A = \frac{A}{1 + A_o\beta} = \frac{100}{1 + 100 \times 0.5} = 1.96 \text{ V/V}$$

**Ex 9.23** Closed loop poles are found using

$$1 + A(s)\beta = 0$$

$$1 + \frac{10^3}{(1 + S/10^4)^3} \beta = 0$$

$$(1 + S/4)^3 + 10^3\beta = 0$$

$$\frac{5^3}{10^{12}} + \frac{3S^2}{10^8} + \frac{3S^4}{10^4} + (1 + 100\beta) = 0$$

$$\equiv S_n^3 + 3S_n + 3S_n + (1 + 100\beta) = 0 \text{ for}$$

$$S_n = \frac{S}{10^4}$$

Roots of this cubic equation are:

$$(-1 - 10\beta^{1/3}), -1 + 5\beta^{1/3} \pm j5\sqrt{3}\beta^{1/3}$$

Amplifier becomes unstable when complex poles are on  $j\omega$  axis i.e. when  $\beta = \beta_{cr}$

$$10\beta_{cr}^{1/3} = \frac{1}{\cos 60^\circ} = 2 \Rightarrow \beta_{cr} = 0.008$$

$$\begin{aligned} \text{Ex: 9.24 } A &= \frac{A_o}{1 + j \frac{\omega}{\omega_p}} = \frac{A_o}{1 + j f/f_p} \\ &= \frac{10^5}{1 + j f/10} \end{aligned}$$

$$\beta = 0.01 \quad |A\beta| = \frac{10^5 \times 0.01}{\sqrt{1 + f^2/100}} = 1$$

thus  $1 + f^2/100 = 10^6 \Rightarrow f = 10^4 \text{ Hz}$

At  $f = 10^4 \text{ Hz}$

$$\phi = -\tan^{-1}(10^4/10) \approx -90^\circ$$

making phase margin  $180^\circ - 90^\circ = 90^\circ$

**Ex: 9.25** From Eqn 9.105

$$|A_f(j\omega_2)| = \frac{1/\beta}{|1 + e^{-j\theta}|} \text{ and } \frac{1}{\beta} \approx \text{low frequency gain } 0 = 180^\circ - \text{Phase margin}$$

For  $PM = 30^\circ, 0 = 150^\circ$

$$|A_f(j\omega_1)|/(1/\beta) = 1.93$$

For  $PM = 60^\circ, 0 = 120^\circ$

$$|A_f(j\omega_2)|/(1/\beta) = 1.0$$

For  $PM = 90^\circ, 0 = 90^\circ$

$$|A_f(j\omega_{av})|/(1/\beta) = 0.707$$



$$\text{Ex: 9.26 } \beta = \frac{1/SC}{R + 1/SC} = \frac{1}{1 + SCR}$$

$$|\beta| = \sqrt{1 + (\omega CR)^2}$$

$$\therefore \frac{1}{2\pi CR} \leq 1 \text{ Hz}$$

$$CR \leq \frac{1}{2\pi}$$


Thus  $CR \geq 0.1595$ .

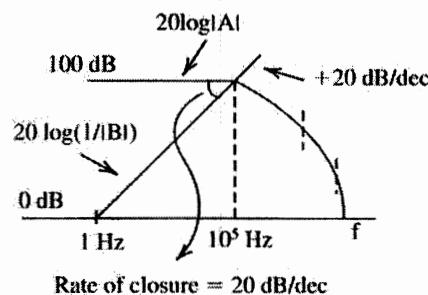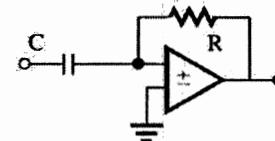

**Ex: 9.27** Must place new dominant pole at

$$f_D = \frac{f_p}{A} = \frac{10^6}{10^4}$$

$$\therefore f_D = 100 \text{ Hz}$$

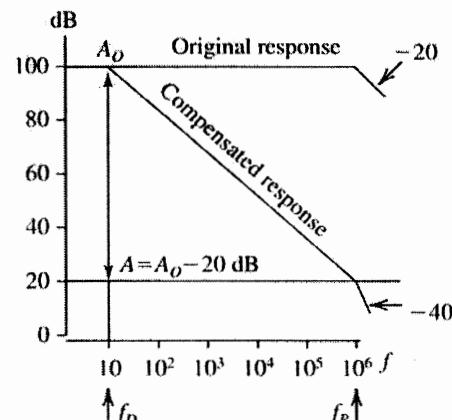

**Ex: 9.28** The pole must be moved  $f_{p1}$  to  $f_D$  where

$$f_D = \frac{\text{Frequency of 2nd pole}}{A_o + A_F}$$

$$= \frac{10 \times 10^6}{10^4} \leftarrow (100 \text{ dB} - 20 \text{ dB}) \\ = 10^3 \text{ Hz}$$

The capacitance at the controlling node must be increased by same factor as  $f$  is lowered.

$$\therefore C_{\text{new}} = C_{\text{old}} \times 1000$$

**Ex 13 . 1**

For  $Q_1$

$$I = \frac{V_{CC} - V_{CEsat}}{R_L} = \frac{15 - 0.2}{1 \text{ k}\Omega}$$

$$I = 14.8 \text{ mA}$$

$$R = \frac{-V_B - (-V_{CC})}{14.8} = \frac{-0.7 - (-15)}{14.8} = 0.97 \text{ k}\Omega$$

$$\begin{aligned} v_{max} &= V_{CC} - V_{CEsat} \\ &= 15 - 0.2 \\ &= 14.8 \text{ V} \end{aligned}$$

$$\begin{aligned} v_{min} &= -V_{CC} + V_{CEsat} \\ &= -15 + 0.2 \\ &= -14.8 \text{ V} \end{aligned}$$

Output signal swing is from 14.8 V to -14.8 V

$$\begin{aligned} \text{Maximum emitter current} &= 2I = 2 \times 14.8 \\ &= 29.6 \text{ mA} \end{aligned}$$

**Ex 13 . 2**

At  $v_o = -10 \text{ V}$ , the load current is -10 mA and the emitter current of  $Q_1$  is  $14.8 - 10 = 4.8 \text{ mA}$ .

$$\begin{aligned} \text{Thus, } v_{BE1} &= 0.6 + 0.025 \ln\left(\frac{14.8}{1}\right) \\ &= 0.64 \text{ V} \end{aligned}$$

$$\text{Thus, } v_I = -10 + 0.64 = -9.36 \text{ V}$$

$$\text{At } v_o = 0 \text{ V}, i_L = 0 \text{ and } i_{E1} = 14.8 \text{ mA}$$

$$\begin{aligned} \text{Thus, } v_{BE1} &= 0.6 + 0.025 \ln\left(\frac{4.8}{1}\right) \\ &= 0.67 \text{ V} \\ v_I &= +0.67 \text{ V} \end{aligned}$$

$$\text{At } v_o = +10 \text{ V}, i_L = 10 \text{ mA} \text{ and } i_{E1} = 24.8 \text{ mA}$$

$$\begin{aligned} \text{Thus, } v_{BE1} &= 0.6 + 0.025 \ln(24.8) \\ &= 0.68 \text{ V} \\ v_I &= 10.68 \text{ V} \end{aligned}$$

To calculate the incremental voltage gain we use

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + r_{e1}}$$

$$\text{At } v_o = -10 \text{ V}, i_{E1} = 4.8 \text{ mA} \text{ and}$$

$$r_{e1} = \frac{25}{4.8} = 5.2 \Omega$$

$$\text{Thus, } \frac{v_o}{v_i} = \frac{1}{1 + 0.0052} = 0.995 \text{ V/V}$$

$$\text{Similarly, at } v_o = 0 \text{ V, } r_{e1} = \frac{25}{14.8} = 1.7 \Omega$$

$$\text{and, } \frac{v_o}{v_i} = \frac{1}{1 + 0.0017} = 0.998 \text{ V/V}$$

$$\text{At } v_o = +10 \text{ V, } i_{E1} = 24.8 \text{ mA} \text{ and } r_{e1} = 1 \Omega$$

$$\text{Thus, } \frac{v_o}{v_i} = \frac{1}{1 + 0.001} = 0.999 \text{ V/V}$$

**Ex 13 . 3**

$$\begin{aligned} \text{a. } P_L &= \frac{(\hat{V}_o / \sqrt{2})^2}{R_L} = \frac{(8 / \sqrt{2})^2}{100} = 0.32 \text{ W} \\ P_S &= 2 V_{CC} \times I = 2 \times 10 \times 100 \times 10^{-3} \\ &= 2 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Efficiency } \eta &= \frac{P_L}{P_S} \times 100 \\ &= \frac{0.32}{2} \times 100 \\ &= 16\% \end{aligned}$$

**Ex 13 . 4**

$$\begin{aligned} \text{(a) } P_L &= \frac{1}{2} \frac{\hat{V}_o^2}{R_L} \\ &= \frac{1}{2} \frac{(4.5)^2}{4} = 2.53 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{(b) } P_+ = P_- &= V_{CC} \times \frac{1}{\pi} \frac{\hat{V}_o}{R_L} \\ &= 6 \times \frac{1}{\pi} \times \frac{4.5}{4} = 2.15 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{(c) } \eta &= \frac{P_L}{P_S} \times 100 = \frac{2.53}{2 \times 2.15} \times 100 \\ &= 59\% \end{aligned}$$

$$\begin{aligned} \text{(d) Peak input currents} &= \frac{1}{\beta + 1} \frac{\hat{V}_o}{R_L} \\ &= \frac{1}{51} \times \frac{4.5}{4} \\ &= 22.1 \text{ mA} \end{aligned}$$

(e) Using Eq. 10 . 22

$$\begin{aligned} P_{DNPmax} &= P_{DPmax} = \frac{V_{CC}^2}{\pi^2 R_L} \\ &= \frac{6^2}{\pi^2 \times 4} = 0.91 \text{ W} \end{aligned}$$

**Ex 13 . 5**

(a) The quiescent power dissipated in each transistor =  $I_Q \times V_{CC}$

Total power dissipated in the two transistors

$$= 2I_Q \times V_{CC}$$

$$= 2 \times 2 \times 10^{-3} \times 15$$

$$= 60 \text{ mW}$$

(b)  $I_V$  is increased to 10 mA

At  $V_a = 0, i_N = i_P = 10 \text{ mA}$

From equation 13 . 31

$$R_{out} = \frac{V_T}{i_P + i_N} \approx \frac{25}{10 + 10} = 1.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{out}} = \frac{100}{100 + 1.25}$$

$$\frac{v_o}{v_i} = 0.988 \text{ at } v_o = 0 \text{ V}$$

At  $v_o = 10 \text{ V}$ ,

$$i_L = \frac{10 \text{ V}}{100 \Omega} = 0.1 \text{ A} = 100 \text{ mA}$$

use equation 13.27 to calculate  $i_N$

$$i_N^2 - i_N i_L - I_Q^2 = 0$$

$$i_N^2 - 100 i_N - 10^2 = 0$$

$$\Rightarrow i_N = 99.99 \text{ mA}$$

using equation 13.26

$$i_P = \frac{I_Q^2}{I_N} \approx 1 \text{ mA}$$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{99.99 + 1} \approx 0.2475 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 0.2475} \approx 1$$

$$\% \text{ change} = \frac{1 - 0.988}{1} \times 100 = 1.2\%$$

In example 13.5  $I_Q = 2 \text{ mA}$ , and for  $v_o = 0$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{2 + 2} = 6.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 6.25} = 0.94$$

$$v_o = 10 \text{ V}$$

$$I_L = \frac{10 \text{ V}}{100 \Omega} = 100 \text{ mA}$$

Again calculate  $i_N$  (for  $I_Q = 2 \text{ mA}$ ) using equation 13.27  $i_N = 99.96 \text{ mA}$

$$i_P = \frac{I_Q^2}{I_N} = \frac{2^2}{99.96} = 0.04 \text{ mA}$$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{99.96 + 0.04} = 0.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} \approx 1$$

$$\% \text{ Change} = \frac{1 - 0.94}{1} \times 100 = 6\%$$

For  $I_Q = 10 \text{ mA}$ , change is 1.2%

For  $I_Q = 2 \text{ mA}$ , change is 6%

(c) The quiescent power dissipated in each transistor =  $I_Q \times V_{CE}$

Total power dissipated =  $2 \times 10 \times 10^{-3} \times 15 = 300 \text{ mW}$

### Ex 13.6

From example 13.4  $V_{CC} = 15 \text{ V}$ ,  $R_L = 100 \Omega$ ,  $Q_N$  and  $Q_P$  matched and  $I_S = 10^{-13} \text{ A}$  and  $\beta = 50$ ,  $I_{\text{Bias}} \approx 3 \text{ mA}$


$$\text{For } v_o = 10 \text{ V}, I_L = \frac{10}{100} = 0.1 \text{ A}$$

As a first approximation  $i_N \approx 0.1 \text{ A}$ ,  $i_P = 0$ ,  $i_{BS} \approx \frac{0.1 \text{ A}}{50 + 1} \approx 2 \text{ mA}$

$$i_D = I_{\text{Bias}} - i_{BS} = 3 - 2 = 1 \text{ mA}$$

$$V_{BS} = 2 V_T \ln \left( \frac{10^{-3}}{\frac{1}{3} \times 10^{-13}} \right)$$

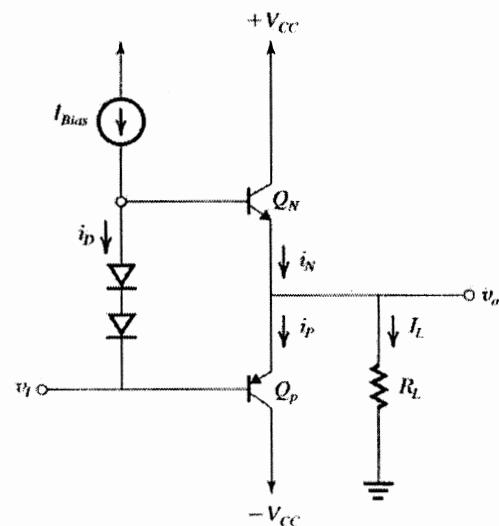This  $\frac{1}{3}$  is because biasing diodes have  $\frac{1}{3}$  area of the output devices.



$$\text{But } V_{BS} = V_{BSN} + V_{BSP} = \quad (1)$$

$$V_T \ln \left( \frac{i_N}{I_S} \right) + V_T \ln \left( \frac{i_N - i_L}{I_S} \right) \\ = V_T \ln \left[ \frac{i_N(i_N - i_L)}{I_S^2} \right] \quad (2)$$

Equating equations 1 and 2

$$2V_T \ln \left( \frac{10^{-3}}{\frac{1}{3} \times 10^{-13}} \right) = V_T \ln \left( \frac{i_N - i_L}{I_S^2} \right)$$

$$\left( \frac{10^{-3}}{\frac{1}{3} \times 10^{-13}} \right)^2 = \frac{i_N(i_N - 0.1)}{(10^{-13})^2}$$

$$i_N(i_N - 0.1) = 9 \times 10^{-6}$$

If  $i_N$  is in mA, then

$$i_N(i_N - 100) = 9$$

$$i_N^2 - 100 i_N - 9 = 0$$

$$\Rightarrow i_N = 100.1 \text{ mA}$$

$$i_P = i_N - i_L = 0.1 \text{ mA}$$

$$\text{For } v_o = -10 \text{ V} \text{ and } i_L = \frac{-10}{100} = -0.1 \text{ A}$$

$$= -100 \text{ mA}$$

As a first approximation assume  $i_P \approx 100 \text{ mA}$ .

$i_N \approx 0$  since  $i_N = 0$ , current through diodes = 3 mA

$$\therefore V_{BB} = 2V_T \ln \left( \frac{3 \times 10^{-3}}{\frac{1}{3} \times 10^{-13}} \right) \quad (3)$$

$$\begin{aligned} \text{But } V_{BB} &= V_T \ln \left( \frac{i_N}{10^{-13}} \right) + V_T \ln \left( \frac{i_P}{10^{-13}} \right) \\ &= V_T \ln \left( \frac{i_P - i_L}{10^{-13}} \right) + V_T \ln \left( \frac{i_P}{10^{-13}} \right) \end{aligned} \quad (4)$$

Here  $i_L = 0.1 \text{ A}$

Equating equations 3 and 4

$$\begin{aligned} 2V_T \ln \left( \frac{3 \times 10^{-3}}{\frac{1}{3} \times 10^{-13}} \right) &= \\ V_T \ln \left( \frac{i_P - 0.1}{10^{-13}} \right) + V_T \ln \left( \frac{i_P}{10^{-13}} \right) & \\ \left( \frac{3 \times 10^{-3}}{\frac{1}{3} \times 10^{-13}} \right)^2 &= \frac{i_P(i_P - 0.1)}{(10^{-13})^2} \end{aligned}$$

$$i_P(i_P - 0.1) = 81 \times 10^{-6}$$

Expressing currents in mA

$$i_P(i_P - 100) = 81$$

$$i_P^2 - 100i_P - 81 = 0$$

$$\Rightarrow i_P = 100.8 \text{ mA}$$

$$i_N = i_P - i_L = 0.8 \text{ mA}$$

### Ex 13 . 7

$$\Delta I_C = g_m \times 2 \text{ mV} / ^\circ\text{C} \times 5 \text{ }^\circ\text{C}, \text{ mA}$$

where  $g_m$  is in mA / mV

$$g_m = \frac{10 \text{ mA}}{25 \text{ mV}} = 0.4 \text{ mA / mV}$$

$$\text{Thus, } \Delta I_C = 0.4 \times 2 \times 5 = 4 \text{ mA}$$

### Ex 13 . 8

Refer to Fig. 10 . 14

(a) To obtain a terminal voltage of 1.2 V, and since  $\beta_1$  is very large, it follows, that  $V_{R1} = V_{R2} = 0.6 \text{ V}$ .

Thus  $I_{C1} = 1 \text{ mA}$

$$I_R = \frac{1.2 \text{ V}}{R_1 + R_2} = \frac{1.2}{2.4} = 0.5 \text{ mA}$$

$$\text{Thus, } I = I_{C1} + I_R = 1.5 \text{ mA}$$

(b) For  $\Delta V_{BB} = +50 \text{ mV}$ :

$$V_{BB} = 1.25 \text{ V} \quad I_R = \frac{1.25}{2.4} = 0.52 \text{ mA}$$

$$V_{BE} = \frac{1.25}{2} = 0.625 \text{ V}$$

$$I_{C1} = 1 \times e^{\frac{\Delta V_{BE} + V_T}{k_n}} = e^{0.025/0.025}$$

$$= 2.72 \text{ mA}$$

$$I = 2.72 + 0.52 = 3.24 \text{ mA}$$

For  $\Delta V_{BB} = +100 \text{ mV}$

$$V_{BB} = 1.3 \text{ V} \quad I_R = \frac{1.3}{2.4} = 0.54 \text{ mA}$$

$$V_{BE} = \frac{1.3}{2} = 0.65 \text{ V}$$

$$I_{C1} = 1 \times e^{\frac{\Delta V_{BE} + V_T}{k_n}} = 1 \times e^{0.05/0.025}$$

$$= 7.39$$

$$I = 7.39 + 0.54 = 7.93 \text{ mA}$$

For  $\Delta V_{BB} = +200 \text{ mV}$ :

$$V_{BB} = 1.4 \text{ V} \quad I_R = \frac{1.4}{2.4} = 0.58 \text{ mA}$$

$$V_{BE} = 0.7 \text{ V}$$

$$I_{C1} = 1 \times e^{0.1/0.025} = 54.60 \text{ mA}$$

$$I = 54.60 + 0.58 = 55.18 \text{ mA}$$

For  $\Delta V_{BB} = -50 \text{ mV}$

$$V_{BB} = 1.15 \text{ V} \quad I_R = \frac{1.15}{2.4} = 0.48 \text{ mA}$$

$$\begin{aligned} V_{BE} &= \frac{1.15}{2} \\ &= 0.575 \end{aligned}$$

$$I_{C1} = 1 \times e^{-0.025/0.025} = 0.37 \text{ mA}$$

$$I = 0.48 + 0.37 = 0.85 \text{ mA}$$

For  $\Delta V_{BB} = -100 \text{ mV}$ :

$$V_{BB} = 1.1 \text{ V} \quad I_R = \frac{1.1}{2.4} = 0.46 \text{ mA}$$

$$V_{BE} = 0.55 \text{ V}$$

$$I_{C1} = 1 \times e^{-0.05/0.025} = 0.13 \text{ mA}$$

$$I = 0.46 + 0.13 = 0.59 \text{ mA}$$

For  $\Delta V_{BB} = -200 \text{ mV}$ :

$$V_{BB} = 1.0 \text{ V} \quad I_R = \frac{1}{2.4} = 0.417 \text{ mA}$$

$$V_{BE} = 0.5 \text{ V}$$

$$I_{C1} = 1 \times e^{-0.1/0.025} = 0.018 \text{ mA}$$

$$I = 0.43 \text{ mA}$$

### Ex 13 . 9

Using equation 13 . 43

$$I_Q = I_{Bias} \frac{(W/L)_n}{(W/L)_t}$$

$$1 = 0.2 \frac{(W/L)_n}{(W/L)_p}$$

$$\frac{(W/L)_n}{(W/L)_t} = 5$$

$$Q: I_{Bias} = \frac{1}{2} k_n \left( \frac{W}{L} \right)_t (V_{GS} - V_{th})^2$$

$$0.2 = \frac{1}{2} \times 0.250 \left( \frac{W}{L} \right)_t (0.2)^2$$

$$\Rightarrow \left( \frac{W}{L} \right)_t = 40$$

$$Q_1: I_{\text{Bias}} = \frac{1}{2} k_p' \left(\frac{W}{L}\right)_2 (V_{GS} - |V_t|)^2$$

$$0.2 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_2 \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_2 = 100$$

$$Q_2: I_Q = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_N (V_{GS} - |V_t|)^2$$

$$1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_N \times 0.2^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_N = 200$$

$$Q_3: I_Q = \frac{1}{2} k_p' \left(\frac{W}{L}\right)_p (V_{GS} - |V_t|)^2$$

$$1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_p \times 0.2^2$$

$$\left(\frac{W}{L}\right)_p = 500$$

$$\begin{aligned} \text{Now } V_{dd} &= V_{GS1} + V_{GS2} \\ &= (V_{ov1} + V_t) + (V_{ov2} + |V_t|) \\ &= (0.2 + 0.5) + (0.2 + 0.5) \\ &= 1.4 \text{ V} \end{aligned}$$

### Ex 13.10

$I_s = i_{\text{Des}} \approx 10 \text{ mA}$

$$\therefore 10 = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_n V_{ov}^2$$

$$10 = \frac{1}{2} \times 0.250 \times 200 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = 0.63 \text{ V}$$

Using equation 13.46

$$\begin{aligned} V_{\text{max}} &= V_{DD} - V_{ov}|_{\text{Bias}} - V_{in} - V_{ovN} \\ &= 2.5 - 0.2 - 0.5 - 0.63 \\ &= 1.17 \text{ V} \end{aligned}$$

### Ex 13.11

New values of W/L are

$$\left(\frac{W}{L}\right)_p = \frac{2000}{2} = 1000$$

$$\left(\frac{W}{L}\right)_N = \frac{800}{2} = 400$$

$$I_Q = \frac{1}{2} k_p' \left(\frac{W}{L}\right)_p V_{ov}^2$$

$$1 \times 10^{-3} = \frac{1}{2} \times 0.1 \times 10^{-3} \times 1000 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = 0.14 \text{ V}$$

Gain Error =

$$\begin{aligned} -\frac{V_{ov}}{4\mu I_Q R_L} &= -\frac{0.14}{4 \times 10 \times 1 \times 10^{-3} \times 100} \\ &\approx -0.035 \end{aligned}$$

Gain Error =  $-0.035 \times 100 = 3.5\%$

$$g_{mn} = g_{mp} = \frac{2I_Q}{V_{ov}} = \frac{2 \times 1 \times 10^{-3}}{0.14}$$

$$= 14.14 \text{ mA/V}$$

$$R_{\text{out}} = \frac{1}{\mu(g_{mp} + g_{mn})} =$$

$$\frac{1}{10 \times (14.14 + 14.14) \times 10^{-3}} \approx 3.5 \Omega$$

### Ex 13.12

See solution on next page

**Ex 13.12**

Need to prove when  $V_{o2} = 4I_Q R_L$  then  $V_{GSN2} = V_m$

Assume  $Q_N$  off ( $V_{GSN} = V_m$ ) so  $i_{N2} = 0$  and

$$i_{p2} = i_{L2}$$

$$i_{p2} = i_{L2} = \frac{V_{o2}}{R_L} = 4I_Q$$

$$4I_Q = \frac{1}{2}k_p' \left(\frac{W}{L}\right)_p (V_{SGP2} - |V_{tp}|)^2$$

$$\sqrt{4 \left( \frac{1}{2} k_p' \left(\frac{W}{L}\right)_p (V_{SGPQ} - |V_{tp}|)^2 \right)}$$

$$= \sqrt{\frac{1}{2} k_p' \left(\frac{W}{L}\right)_p (V_{SGP2} - |V_{tp}|)^2}$$

$$2(V_{SGPQ} - |V_{tp}|) = (V_{SGP2} - |V_{tp}|)$$

$$V_{SGP2} = 2V_{SGPQ} - 2|V_{tp}| + |V_{tp}|$$

$$= 2V_{SGPQ} - |V_{tp}|$$

(1)

Find  $V_{i2}$  for the gate voltage,  $V_{GP2}$ :

$$V_{GP2} = (V_{DD} - V_{SGPQ}) + \mu(V_{o2} - V_{i2})$$

$$(V_{GP2} - V_{DD}) = -V_{SGPQ} + \mu(V_{o2} - V_{i2})$$

$$[V_{GP2} \text{ OR}] - V_{SGP2} = -V_{SGPQ} + \mu(V_{o2} - V_{i2})$$

using (1):

$$-2V_{SGPQ} + |V_{tp}| = -V_{SGPQ} + \mu(V_{o2} - V_{i2})$$

$$\mu(V_{i2} - V_{o2}) = -V_{SGPQ} + 2V_{SGPQ} - |V_{tp}|$$

$$V_{i2} = +V_{o2} + \frac{(V_{SGPQ} - |V_{tp}|)}{\mu} = V_{o2} + \frac{V_{ovQ}}{\mu}$$

Plug this value for  $V_{i2}$  into the value for  $V_{GSN2}$

$$\text{and show } V_{GSN2} = V_m$$

$$(-V_{fs} + V_{GSNQ}) + \mu(V_{o2} - V_{i2}) = V_{GSN2} - (-V_{fs})$$

$$V_{GSNQ} + \mu(V_{o2} - V_{o2} - \frac{V_{ovQ}}{\mu}) = V_{GSN2}$$

where

$$V_{ovQ} = (V_{GSNQ} - V_m) = (V_{SGPQ} - |V_{tp}|)$$

$$V_{GSNQ} - V_{GSNQ} + V_m = V_{GSN2} \text{ Q.E.D.}$$

Same proof for p transistor.

**Ex: 10 . 1**

$$V_{ICM(max)} \leq V_{DD} - |V_{OVS}| - |V_{op}| - |V_{ov}| \\ \leq +1.65 - 0.3 - 0.5 - 0.3$$

$$\leq +0.55 \text{ V}$$

$$V_{ICM(min)} \geq -V_{SS} + V_{OV3} + V_m - |V_{op}| \\ \geq -1.65 + 0.3 + 0.5 - 0.5 \\ \geq -1.35 \text{ V}$$

$$V_{0(min)} \leq V_{DD} - |V_{ov}| \\ \leq +1.65 - 0.5$$

$$\leq +1.15 \text{ V}$$

$$V_{0(min)} \geq -V_{SS} + V_{OV6} \\ \geq -1.65 + 0.5 \\ \geq -1.15 \text{ V}$$

**Ex: 10 . 2**

$$|V_A| = 30 \text{ V}, I_6 = 0.5 \text{ mA},$$

$$V_{OV1} = 0.2 \text{ V}, V_{OV6} = 0.5 \text{ V}$$

$$I = K(V_{ov})^2$$

$$\text{For } Q_6: 0.5 = K(0.5)^2 \Rightarrow K = 2 \text{ mA/V}^2$$

$$\text{For } Q_2: I_2 = 2(0.2)^2 \Rightarrow I_2 = 0.8 \text{ mA}$$

$$g_m = \frac{I}{V_{ov}} \Rightarrow g_{m2} = \frac{0.8}{0.2} = 4 \text{ mA/V}$$

$$\Rightarrow g_{m6} = \frac{0.5}{0.5} = 1 \text{ mA/V}$$

$$r_o = \frac{V_A}{I} \Rightarrow r_{o2} = \frac{20}{0.8} = 25 \text{ k}\Omega$$

$$\Rightarrow r_{o6} = r_{o7} = \frac{20}{0.5} = 40 \text{ k}\Omega$$

$$A_1 = -g_{m2}r_{o2} = -4 \times 25 = -100 \text{ V/V}$$

$$A_2 = -g_{m6}r_{o6} = -1 \times 40 = -40 \text{ V/V}$$

$$A = A_1 A_2 = (-100)(-40) = +4000 \text{ V/V}$$

$$R_o = (r_{o6} \parallel r_{o7}) = \frac{40\text{k}}{2} = 20 \text{ k}\Omega$$


**Ex: 10 . 3**

The small-signal equivalent circuit for the op-amp in Fig. 10.1 on page of the Text is redrawn below for a unity-gain buffer.

From Eq 10.8, 10.9, 10.14, 10.15 on page of the

Text :  $G_{m1} = g_{m1}, G_{m2} = g_{m6}$

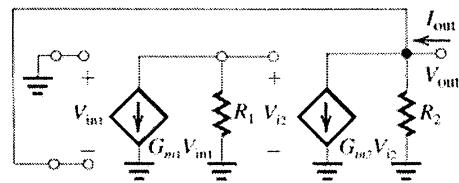$R_1 = r_{o2} \parallel r_{o4}, R_2 = r_{o6} \parallel r_{o7}$



From the above we can write :

$$I_{out} = G_{m2}V_{i2} + \frac{V_{out}}{R_2} \text{ where}$$

$$V_{i2} = -G_{m1}V_{in1}R_1 \text{ and}$$

$$V_{in1} = -V_{out} \Rightarrow V_{i2} = G_{m1}R_1V_{out} \text{ therefore :}$$

$$I_{out} = g_{m6}g_{m1}R_1V_{out} + \frac{V_{out}}{R_2}$$

$$I_{out} = V_{out} \left( g_{m6}g_{m1}R_1 + \frac{1}{R_2} \right) \text{ or}$$


$$R_o = \frac{1}{g_{m6}g_{m1}(r_{o2} \parallel r_{o4}) + \frac{1}{r_{o6} \parallel r_{o7}}}$$

Since  $r_{o6} \parallel r_{o7}$  is huge, we can neglect  $\frac{1}{r_{o6} \parallel r_{o7}}$

and have :

$$R_o \approx \frac{1}{g_{m6}g_{m1}(r_{o2} \parallel r_{o4})}$$

**Ex: 10 . 4**

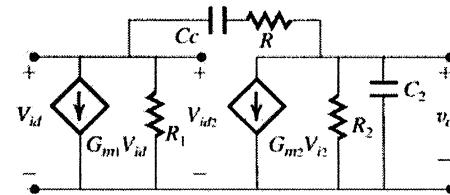

$$G_{m1} = 1 \text{ mA/V}, G_{m2} = 2 \text{ mA/V}$$

$$C_c = 1 \text{ pF}$$

$$r_{o2} = r_{o4} = 100 \text{ k}\Omega, r_{o6} = r_{o7} = 40 \text{ k}\Omega$$

$$(a) f_t = \frac{G_{m1}}{2\pi C_c} = \frac{1 \text{ mA/V}}{2\pi \cdot 1 \text{ pF}} = 100 \text{ MHz}$$

$$\Rightarrow C_c = 1.6 \text{ pF}$$

$$A_1 = -G_{m1}R_1 = (1 \times 10^{-3})(r_{o2} \parallel r_{o4})$$

$$= (1 \times 10^{-3})(100 \text{ k}\Omega / 2) = -50 \text{ V/V}$$

$$A_2 = -G_{m2}R_2 = (2 \times 10^{-3})(r_{o6} \parallel r_{o7})$$

$$= (2 \times 10^{-3})(40 \text{ k}\Omega / 2) = -40 \text{ V/V}$$

$$A = A_1 \cdot A_2 = (-50)(-40) = +2000$$

$$f_p = f_t / A = 100 \times 10^6 / 2 \times 10^3 = 50 \text{ KHz}$$

(b) to move zero to  $S = \infty$

$$R = \frac{1}{G_{m2}} = \frac{1}{2 \times 10^{-3}} = 500 \text{ }\Omega$$

$$f_{p2} \approx \frac{G_m}{2\pi C_2} = \frac{0.2 \times 10^{-3}}{2\pi 10^{-9}} = 318 \times 10^6 \text{ Hz}$$

$$\theta = \tan^{-1} \frac{f_t}{f_p} = \tan^{-1} \frac{100 \times 10^6}{318 \times 10^6} = 17.4^\circ$$

$$\text{PM} = 90 - \theta = 72.6^\circ$$

### Ex: 10.5

Find SR for  $f_t = 100 \text{ MHz}$

$$V_{OV1} = 0.2 \text{ V}$$

$$\text{SR} = 2\pi f_t V_{OV} = 2\pi \times 100 \times 10^6 \times 0.2 = 125.67 \approx 126 \text{ V}/\mu\text{A}$$

$$\text{SR} = \frac{I}{C_C} \Rightarrow I = \text{SR} \times C_C$$

$$\therefore I = 126 \times 10^6 \times 1.6 \times 10^{-12} = 200 \mu\text{A}$$

### Ex: 10.6

$$V_{ICM(\max)} \leq V_{DD} - V_{OV9} + V_m$$

$$\leq +1.65 - 0.3 + 0.5 = +1.85 \text{ V}$$

$$V_{ICM(\min)} \geq -V_{SS} + V_{OV11} + V_{OV1} + V_m \geq -1.65 + 0.3 + 0.3 + 0.5 = -0.55 \text{ V}$$

$$V_{o(\max)} \leq V_{DD} - |V_{OV9}| - |V_{OV}|$$

$$\leq +1.65 - 0.3 - 0.3 = +1.05 \text{ V}$$

$$V_{o(\min)} \geq -V_{SS} + V_{OV11} + V_{OV1} + V_m \geq -1.66 + 0.3 + 0.3 + 0.5 = -0.55 \text{ V}$$

### Ex: 10.7

$$|V_A| = 20 \text{ V}, V_{OV} = 0.2 \text{ V}, I = 100 \mu\text{A}$$

$$G_m = \frac{2I}{V_{OV}} = \frac{2 \times 100 \times 10^{-6}}{0.2} = 1.0 \text{ mA/V}$$

$$r_o = \frac{V_A}{I} = \frac{20 \times 10^6}{100} = 200 \text{ k}\Omega$$

$$R_o = [g_m r_{o4}(r_{o2} \parallel r_{o10})] \parallel [g_m r_{o6} r_{o8} r_{o5}]$$

$$= g_m r_o^2 \left[ \frac{1}{2} (1 \parallel 2) \right]$$

$$= 1.0 \times 200^2 \times 1/3 \times 10^6 = 13.33 \text{ M}\Omega$$

$$A = G_o R_o = 1.0 \times 10^{-3} \times 13.33 \times 10^6$$

$$= 13.33 \times 10^3 \text{ V/V}$$

### Ex: 10.8

Given : all  $V_{OV} = 0.3 \text{ V}$ ,  $|V_T| = 0.7 \text{ V}$

$$V_{DD} = V_{SS} = 2.5 \text{ V}$$

(a)  $V_{IC(\max)}$  for NMOS

$$V_{ICM(\max)} \leq V_{DD} - V_{OV} + V_T$$

$$\leq +2.5 - 0.3 + 0.7 = +2.9 \text{ V}$$

$$V_{ICM(\min)} \geq -V_{SS} + V_{OV} + V_{OV} + V_T$$

$$\geq -2.5 + 0.3 + 0.3 + 0.7 = -1.2 \text{ V}$$

$$\therefore -1.2 \text{ V} \leq (V_{ICM})_N \leq +2.9 \text{ V}$$

(b) By Sym.

$$-2.9 \text{ V} \leq (V_{ICM})_P \leq +1.2 \text{ V}$$

$$(c) -1.2 \text{ V} \leq (V_{ICM})_{\text{BOTH}} \leq +1.2 \text{ V}$$

$$(d) -2.9 \text{ V} \leq (V_{ICM})_{\text{overall}} \leq +2.9 \text{ V}$$

### Ex: 10.9

$$I_1 = \frac{1}{2} K(W/L)(V_{GS1} - V_T)^2$$

$$I_2 = \frac{1}{2} K(W4/L)(V_{GS2} - V_T)^2$$

For  $I_1 = I_2$ :

$$(V_{GS1} - V_T)^2 = 4(V_{GS2} - V_T)^2$$

$$\text{i.e., } V_{GS1} - V_T = 2(V_{GS2} - V_T)$$

$$\text{or } V_{GS1} = 2V_{GS2} - V_T$$

### Ex: 10.10

$$\text{npn : } I_S = 10^{-14} \text{ A}, \beta = 200, V_A = 125 \text{ V}$$

$$\text{pnp : } I_S = 10^{-14} \text{ A}, \beta = 50, V_A = 50 \text{ V}$$

$$I = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\Rightarrow V_{BE} = V_T \ln \frac{I}{I_S}$$

$$V_{BE} = 25 \text{ mV} \ln \frac{10^{-3}}{10^{-14}} = 633 \text{ mV}$$

$$g_m = \beta / r_E = 200 / 5k = 40 \text{ mA/V}$$

$$r_\pi = \beta_{ee} = 200 \times 25 = 5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{125 \text{ V}}{1 \text{ mA}} = 125 \text{ k}\Omega$$

### Ex: 10.11

$$I = I_S e^{\frac{V_B - V_T}{V_T}} \Rightarrow V_{BE} = V_T \ln(I/I_S)$$

$$\text{and } I_3 = I_4, I_1 = I_2$$

$$\text{From ect : } V_{BE1} + V_{BE2} = V_{BE3} + V_{BE4}$$

$$V_T \ln \left[ \frac{I_1}{I_{S1}} \right] + V_T \ln \left[ \frac{I_2}{I_{S2}} \right] = V_T \ln \left[ \frac{I_3 I_4}{I_{S3} I_{S4}} \right]$$

$$\therefore \ln \left[ \frac{I_1^2}{I_{S1} I_{S2}} \right] = \ln \left[ \frac{I_3^2}{I_{S3} I_{S4}} \right]$$

$$\therefore I_3 = I_1 \left[ \frac{I_{S3} I_{S4}}{I_{S1} I_{S2}} \right]^{\frac{1}{2}}$$

**Ex: 10.12**

$V_{BE} = 0.7 \text{ V}$  for  $I_C = 1 \text{ mA}$  for Q11

$I_C = 10 \mu\text{A}$  for Q10

$$V_{BE10} = 0.7 + V_t \ln \left[ \frac{10 \mu\text{A}}{1 \text{ mA}} \right] = 0.585 \text{ V}$$

Voltage across  $R_4 = V_{BE10} - V_{BE11}$

$$= 0.7 - 0.585 = 0.115 \text{ V}$$

$$\Rightarrow I_{R4} = \frac{V_{R4}}{R_4} \Rightarrow R_4 = \frac{0.115 \text{ V}}{10 \mu\text{A}} = 11.5 \text{ k}\Omega$$

**Ex: 10.13**

$$V_{ICM(max)} = V_{DD} - V_{BES} - V_{iss} + V_{BE}$$

$$= +15 - 0.6 - 0.3 + 0.6$$

$$= +14.7 \text{ V}$$

$$V_{ICM(min)} = -V_{SS} + V_{BE5} + V_{BE7} + V_{3sat} + V_{BE1}$$

$$= -15 + 0.6 + 0.6 + 0.3 + 0.6$$

$$= -12.9 \text{ V}$$

(neglecting  $R_1$  &  $R_2$  drops)

**Ex: 10.14**

Assume Q18, Q19 (now diode connected transistors) have normal area

Q14, Q20 have area = 3 \* normal

$$I_{14} = 0.25I_{REF} \sqrt{\frac{I_{S14} \cdot I_{S20}}{I_{S18} \cdot I_{S19}}}$$

$$I_{14} = 180 \mu\text{A} \sqrt{\frac{3I}{I} \cdot \frac{3I}{I}}$$

$$I_{14} = 180 \mu\text{A} \times 3 = 540 \mu\text{A}$$

**Ex: 10.15**

Assume  $I_{C7} = I_{C5} = I_{C6} = 9.5 \mu\text{A}$

$$(a) V_{B6} = I_E(R_2 + r_{e6}) = i_e(1 + 2.63) \\ = 3.63I_E$$

$$(b) I_{E7} = \frac{V_{B6}}{R_3} + I_{B5} + I_{B6}$$

$$= \frac{V_{B6}}{R_3} + \frac{2I_E}{\beta + 1} = \frac{3.63I_E}{50} + \frac{2I_E}{201} \\ = 0.08I_E$$

$$(c) I_{R7} = \frac{V_{E7}}{\beta + 1} = \frac{0.08I_E}{201} \approx 0.0004I_E$$

$$(d) V_{R7} = V_{B6} + I_{E7}r_{e7} \\ = 3.63I_E + 0.08I_E \times \frac{25 \text{ mV}}{9.5 \mu\text{A}} \\ = 3.84 \text{ k}\Omega \times I_E$$

$$(e) R_{in} = \frac{(\beta + 1)V_{B7}}{I_E} \approx 3.84 \text{ k}\Omega$$

**Ex:**

See Fig 10.22 on page of the Text, Let  $R_1 = R$ ,

$R_2 = R + \Delta R$  Assume  $\beta \gg 1$  and  $r_{e5} = r_{e6}$ , then

$$V_{B5} = V_{B6} = i(r_{e5} + R_1) = i(r_{e6} + R_2)$$

$$\therefore i_{C6} = \frac{i(r_{e5} + R)}{r_{e5} + R + \Delta R}$$

$$i_o = i_{C6} - i = i$$

$$\therefore i_6 = \frac{i(r_{e5} + R)}{r_{e5} + R + \Delta R} - i = i \frac{\Delta R}{r_{e5} + R + \Delta R}$$

$$\Rightarrow \epsilon_m = \frac{\Delta R}{r_{e5} + R + \Delta R}$$

For  $\frac{\Delta R}{R} = 0.02$  :

$$\epsilon_m = \frac{0.02R}{R + 0.02R + r_{e5}} = \frac{0.02}{1.02 + \frac{r_{e5}}{R}}$$

Substituting  $R = 1 \text{ k}\Omega$  and  $r_e = 2.63 \text{ k}\Omega$  for 741 op-amp, we have

$$\epsilon_m = \frac{0.02}{1.02 + \frac{2.63}{1}} = 5.5 \times 10^{-3}$$

**Ex: 10.17**

From Fig 10.23 on page of the Text:

$$R_o = R_{o9} \parallel R_{o10}$$

$$R_{o9} = r_{o9} = \frac{V_A}{I} = \frac{50}{19 \times 10^{-6}} = 2.63 \text{ M}\Omega$$

$$R_{o10} = r_{o10}(1 + g_{m10}(r_{o10} \parallel R_4)) = \frac{125}{19 \times 10^{-6}}$$

$$\left( 1 + \frac{19 \times 10^{-6}}{25 \times 10^{-3}} \left( \frac{200 \times 25 \times 10^{-3}}{19 \times 10^{-6}} \parallel 5 \times 10^3 \right) \right)$$

$$R_{o10} = 31.1 \text{ M}\Omega$$

$$R_o = 2.63 \parallel 31.1 = 2.42 \text{ M}\Omega$$

**Ex: 10.18**

From Eq. 10.93 we have:  $G_{mem} = \frac{\epsilon_m}{2R_o}$ . From

Ex. 10.16 and 10.17 in the Text, we have:

$$\epsilon_m = 5.5 \times 10^{-3}, R_o = 2.43 \text{ M}\Omega$$

Hence:

$$G_{mem} = \frac{5.5 \times 10^{-3}}{2 \times 2.43 \times 10^6} = 1.13 \times 10^{-6} \text{ mA/V}$$

From Eq. 10.95 we have:

$$CMRR = 2g_{m1}(R_{o9} \parallel R_{o10}) / \epsilon_m$$

$$CMRR = \frac{2 \left( \frac{9.5 \times 10^{-6}}{25 \times 10^{-3}} \right) \left( \frac{2.63 \mu \times 31.1 \mu}{2.63 \mu + 31.1 \mu} \right)}{5.5 \times 10^{-3}}$$

$1.68 \times 10^5$  or 104.5 dB

If the common-mode feedback is not present, as explained in the text, common-mode transconductance and common-mode gain are both reduced by a factor of  $\beta_p$ . Hence,

$$CMRR = \frac{1.68 \times 10^5}{50} = 3360 \text{ or}$$

$$CMRR = 70.5 \text{ dB}$$

Ex: 10.19

$$\beta_{16} = \beta_{17} = 200$$

$$r_{e16} = \frac{25 \text{ mV}}{16.2 \mu\text{A}} = 1.54 \text{ k}\Omega$$

$$r_{e17} = \frac{25 \text{ mV}}{0.55 \text{ mA}} = 45.5 \Omega$$

$$R_g = 100 \Omega, R_9 = 50 \text{ k}\Omega$$

Substituting into Eq. 10.77

$$R_{i2} = 201[1.54 + 50 \parallel (201 \times 0.0455)] \\ \approx 4 \text{ M}\Omega$$

Ex: 10.20

$$i_{e17} = \frac{\beta}{\beta + 1} \cdot \frac{V_{b17}}{r_{e17} + R_g} \approx \frac{V_{b17}}{45.5 + 100} = \frac{V_{b17}}{145.5}$$

$$V_{b17} = V_{i2} \frac{(R_9 \parallel R_{i17})}{(R_9 \parallel R_{i17}) + r_{e16}}$$

$$\text{needs } R_{i17} = (\beta + 1)(r_{e17} + R_g)$$

$$= 201(45.5 + 100) = 29.2 \text{ k}\Omega$$

$$\therefore V_{b17} \approx V_{i2} \times 0.92$$

Ex: 10.21

$$R_{o2} = R_{o13B} \parallel R_{o17}$$

$$\text{where } R_{o13B} = r_{o13B} = \frac{50\text{V}}{0.55 \text{ mA}} = 90.9 \text{ k}\Omega$$

$$R_{o17} = r_{o17}(1 + g_{m17}(R_8 \parallel r_{\pi17}))$$

$$r_{o17} = \frac{125\text{V}}{0.55 \text{ mA}} = 227.3 \text{ k}\Omega$$

$$g_{m17} = \frac{0.55 \text{ mA}}{0.025 \text{ mV}} = 22 \text{ mA/V}$$

$$r_{o17} = \frac{\beta}{g_m} = \frac{200}{22} = 9.09 \text{ k}\Omega$$

$$R_8 = 100 \Omega$$

Thus  $R_{o17} \Rightarrow 722 \text{ k}\Omega$

Hence  $R_{o2} = 90.9 \parallel 722k \approx 81 \text{ k}\Omega$

Ex: 10.22


$$\frac{I_T}{V_T} = \frac{1}{18.8} + 6.6 \times 0.917 = 0.05 + 6.05$$

$$= 6.11$$

open-circuit voltage gain

$$(A_2)_{\text{oc}} = -G_{m2} R_{o2} \\ = -6.5 \times 8.1 = -52.65 \text{ V/V}$$

Ex: 10.23

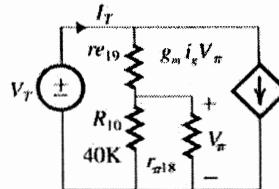

$$r_{e19} = \frac{25 \text{ mV}}{16 \mu\text{A}} = 1.56 \text{ K}$$

$$r_{\pi18} = \frac{200}{40 \times 0.165} = 30.3 \text{ k}\Omega$$

$$I_T = \frac{V_T}{r_{e19} + (R_{10} \parallel r_{\pi18})} + \frac{g_{m18} V_T (R_{10} \parallel r_{\pi18})}{r_{e19} + (R_{10} \parallel r_{\pi18})}$$

$$\therefore I_T = V_T \left[ \frac{1}{18.8 \text{ K}} + \frac{6.6 \times 0.917}{18.8 \text{ K}} \right] \\ = V_T [0.05 + 6.05]$$

$$\Rightarrow R_T = \frac{V_T}{I_T} = 163 \Omega$$

Ex: 10.24

$$R_O = r_{e14} + \frac{\left[ R_{18,19} + r_{e23} + \frac{R_{O2}}{\beta_{23} + 1} \right]}{\beta_{14} + 1}$$

$$R_O \approx \frac{0.025}{0.005} + \frac{\left( 163 + \frac{25 \text{ M}}{180 \mu\text{A}} + \frac{81 \text{ K}}{51} \right)}{201}$$

Assuming  $\beta_{23} = 50$  and  $\beta_{14} = 200$  and

$$I_{e13A} = 180 \mu\text{A}$$
 from Table

$$R_O \approx \frac{5 + (163 + 139 + 1588)}{201} = 5 + 94$$

$$R_O \approx 14.4 \Omega$$


**Ex: 10.25**

$$SR = 0.63 \text{ V}/\mu\text{S}$$

using eq.

$$f_p = \frac{SR}{2\pi V_{O \text{ max}}} = \frac{0.63}{2\pi(10) \times 1 \times 10^{-6}} = 10 \text{ kHz}$$

**Ex: 10.26**

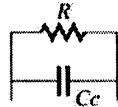

$$A_o = 2.43147 \times 10^4$$

$$G_{m1} = \frac{1}{5.26} \times 10^{-3}$$

$$\therefore A_o = G_{m1} R$$

$$\therefore R = A_o / G_{m1} \Rightarrow 1279 \text{ MHz}$$

**Ex: 10.27**

$$SR = \frac{W_t}{a} \text{ where}$$

$$a = \frac{G_{m1}}{2I} \Rightarrow SR = \frac{2I}{G_{m1}} \times w_t$$

with  $R_E$  inserted in emitters of  $Q_3, Q_4$

$$\begin{aligned} G_{m1} &= 2 \times \frac{1}{4r_e + 2R_E} = \frac{1}{2r_e + R_E} \\ &= \frac{1}{2 \times \frac{0.025 \text{ mV}}{I} + R_E} = \frac{I}{2r_T + IR_E} \end{aligned}$$

for  $I = 9.5 \times 10^{-6} \text{ A}$

$$R_E = \frac{0.050}{9.5 \times 10^{-6}} = 5.26 \text{ k}\Omega$$

$$\text{now } SR = \frac{2Iw_t}{I} \times (2V_T + IR_E)$$

$$= 4[V_T + I_R E/2]^w_t \text{ QED}$$

$$\text{new } C_c : \frac{G_{m1}^2}{C_c} = \frac{G_{m1}}{2C_c}$$

$\therefore C_c$  must be reduced  $\times$  factor of 2

$$C_{c \text{ new}} = \frac{C_{c \text{ old}}}{2} = \frac{30}{2} = 15 \text{ pF}$$

Gain  $\propto G_{m1} \therefore A$  also halved

$$A_{\text{new}} = A_{\text{old}} - 6 \text{ dB} = 101.7 \text{ dB}$$

$$f_p = f_t / A = f_t \text{ has been halved}$$

$$f_{p \text{ new}} = 2 \times f_{p \text{ old}} = 8.2 \text{ Hz}$$

**Ex: 10.28**

using eq. (10.129)

$$I = \frac{V_T}{R_2} \ln\left(\frac{I_{S2}}{I_{S1}}\right) \text{ where } V_T = 25 \text{ mV}$$

$$R_3 = R_4 = \frac{0.2}{10 \mu} = 20,000 \Omega$$

$$R_2 = \frac{V_T}{I} \ln\left(\frac{I_{S2}}{I_{S1}}\right)$$

$$R_2 = \frac{25 \text{ m}}{10 \mu} \ln(2) = 1,733 \Omega$$

**Ex: 10 . 29**

use  $R_3 = R_4 = 20 \text{ k}\Omega$

and  $I = 10 \mu\text{A}$  from Exercise 10 . 28

$$\text{For } I_8 = 10 \mu\text{A} = I, \text{ then } \left(\frac{W}{L}\right)_8 = \left(\frac{W}{L}\right)_3$$

$$\text{For } I_9 = 20 \mu\text{A} = 2I, \text{ then } \left(\frac{W}{L}\right)_9 = 2\left(\frac{W}{L}\right)_3$$

$$\text{For } I_{10} = 5 \mu\text{A} = \frac{I}{2}, \text{ then } \left(\frac{W}{L}\right)_{10} = \frac{1}{2}\left(\frac{W}{L}\right)_3$$

Since  $V_S$  has to equal the original

$(V_{CC} - I \cdot R_4) = V_{CC} - 0.2$  so  $R_8$ ,  $R_9$ , and  $R_{10}$  can be found by


$$R_8 = \frac{0.2}{10 \mu} = 20 \text{ k}\Omega$$

$$R_9 = \frac{0.2}{20 \mu} = 10 \text{ k}\Omega$$

$$R_{10} = \frac{0.2}{5 \mu} = 40 \text{ k}\Omega$$

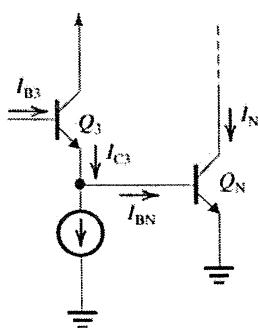**Ex: 10 . 30**

$$(a) \text{Find } \frac{i_N}{i_{B3}} \text{ for } (V_{IN})$$



Assume

$$i_{C3} \approx i_{BN}$$

$$i_{B3} \leq \frac{i_{C3}}{\beta_N}$$


$$i_{C3} \approx i_{BN} = \frac{i_N}{\beta_N}$$

$$\therefore \frac{i_N}{i_{B3}} = \frac{i_N}{\left(\frac{i_N}{\beta_N}\right)\left(\frac{1}{\beta_N}\right)} = \beta_N^2$$

$$\text{Find } \frac{i_P}{i_{B1}} \text{ for } (V_{IP})$$

Assume  $i_{BP} \approx i_{E2}$  and  $i_{C1} \approx i_{B2}$
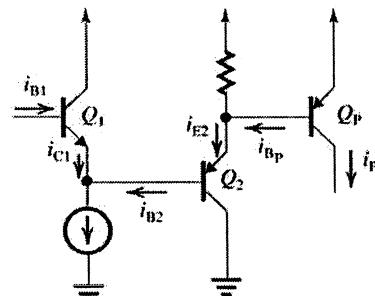
$$\therefore \frac{i_P}{i_{B1}} = \frac{i_P}{\left(\frac{i_P}{\beta_P}\right)\left(\frac{1}{\beta_P}\right)\left(\frac{1}{\beta_N}\right)} = \beta_P^2 \cdot \beta_N$$



$$(b) i_{B3} = \frac{i_N}{\beta_N^2} \text{ (Assume } \beta_N \approx 40 \text{ )}$$

$$i_{B3} = \frac{10 \text{ mA}}{(40)^2} = 6.25 \mu\text{A}$$

$$i_{B1} = \frac{i_P}{\beta_P \beta_N} \text{ (Assume } \beta_P \approx 10 \text{ )}$$

$$i_{B1} = \frac{10 \text{ mA}}{(10)^2 \cdot 40} = 2.5 \mu\text{A}$$

**Ex: 11.1**

$$A = -20 \log |T| \text{ [dB]}$$

$ T  = 1$	0.99	0.9	0.8	0.7	0.5	0.1	0
$A \approx 0$	0.1	1	2	3	6	20	$\infty$

**Ex: 11.2**

$$A_{\max} = 20 \log 1.05 - 20 \log 0.95 = 0.9 \text{ dB}$$

$$A_{\min} = 20 \log \left[ \frac{1}{0.001} \right] = 40 \text{ dB}$$

**Ex: 11.3**

$$\begin{aligned} T(s) &= k \frac{(s+j2)(s-j2)}{\left(s+\frac{1}{2}+j\sqrt{\frac{3}{2}}\right)\left(s+\frac{1}{2}-j\sqrt{\frac{3}{2}}\right)} \\ &= k \frac{(s^2+4)}{s^2+s+\frac{1}{4}+\frac{3}{4}} \\ &= k \frac{(s^2+4)}{s^2+s+1} \end{aligned}$$

$$T(o) = k \frac{4}{1} = 1$$


$$k = \frac{1}{4}$$

$$\therefore T(s) = \frac{1}{4} \frac{(s^2+4)}{s^2+s+1}$$

**Ex: 11.4**

$$\begin{aligned} T(s) &= k \frac{s(s^2+4)}{(s+0.1+j8)(s+0.1-j8)} \\ &\quad (s+0.1+j1.2)(s+0.1-j1.2) \\ &= k \frac{s(s^2+4)}{(s^2+0.23+0.65)(s^2+0.23+1.45)} \end{aligned}$$

**Ex: 11.5**

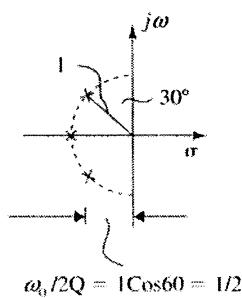

$$\omega_0/2Q = 1 \cos 60^\circ = 1/2$$

As shown, the pair of complex poles has  $\omega_0 = 1$  and  $Q = 1$

$$\omega_0/zQ = 1 \cos 60^\circ = \frac{1}{2}$$

$$\frac{1}{2Q} = \frac{1}{2}$$

$$Q = 1$$

$$\therefore T(s) = k \frac{1}{(s+1)(s^2+s+1)}$$

$$\text{since } T(0) = 1, k = 1$$

$$\text{Thus: } T(s) = \frac{1}{(s+1)(s^2+s+1)}$$

$$T(j\omega) = \frac{1}{\sqrt{1+\omega^2}\sqrt{(1-\omega^2)^2+\omega^2}}$$

$$= \frac{1}{\sqrt{(1-\omega^4)(1-\omega^2)+\omega^2(1+\omega^2)}}$$

$$= \frac{1}{\sqrt{1-\omega^4-\omega^2+\omega^6+\omega^2+\omega^4}}$$

$$\frac{1}{\sqrt{1+\omega^6}} \text{ Q.E.D}$$

$$\text{Thus: } \frac{1}{\sqrt{2}} = \frac{1}{(1+\omega_{3\text{dB}}^6)^{1/2}} \Rightarrow \omega_{3\text{dB}} = 1 \text{ rad/s}$$

$$A(3) = -20 \log \frac{1}{\sqrt{1+3^6}} = 28.6 \text{ dB}$$

**Ex: 11.6**

$$\epsilon = \sqrt{10^{-10} - 1} = \sqrt{10^{-10}} - 1 = 0.5088$$

$$|T(j\omega)| = \frac{1}{\sqrt{1+\epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}}}$$

$$A(\omega_s) = -20 \log |T(j\omega_s)|$$

$$= 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$$

$$\text{Thus, } 10 \log [1 + 0.5888^2 \times 1.5^{2N}] \geq 30$$

$$N = 10 \text{ LHS} = 29.35 \text{ dB}$$

$$N = 11 \text{ LHS} = 32.87 \text{ dB}$$

∴ Use  $N = 11$  and obtain

$$A_{\min} = 32.87 \text{ dB}$$

For  $A_{\max}$  to be exactly 30 dB

$$10 \log [1 + \epsilon^2 \times 1.5^{22}] = 30$$

$$\epsilon = 0.3654 \Rightarrow A_{\max} + 20 \log \sqrt{1 + 0.3654^2} = 0.54 \text{ dB}$$


**Ex: 11.7**

The real pole is at  $s = -1$

The complex conjugate poles are at


$$s = 2 \cos 60^\circ \pm j \sin 60^\circ$$

$$= -0.5 \pm j\sqrt{\frac{3}{2}}$$

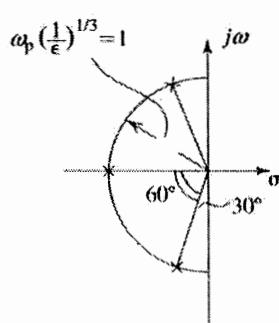

$$\begin{aligned} T(s) &= \frac{1}{(s+1)(s+0.5+j\sqrt{\frac{3}{2}})(s+0.5-j\sqrt{\frac{3}{2}})} \\ &= \frac{1}{(s+1)(s^2+s+1)} \text{ for } DC_{\text{pass}} = 1 \end{aligned}$$

Ex: 11.8

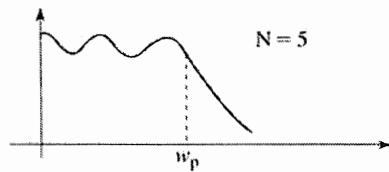

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \cos^2 \left[ N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right]}}$$

for  $\omega < \omega_p$ .

Peaks are obtained when

$$\cos^2 N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) = 0$$

$$\cos^2 N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) = 0$$

$$N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) = (2k+1)\frac{\pi}{2}, k = 0, 1, 2$$

$$\hat{\omega} = \omega_p \cos \left[ \frac{(2k+1)\pi}{10} \right], k = 0, 1, 2$$

$$\hat{\omega}_1 = \omega_p \cos \left( \frac{\pi}{10} \right) = 0.95\omega_p$$

$$\hat{\omega}_2 = \omega_p \cos \left( \frac{3}{10}\pi \right) = 0.59\omega_p$$

$$\hat{\omega}_3 = \omega_p \cos \left( \frac{5}{10}\pi \right) = 0$$

Valleys are obtained when

$$\cos^2 \left[ N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right] = 1$$

$$N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) = k\pi, k = 0, 1, 2$$

$$\therefore \hat{\omega} = \omega_p \cos \left( \frac{k\pi}{5} \right), k = 0, 1, 2$$

$$\hat{\omega}_1 = \omega_p \cos 0 = \omega_p$$

$$\hat{\omega}_2 = \omega_p \cos \frac{\pi}{5} = 0.81\omega_p$$

$$\hat{\omega}_3 = \omega_p \cos \frac{2\pi}{5} = 0.31\omega_p$$

Ex: 11.9

$$\epsilon = \sqrt{10^{10} - 1} = \sqrt{10^{10} - 1} = 0.3493$$

$$A(\omega_3) = 10 \log \left[ 1 + \epsilon^2 \cosh^2 \left( N \cosh^{-1} \frac{\omega_3}{\omega_p} \right) \right]$$

$$= 10 \log [1 + 0.3493^2 \cosh^2 (7 \cosh^{-1} 2)]$$

$$= 64.9 \text{ dB}$$

$$\text{For } A_{\text{max}} = 1 \text{ dB}, \epsilon = \sqrt{10^{0.1} - 1} = 0.5088$$

$$A(\omega_3) = 10 \log [1 + 0.5088^2 \cosh^2 (7 \cosh^{-1} 2)]$$

$$= 68.2 \text{ dB}$$

This is an increase of 3.3 dB

Ex: 11.10

$$\epsilon = \sqrt{10^{10} - 1} = 0.5088$$

(a) For the Chebyshev Filter:

$$A(\omega_s) = 10 \log [1 + 0.5088^2 \cosh^2 (N \cosh^{-1} 1.5)]$$

$$\geq 50 \text{ dB}$$

$$N = 7.4 \therefore \text{choose } N = 8$$

Excess Attenuation =

$$10 \log [1 + 0.5088^2 \cosh^2 (8 \cosh^{-1} 1.5)] - 50$$

$$= 55 - 50 = 5 \text{ dB}$$

(b) For a Butterworth Filter

$$\epsilon = 0.5088$$

$$A(\omega_s) = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$$


$$= 10 \log [1 + 0.5088^2 (1.5)^{16}] \geq 50$$

$$N = 15.9 \therefore \text{choose } N = 16$$

Excess attenuation =

$$10 \log [(1 + 0.5088^2 (1.5)^{12}) - 50] = 0.5 \text{ dB}$$

**Ex: 11.11**

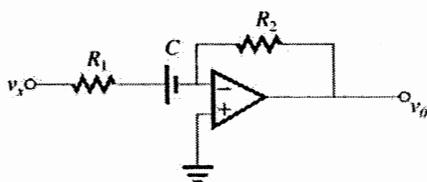

$$10^4 = \frac{1}{CR_1} \quad R_1 = 10 \text{ k}\Omega$$

$$C = 0.01 \mu\text{F}$$

$$\text{H.F. Gain} = \frac{-R_2}{R_1} = -10$$

$$R_2 = 100 \text{ k}\Omega$$

**Ex: 11.12**

Refer to Fig. 11.14

$$\omega_0 = \frac{1}{CR} = 10^3 \text{ rad/s}$$

For R arbitrarily selected to be

$$10 \text{ k}\Omega \quad C = \frac{1}{10^3 \times 10^4} = 0.1 \mu\text{F}$$

The two resistors labelled  $R_i$  can also be selected to be 10 kΩ each.

**Ex: 11.13**

$$T(s) = \frac{\omega_0^2}{s + s\sqrt{2\omega_0 + \omega_0^2}}$$

(for dc gain = 1)

$$|T(j\omega)| = \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\omega_0^2\omega^2)}}$$

$$= \frac{\omega_0^2}{\sqrt{\omega_0^4 + \omega^4}}$$

$$= \frac{\omega_0^2}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^4}}$$

At  $\omega = \omega_0$ ,  $|T| = \frac{1}{\sqrt{2}}$  which is 3 dB below the value at dc(unity) Q.E.D.

**Ex: 11.14**



$$\text{This } T(s) = \frac{10^4 s}{s^2 + 10^3 s + 10^{10}}$$


$$\omega_0 = 10^5 \text{ rad/s}$$

$$\frac{\omega_0}{Q} = 10^3 \text{ rad/s}$$

selected to yield a centre frequency gain of 10.

**Ex: 11.15**

(a)

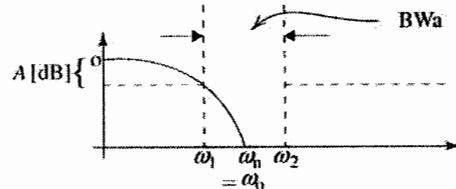

$$T(S) = \frac{s^2 + \omega_0^2}{s^2 + s\omega_0/Q + \omega_0^2}$$

$$|T(j\omega)| = \frac{\omega_0^2 - \omega^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + \frac{\omega^2\omega_0^2}{Q^2}}}$$

$$= \frac{1}{\sqrt{1 + \frac{\omega_0^2\omega^2}{(\omega_0^2 - \omega^2)^2Q^2}}}$$

for any two frequencies  $\omega_1$  and  $\omega_2$  at which  $|T|$  is the same

$$\frac{\omega_1^2\omega_2^2}{(\omega_0^2 - \omega_1^2)^2} = \frac{\omega_1^2\omega_2^2}{(\omega_0^2 - \omega_2^2)^2}$$

$$\omega_1(\omega_0^2 - \omega_2^2) = \omega_2(\omega_0^2 - \omega_1^2)$$

$$\Rightarrow \omega_1\omega_2 = \omega_0^2 \quad (1)$$

Now to obtain attenuation  $\geq A$  dB at  $\omega_1$  and  $\omega_2$  where  $\omega_2 - \omega_1 = BW_a$

$$10 \log \left[ 1 + \frac{\omega_0^2\omega_1^2}{(\omega_0^2 - \omega_1^2)^2Q^2} \right] \geq A$$

$$\frac{\omega_1\omega_0}{\omega_0^2 - \omega_1^2} \frac{1}{Q} \geq \sqrt{10^{A/10} - 1} \quad \text{SUB (1)}$$

$$\frac{\omega_1\omega_0}{\omega_1\omega_2 - \omega_1^2} \frac{1}{Q} \geq \sqrt{10^{A/10} - 1}$$

$$\frac{\omega_0}{\omega_2 - \omega_1} \frac{1}{Q} \geq \sqrt{10^{A/10} - 1}$$

$$\frac{\omega_0}{BW_a} \frac{1}{Q} \geq \sqrt{10^{A/10} - 1}$$

$$\Rightarrow Q \leq \frac{\omega_0}{BW_a \sqrt{10^{A/10} - 1}} \quad \text{Q.E.D.}$$

(b) For  $A = 3$  dB

$$Q = \frac{\omega_0}{BW_3 \sqrt{10^{0.3} - 1}} = \frac{\omega_0}{BW_3}$$

OR  $BW_3 = \omega_0/Q \quad \text{Q.E.D.}$

**Ex: 11.16**

From Fig 10.16(c)

$$\omega_{\max} = \omega_0 \sqrt{\frac{(\omega_n/\omega_0)^2 \left(1 - \frac{1}{2Q^2}\right) - 1}{(\omega_n/\omega_0)^2 + \frac{1}{2Q^2} - 1}}$$

For  $\omega_0 = 1 \text{ rad/s}$ ,  $\omega_n = 1.2 \text{ rad/s}$ ,  $Q = 10$

$$\text{dc gain} = |a_2| \left( \frac{\omega_p^2}{\omega_n^2} \right) = 1$$

$$|a_2| = \omega_0^2 / \omega_n^2 = \frac{1}{1.44}$$

$$\omega_{\max} = 1 \sqrt{\frac{1.44 \left(1 - \frac{1}{200}\right) - 1}{1.44 + \frac{1}{200} - 1}}$$

$$= 0.986 \text{ rad/s}$$

$$|T(j\omega_{\max})| = \frac{|a_2| (\omega_n^2 - \omega_{\max}^2)}{\sqrt{(\omega_n^2 - \omega_{\max}^2)^2 + \left(\frac{\omega_0 \omega_{\max}}{Q}\right)^2}}$$

$$= 3.17$$

$$|T(j\infty)| = Q_2 = \frac{1}{1.44} = 0.69$$

**Ex: 11.17**


$$\text{Maximally flat } \Rightarrow Q = \frac{1}{\sqrt{2}}$$

$$\omega_0 = 2\pi \times 100 \times 10^3$$

Arbitrarily selecting  $R = 1 \text{ k}\Omega$

$$Q = \omega_0 CR \Rightarrow C = \frac{1}{\sqrt{2} \times 2\pi 10^3 \times 10^3}$$


$$= 1125 \text{ pF}$$

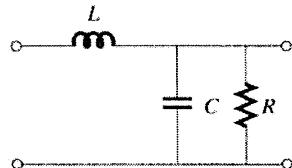

$$\text{Also } Q = \frac{R}{\omega_0 L}$$

$$\therefore L = \frac{R}{\omega_0 Q} = \frac{10^3}{2\pi 10^3 \times \frac{1}{\sqrt{2}}} = 2.25 \text{ mH}$$

**Ex: 11.18**

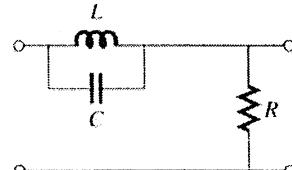

From Exercise 11.16 above 3dB bandwidth

$$= \omega_0 / Q$$

$$2\pi 10 = 2\pi 60 / Q \Rightarrow Q = 6$$

$$Q = \omega_0 CR$$

$$6 = 2\pi 60 \times C \times 10^4 \Rightarrow C = 1.6 \mu\text{F}$$

$$Q = \frac{R}{\omega_0 L}$$

$$L = \frac{R}{\omega_0 Q} = \frac{10^4}{2\pi 60 \times 6} = 4.42 \text{ H}$$

**Ex: 11.19**

$$f_o = 10 \text{ kHz } \Delta f_{3\text{dB}} = 500 \text{ Hz}$$

$$Q = \frac{f_o}{\Delta f_{3\text{dB}}} = \frac{10^4}{500} = 20$$

Using the data at the top of Table 11.1

$$C_A = C_6 = 1.2 \text{ nF}$$

$$R_1 = R_2 = R_3 = R_5 = \frac{1}{\omega_0 C}$$

$$= \frac{1}{2\pi 10^4 \times 1.2 \times 10^{-9}} = 13.26 \text{ k}\Omega$$

$$R_6 = Q / \omega_0 C = \frac{20}{2\pi 10^4 \times 1.2 \times 10^{-9}} = 265 \text{ k}\Omega$$

Now using the data in Table 11.1 for the bandpass case

$$K = \text{centre-frequency gain} = 10$$

$$1 + r_2/r_1 = 10$$

Selecting  $r_1 = 10 \text{ k}\Omega$  then  $r_2 = 90 \text{ k}\Omega$

**Ex: 11.20**

$$\text{Eq (16.25)} \sim \omega_p = 2\pi 10^4$$


$$T(s) = \frac{\omega_p^5}{8.1408(s + 0.2895\omega_p)} \times$$

$$\frac{1}{(s^2 + s0.4684\omega_p + 0.4293\omega_p^2)} \times$$

$$\frac{1}{(s^2 + s0.1789\omega_p + 0.9883\omega_p^2)}$$

The circuit consists of 3 sections in cascade:

(a) First order section

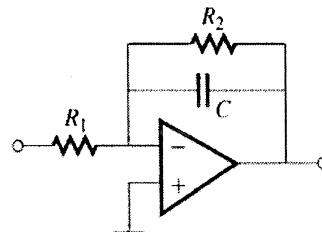

the number coefficient was set so that the dc gain = 1.

$$T(s) = \frac{-0.2895\omega_p}{s + 0.2895\omega_p}$$

Let  $R_1 = 10 \text{ k}\Omega$

dc gain =  $R_2/R_1 = 1 = R_2 = 10 \text{ k}\Omega$

as  $j\omega \rightarrow \infty$


$$|T(j\omega)| \rightarrow \frac{0.2985\omega_p}{\omega} = \frac{1}{\omega CR_1}$$

$$C = \frac{1}{0.2895 \times 2\pi 10^4 \times 10^4} = 5.5 \text{ nF}$$

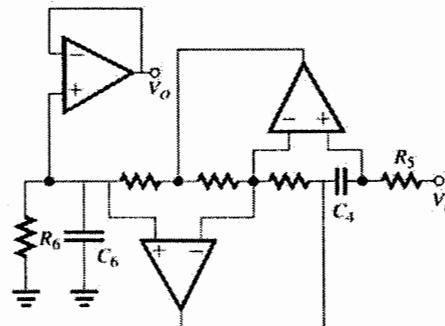(b) Second-Order section with transfer function:

$$T(s) = \frac{0.4295\omega_p^2}{s^2 + 0.4684\omega_p + 0.4293\omega_p^2}$$

where the numerator coefficient was selected to yield a dc gain of unity.



Select  $R_1 = R_2 = R_3 = R_5 = 10 \text{ k}\Omega$

$$\Rightarrow C = \frac{1}{\sqrt{0.4293} \times 2\pi 10^4 \times 10^4} = 2.43 \text{ nF}$$

$$C_4 = C_6 = C = 2.43 \text{ nF}$$

$$Q = \frac{\sqrt{0.4293}\omega_p}{0.4684\omega_p} = 1.4 \Rightarrow R_6 = \frac{Q}{\omega_0 C} = 14 \text{ k}\Omega$$

(c) Second-Order Section with Transfer-function:

$$T(s) = \frac{0.9883\omega_p^2}{s^2 + s0.1789\omega_p + 0.9883\omega_p^2}$$

The circuit is similar to that in (b) above but with

$$R_1 = R_2 = R_3 = R_5 = 10 \text{ k}\Omega$$

$$C_4 = C_6 = \frac{1}{\omega_0 \times 10^4} = \frac{1}{\sqrt{0.9883} \times 2\pi 10^4 \times 10^4} = 1.6 \text{ nF}$$

$$Q = \frac{\sqrt{0.9883}}{0.1789} = 5.56$$

Thus  $R_6 = Q/\omega_0 C = 55.6 \text{ k}\Omega$

Placing the three sections in cascade, i.e. connecting the output of the first-order section to the input of the second-order section in (b) and the output of section (b) to the input of (c) results in the overall transfer function in eq. 11.25

### Ex: 11.21

Refer to the KHN circuit in Fig. 11.24 Choosing  $C = \ln F$

$$R = \frac{1}{\omega_0 C} = \frac{1}{2\pi 10^4 \times 10^{-9}} = 15.9 \text{ k}\Omega$$

Using Eq. 11.62 and selecting  $R_1 = 10 \text{ k}\Omega$

$$R_f = R_1 = 10 \text{ k}\Omega$$

Using Eq. 11.63 and setting  $R_2 = 10 \text{ k}\Omega$

$$R_3 = R_2(2Q - 1) = 10(2 \times 2 - 1) = 30 \text{ k}\Omega$$

$$\text{High frequency gain } K = 2 - \frac{1}{Q} = 1.5 \text{ V/V}$$


The transfer function to the output of the first integrator is

$$\frac{V_{np}}{V_i} = -\frac{1}{SCR} = \frac{V_{np}}{V_i} = \frac{sK/(CR)}{s^2 + s\omega_0/Q + \omega_0^2}$$

Thus the centre-frequency gain

$$= \frac{K \cdot Q}{CR\omega_0} = KQ = 1.5 \times 2 = 3 \text{ V/V}$$

### Ex: 11.22

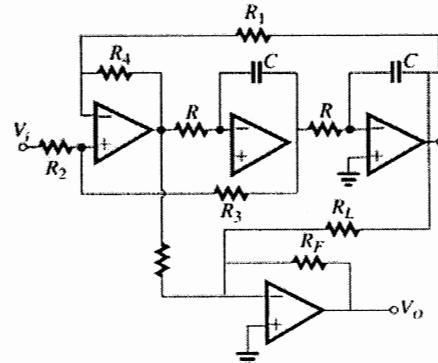

$$\frac{V_o}{V_i} = -K \frac{(R_F/R_H)s^2 + (R_F/R_L)\omega_0^2}{s^2 + s\omega_0/Q + \omega_0^2}$$

given  $C = \ln F$   $R_L = 10 \text{ k}\Omega$

$$R = \frac{1}{\omega_0 C} = \frac{1}{2\pi 5 \times 10^3 \times 10^{-9}} = 31.83 \text{ k}\Omega$$

$$R_1 = 10 \text{ k}\Omega \Rightarrow R_F = 10 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega \Rightarrow R_3 = R_2(2Q - 1)$$

$$= 10(10 - 1) = 90 \text{ k}\Omega$$

$$\frac{R_H}{R_L}\omega_0^2 = \omega_0^2 \Rightarrow R_H = 10 \left(\frac{8}{5}\right)^2 = 25.6 \text{ k}\Omega$$

$$\text{DC gain } K \frac{R_F}{R_L} = \left(2 - \frac{1}{Q}\right) \frac{R_F}{R_L} = 3$$

$$R_F = \frac{3 \times 10}{2 - 1/5} = 16.7 \text{ k}\Omega$$

**Ex: 11.23**

Refer to Fig. 11.25(b)

$$CR = \frac{1}{\omega_0} \Rightarrow C = \frac{1}{2\pi 10^3 \times 10^3} = 1.59 \text{ nF}$$

$$R_d = QR = 20 \times 10 = 200 \text{ k}\Omega$$

Centre frequency gain =  $KQ = 1$

$$\therefore K = \frac{1}{Q} = \frac{1}{20}$$

$$R_s = R/K = 20R = 200 \text{ k}\Omega$$

**Ex: 11.24**

Refer to Fig 11.26 and Table 11.2

$$C = 10 \text{ nF}$$

$$R = \frac{1}{\omega_0 C} = \frac{1}{10^4 \times 10 \times 10^{-9}} = 10 \text{ k}\Omega$$

$$QR = 5 \times 10 = 50 \text{ k}\Omega$$

$$C_1 = C \times \text{flat gain} = 10 \times 1 = 10 \text{ nF}$$

$$R_1 = \infty$$

$$R_2 = \frac{R}{\text{gain}} = R/1 = 10 \text{ k}\Omega$$

$$r = 10 \text{ k}\Omega$$

$$R_3 = \frac{Q_r}{\text{gain}} = \frac{5 \times 10}{1} = 50 \text{ k}\Omega$$

**Ex: 11.25**

From eq 11.76

$$CR = \frac{2Q}{\omega_0} = \frac{2 \times 1}{10^4} = 2 \times 10^4 \text{ s}$$

For  $C = C_1 = C_2 = 1 \text{ nF}$

$$R = \frac{2 \times 10^{-4}}{10^{-9}} = 200 \text{ k}\Omega$$

Thus  $R_3 = 200 \text{ k}\Omega$

From eq. 11.75

$$m = 4Q^2 = 4$$

$$\text{Thus, } R_4 = \frac{R}{M} = \frac{200}{4} = 50 \text{ k}\Omega$$

**Ex: 11.26**

The transfer function of the feedback network is given in Fig. 11.28a. The poles are the roots of the denominator polynomial,

$$s^2 + s \left( \frac{1}{C_1 R_3} + \frac{1}{C_2 R_3} + \frac{1}{C_1 R_4} \right) + \frac{1}{C_1 C_2 R_3 R_4} = 0$$

For  $C_1 = C_2 = 10^{-9} \text{ F}$ ,  $R_3 = 2 \times 10^5 \text{ }\Omega$ ,

$$R_4 = 5 \times 10^4 \text{ }\Omega$$


$$s^2 + s \left( \frac{2}{10^{-9} \times 2 \times 10^5} + \frac{1}{10^{-9} \times 5 \times 10^4} \right) + \frac{1}{10^{-18} 10^{10}} = 0$$

$$s^2 + s(3 \times 10^4) + 10^8 = 0$$

$$s = \frac{-3 \times 10^4 \pm \sqrt{9 \times 10^8 - 4 \times 10^8}}{2}$$

$$= -0.382 \times 10^4 \text{ and } -2.618 \times 10^4 \frac{\text{rad}}{\text{s}}$$

**Ex: 11.27**

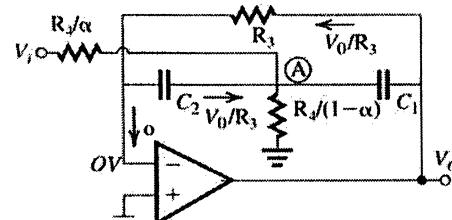

$$V_A = O - \frac{V_o}{SC_2 R_3}$$

$\Sigma I$  at (A)

$$\begin{aligned} \frac{V_o}{R_3} + SC_1(V_o - V_A) + \frac{-V_A}{R_4/(1-\alpha)} \\ + \frac{V_i - V_A}{R_3/\alpha} = 0 \end{aligned}$$

$$\begin{aligned} \frac{V_o}{R_3} + SC_1 V_o + \frac{SC_1 V_o}{SC_2 R_3} + \frac{(1-\alpha)V_o}{SC_2 R_3 R_4} + \frac{\alpha V_i}{R_4} \\ + \frac{\alpha V_o}{SC_2 R_3 R_4} = 0 \end{aligned}$$

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{-\alpha/R_4}{SC_1 + 1/R_3 + \frac{C_1}{C_2 R_3} + \frac{1}{SC_2 R_3 R_4}} \\ &= \frac{-S\alpha/(C_1 R_4)}{S^2 + S \left( \frac{1}{C_1 R_3} + \frac{1}{C_2 R_3} \right) + \frac{1}{C_1 C_2 R_3 R_4}} \end{aligned}$$

This is a bandpass function whose poles are identical to the zeros of  $t(s)$  in Fig. 11.28a).

For  $C_1 = C_2 = 10^{-9} \text{ F}$ ,  $R_1 = 2 \times 10^5 \text{ }\Omega$  &  $R_4 = 5 \times 10^4 \text{ }\Omega$


$$\frac{V_o}{V_i} = \frac{-S \times 2 \times 10^4 \times \alpha}{S^2 + S \times 10^4 + 10^8}$$

For unity centre-frequency gain

$$2 \times 10^4 \times \alpha = 10^4 \Rightarrow \alpha = 0.5$$

$$\text{Thus } \frac{R_4}{\alpha} = 100 \text{ k}\Omega; \frac{R_4}{1-\alpha} = 100 \text{ k}\Omega$$

**Ex: 11.28**

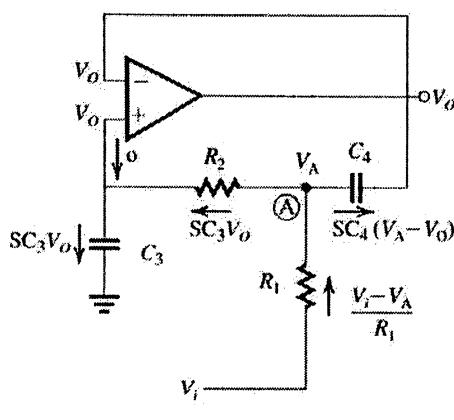

$$V_A = V_o + SC_3 V_o R_2 \\ = V_o (1 + SC_3 R_2)$$

$\Sigma I$  at (A)

$$SC_3 V_o = \frac{V_i}{R_1} + \frac{V_o}{R_1} + \frac{V_o}{R_1} SC_3 R_2 + V_o SC_4 (SC_3 R_2)$$

$$\frac{V_i}{R_1} = V_o \left[ S^2 C_3 C_4 R_2 + \frac{SC_3 R_2}{R_1} + SC_3 + \frac{1}{R_1} \right]$$

$$\frac{V_o}{V_i} = \frac{1/C_3 C_4 R_1 R_2}{S^2 + S \frac{1}{C_4 R_2} \left( 1 + \frac{R_2}{R_1} \right) + \frac{1}{C_3 C_4 R_1 R_2}}$$

$$\omega_o = \frac{1}{\sqrt{C_3 C_4 R_1 R_2}} \text{ as in Eq. (16.77)}$$

$$Q = \frac{1}{\sqrt{C_3 C_4 R_1 R_2}} \frac{C_4}{\left( \frac{1}{R_1} + \frac{1}{R_2} \right)} \text{ as in Eq. 11.78}$$

D.C. gain = 1 Q.E.D.

**Ex: 11.29**

From Fig 11.34(c)

$$R_1 = R_2 = R = 10 \text{ k}\Omega$$

$$CR = 2Q/\omega_o$$

$$C = \frac{2Q}{\omega_o R} = \frac{2/\sqrt{2}}{2\pi(4 \times 10^3)10^4} = 5.63 \text{ nF}$$

$$m = 4Q^2 = 4\left(\frac{1}{2}\right) = 2$$

$$C_i = 2.81 \text{ nF}$$

**Ex: 11.30**

Refer to the results in Example 11.2

(a)  $\Delta R/R_i = +2\%$

$$S_{R3}^{w_o} = -1/2 \Rightarrow \frac{\Delta \omega_o}{\omega_o} = -\frac{1}{2} \times 2 = -1\%$$

$$S_{R3}^Q = -\frac{1}{2} \Rightarrow \Delta Q/Q = \frac{1}{2} \times 2 = 1\%$$

(b)  $\Delta R_i/R_i = 2\%$

$$S_{R_i}^{w_o} = -\frac{1}{2} \Rightarrow \frac{\Delta \omega_o}{\omega_o} = -1\%$$

$$S_{R_i}^Q = -\frac{1}{2} \Rightarrow \frac{\Delta Q}{Q} = -\frac{1}{2} \times 2 = -1\%$$

(c) Combining the results in (a) & (b)

$$\frac{\Delta \omega_o}{\omega_o} = -1 - 1 = -2\%$$

$$\frac{\Delta Q}{Q} = 1 - 1 = 0\%$$

(d) using the results in (c) for both resistors being 2% high we have:

$$\frac{\Delta \omega_o}{\omega_o} = S_{C1}^{w_o} \frac{\Delta C_1}{C_1} + S_{C2}^{w_o} \frac{\Delta C_2}{C_2} - 2$$

$$= -\frac{1}{2}(-2) + \frac{-1}{2}(-2) - 2$$

$$= 2 - 2 = 0\%$$

$$\frac{\Delta Q}{Q} = S_{C1}^Q \frac{\Delta C_1}{C_1} + S_{C2}^Q \frac{\Delta C_2}{C_2} + 0$$

$$= 0(-2) + (0)(-2) + 0 = 0\%$$

**Ex: 11.31**

From Eq 11.96 & 11.97

$$C_3 = C_4 = \omega_o T_C C$$

$$= 2\pi 10^4 \times \frac{1}{200 \times 10^3} \times 20$$

$$= 6.283 \text{ pF}$$

From Eq. 11.99

$$C_5 = \frac{C_4}{Q} = \frac{6.283}{20} = 0.314 \text{ pF}$$

From Eq 11.100

$$\text{Centre-frequency gain} = \frac{C_6}{C_5} = 1$$

$$C_6 = C_5 = 0.314 \text{ pF}$$

**Ex: 11.32**

$$R_p = \omega_o L Q_o = 2\pi 10^6 \times 3.2 \times 10^{-6} \times 150 = 3 \text{ k}\Omega$$

$$R = R_L \parallel r_o \parallel R_p = 2 \text{ k}\Omega \Rightarrow R_L = 15 \text{ k}\Omega$$

**Ex: 11.33**

$$Q = (R_1 \parallel R_{in}) / \omega_o L$$

$$= \frac{10^3 \parallel 10^3}{(2\pi \times 455 \times 10^3) \times 5 \times 10^{-6}} = 35$$

$$BW = f_o/Q = 455/35 = 13 \text{ KHz}$$

$$C_1 + C_{in} = \frac{1}{\omega_o^2 L}$$

$$= \frac{1}{(2\pi \times 455 \times 10^3)^2 \times 5 \times 10^{-6}}$$

$$= 24.47 \text{ nF}$$

$$C_1 = 24.47 - 0.2 = 24.27 \text{ nF}$$

**Ex: 11 . 34**

To just meet specifications

$$Q = \frac{f_o}{BW} = \frac{455}{10} = 45.5$$

$$\therefore \frac{R_1 \parallel n^2 R_{in}}{\omega_o L} = 45.5$$

$$R_1 \parallel n^2 R_{in} = 45.5 \times 455 \times 10^3 \times 5 \times 10^{-6}$$

$$= 650 \Omega$$

$$n^2 R_{in} = 1.86 \text{ k}\Omega$$

$$n = \sqrt{\frac{1.86}{1}} = 1.36$$

$$C_1 + \frac{C_{in}}{n^2} = \frac{1}{\omega_o^2 L} = 24.47$$

$$C_1 = 24.36 \text{ nF}$$

At resonance, the voltage developed across  $R_1$  is

$$I(R_1 \parallel n^2 R_{in})$$

, Thus,  $V_{Dc} = IR/n$  &

$$I_C = g_m V_{Dc} = g_m IR/n, \text{ here}$$

$$\frac{I_C}{I} = g_m R/n = \frac{40 \times 0.65}{1.36} = 19.1 \text{ A}$$

**Ex: 11 . 35**

$$200 = f_o Q \sqrt{2^{1/2} - 1} \quad \text{Eq (16.110)}$$

$$\frac{f_o}{Q} = 310.8 \text{ kHz}$$

$$C = \frac{1}{\omega_o^2 L} = \frac{1}{(2\pi \times 10.7 \times 10^6)^2 \times 3 \times 10^{-6}}$$

$$= 73.7 \text{ pF}$$

$$\frac{\omega_o}{Q} = \frac{1}{C_R}$$

$$R = \frac{1}{73.7 \times 10^{-12} \times 2\pi \times 310.8 \times 10^3}$$

$$= 6.95 \text{ k}\Omega$$

**Ex: 11 . 36**

$$f_{o1} = f_o + \frac{2\pi B}{2\sqrt{2}} \quad \text{Eq(16.115)}$$

$$= 10.7 \text{ MHz} + \frac{200}{2\sqrt{2}} \text{ kHz} = 10.77 \text{ MHz}$$

$$B_1 = B/\sqrt{2} = 200/\sqrt{2} = 141.4 \text{ kHz}$$

$$f_{o2} = f_o - \frac{2\pi B}{2\sqrt{2}} \quad \text{Eq(16.116)}$$

$$= 10.7 \text{ MHz} - 200/2\sqrt{2} = 10.63 \text{ MHz}$$

$$B_2 = \frac{200}{\sqrt{2}} = 141.4 \text{ kHz}$$

For stage 1

$$C = \frac{1}{\omega_{o1}^2 L} = \frac{1}{(2\pi 10.77 \times 10^6)^2 \times 3 \times 10^{-6}}$$

$$= 72.8 \text{ pF}$$

$$R = \frac{1}{CB_1} = \frac{1}{72.8 \times 10^{-12} \times 141.4 \times 2\pi 10^3}$$

$$= 15.5 \text{ k}\Omega$$

For stage 2

$$C = \frac{1}{\omega_{o2}^2 L} = \frac{1}{(2\pi 10.63 \times 10^6)^2 \times 3 \times 10^{-6}}$$

$$= 74.7 \text{ pF}$$

$$R = \frac{1}{CB_2} = \frac{1}{74.7 \times 10^{-12} \times 141.4 \times 2\pi 10^3}$$

$$= 15.1 \text{ k}\Omega$$

**Ex: 11 . 37**

Gain of stagger-tuned amplifier at  $f_O$  is proportional to

$$\frac{1}{\sqrt{2}} R_{stage1} \times \frac{1}{\sqrt{2}} R_{stage2}$$

$$= \frac{1}{2} \times 15.5 \times 15.1 = 117$$

Gain of synchronous-tuned amplifier at to

$$\propto R_{stage1} \times R_{stage2}$$

$$= 6.95 \times 6.95$$

$$= 48.3$$

$$\therefore \text{Ratio} = \frac{117}{48.3} = 2.42$$

**Ex: 12 . 1**

Pole frequency  $f_p = 1 \text{ kHz}$

$$\begin{aligned} \text{Centre frequency gain} &= \frac{1}{\text{AMPLIFIER GAIN}} \\ &= \frac{1}{2} \text{ V/V} \end{aligned}$$

**Ex: 12 . 2**

$$L_+ = V \frac{R_1/R_3}{R_1 + R_3} + V_D \left(1 + \frac{R_4}{R_5}\right)$$

$$= 15 \left(\frac{3}{9}\right) + 0.7 \left(1 + \frac{3}{9}\right)$$

$$= 5 + 0.93 = +5.93 \text{ V}$$

$$L_- = -V \frac{R_3}{R_2} - V_D \left(1 + \frac{R_3}{R_2}\right)$$

$$= -15 \times \frac{3}{9} - 0.7 \left(1 + \frac{3}{9}\right)$$

$$= -5.93 \text{ V/V}$$

$$\text{Limiter gain} = \frac{-R_f}{R_1} = \frac{-60}{30} = -2 \text{ V/V}$$

Thus limiting occurs at  $\frac{\pm 5.93}{2}$

$$= \pm 2.97 \text{ V}$$

Slope in the limiting regions

$$= \frac{-R_f \parallel R_1}{R_1} = -\frac{60 \parallel 3}{30} = -0.095 \text{ V/V}$$

**Ex: 12 . 3**

$$(a) L(s) = \left(1 + \frac{R_2}{R_1}\right) \frac{Z_p}{Z_p + Z_s}$$

$$= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{1}{1 + Z_s Y_p}\right)$$

$$= \left(1 + \frac{20.3}{10}\right) \left(\frac{1}{1 + \left(R + \frac{1}{SC}\right) \left(\frac{1}{R} + SC\right)}\right)$$

$$= \frac{3.03}{3 + SCR + \frac{1}{SCR}}$$

where  $R = 10 \text{ k}\Omega$  and  $C = 16 \text{ nF}$

Thus

$$L(s) = \frac{3.03}{3 + S16 \times 10^{-5} + \frac{1}{S \times 16 \times 10^{-5}}}$$

The closed loop poles are found by setting  $L(s) = 1$ , that is, they are the values of  $s$ , satisfying

$$3 + S \times 16 \times 10^{-5} + \frac{1}{S \times 16 \times 10^{-5}} = 3.03$$

$$\Rightarrow S = \frac{10^5}{16}(0.015 \pm j)$$

(b) The frequency of oscillation is  $(10^5/16) \text{ rad/s}$  or  $1 \text{ kHz}$

(c) Refer to fig. 12.5 At the positive peak  $\hat{V}_o$ , the voltage at node  $b$  will be one diode drop ( $0.7 \text{ V}$ ) above the voltage  $V_b$  which is about  $1/3$  of  $V_o$ ; thus  $V_b = 0.7 + \hat{v}_o/3$ . Now if we neglect the current through  $D_2$  in comparison with the currents through  $R_4$  and  $R_5$  we find that

$$\frac{\hat{V}_o - V_b}{R_5} = \frac{V_b - (-15)}{R_6}$$

Thus,

$$\frac{\hat{V}_o - V_b}{1} = \frac{V_b + 15}{3}$$

$$\hat{V}_o = \frac{4}{3}V_b + 5$$

$$\hat{V}_o = \frac{4}{3}(0.7 + \frac{\hat{V}_o}{3}) + 5$$

$$\Rightarrow \hat{V}_o = 10.68 \text{ V}$$

from symmetry, we see that the negative peak is equal to the positive peak. Thus the output peak-to-peak voltage is  $21.36 \text{ V}$

**Ex: 12 . 4**

a) for oscillations to start,  $R_1/R_i = 2$  thus the potentiometer should be set so that its resistance to ground is  $20 \text{ k}\Omega$

$$(b) f_o = \frac{1}{2\pi RC} = \frac{1}{2\pi 10 \times 10^3 \times 16 \times 10^{-9}} = 1 \text{ kHz}$$

**Ex: 12 . 5**

Working from the output back to the input and continuing the equations we get I

$$I = \frac{V_o}{R_f} + \frac{V_o}{SCR_f R} + \frac{V_o}{SCR_f R} + \frac{1}{SCR}$$


$$\left(\frac{V_o}{R_f} + \frac{V_o}{SCR_f R}\right)$$

$$V_x = \frac{-V_o}{SCR_f} - \frac{1}{SC} \left(\frac{V_o}{R_f} + \frac{V_o}{SCR_f R}\right) - \frac{I}{SC}$$

$$V_x = \frac{-V_o}{SCR_f} \left(2 + \frac{1}{SCR}\right)$$

$$= \frac{-V_o}{SCR_f} \left[1 + \frac{1}{SCR} + \frac{1}{SCR} + \frac{1}{SCR} \left(1 + \frac{1}{SCR}\right)\right]$$
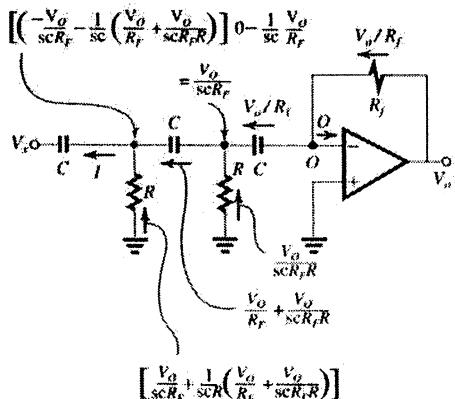
$$= \frac{-V_o}{SCR_f} \left(3 + \frac{4}{SCR} + \frac{1}{S^2 C^2 R^2}\right)$$



Thus:

$$\frac{V_o}{V_x} = \frac{-SCR_f}{3 + \frac{4}{SCR} + \frac{1}{S^2 C^2 R^2}}$$

$$\frac{V_o(j\omega)}{V_x} = \frac{-j\omega CR_f}{4 + j\left(3\omega CR - \frac{1}{\omega CR}\right)}$$

Ex: 12.6

The circuit will oscillate at the value of  $\omega$  that makes  $\frac{V_o(j\omega)}{V_x}$  a real number.

It follows that  $\omega_0$  is obtained from

$$3\omega_0 CR = \frac{1}{\omega_0 CR} \Rightarrow \omega_0 = \frac{1}{\sqrt{3}CR}$$

$$\text{Thus, } f_0 = \frac{1}{2\pi\sqrt{3} \times 16 \times 10^{-9} \times 10 \times 10^3} \\ = 574.3 \text{ Hz}$$

For oscillations to begin, the magnitude of

$\frac{V_o(j\omega)}{V_x}$  should equal to (or greater than) unity, that is

$$\frac{\omega_0^2 C^2 RR_f}{4} \geq 1$$

Thus the minimum value of  $R_f$  is

$$R_f = \frac{4}{\omega_0^2 C^2 R} = \frac{4 R}{\omega_0^2 C^2 R^2} = \frac{4 R}{\frac{1}{3}} \\ = 12 \text{ R or } 120 \text{ k}\Omega$$

Ex: 12.7


$$\omega_0 = \frac{1}{CR} \Rightarrow CR = \frac{1}{2\pi 10^3}$$

For  $C \approx 16 \text{ nF}$   $R = 10 \text{ k}\Omega$

∴ the output is twice as large as the voltage across the resonator, the peak-to-peak amplitude is

$$\frac{4 \text{ V}}{\pi} = \frac{4(2 \times 1.4)}{\pi} = 3.6 \text{ V}$$

Ex: 12.8

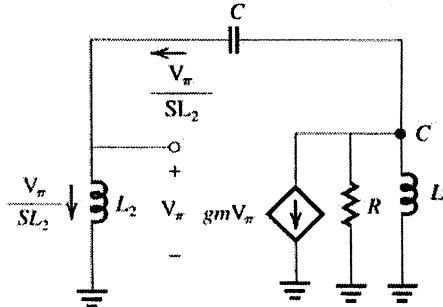

Node equation at collector:

$$\frac{V_\pi}{SL_2} + g_m V_\pi + \frac{V_c}{R} + \frac{V_c}{SL_1} = 0$$

$$\frac{V_\pi}{SL_2} + g_m V_\pi + \frac{V_\pi}{R} \left( 1 + \frac{1}{S^2 CL_2} \right)$$

$$+ \frac{V_\pi}{S_4} \left( 1 + \frac{1}{S^2 CL_2} \right) = 0$$

Since  $V_\pi \neq D$ , (oscillations have started) it can be eliminated resulting in

$$S^3 L_1 L_2 C \left( g_m + \frac{1}{R} \right) + S^2 (L_1 C + L_2 C)$$

$$+ S \frac{L_1}{R} + 1 = 0$$

Substituting  $S = j\omega$

$$[1 - \omega^2 C(L_1 + L_2)] + j\omega$$

$$\left[ \frac{L_1}{R} - \left( g_m + \frac{1}{R} \right) \times \omega^2 L_1 L_2 C \right] = 0$$

$$R_E = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{C(L_1 + L_2)}} \text{ Q.E.D.}$$

$$I_m = 0 \Rightarrow g_m R + 1 = \frac{1}{\omega_0^2 L_2 C}$$

$$= \frac{L_1 + L_2}{L_2}$$

$$\Rightarrow g_m R = L_1 / L_2$$

for oscillations to start

$g_m R > L_1 / L_2$  Q.E.D.

Ex: 12.9

$$R = \frac{Q}{\omega_0} \parallel R_L \parallel \Gamma_o$$

$$= \frac{100}{10^6 \times 10^{-8}} \parallel 2 \times 10^3 \parallel 100 \times 10^3 \\ = 10 \parallel 2 \parallel 100 = 1.64 \text{ k}\Omega$$

$$\frac{C_2}{C_1} = g_m R = 40 \times 1.64 = 65.6$$

$$C_2 = 65.6 \times 0.01 = 0.66 \mu\text{F}$$

$$\begin{aligned} L &= \frac{1}{\omega_0^2 C_1 C_2} \\ &= \frac{1}{10^{12} \times \frac{0.01 \times 0.66 \times 10^{-6}}{0.01 + 0.66}} \approx 100 \mu\text{A} \end{aligned}$$

Ex: 12.10

from Eq (12.24)

$$\begin{aligned} f_s &= \frac{1}{2\pi\sqrt{LC_s}} = \frac{1}{2\pi\sqrt{0.52 \times 0.012 \times 10^{-12}}} \\ &= 2.015 \text{ MHz} \end{aligned}$$

from Eq (12.25)

$$\begin{aligned} f_p &= \frac{1}{2\pi\sqrt{\frac{C_s C_p}{C_D + C_p}}} \\ &= \frac{1}{2\pi\sqrt{0.52 \times \frac{0.012 \times 4 \times 10^{-12}}{0.012 + 4}}} \\ &= 2.018 \text{ MHz} \end{aligned}$$

$$Q = \frac{\omega_o L}{r} \approx \frac{\omega_s L}{r}$$

$$\approx \frac{2\pi \times 2.015 \times 10^6 \times 0.52}{120}$$

$$\approx 55,000$$

Ex: 12.11

$$V_{TH} = V_{TL} = \beta |L \pm |$$

$$5 = \frac{R_1}{R_1 + R_2} \times 13$$

$$\frac{R_2}{R_1} = 1.6$$

$$R_2 = 16 \text{ k}\Omega$$

Ex: 12.12


$$V_{TH} - V_{TL} = \frac{R_1}{R_2} |L|$$

$$5 = \frac{R_1}{R_2} \times 10$$


$$R_2 = 2R_1$$

Possible choice  $R_1 = 10 \text{ k}\Omega$   $R_2 = 20 \text{ k}\Omega$

Ex: 12.13

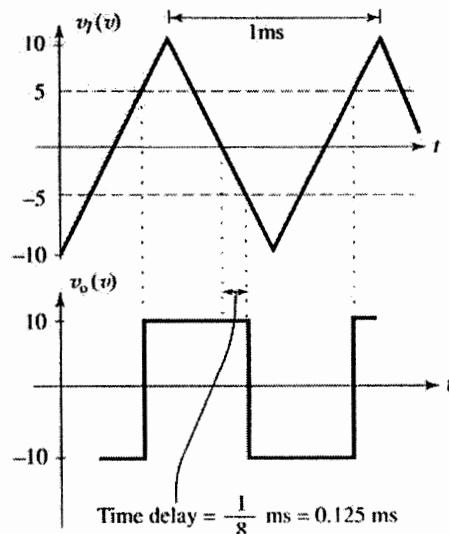

Ex: 12.14

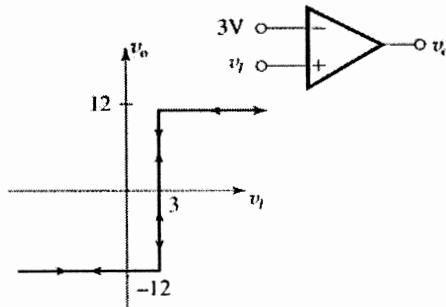

A comparator with a threshold of 3 V and output levels of  $\pm 12 \text{ V}$

Ex: 12.15

$$|V_T| = \frac{100}{2} = 50 \text{ mV}$$

$$50 \times 10^{-3} = 10 \frac{R_1}{R_2}$$

$$\frac{R_2}{R_1} = \frac{10}{0.06}$$

$$R_2 = 200 R_1$$

for  $R_1 = 1 \text{ k}\Omega$   $R_2 = 200 \text{ k}\Omega$

Ex: 12.16

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{100}{100 + 1000} = 0.091 \frac{\text{V}}{\text{V}}$$


$$T = 2\pi \ln \frac{1 + \beta}{1 - \beta}$$

$$2 \times 0.01 \times 10^{-6} \times 10^6 \times \ln \left( \frac{1.091}{1 - 0.091} \right)$$




$$= 0.00365 \text{ s}$$

$$f_o = \frac{1}{T} = 274 \text{ Hz}$$

Ex: 12.17

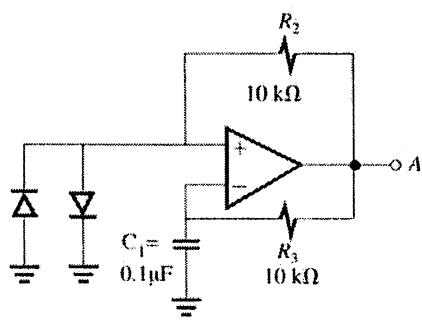

$$T_1 = T_2 = T/2$$

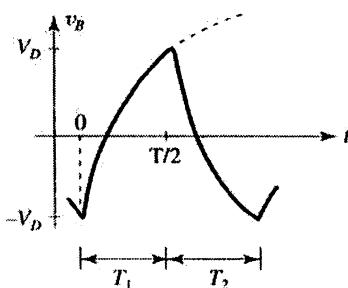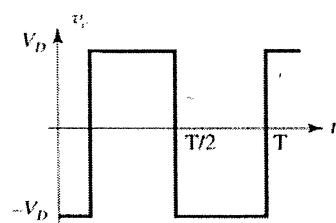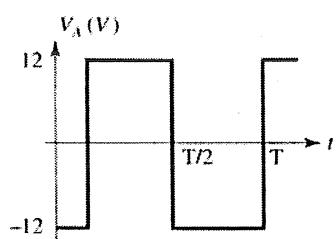

During  $T_1$ ,

$$V_B(t) = 12 - (12 + V_D)e^{-t/T_1}$$

$$V_B = V_D \text{ at } t = T/2$$

$$V_D = 12 - (12 + V_D)e^{-T/2T_1}$$

$$T = 2\pi \ln \left( \frac{12 + V_D}{12 - V_D} \right)$$

$$= 2 \times 0.1 \times 10^{-6} \times 10 \times 10^3 \times \ln \left( \frac{12 + V_D}{12 - V_D} \right)$$

$$f = \frac{1}{T} = \frac{500}{\ln \left( \frac{12 + V_D}{12 - V_D} \right)}$$

$$f|_{25^\circ\text{C}} = \frac{500}{\ln \left( \frac{12.7}{11.3} \right)}$$

$$= 4281 \text{ Hz}$$

$$\text{At } 0^\circ\text{C}, V_D = 0.7 + .05 = 0.75 \text{ V}$$

$$f|_{0^\circ\text{C}} = \frac{500}{\ln \left( \frac{12.75}{11.25} \right)} = 3,995 \text{ Hz}$$

$$\text{At } 50^\circ\text{C}, V_D = 0.7 - 0.05 = 0.65 \text{ V}$$

$$f|_{50^\circ\text{C}} = \frac{500}{\ln \left( \frac{12.65}{11.35} \right)} = 4,611 \text{ Hz}$$

$$\text{At } 100^\circ\text{C}, V_D = 0.7 - 0.15 = 0.55 \text{ V}$$

$$f|_{100^\circ\text{C}} = \frac{500}{\ln \left( \frac{12.55}{11.45} \right)} = 5,451 \text{ Hz.}$$

Ex: 12.18

To obtain a triangular waveform with 10-V peak-to-peak amplitude we should have

$$V_{TH} = -V_{TL} = 5 \text{ V}$$

$$\text{But } V_{TL} = -L + \frac{R_1}{R_2}$$

$$\text{Thus } -5 = -10 \times \frac{10}{R_2}$$

$$R_2 = 20 \text{ k}\Omega$$

For 1 kHz frequency,  $T = 1\text{ms}$

Thus,

$$T/2 = 0.5 \times 10^{-3} = CR \frac{V_{TH}-V_{IN}}{4}$$

$$= 0.01 \times 10^{-6} \times R \times 10/10$$

$$R = 50 \text{k}\Omega$$

**Ex: 12.19**

Using Eq (12.37)

$$100 \times 10^{-6} = 0.1 \times 10^{-6} \times R_3 \ln\left(\frac{12.7}{10.8}\right)$$

$$R_3 = 6171 \text{\Omega}$$

**Ex: 12.20**

$$T = 1.1CR \Rightarrow R = T/1.1C = 9.1 \text{k}\Omega$$

**Ex: 12.21**

$$T = 0.69C(R_A + 2R_B)$$

$$\frac{1}{100 \times 10^{-3}} = 0.69 \times 10^3 \times 10^{-12}(R_A + 2R_B)$$

$$\Rightarrow R_A + 2R_B = \frac{1}{0.69 \times 10^{-4}} = 14.49 \text{k}\Omega \quad (1)$$

Using Eq (13.45)

$$0.75 = \frac{A + R_B}{R_A + 2R_B}$$

$$R_A + R_B = 0.75 \times 14.44 = 10.88 \text{k}\Omega \quad (2)$$


$$(1) - (2) \Rightarrow R_B = 3.61 \text{k}\Omega$$

Now, substituting into (2)

$$R_A = 7.27 \text{k}\Omega$$

Use 7.2 k\Omega and 3.6 k\Omega, standard 5% resistors.

**Ex: 12.22**

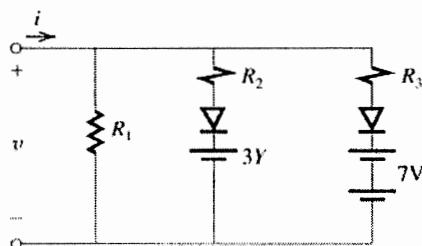

$$i = 0.1v^2$$

$$\text{At } v = 2 \text{ V}, i = 0.4 \text{ mA}$$

$$\text{Thus } R_1 = \frac{2}{0.4} = 5 \text{k}\Omega$$

For  $3V \leq V \leq 7V$

$$i = \frac{v}{R_1} + \frac{v-3}{R_2}$$

To obtain a perfect match at  $V = 4 \text{ V}$  (i.e. to obtain  $i = 1.6 \text{ mA}$ )

$$1.6 = \frac{4}{5} + \frac{4-3}{R_2}$$

$$R_2 = 1.25 \text{k}\Omega$$

for  $v \geq 7 \text{ V}$

$$i = \frac{v}{R_1} + \frac{v-3}{R_2} + \frac{v-7}{R_3}$$

To obtain a perfect match at  $v = 8 \text{ V}$  we must have to select  $R_3$  so that  $i = 6.4 \text{ mA}$ ,

$$6.4 = \frac{8}{5} + \frac{8-3}{1.25} + \frac{8-7}{R_3}$$

$$\Rightarrow R_3 = 1.25 \text{k}\Omega$$

At  $v = 3 \text{ V}$ , the circuit provides

$$i = \frac{3}{5} = 0.6 \text{ mA} \text{ while ideally}$$

$$i = 0.1 \times 9 = 0.9 \text{ mA} \text{ Thus the error is} \\ -0.3 \text{ mA.}$$

\* At  $V = 5 \text{ V}$ , the circuit provides

$$i = \frac{5}{5} + \frac{5-3}{1.25} = 2.6 \text{ mA, while ideally}$$

$$i = 0.1 \times 25 = 2.5 \text{ mA. Thus the error is} \\ +0.1 \text{ mA.}$$

\* At  $v = 7 \text{ V}$ , the circuit provides


$$i = \frac{7}{5} + \frac{7-3}{1.25} = 4.6 \text{ mA, while ideally. Thus}$$

the error is  $-0.3 \text{ mA}$


\* At  $v = 10 \text{ V}$ , the circuit provides,

$$i = \frac{10}{6} + \frac{10-3}{1.25} + \frac{10-7}{1.25} = 10 \text{ mA, while}$$

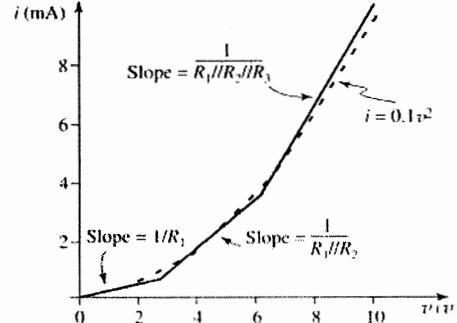ideally  $i = 10 \text{ mA}$ . Thus the error is 0 A.



Ex: 12.23

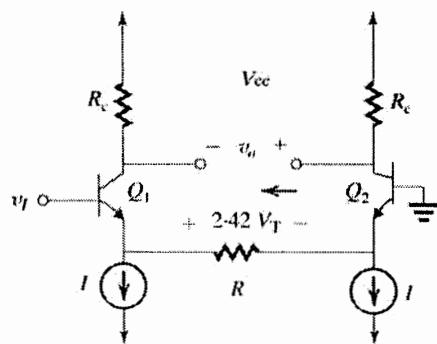


$$\begin{aligned} I_{e1} &= I + (2.42 V_T) / R \\ &= I \left[ 1 + \frac{2.42 V_T}{I_R} \right] \\ &= I \left[ 1 + \frac{2.42 V_T}{2.5 V_T} \right] \\ &= I \left( 1 + \frac{2.42}{2.5} \right) \end{aligned}$$

$$I_{e2} \cong I \left( 1 + \frac{2.42}{2.5} \right)$$

$$I_{e2} \cong I \left( 1 - \frac{2.42}{2.5} \right)$$

$$\begin{aligned} v_O &= (V_{cc} - I_{e2} R_e) - (V_{cc} - I_{e1} R_c) \\ &= (I_{e1} - I_{e2}) R_c \\ &= IR_c \times 2 \times \frac{2.42}{2.5} \\ &\cong 0.25 \times 10 \times 2 \times \frac{2.42}{2.5} \cong 4.84 \text{ V} \end{aligned}$$

Ex: 12.24

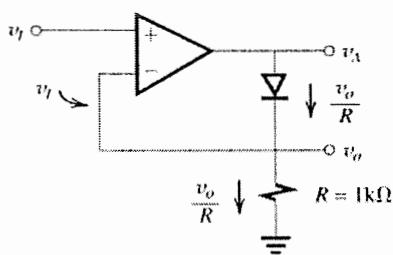

∴ The opamp is ideal  $v_o = v_i$  for  $v > 0$ .

$$v_i = 10 \text{ mV} \quad v_o = 10 \text{ mV}$$

$$i_D = \frac{10 \text{ mV}}{R} = 10 \mu\text{A}$$

Given  $\Rightarrow i_D = 1 \text{ mA} \quad 0.1 \text{ mA} \quad 10 \mu\text{A}$

$$v_D = 0.7 \text{ V} \quad 0.6 \text{ V} \quad 0.5 \text{ V}$$

Thus,  $v_D = 0.5 \text{ V}$  so


$$v_A = v_o + v_D = 0.51 \text{ V}$$

$$v_I = 1 \text{ V} \Rightarrow v_o = 1 \text{ V}$$


$$i_D = 1 \text{ mA}, v_D = 0.7 \text{ V}, v_A = 1.7 \text{ V}$$

$v_I = -1 \text{ V}$  ~ The negative feedback loop is not operative.
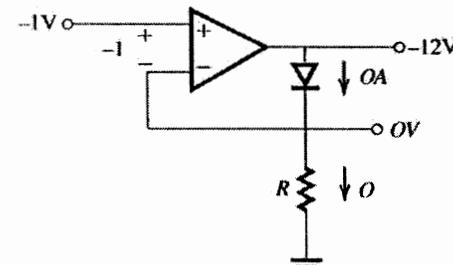
$$v_o = 0 \text{ V}, v_A = -12 \text{ V}$$



Ex: 12.25

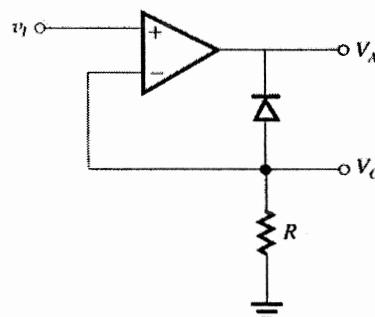

For the diode to conduct and close the negative feedback loop,  $v_o$  must be negative, in which case, the negative feedback causes a virtual short circuit to appear between the input terminals of the op amp and thus  $v_o = v_I$ . For positive  $v_I$ , the op amp saturates in the positive saturation level. The diode will be cut off and  $v_D = 0$ .

In summary

$$v_o = 0 \text{ for } v_I \geq 0$$

$$v_o = v_I \text{ for } v_I \leq 0$$

Ex: 12.26

Refer to Fig 12.34

For  $v_I = +1 \text{ V}$ :

$D_2$  will conduct and close the negative feedback loop around the op amp.  $v_- = 0$ , the current through  $R_1$  and  $D_2$  will be 1 mA. Thus the voltage at the op amp output,  $v_A = -0.7 \text{ V}$  which will set

$D_1$  off and no current will flow through  $R_2$ . Thus

$$v_D = 0 \text{ V}$$

For  $v_I = -10 \text{ mV}$

$D_1$  will conduct through  $R_1$  &  $R_2$  to  $v_O$ . The negative feedback loop of the op amp will thus be closed and a virtual ground will appear at the inverting input terminal.  $D_2$  will be cutoff. The current through  $R_1$ ,  $R_2$  and  $D_1$  will be

$$\frac{10 \text{ mV}}{1 \text{ k}\Omega} = 10 \mu\text{A} \text{. Thus the diode, } D_1 \text{, voltage}$$

will be 0.5 V.

$$v_o = 0 + 10 \mu\text{A} \times 10 \text{ k}\Omega = +0.1 \text{ V}$$

$$v_A = v_{D1} + v_o = 0.5 + 0.1 = 0.6 \text{ V}$$

For  $v_I = -1 \text{ V}$

This is similar to the case when  $v_I = -10 \text{ mV}$ .

The current through  $R_1$ ,  $R_2$ ,  $D_1$  will be


$$I = \frac{1}{1 \text{ k}\Omega} = 1 \text{ mA}$$

$$\therefore v_{D1} = 0.7 \text{ V}$$

$$v_o = 0 + 1 \text{ mA} \times 10 \text{ k}\Omega = 10 \text{ V}$$


$$v_A = 10 + v_{D1} = 10.7 \text{ V}$$

Ex: 12.27

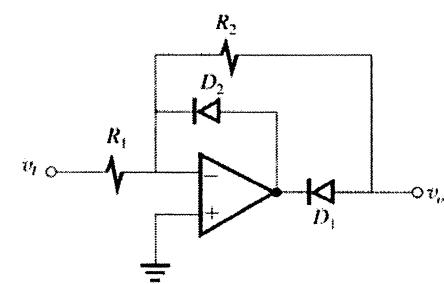

$$v_I > 0$$

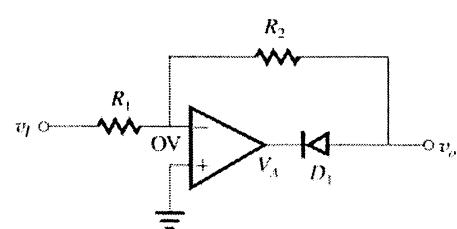Current flows from  $v_I$  through  $R_1$ ,  $R_2$ ,  $D_1$  into the output terminal of the opamp.  $v_o$  goes negative and is thus off. The following circuit results:



$$\frac{v_o}{v_I} = \frac{-R_2}{R_1}$$


$$v_I < 0 \sim D_2 \text{ on}$$

$\sim v_0$  goes the & forms  $D_1$  off


$\sim$  no current flows through

$$R_2 = v_0 = 0 \text{ V}$$

$$\sim V_A = 0.7 \text{ V}$$

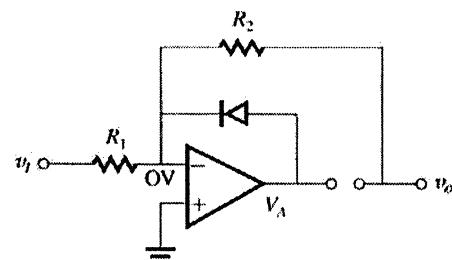


Ex: 12.28

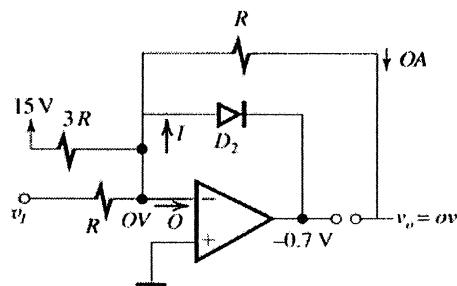

$vI > 0$  - Equivalent Circuit

$\sim D_2$  on,  $D_1$  off

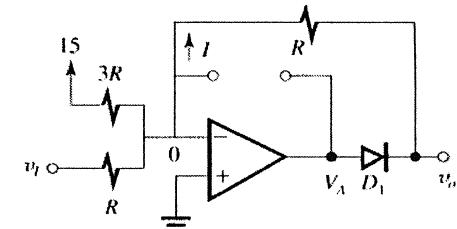


$$I = \frac{15}{3R} + \frac{v_I}{R}$$

As  $v_I$  goes negative, the above circuit holds so that  $v_0 = 0$ . This occurs as the 15 V supply sources the current I even for small negative  $v_I$ . This situation remains the case until  $I = 0$

$$\therefore \frac{15}{3R} + \frac{v_I}{R} = 0$$

$$v_I = -5 \text{ V}$$

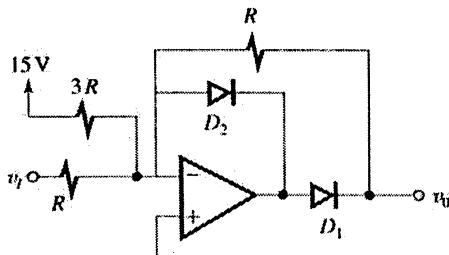$v_I < -5 \text{ V} \sim D_2$  off,  $D_1$  on




$$v_0 = 0 - IR$$

$$= 0 - \left( \frac{15}{3R} + \frac{v_i}{R} \right) R$$


$$= -v_i - 5$$

$$\text{note } v_A = v_o + 0.7 = -v_i - 4.3 > 0$$

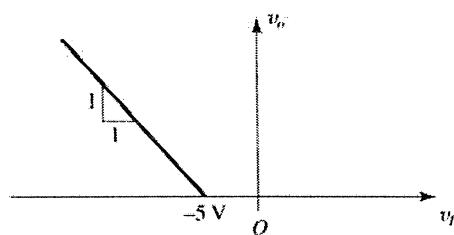$\therefore v_{D2} \approx 0 - V_A < 0 - D_2 \text{ off!}$



Ex: 12.29

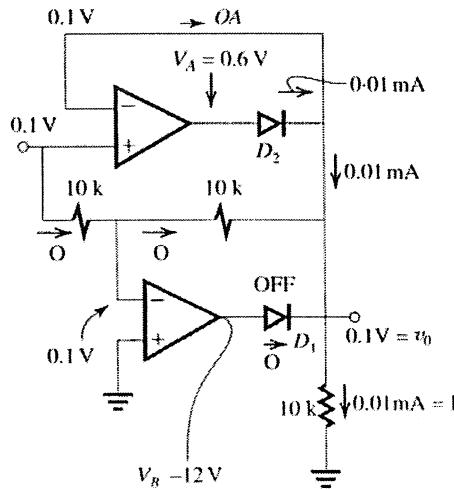

$$\text{a) } v_i = 0.1 \text{ V}$$

NB

for all circuits, currents are given in mA, resistance in kΩ & voltages in V.

b)  $v_i = 1 \text{ V}$  ~ similar to the circuit in (a) but with all of the ungrounded opamp input terminals at  $v_i = 1 \text{ V}$

$$v_0 = 1 \text{ V}$$

$$I = 1 / 10 \text{ k}\Omega = 0.1 \text{ mA}$$

$$v_A = 1 + U_{D2}$$

$$= 1 + 0.7 + 0.1 \log\left(\frac{0.1}{1}\right)$$

$$= 1.6 \text{ V}$$

(c)

$$v_i = 10 \text{ V} \sim \text{similar to (a) \& (b)}$$

~ all input terminals (not grounded) of opamps is equal to 10 V.

$$v_0 = 10 \text{ V}$$

$$I = \frac{10}{10} = 1 \text{ mA} \sim \text{diode voltages} = 0.7 \text{ V}$$


$$V_A = v_0 + U_{D2} = 10 + 0.7 = 10.7 \text{ V}$$

$$\text{d) } v_i = 0.1 \text{ V}$$

$$V_R = V_D + V_{D1}$$

$$= 0.1 + 0.7 + 0.1 \log\left(\frac{0.02}{1}\right)$$

$$= 0.63 \text{ V}$$

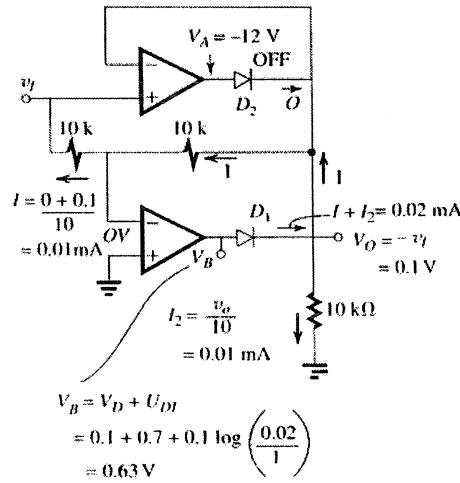

$$\text{e) } v_i = -1 \text{ V} \sim \text{use circuit in (d)}$$

$$I = 0.1 \text{ mA}$$

$$V_0 = -v_i = 1 \text{ V}$$

$$I_1 = 0.1 \text{ mA}$$

$$I_{in} = I + I_1 = 0.2 \text{ mA}$$

$$V_R = V_o + V_{D1}$$

$$= 1 + 0.7 + 0.1 \log\left(\frac{0.2}{1}\right)$$

$$= 1.63 \text{ V}$$

(f)  $v_f = -10$  V, use circuit (d)

$I = 0$  mA


$v_0 = -v_1 = 10$  V

$I_2 = 1.0$  mA

$I_m = 2$  mA

$$V_B = V_0 + V_{D1} = 10 + 0.7 + 0.1 \log\left(\frac{2}{1}\right) \\ = 10.73 \text{ V}$$

Ex: 12.30

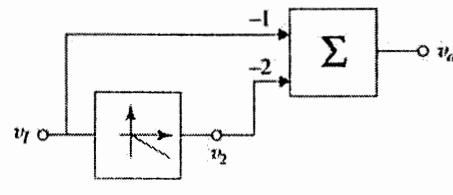

For  $v_I \geq 0$ , i.e.  $v_I = |v_I|$ ,

$v_2 = -|v_I|$  and

$$v_0 = -|v_I| - 2 \times -|v_I| = +|v_I|$$


For  $v_I \leq 0$ , i.e.  $v_I = -|v_I|$

$$v_2 = 0, v_0 = -|x - |v_I||$$

$$= +|v_I|$$

Thus, the block diagram implements the absolute value operation.

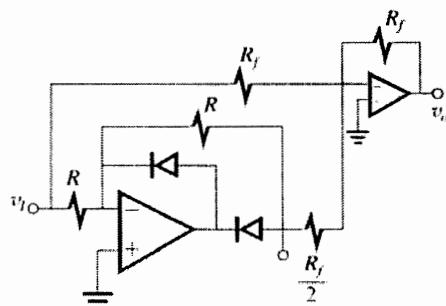Using the circuits of Fig 12.34 a), with the diodes reversed, to implement the half-wave rectifier, and a weighted summer results in the circuit shown below.



Use  $R = R_f = 10$  kΩ

Ex: 12.31

$v_A$  is a sinusoid of 5-V rms (peak voltage of

$5\sqrt{2}$ ) The average current through the meter will

be  $\frac{2}{\pi} \times \frac{5\sqrt{2}}{R}$ . To obtain full-scale leading. This

current must be equal to 1 mA. Thus  $\frac{2}{\pi} \times \frac{5\sqrt{2}}{R} = 1$  mA, which leads to  $R = 4.5$  kΩ

$V_c$  will be maximum when  $V_A$  is at its positive peak, i.e.  $v_A = 5\sqrt{2}$  V. At this value of  $V_A$ , we obtain

$$v_c = V_{D1} + V_M + V_{D3} + V_R \text{ where}$$

$$V_{D1} = V_{D3} \approx 0.7 \text{ V and}$$

$$V_M = \frac{5\sqrt{2}}{4.5} \times 0.05 = 0.08 \text{ V}$$

Thus

$$V_c|_{\max} = 0.7 + 0.8 + 0.7 + 5\sqrt{2} = 8.55 \text{ V}$$

Similarly we can calculate :

$$V_c|_{\min} = -8.55 \text{ V}$$

### Ex 13.1

For  $Q_1$

$$I = \frac{V_{CC} - V_{CEsat}}{R_L} = \frac{15 - 0.2}{1 \text{ k}\Omega}$$

$$I = 14.8 \text{ mA}$$

$$R = \frac{-V_D - (-V_{CC})}{14.8} = \frac{-0.7 - (-15)}{14.8} \\ = 0.97 \text{ k}\Omega$$

$$v_{omax} = V_{CC} - V_{CEsat} \\ = 15 - 0.2 \\ = 14.8 \text{ V}$$

$$v_{omin} = -V_{CC} + V_{CEsat} \\ = -15 + 0.2 \\ = -14.8$$

Output signal swing is from 14.8 V to -14.8 V  
Maximum emitter current =  $2I = 2 \times 14.8$   
 $= 29.6 \text{ mA}$

### Ex 13.2

At  $v_o = -10 \text{ V}$ , the load current is -10 mA and the emitter current of  $Q_1$  is  $14.8 - 10 = 4.8 \text{ mA}$ .

$$\text{Thus, } v_{BE1} = 0.6 + 0.025 \ln\left(\frac{14.8}{1}\right) \\ = 0.64 \text{ V}$$

$$\text{Thus, } v_I = -10 + 0.64 = -9.36 \text{ V}$$

At  $v_o = 0 \text{ V}$ ,  $i_L = 0$  and  $i_{E1} = 14.8 \text{ mA}$

$$\text{Thus, } v_{BE1} = 0.6 + 0.025 \ln\frac{4.8}{1} \\ = 0.67 \text{ V}$$

$$v_I = +0.67 \text{ V}$$

At  $v_o = +10 \text{ V}$ ,  $i_L = 10 \text{ mA}$  and  $i_{E1} = 24.8 \text{ mA}$

$$\text{Thus, } v_{BE1} = 0.6 + 0.025 \ln(24.8) \\ = 0.68 \text{ V}$$

$$v_I = 10.68 \text{ V}$$

To calculate the incremental voltage gain we use

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + r_{e1}}$$

At  $v_o = -10 \text{ V}$ ,  $i_{E1} = 4.8 \text{ mA}$  and

$$r_{e1} = \frac{25}{4.8} = 5.2 \Omega$$

$$\text{Thus, } \frac{v_o}{v_i} = \frac{1}{1 + 0.0052} = 0.995 \text{ V/V}$$

$$\text{Similarly, at } v_o = 0 \text{ V}, r_{e1} = \frac{25}{14.8} = 1.7 \Omega$$

$$\text{and, } \frac{v_o}{v_i} = \frac{1}{1 + 0.0017} = 0.998 \text{ V/V}$$

At  $v_o = +10 \text{ V}$ ,  $i_{E1} = 24.8 \text{ mA}$  and  $r_{e1} = 1 \Omega$

$$\text{Thus, } \frac{v_o}{v_i} = \frac{1}{1 + 0.001} = 0.999 \text{ V/V}$$

### Ex 13.3

$$\text{a. } P_L = \frac{(\hat{V}_o / \sqrt{2})^2}{R_L} = \frac{(8 / \sqrt{2})^2}{100} = 0.32 \text{ W}$$

$$P_s = 2 V'_{CC} \times I = 2 \times 10 \times 100 \times 10^{-3} \\ = 2 \text{ W}$$

$$\text{Efficiency } \eta = \frac{P_L}{P_s} \times 100 \\ = \frac{0.32}{2} \times 100 \\ = 16\%$$

### Ex 13.4

$$\text{a) } P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L} \\ = \frac{1}{2} \frac{(4.5)^2}{4} = 2.53 \text{ W}$$

$$\text{b) } P_+ = P_- = V_{CC} \times \frac{1}{\pi} \frac{\hat{V}_o}{R_L} \\ = 6 \times \frac{1}{\pi} \times \frac{4.5}{4} = 2.15 \text{ W}$$

$$\text{c) } \eta = \frac{P_L}{P_s} \times 100 = \frac{2.53}{2 \times 2.15} \times 100 \\ = 59\%$$

$$\text{d) Peak input currents} = \frac{1}{\beta + 1} \frac{\hat{V}_o}{R_L} \\ = \frac{1}{51} \times \frac{4.5}{4} \\ = 22.1 \text{ mA}$$

(e) Using Eq. 10.22

$$P_{DNmax} = P_{DPmax} = \frac{V_{CC}^2}{\pi^2 R_L} \\ = \frac{6^2}{\pi^2 \times 4} = 0.91 \text{ W}$$

### Ex 13.5

(a) The quiescent power dissipated in each transistor is  $I_Q \times V_{CC}$

$$\text{Total power dissipated in the two transistors} \\ = 2I_Q \times V_{CC} \\ = 2 \times 2 \times 10^{-3} \times 15 \\ = 60 \text{ mW}$$

(b)  $I_Q$  is increased to 10 mA

At  $V_o = 0$ ,  $i_N = i_P = 10 \text{ mA}$

From equation 13.31

$$R_{out} = \frac{V_T}{i_P + i_N} = \frac{25}{10 + 10} = 1.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{out}} = \frac{100}{100 + 1.25}$$

### Exercise 13--1

$$\frac{v_o}{v_i} = 0.988 \text{ at } v_o = 0 \text{ V}$$

At  $v_o = 10 \text{ V}$ ,

$$i_L = \frac{10 \text{ V}}{100 \Omega} = 0.1 \text{ A} = 100 \text{ mA}$$

use equation 13.27 to calculate  $i_N$

$$i_N^2 - i_N i_L - I_Q^2 = 0$$

$$i_N^2 - 100 i_N - 10^2 = 0$$

$$\Rightarrow i_N = 99.99 \text{ mA}$$

using equation 13.26

$$i_P = \frac{I_Q^2}{I_N} \approx 1 \text{ mA}$$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{99.99 + 1} \approx 0.2475 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 0.2475} \approx 1$$

$$\% \text{ change} = \frac{1 - 0.988}{1} \times 100 = 1.2\%$$

In example 13.5  $I_Q = 2 \text{ mA}$ , and for  $v_o = 0$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{2 + 2} = 6.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 6.25} = 0.94$$

$$v_o = 10 \text{ V}$$

$$I_L = \frac{10 \text{ V}}{100 \Omega} = 100 \text{ mA}$$

Again calculate  $i_N$  (for  $I_Q = 2 \text{ mA}$ ) using equation 13.27  $i_N = 99.96 \text{ mA}$

$$i_P = \frac{I_Q^2}{I_N} = \frac{2^2}{99.96} = 0.04 \text{ mA}$$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{99.96 + 0.04} = 0.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} \approx 1$$

$$\% \text{ Change} = \frac{1 - 0.94}{1} \times 100 = 6\%$$

For  $I_Q = 10 \text{ mA}$ , change is 1.2%

For  $I_Q = 2 \text{ mA}$ , change is 6%

(c) The quiescent power dissipated in each transistor =  $I_Q \times V_{CC}$

$$\text{Total power dissipated} = 2 \times 10 \times 10^{-3} \times 15 = 300 \text{ mW}$$

### Ex 13.6

From example 13.4  $V_{CC} = 15 \text{ V}$ ,  $R_L = 100 \Omega$ ,  $Q_N$  and  $Q_P$  matched and  $I_S = 10^{-13} \text{ A}$  and  $\beta = 50$ ,  $I_{\text{Bias}} = 3 \text{ mA}$


$$\text{For } v_o = 10 \text{ V}, I_L = \frac{10}{100} = 0.1 \text{ A}$$

$$\text{As a first approximation } i_N \approx 0.1 \text{ A}, i_P = 0, i_{BN} \approx \frac{0.1 \text{ A}}{50 + 1} \approx 2 \text{ mA}$$

$$i_D = I_{\text{Bias}} - i_{BN} = 3 - 2 = 1 \text{ mA}$$

$$V_{BB} = 2 V_T \ln \left( \frac{10^{-3}}{\frac{1}{3} \times 10^{-13}} \right)$$

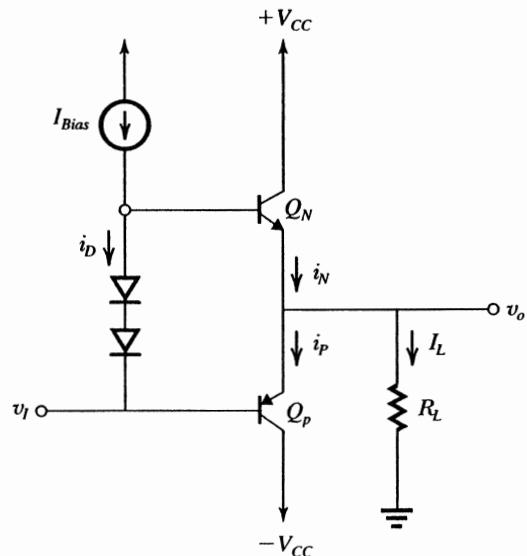This  $\frac{1}{3}$  is because biasing diodes have  $\frac{1}{3}$  area of the output devices.



$$\text{But } V_{BB} = V_{BEN} + V_{BEP} = \quad (1)$$

$$V_T \ln \left( \frac{i_N}{I_S} \right) + V_T \ln \left( \frac{i_N - i_L}{I_S} \right) \\ = V_T \ln \left[ \frac{i_N(i_N - i_L)}{I_S^2} \right] \quad (2)$$

Equating equations 1 and 2

$$2V_T \ln \left( \frac{10^{-3}}{\frac{1}{3} \times 10^{-13}} \right) = V_T \ln \left( \frac{i_N - i_L}{I_S^2} \right)$$

$$\left( \frac{10^{-3}}{\frac{1}{3} \times 10^{-13}} \right)^2 = \frac{i_N(i_N - 0.1)}{(10^{-13})^2}$$

$$i_N(i_N - 0.1) = 9 \times 10^{-6}$$

If  $i_N$  is in mA, then

$$i_N(i_N - 100) = 9$$

$$i_N^2 - 100 i_N - 9 = 0$$

$$\Rightarrow i_N = 100.1 \text{ mA}$$

$$i_P = i_N - i_L = 0.1 \text{ mA}$$

$$\text{For } v_o = -10 \text{ V} \text{ and } i_L = \frac{-10}{100} = -0.1 \text{ A}$$

$$= -100 \text{ mA}$$

As a first approximation assume  $i_P \approx 100 \text{ mA}$ ,  $i_N \approx 0$  since  $i_N = 0$ , current through diodes = 3 mA

### Exercise 13-2

$$\therefore V_{BB} = 2V_T \ln \left( \frac{\frac{3 \times 10^{-3}}{1}{\times}10^{-13}}{3} \right) \quad (3)$$

$$\begin{aligned} \text{But } V_{BB} &= V_T \ln \left( \frac{i_N}{10^{-13}} \right) + V_T \ln \left( \frac{i_P}{10^{-13}} \right) \\ &= V_T \ln \left( \frac{i_P - i_L}{10^{-13}} \right) + V_T \ln \left( \frac{i_P}{10^{-13}} \right) \quad (4) \end{aligned}$$

Here  $i_L = 0.1 \text{ A}$

Equating equations 3 and 4

$$2V_T \ln \left( \frac{\frac{3 \times 10^{-3}}{1}{\times}10^{-13}}{3} \right) =$$

$$V_T \ln \left( \frac{i_P - 0.1}{10^{-13}} \right) + V_T \ln \left( \frac{i_P}{10^{-13}} \right)$$

$$\left( \frac{\frac{3 \times 10^{-3}}{1}{\times}10^{-13}}{3} \right)^2 = \frac{i_P(i_P - 0.1)}{(10^{-13})^2}$$

$$i_P(i_P - 0.1) = 81 \times 10^{-6}$$

Expressing currents in mA

$$i_P(i_P - 100) = 81$$

$$i_P^2 - 100i_P - 81 = 0$$

$$\Rightarrow i_P = 100.8 \text{ mA}$$

$$i_N = i_P - i_L = 0.8 \text{ mA}$$

### Ex 13 . 7

$$\Delta I_C = g_m \times 2 \text{ mV} / ^\circ\text{C} \times 5 \text{ }^\circ\text{C}, \text{ mA}$$

where  $g_m$  is in mA / mV

$$g_m = \frac{10 \text{ mA}}{25 \text{ mV}} = 0.4 \text{ mA / mV}$$

$$\text{Thus, } \Delta I_C = 0.4 \times 2 \times 5 = 4 \text{ mA}$$

### Ex 13 . 8

Refer to Fig. 10 . 14

(a) To obtain a terminal voltage of 1.2 V, and since  $\beta_1$  is very large, it follows, that  $V_{R1} = V_{R2} = 0.6 \text{ V}$ .

Thus  $I_{C1} = 1 \text{ mA}$

$$I_R = \frac{1.2 \text{ V}}{R_1 + R_2} = \frac{1.2}{2.4} = 0.5 \text{ mA}$$

$$\text{Thus, } I = I_{C1} + I_R = 1.5 \text{ mA}$$

(b) For  $\Delta V_{BB} = +50 \text{ mV}$ :

$$V_{BB} = 1.25 \text{ V} \quad I_R = \frac{1.25}{2.4} = 0.52 \text{ mA}$$

$$V_{BE} = \frac{1.25}{2} = 0.625 \text{ V}$$

$$I_{C1} = 1 \times e^{\frac{\Delta V_{BE}}{V_T}} = e^{0.025/0.025}$$

$$= 2.72 \text{ mA}$$

$$I = 2.72 + 0.52 = 3.24 \text{ mA}$$

For  $\Delta V_{BB} = +100 \text{ mV}$

$$V_{BB} = 1.3 \text{ V} \quad I_R = \frac{1.3}{2.4} = 0.54 \text{ mA}$$

$$V_{BE} = \frac{1.3}{2} = 0.65 \text{ V}$$

$$I_{C1} = 1 \times e^{\frac{\Delta V_{BE}}{V_T}} = 1 \times e^{0.05/0.025}$$

$$= 7.39$$

$$I = 7.39 + 0.54 = 7.93 \text{ mA}$$

For  $\Delta V_{BB} = +200 \text{ mV}$ :

$$V_{BB} = 1.4 \text{ V} \quad I_R = \frac{1.4}{2.4} = 0.58 \text{ mA}$$

$$V_{BE} = 0.7 \text{ V}$$

$$I_{C1} = 1 \times e^{0.1/0.025} = 54.60 \text{ mA}$$

$$I = 54.60 + 0.58 = 55.18 \text{ mA}$$

For  $\Delta V_{BB} = -50 \text{ mV}$

$$V_{BB} = 1.15 \text{ V} \quad I_R = \frac{1.15}{2.4} = 0.48 \text{ mA}$$

$$V_{BE} = \frac{1.15}{2} = 0.575$$

$$I_{C1} = 1 \times e^{-0.025/0.025} = 0.37 \text{ mA}$$

$$I = 0.48 + 0.37 = 0.85 \text{ mA}$$

For  $\Delta V_{BB} = -100 \text{ mV}$ :

$$V_{BB} = 1.1 \text{ V} \quad I_R = \frac{1.1}{2.4} = 0.46 \text{ mA}$$

$$V_{BE} = 0.55 \text{ V}$$

$$I_{C1} = 1 \times e^{-0.05/0.025} = 0.13 \text{ mA}$$

$$I = 0.46 + 0.13 = 0.59 \text{ mA}$$

For  $\Delta V_{BB} = -200 \text{ mV}$ :

$$V_{BB} = 1.0 \text{ V} \quad I_R = \frac{1}{2.4} = 0.417 \text{ mA}$$

$$V_{BE} = 0.5 \text{ V}$$

$$I_{C1} = 1 \times e^{-0.1/0.025} = 0.018 \text{ mA}$$

$$I = 0.43 \text{ mA}$$

### Ex 13 . 9

Using equation 13 . 43

$$I_Q = I_{\text{Bias}} \frac{(W/L)_n}{(W/L)_1}$$

$$1 = 0.2 \frac{(W/L)_n}{(W/L)_P}$$

$$\frac{(W/L)_n}{(W/L)_1} = 5$$

$$Q_i: I_{\text{Bias}} = \frac{1}{2} k'_n \left( \frac{W}{L} \right)_1 (V_{GS} - V_{tn})^2$$

$$0.2 = \frac{1}{2} \times 0.250 \left( \frac{W}{L} \right)_1 (0.2)^2$$

$$\Rightarrow \left( \frac{W}{L} \right)_1 = 40$$

Exercise 13--3

$$Q_2: I_{\text{Bias}} = \frac{1}{2} k_p' \left(\frac{W}{L}\right)_2 (V_{GS} - |V_t|)^2$$

$$0.2 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_2 \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_2 = 100$$

$$Q_N: I_Q = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_N (V_{GS} - V_t)^2$$

$$1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_N 0.2^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_N = 200$$

$$Q_P: I_Q = \frac{1}{2} k_p' \left(\frac{W}{L}\right)_P (V_{GS} - |V_t|)^2$$

$$1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_P \times 0.2^2$$

$$\left(\frac{W}{L}\right)_P = 500$$

$$\text{Now } V_{GG} = V_{GS1} + V_{GS2}$$

$$= (V_{ov1} + V_t) + (V_{ov2} + |V_t|)$$

$$= (0.2 + 0.5) + (0.2 + 0.5)$$

$$= 1.4 \text{ V}$$

### Ex 13.10

$$I_N = i_{L_{\max}} = 10 \text{ mA}$$

$$\therefore 10 = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_n V_{ov}^2$$

$$10 = \frac{1}{2} \times 0.250 \times 200 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = 0.63 \text{ V}$$

Using equation 13.46

$$V_{omax} = V_{DD} - V_{ov}|_{\text{Bias}} - V_{tn} - V_{ovN}$$

$$= 2.5 - 0.2 - 0.5 - 0.63$$

$$= 1.17 \text{ V}$$

### Ex 13.11

New values of W/L are

$$\left(\frac{W}{L}\right)_P = \frac{2000}{2} = 1000$$

$$\left(\frac{W}{L}\right)_N = \frac{800}{2} = 400$$

$$I_Q = \frac{1}{2} k_p' \left(\frac{W}{L}\right)_P V_{ov}^2$$

$$1 \times 10^{-3} = \frac{1}{2} \times 0.1 \times 10^{-3} \times 1000 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = 0.14 \text{ V}$$

Gain Error =

$$-\frac{V_{ov}}{4\mu I_Q R_L} = -\frac{0.14}{4 \times 10 \times 1 \times 10^{-3} \times 100}$$

$$= -0.035$$

$$\text{Gain Error} = -0.035 \times 100 = 3.5\%$$

$$g_{mn} = g_{mp} = \frac{2I_Q}{V_{ov}} = \frac{2 \times 1 \times 10^{-3}}{0.14}$$

$$= 14.14 \text{ mA/V}$$

$$R_{\text{out}} = \frac{1}{\mu(g_{mp} + g_{mn})} =$$

$$\frac{1}{10 \times (14.14 + 14.14) \times 10^{-3}}$$

$$\approx 3.5 \Omega$$

### Ex 13.12

See solution on next page

**Ex 13 . 12**

Need to prove when  $V_{o2} = 4I_Q R_L$  then  $V_{GSN2} = V_m$

Assume  $Q_N$  off ( $V_{GSN} = V_m$ ) so  $i_{N2} = 0$  and

$$i_{p2} = i_{L2}$$

$$i_{p2} = i_{L2} = \frac{V_{o2}}{R_L} = 4I_Q$$

$$4I_Q = \frac{1}{2}k'_p \left(\frac{W}{L}\right)_p (V_{SGP2} - |V_{tp}|)^2$$

$$\begin{aligned} & \sqrt{4 \left( \frac{1}{2} k'_p \left( \frac{W}{L} \right)_p (V_{SGPQ} - |V_{tp}|)^2 \right)} \\ &= \sqrt{\frac{1}{2} k'_p \left( \frac{W}{L} \right)_p (V_{SGP2} - |V_{tp}|)^2} \end{aligned}$$

$$2(V_{SGPQ} - |V_{tp}|) = (V_{SGP2} - |V_{tp}|)$$

$$\begin{aligned} V_{SGP2} &= 2V_{SGPQ} - 2|V_{tp}| + |V_{tp}| \\ &= 2V_{SGPQ} - |V_{tp}| \end{aligned} \quad (1)$$

Find  $V_{i2}$  for the gate voltage,  $V_{GP2}$ :

$$V_{GP2} = (V_{DD} - V_{SGPQ}) + \mu(V_{o2} - V_{i2})$$

$$(V_{GP2} - V_{DD}) = -V_{SGPQ} + \mu(V_{o2} - V_{i2})$$

$$[V_{GSP2} \text{ OR}] - V_{SGP2} = -V_{SGPQ} + \mu(V_{o2} - V_{i2})$$

using (1):

$$-2V_{SGPQ} + |V_{tp}| = -V_{SGPQ} + \mu(V_{o2} - V_{i2})$$

$$\mu(V_{i2} - V_{o2}) = -V_{SGPQ} + 2V_{SGPQ} - |V_{tp}|$$

$$V_{i2} = +V_{o2} + \frac{(V_{SGPQ} - |V_{tp}|)}{\mu} = V_{o2} + \frac{V_{ovQ}}{\mu}$$

Plug this value for  $V_{i2}$  into the value for  $V_{GN2}$

$$\text{and show } V_{GSN2} = V_{iN}$$

$$(-V_{SS} + V_{GSNQ}) + \mu(V_{o2} - V_{i2}) = V_{GN2} - (-V_{SS})$$

$$V_{GSNQ} + \mu \left( V_{o2} - V_{i2} - \frac{V_{ovQ}}{\mu} \right) = V_{GSN2}$$

where

$$V_{ovQ} = (V_{GSNQ} - V_m) = (V_{SGPQ} - |V_{tp}|)$$

$$V_{GSNQ} - V_{GSNQ} + V_m = V_{GSN2} \text{ Q.E.D.}$$

Same proof for p transistor.

**Ex 13.13**

$$T_J - T_A = \theta_{JA} P_D$$

$$200 - 25 = \theta_{JA} \times 50$$

$$\theta_{JA} = \frac{175}{50} = 3.5^\circ\text{C/W}$$

$$\text{But, } \theta_{JA} = \theta_{JC} + \theta_{CS} + \theta_{SA}$$

$$3.5 = 1.4 + 0.6 + \theta_{SA}$$

$$\Rightarrow \theta_{SA} = 1.5^\circ\text{C/W}$$

$$T_J - T_C = \theta_{JC} \times P_D$$

$$T_C = T_J - \theta_{JC} \times P_D$$


$$= 200 - 1.4 \times 50$$

$$= 130^\circ\text{C}$$

$$V_{E1} = 10.7 \text{ V}$$

and,


$$I_1 = \frac{15 - 10.7}{5} = 0.86 \text{ mA}$$

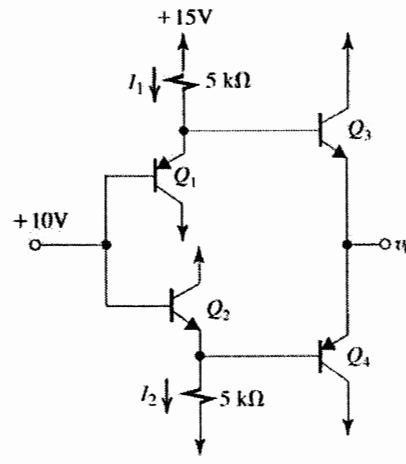

**Ex 13.14**

(a) From symmetry we see that all transistors will conduct equal currents and have equal  $V_{BE}$ 's. Thus.

$$v_o = 0 \text{ V}$$

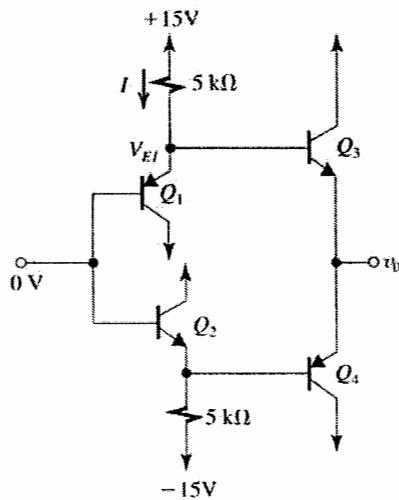

If  $V_{BE} \geq 0.7 \text{ V}$  Then

$$V_{E1} = 0.7 \text{ V} \text{ and } I_1 = \frac{15 - 0.7}{5} = 2.86 \text{ mA}$$

If we neglect  $I_{B3}$  then

$$I_{C1} \approx 2.86 \text{ mA}$$

At this current,  $V_{BE}$  is given by

$$V_{BE} = 0.025 \ln\left(\frac{2.86 \times 10^{-3}}{3.3 \times 10^{-14}}\right) \approx 0.63 \text{ V}$$

Thus  $V_{E1} = 0.63 \text{ V}$  and  $I_1 = 2.87 \text{ mA}$

No more iterations are required and

$$I_{C1} = I_{C2} = I_{C3} = I_{C4} \approx 2.87 \text{ mA}$$

(b) For  $v_t = +10 \text{ V}$ :

To start the iterations let  $V_{BE1} \geq 0.7 \text{ V}$

Thus,

Neglecting  $I_{B3}$ ,

$$I_{C1} \approx I_{E1} \approx J_1 = 0.86 \text{ mA}$$

But at this current

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right)$$

$$= 0.025 \ln\left(\frac{0.86 \times 10^{-3}}{3.3 \times 10^{-14}}\right)$$

$$= 0.6 \text{ V}$$

Thus,  $V_{E1} = +10.6 \text{ V}$  and  $I_1 = 0.88 \text{ mA}$ . No further iterations are required and  $I_{C1} \approx 0.88 \text{ mA}$ .

To find  $I_{C2}$  we use an identical procedure :

$$V_{BE2} \approx 0.7 \text{ V}$$

$$V_{E2} = 10 - 0.7 = +9.3 \text{ V}$$

$$I_2 = \frac{9.3 - (-15)}{5} = 4.86 \text{ mA}$$

$$V_{BE2} = 0.025 \ln\left(\frac{4.86 \times 10^{-3}}{3.3 \times 10^{-14}}\right)$$

$$= 0.643 \text{ V}$$

$$V_{E2} = 10 - 0.643 = +9.357 \text{ V}$$

$$I_2 = 4.87 \text{ mA}$$

$$I_{C2} \approx 4.87 \text{ mA}$$

Finally,

$$I_{C3} = I_{C4} = 3.3 \times 10^{-14} e^{\frac{V_{BE}}{V_T}}$$

Where

$$V_{BE} = \frac{V_{E1} - V_{E2}}{2} = 0.62 \text{ V}$$

$$\text{Thus, } I_{C3} = I_{C4} \approx 1.95 \text{ mA}$$

The symmetry of the circuit enables us to find the values for  $v_I = -10 \text{ V}$  as follows:

$$I_{C1} = 4.87 \text{ mA} \quad I_{C2} = 0.88 \text{ mA}$$

$$I_{C3} = I_{C4} = 1.95 \text{ mA}$$

$$\text{For } v_I = +10 \text{ V}, v_o = V_{E1} - V_{BE3} \\ = 10.6 - 0.62 = +9.98 \text{ V}$$

$$\text{For } v_I = -10 \text{ V}, v_o = V_{E1} - V_{BE3} \\ = -9.357 - 0.62 = -9.98 \text{ V}$$

(c) For  $v_I = +10 \text{ V}$ ,


$$v_O \approx 10 \text{ V}$$

$$I_L \approx 100 \text{ mA}$$

$$I_{C3} \approx 100 \text{ mA}$$

$$I_{B3} = \frac{100}{201} \\ \approx 0.5 \text{ mA}$$

$$\approx 0.5 \text{ mA}$$

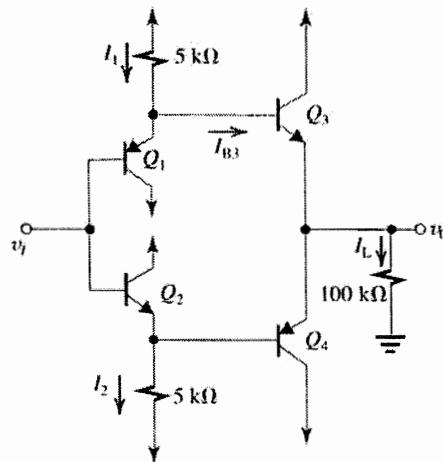

Assuming that  $V_{BE1}$  has not changed much from 0.6 V, then

$$V_{E1} \approx 10.6 \text{ V}$$

$$I_1 = \frac{15 - 10.6}{5} = 0.88 \text{ mA}$$

$$I_{E1} = I_1 - I_{B3} = 0.88 - 0.5 = 0.38 \text{ mA}$$

$$I_{C1} \approx 0.38 \text{ mA}$$

$$V_{BE1} = 0.025 \ln\left(\frac{0.38 \times 10^{-3}}{3.3 \times 10^{-14}}\right)$$

$$= 0.58 \text{ V}$$

$$V_{E1} = 10.88 \text{ V}$$

$$I_1 = \frac{15 - 10.88}{5} = 0.88 \text{ mA}$$

Thus,  $I_{C1} \approx 0.30 \text{ mA}$

Now for  $Q_2$  we have:

$$V_{BE2} = 0.643 \text{ V}$$

$$V_{E2} = 10 - 0.643 = 9.357$$

$$I_2 = 4.87 \text{ mA}$$

$$I_{B4} \approx 0$$

$$I_{C2} \approx 4.87 \text{ mA} \text{ (as in (b))}$$

Assuming that  $I_{C3} \approx 100 \text{ mA}$ ,

$$V_{BE3} = 0.025 \ln\left(\frac{100 \times 10^{-3}}{3.3 \times 10^{-14}}\right)$$

$$= 0.72 \text{ V}$$

$$\text{Thus, } v_o = V_{E1} - V_{BE3} \\ = 10.58 - 0.72 = +9.86 \text{ V}$$

$$V_{BE4} = v_o - V_{E2} \\ = 9.86 - 9.36 = 0.5 \text{ V}$$

$$\text{Thus, } I_{C4} = 3.3 \times 10^{-14} e^{0.5/0.025} \\ \approx 0.02 \text{ mA}$$

For symmetry we find the value for the case

$$v_I = -10 \text{ V} \text{ as.}$$

$$I_{C1} = 4.87 \text{ mA} \quad I_{C2} = 0.38 \text{ mA}$$

$$I_{C3} = 0.02 \text{ mA} \quad I_{C4} = 100 \text{ mA}$$

$$v_o = -9.86 \text{ V.}$$

### Ex 13.15


For  $Q_1$ :

$$i_{C1} = I_{SP} e^{\frac{v_{EB}}{V_T}}$$

$$\frac{i_C}{\beta_N + 1} = I_{SP} e^{\frac{v_{EB}}{V_T}}$$

$$i_C \approx \beta_N I_{SP} e^{\frac{v_{EB}}{V_T}}$$

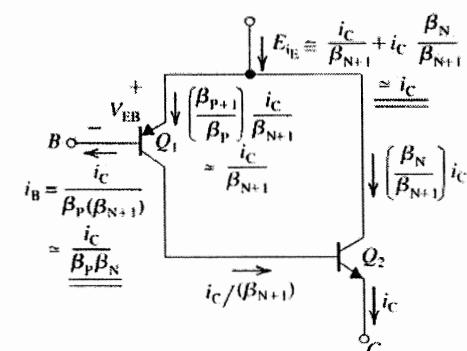Thus, Effective scale current =  $\beta_N I_{SP}$



$$(b) \text{ Effective current gain } = \frac{i_C}{i_B} = \beta_P \beta_N$$

$$= 20 \times 50 = 1000$$

$$100 \times 10^{-3} = 50 \times 10^{-14} e^{\frac{v_{EB}}{0.025}}$$

$$v_{EB} = 0.025 \ln(2 \times 10^{11})$$

$$= 0.651 \text{ V}$$

### Ex 13.16

See Figure 13.34

When  $V_{RES} = 150 \times 10^{-4} \times R_{E1}$ , then  $I_{C5} = I_{B5}$   
= 2 mA

$$V_{BB5} = V_T \ln\left(\frac{I_{C5}}{I_S}\right)$$

$$= 25 \times 10^{-3} \ln\left(\frac{2 \times 10^{-3}}{10^{-14}}\right)$$

$$= 0.651 \text{ V}$$

### Exercise 13-7

$$150 \times 10^{-3} R_B = 0.651$$

$$R_B = 4.34 \Omega$$

If peak output current = 100 mA

$$V_{BE} = R_E \times 100 \text{ mA} = 4.34 \times 100 \times 10^{-3}$$

$$= 0.434 \text{ V}$$

$$i_{CS} = I_S e^{V_{BE5}/V_T}$$

$$= 10^{-14} e^{0.434/25 \times 10^{-3}}$$

$$\approx 0.35 \mu\text{A}$$

### Ex 13.17

$$\text{Total current out of mode B} = \frac{2v_i}{R_3} + \frac{v_o}{R_2}$$

Thus


$$\left( \frac{2v_i}{R_3} + \frac{v_o}{R_2} \right) R = -\frac{v_o}{A}$$

$$\Rightarrow v_o \left( \frac{1}{A} + \frac{R}{R_1} \right) = -\frac{2R}{R_3} v_i$$

$$\frac{v_o}{v_i} = \frac{-\frac{2R}{R_3}}{\frac{1}{A} + \frac{R}{R_1}}$$

$$= \frac{-2R_2/R_3}{1 + (R_2/AR)}$$

Q.E.D

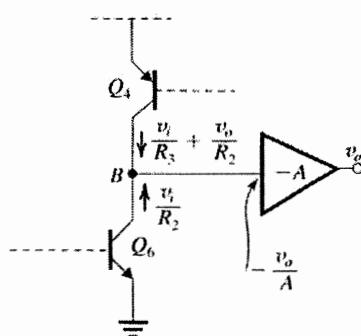

For  $AR \gg R_2$

$$\frac{v_o}{v_i} \approx -\frac{2R_2}{R_3}$$

### Ex 13.18

$$P_{Dmax} = \frac{T_{Jmax} - T_A}{\theta_{JA}}$$

$$= \frac{150 - 50}{35} = 2.9 \text{ W}$$

### Ex 13.19

For Fig. 13.32 we see that for  $P_{dissipation}$  to be less than 2.9 W, a maximum supply voltage of 20 V is called for. The 20-V-supply curve intersects the 3% distortion line at a point for which the output power is 4.2 W. Since

$$P_L = \frac{(\hat{V}_o / \sqrt{2})^2}{R_L}$$

$$\text{Thus } \hat{V}_o = \sqrt{4.2 \times 2 \times 8} = 8.2 \text{ V}$$

or 16.4 V peak-to-peak

### Ex 13.20

Voltage gain = 2 K

$$\text{where } K = \frac{R_4}{R_3} = 1 + \frac{R_2}{R_1} = 1.5$$

Thus,  $A_v = 3 \text{ V/V}$

Input resistance =  $R_3 = 10 \text{ k}\Omega$

$$\text{Peak-to-Peak } v_o = 3 \times 20 = 60 \text{ V}$$

$$\text{Peak load current} = \frac{30 \text{ V}}{8 \Omega} = 3.75 \text{ A}$$

$$P_L = \frac{(30/\sqrt{2})^2}{8} = 56.25 \text{ W}$$

### Ex 13.21

We wish to value

$$\frac{\partial V_{GG}}{\partial T} = -3 - 3 = -6 \text{ mV/}^\circ\text{C}$$

but From Eq. 10.58

$$\frac{\partial V_{GG}}{\partial T} = \left( 1 + \frac{R_3}{R_4} \right) \frac{\partial V_{BE6}}{\partial T}$$

$$\text{Thus } -6 = \left( 1 + \frac{R_3}{R_4} \right) \times -2$$

$$\Rightarrow \frac{R_3}{R_4} = 2$$

### Ex 13.22

Refer to Figure 13.44

$$I_{DN} = I_{DP} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (|V_{GS}| - V_t)^2$$

$$100 \times 10^{-3} = \frac{1}{2} \times 2 (|V_{GS}| - 3)^2$$

$$0.1 = (|V_{GS}| - V_t)^2$$

$$\Rightarrow V_{GS} = 3.32 \text{ V}$$

$$V_{os} = 2 V_{GS} = 6.64 \text{ V}$$

$$R = \frac{V_{GG}}{20 \text{ mA}} = \frac{6.64}{20 \times 10^{-3}} = 3.32 \Omega$$

Using equation

$$V_{GG} = \left( 1 + \frac{R_3}{R_4} \right) V_{BE6} + \left( 1 + \frac{R_1}{R_2} \right) V_{BE5} - 4 V_{BE}$$

$$6.64 = (1 + 2) \times 0.7 + \left( 1 + \frac{R_1}{R_2} \right) \times 0.7 - 4 \times 0.7$$

$$\Rightarrow \frac{R_1}{R_2} \geq 9.5$$

**Ex: 14 . 1**

In the low-output state, the transistor is on and

$$R_{on} = r_{DS} \approx \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)}$$

Therefore, the current drawn from the supply in this state can be calculated as:

$$\begin{aligned} I_{DD} &= \frac{V_{DD}}{R_D + r_{DS}} = 50 \text{ } \mu\text{A} \Rightarrow R_D + r_{DS} \\ &= \frac{2.5 \text{ V}}{50 \text{ } \mu\text{A}} = 50 \text{ k}\Omega \end{aligned}$$

$$\text{Also: } V_{OL} = V_{DD} \frac{r_{DS}}{R_D + r_{DS}}$$

Substituting for

$$R_D + r_{DS} : 0.1 = 2.5 \frac{r_{DS}}{50 \text{ k}\Omega} \Rightarrow r_{DS} = 2 \text{ k}\Omega$$

and hence:  $R_D = 48 \text{ k}\Omega$

To obtain  $\frac{W}{L}$ , we use:

$$\begin{aligned} r_{DS} &= \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)} \Rightarrow \frac{W}{L} \\ &= \frac{1}{2 \times 10^3 \times 125 \times 10^{-6} \times (2.5 - 0.5)} \\ &\therefore \frac{W}{L} = 2 \end{aligned}$$

When the switch is closed or in low-output state, the current drawn from the supply is 50  $\mu\text{A}$ .

$$P_{DD} = V_{DD} I_{DD} = 2.5 \times 50 \times 10^{-6} = 125 \mu\text{W}$$

When the switch is open, no current is drawn from the supply:  $P_{DD} = 0$

**Ex: 14 . 2**

When input is low, the output is high and equal to  $V_{OH}$ . In this case, the switch is connected to  $R_{C2}$ , therefore the current through  $R_{C1}$  is zero.

Hence,  $V_{ON} = V_{CC} = 5\text{V}$ .

When the input is high, the output is low and equal to  $V_{OL}$ . The switch is connected to  $R_{C1}$ . Hence

$$V_{OL} = V_{CC} - R_{C1} I_{EE} = 5 - 2 \times 1 = 3\text{V}$$

**Ex: 14 . 3**

To determine  $\frac{W}{L}$ , we use:  $K_n R_D = \frac{1}{V_t}$  and sub-

stitute  $V_t = 0.089\text{V}$ ,  $R_D = 10^{10}$ ,

$$k_n' = 300 \text{ } \mu\text{A/V}^2$$

$$300 \times 10^{-6} \times \frac{W}{L} \times 10 \times 10^3 = \frac{1}{0.089} \Rightarrow \frac{W}{L} = 3.75$$

Noise margins stay unchanged, because

$V_{OL}, V_{OH}, V_{IH}, V_{TH}$  only depend on  $V_{DD}$ ,  $V_t$ , and  $V_x$ . Since  $V_x$  has not changed, noise margins stay the same.

Inorder to calculate the power dissipation, we need to first recalculate

$$\begin{aligned} I_{DD} &= \frac{V_{DD} - V_{OL}}{R_D} = \frac{1.8 - 0.12}{10 \text{ k}\Omega} = 168 \text{ } \mu\text{A} \\ P_{DD} &= V_{DD} I_{DD} = 1.8 \times 168 \text{ } \mu\text{A} = 302.4 \text{ } \mu\text{W} \\ P_{D_{average}} &= \frac{1}{2} P_{DD} = 151 \text{ } \mu\text{W} \end{aligned}$$

Note that keeping  $V_x$  unchanged resulted in higher power consumption, but noise margins stayed the same.

**Ex: 14 . 4**

To determine  $V_x$ , we use:

$$K_n R_D = \frac{1}{V_t} \text{ and with } R_D = 10 \text{ k}\Omega \text{ and } K_n$$

unchanged:

$$\frac{V_{x2}}{V_{x1}} = \frac{R_{D1}}{R_{D2}} \Rightarrow V_x = 0.089 \times \frac{25}{10} = 0.22\text{V}$$

To calculate the new noise margins, we have to find  $V_{OH}$ ,  $V_{IH}$ ,  $V_{IL}$ ,  $V_{OL}$ .

$$V_{OH} = V_{DD} = 1.8 \text{ V unchanged}$$

$$V_{IL} = V_t + V_x = 0.5 + 0.22 = 0.72 \text{ V}$$

$$V_{IH} = V_t + 1.63 \sqrt{V_{DD} V_x} - V_x$$

$$= 0.5 + 1.63 \sqrt{1.8 \times 0.22} - 0.22 = 1.31\text{V}$$

$$V_{OL} = \frac{V_{DD}}{1 + \frac{V_{DD} - V_t}{V_x}} = \frac{1.8}{1 + \frac{1.8 - 0.5}{0.22}} = 0.26 \text{ V}$$

$$NM_H = V_{OH} - V_{IH} = 1.8 - 1.31 = 0.49 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 0.72 - 0.26 = 0.46 \text{ V}$$

The power dissipation becomes:

$$P_{D_{average}} = \frac{1}{2} P_D = \frac{1}{2} V_{DD} I_{DD} = \frac{1}{2} V_{DD}$$

$$= \frac{V_{DD} - V_{OL}}{R_D}$$

$$P_{D_{average}} = \frac{1}{2} \times 1.8 \times \frac{1.8 - 0.26}{10 \text{ k}\Omega} = 139 \text{ } \mu\text{W}$$

Note that keeping  $\frac{W}{L}$  unchanged resulted in lower noise margins and higher power dissipation.

**Ex: 14 . 5**

$$k_r = \sqrt{\frac{(W/L)_1}{(W/L)_2}} = \sqrt{\frac{3}{1/3}} = 3$$

From Eq. 14.20:  $V_{OH} = V_{DD} - V_t = 1.3$  V  
unchanged  
From Eq. 14.28:

$$V_{OL} = \frac{(V_{DD} - V_p)^2}{2k_r^2(V_{DD} - 2V_t)} = \frac{(1.8 - 0.5)^2}{2 \times 3^2(1.8 - 2 \times 0.5)} = 0.12 \text{ V}$$

From Eq. 14.22  $V_{IL} = V_t = 0.5$  V  
unchanged.

From Eq. 14.23

$$V_M = \frac{V_{DD} + (k_r - 1)V_t}{k_r + 1} = \frac{1.8 + (3 - 1)0.5}{3 + 1} = 0.7 \text{ V}$$

From Eq. 14.26 together with setting

$$\frac{dv_o}{dv_t} = -1;$$

$$2k_r^2[(v_t - v_i)v_o - \frac{1}{2}v_o^2] = (V_{DD} - v_t - v_o)^2$$

$$2k_r^2[v_o + (v_t - v_i)\frac{dv_o}{dv_t} - v_o\frac{dv_o}{dv_t}]$$

$$= -2(V_{DD} - v_t - v_o)\frac{dv_o}{dv_t}$$

Now if we substitute for  $\frac{dv_o}{dv_t} = -1$  then:

$$k_r^2[v_{OL} - v_{IH} + v_t - v_{OL}] = +V_{DD} - V_t - V_{OL}$$

$$\therefore 3^2[0.12 - V_{IH} + 0.5 + 0.12] = 1.8 - 0.5 - 0.12$$

$$9[0.74 - V_{IH}] = 1.18 \Rightarrow V_{IH} = 0.61 \text{ V}$$

$$NM_H = V_{OH} - V_{IH} = 1.3 - 0.61 = 0.69 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 0.5 - 0.12 = 0.38 \text{ V}$$

**Ex: 14 . 6**

The inverter area is approximately

$$A = W_1 L_1 + W_2 L_2 \text{ Since } \frac{W_1}{L_1} = K_r \text{ and}$$

$$\frac{W_2}{L_2} = \frac{1}{K_r}, \text{ we have } W_1 = k_r L_1, \text{ and}$$

$L_2 = k_r W_2$ . Assuming  $k_r > 1$ , we have

$$L_1 = d \text{ and } W_2 = L_1$$

Thus:

$$A = k_r L_1 L_1 + W_2 k_r W_2 = k_r L_1^2 + k_r W_2^2$$

$$= k_r d^2 + k_r d^2 = 2k_r d^2$$

**Ex: 14 . 7**

From Eq. 14.36 we have:  $P_{dyn} = f C V_{DD}^2$

$$P_{dyn} = 100 \times 10^6 \times 100 \times 10^{-15} \times 1.8^2 = 32.4 \times 10^{-6} = 32.4 \mu\text{W}$$

**Ex: 14 . 8**

$$P_{dyn} \alpha C_1 V_{DD}^2 \Rightarrow \frac{P_{dyn1}}{P_{dyn2}} = \frac{C_1 V_{DD1}^2}{C_2 V_{DD2}^2}$$

$$= \frac{0.5}{0.13} \times \frac{5^2}{1.2^2} = 66.73 \approx 66.8$$

**Ex: 14 . 9**

$$V_o(t) = V_o(\infty) - (V_o(\infty) - V_o(O^+))e^{-t/\tau}$$

$$\frac{V_{DD}}{2} = V_{DD} - (V_{DD} - O)e^{-t_{PLH}/(\frac{V_{DD}}{I}) \cdot C}$$

$$\ln\left(-\frac{1}{2}\right) = -\frac{(-t_{PLH})}{V_{DD} \cdot C}$$

$$\therefore t_{PLH} = \frac{V_{DD} \cdot C}{I} \cdot 0.69$$

for  $t_{PLH} = 10$  psec. with  $C = 10 \text{ fF}$  and  $V_{DD} = 1.8 \text{ V}$

$$I = \frac{1.8 \cdot 10f}{10 \text{ P}} \cdot 0.69 = 1.2 \text{ mA}$$

**Ex: 14 . 10**

For  $t_{PLH}$  the output starts at  $V_{OL}$  and goes to  $V_{OH}$  through the Pu which is  $20 \text{ k}\Omega$ :

$$\begin{aligned} V_o(t) &= V_o(\infty) - (V_o(\infty) - V_o(O^+))e^{-t/\tau} \\ \frac{1}{2}(V_{OH} + V_{OL}) &= V_{OH} - (V_{OH} - V_{OL})e^{-t_{PLH}/\tau} \\ \frac{\left(-\frac{1}{2}V_{OH} + \frac{1}{2}V_{OL}\right)}{-\left(V_{OH} + V_{OL}\right)} &= e^{-t_{PLH}/\tau} \\ \tau\left(-\ln\left(\frac{1}{2}\right)\right) &= t_{PLH} \end{aligned}$$

$$t_{PLH} = 0.69 \text{ R.C} = 0.69 (20 \text{ K}) (10f) = 138 \text{ pSec}$$

For  $t_{PHL}$ , the output starts at  $V_{OH}$  and goes to  $V_{OL}$  through  $P_O$  which is  $10 \text{ k}\Omega$ .

$$\begin{aligned} \frac{1}{2}(V_{OH} + V_{OL}) &= V_{OL} - (V_{OL} - V_{OH})e^{-t_{PHL}/\tau} \\ \frac{\left(\frac{1}{2}V_{OH} + \frac{1}{2}V_{OL} - \frac{2}{2}V_{OL}\right)}{-V_{OL} + V_{OH}} &= e^{-t_{PHL}/\tau} \\ \tau\left(-\ln\left(\frac{1}{2}\right)\right) &= t_{PHL} \\ t_{PHL} &= 0.69 \cdot \text{R.C} = 0.69 \times 10 \text{ K} \times 10f = 69 \text{ psec} \\ t_P &= \frac{1}{2}(t_{PHL} + t_{PLH}) = \frac{1}{2}(138 \text{ p} + 69 \text{ p}) = 10^4 \text{ psec} \end{aligned}$$

**Ex: 14 . 11**

$$V_o(t) = V_o(\infty) - [V_o(\infty) - V_o(0^+)]e^{-t/\tau}$$

$$V_o(t) = O - [V_{DD} - O]e^{-t/(2 K \cdot 100 f)} = \tau$$

$t_f$  is when voltage is  $= .1 V_{DD}$ .

$$.1 V_{DD} = -V_{DD} e^{-(0 - t_f)/\tau}$$

$$-\ln(.1) = t_f \frac{1}{\tau}$$

$$2.3 \cdot \tau \approx t_f$$

$$t_f = 2.3 \cdot 2 K \cdot 100 f = 0.46 \text{ nsec}$$

**Ex: 14.12**

a) From Eq. 14.58

$$V_M = \frac{r(V_{DD} - |V_{tp}|) + V_m}{r+1} \text{ or}$$

$$0.6 = \frac{r(1.2 - 0.4) + 0.4}{1+r} \Rightarrow 0.6 + 0.6r \\ = 0.8r + 0.4 \Rightarrow r = 1$$

$$r = \sqrt{\frac{\mu_p w_p}{\mu_n w_n}} = \sqrt{\frac{1}{4} \times \frac{w_p}{w_n}} = 1 \Rightarrow \frac{w_p}{w_n} = 4$$

$$\Rightarrow (w_p = 4 \times 0.13 \mu\text{m} = 0.52 \mu\text{m})$$

$$\text{b) } V_{OH} = V_{DD} = 1.2\text{V}, V_{OL} = 0\text{V}$$

$$V_{IH} = \frac{1}{8}(5V_{DD} - 2V_t) = \frac{1}{8}(5 \times 1.2 - 2 \times 0.4) \\ = 0.65\text{V}$$

$$V_{IL} = \frac{1}{8}(3V_{DD} + 2V_t) = \frac{1}{8}(3 \times 1.2 + 2 \times 0.4) \\ = 0.55\text{V}$$

$$NM_H = V_{OH} - V_{IH} = 1.2 - 0.65 = 0.55\text{V}$$

$$NM_L = V_{IL} - V_{OL} = 0.55\text{V}$$

c) The output resistance of the inverter in the low-output state is:

$$r_{DSN} = \frac{1}{\mu_n C_m \left(\frac{W}{L}\right)_n (V_{DD} - V_m)}$$

$$= \frac{1}{430 \times 10^{-6} \times 1(1.2 - 0.4)} \\ = 2.9 \text{k}\Omega$$

Since  $Q_N$  and  $Q_P$  are matched, the output resistance in the high-output state is the same:

$$r_{DSP} = r_{DSN} = 2.9 \text{k}\Omega$$

d) For  $\left(\frac{W}{L}\right)_p = \left(\frac{W}{L}\right)_n = 1.0$ , we have

$$r = \sqrt{\frac{1}{4} \times 1} = 0.5,$$

$$\text{hence: } V_M = \frac{0.5(1.2 - 0.4) + 0.4}{1 + 0.5} = 0.53\text{V}$$

**Ex: 14.13**

Using Eq. 14.58 and 14.59

$$V_M = \frac{r(V_{DD} - |V_{tp}| + V_m)}{r+1} \Rightarrow 2.5$$

$$= \frac{r(5-1)+1}{r+1} \Rightarrow r = 1$$

$$r = \sqrt{\frac{\mu_p w_p}{\mu_n w_n}} \Rightarrow \frac{w_p}{w_n} = \frac{1}{1/2} = 2$$

When  $V_I = V_{DD}$  and  $V_O = 0.2\text{V}$ ,  $Q_N$  operates in triode region and hence the circuit is given as:

$$i_D = k_n' \left(\frac{W}{L}\right)_n [(V_I - V_m)V_O - \frac{1}{2}V_O^2]$$

$$\Rightarrow 0.2 \times 10^{-3} = 50 \times 10^{-6} \times \left(\frac{W}{L}\right)_n$$

$$[(5-1)0.2 - \frac{1}{2} \times 0.2^2] \Rightarrow \left(\frac{W}{L}\right)_n = 5$$

$$\text{From above: } w_p = 2w_n \Rightarrow \left(\frac{W}{L}\right)_p = 10$$

**Ex: 14.14**

Using Eqs 14.63 to 14.67 we have:

$$t_{PHL} = \frac{\alpha_n C}{k_n' \left(\frac{W}{L}\right)_n V_{DD}},$$

$$\alpha_n = 2\frac{7}{4} - \frac{3V_m}{V_{DD}} + \left(\frac{V_m}{V_{DD}}\right)^2$$

$$= 2\frac{7}{4} - \frac{3 \times 0.5}{1.8} + \left(\frac{0.5}{1.8}\right)^2 = 1.99$$

Noting that  $V_m = |V_{tp}|$ , then  $\alpha_n = \alpha_p = 1.99$

$$t_{PHL} = \frac{1.99 \times 10 \times 10^{-15}}{300 \times 10^{-6} \times 1.5 \times 1.8} = 24.7\text{ps}$$

$$t_{PLH} = \frac{\alpha_p C}{k_p' \left(\frac{W}{L}\right)_p V_{DD}} \text{ or}$$

$$\frac{t_{PLH}}{t_{PHL}} = \frac{k_n' \left(\frac{W}{L}\right)_n}{k_p' \left(\frac{W}{L}\right)_p} \Rightarrow t_{PLH} = 24.6 \times 4 \times \frac{1.5}{3}$$

$$= 49.4\text{ps}$$

$$t_p = \frac{1}{2}(t_{PLH} + t_{PHL}) = \frac{1}{2}(24.7 + 49.4) = 37\text{ps}$$

**Ex: 14.15**

From Eq. 14.68 we have:

$$t_{PHL} = 0.69 R_N C \text{ and if we substitute for } R_N$$

$$\text{from Eq. 14.70 i.e. } R_N = \frac{12.5}{\left(\frac{W}{L}\right)_n} \text{ k}\Omega \text{ then:}$$

$$t_{PHL} = 0.69 \times \frac{12.5}{\left(\frac{W}{L}\right)_n} \times 10^3 \times C = \frac{8625C}{\left(\frac{W}{L}\right)_n} \text{ or}$$

$$50 \times 10^{-12} = \frac{8625 \times 20 \times 10^{-15}}{\left(\frac{W}{L}\right)_n}$$

$$\therefore \left(\frac{W}{L}\right)_n = 3.5$$

Similarly, using Eqs. 14.69 and 14.71 we obtain:

$$t_{PLH} = 0.69R_p C = 0.69 \times 30 \times 10^3 \frac{C}{\left(\frac{W}{L}\right)_p}$$

or

$$\begin{aligned} t_{PLH} &= 20.7 \times 10^3 \frac{C}{\left(\frac{W}{L}\right)_p} \Rightarrow 50 \times 10^{-12} \\ &= 20.7 \times 10^3 \times \frac{20 \times 10^{-15}}{\left(\frac{W}{L}\right)_p} \Rightarrow \left(\frac{W}{L}\right)_p = 8.3 \end{aligned}$$

#### Ex: 14 . 16

$t_{PHL}$  and  $t_{PLH}$  are proportional to  $C$

$$\therefore t_{PHL} = t_{PHL} - \text{original} * \frac{C_{\text{new}}}{C_{\text{old}}}$$

and

$$t_{PHL} = t_{PLH} - \text{original} * \frac{C_{\text{new}}}{C_{\text{old}}}$$

$$C_{\text{new}} = C_{\text{old}} + .1p = 6.25f + .1p$$

$$C_{\text{new}} = .10625 \text{ pF}$$

$$t_p = \frac{1}{2}(t_{PHL} + t_{PLH}) = t_{p\text{OLD}} * \frac{C_{\text{new}}}{C_{\text{old}}}$$

$$t_p = 28p * \frac{.10625p}{6.25f} = 476 \text{ psec}$$

#### Ex: 14 . 17

$W_p$  is reduced from  $1.125 \mu\text{m}$  to  $0.375 \mu\text{m}$

$$\therefore \frac{0.375}{1.125} \times 100 = 33\% \text{ reduction}$$

$$C_{gd2} = C_{gd1} \approx 0.3375 \text{ fF}$$

$$C_{g3} = C_{g4} \approx 0.7875 \text{ fF}$$

$$\begin{aligned} C &= (4 \times 0.3375f) + 1f + 1f + (2 \times .7875f) + .2f \\ &\approx 4.225 \text{ fF} \end{aligned}$$

$$t_{PHL} = 24.6 \times 10^{-12} \times \left(\frac{4.225f}{6.25f}\right) = 16.6 \text{ psec}$$

$$t_{PLH} = 31.5 \times 10^{-12} \times \left(\frac{4.225f}{6.25f}\right) = 21.3 \text{ psec}$$

$$t_p = \frac{1}{2}(t_{PHL} + t_{PLH}) = \frac{1}{2}(16.6p + 21.3p) = 19 \text{ psec}$$

#### Ex: 14 . 18

$$f_{\text{max}} = \frac{1}{2t_p} = \frac{1}{2(28 \times 10^{-12})} = 17.9 \text{ GHz}$$

The minimum period at which the inverter can reliably operate is

$$T_{\min} = t_{PHL} + t_{PLH}. \text{ Thus,}$$

$$\begin{aligned} F_{\text{max}} &= \frac{1}{T_{\min}} = \frac{1}{t_{PHL} + t_{PLH}} = \frac{1}{2t_p} = \frac{1}{2 \times 28} \\ &\approx 17.96 \text{ Hz} \end{aligned}$$

#### Ex: 14 . 19

a) As mentioned on page of the Text,  $C_{\text{int}}$  is the contribution of intrinsic capacitances of  $Q_N$  and  $Q_P$ . Therefore,

$$C_{\text{int}} = 2C_{gd2} + 2C_{gd2} + C_{db} + C_{db2}$$

$$\therefore C_{\text{int}} = 2 \times 0.1125 + 2 \times 0.3375 + 1 + 1 = 2.9 \text{ fF}$$

$$C_{\text{ext}} = C_{g3} + C_{g4} + C_w = 0.7875 + 2.3625 + 0.2$$

$$= 3.35 \text{ fF}$$

b) From Eq. 14 . 79 we have:

$$t_p = 0.69 \left( R_{eq} C_{at} + \frac{1}{S} R_{eq} C_{ext} \right)$$

The extrinsic

part of  $t_p$  is:  $0.69 \frac{1}{S} R_{eq} C_{ext}$  and in order to reduce

the extrinsic part by a factor of 2, S has to be

increased by a factor of 2. Note that  $S = \frac{R_{eq}}{R_{eq}}$ .

Therefore,  $R_{eq}$  has to be reduced by a factor of 2

or equivalently  $\left(\frac{W}{L}\right)_n$  and  $\left(\frac{W}{L}\right)_p$  have to be

increased by factor of 2.

c) From Eq. 14 . 79

$$= 0.69 \left( R_{eq0} C_{int0} + \frac{1}{S} R_{eq0} C_{ext} \right)$$

Hence,

$$\frac{t_{p\text{new}}}{t_{p\text{old}}} = \frac{C_{\text{int}} + C_{at}/S}{C_{\text{int}} + C_{\text{ext}}}$$

$$\text{For } S = 2: t_{p\text{new}} = \frac{2.9 + 3.35/2}{2.9 + 3.35} \times 28 \text{ ps}$$

$$= 20.5 \text{ ps}$$

d)  $A = W \times L$  and since  $\left(\frac{W}{L}\right)$  is doubled and L is constant, then A or area is also doubled.

#### Ex: 14 . 20

Using Eq. 14 . 35

$$P_{dm} = fCV_{DD}^2 = 1 \times 10^9 \times 6.25 \times 10^{-15} \times 2.5^2$$

$$= 39.1 \mu\text{W}$$

The maximum possible operating frequency is:

$$f_{\text{max}} = \frac{1}{2t_p} \text{ Hence,}$$

$$PDP = P_{dm} \times t_p = f_{\text{max}} CV_{DD}^2 \times t_p$$

$$= \frac{1}{2t_p} \times C \times V_{DD}^2 \times t_p = \frac{CV_{DD}^2}{2}$$

$$= \frac{6.25 \times 10^{-15} \times 2.5^2}{2} = 19.5 \text{ fF/J}$$

**Ex: 14.21**

a) For NMOS devices:

$$\frac{W}{L} = n = \frac{0.18}{0.18} \times 1.5 = \frac{0.27}{0.18}$$

For PMOS devices:

$$\frac{W}{L} = 4p = \frac{0.18}{0.18} \times 4 \times 3 = \frac{2.16}{0.18}$$

b) For NMOS devices:

$$\frac{W}{L} = 4n = \frac{0.18}{0.18} \times 4 \times 1.5 = \frac{1.08}{0.18}$$

For PMOS devices:

$$\frac{W}{L} = p = \frac{0.18}{0.18} \times 3 = \frac{0.54}{0.18}$$

**Ex: 14.22**

(a) The minimum current available to charge a load capacitance is that provided by a single PMOS device. The maximum current available to charge a load capacitance is that provided by four PMOS transistors. Thus, the ratio is 4.

(b) There is only one possible configuration (or path) for capacitor discharge. Thus the minimum and maximum currents are the same

⇒ ratio is 1.

**Ex: 14.23**

Since dynamic power dissipation is scaled by  $\frac{1}{S^2}$

and propagation delay is scaled by  $\frac{1}{S}$ , hence, PDP

is scaled by  $\frac{1}{S^2} \times \frac{1}{S} = \frac{1}{S^3} = \frac{1}{8}$  So PDP

decreases by a factor of 8.

**Ex: 14.24**

If  $V_{DD}$  and  $V_t$  are kept constant, the entries in Table 14-2 that change are as follows:

Obviously,  $V_{DD}$  and  $V_t$  do not scale by  $\frac{1}{S}$  anymore. They are kept constant!

$t_p \propto \frac{\alpha C}{k' V_{DD}}$  since  $\alpha \propto \frac{V_t}{V_{DD}}$ , thus  $\alpha$  remains

unchanged, while  $C$  is scaled by  $\frac{1}{S}$ , and  $K'$  is

scaled by  $S$ , therefore  $t_p$  is scaled by  $\frac{1/S}{S} = \frac{1}{S^2}$

Energy/Switching cycle, i.e.,  $CV^2_{DD}$ , is scaled by

$\frac{1}{S}$

$P_{dyn} \propto \frac{CV^2_{DD}}{2t_p}$  and thus is scaled by  $\frac{1/S}{1/S^2} = S$

thus  $P_{dyn}$  increases.

The power density, i.e.,  $\frac{P_{dyn}}{\text{device area}}$  is scaled

$$\text{by } \frac{S}{1/S^2} = S^3$$

**Ex: 14.25**

Using Eq. 14.94 we have:

$$\begin{aligned} V_{DSat} &= \frac{L}{\mu_n} V_{in} = \frac{0.25 \times 10^{-6}}{400 \times 10^{-4}} \times 10^7 \times 10^{-2} \\ &= 0.63 \text{ V} \end{aligned}$$

**Ex: 14.26**

For the NMOS transistor,  $V_{GS} = 1.2 \text{ V}$  results

in  $V_{GS} - V_m = 1.2 - 0.4 = 0.8 \text{ V}$  which is greater than  $V_{DSat} = 0.34 \text{ V}$ . Also,

$V_{DS} = 1.2 \text{ V}$  is greater than  $V_{DSat}$  thus both conditions in

Eq. 14.101 are satisfied and the NMOS transistor will be operating in the velocity-saturation region and thus  $i_D$  is given by Eq. 14.100

$$i_D = 430 \times 10^{-6} \times 1.5 \times 0.34 \left( 1.2 - 0.4 - \frac{1}{2} \times 0.34 \right)$$

$$(1 + 0.1 \times 1.2) = 154.7 \mu\text{A}$$

if velocity-saturation-were absent, the current would be:

$$\begin{aligned} i_D &= \frac{1}{2} \times 430 \times 10^{-6} \times 1.5 (1.2 - 0.4)^2 \\ &\times (1 + 0.1 \times 1.2) = 231.2 \mu\text{A} \end{aligned}$$

Saturation is obtained over the range

$V_{DS} = 0.34 \text{ V}$  to  $1.2 \text{ V}$  compared to

$V_{DS} = V_{ov} = (1.2 - 0.4) = 0.8 \text{ V}$  to  $1.2 \text{ V}$

in the absence of velocity saturation.

For the PMOS transistor, we see that since

$|V_{GS}| - |V_{tp}| = 0.8 \text{ V}$  and  $|V_{DS}| = 1.2 \text{ V}$  are both larger than  $|V_{DSat}| = 0.6 \text{ V}$  the device will be operating in velocity saturation and

$$i_D = 110 \times 10^{-6} \times 1.5 \times 0.6 \left( 1.2 - 0.4 - \frac{1}{2} \times 0.6 \right)$$

$$(1 + 0.1 \times 1.2) = 55.4 \mu\text{A}$$

$0.6 \leq V_{DS} \leq 1.2 \text{ V}$

without velocity saturation

$$\begin{aligned} i_D &= \frac{1}{2} \times 110 \times 1.5 \times 0.6 (1.2 - 0.4)^2 (1 + 0.1 \times 1.2) \\ &= 59.1 \mu\text{A} \end{aligned}$$

$V_{ov} \leq V_{DS} \leq 1.2 \text{ V}$  or  $0.8 \text{ V} \leq V_{DS} \leq 1.2 \text{ V}$

Note that the velocity saturation reduces the NMOS current by 33% and the PMOS current by ~7%.

**Ex: 14 . 27**

a) Using Eq. 14 . 102 we have

$$i_D = I_{se} V_{GS} / nV_T$$

$$\text{Thus, } \log i_D = \log I_s + \frac{V_{GS}}{nV_T} \log(e)$$

Therefore, the slope of the straight line representing subthreshold conduction is given by:

$$\frac{nV_T}{\log(e)} = 2.3nV_T$$

$$\text{b) } V_T = 25 \text{ mV for } i_D = 100 \text{ nA}$$

$$\text{at } V_{GS} = .21 \text{ V}$$

$$100 \text{ nA} = I_s e^{21/(1.22(25))}$$

$$I_s = .1 \text{ nA}$$

$$i_D = .1 nA e^{\frac{-0.21}{0.1 \times 25}} = .1 \text{ nA}$$

$$\text{c) For } V_{GS} = 0, i_D = .1 \text{ nA}$$

$$I_{total} = 500 \times 10^6 \times .1 \times 10^{-9} = 50 \text{ mA}$$

$$P_{diss} = I_{total} \times V_{DD} = 50 \text{ mA} \times 1.2 = 60 \text{ mW}$$

**15.1**

$$(W/L)_n = 1.5 \quad (W/L)_p = 0.32$$

$$t_{PLH} = 0.5 \text{ ns}$$

$$t_{PLH} = 0.03 \text{ ns}$$

THE NOISE MARGINS WILL NOT CHANGE

**15.2**

Using eq. 15.11

$$V_{OL} = (V_{DD} - V_t) \left[ 1 - \sqrt{1 - \frac{1}{\gamma}} \right] = (2.5 - 0.5) \times \left[ 1 - \sqrt{1 - \frac{1}{4}} \right]$$

$$V_{OL} = 0.27 \text{ V}$$

using eq. 15.13 and 15.14

$$NM_L = V_t - (V_{DD} - V_t) \left[ 1 - \sqrt{1 - \frac{1}{\gamma} - \frac{1}{\sqrt{\gamma(\gamma + 1)}}} \right]$$

$$NM_L = 0.5 - (2) \left[ 1 - \sqrt{1 - \frac{1}{4} - \frac{1}{\sqrt{4(5)}}} \right] = 0.7 \text{ V}$$

$$NM_H = (V_{DD} - V_t) \left( 1 - \frac{2}{\sqrt{3}\gamma} \right) = (2) \times$$

$$\left( 1 - \frac{2}{\sqrt{3.4}} \right) = 0.85 \text{ V}$$

$$\gamma = \frac{\mu_n C_{ox} \left( \frac{W}{L} \right)_n}{\mu_p C_{ox} \left( \frac{W}{L} \right)_p} = \frac{115 \mu \left( \frac{0.375}{0.25} \right)}{30 \mu \left( \frac{W}{L} \right)_p} = 4$$

$$\therefore \left( \frac{W}{L} \right)_p = 1.44$$

using eq. 15.12

$$I_{stat} = \frac{1}{2} (30 \mu) (1.44) (2.5 - 0.5)^2 = 86.4 \mu\text{A}$$

$$P_D = I_{stat} V_{DD} = 86.4 \mu \cdot 2.5 = 0.22 \text{ mW}$$

using eq 15.15 and 15.16

$$\alpha_p = 2 / \left[ \frac{7}{4} - 3 \left( \frac{0.5}{2.5} \right) + \left( \frac{0.5}{2.5} \right)^2 \right] = 1.68$$

$$t_{PLH} = \frac{1.68 \times 7 \times 10^{-15}}{30 \times 10^{-6} \times 1.44 \times 2.5} = 0.11 \text{ nsec}$$

using eq. 15.17 and 15.18

$$\alpha_n = 2 / \left[ 1 + \frac{3}{4} \left( 1 - \frac{1}{\gamma} \right) - \left( 3 - \frac{1}{\gamma} \right) \left( \frac{0.5}{2.5} \right) + \left( \frac{0.5}{2.5} \right)^2 \right] = 1.9$$

$$t_{PHL} = \frac{1.9 \times 7 \times 10^{-15}}{115 \times 10^{-6} \times \left( \frac{0.375}{0.25} \right) \times 2.5} = 0.03 \text{ nsec}$$

$$t_p = \frac{1}{2} (t_{PHL} + t_{PLH}) = \frac{1}{2} (0.11 + 0.03) = 0.07 \text{ nsec}$$

**15.3**

$$V_t = V_m + \gamma (\sqrt{V_{OH} + 2\phi_f} - \sqrt{2\phi_f})$$

$$\text{since } V_{OH} = V_{DD} - V_t,$$

$$V_t = V_m + \gamma (\sqrt{V_{DD} - V_t + 2\phi_f} - \sqrt{2\phi_f})$$

Substituting values, we get

$$V_t = 0.5 + 0.3 V^{1/2}$$

$$(\sqrt{1.8 \text{ V} - V_t + 0.85 \text{ V}} - \sqrt{0.85 \text{ V}})$$

$$V_t = 0.5 + 0.3 V^{1/2}$$

$$\sqrt{2.65 \text{ V} - V_t} = 0.3 V^{1/2} \sqrt{0.85 \text{ V}}$$

$$V_t = 0.223 = 0.3 \sqrt{2.65 - V_t}$$

Squaring both sides yields

$$V_t^2 - 0.446 V_t + 0.05 = 0.09 (2.65 - V_t)$$

$$\text{so that, } V_t^2 - 0.356 V_t - 0.189 = 0$$

Solving this quadratic equation, yields one practical value for  $V_t$ :

$$V_t = 0.648 \text{ V}$$

$$V_{OH} = V_{DD} - V_t = 1.8 \text{ V} - 0.648 \text{ V}$$

$$= 1.15 \text{ V}$$

**15.4**

(a) Referring to Fig 15.12 without loading,

$$V_{OH} \rightarrow 5 \text{ V}$$

$$V_{OL} \rightarrow 0 \text{ V}$$

(b) Referring to Fig. 15.12(a),

$$i_{DN}(o) = \frac{1}{2} k_n \left( \frac{W}{L} \right)_n (V_{DD} - V_m)^2$$

$$= \frac{1}{2} (50 \mu\text{A/V}^2) \left( \frac{4 \mu\text{m}}{2 \mu\text{m}} \right) (5 \text{ V} - 1 \text{ V})^2 = 800 \mu\text{A}$$

$$i_{DP}(o) = \frac{1}{2} k_p \left( \frac{W}{L} \right)_p (V_{DD} - V_m)^2$$

$$= \frac{1}{2} (20 \mu\text{A/V}^2) \left( \frac{4}{2} \right) (5 \text{ V} - 1 \text{ V})^2 = 320 \mu\text{A}$$

Capacitor current is

$$i_C(o) = i_{DN}(o) + i_{DP}(o) = 800 \mu\text{A} + 320 \mu\text{A}$$

$$= 1120 \mu\text{A}$$

To obtain  $i_{DN}(t_{PLH})$ , we note that this situation is identical to that in Example 15.2 and we can use the result of part (c):

$$i_{DN}(t_{PLH}) = 50 \mu\text{A}$$

$$i_{DP}(t_{PLH}) = k_p \left( \frac{W}{L} \right)_p \times \gamma$$

$$\left[ (V_{DD} - V_m) \frac{V_{DD}}{2} - \frac{1}{2} \left( \frac{V_{DD}}{2} \right)^2 \right]$$

$$= (20 \mu\text{A/V}^2) \left(\frac{4}{2}\right) \left[ (5 \text{ V} - 1 \text{ V}) \left(\frac{5 \text{ V}}{2}\right) - \frac{1}{2} \left(\frac{5 \text{ V}}{2}\right)^2 \right]$$

$$= 275 \mu\text{A}$$

$$\text{Thus, } i_c(t_{PLH}) = 50 \mu\text{A} + 275 \mu\text{A} = 325 \mu\text{A}$$

$$i_C|_{av} = \frac{1}{2}(1120 \mu\text{A} + 325 \mu\text{A}) = 722.5 \mu\text{A}$$

$$t_{PLH} = \frac{C \left(\frac{V_{DD}}{2}\right)}{i_C|_{av}} = \frac{70(10^{-15})F \left(\frac{5 \text{ V}}{2}\right)}{722.5(10^{-6})\text{A}}$$

$$= 0.24 \text{ ns}$$

(c) Referring to Fig.15.12(b),

$$i_{DN}(0) = \frac{1}{2}k_n \left(\frac{W}{L}\right)_n (V_{DD} - V_{to})^2$$

$$= \frac{1}{2}(50 \mu\text{A/V}^2) \left(\frac{4}{2}\right) (5 \text{ V} - 1 \text{ V})^2 = 800 \mu\text{A}$$

$$i_{DP}(0) = \frac{1}{2}k_p \left(\frac{W}{L}\right)_p (V_{DD} - V_{to})^2$$

$$= \frac{1}{2}(20 \mu\text{A/V}^2) \left(\frac{4}{2}\right) (5 \text{ V} - 1 \text{ V})^2 = 320 \mu\text{A}$$

$$i_C(0) = i_{DN}(0) + i_{DP}(0) = 800 \mu\text{A} + 320 \mu\text{A} = 1120 \mu\text{A}$$

$$i_{DD}(t_{PHL}) = k_n \left(\frac{W}{L}\right)_n \times$$

$$\left[ (V_{DD} - V_{to}) \frac{V_{DD}}{2} - \frac{1}{2} \left(\frac{V_{DD}}{2}\right)^2 \right]$$

$$= 50 \mu\text{A/V}^2 \left(\frac{4}{2}\right) \left[ (5 \text{ V} - 1 \text{ V}) \left(\frac{5 \text{ V}}{2}\right) - \frac{1}{2} \left(\frac{5 \text{ V}}{2}\right)^2 \right]$$

$$= 688 \mu\text{A}$$

To find  $i_{DP}(t_{PHL})$ , we first determine  $V_{tp}$  when

$$v_o = \frac{V_{DD}}{2} \text{ which corresponds to } V_{sG} = \frac{V_{DD}}{2}$$

$$|V_{tp}| = V_{to} + \gamma \left[ \sqrt{\frac{V_{DD}}{2} + 2\phi_f} - \sqrt{2\phi_f} \right]$$

$$= 1 \text{ V} + 0.5 \text{ V}^{1/2} \left[ \sqrt{\frac{5 \text{ V}}{2} + 0.6 \text{ V}} - \sqrt{0.6 \text{ V}} \right] = 1.49 \text{ V}$$

$$\text{Thus, } i_{DP}(t_{PHL}) = \frac{1}{2}k_p \left(\frac{W}{L}\right)_p \left[ \frac{V_{DD}}{2} - |V_{tp}| \right]^2$$

$$= \frac{1}{2}(20 \mu\text{A/V}^2) \left(\frac{4}{2}\right) \left[ \frac{5 \text{ V}}{2} - 1.49 \text{ V} \right]^2 = 20 \mu\text{A}$$

$$i_C(t_{PHL}) = i_{DN}(t_{PHL}) + i_{DP}(t_{PHL})$$

$$= 688 \mu\text{A} + 20 \mu\text{A} = 708 \mu\text{A}$$

$$i_C|_{av} = \frac{1120 \mu\text{A} + 708 \mu\text{A}}{2} = 914 \mu\text{A}$$

So,

$$t_{PHL} = \frac{C \left(\frac{V_{DD}}{2}\right)}{i_C|_{av}} = \frac{70(10^{-15})F \left(\frac{5 \text{ V}}{2}\right)}{914(10^{-6})\text{A}} = 0.19 \text{ ns}$$

$Q_p$  will turn off when  $V_o = |V_{tp}|$

where

$$|V_{tp}| = V_{to} + \gamma [\sqrt{V_{DD}} - |V_{tp}| + 2\phi_f] - \sqrt{2\phi_f}$$

Solving for  $|V_{tp}|$ ,

$$|V_{tp}| = 1 \text{ V} + 0.5 \text{ V}^{1/2}$$

$$[\sqrt{5 \text{ V}} - |V_{tp}| + 0.6 \text{ V} = \sqrt{0.6 \text{ V}}]$$

$$|V_{tp}| = 0.613 \text{ V} = 0.5 \text{ V}^{1/2} \sqrt{5.6 \text{ V}} - |V_{tp}|$$

squaring both sides and setting one side equal to zero, we have the quadratic equation,

$$|V_{tp}|^2 - 0.976|V_{tp}| - 1.024 \text{ V}^2 = 0$$

solving, we get  $|V_{tp}| = 1.6 \text{ V}$

(d)

$$t_p = \frac{1}{2}(t_{PLH} + t_{PHL}) = \frac{1}{2}(0.24 \text{ ns} + 0.19 \text{ ns})$$

$$\approx 0.22 \text{ ns}$$

### 15.5

$$R_{TG_{AV}} = \frac{R_{TG1} + R_{TG2}}{2} = \frac{4.5 \text{ k}\Omega + 6.5 \text{ k}\Omega}{2}$$

$$= 5.5 \text{ k}\Omega$$

$$t_{PLH} = 0.69RC = 0.69(5.5 \text{ k}\Omega)(70)(10^{-15})F$$

$t_{PLH} = 0.27 \text{ ns}$  which is close to the value of 0.24ns obtained in Exercise 15.14

### 15.6

$$\left(\frac{W}{L}\right)_n = \left(\frac{W}{L}\right)_p = 1.5$$

Using Eq. 15.36

$$R_{TG} = \frac{12.5}{(W/L)_n} = \frac{12.5}{1.5} = 8.3 \text{ k}\Omega$$

### 15.7

Using Eq.14.71

$$R_{P1} = \frac{30}{\left(\frac{W}{L}\right)_p} \text{ k}\Omega = \frac{30}{(2)} \text{ k}\Omega = 15 \text{ k}\Omega$$

with Eq. 15.36 we see that


$$R_{TG} = \frac{12.5}{\left(\frac{W}{L}\right)_n} \text{ k}\Omega = \frac{12.5}{(1)} \text{ k}\Omega = 12.5 \text{ k}\Omega$$

Using Eq.15.38

$$t_p = 0.69[(C_{out1} + C_{TG1})R_1 + (C_{in2} + C_{TG2}) \\ \times (R_1 + R_2)] \\ = 0.69[(10fF + 5fF)(15k\Omega) + (10fF + 5fF) \\ \times (15k\Omega + 12.5k\Omega)]$$

$$t_p = 0.64 \text{ ns}$$

15.8

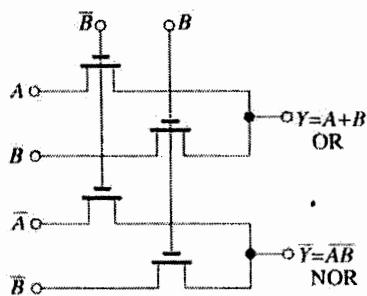

$$= \frac{1}{2} \times 50 \times 1(5 - 1)^2$$

$$= 400 \mu\text{A}$$

$$i_{D1}(v_{y1} = V_t) = k_n \left(\frac{W}{L}\right)_{eq1} \left[ (V_{DD} - V_t)V_t - \frac{1}{2}v_t^2 \right]$$

$$= 50 \times 1 \left[ (5 - 1)1 - \frac{1}{2} \times 1 \right]$$

$$= 175 \mu\text{A}$$

$$i_{D1}|_{av} = \frac{400 + 175}{2} = 288 \mu\text{A}$$

$$(c) i_{D1}|_{av} \Delta t = C_{L1} \Delta v_{y1}$$

$$\Delta t = \frac{C_{L1}(V_{DD} - V_t)}{i_{D1}|_{av}} = \frac{40 \times 10^{-15} \times 4}{288 \times 10^{-6}}$$

$$= 0.56 \text{ ns}$$

(d) Following the hint we assume that  $Q_{eq}$  remains saturated during  $\Delta t$ .

$$i_{D2}|_{av} = i_{D2}(v_{y1} = 3\text{V}) = \frac{1}{2}k_n \left(\frac{W}{L}\right)_{eq2} (3 - 1)^2$$

$$i_{D2}|_{av} = \frac{1}{2} \times 50 \times 1(3 - 1)^2$$

$$= 100 \mu\text{A}$$

$$(e) \Delta v_{y2} = -\frac{i_{D2}|_{av} \cdot \Delta t}{C_{L2}}$$

$$= -\frac{100 \times 10^{-6} \times 0.56 \times 10^{-9}}{40 \times 10^{-15}}$$

$$= -1.4 \text{ V}$$

Thus,  $v_{y2}$  decrease to 3.6 V.

15.11

$$V_{OH} = 0$$

$$V_{OL} = -0.88 \text{ V}$$

SHOULD BE SHIFTED BY  $\sim 0.88 \text{ V}$

$$V_{OH} = -0.88 \text{ V AFTER SHIFTING}$$

$$V_{OL} = -1.76 \text{ V AFTER SHIFTING}$$

15.12

Refer to Fig. 15.12 Neglecting the base current of  $Q_1$ , the current through  $R_1$ ,  $D_1$ ,  $D_2$  and  $R_2$  is

$$I = \frac{5.2 - V_{D1} - V_{D2}}{R_1 + R_2}$$

$$= \frac{5.2 - 0.75 - 0.75}{0.907 + 4.98} = 0.6285 \text{ mA}$$

$$\text{Thus, } V_B = -I_{R1} = -0.57 \text{ V}$$

$$V_R = V_B - V_{RE1} = -0.57 - 0.75 = -1.32 \text{ V}$$

15.10

$$\text{Since } i_D(V_{DD}) = \frac{1}{2}(\mu_n C_{ov}) \left(\frac{W}{L}\right)_{eq} (V_{DD} - V_t)^2.$$

$$\text{doubling } \left(\frac{W}{L}\right) \text{ will double } \left(\frac{W}{L}\right)_{eq} \text{ and } i_D(V_{DD})$$

$$\text{so } i_D(V_{DD}) = 2(76.1 \mu\text{A}) = 152.2 \mu\text{A}$$

$$\text{This new } \left(\frac{W}{L}\right)_{eq} \text{ will also double } i_D \left(\frac{V_{DD}}{2}\right) :$$

$$i_D \left(\frac{V_{DD}}{2}\right) = 2(68.9 \mu\text{A}) = 137.8 \mu\text{A}$$

$$\text{This doubles } I_{av} \text{ to } 2(72.5 \mu\text{A}) = 145 \mu\text{A}$$

$$\text{the new } t_{PHL} \text{ is}$$

$$t_{PHL} = \frac{C \left(V_{DD} - \frac{V_{DD}}{2}\right)}{I_{av}}$$

$$= \frac{30(10^{-15})F(1.8\text{V} - 0.9\text{V})}{145(10^{-6})\text{A}} = 0.19 \text{ ns}$$

15.10

Refer to Fig. E15.10

$$(a) \left(\frac{W}{L}\right)_{eq1} = \frac{1}{2} \left(\frac{W}{L}\right) = \frac{1}{2} \times \frac{4}{2} = 1$$

$$\left(\frac{W}{L}\right)_{eq2} = \frac{1}{2} \left(\frac{W}{L}\right) = \frac{1}{2} \times \frac{4}{2} = 1$$

$$(b) i_{D1}(v_{r1} = V_{DD}) = \frac{1}{2}k_n \left(\frac{W}{L}\right)_{eq1} (V_{DD} - V_t)^2$$

### 15.13

Refer to Fig. 15.26

$$I_E = \frac{V_R - V_{BE}|_{QR} - (-V_{EE})}{R_E}$$

$$= \frac{-1.32 - 0.75 + 5.2}{0.779} \approx 4 \text{ mA}$$

$$V_C|_{QR} = -\gamma \times 4 \times R_{C2} \approx -4 \times 0.245 = -1 \text{ V}$$

$V_C|_{Q_A Q_B} = 0 \text{ V}$  (because the current through  $R_{C1}$  is zero)

### 15.14

Refer to Fig. 15.28

For  $V_I = V_{IH}$ ,  $I_{QR} = 99 I_{QA}$ ,

$$I_E = \frac{-1.32 - V_{BE}|_{QR} + 5.2}{0.779}$$

Assume  $V_{BE}|_{QR} = 0.75 \text{ V}$ ,  $I_E = 4.018 \text{ mA}$

$$I_{QR} = 0.99 \times 4.018 = 3.98 \text{ mA}$$

Thus a better estimate of  $V_{BE}|_{QR}$  is

$$V_{BE}|_{QR} = 0.75 + 0.025 \ln\left(\frac{3.98}{1}\right)$$

$$= 0.785 \text{ V}$$

and correspondingly,

$$I_E = \frac{-1.32 - 0.785 + 5.2}{0.779} = 3.97 \text{ mA}$$

For  $V_I = -1.32 \text{ V}$ ,  $I_{QR} = I_{QA} = I_E/2$ ,

$$I_E = \frac{-1.32 - 0.75 + 5.2}{0.779} = 4.018 \text{ mA}$$

Thus a better estimate for  $V_{BE}|_{QR}$  is

$$V_{BE}|_{QR} = 0.75 + 0.025 \ln\left(\frac{2.009}{1}\right)$$

$$= 0.767 \text{ V}$$

and correspondingly,

$$I_E = 4.00 \text{ mA}$$

For  $V_I = V_{IH} = -1.205 \text{ V}$ ,

$$I_{QA} = 99 I_{QR}$$

$$I_E = \frac{-1.205 - 0.75 + 5.2}{0.779} = 4.166 \text{ mA}$$

Thus a better estimate for  $V_{BE}|_{QA}$  is

$$V_{BE}|_{QA} = 0.75 + 0.025 \ln\left(\frac{0.99 \times 4.166}{1}\right)$$

$$= 0.788 \text{ V}$$

and correspondingly

$$I_E = \frac{-1.205 - 0.788 + 5.2}{0.779} = 4.12 \text{ mA}$$

At  $V_I = V_R$ ,  $I_{QR} = \frac{1}{2} I_E = 2 \text{ mA}$

Thus,  $V_C|_{QR} = -2 \times 0.245 = -0.49 \text{ V}$

$$v_{OR} = -0.49 - 0.75 = -1.24 \text{ V}$$

$$I_E|_{Q2} = \frac{-1.24 + 2}{0.05} = 15.2 \text{ mA}$$

A better estimate for  $V_{BE}|_{Q2}$  is

$$V_{BE}|_{Q2} = 0.75 + 0.025 \ln\left(\frac{15.2}{1}\right)$$

$$= 0.818 \text{ V}$$

Thus a better estimate for  $v_{OR}$  is

$$v_{OR} = -0.49 - 0.818 = -1.31 \text{ V}$$

### 15.15

REFER TO FIG. 15.32 for

$$V_I = V_{IH} = -1.205$$

The value of  $I_E$  we found in Exercise 15.14 to be

4.12 mA. The  $V_C|_{QR} \approx -0.22 \times 4.12$

$$= -0.906 \text{ V}$$

$$v_{NOR} \approx -0.906 - 0.75 = -1.656 \text{ V}$$

$$I|_{Q3} = \frac{-1.656 + 2}{0.05} = 6.88 \text{ mA}$$

A better estimate for  $V_{BE}|_{Q3}$  is

$$V_{BE}|_{Q3} = 0.75 + 0.025 \ln\left(\frac{6.88}{1}\right)$$

$$= 0.798 \text{ V}$$

and correspondingly

$$V_{NOR} = -0.906 - 0.798 = -1.704 \text{ V}$$

(b) For  $v_I = V_{OH} = -0.88 \text{ V}$ ,

$$I_E \approx \frac{-0.88 - 0.75 + 5.2}{0.779} = 4.58 \text{ mA}$$

A better estimate for  $V_{BE}|_{QA}$  is

$$V_{BE}|_{QA} = 0.75 + 0.025 \ln\left(\frac{4.58}{1}\right) = 0.788 \text{ V}$$

$$\text{Thus, } I_E = \frac{-0.88 - 0.788 + 5.2}{0.779} = 4.53 \text{ mA}$$

$$V_C|_{QA} = -0.22 \times 4.53 = -1 \text{ V}$$

$$V_{NOR} = -1 - 0.75 = -1.75 \text{ V}$$

$$I|_{RT} = \frac{-1.75 + 2}{0.05} = 5 \text{ mA}$$

$$V_{BE}|_{Q3} = 0.75 + 0.025 \ln\left(\frac{5}{1}\right)$$

$$= 0.79 \text{ V}$$

$$V_{NOR} = -1 - 0.79 = -1.79 \text{ V}$$

(c) The input resistance into the base of  $Q_3$  is

$$(\beta + 1)[r_{e3} + R_T]$$

$$= 101 \left[ \frac{25}{5} + 50 \right] = 5.55 \text{ k}\Omega$$


$$\frac{V_C|_{Q_A}}{V_i} = \frac{-(5.55 \text{ k}\Omega \parallel 0.22 \text{ k}\Omega)}{r_e|_{Q_A} + R_E}$$

$$= \frac{-5.55 \parallel 0.22}{\left(\frac{25}{4.53} + 771\right) \times 10^{-3}} = -0.269$$

$$\frac{v_{NOR}}{v_C|_{Q_A}} = \frac{50 \text{ }\Omega}{50 \text{ }\Omega + 5 \text{ }\Omega} = 0.909$$

$$\text{Thus, } \frac{v_{NOR}}{v_C|_{Q_A}} = -0.269 \times 0.909 = -0.24 \text{ V/V}$$

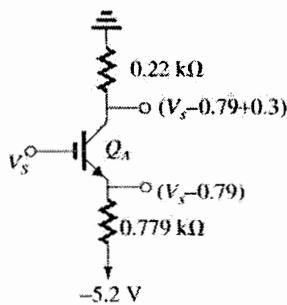d) See figure below. Assume  $V_{BE} \approx 0.79 \text{ V}$



(because the current will be 4 to 5 mA). At the range of saturation,

$$I_C = \alpha I_E = 0.99 I_E$$

$$\text{Thus, } \frac{0 - V_s + 0.79 - 0.3}{0.22} = 0.99 \times$$

$$\frac{V_i - 0.79 + 5.2}{0.779}$$

$$\Rightarrow V_s = -0.58 \text{ V}$$

### 15.16

Refer to Fig. 15.26 For the reference circuit, the current through  $R_1$ ,  $D_1$ ,  $D_2$ , and  $R_2$

$$\text{is } \frac{5.2 - 2 \times 0.75}{4.98 + 0.907} = 0.629 \text{ mA}$$

$$V_{B|Q_1} = -0.57 \text{ V}$$

$$V_R = -0.57 - 0.75 = -1.32 \text{ V}$$

$$I_{E|Q_1} = \frac{-1.32 + 5.2}{6.1} = 0.636 \text{ mA}$$

Thus the reference circuit draws a current of  $(0.629 + 0.636) = 1.265 \text{ mA}$  from the  $5.2 \text{ V}$  supply. It follows that the power dissipated in the reference circuit is  $1.265 \times 5.2 = 6.6 \text{ mW}$ . Since the reference circuit supplies four gates, the dissipation attributed to a gate is  $\frac{6.6}{4} = 1.65 \text{ mW}$

In addition, the gate draws a current

$I_E \approx 4 \text{ mA}$  from the  $5.2 \text{ V}$  supply. Thus the total power dissipation / gate is

$$P_D = 4 \times 5.2 + 1.65 = 22.4 \text{ mW}$$

### Ex 16.1

Refer to Fig. 16.5(a)

when  $v_{\phi} = v_s = \frac{V_{DD}}{2}$  then  $Q_{eq}$  will be

saturated  $v_{\bar{Q}} = \frac{V_{DD}}{2}$  and  $Q_2$  will be in triode

$$Q_{eq} \left( \frac{W}{L} \right) = \frac{1}{2} \left( \frac{W}{L} \right)_{s,6}$$

$$\frac{1}{2} k'_n \left( \frac{W}{L} \right)_{eq} \left( \frac{V_{DD}}{2} - V_t \right)^2 = \frac{1}{2} k_p \left( \frac{W}{L} \right)_2$$

$$\left[ (V_{DD} - V_t) \frac{V_{DD}}{2} - \frac{1}{2} \left( \frac{V_{DD}}{2} \right)^2 \right]$$

From Example 16.1

$$k'_n = 4k'_p = 300 \mu A/V^2$$

$$|V_t| = 0.5; V_{DD} = 1.8$$

$$\begin{aligned} \frac{1}{2} (300 \times 10^{-6}) \left( \frac{1}{2} \right) \left( \frac{W}{L} \right)_s \left( \frac{1.8}{2} - 0.5 \right)^2 \\ = \frac{1}{2} \left( \frac{300 \mu}{4} \right) \left( \frac{1.08}{0.18} \right) \left[ (1.8 - 0.5) \left( \frac{1.8}{2} \right) - \frac{1}{2} (0.9)^2 \right] \end{aligned}$$

$$(12 \times 10^{-6}) \left( \frac{W}{L} \right)_s = 172 \times 10^{-6}$$

$$\left( \frac{W}{L} \right)_s = 14.3 \approx \frac{2.6 \mu m}{0.18 \mu m}$$

### Ex 16.2

Bits for row address:

$$2^M = 1,024$$

$$\log_2(2^M) = \log_2(1,024)$$

$$\mu * \log_2(2) = \log_2(1,024)$$

$$\mu = \frac{\log_2(1,024)}{\log_2(2)} = 10$$

Bits for column address:

$$2^N = 128$$

$$N = \frac{\log_2(128)}{\log_2(2)} = 7$$

Bits for block address:


$$2^{B_{BS}} = 32$$

$$\text{Bits} = \frac{\log_2(32)}{\log_2(2)} = 5$$
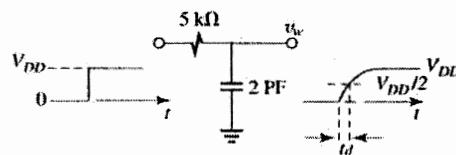
### Ex 16.3

$$v_w = V_{DD}(1 - e^{-t/C_R})$$

$$\frac{V_{DD}}{2} = V_{DD}(1 - e^{t_d/C_R})$$



$$t_d = CR \ln 2$$

$$\approx 2 \times 10^{-12} \times 5 \times 10^3 \times 0.69 \\ \approx 6.9 \text{ ns}$$

### Ex 16.4

$$\left. \left( \frac{W}{L} \right)_a \right|_{max} = \frac{1}{\left( 1 - \frac{V_m}{V_{DD} - V_m} \right)^2} - 1$$

$$\left. \left( \frac{W}{L} \right)_a \right|_{max} = 1.5 \times \left[ \frac{1}{\left( 1 - \frac{0.5}{1.8 - 0.5} \right)^2} - 1 \right] = 2.5$$

$$\Rightarrow \left( \frac{W}{L} \right)_a \leq 2.5$$

### Ex 16.5

$$\Delta t = \frac{C_B \times \Delta V}{I_5}; \text{ To find } I_5, \text{ we use}$$

$$I_5 = \frac{1}{2} (\mu_n C_{ov}) \left( \frac{W}{L} \right) (V_{DD} - V_m - V_{\bar{Q}})^2$$

$$(a) \left( \frac{W}{L} \right)_a = 2.5$$

$$\begin{aligned} I_5 &= \frac{1}{2} \times 300 \times 10^{-6} \times 2.5 \times (1.8 - 0.5 - 0.5)^2 \\ &= 240 \mu A \end{aligned}$$

$$\Delta t = \frac{2 \times 10^{-12} \times 0.2}{240 \mu A} = 1.7 \text{ ns}$$

$$(b) \left( \frac{W}{L} \right)_a = 1.5$$

$$\begin{aligned} I_5 &= \frac{1}{2} \times 300 \times 10^{-6} \times 1.5 \times (1.8 - 0.5 - 0.5)^2 \\ &= 144 \mu A \end{aligned}$$

$$\Delta t = \frac{2 \times 10^{-12} \times 0.2}{144 \mu A} = 2.8 \text{ ns}$$

$$\text{or: } \Delta t \propto \frac{1}{I_5} \propto \frac{1}{\left( \frac{W}{L} \right)_a}$$

$$\Delta t = 1.7 \text{ ns} \times \frac{2.5}{1.5} = 2.8 \text{ ns}$$

**Ex 16 . 6**

$$\left(\frac{W}{L}\right)_p \leq \left(\frac{W}{L}\right)_a \times \frac{\mu_n}{\mu_p} \left[ 1 - \left( 1 - \frac{V_{in}}{V_{DD} - V_{in}} \right)^2 \right]$$

$$\left(\frac{W}{L}\right)_p \leq \left(\frac{W}{L}\right)_a \times 4 \times \left[ 1 - \left( 1 - \frac{0.5}{1.8 - 0.5} \right)^2 \right]$$

$$\left(\frac{W}{L}\right)_p \leq 2.5 \left(\frac{W}{L}\right)_a \text{ or}$$

$$\left(\frac{W}{L}\right)_p \leq 2.5 \times 2.5 \Rightarrow \left(\frac{W}{L}\right)_p \leq 6.25$$

For minimum area: select

$$W_a = W_p = W_u = 0.18 \mu\text{m}$$

**Ex 16 . 7**

From Eqs.16.14 and 16.15 we have:

$$\Delta V_{(1)} \approx$$

$$\frac{C_s}{C_B} \times \frac{V_{DD}}{2} = \frac{30 \times 10^{-15}}{0.3 \times 10^{-12}} \times \frac{1.2}{2} = 6.0 \text{ mV}$$

$$\Delta V_{(0)} \approx$$

$$-\frac{C_s}{C_B} \times \frac{V_{DD}}{2} = -\frac{-30 \times 10^{-15}}{0.3 \times 10^{-12}} \times \frac{1.2}{2} = -0.06 \text{ V}$$

$$= -60 \text{ mV}$$

**Ex 16 . 8**

Area of the storage array

$$= 64 \times 1024 \times 1024 \times 2 = 134217728 \mu\text{m}^2$$

= 134.2 mm<sup>2</sup> or equivalently

$$= 11.6 \text{ mm} \times 11.6 \text{ mm}$$

Total chip area

$$= 1.3 \times 134.2 = 174.46 \text{ mm}^2 = 13.2 \times 13.2 \text{ mm}^2$$

**Ex 16 . 9**

Refer to Example 16 . 2

Since  $\Delta t$  is proportional to  $\tau = \frac{C}{G_m}$ , we can

reduce  $\Delta t$  by a factor of 2 by decreasing  $\tau$  by the

$$\text{same factor. } \Delta t \propto \tau \propto \frac{1}{G_m}$$

Hence,  $G_m$  has to be doubled.  $G_m = g_{mn} + g_{mb}$  and both  $g_{mn}$  and  $g_{mb}$  have to be increased by a factor of 2. The increase in  $g_m$  can be achieved by

increasing the corresponding  $\frac{W}{L}$ , thus:

$$\left(\frac{W}{L}\right)_p = 2 \times \frac{0.54}{0.18} = 6$$

$$\left(\frac{W}{L}\right)_p = 2 \times \frac{2.16}{0.18} = 24$$

**Ex 16 . 11**

$$\text{From Eq.16.18 } \Delta t = \frac{CV_{DD}}{I} \text{ or}$$

$$I = \frac{CV_{DD}}{\Delta t} = \frac{50 \text{ pF} \times 1.8}{0.5 \text{ ns}} = 180 \mu\text{A}$$

$$P = V_{DD}I = 1.8 \times 180 \mu\text{A} = 324 \mu\text{W}$$

**Ex 16 . 12**

Refer to Fig. 13.26

Our decoder is an extension of that show:

We have M bits is the address (as opposed to 3) and correspondingly there will be  $2^M$  word lines. Now, each of the  $2^M$  word lines is connected to M NMOS devices and to one PMOS transistor. Thus the total number of devices required is

$$M2^M (\text{NMOS}) + 2^M (\text{PMOS})$$

$$= 2^M (M + 1)$$

**Ex 16 . 13**

Refer to Fig.13.28 Our tree decoder will have  $2^N$  bit lines. Thus it will have N levels: At the first levels there will be 2 transistors, at the second  $2^2$ , ..., at the Nth level there will be  $2^N$  transistors. Thus the total number of transistors, can be find as

$$\text{Number} = 2 + 2^2 + 2^3 + \dots + 2^N$$

$$= 2 \underbrace{(1 + 2 + 2^2 + \dots + 2^{N-1})}_{\text{Geometric series r=2}}$$

$$\text{Sum} = \frac{r^N - 1}{r - 1} = \frac{2^N - 1}{2 - 1}$$

Thus,

$$\text{Number} = 2(2^N - 1)$$

**Ex 16 . 14**



$$f = \frac{1}{2 \times 5t_p}$$

$$= \frac{1}{2 \times 5 \times 10^{-9}} = 100 \text{ MHz}$$


**Ex 16.15**

$$\begin{aligned} \text{(a)} I_{av} &= k'_p \left( \frac{W}{L} \right)_p \left[ (5 - 1)2.5 - \frac{1}{2} 2.5^2 \right] \\ &= 20 \times \frac{24}{2} [10 - 3.125] \\ &= 1.65 \text{ mA} \end{aligned}$$

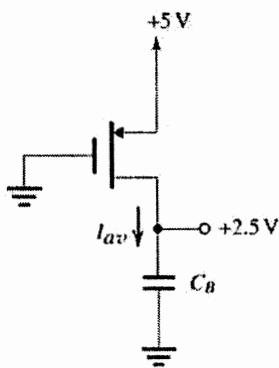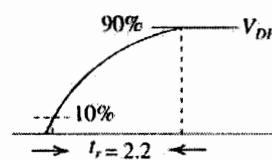(c) In one time-constant the voltage reached is



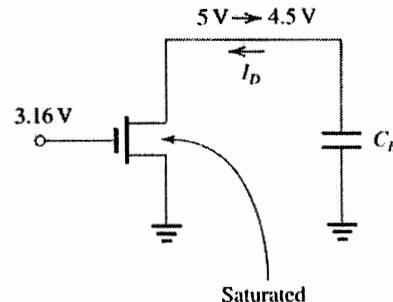
$$\begin{aligned} V_{D0}(1 - e^{-1}) &= 0.632 V_{D0} \\ &= 3.16 \text{ V} \end{aligned}$$



$$\text{Thus, } t_{\text{Charging}} = \frac{2 \times 10^{-12} \times 2}{1.65 \times 10^{-3}} = 6.1 \text{ ns}$$

(b)

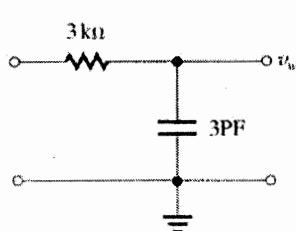

$$\begin{aligned} I_D &= \frac{1}{2} k'_n \left( \frac{W}{L} \right)_n (3.16 - 1)^2 \\ &= \frac{1}{2} \times 50 \times \frac{6}{2} \times 2.16^2 \\ &= 0.35 \text{ mA} \\ \Delta t &= \frac{C_B \Delta V}{I_D} \\ &= \frac{2 \times 10^{-12} \times 0.5}{0.35 \times 10^{-3}} = 2.9 \text{ ns} \end{aligned}$$

$$t_r \approx 2.25$$

$$\begin{aligned} &\approx 2.2 \times 3 \times 10^{-12} \times 3 \times 10^3 \\ &\approx 19.8 \text{ ns} \end{aligned}$$

### 1.1

- $I = \frac{V}{R} = \frac{10 \text{ V}}{1 \text{ k}\Omega} = 10 \text{ mA}$
- $R = \frac{V}{I} = \frac{10 \text{ V}}{1 \text{ mA}} = 10 \text{ k}\Omega$
- $V = IR = 10 \text{ mA} \times 10 \text{ k}\Omega = 100 \text{ V}$
- $I = \frac{V}{R} = \frac{10 \text{ V}}{100 \text{ }\Omega} = 0.1 \text{ A}$

Note: Volts, millamps, and kilo-ohms constitute a consistent set of units.

### 1.2

- $V = IR = 10 \text{ mA} \times 1 \text{ k}\Omega = 10 \text{ V}$
- $P = I^2 R = (10 \text{ mA})^2 \times 1 \text{ k}\Omega = 100 \text{ mW}$
- $R = V/I = 10 \text{ V}/1 \text{ mA} = 10 \text{ k}\Omega$
- $P = VI = 10 \text{ V} \times 1 \text{ mA} = 10 \text{ mW}$
- $(c) I = P/V = 1 \text{ W}/10 \text{ V} = 0.1 \text{ A}$
- $R = V/I = 10 \text{ V}/0.1 \text{ A} = 100 \Omega$
- $(d) V = P/I = 0.1 \text{ W}/10 \text{ mA}$   
 $= 100 \text{ mW}/10 \text{ mA} = 10 \text{ V}$

$$R = V/I = 10 \text{ V}/10 \text{ mA} = 1 \text{ k}\Omega$$

$$(e) P = I^2 R \Rightarrow I = \sqrt{P/R}$$

$$I = \sqrt{1000 \text{ mW}/1 \text{ k}\Omega} = 31.6 \text{ mA}$$

$$V = IR = 31.6 \text{ mA} \times 1 \text{ k}\Omega = 31.6 \text{ V}$$

Note: V, mA, kΩ, and mW constitute a consistent set of units.

### 1.3

Thus, there are 17 possible resistance values.

### 1.4

Shunting the  $10 \text{ k}\Omega$  by a resistor of value of  $R$  result in the combination having a resistance  $R_{eq}$ .

$$R_{eq} = \frac{10R}{R+10}$$

Thus, for a 1% reduction,

$$\frac{R}{R+10} = 0.99 \Rightarrow R = 990 \text{ k}\Omega$$

For a 5% reduction,

$$\frac{R}{R+10} = 0.95 \Rightarrow R = 190 \text{ k}\Omega$$

For a 10% reduction,

$$\frac{R}{R+10} = 0.90 \Rightarrow R = 90 \text{ k}\Omega$$

For a 50% reduction,

$$\frac{R}{R+10} = 0.50 \Rightarrow R = 10 \text{ k}\Omega$$

Shunting the  $10 \text{ k}\Omega$  by

(a)  $1 \text{ M}\Omega$  result in

$$R_{eq} = \frac{10 \times 1000}{1000 + 10} = \frac{10}{1.01} = 9.9 \text{ k}\Omega$$

a 1% reduction;

(b)  $100 \text{ k}\Omega$  results in

$$R_{eq} = \frac{10 \times 100}{100 + 10} = \frac{10}{1.1} = 9.09 \text{ k}\Omega$$

a 9.1% reduction;

(c)  $10 \text{ k}\Omega$  results in

$$R_{eq} = \frac{10}{10 + 10} = 5 \text{ k}\Omega$$

a 50% reduction.

### 1.5

$$V_O = V_{DD} \frac{R_2}{R_1 + R_2}$$

To find  $R_O$ , we short circuit  $V_{DD}$  and look back into node X.

$$1.6 \quad R_O = R_2 \parallel R_1 = \frac{R_1 R_2}{R_1 + R_2}$$

Use voltage divider to find  $V_o$

$$V_o = 9 \frac{3.3}{3.3 + 6.8} = 2.94 \text{ V}$$


Equivalent output resistance  $R_O$  is


$$R_O = (3.3 \text{ k}\Omega \parallel 6.8 \text{ k}\Omega) = 2.22 \text{ k}\Omega$$

The extreme values of  $V_o$  for  $\pm 5\%$  tolerance resistor are

$$V_{O-\text{min}} = 9 \frac{3.3(1 - 0.05)}{3.3(1 - 0.05) + 6.8(1 + 0.05)} = 2.75 \text{ V}$$

This figure is for 1.3

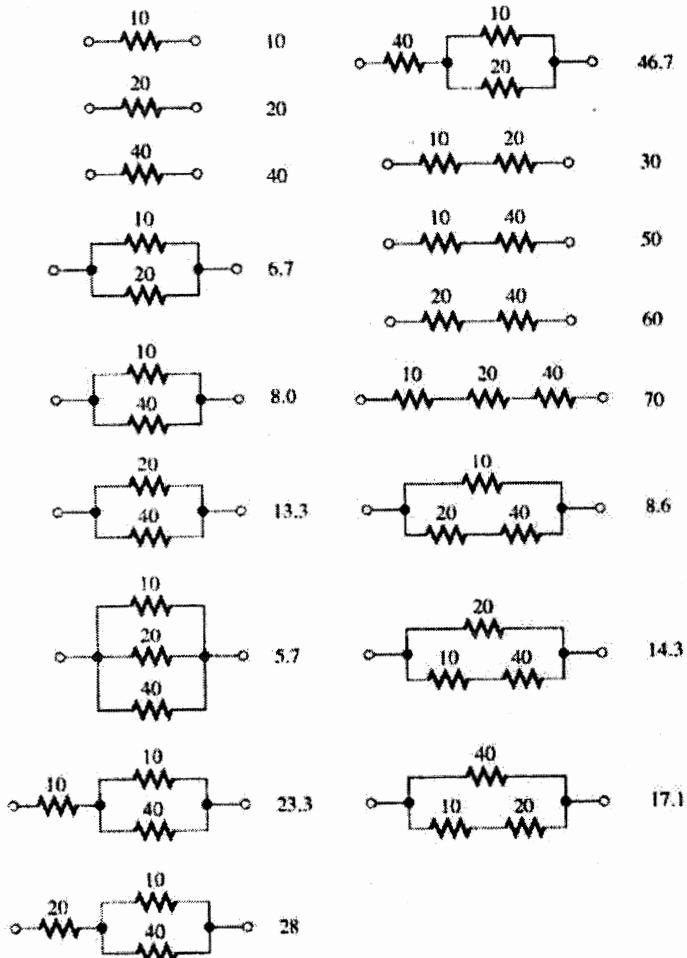

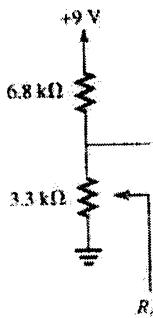

$$V_{O_{\text{max}}} = 9 \frac{3.3(1 + 0.05)}{3.3(1 + 0.05) + 6.8(1 - 0.05)} = 3.14 \text{ V}$$


The extreme values of  $R_O$  for  $\pm 5\%$  tolerance resistors are

$$R_{O_{\text{min}}} = \frac{3.3(1 - 0.05) \times 6.8(1 - 0.05)}{3.3(1 - 0.05) + 6.8(1 - 0.05)} = 2.11 \text{ k}\Omega$$

$$R_{O_{\text{max}}} = \frac{3.3(1 + 0.05) \times 6.8(1 + 0.05)}{3.3(1 + 0.05) + 6.8(1 + 0.05)} = 2.33 \text{ k}\Omega$$

- Voltage generated**
- +3V (two ways: (a) and (c) with (c) having lower output resistance)
  - +4.5V (b)
  - +6V (two ways: (a) and (d) with (d) having a lower output resistance)

1.8

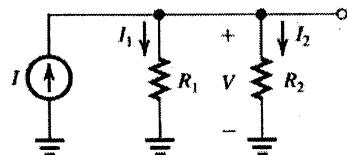


$$V = I(R_1 \parallel R_2)$$

$$= I \frac{R_1 R_2}{R_1 + R_2}$$


$$I_1 = \frac{V}{R_1} = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = \frac{V}{R_2} = I \frac{R_1}{R_1 + R_2}$$


1.7

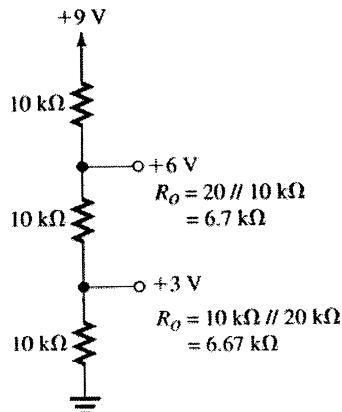


(a)

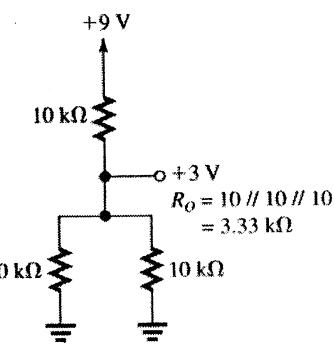

(c)

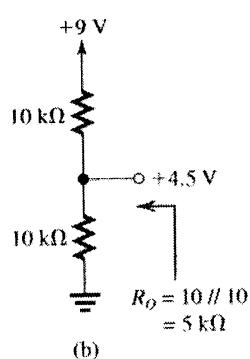

(b)

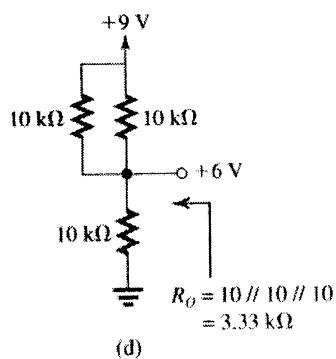


(d)

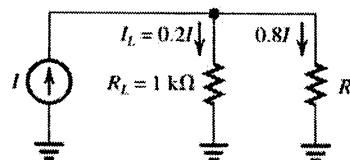1.9





Connect a resistor  $R$  in parallel with  $R_L$ .

To make  $I_L = 0.2I$  (and thus the current through  $R$ ,  $0.8I$ ),  $R$  should be such  
 $0.2I \times 1\text{ k}\Omega = 0.8IR$   
 $\Rightarrow R = 250\text{ k}\Omega$



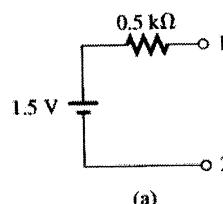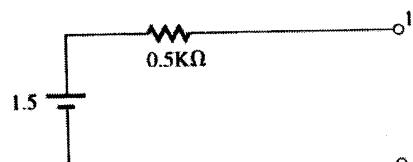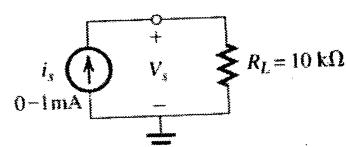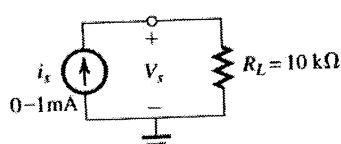1.10


For  $R_L = 10\text{ k}\Omega$ , when signal source generates 0–1 mA, a voltage of 0–10 V may appear across the source



$$V_{TH} = 3 \left( \frac{1\text{ k}}{1\text{ k} + 1\text{ k}} \right) = 1.5\text{ V}$$

$$R_{TH} = 1\text{ k} \parallel 1\text{ k} = 0.5\text{ k}$$

Same procedure is used for b) & c)

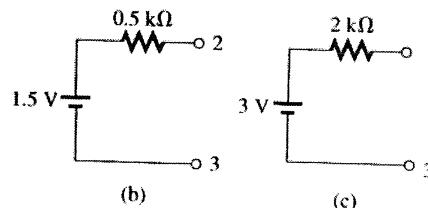

1.11

To limit  $V_S \leq 1\text{ V}$ , the net resistance has to be  $\leq 1\text{ k}\Omega$ . To achieve this we have to shunt  $R_L$  with a resistor  $R$  so that  $(R \parallel R_L) \leq 1\text{ k}\Omega$ .

$$R \parallel R_L \leq 1\text{ k}\Omega.$$




$$\frac{RR_L}{R + R_L} \leq 1\text{ k}\Omega$$

For  $R_L = 10\text{ k}\Omega$

$$R \approx 1.11\text{ k}\Omega$$


The resulting circuit needs only one additional resistance of  $1.11\text{ k}\Omega$  in parallel with  $R_L$  so that  $V_S \leq 1\text{ V}$

1.11

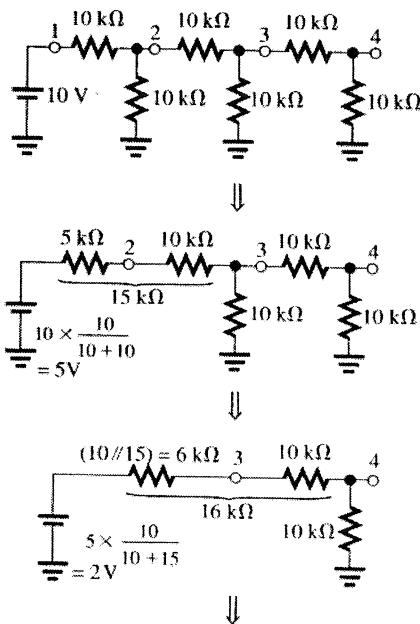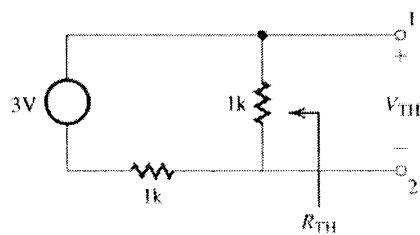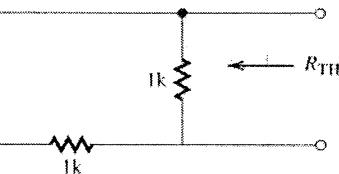

Thévenin equivalent:  $(10//16) = 6.15\text{ k}\Omega$
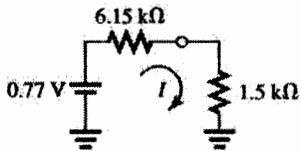
$$2 \times \frac{10}{10 + 16} = 0.77\text{ V}$$



Now, when a resistance of  $1.5 \text{ k}\Omega$  is connected between 4 and ground,


$$I = \frac{0.77}{6.15 + 1.5} = 0.1 \text{ mA}$$

(a) Node equation at the common mode yields

$$I_3 = I_1 + I_2$$

Using the fact that the sum of the voltage drops across  $R_1$  and  $R_3$  equals 15 V, we write
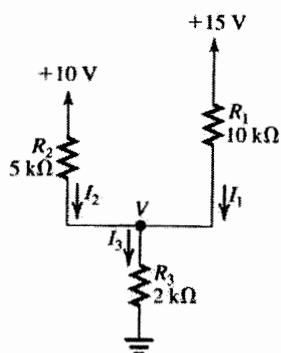
$$\begin{aligned} 15 &= I_1 R_1 + I_3 R_3 \\ &= 10I_1 + (I_1 + I_2) \times 2 \\ &= 12I_1 + 2I_2 \end{aligned}$$



That is,

$$12I_1 + 2I_2 = 15 \quad (1)$$

Similarly, the voltage drops across  $R_2$  and  $R_3$  add up to 10 V, thus

$$\begin{aligned} 10 &= I_2 R_2 + I_3 R_3 \\ &= 5I_2 + (I_1 + I_2) \times 2 \end{aligned}$$

which yields

$$2I_1 + 7I_2 = 10 \quad (2)$$

Equations (1) and (2) can be solved together by multiplying (2) by 6,

$$12I_1 + 42I_2 = 60 \quad (3)$$

Now, subtracting (1) from (3) yields

$$40I_2 = 45$$

$$\Rightarrow I_2 = 1.125 \text{ mA}$$

Substituting in (2) gives

$$2I_1 = 10 - 7 \times 1.125 \text{ mA}$$

$$\Rightarrow I_1 = 1.0625 \text{ mA}$$

$$I_3 = I_1 + I_2$$

$$= 1.0625 + 1.1250$$

$$= 1.1875 \text{ mA}$$

$$V = I_3 R_3$$

$$= 1.1875 \times 2 = 2.3750 \text{ V}$$

To summarize:

$$I_1 \approx 1.06 \text{ mA} \quad I_2 \approx 1.13 \text{ mA}$$

$$I_3 \approx 1.19 \text{ mA} \quad V \approx 2.38 \text{ V}$$

(b) A node equation at the common node can be written in terms of  $V$  as

$$\frac{15 - V}{R_1} + \frac{10 - V}{R_2} = \frac{V}{R_3}$$

Thus,

$$\frac{15 - V}{10} + \frac{10 - V}{5} = \frac{V}{2}$$

$$\Rightarrow 0.8 \text{ V} = 3.5$$

$$\Rightarrow V = 2.375 \text{ V}$$

Now,  $I_1$ ,  $I_2$ , and  $I_3$  can be easily found as

$$I_1 = \frac{15 - V}{10} = \frac{15 - 2.375}{10}$$

$$= 1.0625 \text{ mA} \approx 1.06 \text{ mA}$$

$$I_2 = \frac{10 - V}{5} = \frac{10 - 2.375}{5}$$

$$= 1.125 \text{ mA} \approx 1.13 \text{ mA}$$


$$I_3 = \frac{V}{R_3} = \frac{2.375}{2} = 1.1875 \text{ mA} \approx 1.19 \text{ mA}$$

Method (b) is much preferred; faster, more insightful and less prone to errors. In general, one attempts to identify the least possible number of variables and write the corresponding minimum number of equations.
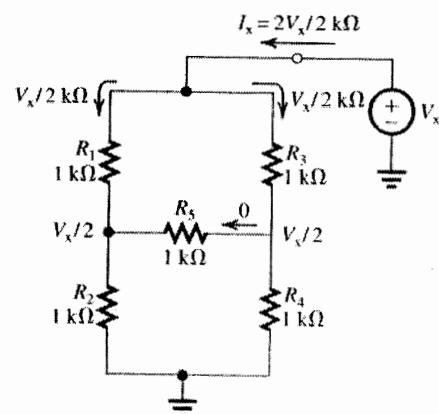
### 1.13

From the symmetry of the circuit, there will be no current in  $R_5$ . (Otherwise the symmetry would be violated.) Thus each branch will carry a current  $V_x/2 \text{ k}\Omega$  and  $I_x$  will be the sum of the two currents,

$$I_x = \frac{2V_x}{2 \text{ k}\Omega} = \frac{V_x}{1 \text{ k}\Omega}$$



### 1.14




Thus,

$$R_{eq} = \frac{V_x}{I_x} = 1 \text{ k}\Omega$$

Now, if  $R_4$  is raised to  $1.2 \text{ k}\Omega$  the symmetry will be broken. To find  $I_x$  we use Thévenin's theorem as follows:

$$I_x = \frac{0.545V_x - 0.5V_x}{0.5 + 1 + 0.545} = 0.022V_x$$
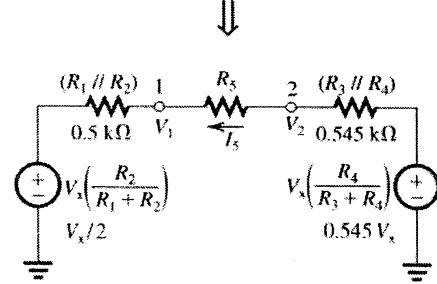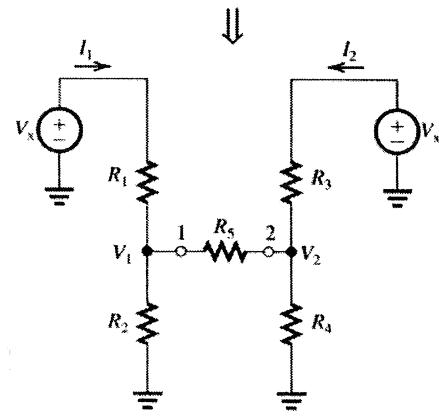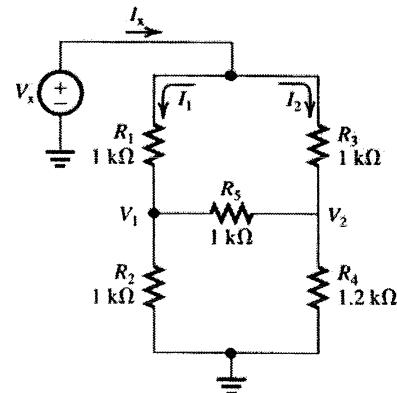
$$V_1 = \frac{V_x}{2} + 0.022V_x \times 0.5$$



$$= 0.5V_x \times 1.022 = 0.511V_x$$

$$V_2 = V_1 + I_5 R_5 = 0.533V_x$$

$$I_1 = \frac{V_x - V_2}{1 \text{ k}\Omega} = 0.489V_x$$

$$I_2 = \frac{V_x - V_2}{1 \text{ k}\Omega} = 0.467V_x$$

$$I_x = I_1 + I_2 = 0.956V_x$$

$$\Rightarrow R_{eq} = \frac{V_x}{I_x} = 1.05 \text{ k}\Omega$$

(a)  $Z = 1 \text{ k}\Omega$  at all frequencies

(b)  $Z = 1/j\omega C = -j\frac{1}{2\pi f \times 10 \times 10^{-9}}$

At  $f = 60 \text{ Hz}$ ,  $Z = -j265 \text{ k}\Omega$

At  $f = 100 \text{ kHz}$ ,  $Z = -j159 \text{ }\Omega$

At  $f = 1 \text{ GHz}$ ,  $Z = -j0.016 \text{ }\Omega$

(c)  $Z = 1/j\omega C = -j\frac{1}{2\pi f \times 2 \times 10^{-12}}$

At  $f = 60 \text{ Hz}$ ,  $Z = -j1.33 \text{ G}\Omega$

At  $f = 100 \text{ kHz}$ ,  $Z = -j0.8 \text{ M}\Omega$

At  $f = 1 \text{ GHz}$ ,  $Z = -j79.6 \text{ }\Omega$

(d)  $Z = j\omega L = j2\pi fL = j2\pi f \times 10 \times 10^{-3}$

At  $f = 60 \text{ Hz}$ ,  $Z = j3.77 \text{ }\Omega$

At  $f = 100 \text{ kHz}$ ,  $Z = j6.28 \text{ k}\Omega$

At  $f = 1 \text{ GHz}$ ,  $Z = j62.8 \text{ }\Omega$

(e)  $Z = j\omega L = j2\pi fL = j2\pi f(1 \times 10^{-9})$

$f = 60 \text{ Hz}$ ,  $Z = j3.77 \times 10^{-7} = j0.377 \mu\Omega$

$f = 100 \text{ kHz}$ ,

$Z = j6.28 \times 10^{-4} = j0.628 \text{ m}\Omega$

$f = 16 \text{ Hz}$ ,  $Z = j62.8 \text{ }\Omega$

### 1.15

(a)  $Z = R + \frac{1}{j\omega C}$

$$= 10^3 + \frac{1}{j2\pi \times 10 \times 10^3 \times 10 \times 10^{-9}} \\ = (1 - j1.59) \text{ k}\Omega$$

(b)  $Y = \frac{1}{R} + j\omega C$

$$= \frac{1}{10^3} + j2\pi \times 10 \times 10^3 \times 0.01 \times 10^{-6} \\ = 10^{-3}(1 + j0.628) \text{ }\Omega$$

$Z = \frac{1}{Y} = \frac{1000}{1 + j0.628}$

$$= \frac{1000(1 - j0.628)}{1 + 0.628^2}$$

= (717.2 - j45.04) \text{ }\Omega

(c)  $Y = \frac{1}{R} + j\omega C$

$$= \frac{1}{100 \times 10^3} + j2\pi \times 10 \times 10^3 \times 100 \times 10^{-12} \\ = 10^{-5}(1 + j0.628)$$

$Z = \frac{10^5}{1 + j0.628}$

= (71.72 - j450.4) \text{ k}\Omega


(d)  $Z = R + j\omega L$

$$= 100 + j2\pi \times 10 \times 10^3 \times 10 \times 10^{-3}$$

= 100 + j6.28 \times 100

= (100 + j628) \text{ }\Omega

1.16

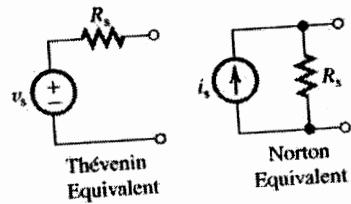

$$v_{OC} = v_s$$

$$i_{SC} = i_s$$

$$v_s = i_s R_s$$

Thus,

$$R_s = \frac{v_{OC}}{i_{SC}}$$

$$(a) v_s = v_{OC} = 10 \text{ V}$$

$$i_s = i_{SC} = 100 \mu\text{A}$$


$$R_s = \frac{v_{OC}}{i_{SC}} = \frac{10 \text{ V}}{100 \mu\text{A}} = 0.1 \text{ M}\Omega = 100 \text{ k}\Omega$$

$$(b) v_s = v_{OC} = 0.1 \text{ V}$$

$$i_s = i_{SC} = 10 \mu\text{A}$$

$$R_s = \frac{v_{OC}}{i_{SC}} = \frac{0.1 \text{ V}}{10 \mu\text{A}} = 0.01 \text{ M}\Omega = 10 \text{ k}\Omega$$

1.17

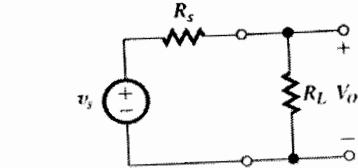

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_s}$$

$$v_o = v_s / \left( 1 + \frac{R_s}{R_L} \right)$$

Thus,

$$\frac{v_s}{1 + \frac{R_s}{100}} = 30$$

and

$$\frac{v_s}{1 + \frac{R_s}{10}} = 10$$

Dividing (1) by (2) gives

$$\frac{1 + (R_s/10)}{1 + (R_s/100)} = 3$$

$$\Rightarrow R_s = 28.6 \text{ k}\Omega$$


Substituting in (2) gives

$$v_s = 38.6 \text{ mV}$$

The Norton current  $i_s$  can be found as

$$i_s = \frac{v_s}{R_s} = \frac{38.6 \text{ mV}}{28.6 \text{ k}\Omega} = 1.35 \mu\text{A}$$

1.18

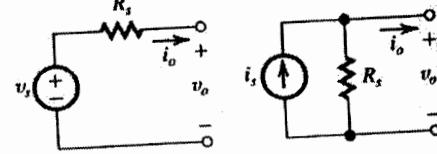


$$v_o = v_s - i_o R_s$$

$$v_o = (i_s - i_o) R_s$$

$$= i_s R_s - i_o R_s$$


$$v_o = v_s - i_o R_s$$

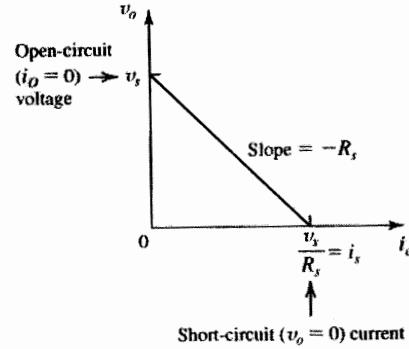

1.19

(1) 1.26

(2)

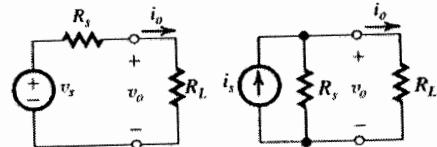

$R_L$  represents the input resistance of the processor

For  $v_o = 0.9 v_s$

$$0.9 = \frac{R_L}{R_L + R_s} \Rightarrow R_L = 9R_s$$

For  $i_o = 0.9 i_s$

$$0.9 = \frac{R_s}{R_s + R_L} \Rightarrow R_L = R_s / 9$$

1.20

Case	$\omega$ (rad/s)	$f$ (Hz)	$T$ (s)
a	$6.28 \times 10^9$	$1 \times 10^6$	$1 \times 10^{-6}$
b	$1 \times 10^9$	$1.59 \times 10^6$	$6.28 \times 10^{-9}$
c	$6.28 \times 10^{10}$	$1 \times 10^9$	$1 \times 10^{-10}$
d	$3.77 \times 10^2$	60	$1.67 \times 10^2$
e	$6.28 \times 10^3$	$1 \times 10^3$	$1 \times 10^{-3}$
f	$6.28 \times 10^6$	$1 \times 10^6$	$1 \times 10^{-6}$

**1.21**

- (a)  $V_{peak} = 117 \times \sqrt{2} = 165 \text{ V}$
- (b)  $V_{rms} = 33.9 \times \sqrt{2} = 24 \text{ V}$
- (c)  $V_{peak} = 220 \times \sqrt{2} = 311 \text{ V}$
- (d)  $V_{peak} = 220 \times \sqrt{2} = 311 \text{ kV}$

**1.22**

- (a)  $v = 10 \sin(2\pi \times 10^4 t), \text{ V}$
- (b)  $v = 120\sqrt{2} \sin(2\pi \times 60), \text{ V}$
- (c)  $v = 0.1 \sin(1000t), \text{ V}$
- (d)  $v = 0.1 \sin(2\pi \times 10^{+3}t), \text{ V}$

**1.23**

The two harmonics have the ratio

$126/98 = 9/7$ . Thus, these are the 7th and 9th harmonics. From Eq. 1.2 we note that the amplitudes of these two harmonics will have the ratio 7 to 9, which is confirmed by the measurement reported. Thus the fundamental will have a frequency of  $98/7$  or 14 kHz and peak amplitude of  $63 \times 7 = 441$  mV. The rms value of the fundamental will be  $441/\sqrt{2} = 312$  mV. To find the peak-to-peak amplitude of the square wave we note that  $4V/\pi = 441$  mV. Thus,

Peak-to-peak amplitude

$$= 2V = 441 \times \frac{\pi}{2} = 693 \text{ mV}$$


$$\text{Period } T = \frac{1}{f} = \frac{1}{14 \times 10^3} = 71.4 \mu\text{s}$$

**1.24**

To be barely audible by a relatively young listener, the 5th harmonic must be limited to 20 kHz; thus the fundamental will be 4 kHz. At the low end, hearing extends down to about 20 Hz. For the fifth and higher to be audible the fifth must be no lower than 20 Hz. Correspondingly, the fundamental will be at 4 Hz.

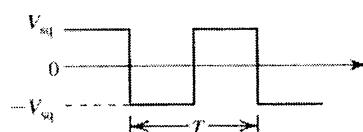**1.25**

If the amplitude of the square wave is  $V_{sq}$  then the power delivered by the square wave to a resistance  $R$  will be  $V_{sq}^2/R$ . If this power is to equal that delivered by a sine wave of peak amplitude  $\hat{V}$  then



$$\frac{V_{sq}^2}{R} = \frac{(\hat{V}/\sqrt{2})^2}{R}$$

Thus,  $V_{sq} = \hat{V}/\sqrt{2}$ . This result is independent of frequency.

**1.26**

Decimal	Binary
0	0
5	101
8	1000
25	11001
57	111001

**1.27**

$b_3$	$b_2$	$b_1$	$b_0$	Value Represented
0	0	0	0	+0
0	0	0	1	+1
0	0	1	0	+2
0	0	1	1	+3
0	1	0	0	+4
0	1	0	1	+5
0	1	1	0	+6
0	1	1	1	+7
1	0	0	0	-0
1	0	0	1	-1
1	0	1	0	-2
1	0	1	1	-3
1	1	0	0	-4
1	1	0	1	-5
1	1	1	0	-6
1	1	1	1	-7

Note that there are two possible representation of zero: 0000 and 1000. For a 0.5-V step size, analog signals in the range  $\pm 3.5 \text{ V}$  can be represented

Input	Steps	Code
+2.5 V	+5	0101
-3.0 V	-6	1110
+2.7	+5	0101
-2.8	-6	1110


## 1.28

(a) For  $N$  bits there will be  $2^N$  possible levels, from 0 to  $V_{FS}$ . Thus there will be  $(2^N - 1)$  discrete steps from 0 to  $V_{FS}$  with the step size given by

$$\text{Step size} = \frac{V_{FS}}{2^N - 1}$$

This is the analog change corresponding to a change in the LSB. It is the value of the resolution of the ADC.

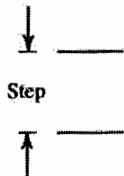(b) The maximum error in conversion occurs when the analog signal value is at the middle of a step. Thus the maximum error is



$$\frac{1}{2} \times \text{step size} = \frac{1}{2} \frac{V_{FS}}{2^N - 1}$$

This is known as the quantization error.

$$(c) \frac{10 \text{ V}}{2^N - 1} \leq 5 \text{ mV}$$

$$2^N - 1 \geq 2000$$

$$2^N \geq 2001 \Rightarrow N = 11,$$

For  $N = 11$

$$\text{Resolution} = \frac{10}{2^{11} - 1} = 4.9 \text{ mV}$$

$$\text{Quantization error} = \frac{4.9}{2} = 2.4 \text{ mV}$$

## 1.29

There will be 44,100 samples per second with each sample represented by 16 bits. Thus the through-put or speed will be  $44,100 \times 16 = 7.056 \times 10^5$  bits per second.

## 1.30

$$(a) A_v = \frac{v_o}{v_i} = \frac{10 \text{ V}}{100 \text{ mV}} = 100 \text{ V/V}$$

$$\text{or, } 20 \log 100 = 40 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o / R_L}{i_i} = \frac{10 \text{ V} / 100 \Omega}{100 \mu\text{A}} = \frac{0.1 \text{ A}}{100 \mu\text{A}}$$

$$= 1000 \text{ A/A}$$

$$\text{or, } 20 \log 1000 = 60 \text{ dB}$$

$$A_p = \frac{v_o i_o}{v_i i_i} = \frac{v_o}{v_i} \times \frac{i_o}{i_i} = 100 \times 1000$$

$$= 10^8 \text{ W/W}$$

$$\text{or, } 20 \log 10^8 = 50 \text{ dB}$$

$$(b) A_u = \frac{v_o}{v_i} = \frac{2 \text{ V}}{10 \mu\text{V}} = 2 \times 10^5 \text{ V/V}$$

$$\text{or, } 20 \log 2 \times 10^5 = 106 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o / R_L}{i_i} = \frac{2 \text{ V} / 10 \text{ k}\Omega}{100 \text{ nA}}$$

$$= \frac{0.2 \text{ mA}}{100 \text{ nA}} = \frac{0.2 \times 10^{-3}}{100 \times 10^{-9}} = 2000 \text{ A/A}$$

$$\text{or, } 20 \log A_i = 66 \text{ dB}$$

## 1.31

$$A_p = \frac{v_o i_o}{v_i i_i} = \frac{v_o}{v_i} \times \frac{i_o}{i_i}$$

$$= 2 \times 10^8 \times 2000$$

$$= 4 \times 10^8 \text{ W/W}$$

$$\text{or } 10 \log A_p = 86 \text{ dB}$$

$$(c) A_v = \frac{v_o}{v_i} = \frac{10 \text{ V}}{1 \text{ V}} = 10 \text{ V/V}$$

$$\text{or, } 20 \log 10 = 20 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o / R_L}{i_i} = \frac{10 \text{ V} / 10 \Omega}{1 \text{ mA}}$$

$$= \frac{1 \text{ A}}{1 \text{ mA}} = 1000 \text{ A/A}$$


$$\text{or, } 20 \log 1000 = 60 \text{ dB}$$

$$A_p = \frac{v_o i_o}{v_i i_i} = \frac{v_o}{v_i} \times \frac{i_o}{i_i}$$

$$= 10 \times 1000 = 10^4 \text{ W/W}$$

$$\text{or } 10 \log_{10} A_p = 40 \text{ dB}$$

## 1.32

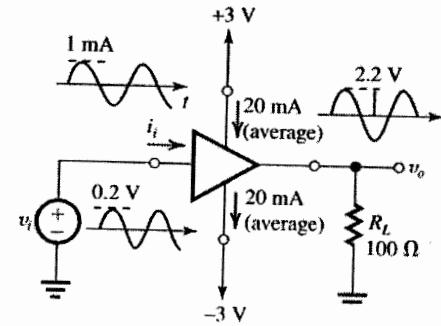

$$A_v = \frac{v_o}{v_i} = \frac{2.2}{0.2}$$

$$= 11 \text{ V/V}$$

$$\text{or } 20 \log 11 = 20.8 \text{ dB}$$

$$A_i = \frac{i_o}{i_i} = \frac{2.2 \text{ V} / 100 \Omega}{1 \text{ mA}}$$

$$= \frac{22 \text{ mA}}{1 \text{ mA}} = 22 \text{ A/A}$$

$$\text{or, } 20 \log A_i = 26.8 \text{ dB}$$

$$A_p = \frac{P_o}{P_i} = \frac{(2.2 / \sqrt{2})^2 / 100}{\frac{0.2}{\sqrt{2}} \times \frac{10^{-3}}{\sqrt{2}}}$$

$$= 242 \text{ W/W}$$

$$\text{or, } 10 \log A_p = 23.8 \text{ dB}$$

$$\text{Supply power} = 2 \times 3 \text{ V} \times 20 \text{ mA} = 120 \text{ mW}$$

$$\text{Output power} =$$

$$\frac{v_{rms}^2}{R_L} = \frac{(2.2 / \sqrt{2})^2}{100 \Omega} = 24.2 \text{ mW}$$


$$\text{Input power} = \frac{24.2}{242} = 0.1 \text{ mW} \text{ (negligible)}$$

$$\text{Amplifier dissipation} \approx \text{Supply power} - \text{Output power}$$

$$= 120 - 24.2 = 95.8 \text{ mW}$$

$$\text{Amplifier efficiency} = \frac{\text{Output power}}{\text{Supply power}} \times 100$$

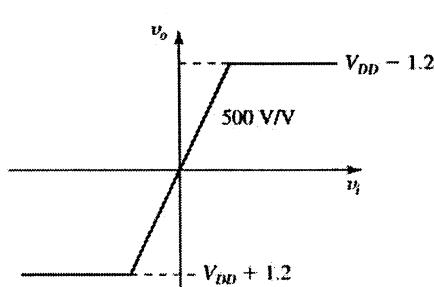
$$= \frac{24.2}{120} \times 100 = 20.2\%$$




For  $V_{DD} = 15$  V, the largest undistorted sine-wave output is of 13.8-V peak amplitude or 9.8 V<sub>peak</sub>. The input needed is 9.8 V/500 = 19.6 mV<sub>peak</sub>.

### 1.33

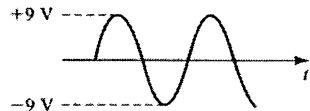(a) For an output whose extremes are just at the edge of clipping, i.e., an output of 9-V<sub>peak</sub>, the input must have  $9 \text{ V}/1000 = 9 \text{ mV}_{\text{peak}}$ .




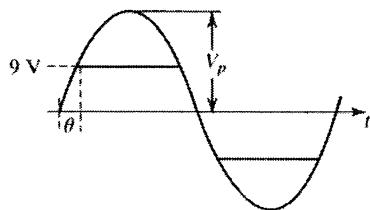(b) For an output that is clipping 90% of the time,  $\theta = 0.1 \times 90^\circ = 9^\circ$  and  $V_p \sin 9^\circ = 9^\circ = 9 \text{ V} \Rightarrow V_p = 57.5 \text{ V}$  which of course does not occur as the output saturates at  $\pm 9 \text{ V}$ . To produce this result, the input peak must be  $57.5/1000 = 57.5 \text{ mV}$ .



(c) For an output that is clipping 99% of the time,  $\theta = 0.01 \times 90^\circ = 0.9^\circ$   
 $V_p \sin 0.9^\circ = 9 \text{ V} \Rightarrow V_p = 573 \text{ V}$  and the input must be  $573 \text{ V}/1000$  or  $0.573 \text{ V}_{\text{peak}}$ .

### 1.34

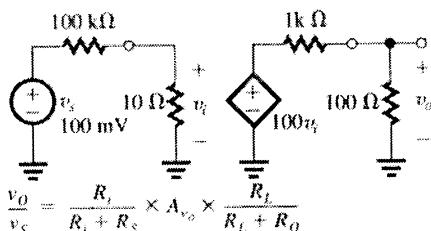

$$\frac{v_o}{v_s} = \frac{R_o}{R_i + R_s} \times A_{vo} \times \frac{R_L}{R_L + R_o}$$

$$(a) \frac{v_o}{v_s} = \frac{10R_s}{10R_s + R_s} \times A_{vo} \times \frac{10R_o}{10R_o + R_o} \\ = \frac{10}{11} \times 10 \times \frac{10}{11} = 8.26 \text{ V/V}$$

or,  $20 \log 8.26 = 18.3 \text{ dB}$

$$(b) \frac{v_o}{v_s} = \frac{R_s}{R_s + R_s} \times A_{vo} \times \frac{R_o}{R_o + R_o} \\ = 0.5 \times 10 \times 0.5 = 2.5 \text{ V/V}$$


or,  $20 \log 2.5 = 8 \text{ dB}$

(c)

$$\frac{v_o}{v_s} = \frac{R_s / 10}{(R_s / 10) + R_s} \times A_{vo} \times \frac{R_o / 10}{(R_o / 10) + R_o} \\ = \frac{1}{11} \times 10 \times \frac{1}{11} = 0.083 \text{ V/V}$$

or  $20 \log 0.083 = -21.6 \text{ dB}$

### 1.35

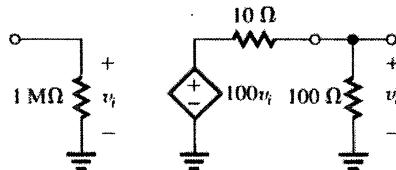

$$20 \log A_{vo} = 40 \text{ dB} \Rightarrow A_{vo} = 100 \text{ V/V}$$

$$A_v = \frac{v_o}{v_i} \\ = 100 \times \frac{100}{100 + 10} \\ = 90.9 \text{ V/V}$$

or,  $20 \log 90.9 = 39.1 \text{ dB}$


$$A_p = \frac{v_o^2 / 100 \Omega}{v_i^2 / 1 \text{ M}\Omega} = A_v^2 \times 10^4 = 8.3 \times 10^7 \text{ W/W}$$

or  $10 \log (8.3 \times 10^7) = 79.1 \text{ dB}$ .

For a peak output sine-wave current of  $100 \text{ mA}$ , the peak output voltage will be  $100 \text{ mA} \times 100 \Omega = 10 \text{ V}$ . Correspondingly  $v_o$  will be a sine wave with a peak value of  $10 \text{ V}/A_v = 10/90.9$  or an rms value of  $10/(90.9 \times \sqrt{2}) = 0.08 \text{ V}$ .


Corresponding output power =
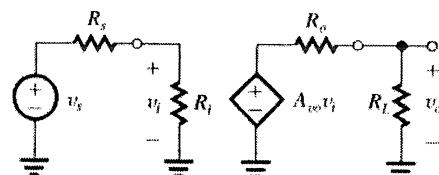
$$(10/\sqrt{2})^2 / 100 \Omega \\ = 0.5 \text{ W}$$



$$\frac{v_o}{v_s} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 100 \text{ k}\Omega} \times 1000 \times \frac{100 \Omega}{100 \Omega + 1 \text{ k}\Omega} \\ = \frac{10}{110} \times 1000 \times \frac{100}{1100} = 8.26 \text{ V/V}$$

This figure is for 1.37

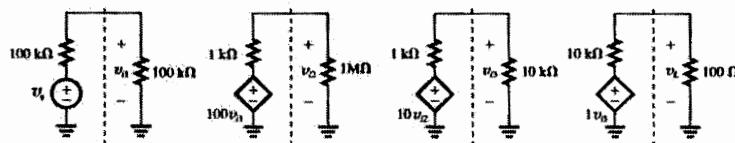


1.36

The signal loses about 90% of its strength when connected to the amplifier input (because  $R_i = R_s/10$ ). Also, the output signal of the amplifier loses approximately 90% of its strength when the load is connected (because  $R_L = R_o/10$ ). Not a good design! Nevertheless, if the source were connected directly to the load,

$$\begin{aligned} \frac{v_o}{v_s} &= \frac{R_L}{R_L + R_S} \\ &= \frac{100\text{ }\Omega}{100\text{ }\Omega + 100\text{ k}\Omega} \\ &\approx 0.001 \text{ V/V} \end{aligned}$$

$$R_S = 100\text{ k}\Omega$$

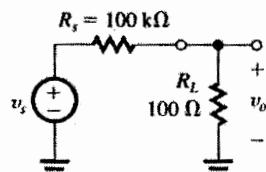

which is clearly a much worse situation. Indeed inserting the amplifier increases the gain by a factor  $8.3/0.001 = 8300$ .

1.37

In example 1.3 when the first and the second stages are interchanged, the circuit looks like the figure above

$$\frac{v_o}{v_s} = \frac{100\text{ k}\Omega}{100\text{ k}\Omega + 100\text{ k}\Omega} = 0.5 \text{ V/V}$$

$$A_{v1} = \frac{v_o}{v_{i1}} = 100 \times \frac{1\text{ M}\Omega}{1\text{ M}\Omega + 1\text{ k}\Omega} = 99.9 \text{ V/V}$$

$$A_{v2} = \frac{v_o}{v_{i2}} = 10 \times \frac{10\text{ k}\Omega}{10\text{ k}\Omega + 1\text{ k}\Omega} = 9.09 \text{ V/V}$$

$$A_{v3} = \frac{v_o}{v_{i3}} = 1 \times \frac{100\text{ }\Omega}{100\text{ }\Omega + 10\text{ }\Omega} = 0.909 \text{ V/V}$$

$$\text{Total gain } A_v = \frac{v_o}{v_{i1}} = A_{v1} \times A_{v2} \times A_{v3}$$

$$= 99.9 \times 9.09 \times 0.909 = 825.5 \text{ V/V}$$

The voltage gain from source to load is

$$\begin{aligned} \frac{v_o}{v_s} &= \frac{v_o}{v_{i1}} \times \frac{v_{i1}}{v_s} = A_v \cdot \frac{v_{i1}}{v_s} \\ &= 825.5 \times 0.5 \\ &= 412.7 \text{ V/V} \end{aligned}$$

The overall voltage has reduced appreciably. It is due to the reason because the input impedance of the first stage,  $R_{in}$ , is comparable to the source resistance  $R_s$ . In example 1.3 the input impedance of the first stage is much larger than the source resistance

1.38

a. Case S-A-B-L

$$\begin{aligned} \frac{V_o}{V_s} &= \frac{V_o}{V_{ib}} \times \frac{V_{ib}}{V_{ia}} \times \frac{V_{ia}}{V_s} = \\ &\left(1 \times \frac{100}{100+100}\right) \times \left(100 \times \frac{100}{100+10}\right) \times \left(\frac{10}{100+10}\right) \end{aligned}$$

$$\frac{V_o}{V_s} = 4.13 \text{ V/V} \text{ and gain in dB } 20 \log 4.1 =$$

12.32 dB (See figure below)


b. Case S-B-A-L

$$\begin{aligned} \frac{V_o}{V_s} &= \frac{V_o}{V_{ia}} \cdot \frac{V_{ia}}{V_{ib}} \cdot \frac{V_{ib}}{V_s} \\ &= \left(100 \times \frac{100}{100+10\text{ K}}\right) \times \left(1 \times \frac{10\text{ K}}{10\text{ K}+100}\right) \times \\ &\left(\frac{100\text{ K}}{100\text{ K}+100}\right) \end{aligned}$$


$$\frac{V_o}{V_s} = 0.49 \text{ V/S and gain in dB is } 20 \log 0.49 =$$


-6.19 dB case a is preferred as it provides higher voltage gain.

This figure is for 1.38 (a)

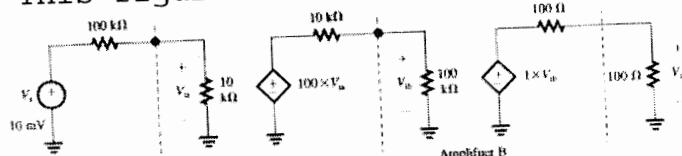

This figure is for 1.38 (b)

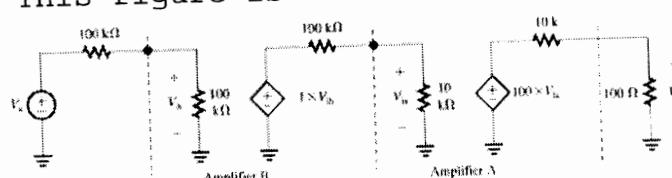

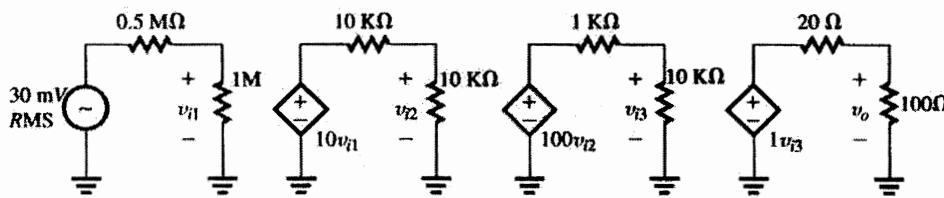


This figure is for 1.39
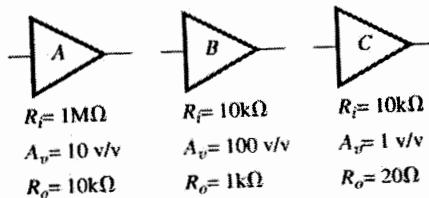
### 1.39

Deliver 0.5W to a 100Ω load

Source is 30mV RMS with 0.5MΩ source resistance. Choose from 3 amplifiers types



Choose order to eliminate loading on input and output

- A - 1st-to minimize loading on 0.5 MΩ source
  - B - 2nd-to boost gain
  - C - 3rd - to minimize loading at 100Ω output.
- (See figure below)

$$\frac{v_o}{v_s} = \frac{2 V}{30 mV} = 235.7 < \left( \frac{1 \mu}{0.5 \mu + 1 \mu} \right) (10)$$

$$\left( \frac{10}{10+10} \right) (100) \left( \frac{10}{10+1} \right) (1) \left( \frac{100}{20+100} \right)$$

$$235.7 < 253.6$$

$$v_o = (253.6)(30mV) = 7.61 \text{ V RMS}$$

$$P = \frac{v_o^2}{R_L} = \frac{(7.61)^2}{100} = 0.58 \text{ W}$$

### 1.40

$$\text{(a) Required voltage gain} = \frac{v_o}{v_s} = \frac{3 \text{ V}}{0.01 \text{ V}} = 300 \text{ V/V}$$

(b) The smallest  $R_i$  allowed is obtained from

$$0.1 \mu A = \frac{10 \text{ mV}}{R_s + R_i} \Rightarrow R_s + R_i = 100 \text{ k}\Omega$$

Thus  $R_i = 90 \text{ k}\Omega$ .

For  $R_i = 90 \text{ k}\Omega$ ,  $i_i = 0.1 \mu\text{A}$  peak, and


$$\text{Overall current gain} = \frac{v_o / R_L}{i_i} = \frac{3 \text{ mV}}{0.1 \mu\text{A}}$$

$$\text{Overall power gain} = \frac{v_o^2 / R_L}{v_{s(rms)}^2 \times i_{i(rms)}} = \frac{\left( \frac{3 \text{ mV}}{0.1 \mu\text{A}} \right)^2 / 1000}{\left( \frac{10 \times 10^{-3}}{\sqrt{2}} \right) \times \left( \frac{0.1 \times 10^{-6}}{\sqrt{2}} \right)}$$

$$= 9 \times 10^6 \text{ W/W}$$

(This takes into acct. the power dissipated in the internal resistance of the source.)

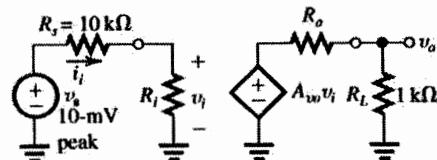(c) If  $(A_{v_o} v_i)$  has its peak value limited to 5 V, the largest value of  $R_o$  is found from



$$= \times \frac{R_L}{R_L + R_o} = 3 \Rightarrow R_o = \frac{2}{3} R_L = 667 \Omega$$

(If  $R_o$  were greater than this value, the output voltage across  $R_L$  would be less than 3 V.)

(d) For  $R_i = 90 \text{ k}\Omega$  and  $R_o = 667 \Omega$ , the required value  $A_{v_o}$  can be found from

$$300 \text{ V/V} = \frac{90}{90+10} \times A_{v_o} \times \frac{1}{1+0.667}$$

$$\Rightarrow A_{v_o} = 555.7 \text{ V/V}$$


$$(e) R_i = 100 \text{ k}\Omega (1 \times 10^5 \Omega)$$

$$R_o = 100 \Omega (1 \times 10^2 \Omega)$$

$$300 = \frac{100}{100+10} \times A_{v_o} \times \frac{1000}{1000+100}$$

$$\Rightarrow A_{v_o} = 363 \text{ V/V}$$

### 1.41

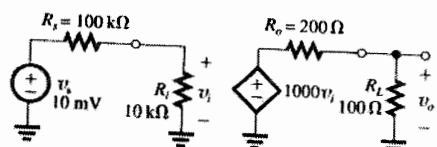


$$(a) v_o = 10 \text{ mV} \times \frac{10}{10+100} \times 1000 \times \frac{100}{100+200} = 303 \text{ mV}$$

$$(b) \frac{v_o}{v_s} = \frac{303 \text{ mV}}{10 \text{ mV}} = 30.3 \text{ V/V}$$

$$(c) \frac{v_o}{v_i} = 1000 \times \frac{100}{100+200} = 333.3 \text{ V/V}$$


(d)

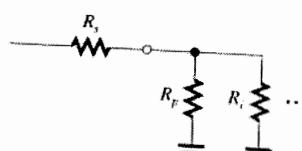

Connect a resistance  $R_p$  in parallel with the input and select its value from

$$\begin{aligned} \frac{(R_p \parallel R_i)}{(R_p \parallel R_i) + R_s} &= \frac{1}{2R_i + R_s} \\ \Rightarrow 1 + \frac{R_s}{R_p \parallel R_i} &= 22 \Rightarrow R_p \parallel R_i = \frac{R_s}{21} = \frac{100}{21} \\ \Rightarrow \frac{1}{R_p} + \frac{1}{R_i} &= \frac{21}{100} \\ R_p &= \frac{1}{0.21 - 0.1} = 9.1 \text{ k}\Omega \end{aligned}$$

### 1.42

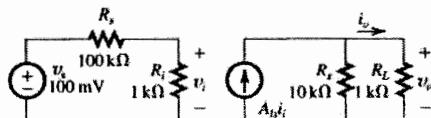


$$\begin{aligned} \text{(a) Current gain} &= \frac{i_o}{i_t} \\ &= A_b \frac{R_o}{R_o + R_L} \\ &= 100 \frac{10}{11} \\ &= 90.9 \frac{\text{A}}{\text{A}} = 39.2 \text{ dB} \end{aligned}$$

$$\begin{aligned} \text{(b) Voltage gain} &= \frac{v_o}{v_s} \\ &= \frac{i_o}{i_t} \frac{R_s}{R_s + R_i} \\ &= 90.9 \times \frac{1}{101} \\ &= 0.9 \text{ V/V} = -0.9 \text{ dB} \end{aligned}$$

$$\begin{aligned} \text{(c) Power gain} &= A_p = \frac{v_o i_o}{v_s i_t} \\ &= 0.9 \times 90.9 \\ &= 81.8 \text{ W/W} = 19.1 \text{ dB} \end{aligned}$$

### 1.43

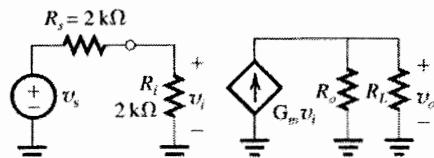

$$G_m = 40 \text{ mA/V}$$

$$R_o = 20 \text{ k}\Omega$$

$$R_i = 1 \text{ k}\Omega$$

$$\begin{aligned} v_i &= \frac{R_i}{R_s + R_i} v_s \\ &= v_s \frac{2}{2+2} = \frac{v_s}{2} \end{aligned}$$


$$v_o = G_m v_i (R_L \parallel R_o)$$

$$= 40 \frac{20 \times 1}{20+1} v_i$$


$$= 40 \frac{20}{21} \frac{v_s}{2}$$

$$\text{Overall voltage gain} = \frac{v_o}{v_s} = 19.05 \text{ V/V}$$

### 1.44

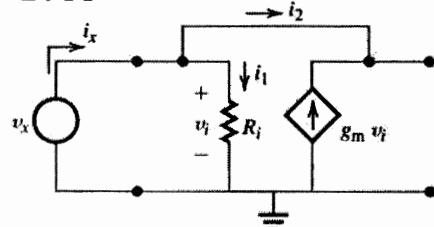
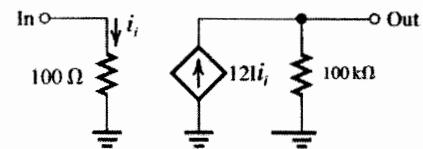
$$\left. \begin{aligned} i_x &= i_1 + i_2 \\ i_1 &= v_t / R_i \\ i_2 &= g_m + v_t \\ v_t &= V_x \end{aligned} \right\} \begin{aligned} i_x &= v_x / R_i + g_m v_x \\ i_x &= v_x + \left( \frac{1}{R_i} + g_m \right) \\ \frac{v_x}{i_x} &= \frac{1}{1/R_i + g_m} \\ &= \frac{R_i}{1 + g_m R_i} = R_{in} \end{aligned}$$



### 1.45

Transresistance amplifier

To limit  $\Delta v_o$  to 10% corresponding to  $R_s$  varying in the range 1 to 10 kΩ, we select  $R_i$  sufficiently low;

$$R_i \leq \frac{R_{s\min}}{10}$$


Thus,  $R_i = 100 \Omega$

To limit  $\Delta v_o$  to 10% while  $R_L$  varies over the range 1 to 10 kΩ, we select  $R_o$  sufficiently low;

$$R_o \leq \frac{R_{L\min}}{10}$$

Thus,  $R_o = 100 \Omega$

Now, for  $i_s = 10 \mu\text{A}$ ,

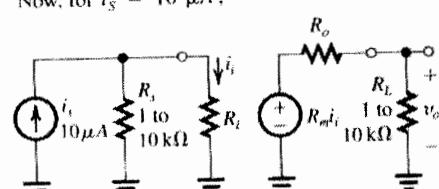


$$v_{O\min} = 10^{-5} \frac{R_{S\min}}{R_{S\min} + R_i} R_m \frac{R_{L\min}}{R_{L\min} + R_o}$$

$$1 = 10^{-5} \frac{1000}{1000 + 100} R_m \frac{1000}{1000 + 100}$$


$$\Rightarrow R_m = 1.21 \times 10^5$$

$$= 121 \text{ k}\Omega$$

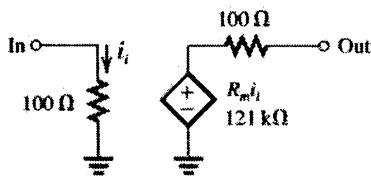

### 1.46

#### Voltage Amplifier

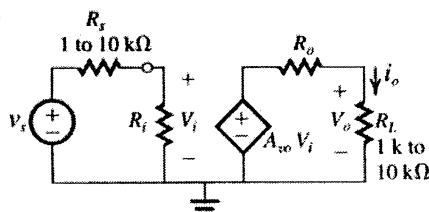

For  $R_s$  varying in the range 1 K to 10 kΩ and  $\Delta i_s$  variation limited to 10%, select  $R_i$  to be sufficiently large:

$$R_i \geq 10 R_{S\max}$$

$$R_i = 10 \times 10 \text{ k}\Omega = 100 \text{ k}\Omega = 1 \times 10^5 \Omega$$

For  $R_f$  varying in the range 1 to 10 kΩ, the load current variation limited to 10%, select  $R_o$  sufficiently low:

$$R_o \leq \frac{R_{L\max}}{10}$$

$$R_o = \frac{1 \text{ k}\Omega}{10} = 100 \Omega = 1 \times 10^2 \Omega$$

Now find  $A_{vo}$


$$i_{o\min} = 10 \text{ mV} \times \frac{R_i}{R_i + R_{S\max}} \times A_{vo} \frac{R_o}{R_o + R_{L\max}}$$

$$1 \times 10^{-3} = 10 \times 10^{-3} \times \frac{100 \text{ k}\Omega}{100 \text{ k}\Omega + 10 \text{ k}\Omega}$$

$$\times A_{vo} \times \frac{1}{100 \Omega + 10 \text{ k}\Omega}$$

$$1 \times 10^{-3} = 10 \times 10^{-3} \times \frac{100}{110} \times A_{vo} \times \frac{1}{1100}$$

$$A_{vo} = 121 \text{ V/V}$$

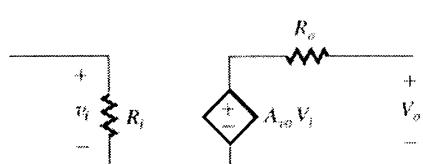


Voltage amplifier equivalent circuit is

$$R_i = 1 \times 10^5 \Omega, A_{vo} = 121 \text{ V/V} \text{ and}$$

$$R_o = 1 \times 10^2 \Omega$$

### 1.47

#### Current Amplifier

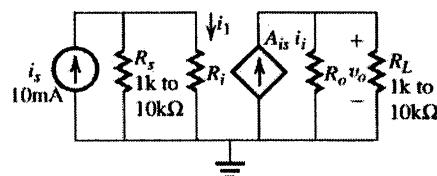

For  $R_s$  varying in the range 1 kΩ to 10 kΩ range and load voltage variation limited to 10%, select  $R_i$  to be sufficiently low:

$$R_i \leq \frac{R_{S\min}}{10}$$

$$R_i = \frac{1 \text{ k}\Omega}{10} = 100 \Omega = 1 \times 10^2 \Omega$$

For  $R_L$  varying in the range 1 kΩ to 10 kΩ and load voltage variation limited to 10%,  $R_o$  is selected sufficiently large:

$$R_o \geq 10 R_{L\max}$$

$$R_o = 10 \times 10 \text{ k}\Omega$$

$$= 100 \text{ k}\Omega = 1 \times 10^5 \Omega$$

Now we find  $A_{is}$


$$V_{O\min} = 10 \mu A \times \frac{R_{S\min}}{R_{S\min} + R_i} \times A_{is} \times R_o \parallel R_{L\min}$$

$$= 10 \times 10^{-6} \frac{R_{S\min}}{R_{S\min} + R_i} \times A_{is} \frac{R_o R_{L\min}}{R_o + R_{L\min}}$$

$$= 10 \times 10^{-6} \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 100 \Omega} \times A_{is} \frac{100 \text{ K} \times 1 \text{ K}}{100 \text{ K} + 1 \text{ K}}$$

$$\Rightarrow A_{is} = 111.1 \text{ A/A}$$

Current amplifier equivalent circuit is

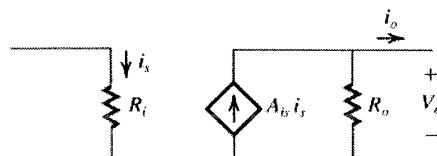


$$R_i = 1 \times 10^2 \Omega, A_{is} = 111.1 \text{ A/s},$$

$$R_o = 1 \times 10^5 \Omega$$
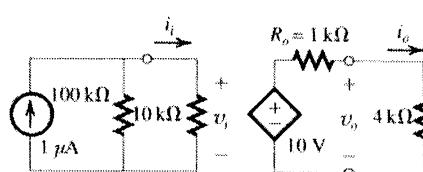
### 1.48

$$R_o = \frac{\text{Open-circuit output voltage}}{\text{Short-circuit output current}} = \frac{10 \text{ V}}{10 \text{ mA}} = 1 \text{ k}\Omega$$

$$v_o = 10 \times \frac{4}{1+4} = 8 \text{ V}$$



$$A_v = \frac{v_o}{v_i} = \frac{8}{1 \times 10^{-3} \times (100 \parallel 10) \times 10^3} = 888 \text{ V/V or } 58.9 \text{ dB}$$


$$A_I = \frac{i_o}{i_i} = \frac{v_o / R_L}{10^{-3} \times \frac{100}{100+10}} = \frac{8/(4 \times 10^3)}{10^{-3} \times \frac{100}{110}} = 2200 \text{ A/A or } 66.8 \text{ dB}$$

$$A_I = \frac{i_o^2 / R_L}{i_i^2 R_i} = \frac{8^2 / (4 \times 10^3)}{\left(10^{-3} \times \frac{100}{100+10}\right)^2 10 \times 10^3} = 19.36 \times 10^5 \text{ W/W or } 62.9 \text{ dB}$$

$$\begin{aligned} \text{Overall current gain} &= \frac{i_o}{1 \mu A} \\ &= \frac{v_o / R_L}{1 \mu A} = \frac{8 / (4 \times 10^3)}{10^{-3}} \\ &= 2000 \text{ A/A or } 66 \text{ dB} \end{aligned}$$


### 1.49

Using the voltage divider rule

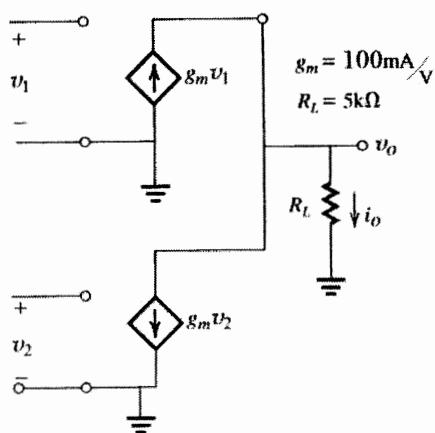

$$\begin{aligned} a. i_o &= g_m v_1 - g_m v_2 \\ v_o &= i_o R_L = g_m R_L (v_1 - v_2) = v_o \\ b. v_1 &= v_2 \therefore v_0 = 0V \\ v_1 = 1.01 & \\ v_2 = 0.99 & \end{aligned} \quad \therefore v_0 = 10V$$

### 1.50

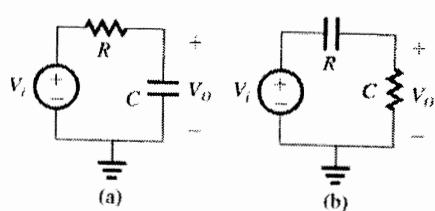

$$\text{for (a)} \quad V_o = V_i \left( \frac{1/SC}{1/SC + R} \right)$$

$$\frac{V_o}{V_i} = \frac{1}{1 + SCR}$$

where  $k=1$

$$\omega_0 = \frac{1}{RC} \text{ from table 1.2 it is low pass.}$$

$$\text{for (b)} \quad V_o = V_i \left( \frac{R}{R + \frac{1}{SC}} \right)$$

$$\frac{V_o}{V_i} = \frac{SRC}{1 + SRC}$$

$$\frac{V_o}{V_i} = \frac{S}{S + \frac{1}{RC}}$$

where  $k=1$

$$\omega_0 = \frac{1}{RC} \text{ from table 1.2 it is high pass.}$$

### 1.51

$$\begin{aligned} \frac{V_o}{V_s} &= \frac{\frac{R_i \frac{1}{sC_i}}{R_i + \frac{1}{sC_i}}}{R_s + \left( \frac{R_i \frac{1}{sC_i}}{R_i + \frac{1}{sC_i}} \right)} = \frac{\frac{R_i}{1 + sC_i R_i}}{R_s + \left( \frac{R_i}{1 + sC_i R_i} \right)} \\ &= \frac{R_i}{R_s + sC_i R_i R_s + R_i} \end{aligned}$$


$$\frac{V_o}{V_s} = \frac{R_i}{(R_s + R_i) + sC_i R_i R_s} = \frac{\frac{R_i}{(R_s + R_i)}}{1 + S \left( \frac{C_i R_i R_s}{R_s + R_i} \right)}$$

$$\text{Where } K = \frac{R_i}{(R_s + R_i)}$$

$$\omega = \frac{R_s + R_i}{C_i R_i R_s} \text{ from table 1.2 low pass for given values } \omega_0 = 12.5 \text{ MHz}$$

### 1.52

Using the voltage-divider rule,

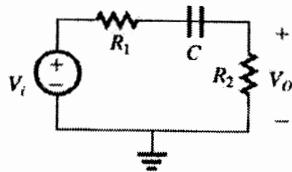

$$T(s) = \frac{V_o}{V_i} = \frac{R_2}{R_2 + R_1 + \frac{1}{sC}}$$

$$T(s) = \left( \frac{R_2}{R_1 + R_2} \right) \left( \frac{s + \frac{1}{C(R_1 + R_2)}}{s} \right)$$

which is from Table 1.2 is of the high-pass type with

$$K = \frac{R_2}{R_1 + R_2}, \omega_0 = \frac{1}{C(R_1 + R_2)}$$

As a further verification that this is a high-pass network and  $T(s)$  is a high-pass transfer function, we assume as  $s \rightarrow 0$ ,  $T(s) \rightarrow 0$ ; and as  $s \rightarrow \infty$ ,  $T(s) = R_2 / (R_1 + R_2)$ . Also, from the circuit observe as  $s \rightarrow \infty$ ,  $(1/sC) \rightarrow 0$  and

$$V_o/V_i = R_2/(R_1 + R_2). \text{ Now, for}$$


$$R_1 = 10 \text{ k}\Omega, R_2 = 40 \text{ k}\Omega, \text{ and } C = 0.1 \mu\text{F}.$$

$$f_o = \frac{\omega_0}{2\pi} = \frac{1}{2\pi \times 0.1 \times 10^{-6} (10 + 40) \times 10^3} = 31.8 \text{ Hz}$$

$$|T(j\omega_0)| = \frac{K}{\sqrt{2}} = \frac{40}{10 + 40\sqrt{2}} = 0.57 \text{ V/V}$$

### 1.53

Using the voltage divider rule,

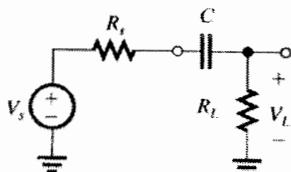

$$\frac{V_o}{V_s} = \frac{R_L}{R_L + R_s + \frac{1}{sC}}$$

$$= \frac{R_L}{R_L + R_s} \frac{s + \frac{1}{C(R_L + R_s)}}{s}$$

which is of the high-pass STC type (see Table 1.2) with

$$K = \frac{R_L}{R_L + R_s}, \omega_0 = \frac{1}{C(R_L + R_s)}$$

For  $f_o \leq 10 \text{ Hz}$


$$\frac{1}{2\pi C(R_L + R_s)} \leq 10$$

$$\Rightarrow C \geq \frac{1}{2\pi \times 10(20 + 5) \times 10^3}$$

Thus, the smallest value of  $C$  that will do the job is  $C = 0.64 \mu\text{F}$ .
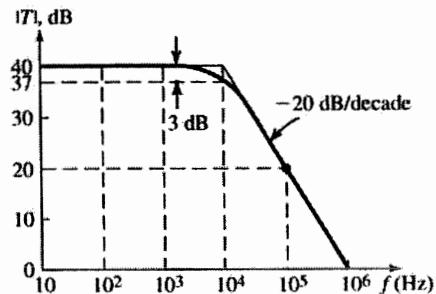
### 1.54

The given measured data indicate that this amplifier has a low-pass STC frequency response with a low-frequency gain of 40 dB, and a 3-dB frequency of  $10^4 \text{ Hz}$ . From our knowledge of the Bode plots for low-pass STC networks (Figure 1.23a) we can complete the Table entries and sketch the amplifier frequency response



$f(\text{Hz})$	$ T (\text{dB})$	$\angle T(\text{°})$
0	40	0
100	40	0
1000	40	0
$10^4$	37	-45°
$10^5$	20	-90°
$10^6$	0	-90°

### 1.55

Since the overall transfer function is that of three identical STC LP circuits in cascade (but with no loading effects since the buffer amplifiers have input and zero output resistances) the overall gain will drop by 3 dB below the value at dc at the frequency for which the gain of each STC circuit is 1 dB down. This frequency is found as follows: The transfer function of each STC circuit is

$$T(s) = \frac{1}{1 + \frac{s}{\omega_0}}$$

where

$$\omega_0 = 1/CR$$

Thus,

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

$$20 \log \frac{1}{\sqrt{1 + \left(\frac{\omega_{1\text{dB}}}{\omega_0}\right)^2}} = -1$$

$$\Rightarrow 1 + \left(\frac{\omega_{1\text{dB}}}{\omega_0}\right)^2 = 10^{0.1}$$


$$\omega_{1\text{dB}} = 0.51\omega_0$$

$$\omega_{1\text{dB}} = 0.51/CR$$
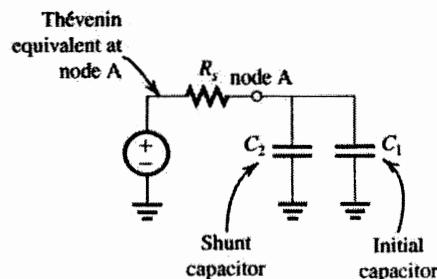
### 1.56

$R_s = 100 \text{ k}\Omega$ , since the 3-dB frequency is reduced by a very high factor (from 6 MHz to 120 kHz)  $C_1$  must be much larger than  $C_2$ . Thus, neglecting  $C_1$  we find  $C_2$  from

$$120 \text{ kHz} \approx \frac{1}{2\pi C_2 R_s}$$



$$= \frac{1}{2\pi C_2 \times 10^5}$$

$$\Rightarrow C_2 = 13.3 \text{ pF}$$

If the original 3-dB frequency (6 MHz) is attributable to  $C_1$  then

$$6 \text{ MHz} = \frac{1}{2\pi C_1 R_s}$$


$$\Rightarrow C_1 = \frac{1}{2\pi \times 6 \times 10^6 \times 10^5} \\ = 0.26 \text{ pF}$$

### 1.57

Since when  $C$  is connected the 3-dB frequency is reduced by a large factor, the value of  $C$  must be much larger than whatever parasitic capacitance originally existed at node A (i.e., between A and ground). Furthermore, it must be that  $C$  is now the dominant determinant of the amplifier 3-dB frequency (i.e., it is dominating over whatever may be happening at node B or anywhere else in the amplifier). Thus, we can write

$$150 \text{ kHz} = \frac{1}{2\pi C(R_{o1} \parallel R_{i2})}$$
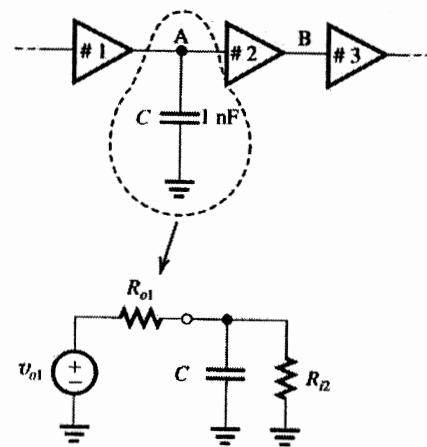
$$\Rightarrow (R_{o1} \parallel R_{i2}) = \frac{1}{2\pi \times 150 \times 10^3 \times 1 \times 10^{-9}} \\ = 1.06 \text{ k}\Omega$$



$$\text{Now } R_{i2} = 100 \text{ k}\Omega.$$

$$\text{Thus } R_{o1} = 1.07 \text{ k}\Omega$$

Similarly, for node B,

$$15 \text{ kHz} = \frac{1}{2\pi C(R_{o2} \parallel R_{i3})}$$

$$\Rightarrow R_{o2} \parallel R_{i3} = \frac{1}{2\pi \times 15 \times 10^3 \times 1 \times 10^{-9}} \\ = 10.6 \text{ k}\Omega$$

$$R_{o2} = 11.9 \text{ k}\Omega$$

She should connect a capacitor of value  $C_p$  to node B where  $C_p$  can be found from,

$$10 \text{ kHz} = \frac{1}{2\pi C_p (R_{o2} \parallel R_{i3})}$$


$$\Rightarrow C_p = \frac{1}{2\pi \times 10 \times 10^3 \times 10.6 \times 10^{-9}} \\ = 1.5 \text{ nF}$$

Note that if she chooses to use node A she would need to connect a capacitor 10 times larger!
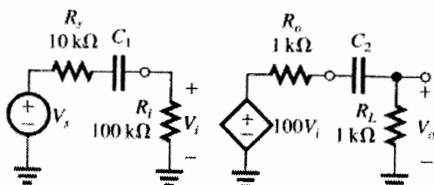
### 1.58

For the input circuit, the corner frequency  $f_{\text{c1}}$  is found from

$$f_{\text{c1}} = \frac{1}{2\pi C_1 (R_s + R_i)}$$



For  $f_{\text{c1}} \leq 100 \text{ Hz}$ ,

$$\frac{1}{2\pi C_1 (10 + 100) \times 10^3} \leq 100$$

$$\Rightarrow C_1 \geq \frac{1}{2\pi \times 110 \times 10^3 \times 10^2} = 1.4 \times 10^{-8}$$

Thus we select  $C_1 = 1 \times 10^{-7} F = 0.1 \mu F$ .

The actual corner frequency resulting from  $C_1$  will be

$$f_{c1} = \frac{1}{2\pi \times 10^{-7} \times 110 \times 10^3} = 14.5 \text{ Hz}$$

For the output circuit,

$$f_{c2} = \frac{1}{2\pi C_2 (R_O + R_L)}$$

For  $f_{c2} \leq 100 \text{ Hz}$ ,

$$\frac{1}{2\pi C_2 (1+1) \times 10^3} \leq 100$$

$$\Rightarrow C_2 \geq \frac{1}{2\pi \times 2 \times 10^3 \times 10^2} = 0.8 \times 10^{-6}$$

Select  $C_2 = 1 \times 10^{-6} = 1 \mu F$

This will place the corner frequency at



$$f_{c2} = \frac{1}{2\pi \times 10^{-6} \times 2 \times 10^3} = 80 \text{ Hz}$$

$$T(s) = \frac{100}{\left(1 + \frac{s}{2\pi f_{c1}}\right)\left(1 + \frac{s}{2\pi f_{c2}}\right)}$$
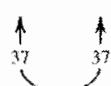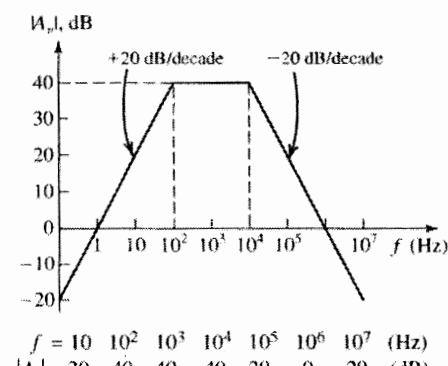
### 1.59

The LP factor  $1/(1+jf/10^4)$  results in a Bode plot like that in Fig. 1.23(a) with the 3dB frequency  $f_O = 10^4 \text{ Hz}$ . The high-pass factor  $1/(1+10^4/jf)$  results in a Bode plot like that in Fig. 1.24(a) with the 3dB frequency  $f_O = 10^4 \text{ Hz}$ .

The Bode plot for the overall transfer function can be obtained by summing the dB values of the two individual plots and then raising the resulting plot vertically by 40 dB (corresponding to the factor 100 in the numerator). The result is as follows:



**Better approximation  
(3-dB frequencies)**

Bandwidth =  $10^4 - 10^2 = 9900 \text{ Hz}$

### 1.60


$$T_i(s) = \frac{V_i(s)}{V_s(s)} = \frac{1/sC_1}{1/sC_1 + R_1} = \frac{1}{sC_1 R_1 + 1}$$

LP

3 dB frequency

$$= \frac{1}{2\pi C_1 R_1} = \frac{1}{2\pi 10^{-11} 10^6} = 15.9 \text{ Hz}$$

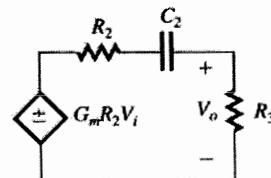For  $T_o(S)$ , the following equivalent circuit can be used:




$$\begin{aligned} T_o(S) &= -G_m R_2 \frac{R_3}{R_2 + R_3 + 1/sC_2} \\ &= -G_m (R_2 \parallel R_3) \frac{S}{S + \frac{1}{C_2(R_2 + R_3)}} \end{aligned}$$

$$3 \text{ dB frequency} = \frac{1}{2\pi C_2 (R_2 + R_3)}$$

$$= \frac{1}{2\pi 100 \times 10^{-9} \times 30 \times 10^3} = 53 \text{ Hz}$$

$$\therefore T(S) = T_i(S)T_o(S)$$
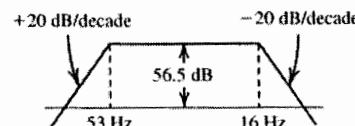
$$= \frac{1}{1 + \frac{S}{2\pi \times 15.9 \times 10^3}} \times -666.7 \times \frac{S}{S + (2\pi \times 53)}$$



Bandwidth =  $16 \text{ kHz} - 53 \text{ Hz} \approx 16 \text{ Hz}$

### 1.61

$$V_i = V_s \frac{R_i}{R_s + R_i}$$

a) To satisfy constraint (1), namely

$$V_i \geq \left(1 + \frac{x}{100}\right) V_s$$

We substitute in Eq.(1) to obtain

$$\frac{R_i}{R_s + R_i} \geq 1 - \frac{x}{100}$$

Thus


$$\frac{R_S + R_i}{R_i} \leq \frac{1}{1 - \frac{x}{100}}$$

$$\frac{R_S}{R_i} \leq \frac{1}{1 - \frac{x}{100}} - 1 = \frac{\frac{x}{100}}{1 - \frac{x}{100}}$$

which can be expressed as

$$\frac{R_i}{R_S} \geq \frac{1 - \frac{x}{100}}{\frac{x}{100}}$$

resulting in

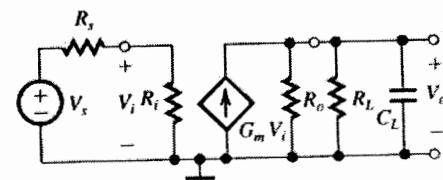

$$R_i \geq R_S \left( \frac{100}{x} - 1 \right)$$

b) The 3-dB frequency is determined by the parallel RC circuit at the output

$$f_0 = \frac{1}{2\pi} \omega_0 = \frac{1}{2\pi C_L (R_L \parallel R_o)}$$

Thus,

$$f_0 = \frac{1}{2\pi C_L} \left( \frac{1}{R_L} + \frac{1}{R_o} \right)$$

To obtain a value for  $f_0$  greater than a specified value  $f_{3dB}$  we select  $R_o$  so that

$$\frac{1}{2\pi C_L} \left( \frac{1}{R_L} + \frac{1}{R_o} \right) \geq f_{3dB}$$

$$\frac{1}{R_L} + \frac{1}{R_o} \geq 2\pi C_L f_{3dB}$$

$$\frac{1}{R_o} \geq 2\pi C_L f_{3dB} - \frac{1}{R_L}$$

$$R_o \leq \frac{1}{2\pi f_{3dB} + C_L} - \frac{1}{R_L} \quad (2)$$

c) To satisfy constraint (3), we first determine the dc gain as

$$\text{dc gain} = \frac{R_i}{R_S + R_i} G_m (R_o \parallel R_L)$$

For the dc gain to be greater than a specified value  $A_O$ ,

$$\frac{R_i}{R_S + R_i} G_m (R_o \parallel R_L) \geq A_O$$

The first factor on the LHS is (from constraint (1)) greater or equal to  $(1 - x/100)$ . Thus

$$G_m \geq \frac{A_O}{\left( 1 - \frac{x}{100} \right) (R_o \parallel R_L)} \quad (3)$$

Substituting  $R_S = 10 \text{ k}\Omega$  and  $x = 20\%$  in (1) results in

$$R_S \geq 10 \left( \frac{100}{20} - 1 \right) = 40 \text{ k}\Omega$$

Substituting  $f_{3dB} = 3 \text{ MHz}$ ,  $C_L = 10 \text{ pF}$  and  $R_L = 10 \text{ k}\Omega$  in Eq. (2) result in

$$R_o \leq \frac{1}{2\pi \times 3 \times 10^6 \times 10 \times 10^{-12} - \frac{1}{10^4}} = 11.3 \text{ k}\Omega$$

Substituting  $A_O = 80$ ,  $x = 20\%$ ,  $R_i = 10 \text{ k}\Omega$ , and  $R_o = 11.3 \text{ k}\Omega$ , eq. (3) results in

$$G_m \geq \frac{80}{\left( 1 - \frac{20}{100} \right) (10 \parallel 11.3) \times 10^3} = 18.85 \text{ mA/V}$$

If the more practical value of  $R_o = 10 \text{ k}\Omega$  is used then

$$G_m \geq \frac{80}{\left( 1 - \frac{20}{100} \right) (10 \parallel 10) \times 10^3} = 20 \text{ mA/V}$$

## 1.62

Using the voltage-divider rule we obtain

$$\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2}$$

where

$$Z_1 = R_1 \parallel \frac{1}{sC_1} \text{ and } Z_2 = R_2 \parallel \frac{1}{sC_2}$$

It is obviously more convenient to work in terms of admittances. Therefore we express  $V_o/V_i$  in the alternate form

$$\frac{V_o}{V_i} = \frac{Y_1}{Y_1 + Y_2}$$

and substitute  $Y_1 = (1/R_1) + sC_1$  and  $Y_2 = (1/R_2) + sC_2$ , to obtain

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{\frac{1}{R_1} + sC_1}{\frac{1}{R_1} + \frac{1}{R_2} + s(C_1 + C_2)} \\ &= \frac{C_1}{C_1 + C_2} \frac{s + \frac{1}{C_1 R_1}}{\frac{1}{(C_1 + C_2)} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)} \end{aligned}$$

This transfer function will be independent of frequency ( $s$ ) if the second factor reduces to unity.

This in turn will happen if

$$\frac{1}{C_1 R_1} = \frac{1}{C_1 + C_2} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

which can be simplified as follows

$$\frac{C_1 + C_2}{C_2} = R_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \quad (1)$$

$$1 + \frac{C_2}{C_1} = 1 + \frac{R_1}{R_2}$$

or

$$C_1 R_1 = C_2 R_2$$

When this condition applies, the attenuator is said to be compensated, and its transfer function is given by

$$\frac{V_o}{V_i} = \frac{C_1}{C_1 + C_2}$$

which, using Eq. (1) can be expressed in the alternate form

$$\frac{V_o}{V_i} = \frac{1}{1 + \frac{R_1}{R_2}} = \frac{R_2}{R_1 + R_2}$$

Thus when the attenuator is compensated ( $C_1 R_1 = C_2 R_2$ ) its transmission can be determined either by its two resistors  $R_1, R_2$  or by its two capacitors,  $C_1, C_2$ , and the transmission is *not* a function of frequency.

### 1.63

The HP STC circuit whose response determines the frequency response of the amplifier in the low-frequency range has a phase angle of  $11.4^\circ$  at  $f = 100$  Hz. Using the equation for  $\angle T(j\omega)$  from Table 1.2 we obtain

$$\tan^{-1} \frac{f_o}{100} = 11.4^\circ \Rightarrow f_o = 20.16 \text{ Hz}$$

The LP STC circuit whose response determines the amplifier response at the high-frequency end has a phase angle of  $-11.4^\circ$  at  $f = 1$  kHz. Using the relationship for  $\angle T(j\omega)$  given in Table 1.2 we obtain for the LP STC circuit,

$$-\tan^{-1} \frac{10^3}{f_o} = -11.4^\circ \Rightarrow f_o = 4959.4 \text{ Hz}$$

At  $f = 100$  Hz the drop in gain is due to the HP STC network, and thus its value is

$$20 \log \frac{1}{\sqrt{1 + \left( \frac{20.16}{100} \right)^2}} = -0.17 \text{ dB}$$

Similarly, at  $f = 1$  kHz the drop in gain is caused by the LP STC network. The drop in gain is

$$20 \log \frac{1}{\sqrt{1 + \left( \frac{1000}{4959.4} \right)^2}} = -0.17 \text{ dB}$$

The gain drops by 3 dB at the corner frequencies of the two STC networks, that is, at  $f = 20.16$  Hz and  $f = 4959.4$  Hz.

### 1.64

Using the expression in (3.2) using

$$B = 7.3 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2};$$

$k = 8.62 \times 10^{-3} \text{ eV/K}$ ;  $E_g = 1.12 \text{ V}$ , we have:

$$T = -70^\circ\text{C} = 203 \text{ K};$$

$$n_i = 2.67 \times 10^4 \text{ cm}^{-3}; \frac{n_i}{N} = 5.33 \times 10^{-18}$$

That is, one out of every  $5.33 \times 10^{18}$  silicon atoms is ionized at this temperature.

$$T = 0^\circ\text{C} = 273 \text{ K};$$

$$n_i = 1.52 \times 10^6 \text{ cm}^{-3}; \frac{n_i}{N} = 3.05 \times 10^{-14}$$

$$T = 20^\circ\text{C} = 293 \text{ K};$$

$$n_i = 8.60 \times 10^6 \text{ cm}^{-3}; \frac{n_i}{N} = 1.72 \times 10^{-11}$$

$$T = 100^\circ\text{C} = 373 \text{ K};$$

$$n_i = 1.43 \times 10^{12} \text{ cm}^{-3}; \frac{n_i}{N} = 2.87 \times 10^{-10}$$

$$T = 125^\circ\text{C} = 398 \text{ K};$$

$$n_i = 4.72 \times 10^{12} \text{ cm}^{-3}; \frac{n_i}{N} = 9.45 \times 10^{-10}$$

### 1.65

Hole concentration in intrinsic  $S_i = n_i$

$$n_i = BT^{3/2} e^{-E_g/KT}$$

$$= 7.3 \times 10^{15} (300)^{3/2} e^{-1.12/2 \times 8.62 \times 10^{-3} \times 300}$$

$$= 1.5 \times 10^{16} \text{ holes/cm}^3$$

In phosphorus doped Si, hole concentration drops below intrinsic level by a factor of  $10^7$

Hole concentration in P doped Si is

$$p_n = \frac{1.5 \times 10^{16}}{10^7} = 1.5 \times 10^3 \text{ cm}^{-3}$$

Phosphorus doped Si, so

$$n_p = N_D = p_n n_i = n_i^2$$

$$n_p = n_i^2/p_n = \frac{(1.5 \times 10^{16})^2}{1.5 \times 10^3}$$

### 1.66

$$N_D = n_p = 1.5 \times 10^{17} \text{ P atoms/cm}^3$$

$$T = 27^\circ\text{C} = 273 + 27 = 300 \text{ K}$$

$$\text{At } 300 \text{ K}, n_i = 1.5 \times 10^{16}/\text{cm}^3$$

Phosphorous doped Si

$$n_n = N_D = 10^{16}/\text{cm}^3$$

$$p_n = \frac{n_i^2}{N_D} = \frac{(1.5 \times 10^{16})^2}{10^{16}} = 2.25 \times 10^4 \text{ cm}^3$$

$$\text{Hole concentration } = p_n = 2.25 \times 10^4/\text{cm}^3$$

$$T = 125^\circ\text{C} = 273 + 125 = 398 \text{ K}$$

At 398 K,  $n_i = BT^{3/2} e^{-E_g/2kT}$

$$= 7.3 \times 10^{15} \times (398)^{3/2} e^{-1.12/2 \times 8.62 \times 10^{-5} \times 398}$$

$$= 4.72 \times 10^{12}/\text{cm}^3$$

$$p_n \approx \frac{n_i^2}{N_D} = 2.23 \times 10^9/\text{cm}^3$$

At 398 K, hole concentration

$$p_n = 2.23 \times 10^9/\text{cm}^3$$

### 1.67

(a) The resistivity of silicon is given

For intrinsic silicon,

$$\rho = n = n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$$

Using  $\mu_n = 1350 \text{ cm}^2/\text{Vs}$  and

$$\mu_p = 480 \text{ cm}^2/\text{Vs}, \text{ we have:}$$

$$\rho = 2.28 \times 10^5 \Omega\text{-cm.}$$

Using  $R = \rho \cdot \frac{L}{A}$  with  $L = 0.01 \text{ cm}$  and

$$A = 3 \times 10^{-8} \text{ cm}^2, \text{ we have}$$

$$R = 7.59 \times 10^9 \Omega.$$

(b)  $n_n \approx N_D = 10^{16} \text{ cm}^{-3}$ :

$$p_n = \frac{n_i^2}{n_n} = 2.25 \times 10^4 \text{ cm}^{-3}$$

Using  $\mu_n = 1110 \text{ cm}^2/\text{Vs}$  and

$$\mu_p = 400 \text{ cm}^2/\text{Vs}, \text{ we have:}$$

$$\rho = 0.56 \Omega\text{-cm}; R = 18.8 \text{ k}\Omega.$$

(c)  $n_n \approx N_D = 10^{18} \text{ cm}^{-3}$ :

$$p_n = \frac{n_i^2}{n_n} = 2.25 \times 10^2 \text{ cm}^{-3}$$

Using  $\mu_n = 1110 \text{ cm}^2/\text{Vs}$  and

$$\mu_p = 400 \text{ cm}^2/\text{Vs}, \text{ we have:}$$

$$\rho = 5.63 \times 10^{-3} \Omega\text{-cm}; R = 188 \Omega.$$

As expected, since ND is increased by 100, the resistivity decreases by the same factor.

$$(d) p_p \approx N_A = 10^{16} \text{ cm}^{-3}; n_p = \frac{n_i^2}{n_n}$$

$$= 2.25 \times 10^4 \text{ cm}^{-3}$$

$$\rho = 1.56 \Omega\text{-cm}; R = 52.1 \text{ k}\Omega$$

(e) Since  $\rho$  is given to be  $2.8 \times 10^{-6} \Omega\text{-cm}$ , we

directly calculate  $R = 9.33 \times 10^{-2} \Omega$ .

### 1.68

$$J_{\text{drift}} = q(n\mu_n + p\mu_p) E$$

Here  $n = N_p$  and since it is n-Si, one can assume  $p \ll n$  and ignore the term  $p\mu_p$ . Also

$$E = \frac{1 \text{ V}}{10 \mu\text{m}} = \frac{1 \text{ V}}{10 \times 10^{-4} \text{ cm}} = 10^3 \text{ V/cm}$$

Need  $J_{\text{drift}} = 1 \text{ mA}/\mu\text{m}^2 = q N_p \mu n E$

$$\frac{10^{-3} \text{ A}}{10^{-8} \text{ cm}^2} = 1.6 \times 10^{-19} N_p \times 1350 \times 10^3$$

$$\Rightarrow N_p = 4.63 \times 10^{17}/\text{cm}^3$$

### 1.69

$$p_{no} = \frac{n_i^2}{N_D} = \frac{(1.5 \times 10^{10})^2}{10^{16}} = 2.25 \times 10^4/\text{cm}^3$$

From Figure p3.10

$$\frac{dp}{dx} = -\frac{10^8 p_{no} - p_{no}}{W} = -\frac{10^8 p_{no}}{0.1 \times 10^{-4}}$$

since  $0.1 \mu\text{m} = 0.1 \times 10^{-4} \text{ cm}$

$$\frac{dp}{dx} = \frac{10^8 \times 2.25 \times 10^4}{0.1 \times 10^{-4}}$$

$$= 2.25 \times 10^{17}$$

Hence

$$J_p = -q D_p \frac{dp}{dx}$$

$$= -1.6 \times 10^{-19} \times 12 \times (-2.25 \times 10^{17})$$

$$= 0.432 \text{ A}/\text{cm}^2$$

### 1.70

$N_A = N_D = 10^{16} \text{ cm}^{-3}$  and  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$  we have  $V_0 = 695 \text{ mV}$ .

Using (3.26) and  $\epsilon_s = 11.7 \times 8.85 \times 10^{-14} \text{ F}/\text{cm}$ , we have  $W = 4.24 \times 10^5 \text{ cm} = 0.424 \mu\text{m}$ . The extension of the depletion width into the n and p regions is given in (3.27) and (3.28) respectively:

$$x_n = W \cdot \frac{N_A}{N_A + N_D} = 0.212 \mu\text{m}$$

$$x_p = W \cdot \frac{N_D}{N_A + N_D} = 0.212 \mu\text{m}$$

Since both regions are doped equally, the depletion region is symmetric.

Using (3.29) and  $A = 10^6 \text{ cm}^2$  the charge magnitude on each side of the junction is:

$$Q_J = 3.39 \times 10^{-14} \text{ C.}$$

1.71


$V_T$  at 300° K = 25.8 mV

built in voltage  $V_o$

$$V_o = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right) = 25.8 \times 10^{-13}$$

$$\ln\left(\frac{10^{16} \times 10^{15}}{(1.5 \times 10^{10})^2}\right)$$

$$= 0.633 \text{ V}$$

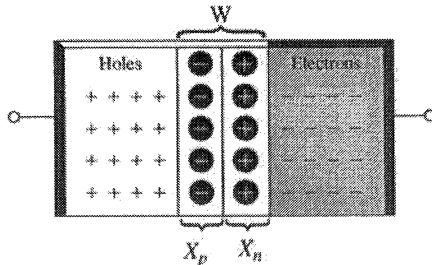

Depletion with

$$W = \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right)} V_o \leftarrow \text{equation 3.26}$$

$$W = \sqrt{\frac{2 \times 1.04 \times 10^{-17}}{1.6 \times 10^{-19}} \left( \frac{1}{10^6} + \frac{1}{10^{15}} \right)} \times 0.633$$

$$= 0.951 \times 10^{-4} \text{ cm} = 0.951 \mu\text{m}$$

to find  $X_n$  and  $X_p$

$$X_n = W \frac{N_A}{N_A + N_D} = 0.951 \times \frac{10^{16}}{10^{16} + 10^{15}}$$

$$= 0.8642 \mu\text{m}$$

$$X_p = W \frac{N_D}{N_A + N_D} = 0.951 \times \frac{10^{15}}{10^{16} + 10^{15}}$$

$$= 0.8642 \mu\text{m}$$

to calculate charge stored on either side

$$Q_J = A q \left( \frac{N_A N_D}{N_A + N_D} \right) W \text{ where junction area}$$

$$= 400 \mu\text{m}^2 = 400 \times 10^{-8} \text{ cm}^2$$

$$= 400 \times 10^{-8} \cdot 1.6 \times 10^{-19} \left( \frac{10^{16} \cdot 10^{15}}{10^{16} + 10^{15}} \right)$$

$$= 0.951 \times 10^{-4}$$

Hence,

$$Q_J = 5.53 \times 10^{-14} \text{ C}$$

1.72

Charge stored  $Q_J = qAXN$

Here  $X = 0.1 \mu\text{m} = 0.1 \times 10^{-4} \text{ cm}$

$$A = 10 \mu\text{m} \times 10 \mu\text{m} = 10 \times 10^{-4} \text{ cm}$$

$$\times 10 \times 10^{-4} \text{ cm}$$

$$= 100 \times 10^{-4} \text{ cm}^2$$

$$\text{So, } Q_J = 1.6 \times 10^{-19} \times 100 \times 10^{-8} \times 0.1$$

$$\times 10^{-4} \times 10^{16}$$

$$= 16 \text{ fC}$$

1.73

$$V_o = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

If  $N_A$  or  $N_D$  is increased by a factor of 10, then new value of  $V_o$  will be

$$V'_o = V_T \ln\left(\frac{10 N_A N_D}{n_i^2}\right)$$

The change in the value of  $V_o$  is

$$= \frac{\ln(10)}{\ln\left(\frac{N_A N_D}{n_i^2}\right)}$$

1.74

with  $N_A = 10^{16} \text{ cm}^{-3}$ ,  $N_D = 10^{16} \text{ cm}^{-3}$ , and  $n_i = 1.5 \times 10^{10}$ , we have  $V_o = 635 \text{ mV}$ .

and  $V_R = 5 \text{ V}$ , we have

$$W = 2.83 \times 10^4 \text{ cm} = 2.83 \mu\text{m}$$

with  $A = 4 \times 10^{-6} \text{ cm}^2$ , we have

$$Q_J = 4.12 \times 10^{-14} \text{ C}$$

1.75

$$W = \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right)} (V_o + V_R)$$

$$= \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right)} V_o \left( 1 + \frac{V_R}{V_o} \right)$$

$$= W_o \sqrt{1 + \frac{V_R}{V_o}}$$

$$\therefore \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right)} V_o = W_o$$

$$Q_J = A \sqrt{2\epsilon_s q \left( \frac{N_A N_D}{N_A + N_D} \right) \cdot (V_o + V_R)}$$

$$= A \sqrt{2\epsilon_s q \left( \frac{N_A N_D}{N_A + N_D} \right) V_o \cdot \left( 1 + \frac{V_R}{V_o} \right)}$$

$$= A \sqrt{2\epsilon_s q \left( \frac{N_A N_D}{N_A + N_D} \right) V_o \cdot \left( 1 + \frac{V_R}{V_o} \right)}$$

$$= Q_{JO} \sqrt{1 + \frac{V_R}{V_o}}$$

$$\therefore A \sqrt{2\epsilon_s q \left( \frac{N_A N_D}{N_A + N_D} \right) V_o} = Q_{JO}$$

1.76

$$I_s = A q n_i^2 \left( \frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$

$$A = 200 \mu\text{m}^2 = 200 \times 10^{-8} \text{ cm}^2$$

$$I_s = 200 \times 10^{-8} \times 1.6 \times 10^{-19} \times (1.5 \times 10^{10})^2$$

$$\frac{10}{5 \times 10^{-4} \times 10^{17}} + \frac{18}{10 \times 10^{-14} \times 10^{16}}$$

$$= 1.44 \times 10^{-6} \text{ A}$$

$$I \cong I_s e^{\frac{V}{V_T}}$$

$$= 1.44 \times 10^{-16} \times e^{700/25.9}$$

$$\cong 79 \mu\text{A}$$

1.77

$$n_i = BT^{3/2} e^{-E_0/(2kT)}$$

At 300 K,

$$n_i = 7.3 \times 10^{15} \times (300)^{3/2} \times e^{-1.12/(2 \times 8.62 \times 10^{-3} \times 300)}$$

$$= 1.4939 \times 10^{10} / \text{cm}^2$$

$$n_i^2 (\text{at } 300 \text{ K}) = 2.232 \times 10^{20}$$

At 305 K,

$$n_i = 7.3 \times 10^{15} \times (305)^{3/2} \times e^{-1.12/(2 \times 8.62 \times 10^{-3} \times 305)}$$

$$= 2.152 \times 10^{10}$$

$$n_i^2 (\text{at } 305 \text{ K}) = 4.631 \times 10^{20}$$

$$\text{so } \frac{n_i^2 (\text{at } 305 \text{ K})}{n_i^2 (\text{at } 300 \text{ K})} = 2.152$$

1.78

$$I = Aq n_i^2 \left( \frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right) (e^{\frac{V}{V_T}} - 1)$$

$$\text{So } I_p = Aq n_i^2 \frac{D_p}{L_p N_D} (e^{\frac{V}{V_T}} - 1)$$

$$I_n = Aq n_i^2 \frac{D_n}{L_n N_A} (e^{\frac{V}{V_T}} - 1)$$

For  $p^+ - n$  junction  $N_A \gg N_D$

$$\therefore I \cong I_p = Aq n_i^2 \frac{D_p}{L_p N_D} (e^{\frac{V}{V_T}} - 1)$$

For this case

$$I_s \cong Aq n_i^2 \frac{D_p}{L_p N_D} = 10^4 \times 10^{-8} \text{ cm}^2 \times 1.6 \times 10^{-19}$$

$$\times (1.5 \times 10^{10})^2 \frac{10}{10 \times 10^{-4} \times 10^{16}}$$

$$= 3.6 \times 10^{-15} \text{ A}$$

$$I = I_s (e^{\frac{V}{V_T}} - 1) = 0.5 \times 10^{-3}$$

$$3.6 \times 10^{-15} \left( e^{\frac{V}{(25.9 \times 10^{-3})}} - 1 \right) = 0.5 \times 10^{-3}$$

$$\Rightarrow V = 0.6645 \text{ V}$$

$$C_J = \frac{C_{J0}}{\left(1 + \frac{V_R}{V_0}\right)^m}$$

$$\text{For } V_R = 1 \text{ V}, C_J = \frac{0.6 \text{ pF}}{\left(1 + \frac{1}{0.75}\right)^{\frac{1}{3}}} \\ = 0.45 \text{ pF}$$

$$\text{For } V_R = 10 \text{ V}, C_J = \frac{0.6 \text{ pF}}{\left(1 + \frac{10}{0.75}\right)^{\frac{1}{3}}} \\ = 0.25 \text{ pF}$$

1.80

$$C_d = \left(\frac{\tau_T}{V_T}\right) I$$

$$10 \text{ pF} = \left(\frac{\tau_T}{25.9 \times 10^{-3}}\right) \times 1 \times 10^{-3}$$

$$\tau_T = 10 \times 10^{-12} \times 25.9 \\ = 259 \text{ pS}$$

For  $I = 0.1 \text{ mA}$

$$C_d = \left(\frac{\tau_T}{V_T}\right) \times I \\ = \left(\frac{259 \times 10^{-12}}{25.9 \times 10^{-3}}\right) \times 0.1 \times 10^{-3} \\ = 1 \text{ pF}$$

1.81

$$\tau_p = \frac{L_p^2}{D_p} = \frac{(10 \times 10^{-4})^2}{10}$$

$$\text{note } 1 \mu\text{m} = 10^{-4} \text{ cm}$$


$$= 100 \text{ ns}$$

$$Q_p = \tau_p I_p \\ = 100 \times 10^{-9} \times 0.2 \times 10^{-3} \\ = 20 \times 10^{-12} \text{ C}$$

$$C_d = \left(\frac{\tau_p}{V_T}\right) I \\ = \left(\frac{100 \times 10^{-9}}{25.9 \times 10^{-3}}\right) \times 0.2 \times 10^{-3} \\ = 772 \text{ pF}$$

1.82

a.

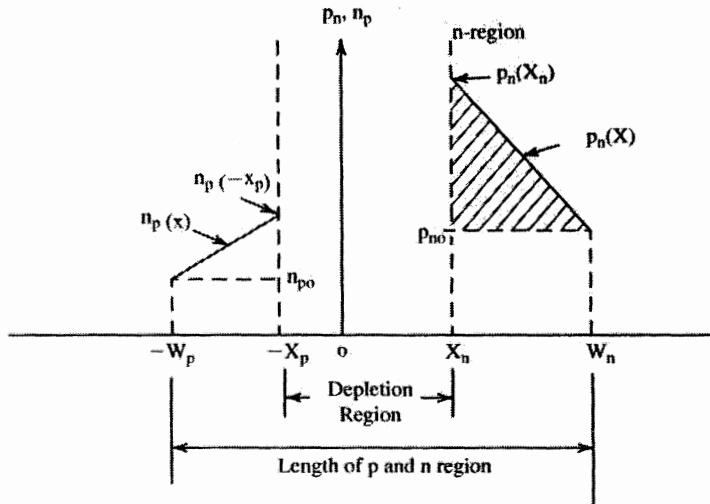

b. The current  $I = I_p + I_n$

Find current component  $I_p$

$$p_n(x_n) = p_{no} e^{V/V_T} \text{ and } p_{no} = \frac{n_i^2}{N_D}$$

$$I_p = AJ_p = AqD_p \frac{dp}{dx}$$

$$\frac{dp}{dx} = \frac{p_n(x_n) - p_{no}}{W_n - X_n} = \frac{p_{no} e^{V/V_T} - p_{no}}{W_n - X_n}$$

$$= p_{no} \frac{(e^{V/V_T} - 1)}{W_n - X_n}$$

$$= \frac{n_i^2}{N_D} \frac{(e^{V/V_T} - 1)}{W_n - X_n}$$

$$\therefore I_p = AqD_p \frac{dp}{dx}$$

$$= Aqn_i^2 \frac{D_p}{(W_n - X_n)N_D} \times (e^{V/V_T} - 1)$$

Similarly

$$I_n = Aqn_i^2 \frac{D_n}{(W_p - X_p)N_A} \times (e^{V/V_T} - 1)$$

$$I = I_p + I_n$$

$$= Aqn_i^2 \left[ \frac{D_p}{(W_n - X_n)N_D} + \frac{D_n}{(W_p - X_p)N_A} \right]$$

$$(e^{V/V_T} - 1)$$

The excess charge,  $Q_p$ , can be obtained by multiplying the area of the shaded triangle of the  $p_n(x)$  distribution graph by  $Aq$ .

$$Q_p = Aq \times \frac{1}{2} [p_n(X_n) - p_{no}](W_n - X_n)$$

$$= \frac{1}{2} Aq [p_{no} e^{V/V_T} - p_{no}] (W_n - X_n)$$

$$= \frac{1}{2} Aq p_{no} + (e^{V/V_T} - 1)(W_n - X_n)$$

$$= \frac{1}{2} \frac{(W_n - X_n)^2}{D_p} \cdot I_p$$

$$\approx \frac{1}{2} \frac{W_n^2}{D_p} \cdot I_p \text{ for } W_n \gg X_p$$

$$\text{c. } C_d = \frac{dQ}{dV} = \tau_T \frac{dI}{dV}$$

$$\text{But } I = I_S (e^{V/V_T} - 1)$$

$$\frac{dI}{dV} = \frac{I_S e^{V/V_T}}{V_T}$$

$$\approx \frac{I}{V_T}$$

$$\text{so } C_d = \tau_T \cdot \frac{I}{V_T}$$

$$\text{d. } C_d = \frac{1}{2} \frac{W_n^2}{10} \frac{1 \times 10^{-3}}{25.9 \times 10^{-3}} = 8 \times 10^{-12} \text{ F}$$

Solve for  $W_n$

$$W_n = 63.25 \mu\text{m}$$

2.1

$$V_o = A V_+ \rightarrow A = \frac{V_o}{V_+} = \frac{4}{4/100} = 100 \quad \frac{V_o}{V_+} = \frac{1K\Omega}{1M\Omega + 1K\Omega} = \frac{4}{100}$$

2.2

The voltage at the positive input has to be -3.000 V.

$$V_+ = -3.020 \text{ V}, A = \frac{V_o}{(V_+ - V_2)} = \frac{-2}{-3.020 - (-3)} = 100$$

2.3

#	$v_1$	$v_2$	$v_d = v_2 - v_1$	$v_o$	$v_o/v_d$
1	0.00	0.00	0.00	0.00	-
2	1.00	1.00	0.00	0.00	-
3	(a)	1.00	(b)	1.00	
4	1.00	1.10	0.10	10.1	101
5	2.01	2.00	-0.01	-0.99	99
6	1.99	2.00	0.01	1.00	100
7	5.10	(c)	(d)	-5.10	

experiments 4,5,6 show that the gain is approximately 100 V/V. The missing entry for experiment #3 can be predicted as follows:

$$(b) v_d = \frac{v_o}{A} = \frac{1.00}{100} = 0.01 \text{ V.}$$

$$(a) v_1 = v_2 - v_d = 1.00 - 0.01 = 0.99 \text{ V}$$


The missing entries for experiment #7:

$$(d) v_d = \frac{-5.10}{100} = -0.051 \text{ V}$$

$$(c) v_1 = v_2 + v_d = 5.10 - 0.051 = 5.049 \text{ V}$$

All the results seem to be reasonable.

2.4

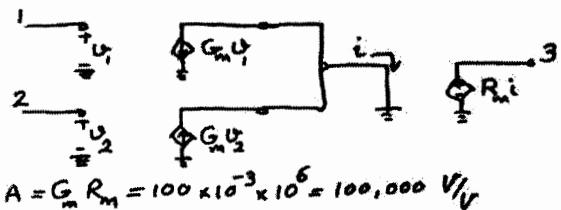

$$A = G_m R_m = 100 \times 10^{-3} \times 10^6 = 100,000 \text{ V/V}$$

2.5

$$v_{cm} = 1 \nu \sin(2\pi 60)t = \frac{1}{2}(v_1 + v_2)$$

$$v_d = 0.01 \sin(2\pi 1000)t = v_1 - v_2$$

$$v_1 = v_{cm} - v_d/2 = \sin(120\pi)t - 0.005 \sin 2000\pi t$$

$$v_2 = v_{cm} + v_d/2 = \sin 120\pi t + 0.005 \sin 2000\pi t$$

2.6

Circuit	$v_o/v_i (\text{V/V})$	$R_{in} (\text{k}\Omega)$
a	$\frac{-100}{10} = -10$	10
b	-10	10
c	-10	10
d	-10	10


virtual ground no current in  $10 \text{ k}\Omega$

2.7


closed loop gain =  $-1 \text{ V/V}$ . for  $V_i = 5 \text{ V} \Rightarrow V_o = -5 \text{ V}$   
 Gain would be in the range of  $\frac{-0.95}{1.05}$  to  $\frac{-1.05}{0.95}$ :  $-0.9 < G < -1.1$   
 for  $V_i = 5 \Rightarrow -45 < V_o < -5.5 \text{ V}$

2.8


There are four possibilities:

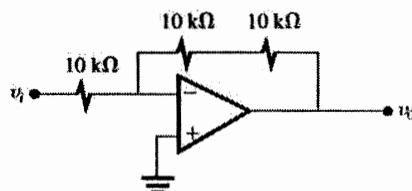

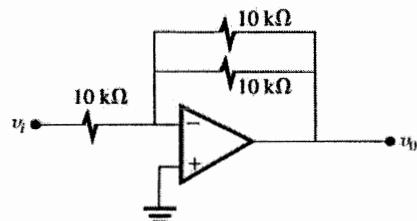
$$\frac{v_o}{v_i} = -2 \text{ V/V} \quad R_{in} = 10 \text{ k}\Omega$$


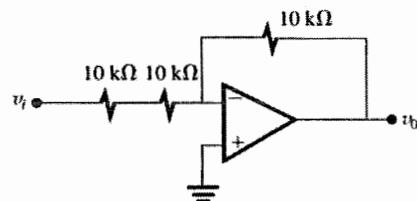
$$\frac{v_o}{v_i} = -0.5 \text{ V/V} \quad R_{in} = 10 \text{ k}\Omega$$


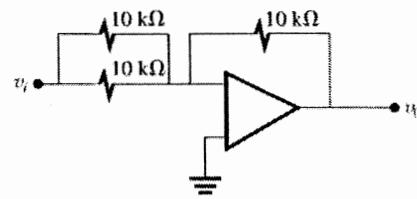
$$\frac{v_o}{v_i} = -0.5 \text{ V/V} \quad R_{in} = 20 \text{ k}\Omega$$



$$\frac{v_o}{v_i} = -2 \text{ V/V} \quad R_{in} = 5 \text{ k}\Omega$$

2.9


- |                 |                 |
|-----------------|-----------------|
| a. G = -1 V/V   | b. G = -10 V/V  |
| c. G = -0.1 V/V | d. G = -100 V/V |
| e. G = -10 V/V  |                 |

2.10

$$\frac{v_o}{v_i} = -5 = -\frac{R_2}{R_1} \Rightarrow R_2 = 5R_1$$

$$R_1 + R_2 = 120 \text{ k}\Omega \Rightarrow 5R_1 + R_1 = 120 \text{ k}\Omega \Rightarrow$$
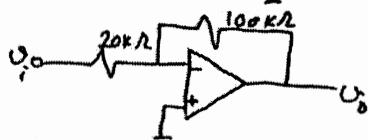
$$R_1 = 20 \text{ k}\Omega \Rightarrow R_2 = 100 \text{ k}\Omega$$



2.11

$$20 \log|G| = 26 \text{ dB} \Rightarrow G = 19.95 \frac{v_o}{v_i} = \frac{v_o}{v_i} = -\frac{R_2}{R}$$

$$\Rightarrow R_2 = 19.95 R_1 \leq 10 \text{ M}\Omega$$

For largest possible input resistance, select  
 $R_2 = 10 \text{ M}\Omega \Rightarrow R_1 \approx 500 \text{ k}\Omega$   
 $R_{in} = 500 \text{ k}\Omega$

2.12



$$G = \frac{v_o}{v_i} = \frac{-R_2}{R_1} = \frac{-100}{10} = -10$$


$$v_{low} = 10 \text{ V}, v_{high} = 0, v_{avg} = -5 \text{ V}$$

2.13

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \Rightarrow v_o = -1 \times \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} = 10 \text{ V}$$

$$i_2 = \frac{v_o}{2 \text{ k}\Omega} = 5 \text{ mA}$$
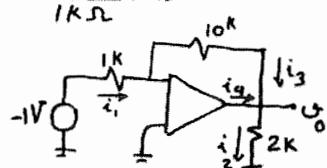
$$i_1 = i_3 = \frac{v_o}{10 \text{ k}\Omega} = 1 \text{ mA}$$



$i_4 = i_2 - i_3 = 4 \text{ mA}$  This additional current comes from the output of the op-amp.

2.14

$$|Gain| = \frac{R_2}{R_1} = \frac{R_2 (1+x/100)}{R_1 (1+x/100)} \approx \frac{R_2}{R_1} (1 \pm \frac{2x}{100})$$


$\Rightarrow 2x\%$  is the tolerance on the closed loop gain ( $G$ ).

$$G = -100 V/V, x=5 \Rightarrow -110 < G < -90$$

or more precisely:  $-100 \times \frac{105}{95} < G < -100 \frac{95}{105}$

$$-110.5 < G < -90.5$$

2.15

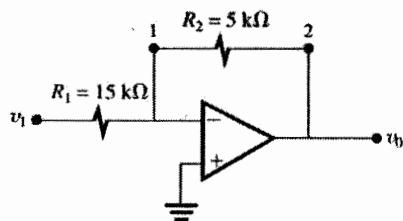

$$G = \frac{v_o}{v_i} = \frac{-R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = \frac{5}{15}$$

$$v_1 = 0V, v_2 = v_o = 5V$$

For  $\pm 1\%$  on  $R_1, R_2$ :  $R_1 = 15 \pm 0.15 \text{ k}\Omega$

$$R_2 = 5 \pm 0.05 \text{ k}\Omega$$

$$v_o = v_i \frac{-R_2}{R_1} = 15 \frac{R_2}{R_1} \Rightarrow 15 \times \frac{4.95}{15.15}$$

$$\leq v_o \leq 15 \times \frac{5.05}{14.85}$$

$$\Rightarrow 4.9 \text{ V} \leq v_o \leq 5.1 \text{ V}$$

$$\text{For } v_i = -15 \pm 0.15 \text{ V} \quad 14.85 \times \frac{4.95}{15.15}$$

$$\leq v_o \leq 15.15 \times \frac{5.05}{14.85}$$

$$\Rightarrow 4.85 \text{ V} \leq v_o \leq 5.15 \text{ V}$$

2.16

2.16

$$V_i = -\frac{V_o}{A} = -\frac{V_o}{200}$$


$$\frac{V_o}{V_i} = 50 V/V$$

$$\frac{V_i - (-\frac{V_o}{A})}{R_1} = \frac{(-\frac{V_o}{A} - V_o)}{100k\Omega} \Rightarrow R_1 = 100k\Omega \times \frac{\frac{V_o}{200} - \frac{V_o}{50}}{\frac{-1V_o}{200} - V_o}$$

$$\Rightarrow R_1 = 100k \times \frac{3}{201} = 1.49k\Omega$$

Shunt Resistor  $R_a$ :  $R_a \parallel 2k\Omega = 1.49k\Omega$
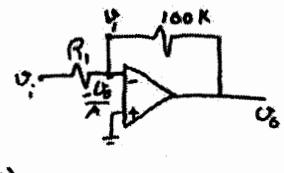
$$\frac{R_a \times 2}{R_a + 2} = 1.49 \Rightarrow R_a = 5.84k\Omega$$




2.17

a)

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \Rightarrow -100 V/V = -\frac{R_2}{1k\Omega} \Rightarrow R_2 = 100k\Omega$$

b)  $A = 1000 V/V$

$$V_i = -\frac{V_o}{A}$$

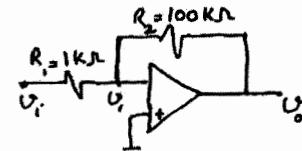

$$\frac{V_i - V_o}{R_1} = \frac{V_i - V_o}{R_2}$$

$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + (1 + \frac{R_2}{R_1})/A} = \frac{-100}{1 + \frac{100}{1000}} = -90.8 V/V$$

$$\Rightarrow \frac{V_o}{V_i} = 90.8 V/V$$

c) Assume  $R'_1 = R_x \parallel R_1$  when  $R_1 = 1k\Omega$

$$\frac{V_o}{V_i} = 100 V/V$$

$$\frac{V_i - V_o}{R'_1} = \frac{V_i - V_o}{R_2} \Rightarrow R'_1 = R_2 \times \left( \frac{V_o}{100} - \frac{-V_o}{1000} \right) / \left( \frac{-V_o}{1000} - V_o \right)$$

$$R'_1 = \frac{1 - 0.1}{1.001} = 0.899 k\Omega = \frac{R_1 R_x}{R_1 + R_x} = \frac{R_x}{1 + R_x}$$

$$\Rightarrow R_x = 8.9 k\Omega \approx 8.87 k\Omega \pm 1\%$$

2.18

Voltage of the inverting input terminal

will vary from  $\frac{-10V}{1000}$  to  $\frac{+10V}{1000}$ . Thus the virtual ground will depart from the ideal voltage of zero by a maximum of  $\pm 10mV$ .

$$v_o = -A v_- = v_- - i_i R_2$$

$$i_i R_2 = v_- (1 + A)$$


$$v_- = \frac{i_i R_2}{1 + A}$$

$$\text{Again } v_i = i_i R_1 + v_-$$

$$= i_i R_1 + i_i \frac{R_2}{1 + A}$$

$$\text{So } R_{in} = \frac{v_i}{i_i} = R_1 + \frac{R_2}{A + 1}$$

2.19

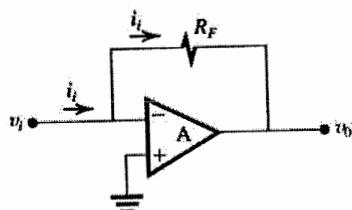

a) For  $A = \infty$ :  $v_o = 0$

$$v_o = -i_i R_F$$

$$R_m = \frac{v_o}{i_i} = -R_F$$


$$R_{in} = \frac{v_i}{i_i} = 0$$

b) For A-finite:  $v_i = -\frac{v_o}{A}$ ,  $v_o = v_i - i_i R_F$

$$\Rightarrow v_o = \frac{-v_o}{A} - i_i R_F \Rightarrow R_m = \frac{v_o}{i_i} = -\frac{R_F}{1 + \frac{1}{A}}$$

$$R_i = \frac{v_i}{i_i} = \frac{R_F}{1 + A}$$

2.20

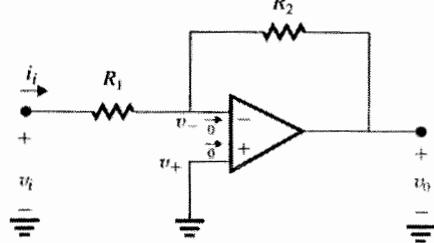

2.21

$$R_1' = R_1 \parallel R_c \quad G' = \frac{-R_2/R_1'}{1 + \frac{1 + R_2/R_1'}{A}}$$

In order for  $G' = G$ :

$$G = \frac{-R_2/R_1'}{1 + \frac{1 + R_2/R_1'}{A}} = \frac{-R_2}{R_1}$$

$$R_1' = \frac{R_1 R_c}{R_1 + R_c}$$

$$\Rightarrow \frac{R_1 + R_c}{R_1 R_c} = \frac{1}{R_1} \left( 1 + \frac{R_2 (R_1 + R_c)}{A R_1 R_c} \right)$$

$$(R_1 + R_c)A = A R_c + R_c + \frac{R_2}{R_1} (R_1 + R_c)$$

$$R_i A = R_c + G R_1 + G R_c$$

$$\frac{R_c}{R_1} = \frac{A - G}{1 + G}$$

2.22

$$G = \frac{-R_2/R_1}{1 + \frac{1 + R_2/R_1}{A}} \quad G_{nominal} = \frac{-R_2}{R_1}$$

$$\epsilon = \left| \frac{G - G_{nominal}}{G_{nominal}} \right| = \left| \frac{G}{G_{nominal}} - 1 \right|$$

$$\epsilon = \left| \frac{1}{1 + \frac{1 + R_2/R_1}{A}} - 1 \right| = \left| \frac{\frac{1 + R_2/R_1}{A}}{1 + \frac{1 + R_2/R_1}{A}} \right| = \frac{1}{\frac{A}{1 + \frac{R_2}{R_1}} + 1}$$

which can be rearranged to yield:

$$\frac{A}{1 + \frac{R_2}{R_1}} + 1 = \frac{1}{\epsilon} \Rightarrow A = (1 + \frac{R_2}{R_1})(\frac{1}{\epsilon} - 1)$$

$$\text{or } A = (1 - \frac{G_{nominal}}{\epsilon})(\frac{1}{\epsilon} - 1)$$

For  $G_{nominal} = -100 \frac{V}{V}$  and  $\epsilon = 10\% = 0.1$

$$A = (1 + 100)(\frac{1}{0.1} - 1) = 909 \frac{V}{V}$$

This is the minimum required value for A.

2.23

$$(a) \frac{\Delta|G|/|G|}{\Delta A/A} = \frac{1 + R_2/R_1}{A}$$

$$(b) \frac{\Delta|G|}{G} = 0.5\%, \frac{\Delta A}{A} = 50\%, \frac{R_2}{R_1} = 100$$

$$\frac{0.005}{.5} = \frac{1 + 100}{A}$$

$$A = \frac{101(.5)}{(.005)} = 10.1 \text{ k}$$

2.24

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_2} + \frac{R_4}{R_3}\right)$$

For  $R_1 = R_2 = R_4 = 1M\Omega \Rightarrow \frac{v_o}{v_i} = -(1 + 1 + \frac{1}{R_3})$

a)  $\frac{v_o}{v_i} = -10 \frac{V/V}{V/V} \Rightarrow 10 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \frac{1}{8} M\Omega = 125 k\Omega$

b)  $\frac{v_o}{v_i} = -100 \frac{V/V}{V/V} \Rightarrow 100 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \frac{1}{98} M\Omega = 10.2 k\Omega$

c)  $\frac{v_o}{v_i} = -2 \frac{V/V}{V/V} \Rightarrow 2 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \infty; \text{ eliminate } R_3.$

2.25

$$R_1/R_1 = 1000, R_2 = 100 k\Omega \Rightarrow R_1 = 1000 \Omega$$

$$a) R_m = R_t = 100 \Omega$$

$$b) \frac{v_o}{v_i} = \frac{-R_2}{R_1} \left(1 + \frac{R_3}{R_2} + \frac{R_4}{R_3}\right) = -1000$$

$$\text{If } R_2 = R_3 = R_4 = 100 \text{ K} \Rightarrow R_3 = \frac{100 \text{ K}}{1000 - 2} \approx 100 \Omega$$

$$R_m = R_t = 100 k\Omega$$

2.26

$$v_x = 0 - i, R_2, i_1 = \frac{v_x}{R_1} \Rightarrow v_{x2} = -v_1 \frac{R_2}{R_1}$$

$$\frac{v_{x2}}{v_x} = -\frac{R_2}{R_1}$$

$$v_x = v_0 \frac{R_2 || R_3}{R_2 || R_3 + R_4} = \frac{v_0 R_2 R_3}{R_2 R_3 + R_4 R_2 + R_4 R_3}$$

$$\frac{v_0}{v_x} = \frac{R_2 R_3 + R_2 R_4 + R_3 R_4}{R_2 R_3} = 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2}$$

$$\frac{v_0/v_x}{v_x/v_x} = \frac{v_0}{v_i} = \frac{(1 + R_4/R_3 + R_4/R_2)}{-R_1/R_2} \Rightarrow$$

$$\frac{v_0}{v_i} = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_3} + \frac{R_4}{R_2})$$

2.27

$$a) R_1 = R$$

$$R_2 = (R \parallel R) + \frac{R}{2} = \frac{R}{2} + \frac{R}{2} = R$$

$$R_3 = (R_2 \parallel R) + \frac{R}{2} = (R \parallel R) + \frac{R}{2} = R$$

$$R_4 = (R_3 \parallel R) + \frac{R}{2} = (R \parallel R) + \frac{R}{2} = R$$

$$b) v = RI = RI_1 \Rightarrow I_1 = I$$


$$I_{12} = I + I = 2I \Rightarrow v_1 + 2I \times \frac{R}{2} = RI_2$$

$$RI + RI = RI_2 \Rightarrow I_2 = 2I$$

$$I_{13} = I_2 + I_{12} = 4I \Rightarrow v_2 + 4I \times \frac{R}{2} = RI_3$$

$$R \times 2I + 4I \times \frac{R}{2} = RI_3 \Rightarrow I_3 = 4I,$$

$$I_4 = -(4I + 4I) I_4 = 8I$$

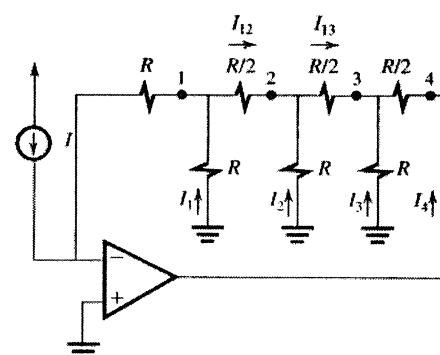

$$c) v_1 = I_1 R = -IR$$

$$v_2 = -I_2 R = -2IR$$

$$v_3 = -I_3 R = -4IR$$

$$v_4 = -I_4 R + I_4 \frac{R}{2} = -4IR - 8I \frac{R}{2} = -8IR$$

2.28

a)  $I_1 = \frac{1V}{10k\Omega} = 0.1mA$   
 $I_2 = I_1 = 0.1mA$ ,  $I_2 \times 10k\Omega = I_3 \times 100\Omega \Rightarrow I_3 = 10mA$   
 $V_x = 10mA \times 100\Omega = 1V$

b)  $V_x = R_L I_2 + V_o$ ,  $I_L = I_2 + I_3 = 10.1mA$   
 $1V = R_L \times 10.1mA + V_o$   
 $R_L = \frac{1-V_o}{10.1} \Rightarrow R_{max} = \frac{1-V_{min}}{10.1} = \frac{14}{10.1}$   
 $R_{max} =$

c)  $100\Omega \leq R_L \leq 1k\Omega$   
 $I_L$  stays fixed at 10.1mA  
 $V_o = V_x - R_L I_L = 1 - R_L \times 10.1 \Rightarrow -9.1 \leq V_o \leq -0.01$

2.29

a)  $\frac{i_L}{i_I} = 20 \Rightarrow i_L = 20 i_I$   
 $-10k\Omega \times i_I = R(i_I - i_L)$   
 $R = \frac{-10k\Omega \times i_I}{20 i_I - i_L} = 0.53k\Omega$

b)  $R_L = 1k\Omega \quad -12 \leq V_o \leq 12V$   
 $V_o = R_L i_L + 10k\Omega \times i_I = i_I (1k\Omega \times \frac{i_L}{i_I} + 10k\Omega)$   
 $V_o = i_I (1 \times 20 + 10) = 30 i_I$   
 $i_I = \frac{V_o}{30} \Rightarrow -12 \leq i_I \leq 12 \Rightarrow -0.4 \leq i_I \leq 0.4$  mA

c)  $R_L = \frac{V_o}{i_I} = \frac{0}{i_I} = 0$   
 $V_o = 0 \Rightarrow i = 0$   
 $\Rightarrow i_L = 1mA$   
From part a:  $i_L = 20 \times i_I = 20$  mA

2.30

$$R_f = 100 k\Omega - 10 \leq \frac{v_o}{v_i} \leq -1 \frac{V}{V}$$

$$\begin{aligned} R_i &= R_f = 100 k\Omega \\ \frac{v_o}{v_i} &= \frac{-R_2(R_4 + R_2 + 1)}{R_1(R_3 + R_2)} \\ R_4 &= 0 \Rightarrow \frac{v_o}{v_i} = \frac{-R_2}{R_1} = -1 \Rightarrow R_2 = 100 k\Omega \\ R_4 &= 10 k\Omega \Rightarrow \frac{v_o}{v_i} = -10 \\ &= -1 \times \left( \frac{10 k\Omega}{R_3} + \frac{10 k\Omega}{100 k\Omega} + 1 \right) \\ &+ 10 = \left( \frac{10}{R_3} + 1.1 \right) \Rightarrow R_3 = 1.12 k\Omega \end{aligned}$$

Potentiometer in the middle:

$$\begin{aligned} \frac{v_o}{v_i} &= -1 \left( \frac{5}{5 + R_3} + \frac{5}{100} + 1 \right) \\ \frac{v_o}{v_i} &= -1.87 V/V \end{aligned}$$

2.31

$$\begin{aligned} U_1 &= \frac{100k\Omega}{100k\Omega + 100k\Omega} U_1 + \frac{100k\Omega}{100k\Omega + 100k\Omega} U_2 + \frac{100k\Omega}{100k\Omega + 100k\Omega} U_3 \\ U_2 &= \left( \frac{50k}{100k} U_1 + \frac{50k}{100k} U_2 + \frac{50k}{100k} U_3 \right) \\ U_3 &= - \left( U_1 + \frac{U_2}{2} \right) \quad U_1 = 3, U_2 = -3 \Rightarrow U_3 = -1.5V \end{aligned}$$

2.32

We choose the weighted summer configuration.

$$U_o = -[4U_1 + \frac{U_2}{3}]$$


$$i_1 = \frac{U_1}{R_1}, \quad i_2 = \frac{U_2}{R_2}$$

$$i_1, i_2 < 0.1 \text{ mA} \text{ for } U_1, U_2 = 1V$$

$$R_1, R_2 \geq 10k\Omega$$

$$\frac{R_F}{R_1} = 4, \text{ if } R_1 = 10k\Omega \Rightarrow R_F = 40k\Omega$$
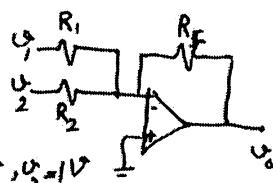
$$\frac{R_F}{R_2} = \frac{1}{3} \Rightarrow R_2 = 120k\Omega$$



2.33

$$v_o = -(2v_1 + 4v_2 + 8v_3)$$

$$R_1, R_2, R_3 \geq 10k\Omega$$

$$\frac{R_F}{R_1} = 2, \frac{R_F}{R_2} = 4, \frac{R_F}{R_3} = 8$$

$$R_1 = 10k\Omega \Rightarrow R_F = 80k\Omega$$

$$R_2 = 20k\Omega$$

$$R_3 = 40k\Omega$$

2.35


$$v_o = v_1 + 2v_2 - 3v_3 - 4v_4:$$

For a weighted summer circuit:

$$v_o = v_1 \frac{R_a R_c}{R_1 R_b} + v_2 \frac{R_a R_c}{R_2 R_b} - v_3 \frac{R_c}{R_3} - v_4 \frac{R_c}{R_4}$$

$$\frac{R_a}{R_1} = \frac{R_c}{R_b} = 1, \frac{R_a}{R_2} = \frac{R_c}{R_b} = 1, \frac{R_c}{R_3} = 3, \frac{R_c}{R_4} = 4$$

assume:

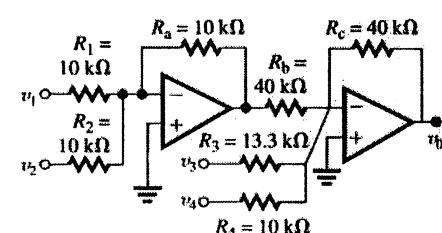

$$R_4 = 10k\Omega \Rightarrow R_c = 40k\Omega \Rightarrow R_3 = \frac{40}{3} = 13.3k\Omega$$

$$\frac{R_a}{R_1} = \frac{40}{10} = 4, \frac{R_a}{R_2} = \frac{40}{10} = 4$$

$$R_b = 40k\Omega, \quad R_1 = R_2 = R_a = 10k\Omega$$

2.36

$$U_1 = 3 \sin(2\pi \times 60t) + 0.01 \sin(2\pi \times 1000t)$$

$$U_2 = 3 \sin(2\pi \times 60t) - 0.01 \sin(2\pi \times 1000t)$$

$$\text{we want to have: } U_o = 10U_1 - 10U_2$$

2.34

The output signal should be:

$$U_o = -5 \sin \omega t - 5$$


If we assume:  $U_1 = 5 \sin \omega t$

$$U_2 = 2V \quad \left\{ \begin{array}{l} U_o = -U_1 + 2.5U_2 \\ U_o = -5 \sin \omega t - 5 \end{array} \right.$$

In a weighted summer configuration:

$$\frac{R_F}{R_1} = +1, \quad \frac{R_F}{R_2} = 2.5$$

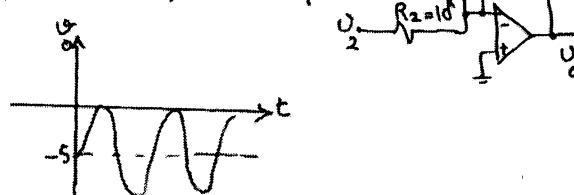
$$R_2 = 10k\Omega \Rightarrow R_F = 25k\Omega = R_1$$



$$U_o = U_1 \frac{R_a}{R_1} \frac{R_c}{R_b} - U_2 \frac{R_c}{R_3}$$

$$\frac{R_a}{R_1} = \frac{R_c}{R_b} = 10 \Rightarrow \frac{R_c}{R_3} = 10, \text{ if } R_3 = 10k\Omega \Rightarrow R_c = 100k\Omega$$
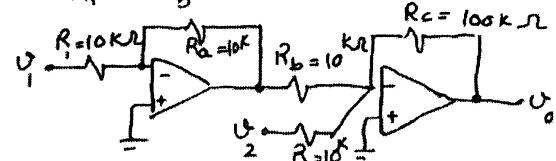
$$\Rightarrow \frac{R_a}{R_1} \times \frac{100k\Omega}{R_2} = 10 \Rightarrow R_a = R_1 = R_2 = 10k\Omega$$



$$U_o = 10U_1 - 10U_2 = 10 \times 0.02 \sin(2\pi \times 1000t)$$

$$U_o = 0.2 \sin(2\pi \times 1000t) - 0.2 \leq U_o \leq 0.2$$

2.37

This is a weighted summer circuit:

$$v_o = -\left(\frac{R_F}{R_0} v_0 + \frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 + \frac{R_F}{R_3} v_3\right)$$

we may write:  $v_0 = 5v \times a_0, v_2 = 5v \times a_2$   
 $v_1 = 5v \times a_1, v_3 = 5v \times a_3$

$$v_o = -R_F \left( \frac{50}{80 \text{ k}\Omega} + \frac{5}{40 \text{ k}\Omega} a_1 + \frac{5}{20 \text{ k}\Omega} a_2 + \frac{5}{10 \text{ k}\Omega} a_3 \right)$$

$$v_o = -R_F \left( \frac{a_0}{16} + \frac{a_1}{8} + \frac{a_2}{4} + \frac{a_3}{2} \right)$$

$$v_o = -\frac{R_F}{16} (2^0 a_0 + 2^1 a_1 + 2^2 a_2 + 2^3 a_3)$$

2.38


a)  $\frac{v_o}{v_i} = 1 = 1 + \frac{R_2}{R_1} \Rightarrow R_2 = 0, R_1 = 10 \text{ k}\Omega$

b)  $\frac{v_o}{v_i} = 2 = 1 + \frac{R_2}{R_1} \Rightarrow R_1 = R_2 = 10 \text{ k}\Omega$

c)  $\frac{v_o}{v_i} = 101 \text{ V/V} = 1 + \frac{R_2}{R_1} \Rightarrow \text{if } R_1 = 10 \text{ k}\Omega \Rightarrow R_2 = 1 \text{ M}\Omega$

d)  $\frac{v_o}{v_i} = 100 \text{ V/V} = 1 + \frac{R_2}{R_1} \Rightarrow \text{if } R_1 = 10 \text{ k}\Omega \Rightarrow R_2 = 990 \text{ k}\Omega$


2.39

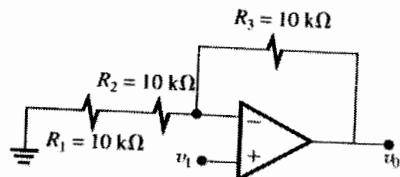

Short-circuit  $R_2$ :

$$\frac{v_o}{v_i} = 2$$

Short-circuit  $R_3$ :

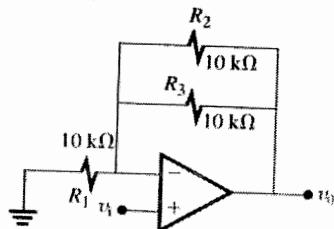

$$\frac{v_o}{v_i} = 1$$

2.40

$$v_+ = v_- = v_o = R \times i, i = 100 \mu\text{A} \text{ when}$$

$$v = 10\text{V}$$

$$\Rightarrow R = \frac{10}{0.1 \text{ mA}} = 100 \text{ k}\Omega$$

As indicated,  $i$  only depends on  $R$  and  $v$  and the meter resistance does not affect  $i$ .

2.41

$$v_o = v_{11} + 3v_{12} - 2(v_{13} + 3v_{14})$$

$$\frac{R_F}{R_{N3}} = 2 \text{ if } R_{N3} = 10 \text{ k}\Omega \Rightarrow R_F = 20 \text{ k}\Omega$$

$$\frac{R_F}{R_{N4}} = 6 \Rightarrow R_{N4} = \frac{20}{6} = 3.3 \text{ k}\Omega$$

$$R_N = R_{N3} \parallel R_{N4} = 10 \text{ k} \parallel 3.3 \text{ k} = 2.48 \text{ k}\Omega$$

$$\left(1 + \frac{R_F}{R_N}\right) \frac{R_P}{R_o} = 1 \Rightarrow \left(1 + \frac{20}{2.48}\right) \frac{R_P}{R_{P1}} = 1 \Rightarrow 9.06 \text{ } R_P = R_{P1}$$

$$R_P = R_{P1} \parallel R_{P2} \parallel R_{P3} \Rightarrow R_P$$

$$= \frac{1}{\frac{1}{R_{P1}} + \frac{1}{R_{P2}} + \frac{1}{R_{P3}}}$$

$$\left(1 + \frac{R_F}{R_N}\right) \frac{R_P}{R_{P2}} = 3 \Rightarrow 9.06 \frac{R_P}{R_{P2}} = 3 \Rightarrow R_{P2} = 3R_P$$

$$R_{P1} \parallel R_{P2} = \frac{9 \times 3R_P}{9 + 3} = 2.25R_P$$


$$R_P = 2.25R_P \parallel R_{P0}$$

$$\Rightarrow R_P + R_{P0} = 2.25R_{P0} \Rightarrow R_{P0} = 1.8R_P$$

$$R_P = 10 \text{ k}\Omega \Rightarrow R_{P0} = 18 \text{ k}\Omega$$

$$R_{P1} = 9 \times 10 \text{ k} = 90 \text{ k}\Omega$$
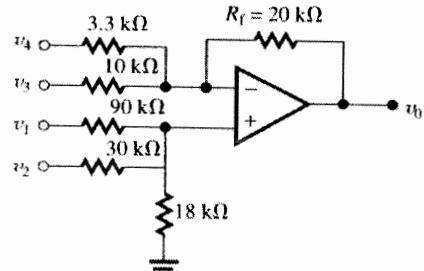
$$R_{P2} = 3 \times 10 \text{ k} = 30 \text{ k}\Omega$$



2.42

$$v_+ = v_I \frac{R_4}{R_3 + R_4} = v$$

$$\frac{v}{R_1} = \frac{v_o - v_+}{R_2} \Rightarrow v_o = v_+ \left( 1 + \frac{R_2}{R_1} \right)$$

From the two above equations:

$$\frac{v_o}{v_I} = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right) = \frac{1 + R_2/R_1}{1 + R_3/R_4}$$

2.43 Setting  $v_2 = 0$ , we obtain the

output component due to  $v_1$  as:

$$v_{o1} = -20 v$$

Setting  $v_1 = 0$ , we obtain the output component due to  $v_2$  as:

$$v_{o2} = v_2 \left( 1 + \frac{20R}{R} \right) \left( \frac{20R}{20R + R} \right) = 20 v_2$$

The total output voltage is:

$$v_o = v_{o1} + v_{o2} = 20(v_2 - v_1)$$

$$\text{For } v_1 = 10 \sin 2\pi \times 60t - 0.1 \sin (2\pi \times 1000t)$$

$$v_2 = 10 \sin 2\pi \times 60t + 0.1 \sin (2\pi \times 1000t)$$


$$v_o = 4 \sin (2\pi \times 1000t)$$

2.44

$$\frac{v_o}{v_i} = 1 + \frac{R_2}{R_1} = 1 + \frac{(1-x)}{x} = 1 + \frac{1}{x} - 1 = \frac{1}{x}$$

$$0 < x \leq 1 \rightarrow 1 < \frac{v_o}{v_i} \leq \infty$$


If we add a resistor on the ground path:

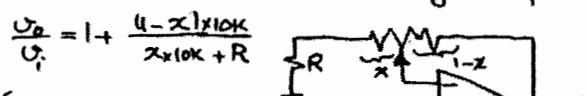

$$\text{Gain}_{\max} = 21 \text{ when}$$

$$x=0 \Rightarrow 21 = 1 + \frac{10k}{R} \Rightarrow R = \frac{10k}{20} = 0.5k\Omega$$


2.45

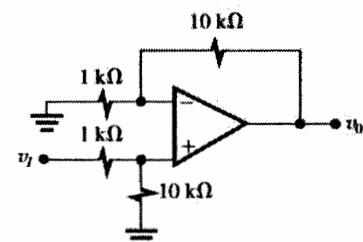

$$v_O = v_I \frac{10}{1 + 10} \left( 1 + \frac{10}{1} \right)$$

$$v_O = 10 v_I$$

2.46

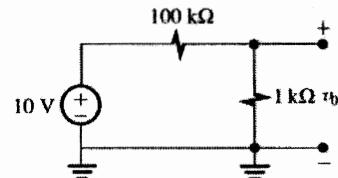


a) Source is connected directly.

$$v_O = 10 \times \frac{1}{101} = 0.099 V$$

$$i_L = \frac{v_O}{1 k\Omega} = \frac{0.099}{1} = 0.099 mA$$

Current supplied by the source is 0.099 mA.

b) inserting a buffer

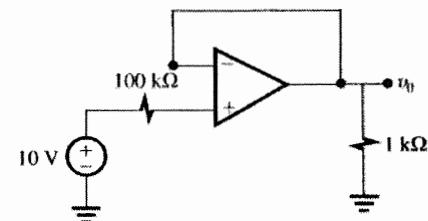


$$v_O = 10 V$$

$$i_L = \frac{10 V}{1 K} = 10 mA$$

current supplied by the source is 0.

The load current  $i_L$  comes from the power supply of the op-amp.

2.47

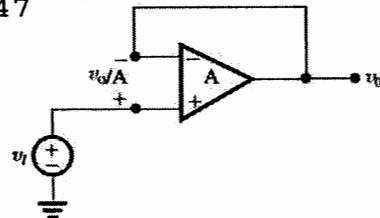

$$v_o = v_i - \frac{v_o}{A}$$

$$\frac{v_o}{v_i} = \frac{1}{1 + \frac{1}{A}}$$

error of Gain magnitude

$$\left| \frac{\frac{v_o}{v_i} - 1}{1} \right| = -\frac{1}{A+1}$$

$A(\frac{V}{V})$	1000	100	10
------------------	------	-----	----

$\frac{V_o(V)}{V_i(V)}$	0.999	0.990	0.909
Gain error	-0.1%	-1%	-9.1%

2.48

$$A = 50 \text{ V/V} \quad 1 + \frac{R_2}{R_1} = 10 \text{ V/V}$$

$$\text{if } R_1 = 10 \text{ k}\Omega \Rightarrow R_2 = 90 \text{ k}\Omega$$

$$G = \frac{v_o}{v_i} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1 + R_2/R_1}{A}}$$


$$G = \frac{1 + 98/10}{1 + \frac{1 + 90/10}{50}} = \frac{10}{1.2} = 8.33 \text{ V/V}$$

In order to compensate the gain drop, we can shunt a resistor with  $R_1$ .

Compensated:

$$R_{sh}: 10 = \frac{1 + \left( \frac{90}{10} + \frac{90}{R_{sh}} \right)}{1 + \frac{90 + 90}{10 + R_{sh}}} \Rightarrow$$
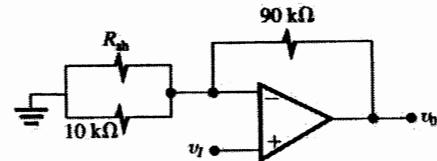
$$10 \times (510R_{sh} + 90R_{sh} + 900) \\ = 50 \times (10R_{sh} + 90R_{sh} + 900) \\ 100R_{sh} = 3600 \Rightarrow R_{sh} = 36 \text{ k}\Omega$$



If  $A = 100$  then:

$$G_{uncompensated} = \frac{1 + \frac{90}{10}}{1 + \frac{1 + 90/10}{100}} = \frac{10}{1.1} = 9.09 \text{ V/V}$$

$$G_{compensated} = \frac{1 + \frac{90}{10} + \frac{90}{36}}{1 + \frac{90 + 90}{100}} \\ = \frac{125}{1.125} = 11.1 \text{ V/V}$$

2.49

$$G = \frac{G_o}{1 + \frac{G_o}{A}}, \frac{G_o - G}{G_o} \times 100 = \frac{G_o/A \times 100}{1 + \frac{G_o}{A}} \leq x$$

$$\text{or } \frac{1 + \frac{G_o}{A}}{\frac{G_o}{A}} \geq \frac{100}{x} \Rightarrow \frac{A}{G_o} \geq \underbrace{\left( \frac{100}{x} - 1 \right)}_F$$

$$\Rightarrow A \geq G_o F \text{ where } F = \frac{100}{x} - 1 \approx \frac{100}{x}$$

x	0.01	0.1	1	10
F	$10^4$	$10^3$	$10^2$	10

Thus for:

x = 0.01: $G_o (\text{V/V})$	1	10	$10^2$	$10^3$	$10^4$
$A (\text{V/V})$	$10^4$	$10^5$	$10^6$	$10^7$	$10^8$

too high to be practical

x = 0.1: $G_o (\text{V/V})$	1	10	$10^2$	$10^3$	$10^4$
$A (\text{V/V})$	$10^3$	$10^4$	$10^5$	$10^6$	$10^7$

x = 1: $G_o (\text{V/V})$	1	10	$10^2$	$10^3$	$10^4$
$A (\text{V/V})$	$10^2$	$10^3$	$10^4$	$10^5$	$10^6$

x = 10: $G_o (\text{V/V})$	1	10	$10^2$	$10^3$	$10^4$
$A (\text{V/V})$	10	$10^2$	$10^3$	$10^4$	$10^5$

### 2.50

for non-inverting amplifier

$$G = \frac{G_o}{1 + \frac{G_o}{A}}, \epsilon = \frac{G_o - G}{G_o} \times 100$$

for inverting amplifier

$$G = \frac{G_o}{1 + \frac{1 - G_o}{A}}, \epsilon = \frac{G_o - G}{G_o} \times 100$$

case	$G_o$ (V/V)	$A(V/V)$ (V/V)	$G$ (V/V)	$\epsilon\%$
a	-1	10	-0.83	16
b	1	10	0.91	9
c	-1	100	-0.98	2
d	10	10	5	50
e	-10	100	-9	10
f	-10	1000	-9.89	1.1
g	+1	2	0.67	33

2.51 when potentiometer is set to the bottom:

$$v_o = v_+ = -15 + \frac{30 \times 20}{20 + 100 + 20} = -10.714 \text{ V}$$

when set to the top:

$$v_o = -15 + \frac{30 \times 20}{20 + 100 + 20} = 10.714 \text{ V}$$

$$\Rightarrow -10.714 \leq v_o \leq +10.714$$

pot has 20 turn, each turn:

$$\Delta v_o = \frac{2 \times 10.714}{20} = 1.07 \text{ V}$$

### 2.52

Notice that

$$\text{we have: } \frac{R_4}{R_3} = \frac{R_2}{R_1} = \frac{100}{10}$$

therefore

$$v_o = \frac{R_2}{R_1} v_{id} \Rightarrow A = \frac{R_2}{R_1} = 10 \text{ V/V}$$

$$R_{id} = 2R_1 = 20 \text{ k}\Omega$$

If  $\frac{R_2}{R_1}, \frac{R_4}{R_3}$  were different by  $\frac{1}{10}$ :

$$\frac{R_2}{R_1} = 0.99 \frac{R_2}{R_1}$$

### 2.53

If we assume  $R_3 = R_1, R_4 = R_2$ , then

$$R_{id} = 2R_1 \Rightarrow R_1 = \frac{20}{2} = 10 \text{ k}\Omega$$

a)  $A_d = \frac{R_2}{R_1} = 1 \text{ V/V} \Rightarrow R_2 = 10 \text{ k}\Omega$

$$R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$$

b)  $A_d = \frac{R_2}{R_1} = 2 \text{ V/V} \Rightarrow R_2 = 20 \text{ k}\Omega = R_4$

$$R_1 = R_3 = 10 \text{ k}\Omega$$

c)  $A_d = \frac{R_2}{R_1} = 100 \text{ V/V} \Rightarrow R_2 = 1 \text{ M}\Omega = R_4$

$$R_1 = R_3 = 10 \text{ k}\Omega$$

d)  $A_d = \frac{R_2}{R_1} = 0.5 \text{ V/V} \Rightarrow R_2 = 5 \text{ k}\Omega = R_4$


$$R_1 = R_3 = 10 \text{ k}\Omega$$

### 2.54


Considering that  $v_- = v_+$ :

$$v_1 + \frac{v_o - v_1}{2} = \frac{v_2}{2} \Rightarrow v_o = v_2 - v_1$$

$v_1$  only:  $R_I = \frac{v_1}{I} = R$

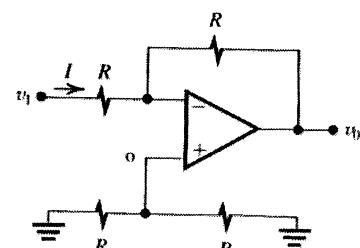


$v_2$  only:  $R_I = \frac{v_2}{I} = 2R$

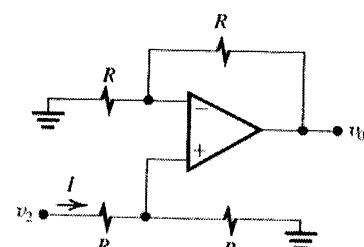

$v_S$  between 2 terminals:

$$R_I = \frac{v}{I} = 2R$$


$$v_+ = v_- = 0$$

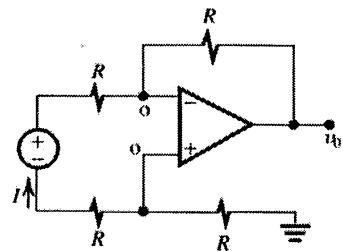


$v_3$  connected to both  $v_1$  &  $v_2$ :

$$R_I = \frac{v}{I} = R$$

$$v_+ = v_- = \frac{v_i}{2}$$

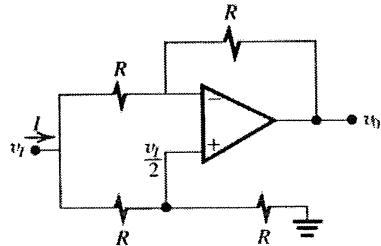

2.55

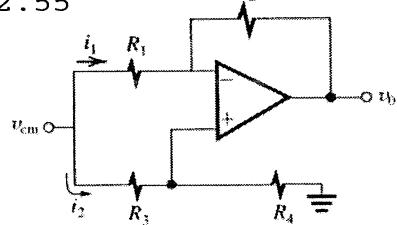

$$v_+ = v_{cm} \frac{R_4}{R_3 + R_4}$$

$$v_+ = v_-$$

$$i_2 = \frac{v_{cm}}{R_3 + R_4}$$

$$i_1 = \frac{v_{cm}}{R_1} - \frac{v_{cm} R_4}{R_3 + R_4} = \frac{1}{R_1} = \frac{v_{cm}}{R_1 R_3 + R_4}$$

$$i = i_1 + i_2 = \frac{v_{cm}}{R_1 R_3 + R_4} + \frac{v_{cm}}{R_3 + R_4}$$

if we replace  $\frac{R_4}{R_3}$  with  $\frac{R_2}{R_1}$ :  $\left( \frac{R_4}{R_3} = \frac{R_2}{R_1} \right)$

$$\frac{1}{R_I} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$$

$$\Rightarrow R_I = (R_1 + R_2) \parallel (R_3 + R_4)$$

2.56

$$A_{cm} = \frac{v_o}{v_{cm}} = \frac{R_4}{R_3 + R_4} \left( 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right)$$

The worst case is when  $A_{cm}$  has its maximum value.

$$A_{cm} = \frac{1}{\frac{R_3}{R_4} + 1} \left( 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right)$$

Max  $A_{cm} \Rightarrow \frac{R_3}{R_4}$  has to be at its minimum value and also  $\frac{R_4}{R_2}$  has to be minimum.

$$\frac{100-x}{100+x} \leq \frac{R_3}{R_4} \leq \frac{100+x}{100-x} \quad \frac{100-x}{100+2x} \leq \frac{R_2}{R_1} \leq \frac{100+x}{100-x}$$

$$\text{so if } \frac{R_3}{R_4} = \frac{100-x}{100+x} \text{ & } \frac{R_2}{R_1} = \frac{100-x}{100+x}$$

$$A_{cm \text{ Max}} = \frac{1}{\frac{100-x}{100+x} + 1} \left( 1 - \frac{100-x}{100+x} \frac{100-x}{100+x} \right)$$

$$A_{cm \text{ Max}} = \frac{1}{200} \frac{(100+x)^2 - (100-x)^2}{100+x} = \frac{2x}{100+x} \approx \frac{x}{50}$$

x	0.1	1	5
$A_{cm \text{ Max}}$	0.002	0.02	0.1

$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right|$ . Now we have to calculate  $A_d$  based on values we chose for  $R_1 - R_4$  that gave us  $A_{cm \text{ Max}}$ .

$$R_2 = R_3 = 100-x \quad R_1 = R_4 = 100+x$$

$V_o = V_{o1} + V_{o2}$  by applying superposition

$$V_{o1} = -\frac{R_2}{R_1} V_+ + V_2 \frac{R_4}{R_3 + R_4} \left( 1 + \frac{R_2}{R_1} \right)$$

$$V_{o2} = -\frac{100-x}{100+x} V_+ + V_2 \frac{100+x}{200} \left( 1 + \frac{100-x}{100+x} \right)$$

$$V_o = -\frac{100-x}{100+x} V_+ + V_2$$

if we consider  $\frac{100-x}{100+x} \approx 1 \Rightarrow \frac{V_o}{V_{id}} \approx 1$  Cont.

$$CMRR = 20 \log \frac{A_d}{A_{cm}} = 20 \log \frac{1}{\frac{1}{2} \epsilon_0} = 20 \log \frac{20}{\epsilon}$$

$\infty$	0.1	1	5
CMRR	54db	34db	20db

2.57

$$A_{cm} = \frac{R_3}{R_3 + R_4} \left( 1 - \frac{R_2 R_3}{R_1 R_4} \right)$$

In order to calculate  $A_d$ , we use Superposition principle:

$$v_o = v_{o1} + v_{o2} = \frac{-R_2}{R_1} v_1 + v_2 \frac{R_4}{R_3 + R_4} \left( 1 + \frac{R_2}{R_1} \right)$$

$$\text{then replace } v_1 = v_{cm} - \frac{v_d}{2}$$

$$v_2 = v_{cm} + \frac{v_d}{2}$$

$$v_o = -\frac{R_2}{R_1} v_{cm} + \frac{R_2}{R} v_{d/2} + v_{cm}$$

$$\frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_3}{R_4}} + \frac{v_o}{2} = \frac{1 + R_2/R_1}{1 + R_3/R_4}$$

$$v_o = \frac{R_2}{2R_1} \left[ 1 + \frac{R_1/R_2 + 1}{R_3/R_4 + 1} \right] v_d + \frac{R_2}{R_1} \left[ -1 + \frac{R_1/R_2 + 1}{R_3/R_4 + 1} \right] v_{cm}$$

Ad

$$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right| = 20 \log \frac{\frac{R_2}{2R_1} \left[ 1 + \frac{R_1/R_2 + 1}{R_3/R_4 + 1} \right]}{\frac{1}{R_1 + 1} \left( 1 - \frac{R_2 R_3}{R_1 R_4} \right)}$$

$$CMRR = 20 \log \left| \frac{\frac{1}{2R_1} \left[ 2 + \frac{R_1}{R_2} + R_3/R_4 \right]}{1 - \frac{R_2}{R_1} \cdot \frac{R_3}{R_4}} \right|$$

$$CMRR = 20 \log \left| \frac{1 + \frac{R_1}{2R_2} + \frac{1}{2R_2}}{\frac{R_1}{R_2} \cdot \frac{R_3}{R_4}} \right|$$

for worst case, minimum CMRR we have to maximize the denominator, which means:

$$R_1 = R_{1n}(1 + \epsilon) \quad R_3 = R_{3n}(1 - \epsilon)$$

$$R_2 = R_{2n}(1 - \epsilon) \quad R_4 = R_{4n}(1 + \epsilon)$$

$$\text{also } \frac{R_{2n}}{R_{1n}} = \frac{R_{4n}}{R_{3n}} = K$$

$$CMRR = 20 \log \left| k \frac{1 + \frac{1}{2K} \frac{1+\epsilon}{1-\epsilon} + \frac{1}{2K} \frac{1-\epsilon}{1+\epsilon}}{\frac{1+\epsilon}{1-\epsilon} - \frac{1-\epsilon}{1+\epsilon}} \right|$$

$$CMRR = 20 \log \left| \frac{k(1 - \epsilon^2) + (1 + \epsilon^2)}{4\epsilon} \right| \approx$$

$$20 \log \left| \frac{k+1}{4\epsilon} \right|$$

for  $\epsilon^2 \ll 1$ .

$$\text{if } k = A_{d\text{ ideal}} = 100, \epsilon = 0.01$$

$$CMRR = 20 \log \frac{101}{0.04} = 68 \text{ db}$$

2.58

$$A_{cm} = \frac{R_4}{R_3 + R_4} \left( 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right)$$


$$= \frac{100}{100 + 100} \left( 1 - \frac{100 \cdot 100}{100 \cdot 100} \right)$$

$$A_{cm} = 0$$

$$\text{Refer to 2.17: } \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

$$\Rightarrow A_d = \frac{R_2}{R_1} = 1$$

b) Since  $A_{cm} = 0$ ,

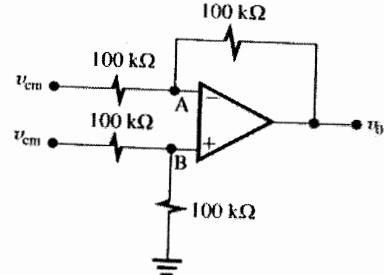

then if we apply  $V_{in}$  to  $V_o$  and  $V_{in}$ ,  $v_o = 0$ .

$$\text{Therefore, } V_A = \frac{v_{cm}}{100 + 100} = \frac{100}{200} = 0.5$$

$$V_A = \frac{v_{cm}}{2}$$

$$\text{Similarly, } v_B = \frac{v_{cm}}{2}$$

we know  $V_A = V_B$  and  $-2.5 \leq v_A \leq 2.5$

$$\Rightarrow -5 \leq v_{cm} \leq 5$$


c) we apply the Superposition principle to calculate  $A_{\text{d}}$

$v_o$  is the output voltage when  $v_{12} = 0$

$v_{o2}$  is the output voltage when  $v_{11} = 0$

$$v_o = v_{o1} + v_{o2}$$
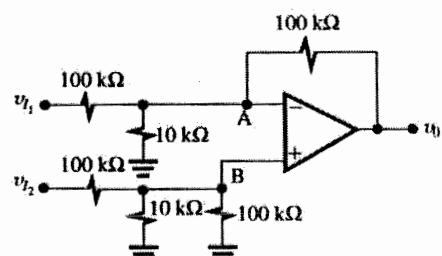
$$v_{o1} = \frac{-R_2}{R_1} v_{11} = -v_{11}$$




$$v_{o2} = v_{12} \frac{100 \text{ k}\Omega \parallel 10 \text{ k}\Omega}{100 \text{ k}\Omega \parallel 10 \text{ k}\Omega + 100}$$

$$\left(1 + \frac{100 \text{ k}\Omega}{100 \text{ k}\Omega \parallel 10 \text{ k}\Omega}\right)$$

$$v_{o2} = v_{12} \times 1$$

$$\Rightarrow v_o = v_{o1} + v_{o2} = -v_{11} + v_{12} \Rightarrow A_d = 1$$

Now we calculate  $A_{\text{cm}}$ :

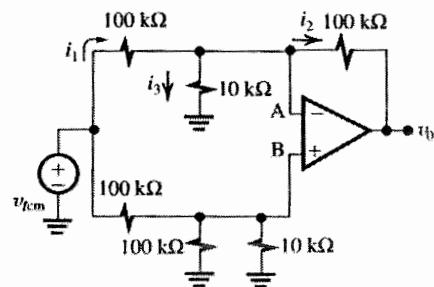

$$v_B = v_{\text{CM}} \frac{100 \text{ k}\Omega \parallel 10 \text{ k}\Omega}{100 \text{ k}\Omega \parallel 10 \text{ k}\Omega + 100 \text{ k}\Omega} \cdot v_A = v_B$$

$$i_1 = \frac{v_{\text{CM}} - v_A}{100 \text{ k}\Omega}$$

$$v_o = v_A - 100 \text{ k}\Omega \times i_2 \text{ and}$$

$$i_2 = i_1 - i_3 = i_1 - \frac{v_A}{10 \text{ k}\Omega}$$

$$v_o = v_A - 100 \text{ k}\Omega \times i_1 + 10 \times v_A$$

$$v_o = v_A - v_{\text{CM}} + v_A + 10 \times v_A$$

$$v_A = v_B \Rightarrow v_o$$

$$= v_{\text{CM}} \left( -1 + 12 \frac{100 \text{ k}\Omega \parallel 10 \text{ k}\Omega}{(100 \text{ k}\Omega \parallel 10 \text{ k}\Omega) + 100 \text{ k}\Omega} \right)$$

$$\frac{v_o}{v_{\text{CM}}} = A_{\text{cm}} = 0$$


Now we calculate  $v_{\text{CM}}$  range:

$$-25 \leq v_B \leq 2.5 \Rightarrow$$

$$-2.5 < v_{\text{CM}} \times \frac{100 \text{ k}\Omega \parallel 10 \text{ k}\Omega}{(100 \text{ k}\Omega \parallel 10 \text{ k}\Omega) + 100 \text{ k}\Omega} < 2.5$$

$$-30 \text{ V} \leq v_{\text{CM}} \leq 30 \text{ V}$$

2.59

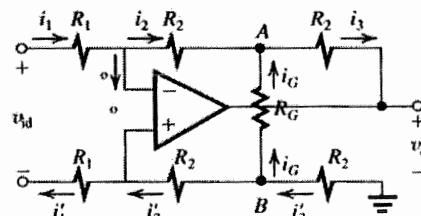

$v_+ = v_-$  so we can consider  $v_+$ ,  $v_-$  a virtual

$$\text{short: } i_1 = v_{id}/2R_1 \Rightarrow i_2 = \frac{v_{id}}{2R_1}$$

$$i_1' = i_2' = \frac{v_{id}}{2R_1}$$

then:

$$i_2 R_2 + v_{AB} + i_2' R_2 = 0 \Rightarrow v_{AB} = -\frac{v_{id}}{R_1} R_2$$

$$i_G = \frac{v_{id}}{R_G} \times \frac{R_2}{R_1}$$

$$i_3 = i_2 + i_G = \frac{v_{id}}{2R_1} + \frac{v_{id}}{R_G} \frac{R_2}{R_1}$$

$$i_3' = i_G + i_2' = i_3$$

$$\Rightarrow v_o = -[i_3 R_2 + v_{BA} + i_3' R_2]$$

$$v_o = -[2i_3 R_2 + v_{BA}]$$

$$v_o = -\left[ \frac{2v_{id}}{2R_1} R_2 + 2v_{id} \frac{R_2}{R_1 R_G} + \frac{v_{id}}{R_1} R_2 \right]$$


$$\frac{v_o}{v_{id}} = A_d = -2 \frac{R_2}{R_1} \left[ 1 + \frac{R_2}{R_G} \right]$$

2.60

a)  $A_d = \frac{R_2}{R_1} = 1$ . Connect c


and o together

a)

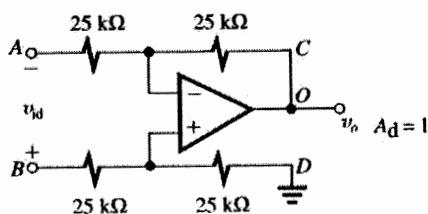


b)  $\frac{v_o}{v_i} = -1 \text{ V/V}$

i)


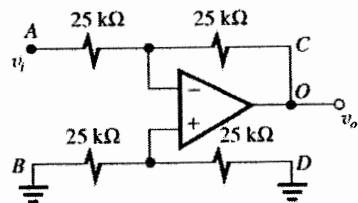


ii)  $\frac{v_o}{v_i} = +1 \text{ V/V}$

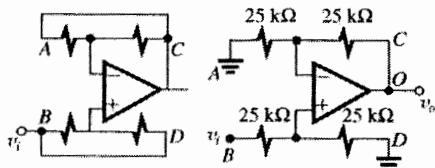

The circuit on the left ideally has infinite input resistance

iii)  $\frac{v_o}{v_i} = +2 \text{ V/V}$

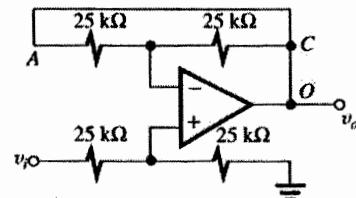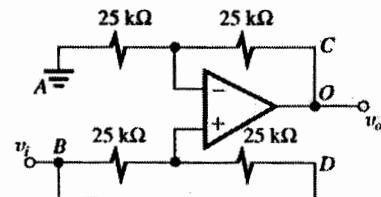


iv)  $\frac{v_o}{v_i} = +\frac{1}{2} \text{ V/V}$

$$v_+ = \frac{v_i}{2} = v_o$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{1}{2}$$

2.61

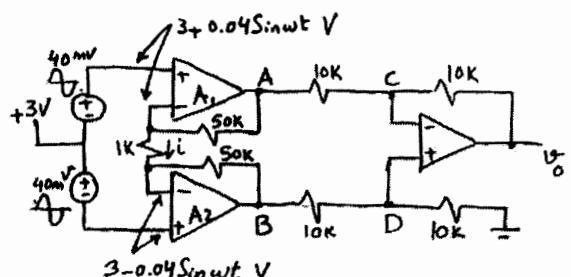

$$i = \frac{3+0.04\sin\omega t - (3-0.04\sin\omega t)}{1K} = 0.08\sin\omega t, \text{ mA}$$

$$v_A = 3+0.04\sin\omega t + 50K \cdot i = 3+4.04\sin\omega t, \text{ V}$$

$$v_B = 3-0.04\sin\omega t - 50K \cdot i = 3-4.04\sin\omega t, \text{ V}$$

$$v_C = v_D = \frac{1}{2} v_B = 1.5 - 2.02\sin\omega t, \text{ V}$$

$$v_o = v_B - v_A = -8.08\sin\omega t, \text{ V}$$

2.62 a.

The gain of the first stage is:  $\left(1 + \frac{R_2}{R_1}\right) = 101$ . If

the opamps of the first stage saturate at  $\pm 14$  V:

$$-14 \leq v_i \leq +14 \Rightarrow -14 \leq 101 v_{\text{cm}} \leq +14$$

$$\Rightarrow -0.14 \leq v_{\text{cm}} \leq 0.14$$

As explained in the text, the disadvantage of circuit in Fig. 2.20a is that  $v_{\text{cm}}$  is amplified by a

gain equal to  $v_{\text{in}} \left(1 + \frac{R_2}{R_1}\right)$  in the first stage and

therefore a very small  $v_{\text{cm}}$  range is acceptable to avoid saturation.

b) In Fig. 2.20b, when  $v_{\text{cm}}$  is applied,  $v_o$  for both  $A_1$  &  $A_2$  is the same and therefore no current flows through  $2R_1$ . This means voltage at the output of  $A_1$  and  $A_2$  is the same as  $v_{\text{cm}}$ .

$$-14 \leq v_o \leq 14 \Rightarrow -14 \leq v_{\text{cm}} \leq 14$$

This circuit allows for bigger range of  $v_{\text{cm}}$ .

2.63

$$A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) = \frac{100\text{k}}{100\text{k}} \left(1 + \frac{100\text{k}}{5\text{k}}\right) = 21 \text{V/V}$$

$$A_{\text{cm}} = 0$$

$$\text{CMRR} = 20 \log \left| \frac{A_d}{A_{\text{cm}}} \right| = \infty$$

If all resistors are  $\pm 1\%$ :

$$A_d \approx 21$$

In order to calculate  $A_{\text{cm}}$ , apply  $V_{\text{cm}}$  to both inputs and note that  $v_{\text{cm}}$  will appear at both output terminals of the first stage. Now we can evaluate  $v_o$  by analyzing the second stage as was done in problem 2.65.

In P2.65 we showed that if each 100k resistor has  $\pm x\%$  tolerance,  $A_{\text{cm}}$  of the differential amplifier is:  $A_{\text{cm}} = \frac{v_o}{v_{\text{cm}}} = \frac{x}{50}$ . Therefore the overall  $A_{\text{cm}}$  is also  $\frac{x}{50}$ .

$$x = 1 \Rightarrow A_{\text{cm}} = \frac{1}{50} = 0.02$$

$$\text{CMRR} = 20 \log \frac{21}{0.02} = 60 \text{db}$$

$$\text{If } 2R_1 = 1\text{k}\Omega : A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) = 201 \text{V/V}$$

$A_{\text{cm}} = 0.02$  unchanged

$$\text{CMRR} = 20 \log \frac{201}{0.02} = 80 \text{db}$$

Conclusion: Large CMRR can be achieved by having relatively large  $A_d$  in the first stage.

2.64

$$A_{d(2)}$$
 of the second stage is  $\frac{R_4}{R_3} = 0.5$

$$R_4 = 100 \text{k}\Omega, R_3 = 200 \text{k}\Omega$$

we use a series configuration of  $R_{1F}$  and  $R_1$  (Pot):  $R_1 = 100 \text{k}\Omega$  Pot (Fixed)

Minimum gain =

$$\left(1 + \frac{R_2}{R_1}\right) = 0.5 \left(1 + \frac{\frac{R_2}{100 \text{k} + R_1}}{2}\right)$$

$$1 \leq A_d \leq 100 \Rightarrow 1 = 0.5 \left(1 + \frac{2R_2}{R_{1F} + 100 \text{k}\Omega}\right)$$

$$\Rightarrow R_{1F} + 100 = 2R_2 \quad (1)$$

$$\text{Maximum gain} = 100 = 0.5 \left(1 + \frac{R_2}{R_{1F}/2}\right) \Rightarrow$$

$$2R_2 = 199 R_{1F} \quad (2)$$

$$(1), (2) \Rightarrow R_{1F} = 0.505 \text{k}\Omega \approx 0.5 \text{k}\Omega$$


$$R_2 = 50.25 \text{k}\Omega \approx 50 \text{k}\Omega$$


2.65

$$\text{a) } \frac{v_B}{v_A} = 1 + \frac{20}{10} = 3 \text{ V/V},$$

$$\frac{v_C}{v_A} = -\frac{30}{10} = -3 \text{ V/V}$$
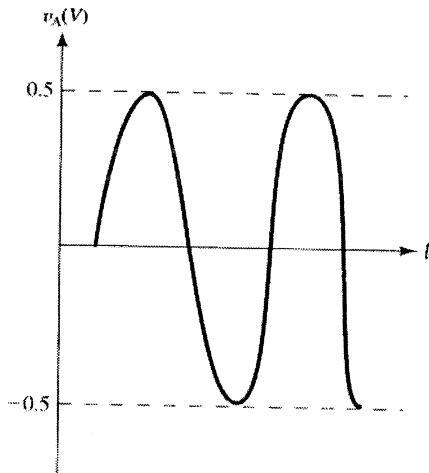
$$\text{b) } v_o = v_B - v_C = 6V_A \Rightarrow \frac{v_o}{v_A} = 6 \text{ V/V}$$



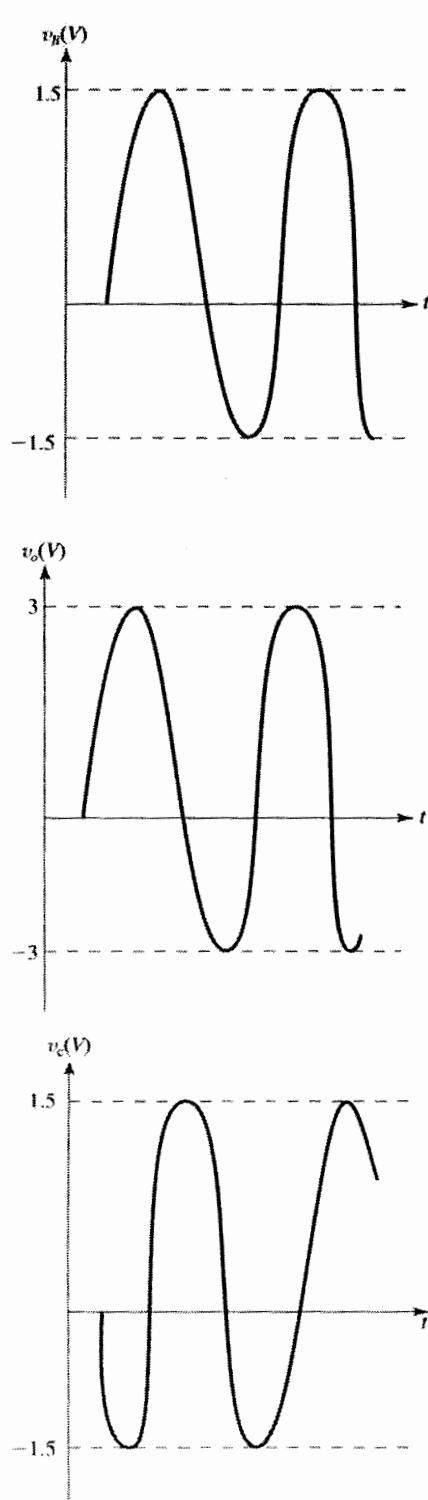


c)  $v_b$  and  $v_c$  can be  $\pm 14$  V or  $28$  V P-P.

$-28 \leq v_b \leq 28$  or  $56$  V P-P.

$$v_{\text{rms}} = 19.8 \text{ V} = \frac{28}{\sqrt{2}}$$

2.66

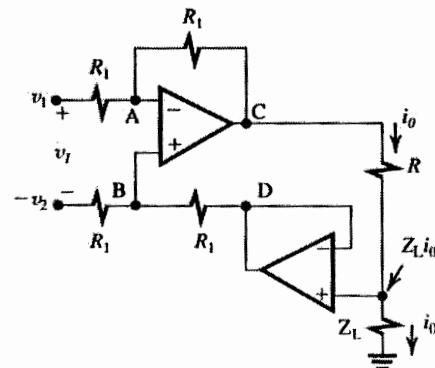

Since the inputs of the op-amp do not draw any current,  $v_1$  appears across  $R_1$

$$i_o = \frac{v_1}{R}$$

$$v_D = Z_L i_o$$

we use superposition:

$$v_1 = v_1 - v_2$$

$$v_1 \text{ only: } V_B = \frac{V_O}{2} = \frac{z_L i_{o1}}{2}$$

$$\frac{v_1 - \frac{z_L i_{o1}}{2}}{R_1} = \frac{\frac{z_L i_{o1}}{2} - i_{o1}(z_L + R)}{R_1}$$

$$\Rightarrow v_1 = i_{o1} R \Rightarrow i_{o1} = \frac{v_1}{R}$$

Now if only  $(-v_2)$  is applied:

$$v_B = \frac{-v_2 + z_L i_{o2}}{2}, \quad v_A = \frac{i_{o2} \times (R + z_L)}{2}$$

$$v_A = v_B \Rightarrow -v_2 + z_L i_{o2} = i_{o2} R + i_{o2} z_L$$

$$-v_2 = i_{o2} R \Rightarrow i_{o2} = \frac{-V_2}{R}$$

The total current due to both sources is:

$$i_o = i_{o1} + i_{o2} = \frac{v_1}{R} - \frac{v_2}{R} = \frac{v_1 - v_2}{R}$$

The circuit has ideally infinite input resistance, and it requires that both terminals of  $Z_L$  be available, while the other circuit has finite input resistance with one side of  $Z_L$  grounded.

2.67

$$\frac{V_o}{V_i} = -\frac{1}{SCR} = -\frac{1}{j\omega CR} = \frac{1}{-j\omega \times 10 \times 10^{-9} \times 100 \times 10^3}$$

$$\frac{V_o}{V_i} = -\frac{10^3}{j\omega}$$

a)  $\frac{V_o}{V_i} = 1 \Rightarrow \omega = 1 \text{ Krad/s}$   $f = 159 \text{ Hz}$

b)  $\frac{1}{j\omega}$  indicates  $90^\circ$  lag, but since its  $\frac{-1}{j\omega}$ , it results in output leading the input by  $90^\circ$ .


c)  $\frac{V_o}{V_i} = -\frac{10^3}{j\omega}$  if frequency is lowered by a factor of 10, then the output would increase by a factor of 10.

d) The phase does not change and the output still leads the input by  $90^\circ$

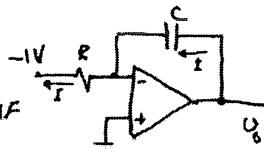2.68

$$R_{in} = R = 100 \text{ k}\Omega$$

$$CR = 1s \Rightarrow C = \frac{1}{100 \times 10^3} = 10 \mu\text{F}$$




with a  $-1 \text{ V}$  dc input applied, the capacitor charges with a constant current:

$$I = \frac{1V}{R} = 0.01 \text{ mA}$$
 and its voltage rises linearly:

$$v_o(t) = -10 + \frac{1}{C} \int_0^t Idt = -10 + \frac{I}{C} t = -10 + \frac{t}{RC}$$

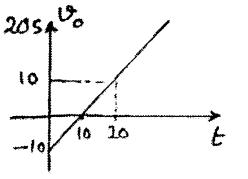the voltage reaches  $0 \text{ V}$  at  $t = 10 \text{ RC} = 10 \text{ s}$  and it reaches  $10 \text{ V}$  at  $t = 20 \text{ s}$



2.69

$$|T| = \frac{1}{\omega RC}$$
 if  $|T| = 100 \text{ V/V}$  for  $f = 1 \text{ kHz}$ ,

then for  $|T| = 1 \text{ V/V}$ ,  $f$  has to be  $1 \text{ kHz} \times 100 = 100 \text{ kHz}$ .

Also

$$RC = \frac{1}{\omega T} = \frac{1}{2\pi \times 1 \text{ kHz} \times 100} = 1.59 \mu\text{s}$$

2.70

$R_o = R$ , Thus  $R = 100 \text{ k}\Omega$ .

$$|T| = \frac{1}{\omega RC} = 1 \text{ at } \omega = \frac{1}{RC}$$



$$\omega = 1000 \text{ rad/s} = \frac{1}{RC} \Rightarrow C = \frac{1}{1000 \times 100^2} = 10 \mu\text{F}$$

with a  $2\text{V}-2\text{ms}$  pulse at the input, the output falls linearly until  $t = 2\text{ms}$  at which

$$v_o = v_i, v_o = \frac{-I}{C} t = \frac{-2}{10 \times 10^{-6}} t = -2t \text{ Volts}$$

where  $t$  in ms

Thus  $v_i = -4 \text{ V}$

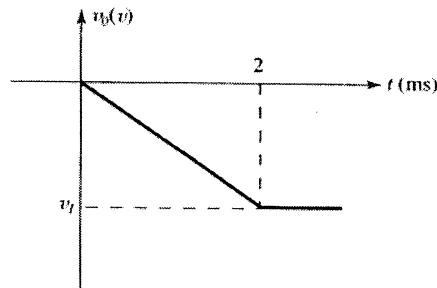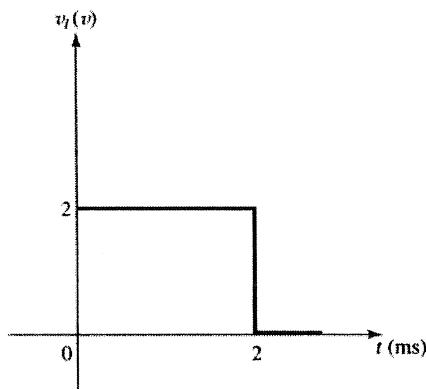

with  $V_r = 2\sin 1000t$  applied at the input,

$$v_o(t) = 2 \times \frac{1}{1000 \times 10^{-3}} \sin(1000t + 90^\circ)$$

$$v_o(t) = 2\sin(1000t + 90^\circ)$$

2.71

$$R_a = R = 20 \text{ k}\Omega$$

$$|T| = \frac{1}{\omega RC} = 1 \text{ at}$$

$$\omega = 2\pi \times 10 \text{ kHz} \Rightarrow C = \frac{1}{2\pi \times 10 \text{ kHz} \times 20 \text{ K}}$$

$$C = 0.796 \text{ nF}$$

$$\frac{v_o}{v_i} = \frac{R_F / R}{1 + S CR_F} \text{ and the finite dc gain is } \frac{-R_F}{R}$$



Therefore for 40db gain or equivalently 100 V/V

$$\text{we have: } \frac{-R_F}{R} = -100 \text{ V/V}$$

$$\Rightarrow R_F = 100 \times 20 \text{ k} = 2 \text{ M}\Omega$$

The corner frequency  $\frac{1}{C / R_F}$  is:
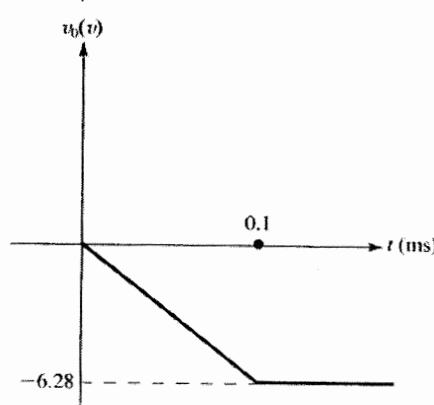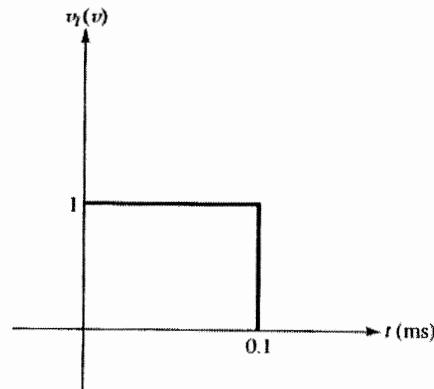
$$\frac{1}{0.796 \text{ m} \times 2 \text{ M}} = 628 \text{ Hz}$$



a) when no  $R_F$

$$v_o(t) = \frac{-1}{RC} \int_0^t 1 \cdot dt = -62.8t \quad 0 \leq t \leq 0.1 \text{ ms}$$


$$v_o(0.1) = -6.28 \text{ V}$$

b) with  $R_F$ :  $v_o(t) = v_o(\infty)(1 - e^{-t/CR_F})$

(Refer to pg. 112)

$$v_o(\infty) = -1 \times R_F = -\frac{1 \text{ V}}{20 \text{ K}} \times 2 \text{ M} = -100 \text{ V}$$

$$v_o(t) = -100(1 - e^{-t/15})$$


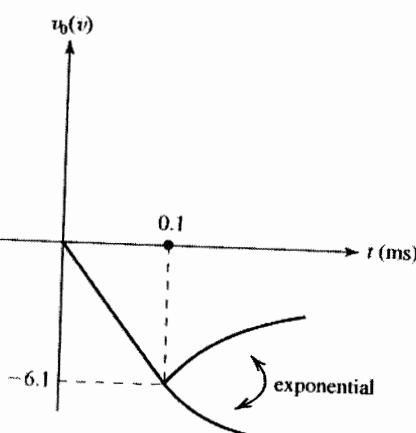


2.72

Each pulse lowers the output voltage by:

$$\Delta v_o = \frac{1}{RC} \int_0^{10\text{ms}} 1 \cdot dt = \frac{10 \mu\text{s}}{RC} = \frac{10 \mu\text{s}}{1 \text{ ms}} = 10 \text{ mV}$$

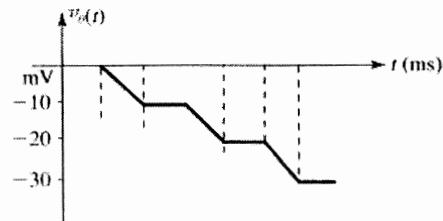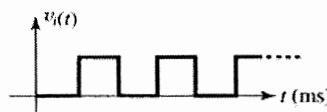Therefore a total of 100 pulses are required to cause a change of 1 V in  $v_o(t)$ .



2.73

$$\frac{v_o}{v_i} = -\frac{R_2}{2R_1} = -\frac{Y_1}{Y_2} = -\frac{Y_{R_1}}{Y_{R_2} + SC} = -\frac{R_2/R_1}{1+SCR_2}$$

which is an STC LP circuit with a dc gain of  $-\frac{R_2}{R_1}$  and a 3-db frequency  $\omega_0 = \frac{1}{CR_2}$ .

The input resistance equal to  $R_1$ . So for:


$$R_i = 1k \Rightarrow R_1 = 1kR_2 \text{ and for dc.gain of } 20 \text{ dB or}$$

$$10 \cdot \frac{R_2}{R_1} = 10 \Rightarrow R_2 = 10 \text{ k}\Omega$$

$$\text{for 3 db Frequency of } 4 \text{ kHz: } \omega_0 = 2\pi \times 4 \times 10^3 = \frac{1}{CR_2}$$

$$\Rightarrow C \approx 4 \text{ nF}$$

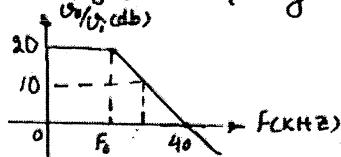the unity gain frequency is (0db) is 40 kHz



2.74

$$\frac{v_o}{v_i}(s) = -sRC = -s \times 0.01 \times 10^{-6} \times 10 \times 10^3 = -10^{-4}s$$

$$\frac{v_o}{v_i}(jw) = -jw \times 10^{-4} \Rightarrow \left| \frac{v_o}{v_i} \right| = -w \times 10^{-4}$$



$$\Rightarrow \left| \frac{v_o}{v_i} \right| = 1 \text{ when } w = 10^4 \text{ rad/s}$$

or  $f = 1.59 \text{ kHz}$

for an input 10 times this frequency, the output will be 10 times as large as the input: 10V peak-to-peak. The (-j) indicates that the output lags the input by  $90^\circ$ . Thus

$$v_o(t) = -5 \sin(10^5 t + 90^\circ) \text{ Volts}$$

2.75

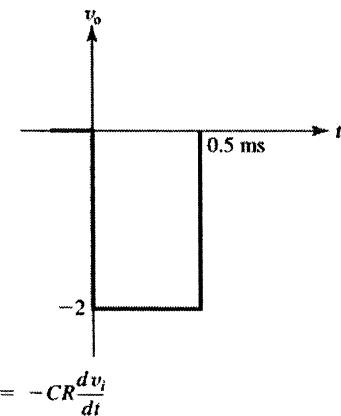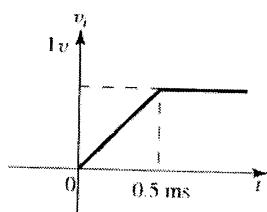

$$v_o = -CR \frac{dv_i}{dt}$$


therefore:

For  $0 \leq t \leq 0.5$ :

$$v_o = -1 \text{ ms} \times \frac{1 \text{ V}}{0.5 \text{ ms}} = -2 \text{ V}$$

and  $v_o = 0$  otherwise

2.76

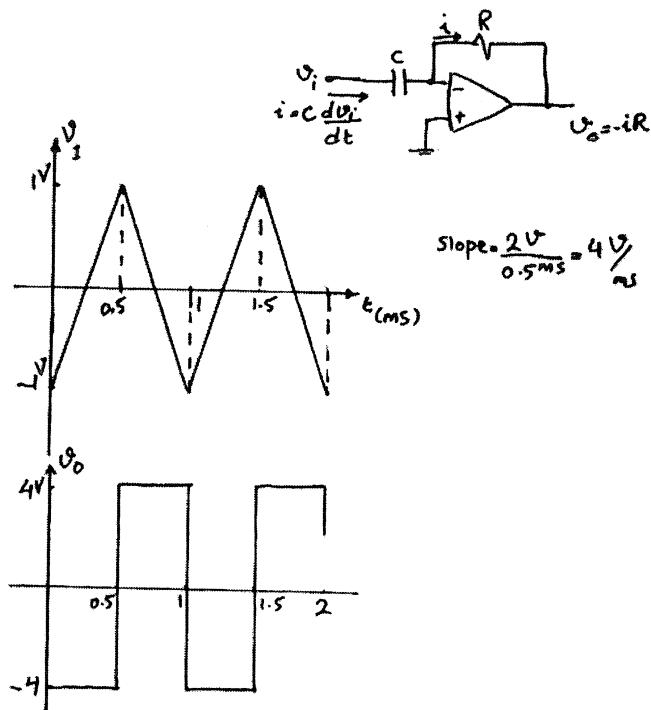

$$C \frac{dV_i}{dt} = 0.1 \times 10^{-6} \times \frac{4}{10^3} = 0.4 \text{ mA}$$

Thus the peak value of the output square wave is  $0.4\text{mA} \times 10^3 \Omega = 4\text{V}$ . The frequency of the output is the same as the input (1KHz).

The average value of the output is 0.

To increase the value of the output to  $10\text{V}$ ,  
R has to be increased to  $\frac{10}{4} = 2.5$ , i.e  $25\text{k}\Omega$ .

When a 1-KHz, 1V peak input sine wave is applied

$$v_i = \sin(2\pi \times 1000t)$$

a sinusoidal signal appears at the output.


It can be determined by one of the following methods:

$$\text{a) } v_o(t) = -RC \frac{dv_i}{dt} = -0.1 \times 10^{-6} \times 10 \times 10^3 \frac{d/v_i}{dt} = -10 \frac{dv_i}{dt}$$

$$v_o(t) = -10 \times 2\pi \times 1000 \times C_0 \sin(2\pi \times 1000t)$$

$$v_o(t) = -2\pi \cos(2\pi \times 1000t)$$

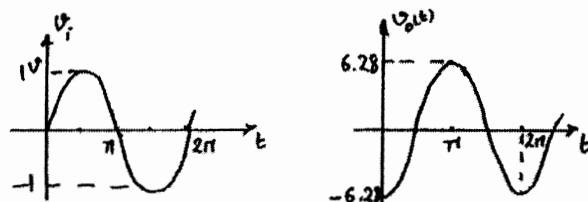Thus the peak amplitude is 6.28V and the negative peaks occur at  $t=0, \frac{2\pi}{2\pi \times 1000}, \dots$



$$\text{b) } \frac{v_o}{v_i} = -SRC \Rightarrow \frac{v_o}{v_i}(j\omega) = -j\omega RC \Rightarrow v_o(j\omega) = -j\omega RC v_i(j\omega)$$

the output is inverted and has  $90^\circ$  phase shift, due to  $(-j)$  factor.

$$v_o(t) = -(wRC) \times 1 \sin(2\pi \times 1000t + 90^\circ)$$

$$v_o(t) = -6.28 \sin(2\pi \times 1000t + 90^\circ)$$

$$v_o(t) = -6.28 \cos(2\pi \times 1000t)$$

Same as before.

c) The peaks of the output waveform are equal to  $RC \times (\text{maximum slope of input wave})$ . Since the maximum slope occurs at the zero crossings, its value is  $2\pi \times 1000$ . Thus the peak output  $= 2\pi \times 1000 \times RC = 6.28\text{V}$

The negative peak occurs at  $wt=0, 2\pi, \dots$

## 2.77

$$RC = 10^{-3}\text{s} \text{ when}$$

$$C = 10\text{mF} \Rightarrow R = 100\text{k}\Omega$$

$$\frac{v_o}{v_i} = -sRC, \frac{v_o}{v_i}(j\omega) = -j\omega RC$$

$\phi = -90^\circ$  always

$$\left| \frac{v_o}{v_i} \right| = 1 \Rightarrow w = \frac{1}{\text{unity } RC} = 1\text{ krad/s}$$

Gain is 10 times the unity gain, when  $\omega = \text{frequency}$  is 10 times the unity gain frequency. Similarly for  $w = 10\text{ krad/s}$ , gain is 0.1 V/V. (for


$w = 10\text{ krad/s}$ , gain = 10 V/V ) for high frequency C is short circuited,

$$\frac{v_o}{v_i} = \frac{-R}{R_1} = -100 \Rightarrow R_1 = 1\text{k}\Omega$$

$$\frac{v_o}{v_i} = \frac{-RCs}{R_1Cs + 1} = \frac{-10^{-3}s}{10^{-5}s + 1}$$

$$\Rightarrow w_{3db} = 100\text{ krad/s or}$$

$$f_{3db} = 15.9\text{ kHz}$$

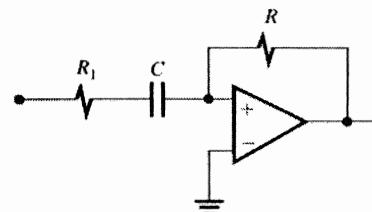

for unity gain:

$$|10^{-3}s| = |10^{-5}s + 1| \Rightarrow w_H = 1.01\text{ krad/s}$$

$$\text{if } w = 10.1\text{ krad/s: } \left| \frac{v_o}{v_i} \right| = \frac{10.1}{1.01} = 10,$$

$$\phi = -95.77^\circ$$

2.78

$$\frac{v_o}{v_i} = -\frac{Z_2}{Z_1} = \frac{-R_2}{R_1 + \frac{1}{sC}} = \frac{-(R_2)s}{s + \frac{1}{R_1C}}$$

which is the

transfer function of an STC HP filter with a high frequency gain  $K = -\frac{R_2}{R_1}$  and a 3-dB frequency  $w_0 = \frac{1}{R_1C}$

The high-frequency input impedance approaches  $R_1$ . (as  $\frac{1}{jwC}$  becomes negligibly small) So we can select  $R_1 = 10k\Omega$


To obtain a high-frequency gain of 40dB (i.e. 100) :  $\frac{R_2}{R_1} = 100 \Rightarrow R_2 = 1M\Omega$ .

For a 3-dB frequency of 1600Hz:

$$\frac{1}{R_1C} = 2\pi \times 1000 \Rightarrow C = 15.9\text{nF}$$

From the Bode-diagram below, we see that

$|\frac{v_o}{v_i}|$  reduces to unity at  $f = 0.01f_0 = 10\text{Hz}$

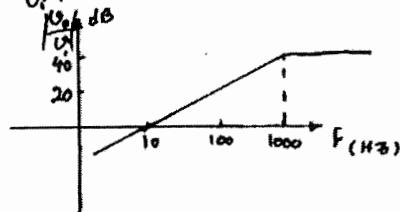

$$\begin{aligned}\frac{v_o}{v_i}(jw) &= \frac{-R_2/R_1}{\left(1 + \frac{1}{jwR_1C_1}\right)(1 + jwR_2C_2)} \\ &= \frac{-R_2/R_1}{\left(1 + \frac{w_1}{jw}\right)\left(1 + j\frac{w}{w_2}\right)}\end{aligned}$$

$$\text{where } w_1 = \frac{1}{R_1C_1}, w_2 = \frac{1}{R_2C_2}$$

a) for  $w = w_1 \ll w_2$

$$\frac{v_o}{v_i}(jw) \approx \frac{-R_2/R_1}{\left(1 + \frac{w}{jw}\right)} \approx \frac{-R_2R_1}{w_1/jw} \approx -j\frac{R_2}{R_1} \frac{w}{w_1}$$


b) for  $w_1 \ll w \ll w_2$

$$\frac{v_o}{v_i}(jw) \approx -\frac{R_2}{R_1}$$

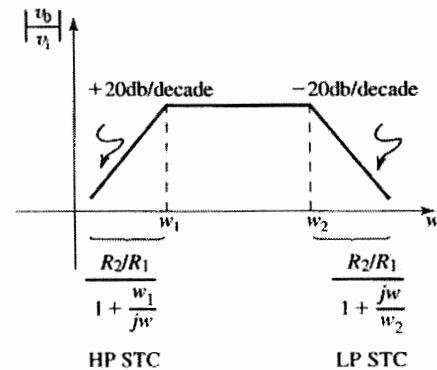c) for  $w \gg w_2$  and  $w_2 \gg w_1$ :

$$\frac{v_o}{v_i}(jw) \approx \frac{-R_2R_1}{1 + jw/w_2} \approx \frac{-R_2R_1}{jw/w_2} = j\left(\frac{R_2}{R_1}\right)\left(\frac{w_2}{w}\right)$$

from the results of a), b) and c) we can draw the Bode-plot:



Design:  $\frac{R_2}{R_1} = 1000$  (40 dB gain in the mid-frequency range)

$R_{1n}$  for  $w \gg w_1$

$$= R_1 = 1\text{k}\Omega \Rightarrow R_2 = 1\text{M}\Omega$$

$$\begin{aligned}f_1 &= 100\text{Hz} \Rightarrow w_1 = 2\pi \times 100 = \frac{1}{R_1C_1} \\ &\Rightarrow C_1 = 1.59\text{\mu F}\end{aligned}$$

$$\begin{aligned}f_2 &= 10\text{Hz} \Rightarrow w_2 = 2\pi \times 10 \times 10^3 = \frac{1}{R_1C_1} \\ &\Rightarrow C_2 = 15.9\text{\textmu F}\end{aligned}$$

2.79

$$\frac{v_o}{v_i} = -\frac{Z_2}{Z_1} = -\frac{1}{Z_1Y_2} = -\frac{1}{\left(R_1 + \frac{1}{sC_1}\right)\left(\frac{1}{R_2} + sC_2\right)}$$

$$\frac{v_o}{v_i} = -\frac{R_2/R_1}{\left(1 + \frac{1}{R_1C_1s}\right)(1 + sR_2C_2)}$$

2.80

$$v_{OS} = \pm 2 \text{ mV}$$

$$v_o = 0.01 \sin \omega t \times 200 + v_{OS} \times 200 \\ = 2 \sin \omega t \pm 0.4 \text{ V}$$

2.81


$$\text{Output DC offset}, v_{OS} = 3 \text{ mV} \times 1000 = 3 \text{ V}$$

Therefore the maximum amplitude of an input sinusoid is the one that results in an output peak amplitude of  $13 - 3 = 10 \text{ V} \Rightarrow v_i = \frac{10}{1000} = 10 \text{ mV}$

If the amplifier is capacity coupled, then:


$$v_{imax} = \frac{13}{1000} = 13 \text{ mV}$$

2.82

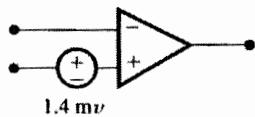

$$v_{OS} = \frac{1.4}{100} = 1.4 \text{ mV}$$

2.83

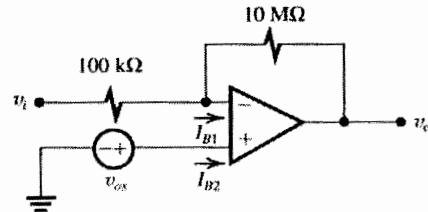

$$\text{a) } I_B = (I_{B1} + I_{B2})/2$$

open input:

$$v_o = v_+ + R_2 I_{B1} = v_{OS} + R_2 I_{B1}$$

$$9.31 = v_{OS} + 10000 I_{B1} \quad (1)$$

input connected to ground:

$$v_o = v_+ + R_2 \left( I_{B1} + \frac{v_{OS}}{R_1} \right)$$

$$= v_{OS} \left( 1 + \frac{R_2}{R_1} + R_2 I_{B1} \right)$$

$$9.09 = v_{OS} \times 101 + 10000 I_{B1} \quad (2)$$


(1), (2)

$$\Rightarrow 100 v_{OS} = -0.22 \Rightarrow v_{OS} = -2.2 \text{ mV}$$

$$\Rightarrow I_{B1} = 930 \text{ nA}$$

$$I_B = I_{B1} = 930 \text{ nA}$$

$$\text{b) } v_{OS} = -2.2 \text{ mV}$$

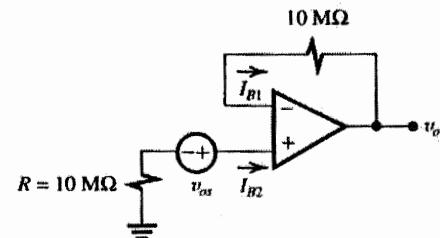

c) In this case, Since R is too large, we may ignore  $v_{OS}$  compare to the voltage drop across R.

$v_{OS} \ll R I_B$ , Also Eq 2.46 holds:


$$R_3 = R_1 \parallel R_2$$

therefore from Eq. 2.47:

$$v_o = I_{OS} \times R_2 \Rightarrow I_{OS} = \frac{0.8}{10 \text{ M}\Omega}$$

$$I_{OS} = -80 \text{ nA}$$

2.84

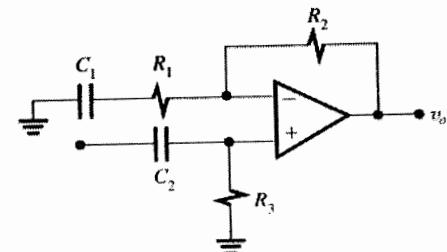

$$R_2 = R_3 = 100 \text{ k}\Omega$$

$$1 + \frac{R_2}{R_1} = 200$$

$$R_1 = \frac{100 \text{ k}}{199} = 502 \Omega$$

$$\frac{1}{R_1 C_1} = 2\pi \times 100 \Rightarrow C_1 = \frac{1}{500 \times 2\pi \times 100} \\ \approx 3.18 \mu\text{F}$$


$$\frac{1}{R_3 C_2} = 2\pi \times 10 \Rightarrow C_2 = \frac{1}{100 \text{ K} \times 2\pi \times 10} \\ = 0.16 \mu\text{F}$$

2.85

The output component due to  $V_{OS}$  is :

$$V_{O1} = V_{OS} \left(1 + \frac{1M}{10k}\right)$$

$$V_{O1} = 4(1+100) = 404 \text{ mV}$$

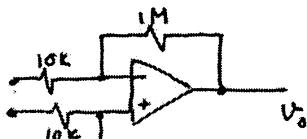

The output component due to  $I_B$  or input bias current is :

$$I_{B1} = I_B + \frac{I_{OS}}{2}, \quad I_{B2} = I_B - \frac{I_{OS}}{2}$$


$$I_{B1} = 0.3 + \frac{0.05}{2} = 0.325 \mu\text{A} \quad I_{B2} = 0.275 \mu\text{A}$$

$$V_+ = -I_{B2} \times (10k || 1M)$$

$$V_+ = -2.72 \text{ mV}$$

$$V_{O2} = V_+ + \left(1M \times \left(I_{B1} + \frac{V_+}{10k}\right)\right)$$

$$V_{O2} = 50 \text{ mV}$$

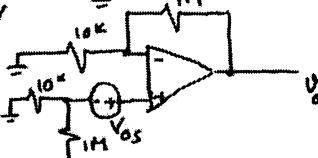

The worst case (largest) DC offset voltage at the output is  $404 + 50 = 454 \text{ mV}$


for capacitively coupled input:

$$V_+ = V_- = V_{OS}$$

$$V_A = V_{OS}$$

$$V_O = V_A + 1M \times \frac{V_{OS}}{1k}$$

$$V_O = 1001 V_{OS} = 1004 \text{ V}$$

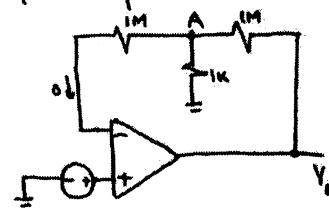


for capacitively coupled 1k to ground:

$$V_+ = V_- = V_{OS}$$

$$V_A = 2V_{OS}$$

$$V_O = 3V_{OS} = 12 \text{ mV}$$

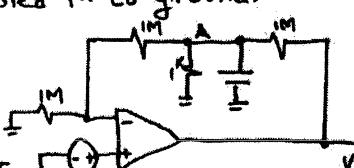This is much smaller than capacitively coupled input case.



2.87

At 0°C, we expect

$$\pm 10 \times 25 \times 1000 \mu = \pm 250 \text{ mV}$$

At 75°C, we expect

$$\pm 10 \times 50 \times 1000 \mu = \pm 500 \text{ mV}$$

We expect these quantities to have opposite polarities.

2.88

$$R_3 = R_1 || R_2 = 9.9 \text{ k}\Omega$$

(Refer to 2.46)




$$V_O = I_{OS} R_2 \quad \text{Eq. 2.47}$$

$$V_O = 0.21 = I_{OS} \times 1M \Rightarrow I_{DS} = 0.21 \mu\text{A}$$

IF  $V_{OS} = 1 \text{ mV}$

$$V_+ = -I_{B2} R_3 \mp V_{OS}$$

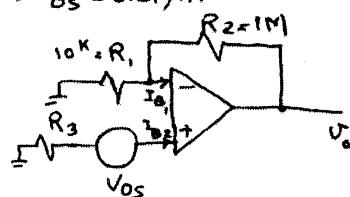

2.86


$$V_- = V_+ = V_{OS} \Rightarrow V_A = 2V_{OS} = 8 \text{ mV}$$

$$i = \frac{V_{OS}}{1M} = V_{OS} (\mu\text{A})$$

$$V_O = V_A + 1M \times \left(i + \frac{V_A}{1k}\right)$$

$$V_O = 2V_{OS} + 1M \left(\frac{V_{OS}}{1M} + 2\frac{V_{OS}}{1k}\right) = 2003 V_{OS} = 2003 \times 4 = 8 \text{ V}$$

$$V_O = 8 \text{ V}$$

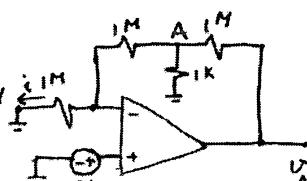

$$I_{B_1} = \frac{R_2 I_{B_2} + V_{os}}{R_1} + \frac{0.2I + R_2 I_{B_2} + V_{os}}{R_2}$$

$$I_{B_1} = R_3 I_{B_2} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + V_{os} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$\frac{1}{R_3} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow I_{B_1} - I_{B_2} = \pm V_{os} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow I_{os} = \pm \frac{1 \text{ mV}}{9.9 \text{ k}} = \pm 0.1 \mu\text{A}$$


If we apply the same current as  $I_{os}$  to the other end of  $R_3$ , then it will cancel out the offset current effect on the output.  $\pm 0.1 \mu\text{A}$

2.89

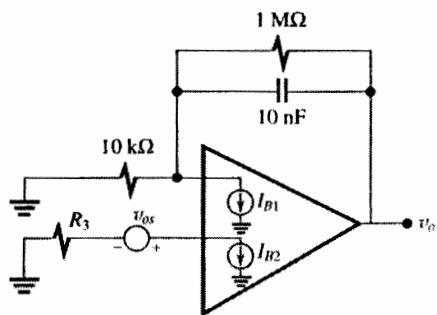a) To compensate for the effect of dc bias current  $I_B$ , we can consider the following model


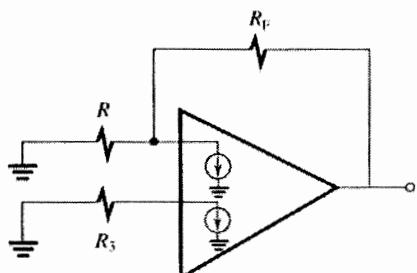
$$R_3 = R \parallel R_F = 10 \text{ k}\Omega \parallel 1 \text{ M}\Omega \Rightarrow R_3 = 9.9 \text{ k}\Omega$$



b) the dc output voltage of the integrator when the input is grounded is:  $V_o = V_{os} \left( 1 + \frac{R_F}{R} \right) + I_{BS} R_F$

$$V_o = 3 \text{ mV} \left( 1 + \frac{1 \text{ M}\Omega}{10 \text{ k}\Omega} \right) + 10 \text{ nA} \times 1 \text{ M}\Omega \\ = 0.303 \text{ V} + 0.01 \text{ V} \\ V_o = 0.313 \text{ V}$$

2.90

$$w_i = A_0 w_b \\ \Rightarrow f_i = A_0 f_b$$

$A_0$	$f_b(\text{Hz})$	$f_i(\text{Hz})$
$10^5$	$10^2$	$10^7$
$10^6$	1	$10^6$
$10^5$	$10^3$	$10^8$
$10^7$	$10^{-1}$	$10^6$
$2 \times 10^5$	10	$2 \times 10^6$

$$2.91 \quad A = \frac{A_0}{1 + j \omega / \omega_b} \Rightarrow |A| = \frac{|A_0|}{\sqrt{1 + \left(\frac{\omega}{\omega_b}\right)^2}}$$


$$A_0 = 86 \text{ dB}, A = 40 \text{ dB} @ F = 100 \text{ kHz}$$

$$20 \log \sqrt{1 + \left(\frac{\omega}{\omega_b}\right)^2} = 20 \log \frac{|A_0|}{|A|} = 20 \log A_0 - 20 \log A \\ = 86 - 40 = 46 \text{ dB}$$

$$1 + \left(\frac{\omega}{\omega_b}\right)^2 = (199.5)^2 \Rightarrow \omega_b = 0.501 \text{ kHz}$$

$$\omega_b = A_0 \omega_b = \underbrace{1.995 \times 10^4}_{86 \text{ dB}} \times 501 = \frac{9.998 \text{ MHz}}{10 \text{ MHz}}$$

2.92

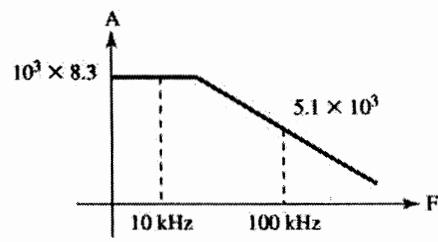

$$A_o = 8.3 \times 10^3 \text{ V/V}$$

$$\text{Eq. 2.25: } A = \frac{A_o}{1 + j\frac{f}{f_b}}$$

$$f_t = A_o f_b$$

$$5.1 \times 10^3 = \frac{8.3 \times 10^3}{\sqrt{1 + \left(\frac{100 \text{ kHz}}{f_b}\right)^2}} \Rightarrow 1 + \left(\frac{100 \text{ kHz}}{f_b}\right)^2 = 2.65$$

$$f_b = 60.7 \text{ kHz}$$

$$f_t = A_o f_b = 8.3 \times 10^3 \times 60.7 \text{ kHz} = 503 \text{ MHz}$$

2.93

we have:

$$A_o(\text{dB}) = 20 \text{ dB} + A(\text{dB})$$

$$20 \text{ dB} = 20 \log 10 \Rightarrow A_o = 10 \text{ A}$$

$$\text{a) } A_o = 10 \times 3 \times 10^5 = 3 \times 10^6 \text{ Hz V/V}$$

$$A = \frac{A_o}{1 + jf/f_b} \Rightarrow \left|1 + j\frac{f}{f_b}\right| = \frac{A_o}{A} = 10 \Rightarrow$$

$$\frac{6 \times 10^2}{f_b} = \sqrt{99}$$

$$\Rightarrow f_b = 60.3 \text{ Hz}$$

$$f_t = A_o f_b = 3 \times 10^6 \times 60.3 = 180.9 \text{ MHz}$$

b)

$$A = 50 \times 10^5 \times 10 \text{ V/V} \Rightarrow A_o = 10 \times 50 \times 10^5$$

$$= 50 \times 10^6 \text{ V/V}$$

$$\left|1 + j\frac{f}{f_b}\right| = \frac{A_o}{A} = 10 \Rightarrow \frac{10 \text{ Hz}}{f_b} = \sqrt{99} \Rightarrow f_b = 1 \text{ Hz}$$

$$f_t = A_o f_b = 50 \text{ MHz}$$

$$\text{c) } A = 1500 \text{ V/V} \Rightarrow A_o = 1500 \text{ V/V}$$

$$\left|1 + j\frac{f}{f_b}\right| = 10 \Rightarrow \frac{0.1 \times 10^9}{f_b} = \sqrt{99} \Rightarrow f_b = 10 \text{ kHz}$$

$$f_t = 15000 \times 10 \text{ K} = 150 \text{ MHz}$$

$$\text{d) } A_o = 10 \times 100 = 1000 \text{ V/V}$$

$$\left|1 + j\frac{f}{f_b}\right| = 10 \Rightarrow \frac{0.1 \times 10^9}{f_b} = \sqrt{99} \Rightarrow f_b = 10 \text{ MHz}$$

$$f_t = 1000 \times 10 \text{ MHz} = 10 \text{ GHz}$$

$$\text{e) } A = 25 \text{ V/mV} \times 10 = 25 \times 10^4 \text{ V/V}$$

$$\left|1 + j\frac{f}{f_b}\right| = 10 \Rightarrow \frac{2.5 \text{ kHz}}{f_b} = \sqrt{99} \Rightarrow f_b = 2.51 \text{ kHz}$$

$$f_t = A_o f_b = 25 \times 10^4 \times 2.51 \times 10^3 = 627.5 \text{ MHz}$$

2.95

$$G_{\text{Nom}} = -\frac{R_2}{R_1} = -20 \quad A_o = 10^4 \text{ V/V}$$

$$f_k = 10^6 \text{ Hz}$$

$$w_{3\text{db}} = \frac{w_t}{1 + R_2 R_1} = \frac{2\pi \times 10^6}{1 + 20}$$

$$= 2\pi \times 47.6 \text{ kHz}$$

$$f_{3\text{db}} = 47.6 \text{ kHz}$$

$$\frac{v_o}{v_t} \approx \frac{-R_2/R_1}{1 + \frac{s}{w_t(1 + R_2/R_1)}} = \frac{-20}{1 + \frac{215}{2\pi \times 10^6}}$$

$$f = 0.1 f_{3\text{db}} \Rightarrow \left| \frac{v_o}{v_t} \right| = \frac{-20}{\sqrt{1 + (0.1)^2}} = 19.9 \text{ V/V}$$

$$f = 10 f_{3\text{db}} \Rightarrow \left| \frac{v_o}{v_t} \right| = \frac{-20}{\sqrt{1 + 100}} = 19.9 \text{ V/V}$$

2.96

$$1 + \frac{R_2}{R_1} = 100 \text{ V/V} \quad , \quad f_k = 20 \text{ MHz}$$

$$f_{3\text{db}} = \frac{f_k}{1 + \frac{R_2}{R_1}} = 200 \text{ kHz}$$

$$G_{\text{id}} = \frac{100}{1 + j \frac{f}{f_{3\text{db}}}} \Rightarrow \varphi = -\tan^{-1} \frac{f}{f_{3\text{db}}} =$$

$$\varphi = -6^\circ \Rightarrow f = f_{3\text{db}} \times \tan 6^\circ = 21 \text{ kHz}$$

$$\varphi = -84^\circ \Rightarrow f = f_{3\text{db}} \times \tan 84^\circ = 1.9 \text{ MHz}$$

### 2.96

a)  $\frac{R_2}{R_1} = -100 \text{ V/V}, f_{3\text{db}} = 100 \text{ kHz}$

$$w_t = w_{3\text{db}} \left(1 + \frac{R_2}{R_1}\right) \Rightarrow f_t = 100 \text{ kHz} \times 100 = 10.1 \text{ MHz}$$

b)  $1 + \frac{R_2}{R_1} = 100 \text{ V/V}, f_{3\text{db}} = 100 \text{ kHz}$

$$f_t = f_{3\text{db}} \left(1 + \frac{R_2}{R_1}\right) = 10 \text{ MHz}$$

c)  $1 + \frac{R_2}{R_1} = 2 \text{ V/V}, f_{3\text{db}} = 10 \text{ kHz}$

$$f_t = 10 \text{ MHz} \times 2 = 20 \text{ MHz}$$

d)  $-\frac{R_2}{R_1} = -2 \text{ V/V}, f_{3\text{db}} = 10 \text{ kHz}$

$$f_t = 10 \text{ MHz}(1 + 2) = 30 \text{ MHz}$$

e)  $-\frac{R_2}{R_1} = -1000 \text{ V/V}, f_{3\text{db}} = 20 \text{ kHz}$

$$f_t = 20 \text{ kHz}(1 + 100) = 20.02 \text{ MHz}$$

f)  $1 + \frac{R_2}{R_1} = 1 \text{ V/V}, f_{3\text{db}} = 1 \text{ MHz}$

$$f_t = 1 \text{ MHz} \times 1 = 1 \text{ MHz}$$

g)  $-\frac{R_2}{R_1} = -1, f_{3\text{db}} = 1 \text{ MHz}$

$$f_t = 1 \text{ MHz}(1 + 1) = 2 \text{ MHz}$$

### 2.97

$$1 + \frac{R_2}{R_1} = 100 \text{ V/V} \quad f_{3\text{db}} = 8 \text{ kHz}$$

$$f_t = 8 \times 100 = 800 \text{ kHz}$$

$$\text{for } f_{3\text{db}} = 20 \text{ kHz} : G_o = \frac{800}{20} = 40 \text{ V/V}$$

### 2.98

$$f_{3\text{db}} = f_t = 1 \text{ MHz}$$

$$|G| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3\text{db}}}\right)^2}} = \frac{1}{\sqrt{1 + f^2}} \text{ f in MHz}$$

$$|G| = 0.99 \Rightarrow f = 0.142 \text{ MHz}$$

The follower behaves like a low-pass STC circuit

$$\text{with a time constant } \tau = \frac{1}{2\pi \times 10^6} = \frac{1}{2\pi} \mu\text{s}$$

$$t_r = 2.20 = 0.35 \mu\text{s} \text{ (Refer to Appendix F)}$$

### 2.99

a) Assume two identical stages, each with a gain

$$\text{function: } G = \frac{G_o}{1 + j\frac{w}{w_1}} = \frac{G_o}{1 + jf/f_1}$$

$$G = \frac{G_o}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}}$$

$$\text{overall gain of the cascade is } \frac{G_o^2}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}}$$

The gain will drop by 3db when:

$$1 + \left(\frac{f_{3\text{db}}}{f_1}\right)^2 = \sqrt{2}, \text{ Note } 3\text{db} = 20 \log \sqrt{2}$$

$$f_{3\text{db}} = F_1 \sqrt{\sqrt{2} - 1}$$

$$\text{b) } 40 \text{ db} = 20 \log G_o \Rightarrow G_o = 100 = 1 + \frac{R_2}{R_1}$$

$$f_{3\text{db}} = \frac{f_1}{1 + \frac{R_2}{R_1}} = \frac{1 \text{ MHz}}{100} = 10 \text{ kHz}$$

c) Each stage should have 20db gain or

$$1 + \frac{R_2}{R_1} = 10 \text{ and therefore a 3db frequency of:}$$

$$f_1 = \frac{10^6}{10} = 10^5 \text{ Hz.}$$

The overall  $f_{3\text{db}} = 10^5 \sqrt{\sqrt{2} - 1} = 64.35 \text{ kHz}$   
which is 6 time greater than the bandwidth  
achieved using single op amp.  
(case b above)

### 2.100

$f_t = 100 \times 5 = 500 \text{ MHz}$  if single op-amp is used.

with op-amp that has only  $f_t = 40 \text{ MHz}$ ,  
the possible closed loop gain at 5 MHz is:

$$|A| = \frac{40}{5} = 8 \text{ V/V}$$

To obtain a overall gain of 100, three such amplifier cascaded, would be required. Now, if each of the 3 stages, has a low-frequency (d) closed loop gain K, then its 3-db frequency will  $\frac{40}{k} \text{ MHz}$ .

Thus for each stage the closed loop gain is:

$$|G| = \frac{k}{\sqrt{1 + \left(\frac{f}{40}\right)^2}}$$

which at  $f = 5$  MHz becomes:

$$|G_{5\text{MHz}}| = \frac{k}{\sqrt{1 + \left(\frac{k}{8}\right)^2}}$$

$$\text{The overall gain of } 100: 100 = \left[ \frac{k}{\sqrt{1 + \left(\frac{k}{8}\right)^2}} \right]^3$$

$$k = 5.7$$

$$\text{Thus for each cascade stage: } f_{3\text{db}} = \frac{40}{5.7}$$

$$f_{3\text{db}} = 7 \text{ MHz}$$

The 3-db frequency of the overall amplifier  $f_1$ , can be calculated as:

$$\left[ \frac{5.7}{\sqrt{1 + \left(\frac{f}{7}\right)^2}} \right]^3 = \frac{(5.7)^3}{\sqrt{2}} \Rightarrow f_1 = 3.6 \text{ MHz}$$

### 2.101

$$\text{a) } \frac{R_2}{R_1} = k, \quad f_{3\text{db}} = \frac{f_t}{1 + \frac{R_2}{R_1}} = \frac{f_t}{1 + k}$$

$$\text{GBP} = \text{Gain} \times f_{3\text{db}}$$

$$\text{GBP} = k \frac{f_t}{1 + k}$$

$$\text{b) } 1 + \frac{R_2}{R_1} = k \quad f_{3\text{db}} = \frac{f_t}{k}$$

$$\text{GBP} = k \frac{f_t}{k} = f_t$$

The non-inverting amplifier realizes a higher GBP and it's independent of k.

### 2.102

To find  $f_{3\text{db}}$  we use superposition:

Set  $V_2 = 0$

Now using Thevenin's


Theorem to Simplify the input circuit results in:

$$\frac{V_o}{V_{1/2}} = \frac{-R/R_{1/2}}{1 + S \frac{R/R_{1/2}}{\omega_L}}$$

which gives:

$$\frac{V_o}{V_1} = \frac{-1}{1 + S \left( \frac{\omega_L}{\omega_B} \right)}$$

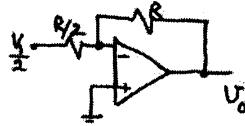$f_{3\text{db}} = \frac{\omega_B}{3}$ . Similar results can be obtained for  $\frac{V_o}{V_2}$ .



Thevenin's equivalent

### 2.103



The peak value of the largest possible sine wave that can be applied at the input without output clipping is:  $\frac{\pm 12V}{100} = 0.12V = 120 \text{ mV rms}$

$$\text{value} = \frac{120}{\sqrt{2}} = 85 \text{ mV}$$

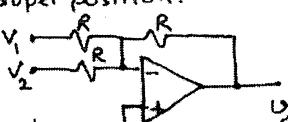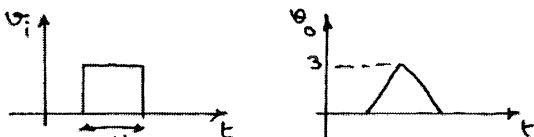
### 2.104

The output is triangular with the slew rate of  $20V/\mu\text{s}$ . In order to reach 3V, it takes  $\frac{3}{20} \mu\text{s} = 0.15 \mu\text{s} = 150 \text{ ns}$ .

Therefore the minimum pulse width is 150 ns.



2.105

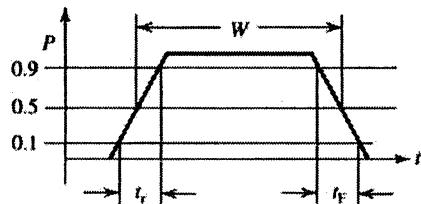

$$W = 2 \mu s$$

$$t_r + t_F = 0.2 \mu s$$

$$t_r = t_F = 0.2 \mu s$$

$$SR = \frac{(0.9 - 0.1)P}{t_r} = \frac{0.8 \times 10}{0.2} = 40 \text{ V}/\mu s$$

2.106

$$\text{Slope of the triangle wave} = \frac{20 \text{ V}}{T/2} = SR$$

$$\text{Thus } \frac{20}{T} \times 2 = 10 \text{ V}/\mu s$$

$$\Rightarrow T = 4 \mu s \text{ or } f = \frac{1}{T} = 250 \text{ kHz}$$

For a sine wave  $v_o = v_s \sin(2\pi \times 250 \times 10^3 t)$

$$\left. \frac{dv_o}{dt} \right|_{\max} = 2\pi \times 250 \times 10^3 \hat{v}_o = SR$$

$$\Rightarrow \hat{v}_o = \frac{10 \times 10^6}{2\pi \times 10^3 \times 250} = 6.37 jV$$

2.107


$$v_o = 10 \sin \omega t \Rightarrow \frac{dv_o}{dt} = 10\omega \cos \omega t \Rightarrow \left. \frac{dv_o}{dt} \right|_{\max} = 10\omega$$

The highest frequency at which this output is possible is that for which:

$$\left. \frac{dv_o}{dt} \right|_{\max} = SR \Rightarrow 10\omega_{\max} = 60 \times 10^6 \Rightarrow \omega_{\max} = 6 \times 10^5$$


$$\Rightarrow f_{\max} = 45.5 \text{ kHz}$$

3 . 1

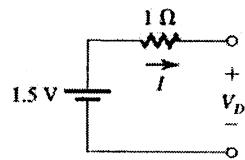

The diode can be reverse-biased and thus no current would flow, or forward-biased where current would flow.

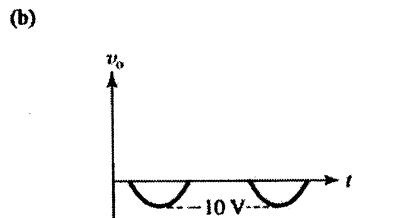- (a) Reverse biased  $I = 0 \text{ A}$   $V_D = 1.5 \text{ V}$   
 (b) Forward biased  $I = 1.5 \text{ A}$   $V_D = 0 \text{ V}$




$$V_{p+} = 0 \text{ V} \quad V_{p-} = -10 \text{ V}$$


$$f = 1 \text{ kHz}_3$$

3 . 2


(a)

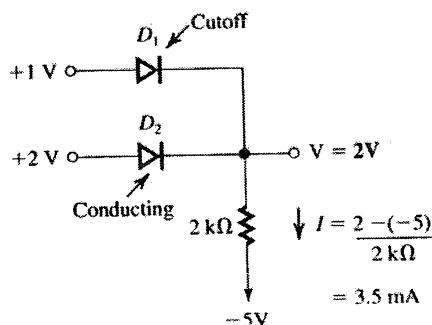

(b)

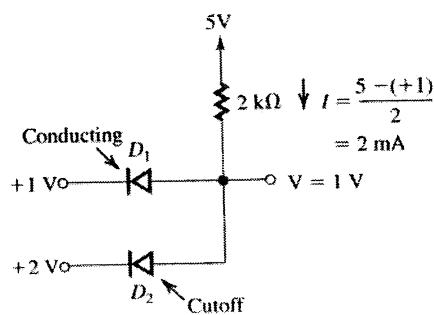


(c)

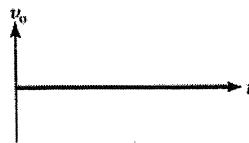

$v_o = 0 \text{ V}$   
 Neither  $D_1$  nor  $D_2$  conducts so there is no output.


(d)

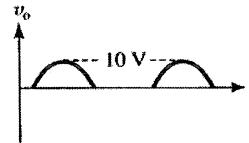

$$V_{p+} = 10 \text{ V} \quad V_{p-} = 0 \text{ V} \quad f = 1 \text{ kHz}_3$$


Both  $D_1$  and  $D_2$  conduct when  $V_I > 0$

(e)

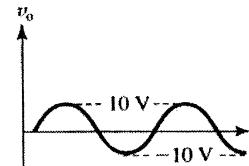

3 . 3

(a)

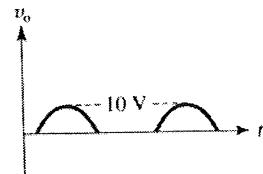


$$V_{p+} = 10 \text{ V} \quad V_{p-} = 0 \text{ V}$$

$$f = 1 \text{ kHz}_3$$

$$V_{p+} = 10 \text{ V} \quad V_{p-} = -10 \text{ V} \quad f = 1 \text{ kHz}_3$$

$D_1$  conducts when  $v_I > 0$  and  $D_2$  conducts when  $v_I < 0$ . Thus the output follows the input.


(f)

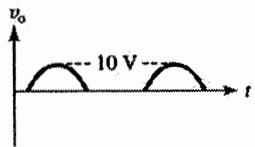

$$V_{p+} = 10 \text{ V} \quad V_{p-} = 0 \text{ V} \quad f = 1 \text{ kHz}_3$$

$-D_1$  is cutoff when  $v_I < 0$


(g)

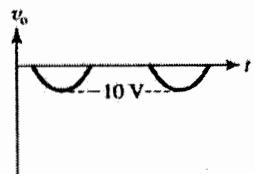

$$V_{p+} = 0 \text{ V} \quad V_{p-} = -10 \text{ V} \quad f = 1 \text{ kHz}_3$$


$D_1$  shorts to ground when  $v_I > 0$  and is cut off when  $v_I < 0$  whereby the output follows  $v_I$

(h)

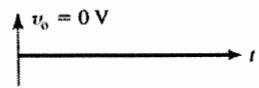

$v_O = 0 \text{ V}$  ~ The output is always shorted to ground as  $D_1$  conducts when  $v_I > 0$  and  $D_2$  conducts when  $v_I < 0$ .


(i)

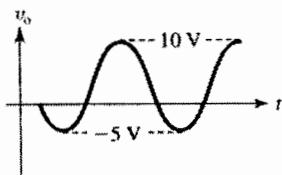

$V_{p+} = 10 \text{ V} \quad V_{p-} = -5 \text{ V} \quad f = 1 \text{ kHz}_3$   
When  $v_I > 0$ ,  $D_1$  is cutoff and  $v_O$  follows  $v_I$   
When  $v_I < 0$ ,  $D_1$  is conducting and the circuit becomes a voltage divider where the negative peak is


$$\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 1 \text{ k}\Omega} \cdot -10 \text{ V} = -5 \text{ V}$$

(j)

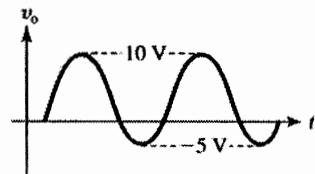

$V_{p+} = 10 \text{ V} \quad V_{p-} = -5 \text{ V} \quad f = 1 \text{ kHz}_3$   
When  $v_I > 0$ , the output follows the input as  $D_1$  is conducting.  
When  $v_I < 0$ ,  $D_1$  is cut off and the circuit becomes a voltage divider.


(k)

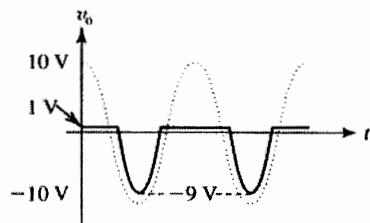


$V_{p+} = 1 \text{ V} \quad V_{p-} = -9 \text{ V} \quad f = 1 \text{ kHz}_3$   
When  $v_I > 0$ ,  $D_1$  is cutoff and  $D_2$  is conducting. The output becomes 1 V.  
When  $v_I < 0$ ,  $D_1$  is conducting and  $D_2$  is cutoff.  
The output becomes:-

$$v_O = v_I + 1 \text{ V}$$

3.4

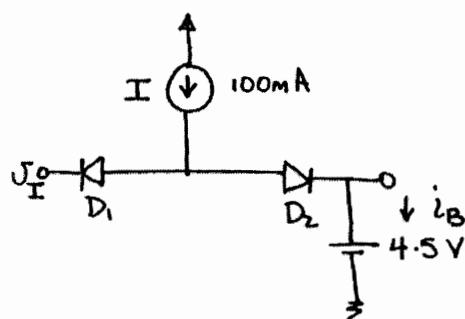

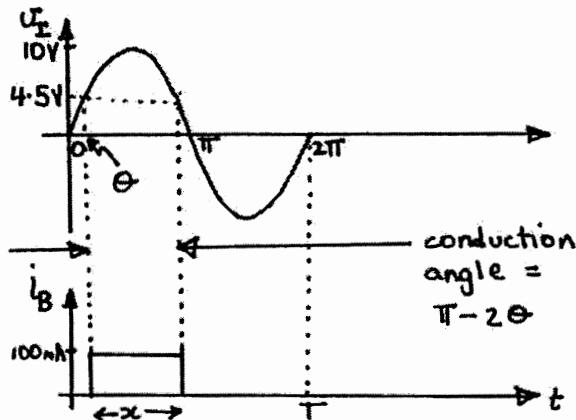

If  $U_I$  is reduced by 10% the peak value of  $i_B$  remains the same

$$i_{B\text{peak}} = 100\text{mA}$$

but the fraction of the cycle for conduction changes

$$\begin{aligned} x &= \frac{\pi - 2\theta}{2\pi} = \frac{\pi - 2\sin^{-1}(4.5/10)}{2\pi} \\ &= \frac{1}{3} \end{aligned}$$

Thus:

$$\begin{aligned} i_{B\text{avg}} &= \frac{1}{T} \left[ 100 \cdot \frac{1}{3} \right] \\ &= \underline{\underline{33.3\text{ mA}}} \end{aligned}$$

- When  $U_I < 4.5\text{ V}$   $D_1$  conducts and  $D_2$  is cutoff so  $i_B = 0\text{ A}$ . For  $U_I > 4.5\text{ V}$   $D_2$  conducts and  $D_1$  is cutoff thus disconnecting the input  $U_I$ . All of the current then flows through the battery.

$$\begin{aligned} 10 \sin \theta &= 4.5 \text{ V} \\ \theta &= \sin^{-1}(4.5/10) \end{aligned}$$

$$\text{conduction angle} = \pi - 2\theta$$

fraction of cycle that  $i_B = \underline{\underline{100\text{ mA}}}$  is given by :-

$$x = \frac{\pi - 2\theta}{2\pi} = 0.35$$

$$i_{B\text{avg}} = \frac{1}{T} \int_T i_B dt$$

$$= \frac{1}{T} \left[ 100 \cdot 0.35 T \right]$$

$$= \underline{\underline{35\text{ mA}}}$$

3.5

$$\frac{5 - 0}{R} \leq 0.1 \text{ mA}$$

$$R \geq \frac{5}{0.1} = \underline{\underline{50\text{ k}\Omega}}$$


3.6

The maximum input current occurs when one input is low and the other two are high.



$$\frac{5 - 0}{R} \leq 0.1 \text{ mA}$$

$$R \geq 50 \text{ k}\Omega$$

3.7

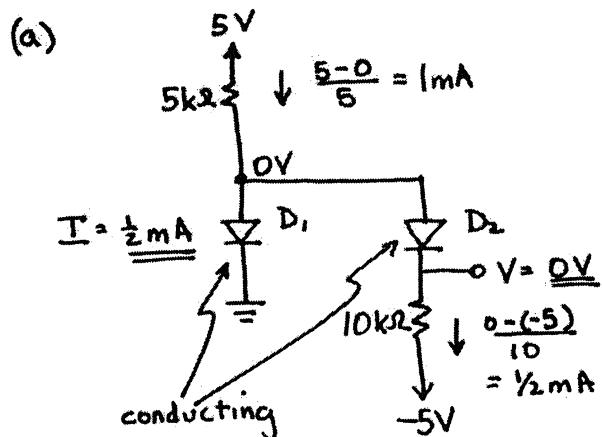

$$V = \frac{20}{(10||20)+20} \times 6 = \underline{\underline{4.5\text{V}}}$$

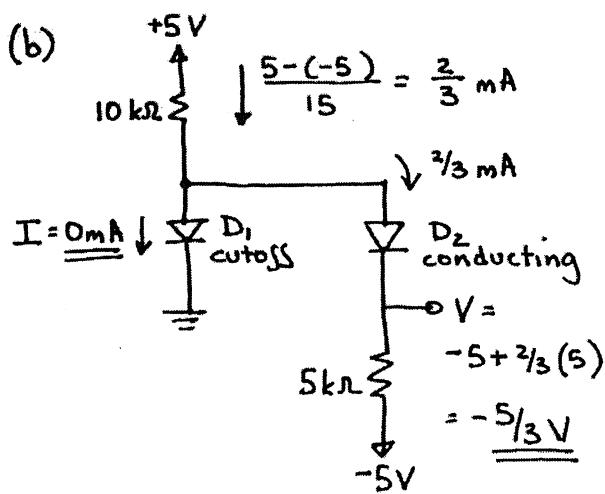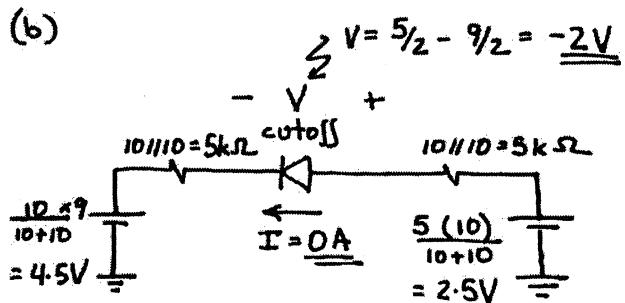


3.9

$$R \geq \frac{120\sqrt{2}}{50} \geq 3.4\text{ k}\Omega$$

The largest reverse voltage appearing across the diode is equal to the peak input voltage


$$120\sqrt{2} = 169.7\text{ V}$$

3.8

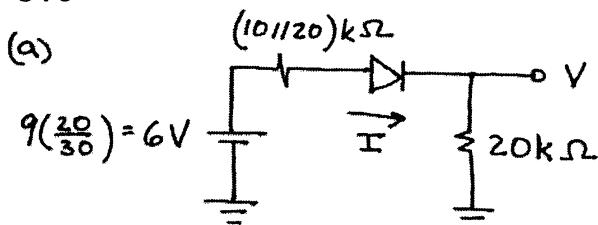


$$I = \frac{6}{(10/120)+20} = \underline{\underline{0.225\text{mA}}}$$



3.10

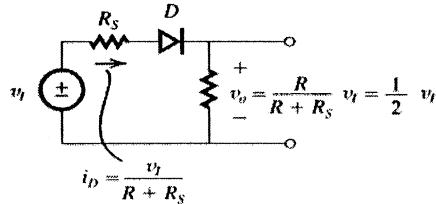

D starts to conduct when  $v_t > 0$

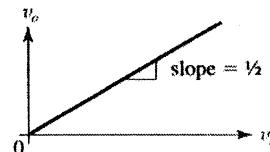

3.11

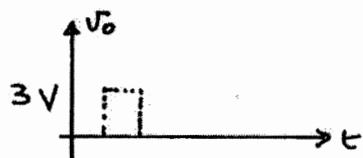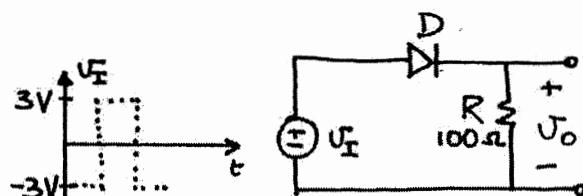

$$U_{O, \text{peak}} = 3V$$



$$\begin{aligned} U_{O, \text{avg}} &= \frac{1}{T} \int U_O dt \\ &= \frac{1}{T} \left[ 3 \frac{T}{2} \right] = \underline{\underline{3/2 V}} \end{aligned}$$

$$i_{D, \text{peak}} = \frac{3}{100} = \underline{\underline{30 \mu A}}$$

$$i_{D, \text{avg}} = \frac{3/2}{100} = \underline{\underline{15 \mu A}}$$

The maximum reverse diode voltage is 3V

3.12

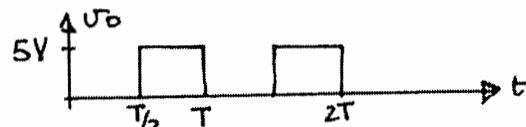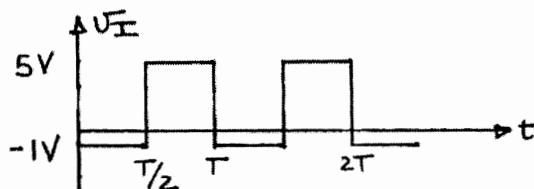

$$U_{O, \text{peak}} = \underline{\underline{5V}}$$

$$U_{O, \text{avg}} = \underline{\underline{2.5V}}$$

$$i_{D, \text{peak}} = \frac{U_{O, \text{peak}}}{100} = \underline{\underline{50 \mu A}}$$

$$i_{D, \text{avg}} = i_{D, \text{peak}}/2 = \underline{\underline{25 \mu A}}$$

$$\text{maximum reverse voltage} = \underline{\underline{1V}}$$

3.13

V	RED	GREEN
3V	ON	OFF
0	OFF	OFF
-3V	OFF	ON

- D<sub>1</sub> conducts  
- No current flows  
- D<sub>2</sub> conducts

3.14

$$i_1 = I_s e^{0.7/V_T} = 10^{-3}$$

$$i_2 = I_s e^{0.5/V_T}$$

$$\frac{i_2}{i_1} = \frac{i_2}{10^{-3}} = e^{\frac{0.5-0.7}{0.025}}$$

$$i_2 = 0.335 \mu A$$

3.15

$$i = I_s e^{v_1/0.025} = I_s e^{0.7/0.025} = 5(10^{-3})$$

$$I_s = 5(10^{-3}) e^{-0.7/0.025} = \underline{\underline{3.46 \times 10^{-5} A}}$$

v	i
0.71V	7.46 mA
0.8V	273.21 mA
0.69V	3.35 mA
0.6V	91.65 μA

$$\text{Let } i_1 = I_s e^{v_1/0.025}$$

$$i_2 = 10 i_1 = I_s e^{v_2/0.025}$$

$$\frac{i_2}{i_1} = 10 = e^{\frac{v_2-v_1}{0.025}}$$

$$\therefore \Delta v = v_2 - v_1 = \underline{\underline{57.56 mV}}$$

3.16

To calculate  $I_s$  use

$$I_s = I e^{-V/nV_T} = I e^{-V/0.025}$$

To calculate the voltage at 1% of the measured current use

$$i_2 = 0.01 i_1 \quad \text{so,}$$

$$\frac{i_2}{i_1} = 0.01 = e^{\frac{V_2 - V_1}{nV_T}}$$

$$V_2 = V_1 + nV_T \ln 0.01 \\ = V + n(0.025) \ln(0.01)$$

V [V]	I [A]	$I_s$ [A]	V [V]	V [V]
	$n=1$	$n=2$	$n=1$	$n=2$
0.7	1A	$6.91 \times 10^{-13}$	$8.32 \times 10^{-7}$	0.585
0.650	1mA	$5.11 \times 10^{-15}$	$2.26 \times 10^{-9}$	0.535
0.650	10μA	$5.11 \times 10^{-17}$	$2.26 \times 10^{-11}$	0.535
0.7	10mA	$6.91 \times 10^{-15}$	$8.32 \times 10^{-9}$	0.584

3.17

Let  $I_1 = I_s e^{V_1/nV_T}$  and

$$I_2 = I_s e^{V_2/nV_T} = I_1/10$$

Calculate  $n$  by :-

$$\frac{I_2}{I_1} = e^{\frac{V_2 - V_1}{nV_T}}$$

$$n = \frac{1}{V_T} \left[ \frac{V_2 - V_1}{\ln \frac{I_2}{I_1}} \right] = \frac{1}{0.025} \left[ \frac{V_2 - V_1}{\ln 0.1} \right]$$

Calculate  $I_s$  by :-

$$I_s = I_1 e^{-V_1/nV_T}$$

Calculate the diode voltage at  $10I_1$ ,  
by :-  $V_3 = nV_T \ln \frac{10I_1}{I_s}$


I	V <sub>1</sub> [V]	V <sub>2</sub> [V]	n	I <sub>s</sub> [A]	V <sub>3</sub> [V]
10mA	0.7	0.6	1.737	$10^{-9}$	0.8
1mA	0.7	0.6	1.737	$10^{-10}$	0.8
10A	0.8	0.7	1.737	$10^{-7}$	0.9
1mA	0.7	0.58	2.085	$1.47 \times 10^{-9}$	0.82
10μA	0.7	0.64	1.042	$2.15 \times 10^{-17}$	0.7

3.18

The voltage across each diode is  $V_0/3$


$$I = I_s e^{\frac{V_0/3}{nV_T}} = 10^{-14} e^{\frac{2/3}{0.025}}$$

$$= 3.81 \text{ mA}$$

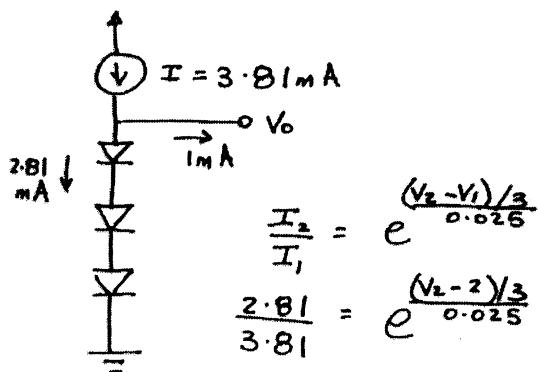

$$\Delta V = V_2 - 2 = -22.8 \text{ mV}$$

3.19

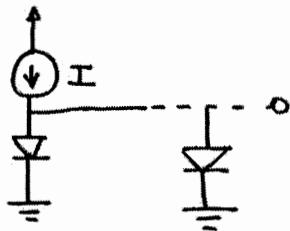

With one diode the current through it is

$$I = I_s e^{\frac{V_1}{nV_T}}$$

With two diodes in parallel, the current splits between each diode so that the diodes each has half the current

$$\frac{I}{2} = I_s e^{\frac{V_2}{nV_T}}$$

$$\therefore \frac{I/2}{I} = e^{\frac{V_2 - V_1}{nV_T}}$$

The change in voltage is

$$\Delta V = V_2 - V_1 = nV_T \ln\left(\frac{1}{2}\right) = \underline{-17.3 \text{ mV}}$$

The current through  $D_1$  is

$$10 I_s e^{\frac{V_1 - V}{nV_T}} = I_2 \quad \textcircled{A}$$

The current through  $D_2$  is

$$I_s e^{\frac{V_2}{nV_T}} = 0.01 - I_2$$

$$I_s = (0.01 - I_2) e^{\frac{V_2}{nV_T}} \quad \textcircled{B}$$

$$\textcircled{B} \rightarrow \textcircled{A} \quad 10(0.01 - I_2) e^{\frac{V_2}{nV_T}} = I_2$$

$$V = -V_T \ln\left(\frac{I_2}{10(0.01 - I_2)}\right)$$

$$= 0.025 \ln\left(\frac{2}{10(8)}\right) = \underline{92.2 \text{ mV}}$$

For  $V = 50 \text{ mV}$


$$-V_T \ln\left(\frac{I_2}{10(10 - I_2)}\right) = 50 \times 10^{-3}$$

$$I_2 = 10(10 - I_2) e^{-2}$$


$$I_2 (1 + 10 e^{-2}) = 100 e^{-2}$$

$$I_2 = \underline{5.75 \text{ mA}}$$

3.20

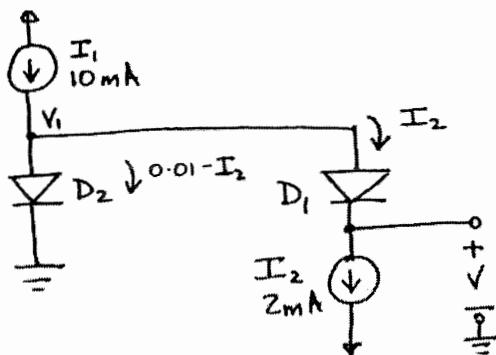

3.21

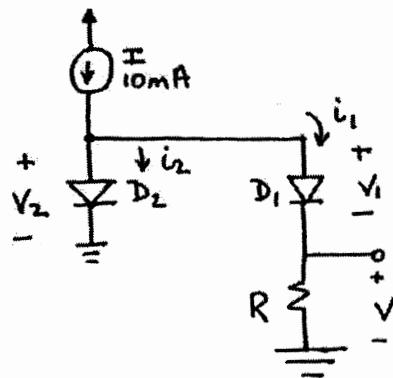

$$i = I_s e^{\frac{V}{nV_T}} \Rightarrow 10 \times 10^{-3} = I_s e^{0.7/n \times 0.025} \quad (1)$$

$$100 \times 10^{-3} = I_s e^{0.8/n \times 0.025} \quad (2)$$

$$\frac{(2)}{(1)} \quad 10 = e^{0.1/n(0.025)}$$

$$n = 1.737$$

$$V = V_2 - V_1 = nV_T \ln\left(\frac{i_2}{i_1}\right) = 80 \text{ mV}$$

$$1.737 (25 \times 10^{-3}) \ln\left(\frac{0.01 - i_1}{i_1}\right) = 80$$

$$i_1 = 1.4 \text{ mA}$$


$$R = 80/i_1 = 80/1.4 = \underline{\underline{57.1 \Omega}}$$

3.22

For a diode conducting a constant current, the diode voltage decreases by approximately 2 mV per increase of 1° C.

$T = -20^\circ \text{C}$  corresponds to a temperature decrease of  $40^\circ \text{C}$ , which results in an increase of the diode voltage by 80 mV. Thus  $V_D = 770 \text{ mV}$ .  
 $T = +70^\circ \text{C}$  corresponds to a temperature increase of  $50^\circ \text{C}$ , which results in a decrease of the diode voltage by 100 mV. Thus  $V_D = 590 \text{ mV}$ .

3.23

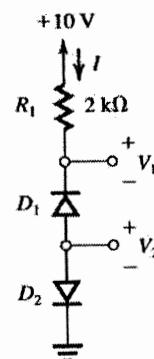


At  $20^\circ \text{C}$ :

$$V_{RI} = V_2 = 520 \text{ mV}$$

$$R_I = 520 \text{ k}\Omega$$

$$I = \frac{520 \text{ mV}}{520 \text{ k}\Omega} = 1 \mu\text{A}$$

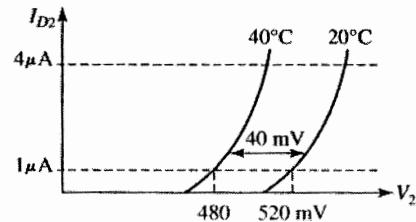At  $40^\circ \text{C}$ ,  $I = 4 \mu\text{A}$



$$V_2 = 480 + 2.3 \times 1 \times 25 \log 4$$

$$= 514.6 \text{ mV}$$

$$V_{RI} = 4 \mu\text{A} \times 520 \text{ k}\Omega = 2.08 \text{ V}$$

$$\text{At } 0^\circ \text{C}, I = \frac{1}{4} \mu\text{A}$$

$$V_2 = 560 - 2.3 \times 1 \times 25 \log 4$$

$$= 525.4 \text{ mV}$$

$$V_{RI} = \frac{1}{4} \times 520 = 0.13 \text{ V}$$

3.24

The voltage drop =  $700 - 580 = 120 \text{ mV}$   
 Since the diode voltage decreases by approximately  $2 \text{ mV}$  for every  $1^\circ\text{C}$  increase in temperature, the junction temperature must have increased by

$$\frac{120}{2} = \underline{\underline{60^\circ\text{C}}}$$

Power being dissipated =

$$580 \times 10^{-3} \times 15 = \underline{\underline{8.7 \text{ W}}}$$

Thermal Resistance =  $\frac{\text{temperature rise}}{\text{Watt}} = \frac{60}{8.7} = \underline{\underline{6.9^\circ\text{C/W}}}$

3.25

$$\begin{aligned} i &= I_s e^{V/nV_T} \\ 10 &= I_s e^{0.8/2(0.025)} \\ I_s &= 1.12 \times 10^{-6} \text{ A} \end{aligned}$$

For current varying between

$i_1 = 0.5 \text{ mA}$  to  $i_2 = 1.5 \text{ mA}$ , the voltage varies from

$$V_1 = 2(0.025) \ln \left( \frac{0.5 \times 10^{-3}}{1.12 \times 10^{-6}} \right) = \underline{\underline{0.305 \text{ V}}}$$

to:

$$V_2 = 2(0.025) \ln \left( \frac{1.5 \times 10^{-3}}{1.12 \times 10^{-6}} \right) = \underline{\underline{0.360 \text{ V}}}$$

∴ the voltage decreases by approximately  $2 \text{ mV}$  for every  $1^\circ\text{C}$  increase in temperature, the voltage may vary by  $\pm 50 \text{ mV}$  for the  $\pm 25^\circ\text{C}$  temperature variation.

3.26


$$\begin{aligned} i &= I_s e^{V/nV_T} \\ \frac{I_{s2}}{I_{s1}} &= \frac{1}{0.1 \times 10^{-3}} = 10^4 \end{aligned}$$

For identical currents

$$\begin{aligned} I_{s1} e^{V_1/nV_T} &= I_{s2} e^{V_2/nV_T} \\ e^{\frac{V_1 - V_2}{nV_T}} &= 10^4 \\ V_1 - V_2 &= nV_T \ln 10^4 \\ &= 2.5 \times 10^{-3} \ln 10^4 \\ &= \underline{\underline{+0.23 \text{ V}}} \end{aligned}$$

I.E. THE VOLTAGE DIFFERENCE BETWEEN THE TWO DIODES IS  $+0.23 \text{ V}$  INDEPENDENT OF THE CURRENT. HOWEVER, SINCE THE TWO CURRENTS CAN VARY BY A FACTOR OF 3 (0.5 mA TO 1.5 mA) THE DIFFERENCE VOLTAGE WILL BE:  
 $0.23 \text{ V} \pm nV_T \ln 3 = 0.23 \text{ V} \pm 2.75 \text{ mV}$   
 SINCE TEMPERATURE CHANGE AFFECTS BOTH DIODES SIMILARLY THE DIFFERENCE VOLTAGE REMAINS CONSTANT.

3.27

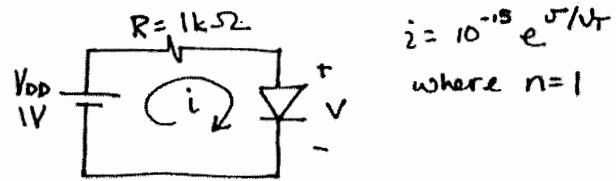


$$i = 10^{-15} e^{V/nV_T}$$

where  $n = 1$

$$V = 0.7 \text{ V} \quad i = 1.45 \text{ mA}$$

$$V = 0.6 \text{ V} \quad i = 0.026 \text{ mA}$$

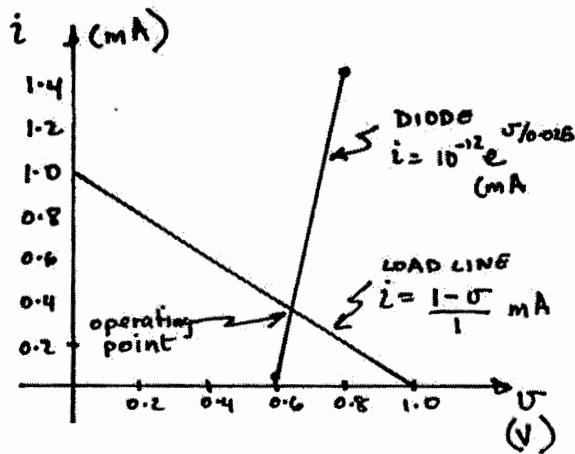A sketch of the graphical construction to determine the operating point is shown below.




From the above sketch we see that the operating point must lie between  $U = 0.6$  and  $0.7$  V and  $i \approx 0.3$  to  $0.4$  mA. To find the point more accurately an enlarged graph is plotted.

$$\text{For } i = 0.3 \text{ mA} = 10^{-12} e^{U/0.025} \\ \Rightarrow U = 660.7 \text{ mV}$$

$$\text{For } i = 0.4 \text{ mA} = 10^{-12} e^{U/0.025} \\ \Rightarrow U = 667.9 \text{ mV}$$

For the load line:
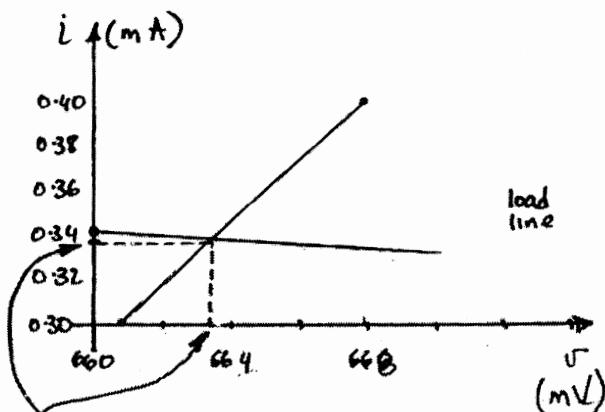
$$U = 660 \text{ mV} \Rightarrow i = 0.34 \text{ mA} \\ U = 670 \text{ mV} \Rightarrow i = 0.33 \text{ mA}$$



Graphical Point  $i = 0.337 \text{ mA}$   
 $U = 663.4 \text{ mV}$

Comparing the graphical results to the exponential model gives:


$$\text{At } i = 0.337 \text{ mA} = 10^{-12} e^{U/0.025}$$

$$\Rightarrow U = 663.6 \text{ mV}$$

which is only  $(663.6 - 663.4) = 0.2 \text{ mV}$  greater than the value found graphically!

### 3.28

Iterative Analysis:

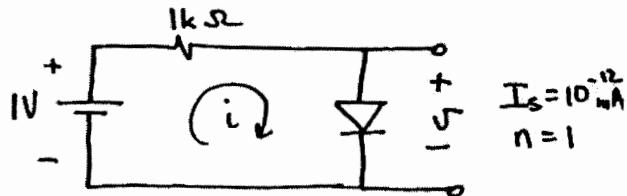

$$\#1 \quad U = 0.7 \text{ V} \quad i = \frac{1 - 0.7}{1} = 0.3 \text{ mA}$$

$$\#2 \quad U = 0.25 \ln\left(\frac{0.3}{10^{-12}}\right) = 0.6607 \text{ V}$$


$$i = \frac{1 - 0.6607}{1} = 0.3393 \text{ mA}$$

$$\#3 \quad U = 0.25 \ln\left(\frac{0.3393}{10^{-12}}\right) = 0.6638 \text{ V}$$

$$i = \frac{1 - 0.6638}{1} = 0.3362$$

∴ i did not change by much stop here.

3.29

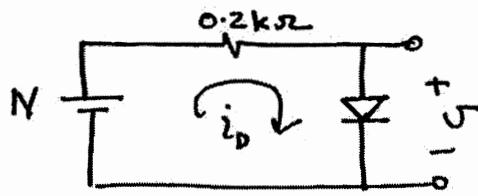

$$(a) i_D = \frac{1-0.7}{0.2} = \underline{1.5 \text{ mA}}$$

(b) Iterative Analysis given  $V_D = 0.7 \text{ V}$   
at  $i_D = 1 \text{ mA}$

$$\#1 \quad V = 0.7 \text{ V} \quad i_D = \frac{1-0.7}{0.2} = 1.5 \text{ mA}$$

$$\#2 \quad i = I_S e^{\frac{V}{nV_T}} \quad n=2$$

$$\frac{i_2}{i_1} = e^{\frac{V_2 - V_1}{0.05}}$$

$$\text{thus } V_2 = V_1 + 0.05 \ln \frac{i_2}{i_1}$$

$$\therefore \text{for } i = 1.5 \text{ mA}$$

$$V = 0.7 + 0.05 \ln \frac{1.5}{1} \quad \frac{1}{i_D} = \frac{1-0.720}{0.2}$$

$$= 0.720 \text{ V} \quad = 1.4 \text{ mA}$$

#3

$$V = 0.720 + 0.05 \ln \left( \frac{1.4}{1.5} \right) \quad \frac{1}{i_D} = \frac{1-0.716}{0.2}$$


$$= 0.716 \text{ V} \quad = 1.42 \text{ mA}$$

#4

$$V = 0.716 + 0.05 \ln \left( \frac{1.42}{1.4} \right) \quad \frac{1}{i_D} = \underline{1.42 \text{ mA}}$$

$$= \underline{0.716 \text{ V}}$$

3.30

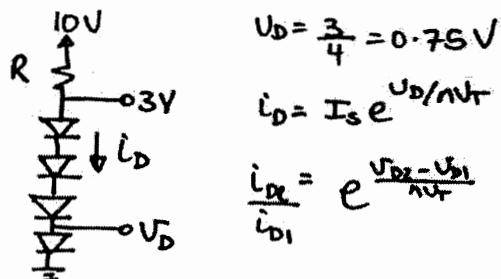

$$V_D = \frac{3}{4} = 0.75 \text{ V}$$

$$i_D = I_S e^{\frac{V_D}{nV_T}}$$

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{V_{D2} - V_{D1}}{nV_T}}$$

$$\therefore i_D = i_{D2} = i_{D1} e^{\frac{V_{D2} - V_{D1}}{nV_T}}$$


$$= 1 \times e^{\frac{0.75 - 0.7}{1 \times 0.025}}$$

$$= 7.389 \text{ mA}$$

$$\therefore R = \frac{10-3}{i_D} = \frac{10-3}{7.389} = \underline{0.947 \text{ k}\Omega}$$

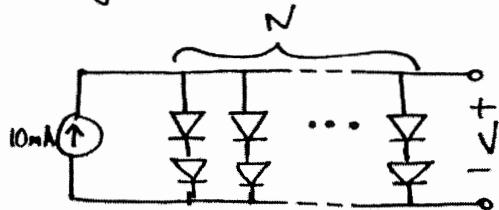3.31

Since  $2V_D = 1.4 \text{ V}$  is close to the required  $1.25 \text{ V}$ , use  $N$  parallel pairs of diodes to split the current evenly.




$$\therefore V = 2 \left[ 0.7 + 0.1 \log \frac{10/N}{20} \right] = 1.25 \text{ V}$$

$$N = 2.8 \Rightarrow \text{Use } \underline{3 \text{ sets of diodes}}$$


$$V = 2 \left( 0.7 + 0.1 \log \frac{10/3}{20} \right) = \underline{1.244 \text{ V}}$$

3.32 ~ CONSTANT VOLTAGE  
DROP MODEL

(a)

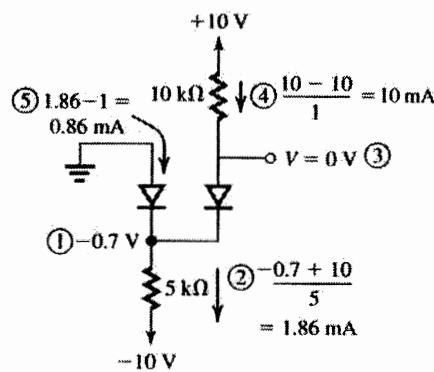


(b)

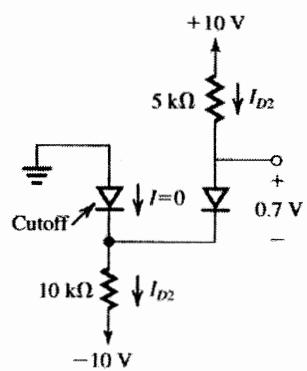


$$v_D = -10 + 1.29(10) + 0.7 = 3.6 \text{ V}$$

3.33

(a)

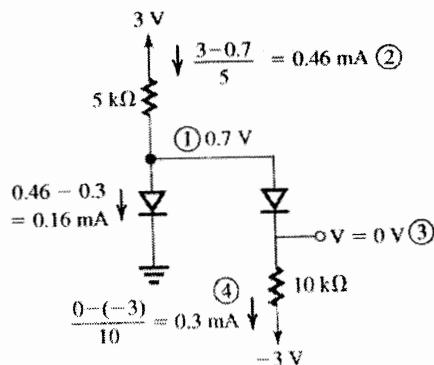


(b)

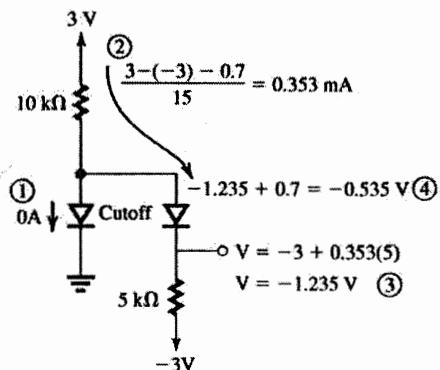


3.34


(a)

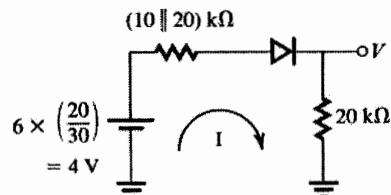

(b)

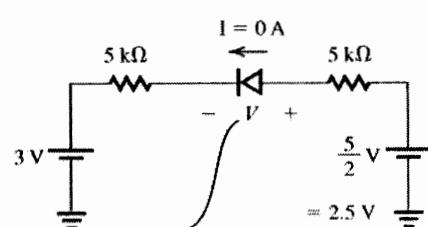

3.35

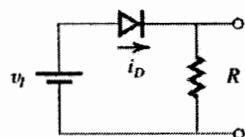

$$i_{D,\text{peak}} = \frac{v_{t,\text{peak}} - 0.7}{R} \leq 50$$

$$R \geq \frac{120\sqrt{2} - 0.7}{50} = 3.38 \text{ k}\Omega$$

Reverse voltage =  $120\sqrt{2} = 169.7 \text{ V}$ .

The design is essentially the same since the supply voltage  $\gg 0.7 \text{ V}$

$$\% \text{ CHANGE} = \begin{cases} (0.670 - 1)100 = -33\% & n=1 \\ (0.819 - 1)100 = -18\% & n=2 \end{cases}$$

For a current change limited to  $\pm 10\%$

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{\Delta V}{n k T / 0.025}} = 0.9 \text{ to } 1.1$$

$$\Delta V = \begin{cases} -2.634 \text{ mV to } 2.383 \text{ mV} & n=1 \\ -5.268 \text{ mV to } 4.766 \text{ mV} & n=2 \end{cases}$$

3.36

Using the exponential model

$$i_D = I_s e^{\frac{\Delta V}{n k T}}$$

FOR A  $+10\text{mV}$  CHANGE


$$\frac{i_{D2}}{i_{D1}} = e^{\frac{\Delta V}{n k T}} = e^{0.01/n(0.025)} \\ = \begin{cases} 1.492 & \sim n=1 \\ 1.221 & \sim n=2 \end{cases}$$

$$\% \text{ CHANGE} = \frac{i_{D2} - i_{D1}}{i_{D1}} \times 100$$

$$= \begin{cases} (1.492 - 1) \times 100 = +49.2\% & n=1 \\ (1.221 - 1) \times 100 = 22.1\% & n=2 \end{cases}$$

FOR A  $-10\text{mV}$  CHANGE
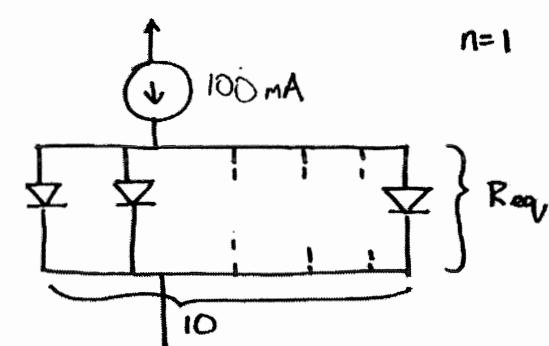
$$\frac{i_{D2}}{i_{D1}} = 10^{-0.01/n(0.025)} = \begin{cases} 0.670 & n=1 \\ 0.819 & n=2 \end{cases}$$



Each diode has the current

$$i_D = \frac{0.1}{10} = 0.01 \text{ A}$$

Each diode has a small-signal resistance

$$r_d = \frac{n k T}{I_D} = \frac{0.025}{0.01} = 2.5 \Omega$$

$$R_{\text{req}} = r_d / 10 = 0.25 \Omega$$

(c)  $I = 10 \mu A$   $I_2 = 990 \mu A$   
 $r_{d1} = \frac{0.025}{10 \times 10^{-6}}$   $r_{d2} = \frac{0.025}{990 \times 10^{-6}}$   
 $= 2.5 k\Omega$   $= 25.25 \Omega$   
 $\frac{V_o}{V_i} = \underline{\underline{0.01 V/V}}$

(d)  $I = 100 \mu A$   $I_2 = 900 \mu A$   
 $r_{d1} = \frac{0.025}{100 \times 10^{-6}}$   $r_{d2} = \frac{0.025}{900 \times 10^{-6}}$   
 $= 250 \Omega$   $= 27.78 \Omega$

$$\frac{V_o}{V_i} = \underline{\underline{0.1 V/V}}$$

(e)  $I = 500 \mu A$   $I_2 = 500 \mu A$   
 $r_{d1} = r_{d2} = \frac{0.025}{500 \times 10^{-6}} = 50 \Omega$


$$\frac{V_o}{V_i} = \underline{\underline{\frac{1}{2} V/V}}$$

(f)  $I = 600 \mu A$   $I_2 = 400 \mu A$   
 $r_{d1} = \frac{0.025}{600 \times 10^{-6}}$   $r_{d2} = \frac{0.025}{400 \times 10^{-6}}$   
 $= 41.67 \Omega$   $= 62.5 \Omega$

WHEN THE BIAS CURRENT IN EACH DIODE IS  $\geq 10 \mu A$ , THE DIODE RESISTANCE WILL BE  $\leq 2.5 \Omega$ . TO LIMIT THE CURRENT SIGNAL TO A MAXIMUM OF 10% OF BIAS, THE CURRENT SIGNAL MUST BE  $\leq 1 \mu A$ . THUS, THE SIGNAL VOLTAGE ACROSS THE "STARVED" DIODE WILL BE 2.5 mV WHICH IS APPROXIMATELY THE VALUE TO WHICH THE INPUT SIGNAL SWING SHOULD BE LIMITED.

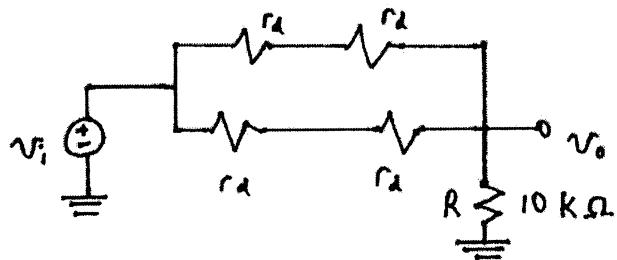3.41  
(a)  $\frac{V_o}{V_i} = \frac{R}{R + (2r_d // 2r_d)}$   
 $= \frac{R}{R + r_d}$

WHERE  $r_d = \frac{V_T}{I/2} = \frac{2V_T}{I}$   
 $= \frac{0.05 V}{I}$



I (mA)	$V_o/V_i (V/V)$
0	0
$10^{-3}$	0.167
0.01	0.667
0.1	0.952
1.0	0.995
10	0.9995

(b) IF THE SIGNAL CURRENT IS TO BE LIMITED TO  $\pm 10I$ , THE CHANGE IN DIODE VOLTAGE  $\Delta V_D$  CAN BE FOUND FROM


$$\frac{i_D}{I} = e^{\Delta V_D / nV_T} = 0.9 \text{ to } 1.1$$

THUS, FOR  $n = 1$

$$\Delta V_D = -2.63 \text{ mV to } +2.38 \text{ mV}$$

OR APPROXIMATELY  $\pm 2.5 \text{ mV}$

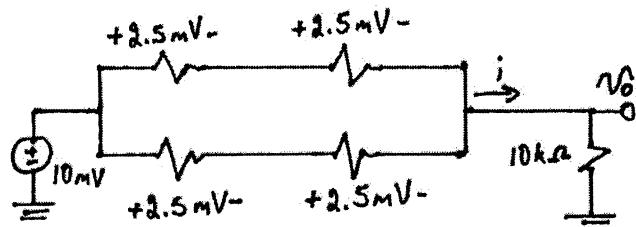(b cont.) FOR THE DIODE CURRENT TO REMAIN WITHIN  $\pm 10\%$  OF THEIR DC BIAS CURRENTS, THE SIGNAL VOLTAGE ACROSS EACH DIODE MUST BE LIMITED TO  $2.5\text{mV}$ . NOW, IF  $V_{i\text{PEAK}} = 10\text{mV}$  WE CAN OBTAIN THE FOLLOWING SITUATION



WE SEE THAT  $V_o = 5\text{mV}$  AND

$$i = \frac{5\text{mV}}{10\text{k}\Omega} = 0.5\mu\text{A}.$$

THUS, EACH DIODE IS CARRYING A CURRENT SIGNAL OF  $0.25\mu\text{A}$ . FOR THIS TO BE AT MOST  $10\%$  OF THE DC CURRENT, THE DC CURRENT IN EACH DIODE MUST BE AT LEAST  $2.5\mu\text{A}$ . IT FOLLOWS THAT THE MINIMUM VALUE OF  $I$  MUST BE  $5\mu\text{A}$ .


(c) FOR  $I = 1\text{mA}$ ,  $I_d = 0.5\text{mA}$ , AND FOR MAXIMUM SIGNAL OF  $10\%$ ,  $I_d = 0.05\text{mA}$ . THUS  $i_d = 2i_d = 0.1\text{mA}$  AND THE CORRESPONDING MAXIMUM  $V_o$  IS  $0.1\text{mA} \times 10\text{k}\Omega = 1\text{V}$ .

THE CORRESPONDING PEAK INPUT CAN BE FOUND BY DIVIDING  $V_o$  BY THE TRANSMISSION FACTOR OF  $0.995$ , THUS


$$V_{i\text{MAX}} = \frac{1\text{V}}{0.995\text{V}} = \underline{\underline{1.005\text{V}}}$$

SEE FIGURE.

EACH DIODE HAS  $r_d = 50\Omega$

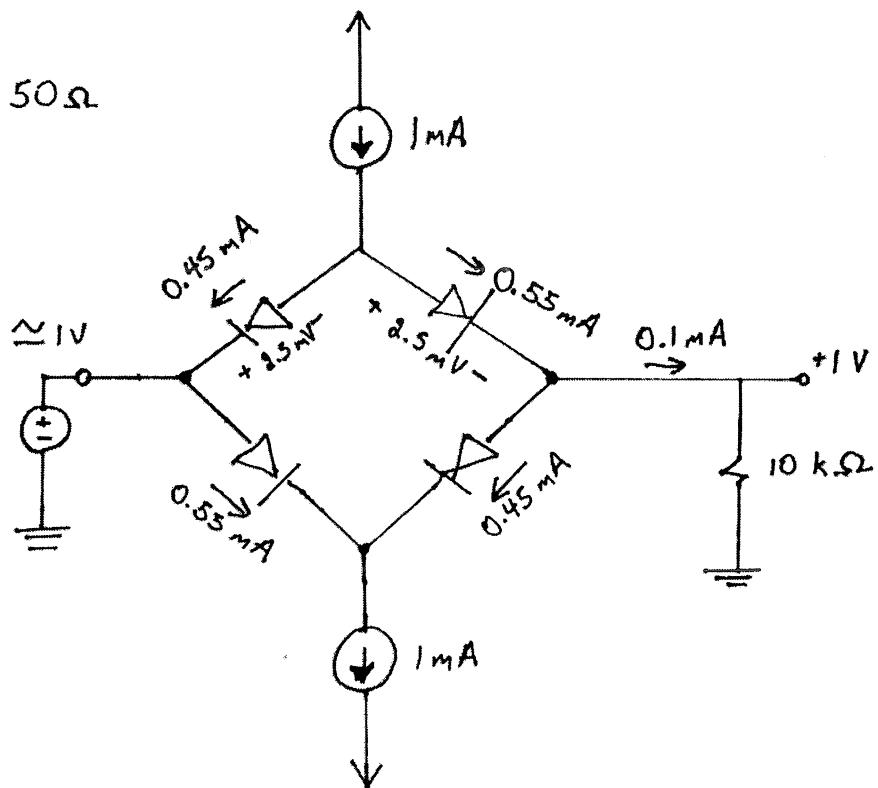

3.42

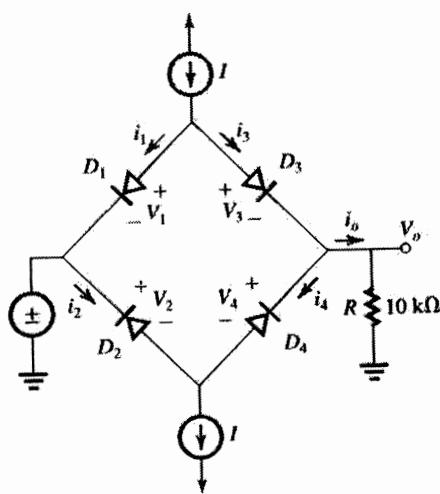

$$I = 1 \text{ mA}$$

Each diode exhibits 0.7 V drop at 1 mA current.  
using diode exponential model we have

$$v_2 - v_1 = V_T \ln\left(\frac{i_2}{i_1}\right)$$

$$\text{and } v_1 = 0.7 \text{ V}, i_1 = 1 \text{ mA}$$

$$\Rightarrow v = 0.7 + V_T \ln\left(\frac{i}{1}\right)$$

$$= 700 + 25 \ln(i)$$

Calculation for different values of  $v_o$

$v_o = 0, i_o = 0$ , the current  $I = 1 \text{ mA}$ , divides equally in  $D_3, D_4$  side and  $D_1, D_2$  side.

$$i_1 = i_2 = i_3 = i_4 = \frac{1}{2} = 0.5 \text{ mA}$$

$$v = 700 + 25 \ln(0.5) \approx 683 \text{ mV}$$

$$v = v_1 = v_3 = 683 \text{ mV}$$

From circuit

$$v_I = -v_1 + v_3 + v_o = -683 + 683 + 0 = 0 \text{ V}$$

$$\text{For } v_o = 1 \text{ V}, i_o = \frac{1}{10 \text{ K}} = 0.1 \text{ mA}$$

Because of symmetry of the circuit

$$i_3 = i_2 = \frac{I}{2} + \frac{i_o}{2} = 0.5 + 0.05 = 0.55 \text{ mA}$$

$$\text{and } i_4 = i_1 = 0.45$$

$$v_3 = v_2 = 700 + 25 \ln\left(\frac{i_2}{1}\right) = 685 \text{ mV}$$

$$v_4 = v_1 = 700 + 25 \ln(i_4) = 680 \text{ mV}$$

$v_o(v)$	$i_o$ (mA)	$i_3 = i_2$ (mA)	$i_4 = i_1$ (mA)	$v_1 = v_2$ (mV)	$v_3 = v_4$ (mV)	$v_I = -v_1 + v_3 + v_o$ (mV)
0	0	0.5	0.5	683	683	0
+1	0.1	0.55	0.45	685	680	1.005
+2	0.2	0.6	0.4	-687	677	2.010
+5	0.5	0.75	0.25	-693	665	5.028
+9	0.9	0.95	0.05	-699	625	9.074
+9.9	0.99	0.995	0.005	-700	568	10.09
9.99	0.999	0.9995	0.0005	-700	510	10.18
10	1	1	0	700	0	10.7

$$v_I = -v_1 + v_2 + v_o = -0.680$$

$$+ 0.685 + 1 = 1.005 \text{ V}$$


Similarly other values are calculated in the table for both positive and negative values of  $v_o$

The largest values of  $v_o$  on positive and negative side are +10 V and -10 V respectively. This restriction is imposed by the current  $I = 1 \text{ mA}$

A similar table can be generated for the negative values. It is symmetrical.


For  $V_I > 10$ ,  $v_o$  will be saturated at 10 V and it is because  $I = 1 \text{ mA}$ .

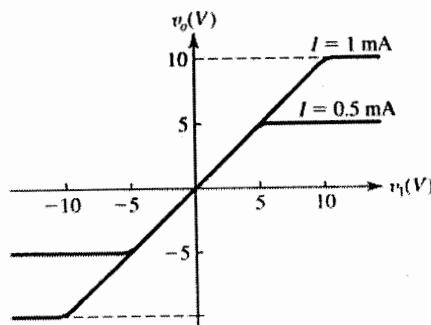For  $I = 0.5 \text{ mA}$ , will saturate at  $0.5 \text{ mA} \times 10 \text{ K} = 5 \text{ V}$



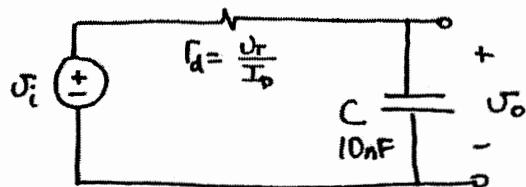3.43

Opening the current source we get the following small-signal circuit :  
(n=1)



$$\frac{V_o}{V_i} = \frac{\frac{1}{sC}}{\frac{1}{sC} + r_d} = \frac{1}{1 + sCr_d}$$

$$\begin{aligned}\text{Phase Shift} &= -\tan^{-1}\left(\frac{wCr_d}{1}\right) \\ &= -\tan^{-1}\left(2\pi 10^5 \times 10 \times 10^{-9} \times 0.025/I\right)\end{aligned}$$

For a phase shift of  $-45^\circ$  we have


$$2\pi 10^5 \times 10(10^{-9}) \times \frac{0.025}{I} = 1$$

$$I = \underline{157 \mu\text{A}}$$

Range of phase shift for  $I = 15.7 \mu\text{A}$  to  $157 \mu\text{A}$  is :

$$\underline{-84.3^\circ \text{ to } -5.71^\circ}$$

3.44

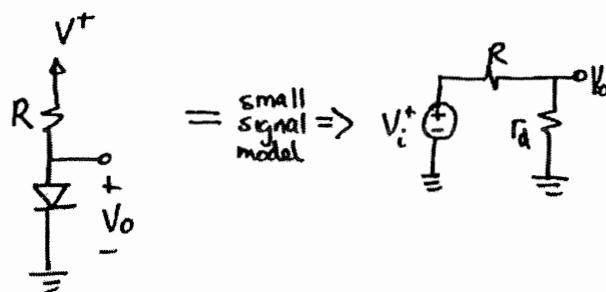

$$\begin{aligned}(a) \frac{\Delta V_o}{\Delta V^+} &= \frac{r_d}{r_d + R} = \frac{nV_T/I}{nV_T/I + R} \\ &= \frac{nV_T}{nV_T + IR} \quad \text{where at No load} \\ &= \frac{nV_T}{nV_T + V^+ - 0.7} \quad I = \frac{V^+ - 0.7}{R} \\ &= \underline{\underline{\frac{nV_T}{nV_T + V^+ - 0.7}}} \quad Q.E.D.\end{aligned}$$

(b) For m diodes in series use

$$I = \frac{V^+ - m \times 0.7}{R}$$

Thus:


$$\begin{aligned}\frac{\Delta V_o}{\Delta V^+} &= \frac{m r_d}{m r_d + R} = \frac{m(nV_T)}{m(nV_T) + IR} \\ &= \frac{m(nV_T)}{m(nV_T) + V^+ - 0.7m}\end{aligned}$$

(c) Line Regulation for  $V^+ = 10\text{V}$ ,  $n=2$

$$i) m=1 \quad \frac{\Delta V_o}{\Delta V^+} = \underline{\underline{5.35 \text{ mV/V}}}$$

$$ii) m=3 \quad \frac{\Delta V_o}{\Delta V^+} = \underline{\underline{18.63 \text{ mV/V}}}$$

3.45

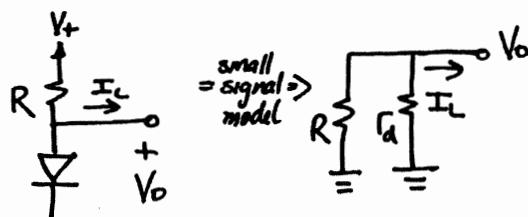

$$\Delta V_o = -I_L (R_L \parallel r_d)$$

$$\frac{\Delta V_o}{I_L} = \underline{-(R_L \parallel r_d)} \quad Q.E.D.$$

$$(b) \text{ Given at DC } I_D = \frac{V^+ - 0.7}{R}$$

$$\text{Also } r_d = \frac{nV_T}{I_D}$$

We have:

$$\begin{aligned} \frac{\Delta V_o}{I_L} &= -\frac{1}{\frac{1}{R} + \frac{1}{r_d}} \\ &= -\frac{1}{\frac{I_D}{V^+ - 0.7} + \frac{I_D}{nV_T}} \\ &= -\frac{nV_T}{I_D} \cdot \frac{1}{1 + \frac{nV_T}{V^+ - 0.7}} \\ &= -\frac{nV_T}{I_D} \cdot \frac{V^+ - 0.7}{V^+ - 0.7 + nV_T} \quad Q.E.D. \end{aligned}$$

$$\text{For } \frac{\Delta V_o}{I_L} \leq 5 \frac{mV}{mA}$$

$$-\frac{2 \times 0.025}{I_D} \times \frac{10 - 0.7}{10 - 0.7 + 0.05} \leq \frac{5 \times 10^{-3}}{10^{-3}}$$

$$I_D \geq 9.947 mA \Rightarrow I_D = \underline{10 mA}$$

$$R = \frac{V^+ - 0.7}{I_D} = \frac{10 - 0.7}{10} = \underline{930 \Omega}$$

Thus the diode should be a 10mA diode.

(c) For  $m$  diodes

$$I_D = \frac{V^+ - 0.7m}{R} \quad \& \quad r_d = \frac{m(nV_T)}{I_D}$$


$$\frac{\Delta V_o}{I_L} = \frac{-1}{\frac{1}{R} + \frac{1}{r_d}}$$

$$= \frac{-1}{\frac{I_D}{V^+ - 0.7m} + \frac{I_D}{mnV_T}}$$

$$= -\frac{mnV_T}{I_D} \cdot \frac{1}{\frac{mnV_T}{V^+ - 0.7m} + 1}$$

$$= -\frac{mnV_T}{I_D} \cdot \frac{V^+ - 0.7m}{V^+ - 0.7m + mnV_T}$$

3.46

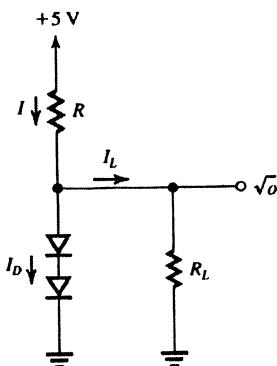

$$R_L = 100 \Omega; \quad I_L = \frac{1.5}{100} = 15 \text{ mA}$$

The diode current reduced by  $= 15 - 10 = 5 \text{ mA}$   
 $\therefore \Delta V_o = -5 \text{ mA} \times r_d = -1.7 \text{ mV}$

$$R_L = 75 \Omega; \quad I_L = \frac{1.5}{75} = 20 \text{ mA}$$

Diode current reduced by  $20 - 10 = 10 \text{ mA}$   
 $\therefore \Delta V_o = -10 \text{ mA} \times r_d = -10 \times 0.34 = -3.4 \text{ mV}$

$$R_L = 50 \Omega; \quad I_L = \frac{1.5}{50} = 30 \text{ mA}$$

Diode current reduced by  $30 - 10 = 20 \text{ mA}$   
 $\Delta V_o = -20 \text{ mA} \times r_d = 6.8 \text{ mV}$

Diode has 0.7 V drop at 10 mA current

$$v_o = 1.5 \text{ V when } R_L = 150 \Omega$$

$$I_D = I_S e^{\frac{V_T}{V_T}}$$

$$10 \times 10^{-3} = I_S e^{0.7/0.025}$$

$$\Rightarrow I_S = 6.91 \times 10^{-15} \text{ A}$$

$$\text{Voltage drop across each diode} = \frac{1.5}{2} = 0.75 \text{ V}$$

$$\therefore I_D = I_S e^{\frac{V_T}{V_T}} = 6.91 \times 10^{-15} \times e^{0.75/0.025} \\ = 73.9 \text{ mA}$$

$$I_L = 1.5 / 150 = 10 \text{ mA}$$

$$I = I_D + I_L = 73.9 \text{ mA} + 10 \text{ mA} \\ = 83.9 \text{ mA}$$

$$\therefore R = \frac{5 - 1.5}{83.9 \text{ mA}} = 41.7 \Omega$$

Use small signal model to find voltage  $v_o$  when load resistor,  $R_L$ , has lower values

$$r_d = \frac{V_T}{I_D} = \frac{0.025}{73.9} = 0.34 \Omega$$

When load is disconnected all the current  $I$  flows through the diode.

$$\therefore I_D = I = 83.9 \text{ mA}$$

$$v_D = V_T \ln\left(\frac{I_D}{I_S}\right) = 0.025 \times \ln\left(\frac{83.9 \times 10^{-3}}{6.91 \times 10^{-15}}\right)$$


$$v_D = 0.753 \text{ V}$$

$$\text{So No load, } v_o = 2 v_D = 2 \times 0.753 = 1.506 \text{ V.}$$

$$\text{Increase in voltage} = 1.506 - 1.5 = 0.006 \text{ V}$$

Now load is changed

3.47

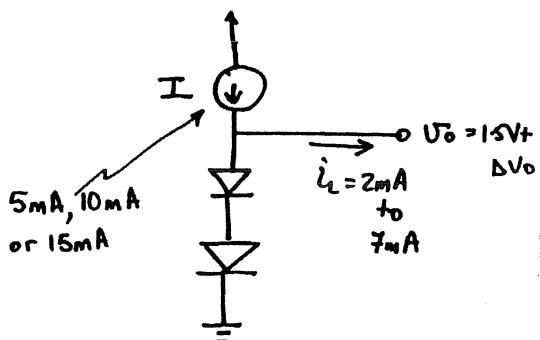

For a load current of 2 to 7 mA,  $I$  must be greater than 7 mA. Thus the 5 mA source would not do.

We are left to choose between the 10 and 15 mA sources. The 15 mA source provides lower load regulation because the diodes will have more current flowing through them at all times.

This is shown below:

Load Regulation if  $I = 10 \text{ mA}$

$$\text{use } \frac{\Delta V_o}{I_{D2}} = e^{\frac{\Delta V_o}{2 \times nV_T}} \cdot z_{\text{diodes}}$$

$$\therefore e^{\frac{\Delta V_o}{0.05 \times 2}} = \frac{3}{10} \text{ to } \frac{8}{10}$$

$$\Delta V_o = -120 \text{ mV} \text{ to } -22.3 \text{ mV}$$

$\therefore$  The peak to peak ripple is  
 $-120 - (-22.3) \approx -100 \text{ mV}$

$$\begin{aligned} \text{Load Regulation} &= \frac{\Delta V_o}{I_L} = \frac{-100}{5} \\ &= -20 \frac{\text{mV}}{\text{mA}} \end{aligned}$$

Load Regulation for  $I = 15 \text{ mA}$ .


Here the current through the diodes change from 8 to 13 mA corresponding to

$$\begin{aligned} \Delta V_o &= 0.1 \ln \left( \frac{8}{13} \right) \\ &= -49 \text{ mV} \end{aligned}$$

$$\text{Load Regulation} = \frac{-49}{5} \approx -10 \frac{\text{mV}}{\text{mA}}$$

The obvious disadvantage of using the 15 mA supply is the requirement of higher current and higher power dissipation.

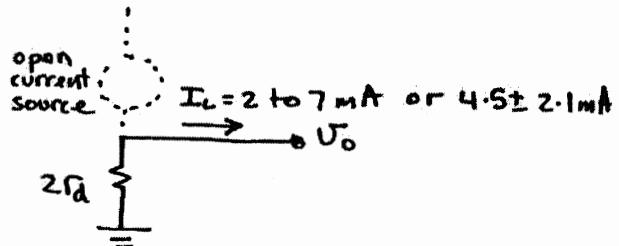Alternate solution of Line Regulation using the small signal model



$$\text{Load Regulation} = \frac{\Delta V_o}{I_L} = -2r_d = -\frac{2nV_T}{I_D}$$


Where the bias current  $I_D = 10 - 4.5$  for the 10 mA source.

$$\Rightarrow \frac{\Delta V_o}{I_L} = -\frac{2 \times 2 \times 0.025}{10 - 4.5} = -18.2 \frac{\text{mV}}{\text{mA}}$$


For 15 mA source  $I_D = 15 - 4.5$

$$\frac{\Delta V_o}{I_L} = -\frac{0.1}{15 - 4.5} = -9.5 \frac{\text{mV}}{\text{mA}}$$

Sketch of output:-

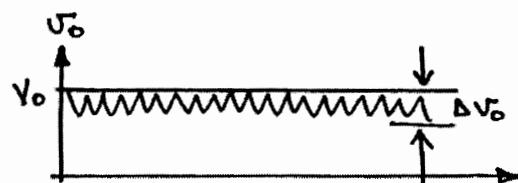

3.48

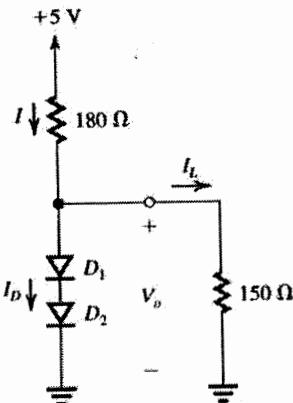

Both diodes are 0.7 V, 10 mA diodes  
First find  $V_o$  with no load, i.e.  $I_L = 0$  and  $I = I_L$ .  
Use iteration to find  $V_o$  and  $I_D$

$$I_D = \frac{5 - 0.7 \times 2}{180 \Omega} = 20 \text{ mA}$$

$$V_2 - V_1 = 2.3V_T \log\left(\frac{I_2}{I_1}\right)$$

$$V_2 = 0.7 + 2.3 \times 25 \times 10^{-3} \times \log\left(\frac{20}{10}\right) = 0.717 \text{ V}$$

$$I_D = \frac{5 - 0.717 \times 2}{180} = 23.79 \text{ mA}$$

$$V_2 = 0.7 + 2.3V_T \log\left(\frac{23.79}{10}\right) = 0.7216 \text{ V}$$

$$I_D = \frac{5 - 2 \times 0.7216}{180} = 19.76 \text{ mA}$$

$$V_2 = 0.7 + 2.3V_T \log\left(\frac{19.76}{10}\right) = 0.717 \text{ V}$$

$$I_D = \frac{5 - 2 \times 0.717}{180} = 19.81 \text{ mA} = I$$

It is almost similar to earlier result, we stop iteration here

$$V_D = 0.717 \text{ V} \text{ and } I_D = 19.81 \text{ mA}$$

$$\text{So } V_o = 2 \times 0.717 = 1.434 \text{ V}$$

a. Load of 150 Ω is connected

$$I_L = \frac{0.717 \times 2}{150} = 9.56 \text{ mA}$$

$$\therefore I_D = I_F 9.56 = 19.81 - 9.56 = 10.25 \text{ mA}$$

So now

$$V_o = 2V_D = 2\left[0.7 + 2.3V_T \log\left(\frac{10.25}{10}\right)\right] = 1.401 \text{ V}$$

b. As found earlier, with no load  $V_o = 1.434 \text{ V}$

c. With 150 Ω load connected and  $V_o$  is lowered by 0.1 V of its nominal value.

$$V_o = 1.401 - 0.1 = 1.301 \text{ V}$$

Voltage across each diode =  $1.301/2 = 0.6505 \text{ V}$

$$I_D = 10 \times 10^{-3} e^{\Delta V / V_T} \text{ where}$$

$$\Delta V = \frac{1.401 - 1.301}{2} = 0.05 \text{ V}$$

$$= 7.4 \text{ mA}$$

$$I_L = \frac{1.301 \text{ V}}{150 \Omega} = 8.7 \text{ mA}$$

$$\therefore I = I_D + I_L = 16.1 \text{ mA}$$

d. New value of 5V supply =

$$180 \Omega \times 16.1 \text{ mA} + V_o \approx 4.2 \text{ V}$$

So the 5 V supply can be lowered to ~ 4.2 V

d. New value of the voltage supply = 5 + (5 - 4.2) = 5.8 V. Now do the problem again as done in the beginning and in parts a and b.

$$I_D = \frac{5.8 - 2 \times 0.7}{180} = 24.4 \text{ mA}$$

$$V_2 = V_1 + 2.3V_T \log\left(\frac{I_2}{I_1}\right)$$

$$= 0.7 + 2.3V_T \log\left(\frac{24.4}{10}\right)$$

$$= 0.722 \text{ V}$$

$$I_D = \frac{5.8 - 2 \times 0.722}{180}$$

$$= 24.2 \text{ mA}$$

Doing one more iteration, almost same value is obtained

$$\therefore V_D = 0.722 \text{ V}, I_D = 24.2 \text{ mA}$$

Now when 150 Ω load is present

$$I_L = \frac{2 \times 0.722}{150} = 9.6 \text{ mA}$$

$$\text{So } I_D = 24.2 - 9.6 = 14.6 \text{ mA}$$

$$\therefore V_D = 0.7 + 2.3 \times V_T \log\left(\frac{14.6}{10}\right)$$

$$= 0.7095 \text{ V}$$

$$V_o = 2 V_D \approx 1.42 \text{ V}$$

e. Loaded output voltage = 1.42 V

f. Percentage change in output voltage

$$= \frac{1.42 - 1.301}{5.8 - 4.2} \times 100$$

$$\approx 7.4\%$$

3.49

$$(a) V_z = V_{z0} + r_z I_{zT}$$

$$10 = 9.6 + r_z \times 50 \times 10^{-3}$$

$$r_z = \underline{8.52}$$

Power rating:

$$V_z = V_{z0} + r_z \times 2I_{zT}$$

$$= 9.6 + 8 \times 100 \times 10^{-3}$$

$$= 10.4 \text{ V}$$

$$P = 10.4 \times 100 \times 10^{-3} = \underline{1.04 \text{ W}}$$

$$(b) V_z = V_{z0} + r_z I_{zT}$$

$$9.1 = V_{z0} + 30 \times 10 \times 10^{-3}$$

$$V_{z0} = \underline{8.8 \text{ V}}$$

$$V_z = 8.8 + 30 \times 20 \times 10^{-3} = 9.4 \text{ V}$$

$$P = 9.4 \times 20 \times 10^{-3} = \underline{188 \text{ mW}}$$

$$(c) 6.8 = 6.6 + 2 \times I_{zT}$$

$$I_{zT} = \underline{100 \text{ mA}}$$

$$V_z = 6.6 + 2 \times 200 \times 10^{-3} = 7 \text{ V}$$

$$P = 7 \times 200 \times 10^{-3} = \underline{1.4 \text{ W}}$$

$$(d) 18 = 17.2 + r_z \times 5 \times 10^{-3}$$

$$r_z = \underline{160 \Omega}$$

$$V_z = 17.2 + 160 \times 10 \times 10^{-3} = 18.8 \text{ V}$$

$$P = 18.8 \times 10 \times 10^{-3} = \underline{188 \text{ mW}}$$

$$(e) 7.6 = V_{z0} + 1.5 \times 200 \times 10^{-3}$$

$$V_{z0} = \underline{7.2 \text{ V}}$$

$$V_z = 7.2 + 1.5 \times 400 \times 10^{-3} = 7.8 \text{ V}$$

$$P = 7.8 \times 400 \times 10^{-3} = \underline{3.12 \text{ W}}$$

3.50


(a) Three 6.8 V zeners provide  $3 \times 6.8 = 20.4 \text{ V}$  with  $3 \times 10 = 30 \Omega$  resistance. Neglecting R, we have

Load Regulation =  $-30 \text{ mV/mA}$ .

(b) For 5.1 V zeners we use 4 diodes to provide 20.4 V with  $4 \times 30 = 120 \Omega$  resistance.  
Load regulation =  $-120 \text{ mV/mA}$

3.51

Small signal model for line regulation:

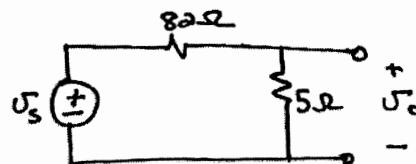

$$\frac{\Delta V_o}{\Delta V_s} = \frac{5}{5+82}$$

$$\Delta V_o = \frac{5}{87} \times \Delta V_s$$

$$= \frac{5}{87} \times 1.3$$

$$= \underline{74.7 \text{ mV}}$$

3.52

$$r_a = 30 \Omega$$

$$I_{ZK} = 0.5 \text{ mA}$$

$$V_Z = 7.5 \text{ V}$$

$$I_Z = 12 \text{ mA}$$

$$7.5 = V_{Z0} + 12 \times 30 \times 10^{-3}$$

$$\Rightarrow V_{Z0} = 7.14 \text{ V}$$


$$I_Z = \frac{7.5}{1.2} = 6.25 \text{ mA}$$

SELECT  $I = 10 \text{ mA}$

SO THAT  $I_Z = 3.7 \text{ mA}$

WHICH IS  $> I_{ZK}$
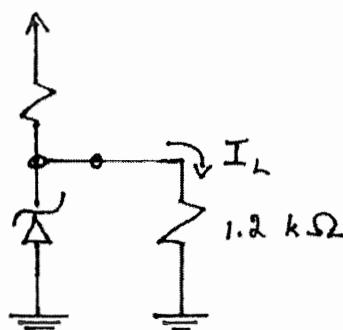
$$R = \frac{10 - 7.5}{10} = \underline{\underline{250 \Omega}}$$



For  $\Delta V^+ = \pm 1 \text{ V}$



$$\Delta V_o = \pm 1 \times \frac{1.2 // 0.03}{0.250 + (1.2 // 0.03)}$$

$$= \pm 0.1 \text{ V}$$

THUS  $V_o = +7.4 \text{ V}$  TO  $+7.6 \text{ V}$   
WITH  $V^+ = 11 \text{ V}$  AND  $I_L = 0$

$$V_o = V_{Z0} + \frac{11 - V_o}{0.25} \times 0.03$$

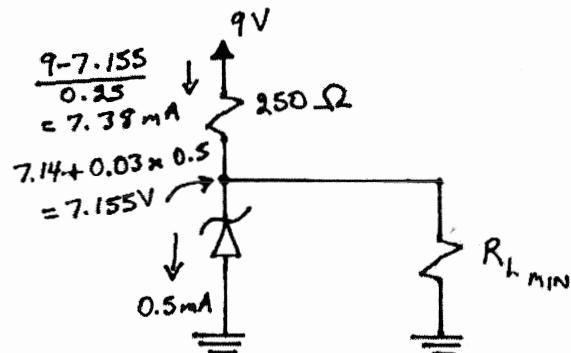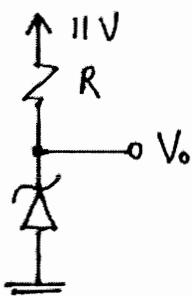
$$\Rightarrow V_o = \underline{\underline{7.55 \text{ V}}}$$



$$R_{L_{\min}} = \frac{7.155}{7.38 - 0.5}$$

$$= \underline{\underline{1.04 \text{ k}\Omega}}$$

3.53

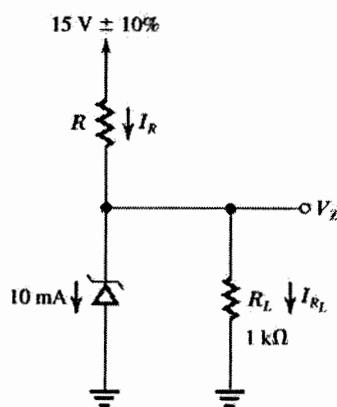

$$V_z = V_{zo} + r_z I_z$$

$$9.1 = V_{zo} + 30(0.009)$$

$$V_{zo} = 8.83 \text{ V}$$

$$V_z = 8.83 + 30(0.01) = 9.13 \text{ V}$$

$$I_{RL} = 9.13 / 1 \text{ k}\Omega = 9.13 \text{ mA}$$

$$I_R = 10 + 9.13 = 19.13 \text{ mA}$$

$$\therefore R = \frac{15 - 9.13}{19.13} = 306.8 \Omega$$

$$\approx 300 \Omega$$

$$V_z = 8.83 + 30 \left( \frac{15 - V_z}{300} - \frac{V_z}{1000} \right)$$

$$= 10.33 - \frac{V_z}{10} - \frac{3}{100} V_z$$

$$V_z = 9.14 \text{ V}$$

$$V_z = 8.83 + 30 \left( \frac{15 \pm 1.5 - V_z}{300} - \frac{V_z}{1000} \right)$$

$$= \frac{1}{1.13} [8.83 + 1.5 \pm 0.15] = 9.14 \pm 0.13 \text{ V}$$

$\pm 0.13 \text{ V}$  variation in output voltage  
Halving the load current  $= R_L$  doubling

$$V_z = 8.83 + 30 \left( \frac{15 - V_z}{300} - \frac{V_z}{2000} \right)$$

$$= \frac{10.33}{1.115} = 9.26 \text{ V}$$


$9.26 - 9.14 = 0.12 \text{ V}$  increase in output voltage.

At the edge of the breakdown region

$$V_z \approx V_{zo} = 8.83 \text{ V} \quad I_{ZK} = 0.3 \text{ mA}$$

$$R_L = \frac{8.83}{\frac{13.5 - 8.83}{300} - 0.0003}$$

$$\approx 578 \Omega$$

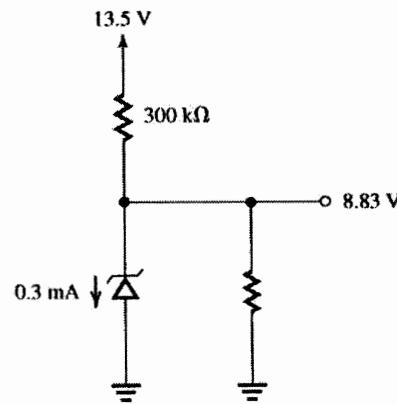


$$\text{Lowest output voltage} = 8.83 \text{ V}$$


$$\begin{aligned} \text{Line Regulation} &= \frac{r_z}{R + r_z} = \frac{30}{300 + 30} \\ &= 90 \frac{\text{mV}}{\text{V}} \end{aligned}$$

$$\text{Load Regulation} = -(r_z \parallel R) = -29.1 \frac{\text{mV}}{\text{mA}}$$



3.54

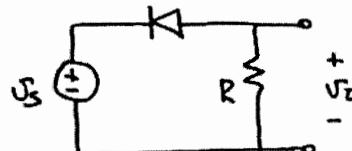

Using the constant voltage drop model:

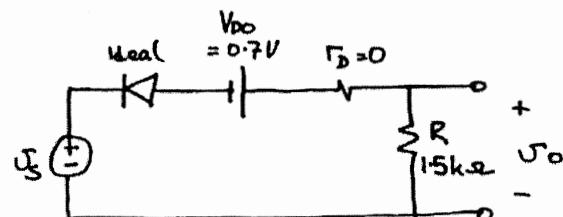

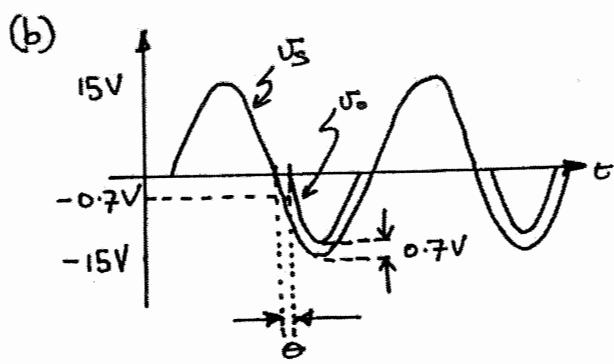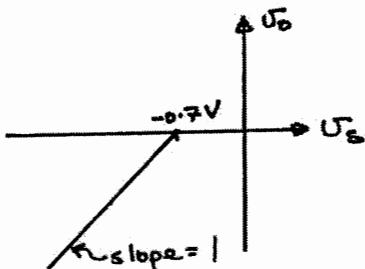(a)  $U_o = U_s + 0.7 \text{ V}$ , for  $U_s \leq -0.7 \text{ V}$   
 $U_o = 0$ , for  $U_s \geq -0.7 \text{ V}$



(c) The diode conducts at an angle  
 $\theta = \sin^{-1} \frac{0.7}{15} = 2.67^\circ$  & stops  
at  $\pi - \theta = 177.33^\circ$

Thus the conduction angle is  $\pi - 2\theta$   
 $= 174.66^\circ$  or  $3.05 \text{ rad.}$

$$U_{o,\text{avg}} = \frac{-1}{2\pi} \int_0^{\pi-\theta} (15 \sin \phi - 0.7) d\phi$$

$$= \frac{-1}{2\pi} \left[ -15 \cos \phi - 0.7\phi \right]_0^{\pi-\theta}$$

$$= \frac{-1}{2\pi} \left[ 15 \times 2 \cos \theta - 0.7 (\pi - 2\theta) \right]$$

$$= \underline{\underline{-4.43 \text{ V}}}$$


(d) Peak current in diode is:

$$\frac{15 - 0.7}{1.5 \times 10^3} = \underline{\underline{9.5 \text{ mA}}}$$

(e) PIV occurs when  $U_s$  is at its  
the peak and  $U_o = 0$ .

$$\text{PIV} = \underline{\underline{15 \text{ V}}}$$

3.55

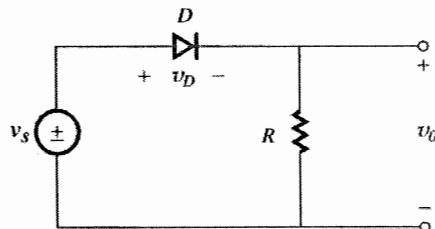

$$i_D = I_S e^{v_D/v_T}$$

$$\frac{i_D}{i_D(1 \text{ mA})} = e^{(v_D - v_D(\text{at } 1 \text{ mA}))/V_T}$$

$$v_D - v_D(\text{at } 1 \text{ mA}) = V_T \ln \frac{i_D}{1 \text{ mA}}$$



$$v_D = v_D(\text{at } 1 \text{ mA}) + V_T \ln \left[ \frac{v_o/R}{10^{-3}} \right]$$

$$v_o = v_s - v_D$$

$$= v_s - v_D(\text{at } 1 \text{ mA}) - V_T \ln \left( \frac{v_o}{R} \right)$$

where  $R$  is in  $\text{k}\Omega$

3.56

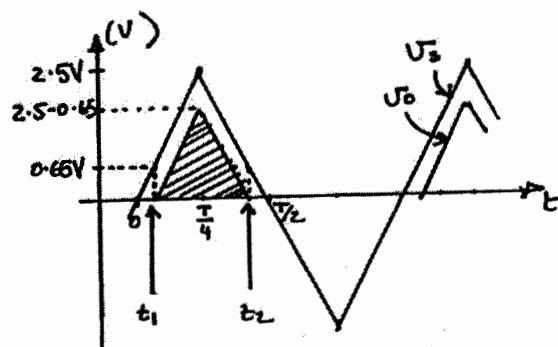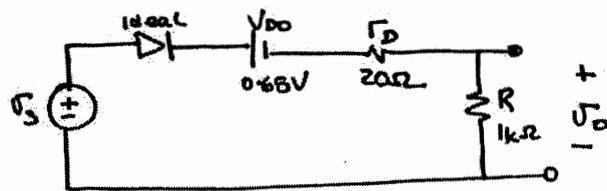

Find  $t_1$  &  $t_2$  by:

$$\frac{2.5}{T/4} = \frac{0.65}{t_1} \Rightarrow t_1 = 0.065T$$

$$t_2 = T/2 - 0.065T = 0.435T$$


$$V_{o,\text{avg}} = \frac{1}{T} \int_T \frac{R}{R+r_D} (V_s - 0.65) dt$$

$$= \frac{1}{T} \frac{R}{R+r_D} (\text{AREA OF SHADED})$$

$$= \frac{1}{T} \frac{R}{R+r_D} (2.5 - 0.65) \left( \frac{T}{4} - 0.065T \right)$$

$$= \frac{1000}{1020} (0.342) = \underline{\underline{0.335V}}$$

3.57

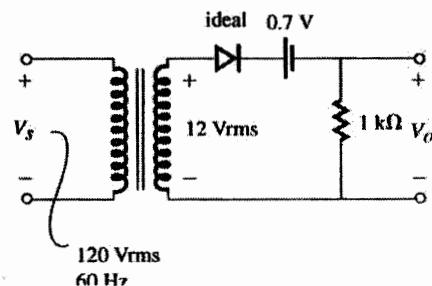

$$V_o = 12\sqrt{2} - 0.7 = 16.27 \text{ V}$$

Conduction begins at

$$v_s = 12\sqrt{2}\sin\theta = 0.7$$

$$\theta = \sin^{-1}\left(\frac{0.7}{12\sqrt{2}}\right)$$

$$= 0.0412 \text{ rad}$$

Conduction ends at  $\pi - \theta$

$$\therefore \text{Conduction angle} = \pi - 2\theta = 3.06 \text{ rad}$$

The diode conducts for


$$\frac{3.06}{2\pi} \times 100 = 48.7\% \text{ of the cycle}$$

$$V_{o,\text{avg}} = \frac{1}{2\pi} \int_0^{\pi-\theta} (12\sqrt{2}\sin\phi - 0.7)d\phi$$

$$= 5.06 \text{ V}$$

$$i_{D,\text{avg}} = \frac{V_{o,\text{avg}}}{R} = 5.06 \text{ mA}$$
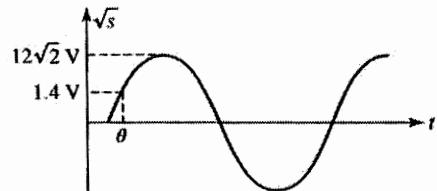
$$\begin{aligned}
 \text{Peak voltage across } R &= 12\sqrt{2} - 2V_D \\
 &= 12\sqrt{2} - 1.4 \\
 &= 15.57 \text{ V}
 \end{aligned}$$



$$\theta = \sin^{-1} \frac{1.4}{12\sqrt{2}} = 0.0826 \text{ rad}$$

Fraction of cycle that  $D_1$  &  $D_2$  conduct is


$$\frac{\pi - 2\theta}{2\pi} \times 100 = 47.4\%$$

Note  $D_3$  &  $D_4$  conduct in the other half cycle so that there is  $2(47.4) = 94.8\%$  conduction interval.

$$\begin{aligned}
 v_{0,\text{avg}} &= \frac{2}{2\pi} \int_0^{\pi} (12\sqrt{2}\sin\phi - 2V_D)d\phi \\
 &= \frac{1}{\pi} [-12\sqrt{2}\cos\phi - 1.4\phi]_0^{\pi} \\
 &= \frac{2(12\sqrt{2}\cos 0)}{\pi} - \frac{1.4(\pi - 2\theta)}{\pi} \\
 &= 9.44 \text{ V}
 \end{aligned}$$

$$i_{R,\text{avg}} = \frac{v_{0,\text{avg}}}{R} = \frac{9.44}{1} = 9.44 \text{ mA}$$

### 3 . 58

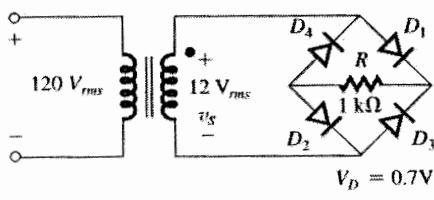

### 3 . 59

$$120\sqrt{2} \pm 10\% : 24\sqrt{2} \pm 10\%$$

⇒ turns Ratio = 5:1

$$v_S = \frac{24\sqrt{2}}{2} \pm 10\%$$

$$\text{PIV} = 2V_S|_{\text{max}} - V_{DO}$$




$$= 2 \times \frac{24\sqrt{2}}{2} \times 1.1 - 0.7$$

$$= 36.6 \text{ V}$$

using a factor of 1.5 for safety we select a diode having a PIV rating of 55 V

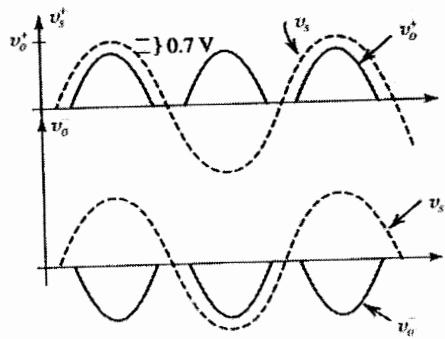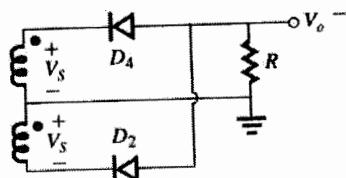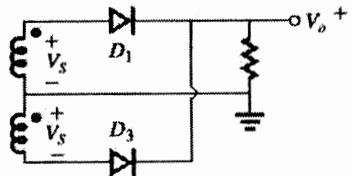3.60

The circuit is a full wave rectifier with centre-tapped secondary winding. The circuit can be analyzed by looking at  $v_0^+$  and  $v_0^-$  separately.



$$v_{0,\text{avg}} = \frac{1}{2\pi} \int (V_s \sin \phi - 0.7) d\phi = 15 \\ = \frac{2V_s}{\pi} - 0.7 = 15$$

assumed  $V_s \gg 0.7$  V

$$V_s = \frac{15 + 0.7}{2}\pi = 24.66 \text{ V}$$

Thus voltage across secondary winding

$$= 2V_s = 49.32 \text{ V}$$



Looking at  $D_4$

$$\text{PIV} = V_s - V_o^- \\ = V_s + (V_s - 0.7) \\ = 2V_s - 0.7 \\ = 48.6 \text{ V}$$

If choosing a diode, allow a safety margin of

$$1.5 \text{ PIV} = 73 \text{ V}$$

3.61

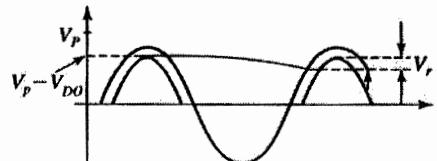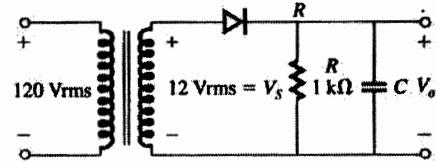

$$(i) v_r \cong (V_p - V_{D0}) \frac{T}{CR} \quad \text{Eq. (4.28)}$$

$$0.1(V_p - V_{D0}) = (V_p - V_{D0}) \frac{T}{CR}$$

$$C = \frac{1}{0.1 \times 60 \times 10^3} = 166.7 \mu\text{F}$$

(ii) for

$$v_r = 0.01(V_p - V_{D0}) = \frac{(V_p - V_{D0})T}{CR}$$

(a)

$$(i) v_{0,\text{avg}} = V_p - V_{D0} - \frac{1}{2}V_f \\ = 12\sqrt{2} - 0.7 - \frac{1}{2}(12\sqrt{2} - 0.7)0.1 \\ = (12\sqrt{2} - 0.7)\left(1 - \frac{0.1}{2}\right) \\ = 15.5 \text{ V}$$

$$(ii) v_{0,\text{avg}} = (12\sqrt{2} - 0.7)\left(1 - \frac{0.01}{2}\right) \\ = 16.19 \text{ V}$$

(b)

i) we have the conduction angle =

$$\begin{aligned}\omega\Delta t &\approx \sqrt{2V_r/(V_p - V_{D0})} \\ &= \sqrt{\frac{2 \times 0.1(V_p - 0.7)}{(V_p - 0.7)}} \\ &= \sqrt{0.2} \\ &= 0.447 \text{ rad}\end{aligned}$$

∴ Fraction of cycle for

$$\begin{aligned}\text{conduction} &= \frac{0.447}{2\pi} \times 100 \\ &= 7.1\%\end{aligned}$$

$$(ii) \omega\Delta t \approx \sqrt{2 \times 0.01 \frac{(V_p - 0.7)}{V_p - 0.7}} = 0.141 \text{ rad}$$

$$\text{Fraction of cycle} = \frac{0.141}{2\pi} \times 100 = 2.25\%$$

(c)(i)

$$\begin{aligned}i_{D,\text{avg}} &= I_L \left( 1 + \pi \sqrt{\frac{2(V_p - V_{D0})}{V_r}} \right) \\ &= \frac{V_{D,\text{avg}}}{R} \left( 1 + \pi \sqrt{\frac{2(V_p - V_{D0})}{0.1(V_p - V_{D0})}} \right) \\ &= \frac{15.5}{10^3} \left( 1 + \pi \sqrt{\frac{2}{0.1}} \right) \\ &= 233 \text{ mA}\end{aligned}$$

$$(ii) i_{D,\text{avg}} = \frac{16.19}{10^3} (1 + \pi \sqrt{200}) \\ = 735 \text{ mA}$$

$$\text{NB next user } I_L \equiv V_p/R = \frac{V_p - V_{D0}}{R}$$

$$\text{but here are used } i_{D,\text{avg}} = \frac{V_p - V_{D0} - \frac{1}{2}V_r}{R}$$

which is more accurate.

$$\begin{aligned}(d) (i) i_{D,\text{peak}} &= I_L \left( 1 + 2\pi \sqrt{\frac{2(V_p - V_{D0})}{V_r}} \right) \\ &= \frac{15.42}{10^3} \left( 1 + 2\pi \sqrt{\frac{2}{0.1}} \right) \\ &= 449 \text{ mA}\end{aligned}$$

$$(ii) i_{D,\text{peak}} = \frac{16.19}{10^3} \left( 1 + 2\pi \sqrt{\frac{2}{0.01}} \right) \\ = 1455 \text{ mA}$$

3.62

$$i) v_r = 0.1(V_p - V_{DO} \times 2) = \frac{V_p 2 V_{DO}}{2 f C R}$$

discharge occurs only over  $\frac{1}{2} T = \frac{1}{2f}$

$$C = \frac{(V_p - 2V_{DO})}{(V_p - 2V_{DO})} \frac{1}{2(0.1)fR} = 83.3 \mu F$$

$$ii) C = \frac{1}{2(0.01)fR} = 833 \mu F$$

$$(b) i) \text{Fraction of cycle} = \frac{2\omega \Delta t}{2\pi} \times 100$$

$$= \sqrt{\frac{2(0.1)}{\pi}} \times 100 = 14.2\%$$

ii) Fraction of cycle

$$= \sqrt{\frac{2(0.01)}{\pi}} \times 100 = 4.5\%$$

$$(c) i) i_{D,\text{avg}} = \frac{14.79}{1} \left(1 + \pi \sqrt{\frac{1}{0.2}}\right) = 119 \text{ mA}$$

$$ii) i_{D,\text{avg}} = \frac{15.49}{1} \left(1 + \pi \sqrt{\frac{1}{0.02}}\right) = 356 \text{ mA}$$

$$(d) i) \hat{i}_D = \frac{14.79}{1} \left(1 + 2\pi \sqrt{\frac{1}{0.2}}\right) = 223 \text{ mA}$$

$$ii) \hat{i}_D = \frac{15.49}{1} \left(1 + 2\pi \sqrt{\frac{1}{0.02}}\right) = 704 \text{ mA}$$

During the diode's off interval, the capacitor discharges through the resistor  $R$  according to:

$$v_o = 9.3 e^{-t/RC} \approx 9.3(1 - t/CR)$$

$$\therefore v_T = 9.3 - 9.3(t/CR)$$

$$= \frac{9.3T}{CR}$$

$$= \frac{9.3}{fCR} \text{ NB this is Eq(4.38)}$$


$$= 0.93 \text{ V}$$

$$v_{o,\text{avg}} = V_D - V_{DO} - 1/2 v_T$$

$$= 9.3 - \frac{1}{2} 0.93$$

$$= 8.84 \text{ V}$$

(b)

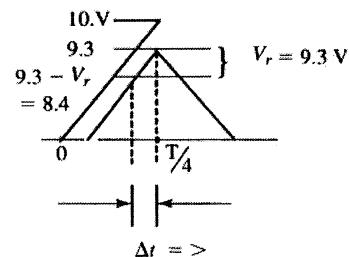

$$\Delta t \Rightarrow \frac{10}{T/4} = \frac{0.93}{\Delta t}$$

$$\Delta t = 0.02325T \\ = 0.02325 \text{ ms}$$



(c)  $\therefore$  Charge gained during conduction = Charge lost during discharge

$$i_{c,\text{avg}} \Delta t = Cv_T$$

$$i_{c,\text{avg}} = \frac{Cv_T}{\Delta t} = \frac{100 \times 10^{-6} \times 0.93}{0.02325 \times 10^{-3}} \\ = 4.0 \text{ A}$$

$$i_{D,\text{avg}} \approx i_{c,\text{avg}} + i_{c,\text{avg}} \frac{v_{D,\text{avg}}}{R} \\ \approx 4.0 + \frac{8.84}{100} = 4.09 \text{ A}$$

3.63

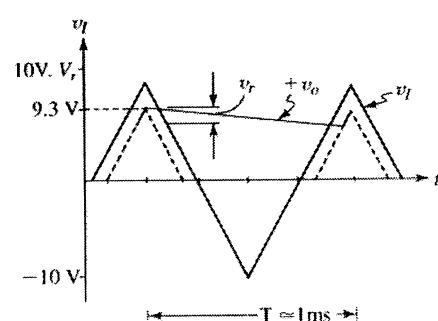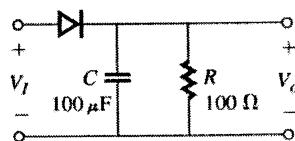

$$(d) i_{c,\max} = C \frac{\partial v_t}{\partial t} \Big|_{\text{at onset of conduction}}$$

$$= C \frac{\partial v_t}{\partial t}$$

$$= 100 \times 10^{-6} \times 40 \times 10^3$$

$$= 4A$$

$$i_{D,\max} = i_{C,\max} + i_{L,\max}$$

$$= 4 + v_{o,\max} / 100$$

$$= 4 + 9.3 / 100$$

$$= 4.09 A.$$

Note that in this case  $i_{D,\max} = i_{c,\max}$  during the linear input ( $i_c$  is constant and  $i_L$  is approximately constant).

**3.64** Let capacitor  $C$  be connected across each of the load resistors  $R$ . The two supplies,  $v_{0+}$  and  $v_{0-}$  are identical. Each is a full-wave rectifier similar to that based on the center-tapped-transformer circuit for each supply, the dc output is 15 V and the ripple is 1 V peak-to-peak. Thus  $v_b = 15 \pm 1/2$  V. It follows that the peak value of  $v_s$  must be  $15.5 + 0.7 = 16.2$  V.

$$\therefore \text{Voltage across secondary} = 2(16.2)$$

$$= 32.4 \text{ V}$$

$$\text{RMS across secondary} = \frac{32.4}{\sqrt{2}} = 22.9 \text{ V rms}$$

$$\text{Turns Ratio} = \frac{120}{22.9} = 5.24:1$$

Use Eq.(4.35) to find

$$i_{D,\max} = I_L(1 + 2\pi\sqrt{V_p/2V_T})$$

$$= 0.2(1 + 2\pi\sqrt{15.5/2})$$

$$= 3.70 A$$

$$v_T = \frac{V_p}{2fCR} = 1$$

Eq (4.28)

$$\text{DISCHARGE OCCURS OVER } T/2 = \frac{1}{2f}$$


$$\Rightarrow C = \frac{15.5}{2 \times 60 \times 75}$$

$$\text{where } 200 \text{ mA} = \frac{15}{R}$$

$$R = \frac{15}{0.2} = 75 \Omega$$

$$C = 1722 \mu\text{F}$$

Consider  $D_3$  when looking at PIV

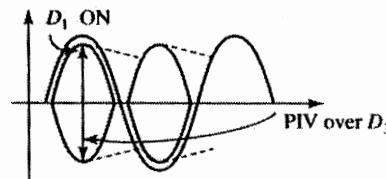

$$\text{PIV} = \hat{v}_0 + \hat{v}_s$$

$$= 15.5 + 16.2 = 31.7 \text{ V.}$$

Allowing for 50 % safety margin

$$\text{PIV} = 1.5 \times 31.7 = 47.6 \text{ V}$$

use Eq(4.34) to find

$$i_{D,\text{avg}} = I_L(1 + \pi\sqrt{V_p/2V_T})$$

$$= 0.2(1 + \pi\sqrt{15.5/2})$$

$$= 1.95 \text{ A}$$

**3.65**

$$U_o = U_x \left( 1 + \frac{R}{R} \right)$$

$= 2U_x$  when the diode is conducting.

$$(a) \quad U_x = +1V \quad U_o = 2V \quad U_A = 1.7V \quad U_- = U_x = 1V$$

b)

$$U_x = 2V \quad U_o = 4V \quad U_A = 4.7V \quad U_- = 2V$$

c)


$$U_x = -1V \quad U_A = -12V \sim \text{diode is cut off}$$

$$U_o = 0V$$

$$U_- = 0V$$


d)
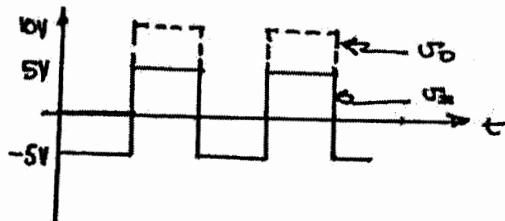
$$U_I = -2 \text{ V} \quad U_A = -12 \text{ V} \quad U_O = 0 \text{ V} \quad U_E = 0 \text{ V}$$





$$U_O, \text{avg} = \underline{\underline{5 \text{ V}}}$$


3.66

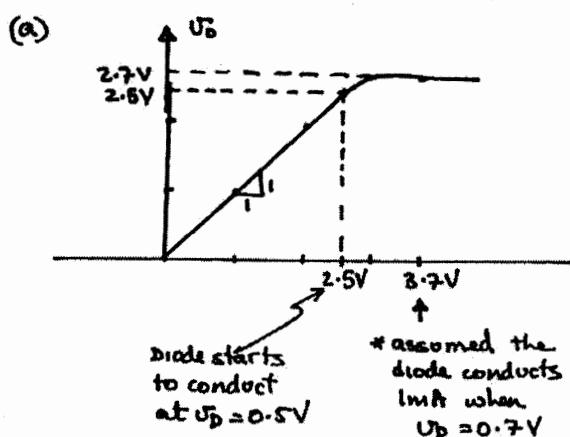


(b)

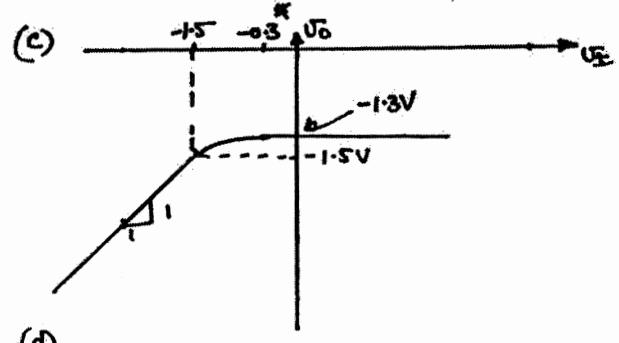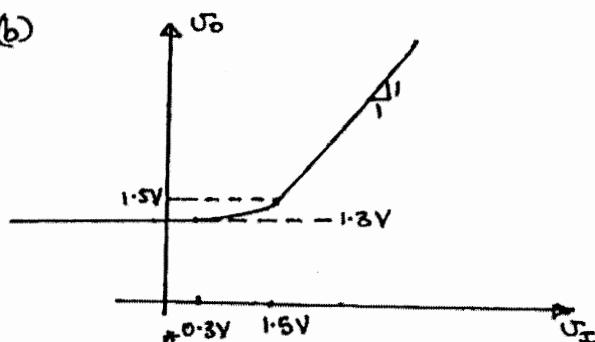

(d)

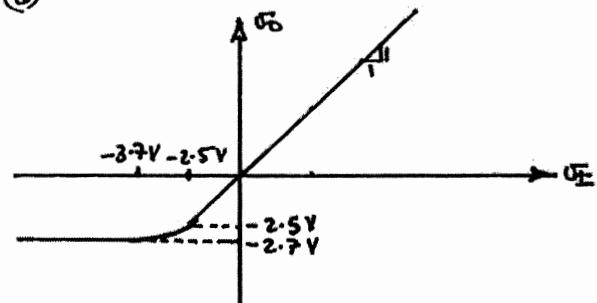

3.67

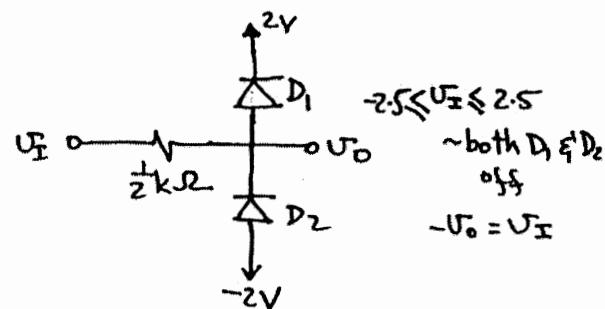


For  $U_I \geq 2.5 \text{ V}$  ~D<sub>1</sub> on  
 $U_{D1} = 0.7 \text{ V}$  at  $i_{D1} \geq 1 \text{ mA}$   
 $U_O = 2.7 \text{ V}$  at  $U_I = 2.7 + \frac{1}{2} \times 1 = \underline{\underline{3.2 \text{ V}}}$

3.69

For each diode



For the zener-diode

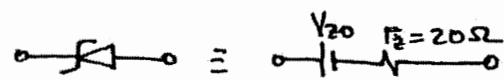

$$8.2 = V_{z0} + 10 \times 10^{-3} \times 20$$




$$V_{z0} = 8.0V$$

The limiter thresholds are


$$\pm (2 \times 0.65 + 8.0) = \pm 9.3V$$

For  $U_I > 9.3$  (as well as for  $U_I < -9.3$ )
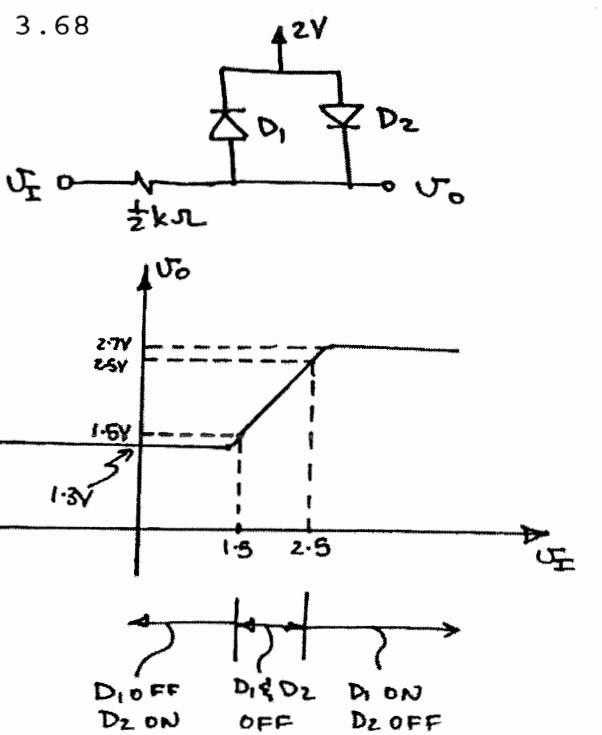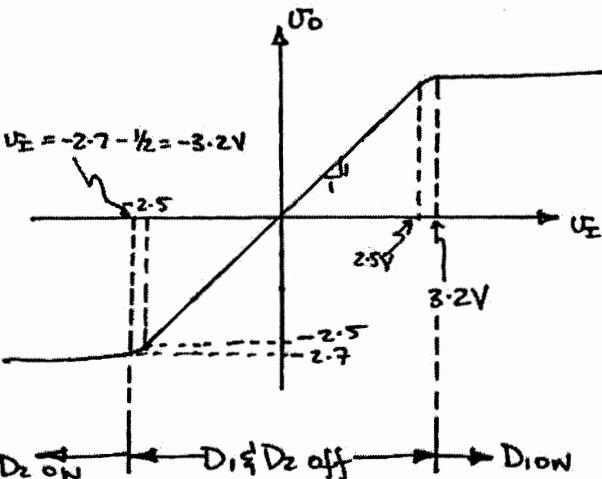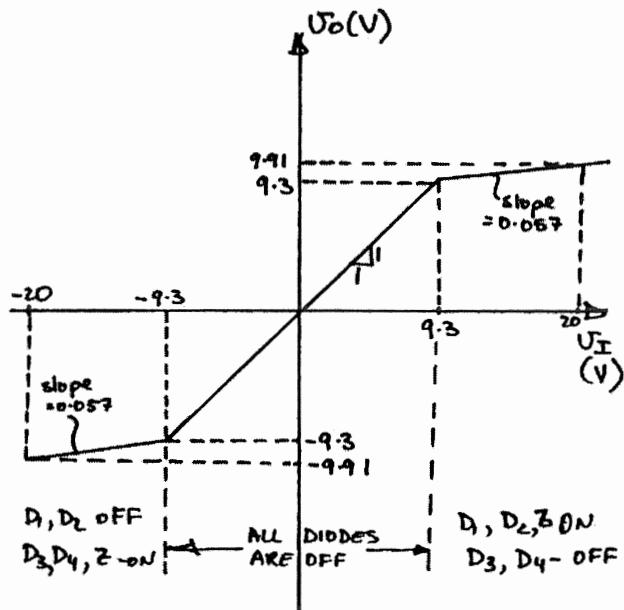
$$\frac{dU_O}{dU_I} = \frac{r_{D1} + r_2 + r_{D2}}{1k\Omega + r_{D1} + r_2 + r_{D2}} = \frac{3(20)}{1k\Omega + 3(20)} = 0.057 \frac{V}{V}$$



3.70

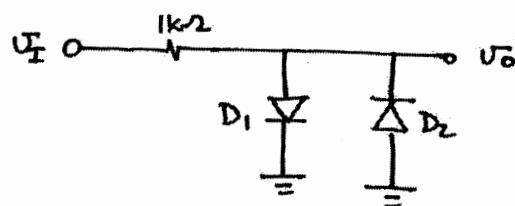

For D<sub>1</sub>

$$\text{Given } \frac{i_D}{I_{mA}} = e^{\frac{U_O - 0.7}{nV_T}}$$

$$(U_O - 0.7) = nV_T \ln\left(\frac{i_D}{I_{mA}}\right)$$

$$= 0.1 \log\left(\frac{i_D}{10^{-3}}\right) \leftarrow \text{can find } U_O \text{ from } i_D$$

$$\therefore i_D = 10^{-3} \times 10^{\frac{U_O - 0.7}{0.1}}$$


$$= 10^{-3} \times 10^{10(U_O - 0.7)}$$

$$\therefore U_I = U_O + i_D \times 10^3$$

$$= U_O + 10^{10(U_O - 0.7)}$$


$$\text{for } D_2: \quad U_I = U_O - 10^{-10(U_O - 0.7)}$$

$U_O(V)$	$U_I(V)$	
0.5	0.510	D <sub>1</sub> ON
0.6	0.7	
0.7	1.7	
0.8	10.7	
0	0	
-0.5	-0.51	D <sub>2</sub> ON
-0.6	-0.7	
-0.7	-1.7	
-0.8	-10.7	

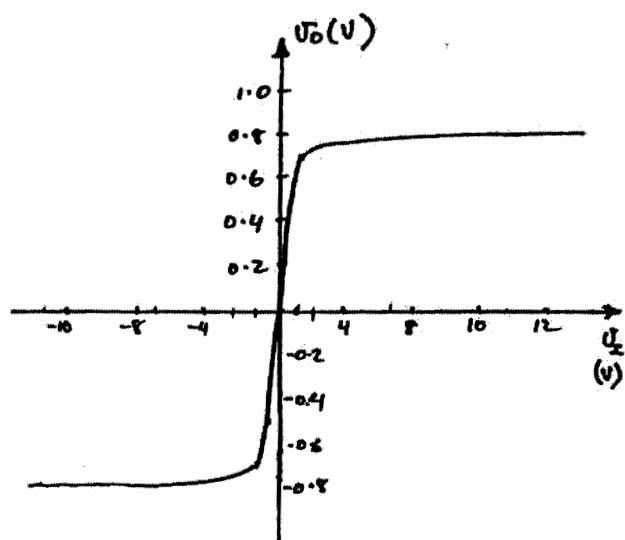

The limiter is fairly hard with a gain  
 $K \approx 1$   
 $L+ \approx 0.8V, \quad L- \approx -0.8V$

3.71

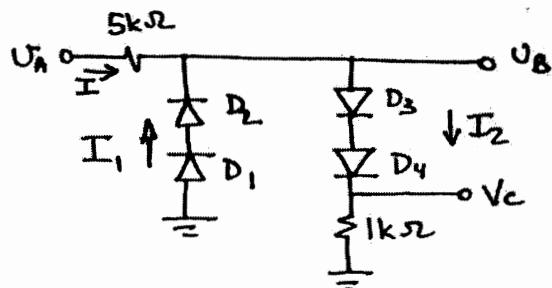

$$U_B = 0.7 + 0.1 \log \left( \frac{I_2}{0.1} \right)$$

(a) For  $U_A > 0$   $D_1, D_2$  off  $\Rightarrow I_1 = 0$

$$I = I_2 = \frac{U_C}{1k\Omega} \quad U_A = U_B + 5I$$

(b) For  $U_A < 0$   $D_3, D_4$  off  $\Rightarrow U_C = 0$

$$I = -I_1 \quad U_B = -(U_{D1} + U_{D2})$$



$$U_A = -(U_B + 5I_1)$$

(a) List of points for  $U_A > 0$


$U_C$ (V)	$I_2$ (mA)	$U_{D3}, U_{D4}$ (V)	$U_B = U_C + U_{D3} + U_{D4}$ (V)	$U_A$ (V)
0.0001	0.0001	0.4	0.8	0.8
0.001	0.001	0.5	1.00	1.01
0.01	0.1	0.6	1.21	1.24
0.1	0.1	0.7	1.50	1.90
0.2	0.2	0.73	1.66	2.66
0.3	0.3	0.75	1.80	3.30
0.4	0.4	0.76	1.92	3.92
0.5	0.5	0.77	2.04	4.54
0.6	0.6	0.78	2.16	5.16

(b) List of Points for  $V_A < 0$

$I_1$ (mA)	$U_{D1}, U_{D2}$ (V)	$U_B$ (V)	$U_A$ (V)
0.0001	0.4	-0.80	-0.80
0.001	0.5	-1.00	-1.01
0.01	0.6	-1.20	-1.25
0.10	0.7	-1.40	-1.90
0.20	0.73	-1.46	-2.46
0.30	0.75	-1.50	-3.00
0.40	0.76	-1.52	-3.52
0.50	0.77	-1.54	-4.04
0.60	0.78	-1.56	-4.56
0.70	0.795	-1.57	-5.07

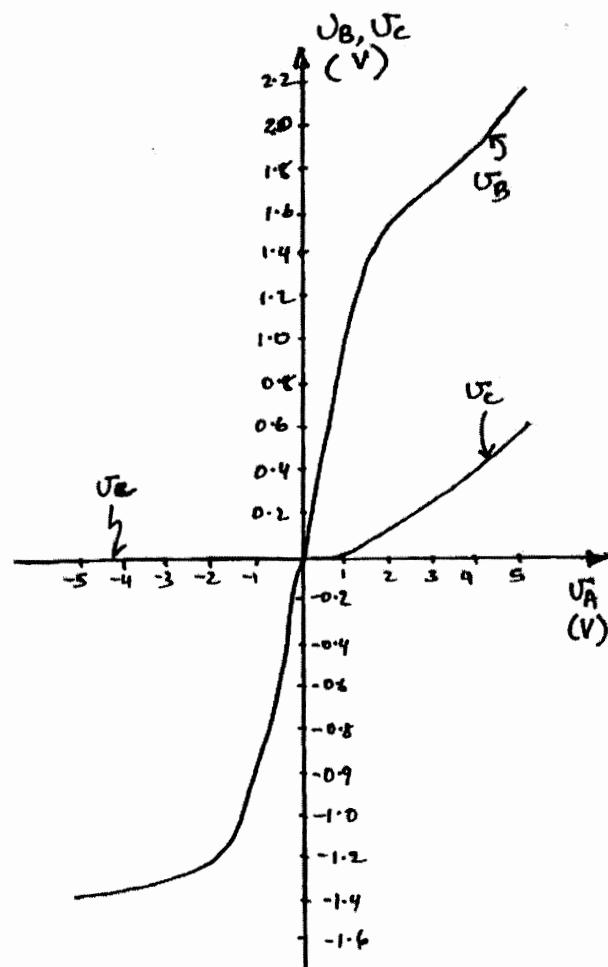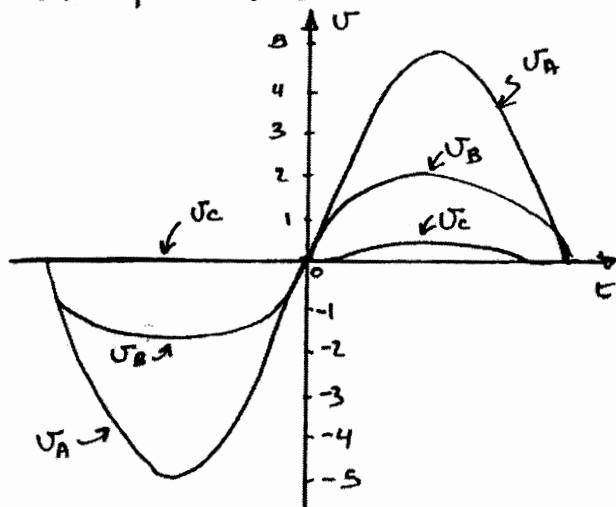

3.72

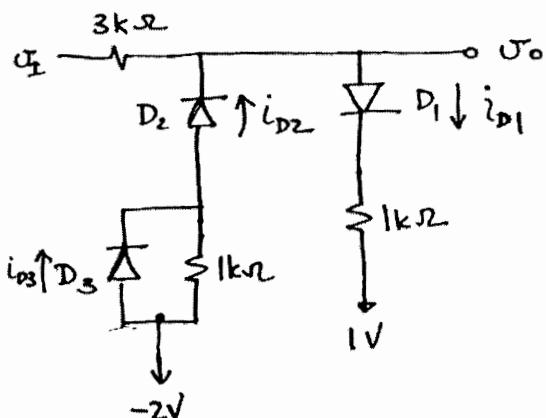

At currents  $i_{D1} > 1mA$ ,  $U_{D1} \approx 0.7V$   
Let  $U_{D1} = 0.7V$     $U_x > 5.7V$


$$U_o = 1.71 + i_{D1} \times 1k\Omega$$

$$= 1.71 + \left( \frac{U_I - 1.71}{4} \right) \times 1$$

$$= \frac{U_I}{4} + 1.2825 \quad \text{NB slope} = \frac{1}{4}$$

For  $U_I > 5V$  slope  $\frac{U_o}{U_I} \approx \frac{1}{4}$

$U_I (V)$	$U_o (V)$
5.8	2.7325
6.0	2.7825
7.0	3.0325
8.0	3.2825
9.0	3.5325
10.0	3.7825

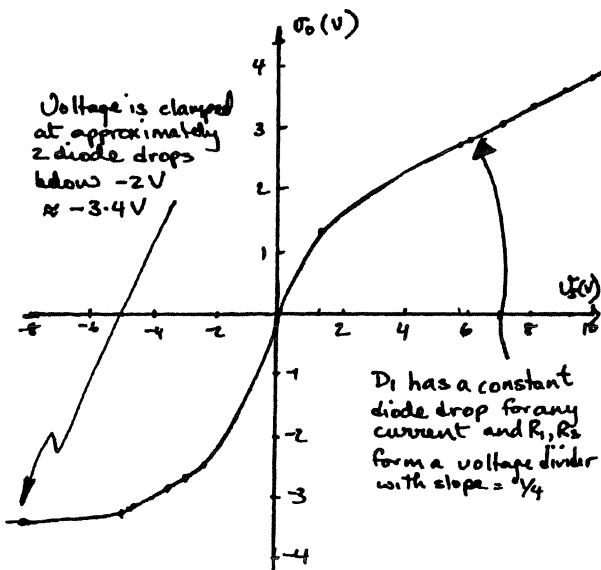

where points for  $-8 \leq U_I \leq 6 V$  are calculated as shown below:

$$i_D = 1mA \text{ at } U_D = 0.7V \quad n=1$$

$$i_D = I_s e^{\frac{U_D - 0.7}{0.025}} = 10^{-3}$$

$$I_s = 6.914 \times 10^{-16} A.$$

$$\text{For Diodes use } i_D = 6.914 \times 10^{-16} e^{\frac{U_D - 0.7}{0.025}}$$

$D_1$  conducting  $i_{D2} = 0$

$i_{D1}$ (A)	$U_{D1}$ (V)	$U_o$ (V)	$U_I = (4k)i_{D1} + U_{D1} + 1$ (V)
$10^{-10}$	0.297	1.297	1.297 ← even at small $i_{D1}$
$10^{-6}$	0.527	1.527	1.5313 $\leftarrow$ $U_o > U_I$ , $U_o \neq U_I$ since $i_{D1} \neq 0$
$10^{-5}$	0.584	1.595	1.625
$10^{-4}$	0.64	1.742	2.042
$10^{-3}$	0.70	2.7	5.7
$0.2 \times 10^{-2}$	0.74	6.74	12.74
$10^{-2}$	0.758	11.75	41.75

For the  $D_2, D_3$  arm conducting use the following equations:  
Note  $U_I < -2.5V$

Starting with a value for  $U_A$  we have

$$U_{D3} = U_A + 2$$

$$i_{D3} = I_s e^{\frac{U_{D3} - 0.7}{0.025}} \quad \textcircled{2}$$

$$i_{D2} = i_{D3} + \frac{U_A + 2}{1} \quad \textcircled{3}$$

$$U_{D2} = 0.025 \ln \left( \frac{i_{D2}}{6.914 \times 10^{-16}} \right) \quad \textcircled{4}$$

$$U_o = U_A - U_{D2} \quad \textcircled{5}$$

$$U_I = U_o - i_{D2} \times 3k\Omega \quad \textcircled{6}$$


$\textcircled{1} U_A$ (V)	$\textcircled{2} i_{D3}$ (A)	$\textcircled{3} i_{D2}$ (A)	$\textcircled{4} U_{D2}$ (V)	$\textcircled{5} U_o$ (V)	$\textcircled{6} U_I$ (V)
-2.001	$7 \times 10^{-16}$	$10^{-6}$	0.527	-2.528	-2.531 $\textcircled{1}$
-2.01	$10^{-15}$	$10^{-5}$	0.585	-2.395	-2.625
-2.10	$3.8 \times 10^{-14}$	$10^{-4}$	0.642	-2.724	-3.024
-2.20	$2 \times 10^{-12}$	$0.2 \times 10^{-3}$	0.659	-2.859	-3.459
-2.5	$33 \mu A$	$0.5 \times 10^{-3}$	0.682	-3.128	-4.628 $\textcircled{2}$
-2.6	$18 \mu A$	$0.6 \times 10^{-3}$	0.687	-3.287	-5.087
-2.7	$1mA$	$1.7 \times 10^{-3}$	0.713	-3.413	-8.516 $\textcircled{3}$
-2.71	$1.5mA$	$2.2mA$	0.720	-3.43	-10

$\textcircled{1}$  for small  $i_{D2}$ ,  $D_3$  is off and  $D_2$  is on  
 $\therefore i_{D2}$  flows through  $1k\Omega$  resistor

CONT.

- ③ 0.5 V drop across  $D_3$  causes  $D_3$  to start to conduct
- ④  $U_A = -2.7V$   
The 0.7 voltage across  $D_3$  clamps the voltage across  $R_3$  so that  $D_3$  controls the current  $i_{D2}$

3.73

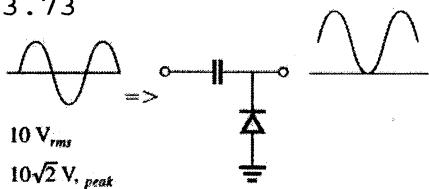

$$\begin{aligned}\text{Average (dc) value of output} &= 10\sqrt{2}/2 \\ &= 14.14 \text{ V}\end{aligned}$$

#### 4.1

Case	Mode
1	active
2	saturation
3	active
4	saturation
5	inverted active mode
6	active
7	cut-off
8	cut-off

#### 4.2

$$i_c = I_s e^{v_{BE}/V_T}$$

For Device #1

$$0.2 \times 10^{-3} = I_{s1} e^{0.72/0.025}$$

$$I_{s1} = \underline{\underline{6.214 \times 10^{-12} A}}$$

For Device #2

$$12 \times 10^{-3} = I_{s2} e^{0.72/0.025}$$

$$I_{s2} = \underline{\underline{3.728 \times 10^{-12} A}}$$

Since  $I_s \approx A$ , the relative junction areas is :

$$\frac{A_2}{A_1} = \frac{I_{s2}}{I_{s1}} = \frac{i_{c2}}{i_{c1}} = \frac{12}{0.2} = \underline{\underline{60}}$$

#### 4.3

$$\begin{aligned} A_{E2} &= 10^{-6} A_{E1} \Rightarrow \\ I_n &= 10^{-6} I_n \\ i_{C1} &= I_{s1} e^{v_{BE1}/V_T} \\ i_{C2} &= I_{s2} e^{v_{BE2}/V_T} \quad \& i_{C1} = i_{C2} \Rightarrow \\ I_{s1} e^{v_{BE1}/V_T} &= i_{C1} \approx i_{C2} = I_{s2} e^{v_{BE2}/V_T} \\ I_{s1} e^{v_{BE1}/V_T} &= 10^{-6} I_{s2} e^{v_{BE2}/V_T} \\ 10^6 &= e^{(v_{BE2} - v_{BE1})/V_T} \\ v_{BE2} - v_{BE1} &= V_T \ln(10^6) = 0.025 \ln(10^6) \\ &= 0.345 \end{aligned}$$

#### 4.4

$$\begin{aligned} i_{C1} &= I_{s1} e^{v_{BE1}/V_T} = 10^{-12} e^{0.72/0.025} = 1.45 \text{ A} \\ i_{C2} &= I_{s2} e^{v_{BE2}/V_T} = 10^{-12} e^{-0.72/0.025} = 1.45 \mu\text{A} \\ \text{If we set } i_C &\text{ to } 1.45 \mu\text{A} \text{ in case 1 and} \\ v_{BE} &\text{ are allowed to vary} \\ 1.45 \times 10^{-6} &= 10^{-12} e^{v_{BE}/0.025} \\ v_{BE} &= 0.354 \end{aligned}$$

#### 4.5

$$\begin{aligned} i_{C,\text{old}} &= I_{s,\text{old}} e^{v_{BE,\text{old}}/V_T} \\ v_{BE,\text{old}} &= V_T \ln \left( \frac{i_{C,\text{old}}}{I_{s,\text{old}}} \right) \\ i_{C,\text{old}} &= 1 \text{ mA}; I_{s,\text{old}} = 5 \times 10^{-15} \text{ A} \\ V_T &= 0.025 \text{ Volts} \\ v_{BE,\text{old}} &= 0.025 \ln \left( \frac{1 \times 10^{-3}}{5 \times 10^{-15}} \right) = 0.651 \\ i_{C,\text{new}} &= 1 \text{ mA}; I_{s,\text{new}} = 5 \times 10^{-18} \text{ A} \\ V_T &= 0.025 \\ v_{BE,\text{new}} &= 0.025 \ln \left( \frac{1 \times 10^{-3}}{5 \times 10^{-18}} \right) = 0.823 \end{aligned}$$

#### 4.6

$$\begin{aligned} i_C &= I_s e^{v_{BE}/V_T} \\ 10 \times 10^{-3} &= I_s e^{0.72/0.025} \Rightarrow I_s = 6.273 \times 10^{-16} \text{ A} \\ \text{For } v_{BE} = 0.7 \text{ V} \Rightarrow i_C &= 6.273 \times 10^{-16} e^{0.7/0.025} \\ &= 0.907 \text{ mA} \end{aligned}$$

$$I_E = I_C + I_S \text{ ranges from} \\ = \underline{\underline{3.05mA}} \text{ to } \underline{\underline{15.05mA}}$$

For

$$i_C = 10 \mu A \Rightarrow 10 \times 10^{-6} = 6.273 \times 10^{-16}$$

$$e^{\frac{v_{BE}}{0.025}}$$

$$\therefore v_{BE} = 0.587 V$$

Alternate way - without calculating  $I_S$

For  $v_{BE} = 0.7 V$

$$\frac{i_C}{10 \text{ mA}} = e^{\frac{0.7 - 0.76}{0.025}}$$

$$\therefore i_C = 0.907 \text{ mA}$$

For  $i_C = 10 \mu A$

$$\frac{10 \times 10^{-6}}{10 \times 10^{-3}} = e^{\frac{v_{BE} - 0.76}{0.025}}$$

$$v_{BE} = 0.587 V$$

4.7


$$i_C = \beta i_B$$

$$400 = \beta \times 7.5$$

$$\beta = \frac{400}{7.5} = \underline{\underline{53.3}}$$

$$\alpha = \frac{\beta}{\beta+1} = \frac{53.3}{54.3} = \underline{\underline{0.982}}$$

4.8

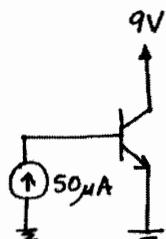

$$\beta = 60 \text{ to } 300$$

$$I_C = \beta I_B \text{ ranges from} \\ = 60 \times 50 \mu A \text{ to } \\ 300 \times 50 \mu A \\ = \underline{\underline{3mA \text{ to } 15mA}}$$

4.9

$$i_C = I_S e^{\frac{v_{BE}}{V_T}}$$

$$i_B = \frac{i_C}{\beta}$$

$$i_E = \frac{\beta+1}{\beta} i_C$$

$$i_C = (5 \times 10^{-15}) e^{0.650/0.025} = 977 \mu A$$

$i_C$  is constant and independent of  $\beta$

$$i_B \text{ ranges from } \frac{i_C}{\beta} = \frac{977 \times 10^{-6}}{50} = 19.6 \mu A$$

$$\text{to } \frac{i_C}{\beta} = \frac{977 \times 10^{-6}}{200} = 4.89 \mu A$$

$i_E$  ranges from

$$\frac{\beta+1}{\beta} i_C = \frac{51}{50} 977 \times 10^{-6} = 998 \mu A$$

$$\text{to } \frac{\beta+1}{\beta} i_C = \frac{201}{200} 977 \times 10^{-6} = 983 \mu A$$

4.10

$$i_E = 1 \text{ mA}$$

Case I:  $i_B = 50 \mu A$

$$i_C = i_E - i_B = 1 \times 10^{-3} - 50 \times 10^{-6} = 950 \mu A$$

$$\beta = \frac{i_C}{i_B} = \frac{950 \times 10^{-6}}{50 \times 10^{-6}} = 19$$

$$\alpha = \frac{\beta}{\beta+1} = \frac{19}{20} = 0.95$$

Case II:  $i_B = 10 \mu A$

$$i_C = i_E - i_B = 1 \times 10^{-3} - 10 \times 10^{-6} \text{ A} \\ = 990 \mu A$$

$$\beta = \frac{i_C}{i_B} = \frac{990 \times 10^{-6}}{10 \times 10^{-6}} = 99$$

$$\alpha = \frac{\beta}{\beta+1} = \frac{99}{100} = 0.99$$

**Case III:**  $i_B = 25 \mu\text{A}$

$$i_C = i_E - i_B = 1 \times 10^{-3} \text{ A} - 25 \times 10^{-6} \text{ A} = 975 \mu\text{A}$$

$$\beta = \frac{i_C}{i_B} = \frac{975 \times 10^{-6}}{25 \times 10^{-6}} = 39$$


$$\alpha = \frac{\beta}{\beta + 1} = \frac{39}{40} = 0.975$$

4.11

$$I_B = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T}} \Rightarrow V_{BE} = V_T \ln \left[ \frac{\beta I_B}{I_S} \right]$$

$$V_{BE} = 25 \ln \left[ \frac{10^{-3}}{5 \times 10^{-15}} \right] = 650 \text{ mV}$$

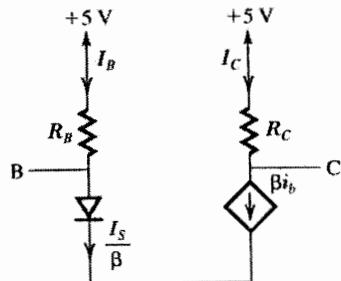
$$I_B = I_C/125 = 1000/125 = 8 \mu\text{A}$$



$$R_B = \frac{V_{BB} - V_{BE}}{I_B} = \frac{5 - 0.65}{0.008} = 544 \text{ k}\Omega$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{5 - 1}{1} = 4 \text{ k}\Omega$$

4.12

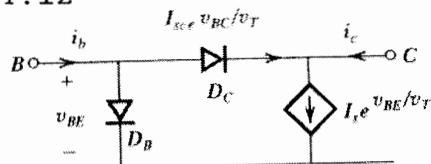

$$I_C = 0 \text{ when } I_{SC} e^{\frac{V_{BE}}{V_T}} = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\frac{I_{SC}}{I_S} = e^{\frac{(V_{BE} - V_{BC})V_T}{V_T}} = 100$$

$$V_{CE} = V_{BE} - V_{BC} = V_T \ln \frac{I_{SC}}{I_S}$$

$$= 25 \ln 100 = 115 \text{ mV}$$

$$\text{For } V_{ce} = 0.4 \text{ V } V_{BC} = 0.7 - 0.4 = 0.3 \text{ V}$$

$$i_{BC} = I_{SC} e^{\frac{0.3V_T}{V_T}} = 10^{-13} e^{12} = 0.0168 \mu\text{A}$$

$$\text{For } V_{CE} = 0.3 \text{ V } V_{BC} = 0.7 - 0.3 = 0.4 \text{ V}$$

$$i_{BC} = I_{SC} e^{\frac{0.4V_T}{V_T}} = 10^{-13} e^{16} = 0.089 \mu\text{A}$$

$$\text{For } V_{CE} = 0.1 \text{ V } V_{BC} = 0.7 - 0.1 = 0.6 \text{ V}$$

$$i_{BC} = I_{SC} e^{\frac{0.6V_T}{V_T}} = 10^{-13} e^{24} = 2.65 \text{ mA}$$

$$\text{For } V_{BE} = 0.7 \text{ V}$$

$$i_{BE} = \frac{I_S}{\beta} e^{\frac{0.7V_T}{V_T}} = \frac{10^{-15}}{100} e^{28} \Rightarrow 14.5 \mu\text{A}$$

$$i_{CE} = I_{SC} e^{\frac{0.7V_T}{V_T}} = 10^{-15} e^{28} = 1.45 \text{ mA}$$

$$\text{For } V_{CE} = 0.4 \text{ V } V_{BC} = 0.3 \text{ V}$$

$$i_B = i_{BE} + i_{BC} = 14.5 + 0.02 = 14.52 \mu\text{A}$$

$$i_C = i_{CE} - i_{BC} = 1.45 - 0 = 1.45 \text{ mA}$$

$$i_C/i_B = 1.45 \text{ mA} / 14.52 \mu\text{A} = 100$$

$$\text{For } V_{CE} = 0.3 \text{ V } V_{BC} = 0.4 \text{ V}$$

$$i_b = 14.5 + 0.089 = 145.89 \mu\text{A}$$

$$i_C = 1.45 - \frac{0.089}{1000} = 1.45 \text{ mA}$$

$$i_C/i_b \approx 1.45 \text{ mA} / 146 \mu\text{A} = 9 \cdot 9$$

$$\text{For } V_{CE} = 0.1 \text{ V } V_{BC} = 0.6 \text{ V}$$

$$i_b = 14.5 + 2.65 = 4.1 \text{ mA}$$

$$i_C = 1.45 - 2.65 = -1.2 \text{ mA}$$

$V_{CE}$  too low for model

4.13

$$\text{given: } i_C = I_S e^{\frac{V_{BE}}{V_T}} - I_{SC} e^{\frac{V_{BC}}{V_T}}$$

$$\text{and } i_C = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T}} + I_{SC} e^{\frac{V_{BC}}{V_T}}$$

$$\text{and } \beta_{\text{forced}} = \left. \frac{i_C}{i_B} \right|_{\text{Sat}} \leq \beta$$

$$\beta_{\text{forced}} = \beta \cdot \frac{I_S e^{\frac{(V_{CE\text{sat}} + V_{BC})V_T}{V_T}} - I_{SC} e^{\frac{V_{BC}}{V_T}}}{I_S e^{\frac{(V_{CE\text{sat}} + V_{BC})V_T}{V_T}} + I_{SC} e^{\frac{V_{BC}}{V_T}}}$$

$$= \beta \cdot \frac{I_S e^{\frac{V_{BC}}{V_T}} [e^{\frac{V_{CE\text{sat}}V_T}{V_T}} - I_{SC}/I_S]}{I_S e^{\frac{V_{BC}}{V_T}} [e^{\frac{V_{CE\text{sat}}V_T}{V_T}} + \beta I_{SC}/I_S]}$$

$$\therefore e^{\frac{V_{CE\text{sat}}}{V_T}} = \frac{-\beta I_{SC} - \beta \frac{I_{SC}}{I_S} \times \beta_{\text{forced}}}{\beta - \beta_{\text{forced}}}$$

$$= \frac{I_{SC} [\beta + \beta \beta_{\text{forced}}]}{I_S [\beta - \beta \beta_{\text{forced}}]}$$

$$= \frac{I_{SC} [1 + \beta_{\text{forced}}]}{I_S [1 - \beta_{\text{forced}}/\beta]} \quad \text{QED}$$

For  $\beta_{\text{forced}} = 50$

$$V_{CE\text{sat}} = 25 \ln \left[ 100 \cdot \frac{1 + 50}{1 - 50/100} \right]$$

$$= 25 \ln[10200] = 230.8 \text{ mV}$$

For  $\beta_{\text{forced}} = 10$

$$V_{CE\text{sat}} = 25 \ln\left[100 \cdot \frac{1+10}{1-10/100}\right]$$

$$= 25 \ln[122.2] = 177.7 \text{ mV}$$

For  $\beta_{\text{forced}} = 5$

$$V_{CE\text{sat}} = 25 \ln\left[100 \cdot \frac{1+5}{1-5/100}\right]$$


$$= 25 \ln[631.6] = 161.2 \text{ mV}$$

For  $\beta_{\text{forced}} = 1$

$$V_{CE\text{sat}} = 25 \ln\left[100 \cdot \frac{1+1}{1-1/100}\right]$$

$$= 25 \ln[202] = 132.7 \text{ mV}$$

4.15

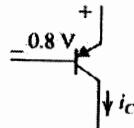

$$\therefore i_C = I_S e^{\frac{V_{EB}}{V_T}}$$


$$\text{Use } \frac{i_C}{1\text{A}} = e^{\frac{v_{EB}-0.8}{0.025}}$$

to calculate  $v_{EB}$  for a particular  $i_C$

$$\text{For } i_C = 10 \text{ mA} \quad v_{EB} = 0.685 \text{ V}$$

$$\text{For } i_C = 5 \text{ A} \quad v_{EB} = 0.840 \text{ V}$$

4.14

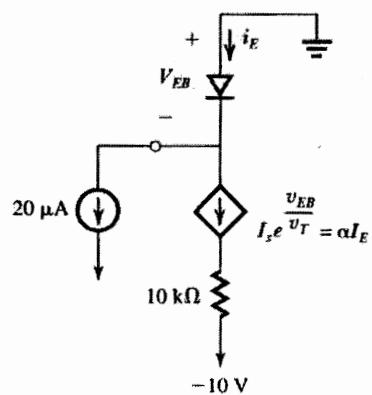

$$\beta = 40$$

$$\alpha_F = \frac{40}{41}$$

$$I_S = 10^{-13} \text{ A}$$

$$i_E = \frac{I_S}{\alpha} e^{\frac{V_{EB}}{V_T}} = I_S e^{\frac{V_{EB}}{V_T}} + 0.02 \times 10^{-3} \text{ A}$$

$$I_S e^{\frac{V_{EB}}{V_T}} \left( \frac{1}{\alpha} - 1 \right) = 0.02 \times 10^{-3} \text{ A}$$

$$10^{-13} e^{\frac{V_{EB}}{0.025}} \left( \frac{41}{40} - 1 \right) = 0.02 \times 10^{-3} \text{ A}$$

$$V_{EB} = 0.570 \text{ V} \Rightarrow V_B = -0.570 \text{ V}$$

$$i_E = \frac{I_S}{\alpha} e^{\frac{V_{EB}}{V_T}} = \frac{10^{-13}}{40} e^{\frac{0.57}{0.025}}$$

$$= 0.82 \text{ mA}$$

$$i_C = \alpha i_E \Rightarrow$$

$$V_C = -10 + \alpha i_E \times 10$$

$$= -10 + \frac{40}{41} \times 0.82 \times 10$$

$$= -2 \text{ V}$$

4.16

$$\beta = 10$$

$$i_C = \alpha i_E = \frac{10}{11} \times 10 = 9.09 \text{ mA}$$

$$i_B = i_E - i_C = 0.91 \text{ nA}$$

$$i_C = I_S e^{\frac{V_{EB}}{V_T}}$$


$$9.09 \times 10^{-3} = 10^{-16} e^{\frac{V_{EB}}{0.025}}$$

$$V_C = V_{EB} = 0.803 \text{ V}$$

For  $\beta = 1000$

$$i_C = \frac{\beta}{\beta + 1} i_E = \frac{1000}{1001} \times 10 = 9.99 \text{ mA}$$

4.17

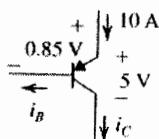

for  $\beta = 15$

$$i_E = (\beta + 1)i_B$$

$$10 = (\beta + 1)i_B$$

$$i_B = \frac{10}{16} = 0.625 \text{ A}$$

Calculating  $I_{S1}$

$$i_C = \frac{\beta}{\beta + 1} i_E = I_{S1} e^{-v_{EB}/v_T}$$

$$\frac{15}{16} \times 10 = I_{S1} e^{0.65/0.025}$$

$$I_{S1} = 1.608 \times 10^{-14} \text{ A}$$

Compare this to

$$I_{S2} = i_C e^{-v_{EB}/v_T}$$

$$= 10^{-3} e^{-0.7/0.025}$$



$$= 6.914 \times 10^{-16}$$

$\therefore I_S \propto \text{area}$

$$\frac{\text{Area1}}{\text{Area2}} = \frac{I_{S1}}{I_{S2}} = \frac{1.608 \times 10^{-14}}{6.914 \times 10^{-16}}$$

= 23.3 times larger


4.18

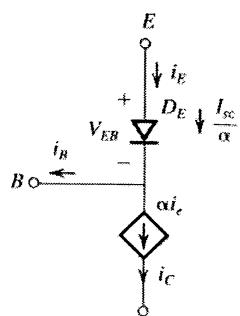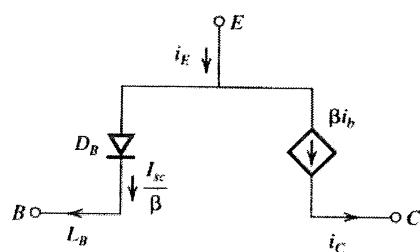


4.19

$$(a) I_1 = \frac{10.7 - 0.7}{10} = 1 \text{ mA}$$


(b)

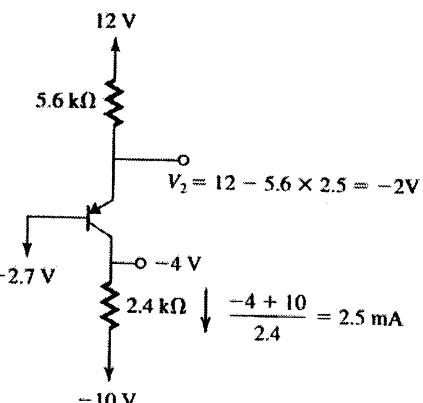

(c)

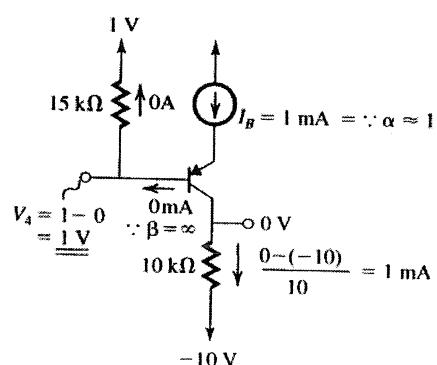

(d)

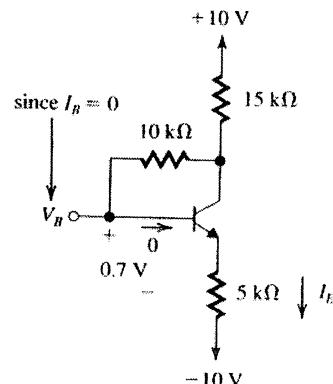

$$I_E = I_C$$

$$\frac{V_B - 0.7 + 10}{5} = \frac{10 - V_E}{15}$$


$$15V_6 + 139.5 = 50 - 5V_6$$

$$V_6 = -4.475 \text{ V}$$

$$I_S = \frac{V_6 - 0.7 + 10}{5}$$

$$= \frac{-4.475 - 0.7 + 10}{5} = 0.965 \text{ mA}$$

4.20

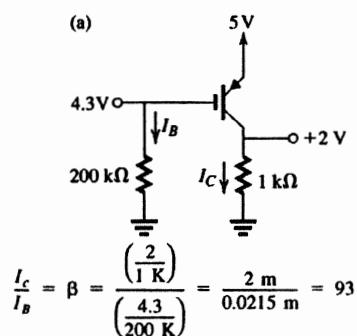

$$I_E = \left( \frac{10 - 7}{1 \text{ K}} \right) = 3 \text{ mA}$$

$$I_E = I_C + I_B = 3 \text{ mA}$$


$$V_c = 3 \text{ m}(1 \text{ K}) = 3 \text{ V}$$

$$I_B = \frac{6.3 - 3}{100 \text{ K}} = 33 \mu\text{A}$$

$$\frac{I_E}{I_B} = \beta + 1 = \frac{3 \text{ m}}{33 \mu} = 90.9$$

$$\beta = 89.9$$

4.21

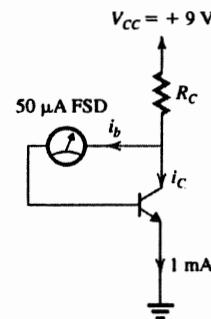

$$\text{For F.S.D } i_b = 50 \mu\text{A}$$

$$i_c = 1000 - 50 = 950 \mu\text{A}$$

$$\text{Since } R_m = 0 \Omega \quad V_{CE} = V_{BE} = 0.7 \text{ V}$$

∴ active mode

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{9 - 0.7}{1 \text{ mA}} = 8.3 \text{ k}\Omega$$

$$I_C = \beta I_B \therefore \beta = \frac{950}{50} = 19$$

$$\text{For FSD/5: } i_b = 10 \mu\text{A}, i_c = 990 \mu\text{A}$$

$$\Rightarrow \beta = 99$$

$$\text{For FSD/10: } i_b = 5 \mu\text{A}, i_c = 995 \mu\text{A}$$



$$\Rightarrow \beta = 199$$

4.22

$$(I_C + I_B) = \frac{2.3}{230} = 10 \text{ mA}$$

$$I_B = \left( \frac{4.3 - 2.3}{20 \text{ K}} \right) = 0.1 \text{ mA}$$
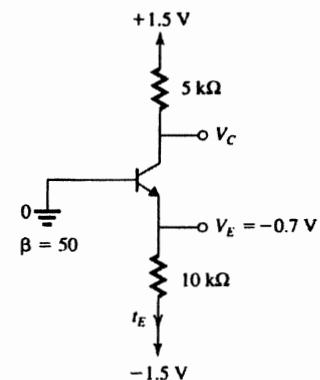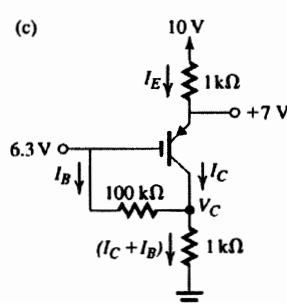
$$\frac{I_C}{I_B} = \left( \frac{10 \text{ m} - 0.1 \text{ m}}{0.1 \text{ m}} \right) = \beta = 99$$




$$I_E = \frac{V_E - V_{EE}}{R_E} = \frac{0.8}{10 \text{ k}\Omega} = 80 \mu\text{A}$$

$$I_C = \frac{\beta}{\beta + 1} I_E = \frac{50}{51} \times 80 = 78 \mu\text{A}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{80}{51} = 1.6 \mu\text{A}$$

$$V_c = V_{cc} - I_c R_C = 1.5 \text{ V} - 0.078 \times 5 \text{ V} = 1.11 \text{ V}$$

4.23

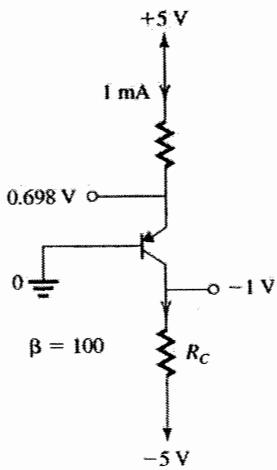

$$V_{BE(1\text{mA})} - V_{BE(0.1\text{mA})}$$

$$= 25 \ln \left[ \frac{1}{0.1} \right]$$

$$\therefore V_{BE(1\text{mA})} = 640 \text{ mV} + 57.9 \text{ mV} = 698 \text{ mV}$$

$$I_C = \frac{100}{101} I_E = 0.99 \text{ mA}$$


$$R_C = \frac{-1 - (-5)}{0.99} = 4.04 \text{ k}\Omega$$

$$R_E = \frac{5 - 0.698}{1} = 4.3 \text{ k}\Omega$$

$V_C$  can be raised until  $= +0.4 \text{ V}$

$$R_C = \frac{5 + 0.4}{0.99} = 5.45 \text{ k}\Omega$$

4.24

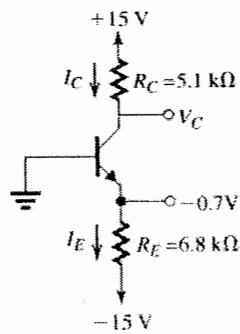


$$\alpha \approx 1$$

$$I_E \approx I_c = \frac{(-0.7 - (-15))}{6.8 \text{ k}\Omega} = 2.1 \text{ mA}$$

$$V_c = 15 - 5.1 \text{ k}\Omega (2.1 \text{ mA})$$

$$V_c = 4.3 \text{ V}$$

4.25

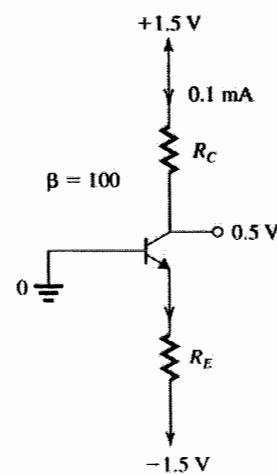

$$\Delta V_{BE} = V_T \ln \left[ \frac{I_{C2}}{I_{C1}} \right]$$

$$= 25 \ln [0.1] = -57.6 \text{ mA}$$

$$V_{BE(0.1)} = 742 \text{ mV}$$

$$R_C = \frac{1.5 - 0.5}{0.1} = 10 \text{ k}\Omega$$

$$V_E = -0.742 \text{ V}$$

$$R_E = \frac{-0.742 + 1.5}{\frac{\beta + 1}{\beta} I_C}$$

$$= \frac{100}{101} \cdot \frac{0.758}{0.1} = 7.5 \text{ k}\Omega$$

4.26

$$(a) V_B = 0 \text{ V}$$

$$V_E = V_B - 0.7 = -0.7 \text{ V}$$

$$I_E = \frac{-0.7 + 3}{2.2} = 1.05 \text{ mA}$$

$$I_c = \frac{30}{31} I_E = \underline{1.02 \text{ mA}}$$

$$V_c = 3 - 1.02 \times 2.2 = \underline{0.756 \text{ V}}$$

$$I_B = \frac{I_c}{\beta} = \frac{1.02}{30} = \underline{0.034 \text{ mA}}$$

$$(b) V_B = \underline{0 \text{ V}}$$

$$V_E = V_B + 0.7 = \underline{0.7 \text{ V}}$$

$$I_E = \frac{3 - V_E}{1} = \frac{3 - 0.7}{1} = \underline{2.3 \text{ mA}}$$

$$I_c = \alpha I_E = \frac{30}{31} \times 2.3 = \underline{2.23 \text{ mA}}$$

$$V_c = -3 + 1 \times I_c = -3 + 2.23$$

$$= \underline{-0.77 \text{ V}}$$

$$I_E = \frac{I_c}{\beta} = \frac{2.23}{30} = \underline{0.0743 \text{ mA}}$$

$$(c) V_B = \underline{3 \text{ V}}$$

$$V_E = V_B + 0.7 = \underline{3.7 \text{ V}}$$

$$I_E = \frac{9 - V_E}{1.1} = \frac{9 - 3.7}{1.1} = \underline{4.82 \text{ mA}}$$

$$I_c = \alpha I_E = \frac{30}{31} \times 4.82 = \underline{4.66 \text{ mA}}$$

$$V_c = I_c \times 0.56 = \underline{2.62 \text{ V}}$$

$$I_B = \frac{I_c}{\beta} = \frac{4.66}{30} = \underline{0.155 \text{ mA}}$$

$$(d) V_B = \underline{3 \text{ V}}$$

$$V_E = 3 - 0.7 = \underline{2.3 \text{ V}}$$

$$I_E = V_E / 0.47 = 2.3 / 0.47 = \underline{4.89 \text{ mA}}$$

$$I_c = \alpha I_E = \frac{30}{31} \times 4.89 = \underline{4.73 \text{ mA}}$$

$$V_c = 9 - 1 \times I_c = 9 - 4.73 = \underline{4.27 \text{ V}}$$

$$I_B = \frac{I_c}{\beta} = \frac{4.73}{30} = \underline{0.158 \text{ mA}}$$


4.27

$I_{CBO}$  doubles for every  $10^\circ\text{C}$  rise in temperature.

Thus if  $I_{CBO} = 20 \text{ nA}$  at  $25^\circ\text{C}$

$$\begin{aligned} \text{At } 85^\circ\text{C} \quad I_{CBO} &= 2^{\frac{85-25}{10}} \times 20 \\ &= \underline{1280 \text{ nA}} \end{aligned}$$

4.28

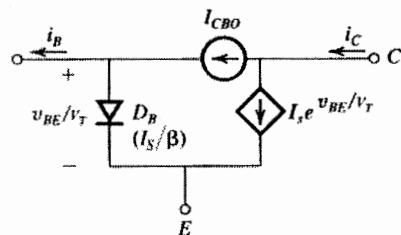

$$i_B = \frac{I_s}{\beta} e^{\frac{v_{BE}}{V_T}} - I_{CBO} \quad (1)$$

$$i_C = I_s e^{\frac{v_{BE}}{V_T}} + I_{CBO} \quad (2)$$

$$i_E = I_s \left(1 + \frac{1}{\beta}\right) e^{\frac{v_{BE}}{V_T}} \quad (3)$$

for  $\beta$  opencircuited,  $i_B = 0$  and (1) gives

$$\frac{I_s}{\beta} e^{\frac{v_{BE}}{V_T}} = I_{CBO} \Rightarrow e^{\frac{v_{BE}}{V_T}} = \frac{\beta I_{CBO}}{I_s}$$

substitute into (2) & (3)  $\Rightarrow$

$$i_C = (\beta + 1) I_{CBO}$$

$$i_E = (\beta + 1) I_{CBO}$$

4.29

GIVEN  $i_E = 0.5\text{mA}$   
 $V_{EB} = 0.692\text{V}$

AT  $20^\circ\text{C}$ 

- (a) The junction temperature rises to  $50^\circ\text{C}$

$$V_{EB} = 0.692 - 2 \times 10^{-3}(50 - 20)$$

$$= 0.632\text{V}$$

- (b) The Base-Emitter Voltage is fixed

$$V_{EB} = 0.7\text{V} \text{ at ALL TEMPERATURES}$$

$$\text{At } 20^\circ\text{C} \sim i_E = 0.5\text{mA} \text{ at } V_{EB} = 0.692\text{V}$$

Thus for  $V_{EB} = 0.7\text{V}$  we have

$$\frac{i_E}{0.5 \times 10^{-3}} = e^{\frac{0.7 - 0.692}{0.025}}$$

$$i_E = 0.689\text{mA}$$

Now if  $T = 50^\circ\text{C} \notin V_{EB} = 0.7\text{V}$

from (a) we see that at  $50^\circ\text{C}$ ,

$$I_E = 0.5\text{mA}, V_{EB} = 0.632\text{V}$$

Therefore for  $V_{EB} = 0.7\text{V}$

$$\frac{i_E}{0.5 \times 10^{-3}} = e^{\frac{0.7 - 0.632}{0.025}}$$

$$i_E = 7.69\text{mA}$$

4.30

$$\frac{i_C}{10\text{mA}} = e^{\frac{V_{BE} - 0.7}{0.025}}$$

$$i_C = \underline{3.35\text{ }\mu\text{A}}$$

Notice the current drops significantly at  $V_{BE} = 0.5\text{V}$

4.31

$V_{BE}$  changes by  $-2\text{ mV}/^\circ\text{C}$  for a particular

current. Given that at  $25^\circ\text{C}$   $V_{BE} = 0.7\text{V}$  and  $i_C = 10\text{mA}$

Thus

$$@ -25^\circ\text{C} \quad V_{BE} = 0.7 - 2 \times 10^{-3}(-50) \\ = 0.8\text{V} \quad \text{and} \quad i_C = 10\text{mA}$$

$$@ 125^\circ\text{C} \quad V_{BE} = 0.7 - 2 \times 10^{-3}(100) \\ = 0.5\text{V} \quad \text{and} \quad i_C = 10\text{mA}$$

4.32

$$r_o = \frac{1}{3 \times 10^{-5}} = \underline{33.3\text{k}\Omega}$$

$$V_A = r_o I_c = 33.3 \times 10^3 \times 3 \times 10^{-3} \\ = \underline{100\text{V}}$$

$$r_o = \frac{V_A}{I_c} = \frac{100}{30} = \underline{3.3\text{k}\Omega}$$

4.33

$$r_o = V_A / I_C = 200 / I_C$$

$$@ I_C = 1 \text{ mA} \quad r_o = \underline{\underline{200 \text{ k}\Omega}}$$

$$@ I_C = 100 \mu\text{A} \quad r_o = \frac{200}{0.1} = \underline{\underline{2.0 \text{ M}\Omega}}$$

4.34

$$V_{BE} = 0.72 \text{ V} - i_C = 1.8 \text{ mA} \quad V_{CE} = 2 \text{ V}$$

$$i_C = 2.4 \text{ mA} \quad V_{CE} = 14 \text{ V}$$

$$r_o = \frac{\Delta V_{CE}}{\Delta i_C} = \frac{14 - 2}{2.4 - 1.8} = 20 \text{ k}\Omega$$

Near saturation  $V_{ce} = 0.3 \text{ V}$

$$\therefore \frac{\Delta V_{CE}}{\Delta i_C} = \frac{0.3 - 2}{i_C - 1.8} = 20 \text{ k}\Omega$$

$$i_C = 1.72 \text{ mA}$$

Calculating  $V_{CE}$  for  $i_C = 2.0 \text{ mA}$

$$\frac{\Delta V_{CE}}{\Delta i_C} = r_o$$

$$\frac{V_{CE} - 2}{2 - 1.8} = 20 \Rightarrow V_{CE} = 6 \text{ V}$$

Take the ratio of currents to find the early voltage (with Eq 5.36)

$$\frac{2.4}{1.8} = \underbrace{\frac{e^{\frac{V_{BE} - V_{RE}}{V_T}}}{1 + 2/V_A}}_{= 1} \left( \frac{1 + 14/V_A}{1 + 2/V_A} \right)$$

$$2.4 + \frac{4.8}{V_A} = 1.8 + \frac{25.2}{V_A}$$

$$V_A = 34 \text{ V}$$

$$r_o = \frac{V_A}{I_C}$$

where  $I_C$  is the current near saturation  $\leftrightarrow$  active boundary. As calculated above  $I_C = 1.72 \text{ mA}$

$$r_o = \frac{34 \text{ V}}{1.72 \text{ mA}} = 19.8 \text{ k}\Omega \text{ compared to the}$$

above calculation of  $20 \text{ k}\Omega$ .

4.35

Large signal or DC  $\beta$ :

$$h_{FE} = \frac{i_C}{i_B} = \frac{1.2 \text{ mA}}{8 \mu\text{A}} = \underline{\underline{150}}$$


$$\text{Small signal } h_{fe} = \frac{0.1 \text{ mA}}{0.8 \mu\text{A}} = \underline{\underline{125}}$$

$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{1.2 \text{ mA}} = 83.3 \text{ k}\Omega$$

$$\begin{aligned} \Delta i_C &= h_{fe} \Delta i_B + \frac{\Delta V_{CE}}{r_o} \\ &= 125 \times 2 \mu\text{A} + \frac{2}{83.3 \text{ k}\Omega} = 0.274 \text{ mA} \end{aligned}$$

$$\therefore i_C = 1.2 \text{ mA} + \Delta i_C = \underline{\underline{1.474 \text{ mA}}}$$

4.36

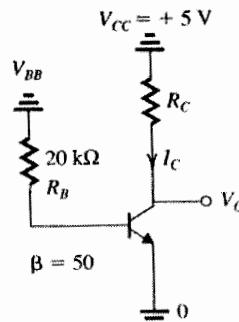

(a) active region

$$I_C = \frac{V_{CC} - V_C}{R_C}$$

$$= \frac{5 - 1}{1 \text{ k}} = 4 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{4}{50} = 0.08 \text{ mA}$$

$$\begin{aligned} V_{BB} &= 0.7 + \frac{20 \times 4}{50} \\ &= +2.3 \text{ V} \end{aligned}$$

(b) edge of saturation  $v_C = 0.3 \text{ V}$ 

$$I_C = \frac{5 - 0.3}{1} = 4.7 \text{ mA}$$

$$I_B = I_C/\beta = 4.7/50 = 0.094 \text{ mA}$$

$$V_{BB} = 0.094 \times 20 + 0.7 = 2.58 \text{ V}$$

(c)  $V_B = 0 \text{ V}$  - cutoff

$$V_E = 0 \text{ V}$$

$$I_E = 0 \text{ A}$$

$$V_C = 5 \text{ V}$$

(c) deep saturation  $v_C = 0.2 \text{ V}$   $\beta_F = 10$ 

$$I_C = (5 - 0.2)/1 = 4.8 \text{ mA}$$

$$I_B = I_C/\beta_{\text{forced}} = 4.8/10 = 0.48 \text{ mA}$$

$$V_{BB} = 0.48 \times 20 + 0.7 = +10.3 \text{ V}$$

4.39

4.37

Assume active:

$$V_E = 3 \text{ V}, V_B = 2.3 \text{ (Assume } V_{BE} = 0.7 \text{ V)}$$

$$I_B = \frac{2.3}{10 \text{ K}} = 2.3 \text{ mA}$$

$$I_c = 2.3 \text{ m}(50) = 115 \text{ mA}$$

$$V_c = 115 \text{ m}(1 \text{ K}) = 115 \text{ V}, \quad V_c < V_B \text{ (not true!)}$$

saturation. Use  $V_{ECSAT} = 0.2 \text{ V}$ 

$$+3 - V_{ECSAT} - V_c = 0$$

$$V_c = 3 - 0.2 = 2.8 \text{ V}$$

$$V_B = 2.3$$

$$V_E = 3 \text{ V}$$

 $V_c > V_B < V_E \therefore \text{SATURATED}$ 

$$\beta_{\text{forced}} = \frac{I_{CSAT}}{I_B} = \frac{\left(\frac{2.8}{1 \text{ K}}\right)}{\left(\frac{3}{10 \text{ K}}\right)} = \frac{2.8 \text{ m}}{0.3 \text{ m}} = 9.33$$

Transistor will operate at edge of saturation when  $V_c = V_B = 2.8 \text{ V}$ 

$$\therefore R_B = \frac{V_B}{I_B} = \frac{2.8}{3 \text{ m}} = 9.3 \text{ k}\Omega$$

4.38

(a)  $V_B = 2 \text{ V}$

$$V_E = 2 - 0.7 = 1.3 \text{ V}$$

$$I_E = \frac{V_E}{1} = 1.3 \text{ mA}$$

(b)  $V_B = 1 \text{ V}$

$$V_E = 1 - 0.7 = 0.3 \text{ V}$$


$$I_E \approx I_c = 0.3 \text{ mA}$$

$$I_c \approx 1.3 \text{ mA}$$

$$V_c = 5 - 0.3$$

$$V_c = 5 - 1.3 = 3.7 \text{ V}$$

$$= 4.7 \text{ V}$$

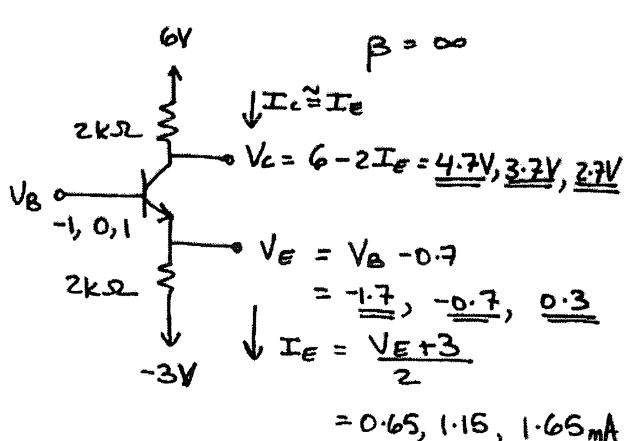

- Want  $V_B$  when  $I_E = \frac{1}{10} \times 1.15 \text{ mA}$   
 $= 0.115 \text{ mA}$

$$V_E = -3 + 0.115 \times 2 = -2.77 \text{ V}$$

$$V_B = V_E + 0.7 = -2.07 \text{ V}$$

- Want  $V_B$  at the edge of conduction  
At the edge of conduction assume  
 $V_{BE} = 0.5 \text{ V}$

$$\therefore V_B - 0.5 - 2I_E + 3 = 0 \leftarrow I_E = 0$$

$$V_B = -2.6 \text{ V} \quad \text{at edge of conduction}$$

$$V_E = V_B - 0.5 = -3V$$

$$I_c \approx 0A \quad \therefore V_c = 6V$$

At saturation assume  $V_{CE} = 0.2V$   
 $V_{CB} = -0.5V$

$$\therefore I_E = \frac{V_B - 0.7 + 3}{2} \approx I_c = \frac{6 - (V_B - 0.5)}{2}$$

$$\therefore V_B + 2 \cdot 3 = 6.5 - V_B$$

$$V_B = 2.1V$$

$$V_E = 2.1 - 0.7 = 1.4V \quad V_C = V_B - 0.5 = 1.6V$$

-Want  $V_B$  at  $\beta_{forced} = 2$ ,  $V_{CE} = 0.2V$   
 $V_{CB} = -0.5V$

$$\beta_{forced} = \frac{I_{Csat}}{I_B} = 2$$

$$I_E = I_B + I_{Csat} = \frac{I_{Csat}}{2} + I_{Csat}$$

$$= \frac{3}{2} I_{Csat}$$

$$V_E = V_B - 0.7 = -3 + 2I_E$$

$$= -3 + 3I_{Csat}$$


$$I_{Csat} = \frac{2 \cdot 3 + V_B}{3}$$

$$I_c = \frac{V_{CE} - (V_B - 0.5)}{2} = I_{Csat}$$

$$6.5 - V_B = \frac{2}{3}(2 \cdot 3) + \frac{2}{3}V_B$$

$$V_B = \frac{6.5 - \frac{2(2 \cdot 3)}{3}}{\frac{1}{2} \cdot 3} = 2.98V$$

4.40

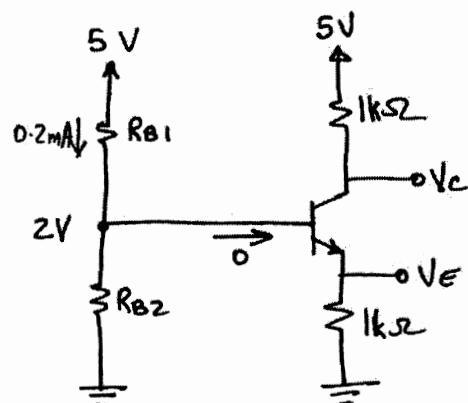

for  $\beta = \infty$


$$\frac{5}{R_{B1} + R_{B2}} = 0.2 \quad \text{and} \quad \frac{R_{B2}}{R_{B1} + R_{B2}} \cdot 5 = 2$$

$$R_{B1} + R_{B2} = 25k\Omega \quad \text{so } R_{B2} = 25k\Omega - R_{B1}$$

$$\Rightarrow \frac{R_{B2}}{25} \times 5 = 2$$

$$R_{B2} = 10k\Omega \quad R_{B1} = 15k\Omega$$

Now for  $\beta = 100$ , use Thevenin's

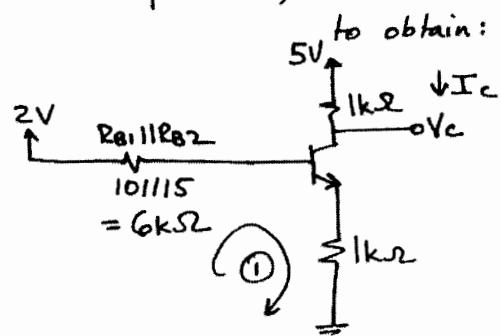


$$\text{Loop ①} \quad 2 - 6 \left( \frac{I_E}{101} \right) - 0.7 - I_E(1) = 0$$

$$I_E = 1.29mA$$

$$I_c = \frac{100}{101} I_e = \frac{100}{101} \times 1.29 = \underline{1.28 \text{ mA}}$$

$$V_c = 5 - 1.28(1) = \underline{3.72 \text{ V}}$$


4.41

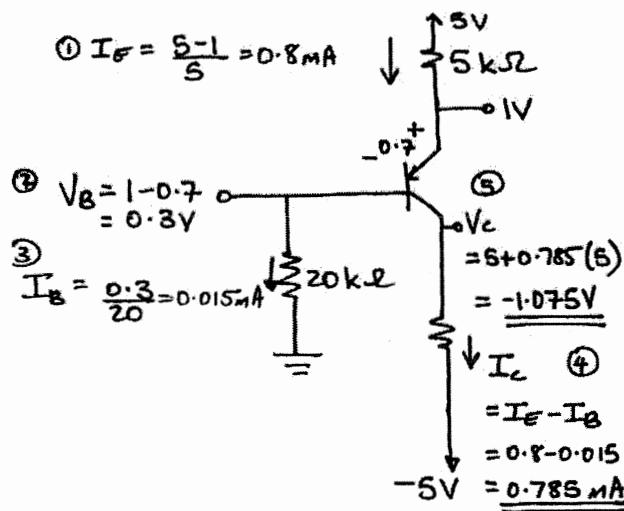

$$\textcircled{6} \quad \beta = \frac{I_C}{I_E} = \frac{0.785}{0.015} = \underline{52.3}$$

$$\textcircled{7} \quad \alpha = \frac{I_C}{I_E} = \frac{0.785}{0.8} = \underline{0.98}$$

4.42

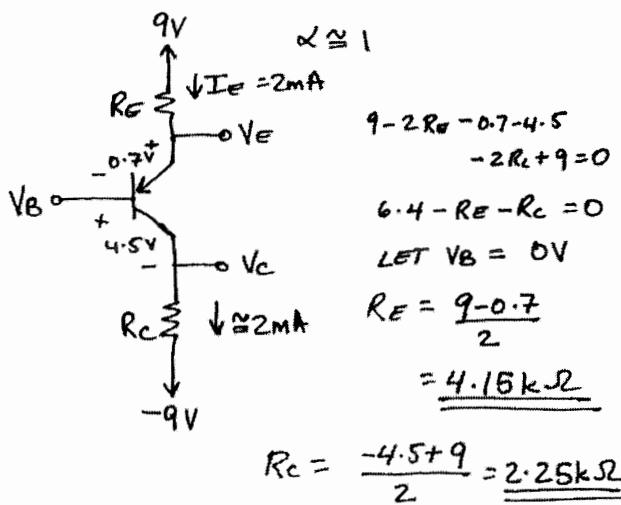

Using 5% resistor values


$$R_E = 3.9 \text{ k}\Omega \quad R_C = 22 \text{ k}\Omega$$

$$I_E = \frac{9 - 0.7}{3.9} = \underline{2.12 \text{ mA}}$$

$$V_c = -9 + 2.12 \times 2.2 = -4.3 \text{ V}$$

$$\therefore V_{BC} = \underline{4.3 \text{ V}}$$

4.43

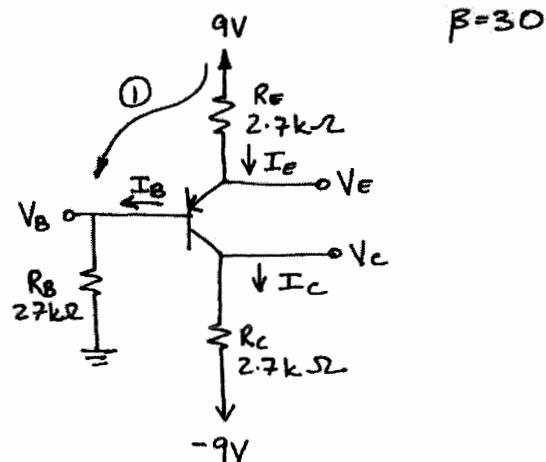

$$\text{Loop } \textcircled{1} \quad 9 - 2.7 I_E - 0.7 - \frac{I_E}{31} R_B = 0$$

$$I_E = 2.3243 \text{ mA}$$

$$V_B = R_B \times I_E / 31 = \underline{2.02 \text{ V}}$$

$$V_E = 9 - 2.7 I_E = \underline{2.72 \text{ V}}$$

$$V_C = -9 + \frac{30}{31} I_E (2.7) = \underline{-2.93 \text{ V}}$$

FOR  $R_B = 270 \text{ k}\Omega$

$$\text{Loop } \textcircled{1} \quad 9 - 2.7 I_E - 0.7 - \frac{R_B}{31} I_E = 0$$

$$I_E = 0.7274 \text{ mA}$$

$$V_B = R_B \times \frac{I_E}{\beta} = \underline{\underline{6.34V}}$$

$$V_E = 9 - 2.7 I_E = \underline{\underline{7.04V}}$$

$$V_C = \frac{30}{31} I_E (2.7) - 9 = \underline{\underline{-7.10V}}$$

To return the voltages to the ones first calculated we have


$$\text{Loop 1} \sim I_E = 2.3243 \text{ mA}$$

$$9 - 2.7 I_E - 0.7 - \frac{270}{\beta+1} I_E = 0$$

$$\beta = \underline{\underline{309}}$$

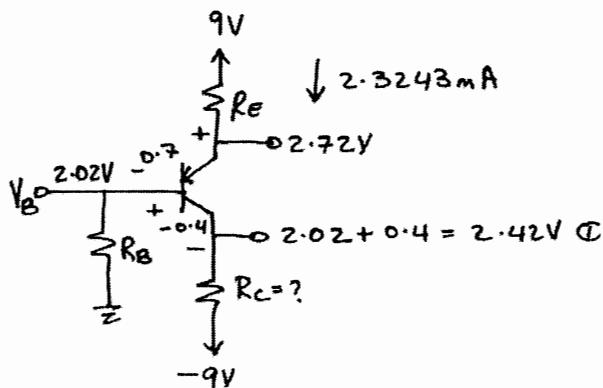4.44

Using the values from the first part of P5.76 and for the edge of saturation  $V_{BC} > -0.4V$



CIRCUIT AT THE EDGE OF SATURATION


$$I_C = \frac{30}{31} I_E = \frac{30}{31} \times 2.3243$$

$$R_C = \frac{2.42 + 9}{\frac{30}{31} \times 2.3243} = \underline{\underline{5.08 \text{ k}\Omega}}$$

4.45

$$\beta = 100$$

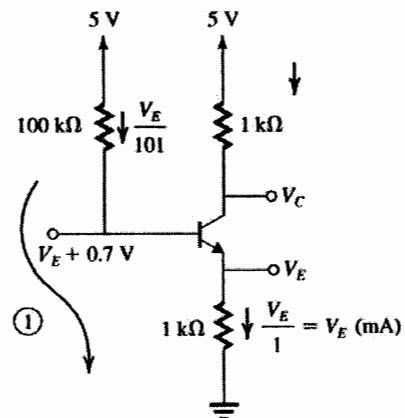(a)  $R_s = 100 \text{ k}\Omega$  -  $\therefore R_s$  is large assume active mode.



$$\frac{100}{101} I_E = \frac{100}{101} V_E (\text{mA})$$

Loop (1)

$$5 - \frac{V_E}{101} \times 100 - 0.7 - V_E \times 1 = 0$$


$$V_E = 2.16 \text{ V}$$

$$V_B = V_E + 0.7 = 2.86 \text{ V}$$

$$V_C = 5 - 1 \times \frac{100}{101} V_E = 2.86 \text{ V}$$

Thus the BJT is in active mode as assumed.

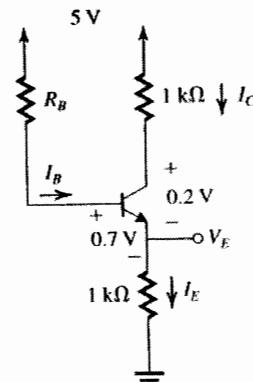(b)  $R_s = 10 \text{ k}\Omega$  - assume saturation



$$I_B = \frac{5 - (V_E + 0.7)}{R_B}$$

$$I_C = \frac{5 - (V_E + 0.2)}{1}$$

$$I_E = \frac{V_E}{1} = I_B + I_C$$

$$\therefore V_E = \frac{4.3 - V_E}{10} + 4.8 - V_E$$

4.46

$$10V_E + V_E + 10V_E = 4.3 + 48$$

$$V_E = 2.49 \text{ V}$$

$$V_C = 2.49 + 0.2 = 2.69 \text{ V}$$

$$V_B = V_E + 0.7 = 3.19 \text{ V}$$

$$\text{Check: } I_C = \frac{5 - 2.69}{1} = 2.31 \text{ mA}$$

$$I_B = \frac{5 - 3.19}{10} = 0.181 \text{ mA}$$

$$\frac{I_C}{I_B} = \frac{2.31}{0.181} = 12.76 < 100$$

Hence, we are in saturation as assumed!

(c)  $R_s = 1 \text{ k}\Omega$  - expect saturation, use circuit in (b)

$$I_B = \frac{5 - (V_E + 0.7)}{R_B} = \frac{4.3 - V_E}{1}$$

$$I_C = \frac{5 - (V_E + 0.2)}{1} = \frac{4.8 - V_E}{1}$$

$$I_E = I_B + I_C = V_E$$

$$4.3 - V_E + 4.8 - V_E = V_E$$

$$V_E = 3 \text{ V}$$

$$V_B = 3.7 \text{ V}$$



$$V_C = 3.2 \text{ V}$$

$$\text{Check } I_B = 4.3 - 3 = 1.3 \text{ mA}$$


$$I_C = 4.8 - 3 = 1.8 \text{ mA}$$

$$\frac{I_C}{I_B} = \frac{1.8}{1.3} = 1.4 < 100$$


$\therefore$  Saturation as assumed

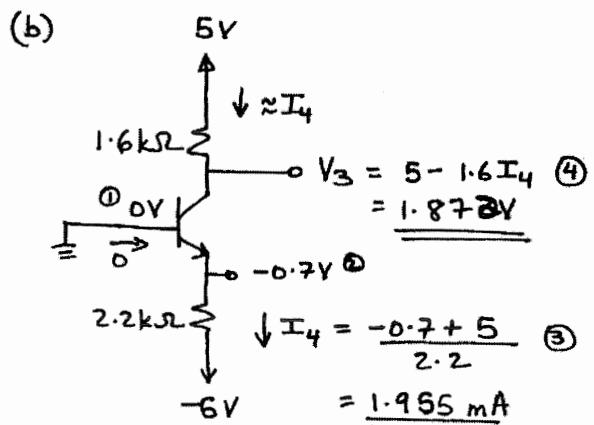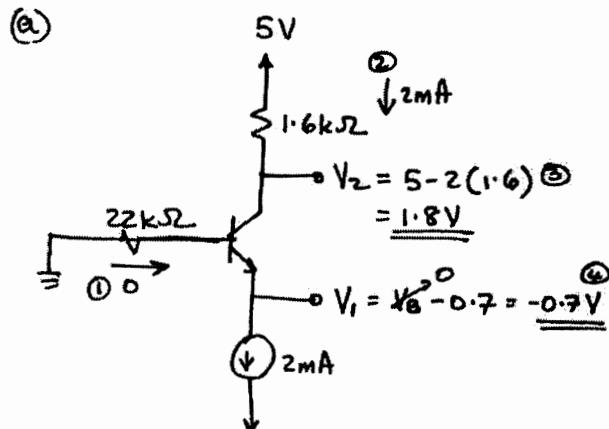


see below for part (c)

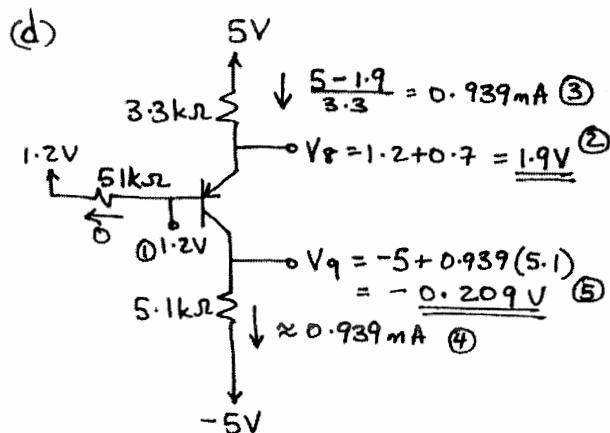

(c)

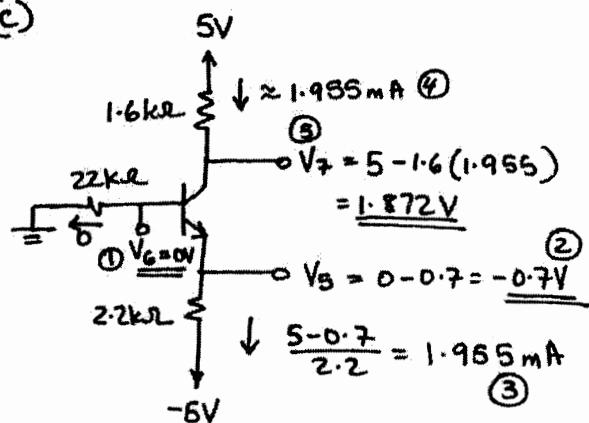

(e)

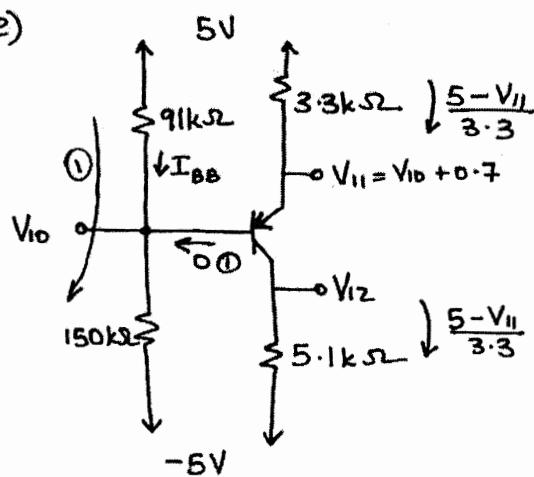

Loop ①

$$5 - 91I_{BB} - 150I_{BB} + 5 = 0$$

$$I_{BB} = \frac{10}{91+150}$$

$$V_{10} = -5 + 150I_{BB}$$

$$= -5 + \frac{150}{91+150} \times 10$$

$$= \underline{\underline{1.224V}}$$


$$V_{11} = V_{10} + 0.7 = \underline{\underline{1.924V}}$$

$$\therefore I_e \approx I_c = \frac{5 - V_{11}}{3.3}$$

$$V_{12} = -5 + \left(\frac{5 - V_{11}}{3.3}\right) 5.1 = \underline{\underline{-0.246V}}$$

4.47

(a)

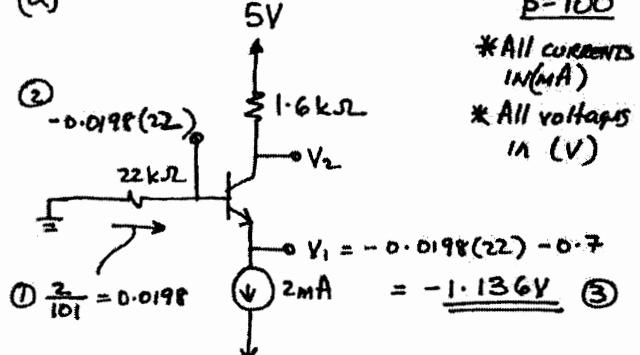


$$B = 100$$

\* All currents in (mA)


\* All voltages in (V)

$$④ V_2 = 5 - 2 \left(\frac{100}{101}\right) 1.6 = \underline{\underline{1.832V}}$$

(b)

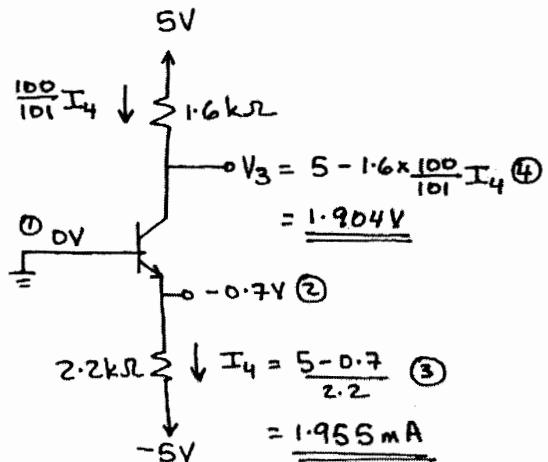

(c)

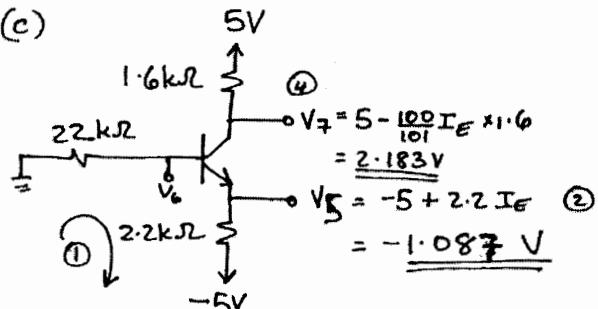


$$\text{Loop ① } 0 - \frac{I_E}{101} 22 - 0.7 - 2.2I_E + 5 = 0$$

$$I_E = 1.778 \text{ mA}$$

$$③ V_G = V_3 + 0.7 = \underline{\underline{-0.387V}}$$

CONT

(d)

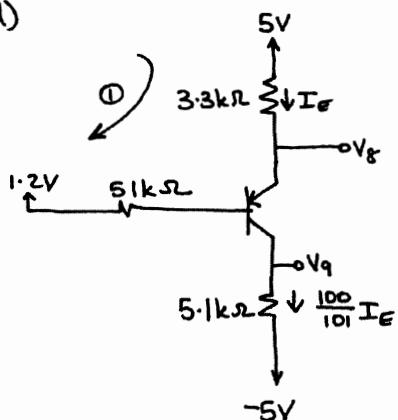

Loop ①

$$5 - 3 \cdot 3 I_E - 0.7 - \frac{I_E}{101} R_{BB} - 1.2 = 0$$

$$I_E = 0.8147 \text{ mA}$$


$$V_{11} = 5 - 3 \cdot 3 I_E = 2.3114 \text{ V}$$

$$V_{12} = -5 + 5.1 \times \frac{100}{101} I_E = -0.8862 \text{ V}$$

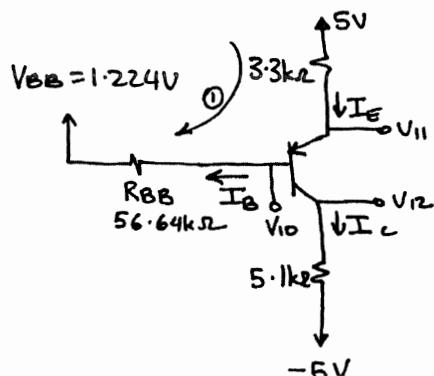(e) Use Thévenin's theorem to simplify the bias network:

$$V_{BB} = -5 + \frac{150}{150+91} \times 10 = 1.224 \text{ V}$$

$$R_{BB} = 150 // 91 = 56.64 \text{ k}\Omega$$



Loop ①

$$5 - 3 \cdot 3 I_E - 0.7 - \frac{I_E}{101} R_{BB} - 1.224 = 0$$


$$I_E = 0.7967 \text{ mA}$$

$$V_{11} = 5 - 3 \cdot 3 I_E = 2.371 \text{ V}$$

$$V_{12} = \frac{100}{101} I_E \times 5.1 - 5 = -0.977 \text{ V}$$

$$V_{10} = V_{11} - 0.7 = 1.67 \text{ V}$$

4.48

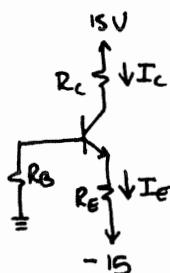Nominal  $\beta = 100$ .

$$\text{Thus, } \text{nominal } \alpha = \frac{100}{101} = 0.99$$

$$\begin{aligned} \text{nominal } I_E &= 1 \text{ mA} \\ \text{nominal } I_C &= 0.99 \text{ mA} \\ \text{nominal } V_C &= 5 \text{ V} \end{aligned}$$

$$\text{Thus, } R_L = \frac{15 - 5}{0.99} = 10.1 \text{ k}\Omega \xrightarrow{\text{use}} 10 \text{ k}\Omega$$

$$I_E = 1 = \frac{15 - 0.7}{R_E + \frac{R_B}{\beta + 1}}$$

$$= \frac{14.3}{R_E + \frac{R_B}{101}}$$

$$\Rightarrow R_E + \frac{R_B}{101} = 14.3 \quad (1)$$

As  $\beta$  varies from 50 to 150, need to limit the variation of  $I_E$  to  $\pm 10\%$  of 1mA. One can reason that the maximum variation in  $I_E$  occurs for  $\beta = 50$  (as opposed to  $\beta = 150$ ). To see this more that when  $\beta$  decreases from 100 to 50 the base current doubles while a change in  $\beta$  from

CONT.

4.49

100 to 150 causes the base current to decrease to  $\frac{2}{3}$  its nominal value. Thus our decision will be based on imposing the 10% limit for  $\beta = 50$ .

$$0.9 = \frac{14.3}{R_E + \frac{R_B}{\beta+1}} = \frac{14.3}{R_E + \frac{R_B}{51}}$$

$$R_E + \frac{R_B}{51} = 15.89 \quad (2)$$

$$(2) - (1) \Rightarrow R_B \left( \frac{1}{51} - \frac{1}{101} \right) = 1.59$$

$$\Rightarrow R_B = 163.8 \text{ k}\Omega \xrightarrow{\text{use}} \underline{\underline{164 \text{ k}\Omega}}$$

Sub into (1) gives

$$R_E = 12.7 \text{ k}\Omega \xrightarrow{\text{use}} \underline{\underline{13 \text{ k}\Omega}}$$

To find the expected range of  $I_C$  &  $V_C$  corresponding to  $\beta$  variation from 50 to 150 we use

$$I_C = \alpha \frac{14.3}{R_E + \frac{R_B}{\beta+1}}$$


$$\text{for } \beta = 50 \quad I_C = \frac{50}{51} \frac{14.3}{13 + \frac{164}{51}} = \underline{\underline{0.864 \text{ mA}}}$$

$$V_C = 15 - 0.864 \times 10 = \underline{\underline{6.36 \text{ V}}}$$

$$\text{for } \beta = 150 \quad I_C = \frac{150}{151} \times \frac{14.3}{13 + \frac{164}{151}}$$

$$= \underline{\underline{1.008 \text{ mA}}}$$
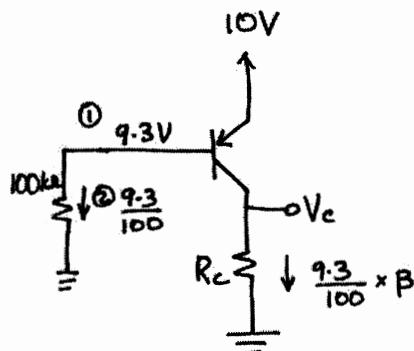
$$V_C = 15 - 1.008 \times 10 = \underline{\underline{4.92 \text{ V}}}$$



$$\text{For } V_C = 5 \text{ V} = \frac{9.3}{100} \times \beta \times R_C \quad \beta = 50$$

$$R_C = \frac{500}{9.3 \times 50} = \underline{\underline{1.08 \text{ k}\Omega}}$$


$$\text{for } \beta = 100$$

$$\begin{aligned} V_C &= \frac{9.3}{100} \times \beta \times R_C = \frac{9.3}{100} \times 100 \times 1.08 \\ &= \underline{\underline{10.04 \text{ V}}} \quad \leftarrow V_{BC} = 9.3 - 10.04 \\ &= -0.74 \end{aligned}$$

Since  $V_{BC} < -0.4 \text{ V}$  the transistor saturates!

4.50

(a)  $\beta = \infty$

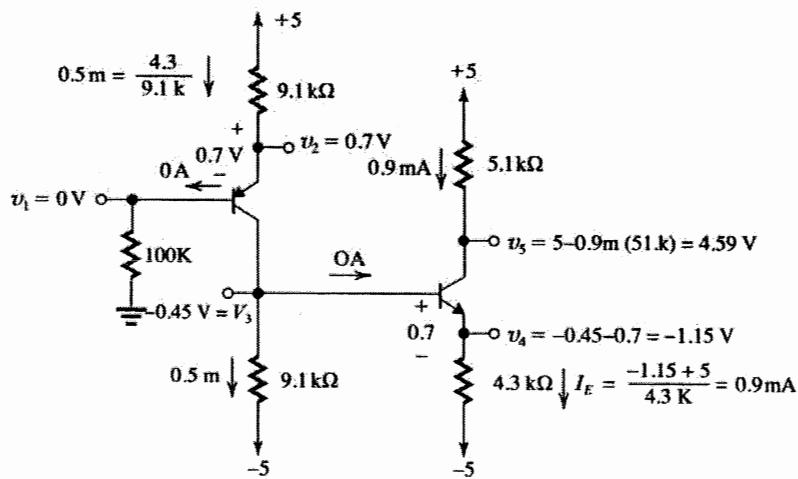

$$+5 - I_{E1}(9.1\text{K}) - 0.7 - I_{B1}(100\text{K}) = 0$$

$$I_{B1} = \frac{I_{E1}}{\beta + 1}$$

$$4.3 = I_{E1} \left( 9.1\text{K} + \frac{100\text{K}}{101} \right)$$

$$I_{E1} = \frac{4.3}{10,090} = .43\text{mA}$$

$$V_2 = 5 - 9.1\text{K}(.43\text{m}) = 1.36\text{V}$$

$$V_1 = 1.36 - 0.7 = .66\text{V}$$

$$I_{C1} = \alpha I_{E1} = .426\text{m}$$

$$-5 + 9.1\text{K}(I_{C1} + I_{B2}) - 0.7 - I_{E2}(4.3\text{K}) + 5 = 0$$


$$9.1\text{K}(.426\text{m}) + \frac{9.1\text{K} I_{E2}}{101} - 0.7 - I_{E2}(4.3\text{K}) = 0$$

$$I_{E2} = \frac{3.2}{4210} = .75\text{mA}$$

$$V_4 = -5 + I_{E2}(4.3\text{K}) = -1.8\text{V}$$

$$V_3 = V_4 + 0.7 = -1.08\text{V}$$

4.50

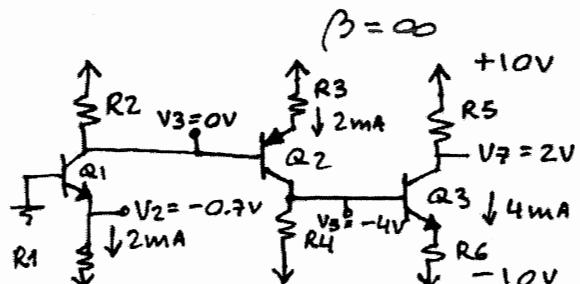

$$R_1 = \frac{9.3}{2} = \underline{\underline{4.7\text{ k}\Omega}}$$

$$R_2 = \frac{10}{2} = 5 \rightarrow \underline{\underline{5.1\text{ k}\Omega}}$$


$$R_3 = \frac{9.3}{2} = \underline{\underline{4.7\text{ k}\Omega}}$$

$$R_4 = \frac{6}{2} = \underline{\underline{3\text{ k}\Omega}}$$

$$R_5 = \frac{8}{4} = \underline{\underline{2\text{ k}\Omega}}$$

$$R_6 = \frac{10 - 4.7}{4} = \underline{\underline{1.3\text{ k}\Omega}}$$

$$\beta = 100$$

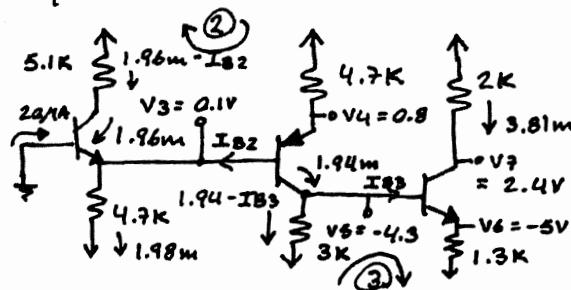

$$\textcircled{2} (1.96 - I_{B2}) \times 5.1 \\ = (\beta + 1) I_{B2} \times 4.7 + 0.7$$

$$I_{B2} = 0.0194 \text{ mA}$$

$$I_{E2} = 1.96 \text{ mA}$$

$$V_3 = \underline{\underline{0.1V}} \quad V_4 = \underline{\underline{0.8V}}$$

$$\textcircled{3} (1.94 - I_{B3}) \times 3 \\ = 0.7 + 1.3 \times (\beta + 1) \cdot I_{B3}$$


$$I_{B3} = 0.038 \text{ mA}$$

$$I_{E3} = 3.85 \text{ mA}$$


$$V_5 = \underline{\underline{-4.3V}} \quad V_6 = \underline{\underline{-5V}}$$

$$V_7 = \underline{\underline{2.4V}}$$

4.51

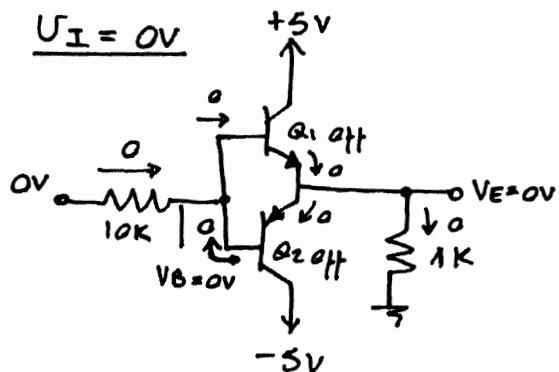


$$U_I = 0V$$

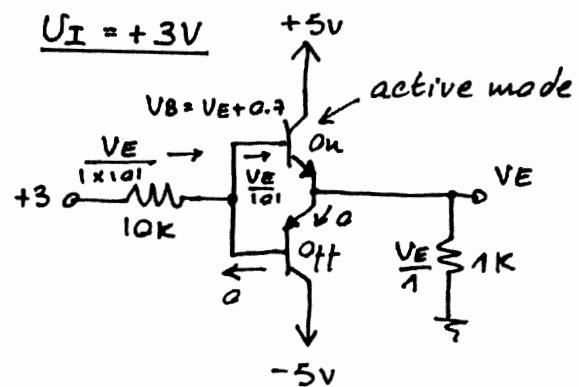

$$3 = \frac{V_E}{10k} \times 10 + 0.7 + V_E$$

$$\Rightarrow V_E = \underline{\underline{2.09V}}$$


$$V_B = \underline{\underline{2.79V}}$$

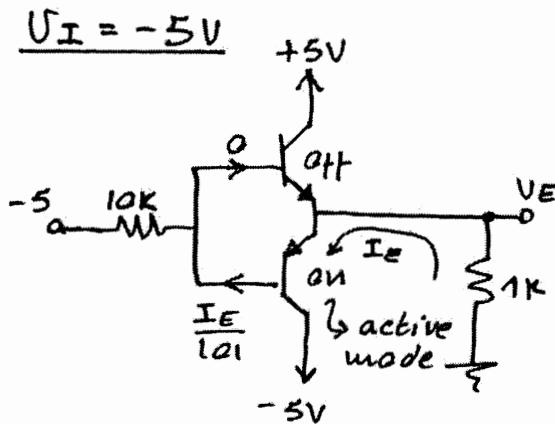

$$I_E = \frac{5 - 0.7}{1 + 10/101} = 3.91 \text{ mA}$$

$$V_E = -3.91 \text{ V}$$

$$V_B = -4.61 \text{ V}$$

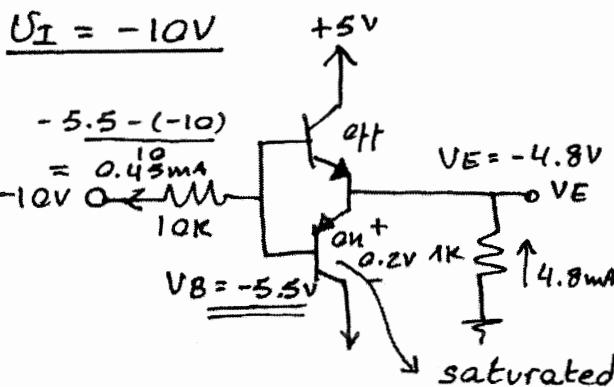


$$\frac{I_C}{I_B} = \frac{4.35}{0.45} = 9.7 < 100$$

thus, Q<sub>2</sub> is saturated as assumed

$$V_E = -4.8 \text{ V} \quad V_B = -5.5 \text{ V}$$

4.52

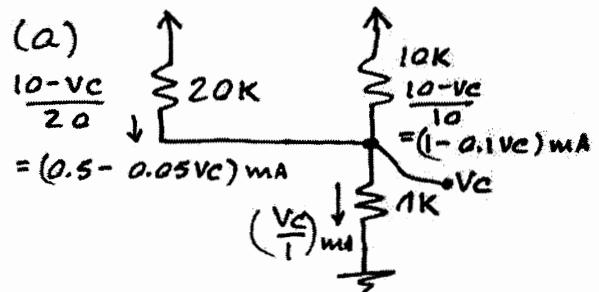

$$(0.5 - 0.005Vc) + (1 - 0.1Vc) = Vc$$


$$Vc = \underline{\underline{1.3 \text{ V}}}$$

$$I_C = \frac{10 - 1.3}{10} = 0.87 \text{ mA}$$

$$I_B = \frac{10 - 1.3}{20} = 0.435 \text{ mA}$$

$$\text{thus } \beta_{\text{forced}} = \frac{0.87}{0.435} = \underline{\underline{2}}$$

(b)

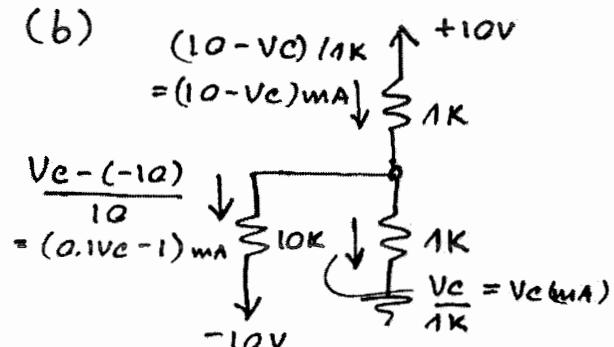

$$10 - Vc = (0.1Vc + 1) + (Vc) \\ \Rightarrow Vc = \underline{\underline{+4.29 \text{ V}}}$$


$$I_C = 4.29 \text{ mA}$$

$$I_B = \frac{4.29 + 10}{10} = 1.43 \text{ mA}$$

$$\beta_{\text{forced}} = \frac{4.29}{1.43} = \underline{\underline{3}}$$

4.53

(C)

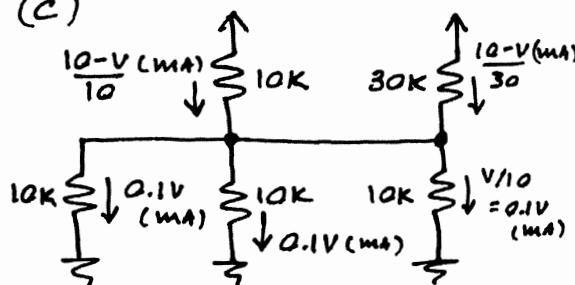

Node equation:

$$\frac{10-V}{10} + \frac{10-V}{30} = 0.1V + 0.1V + 0.1V$$

$$30 - 3V + 10 - V = 9V$$

$$40 = 13V$$

$$\Rightarrow V = \underline{\underline{3.08V}}$$

Thus,  $V_{C3} \approx V_{C4} \approx 3.08V$

$$I_{B3} = 0.1V = 0.308mA$$

$$I_{E3} = \frac{10 - 3.08}{10} \approx 0.692mA$$

$$I_{C3} = 0.692 - 0.308 = 0.384mA$$


$$\beta_3 \text{ forced} = \frac{0.384}{0.308} = \underline{\underline{1.25}}$$

$$I_{C4} = \frac{10 - 3.08}{30} = 0.231mA$$

$$I_{E4} = 0.1V = 0.308mA$$

$$I_{B4} = 0.308 - 0.231 = 0.077mA$$
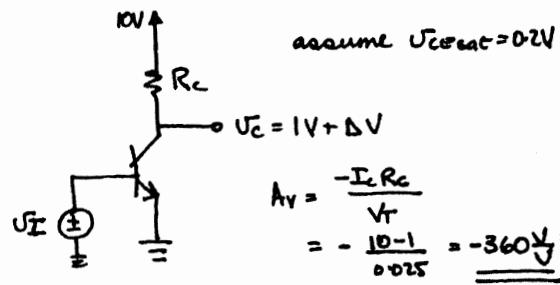
$$\beta_4 \text{ forced} = \frac{0.231}{0.077} = \underline{\underline{3}}$$



then we

At saturation  $V_{C\text{sat}} = 0.3V$

$$\therefore V_C = 1 + \Delta V = 0.3.$$

$$\Delta V = \underline{\underline{-0.7V}}$$

$$\therefore V_O = 0.3V \quad i_C = \frac{10 - 0.3}{R_C}$$

$$\frac{i_{C2}}{i_{C1}} = \frac{9.7/R_C}{(10-1)/R_C} = e^{\Delta V/V_T}$$


$\therefore$  maximum input signal

$$\Delta V = 0.025 \ln \frac{9.7}{9} = \underline{\underline{1.87mV}}$$

If we assume linear operation right to saturation we can use the gain  $A_V$  to calculate the maximum input swing. Thus for an output swing  $\Delta V_O = 0.8$  we have

$$\Delta V_i = \frac{-\Delta V_O}{A_V} = \frac{-0.7}{-360} = \underline{\underline{1.94mV}}$$

4.54

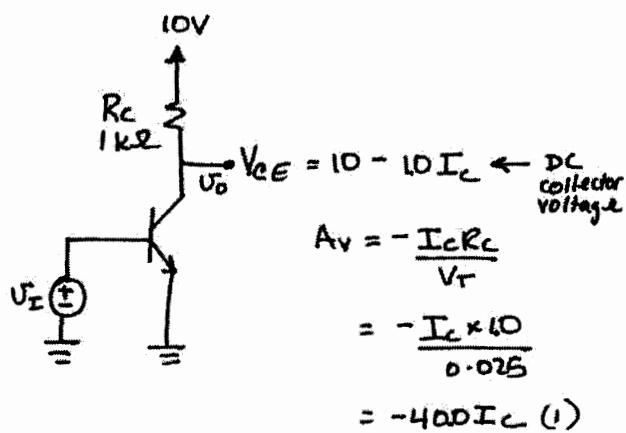

- Assuming the output voltage  $V_O = 0.3V$  is the lowest  $V_{CE}$  to stay out of saturation.

$$\therefore V_O = 0.3 = 10 - I_C R_C$$

$$= 10 - I_C R_C + \Delta V_O$$

$$\Delta V_O = -10 + 0.3 + I_C \times 1 \quad (2)$$

- Max output voltage before the transistor is cut off

$$V_{CE} + \Delta V_O = V_{CC}$$

$$\Delta V_O = V_{CC} - V_{CE}$$

$$= 10 - 10 + 10I_C$$


$$= 10 I_C \quad (3)$$

Use (1) to calculate the gain and (2), (3) to calculate the output limits in order to stay in active mode for a particular bias current  $I_C$ .

$I_C$ (mA)	$A_V$ (V/V)	$\Delta V_O$ (V)
1	-40	-8 to 1
2	-80	-7 to 2
5	-200	-4.7 to 5
8	-320	-1.7 to 8
9	-360	-0.7 to 9

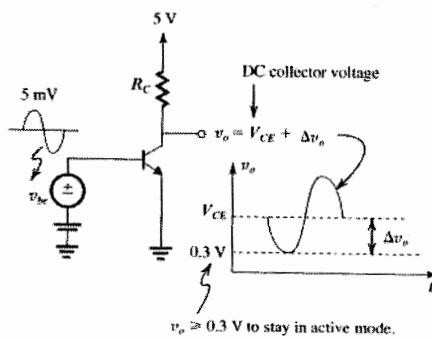
4.55

Since we are assuming linear operation we don't have to go to  $i_C = I_S e^{\frac{V_{BE}}{V_T}}$  equation.



$$A_V = -\frac{I_C R_C}{V_T} = -\frac{V_{CC} - V_{CE}}{V_T}$$


4.57

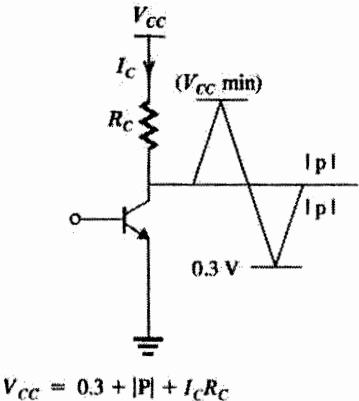

$$V_{cc} = 0.3 + |P| + I_c R_C$$

$$|A_v| = (-)g_m R_C = \frac{I_c R_C}{V_T} \geq \frac{P}{V_T}$$

$$\therefore V_{cc} \text{ min}$$

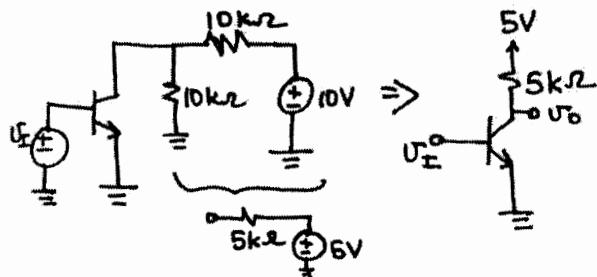

$$\frac{v_o}{v_i} = -\frac{I_c R_L}{V_T} = -\frac{0.5 \times 5}{0.026} = -100 \text{ V/V}$$

4.56

On the verge of Saturation

$$V_{CE} - \Delta v_o = 0.3 \text{ V}$$

for linear operation  $\Delta v_o = A_v v_{be}$

$$V_{CE} - |A_v v_{be}| = 0.3$$

$$(5 - I_c R_C) - A_v \times 5 \times 10^{-3} = 0.3$$

$$5 - |A_v V_T| - |A_v \times 5 \times 10^{-3}| = 0.3$$

$$|A_v(0.025 + 0.005)| = 5 - 0.3$$

$$|A_v| = 156.67 \text{ Note } A_v \text{ is negative.}$$

$$\therefore A_v = -156.67 \text{ V/V}$$

Now we can find the dc collector voltage. Refer to the sketch of the output voltage, we see that

$$|\Delta v_o| = |(A_v \times 0.005)|$$

$$\therefore V_{CE} = 0.3 + |A_v| \cdot 0.005 = 1.08 \text{ V}$$


$$= V_{CEsat} + P + |A_v| V_T$$

$$I_c R_C = |A_v| V_T$$



	$A_v (\text{V/V})$	$P (\text{V})$	$A_v V_T$	$V_{cc} =  A_v  V_T + P + 0.3$
(a)	-20	0.2	0.5	1.0 $\rightarrow$ 1.0 V
(b)	-50	0.5	1.25	2.05 $\rightarrow$ 2.5 V
(c)	-100	0.5	2.5	3.3 $\rightarrow$ 3.5 V
(d)	-100	1.0	2.5	3.8 $\rightarrow$ 4.0 V
(e)	-200	1.0	5.0	6.3 $\rightarrow$ 6.5 V
(f)	-500	1.0	12.5	13.8 $\rightarrow$ 14 V
(g)	-500	2.0	12.5	14.8 $\rightarrow$ 15 V

4.58

(a)

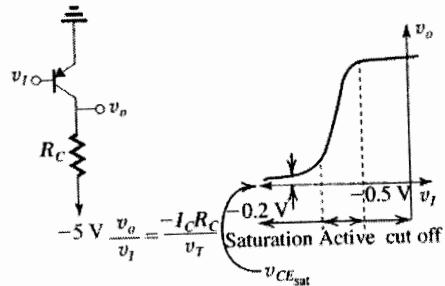

(b)

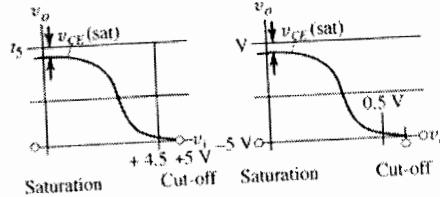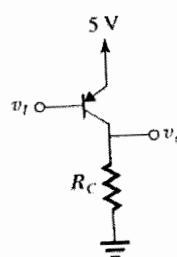

4.59

Including the Early effect we note that:

$$i_c = I_{se} e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$$\text{Also, note } I_c = I_{se} e^{\frac{V_{BE}}{V_T}} \quad \text{Eq (5.38b)}$$

is the value of the collector current with the Early voltage neglected.

Starting with the voltage at the collector we have:

$$\begin{aligned} V_o &= V_{ce} - i_c R_c \\ &= V_{ce} - R_c I_{se} e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{ce}}{V_A} \right) \end{aligned}$$

Take derivative to get gain  $A_v$

$$\begin{aligned} A_v &= \frac{dV_o}{dV_I} \\ &= -R_c I_{se} \left[ \frac{e}{V_T} \left( 1 + \frac{V_{ce}}{V_A} \right) + \frac{e}{V_A} \frac{dV_{ce}}{dV_I} \right] \end{aligned}$$

$$\begin{aligned} A_v &= -R_c I_{se} e^{\frac{V_{BE}}{V_T}} \left[ 1 + \frac{V_{ce}}{V_A} + \frac{V_T}{V_A} \frac{dV_{ce}}{dV_I} \right] \\ &= -\frac{R_c I_c}{V_T} \left[ 1 + \frac{V_{ce}}{V_A} + \frac{V_T}{V_A} A_v \right] \end{aligned}$$

$$-A_v \left[ \frac{i}{R_c I_c} + \frac{V_T}{V_A} \right] = 1 + \frac{V_{ce}}{V_A} = \frac{V_A + V_{ce}}{V_A}$$

$$-A_v \left[ \frac{V_A + R_c I_c}{\frac{R_c I_c V_A}{V_T}} \right] = \frac{V_A + V_{ce}}{V_A}$$

$$\begin{aligned} -A_v \frac{R_c I_c}{V_T} &= \frac{V_A}{V_A + R_c I_c} \times \frac{V_A + V_{ce}}{V_A} \\ &= \frac{V_A + V_{ce}}{V_A + R_c I_c} \quad \div \text{top } \cancel{V_A} \text{ bottom by } V_A + V_{ce} \\ &= \frac{1}{\frac{V_A}{V_A + V_{ce}} + \frac{R_c I_c}{V_A + V_{ce}}} \end{aligned}$$

This term is  $\approx 1$

$\therefore V_A \gg V_{ce}$

$$\therefore A_v \approx \left[ \frac{-R_c I_c / V_T}{\left( 1 + \frac{R_c I_c}{V_A + V_{ce}} \right)} \right]$$

Q.E.D.

For  $V_{cc} = 6V$   $V_{ce} = 2.5V$   $V_A = 100V$

Ignoring the Early Voltage:

$$A_v = -\frac{I_c R_c}{V_T} = \frac{V_{cc} - V_{ce}}{V_T} = \frac{6 - 2.5}{0.025} = 100 \frac{V}{V}$$


With the Early Voltage

$$A_v \approx \frac{-I_c R_c / V_T}{1 + \frac{R_c I_c}{V_A + V_{ce}}}$$

But  $V_{ce} = 0.5V$  &  $\frac{I_c R_c}{V_T} = 100$  as shown above.

$$\begin{aligned} \therefore A_v &= \frac{-100}{1 + \frac{2.5}{100 + 2.5}} \\ &= -\underline{97.7 \frac{V}{V}} \end{aligned}$$

4.60

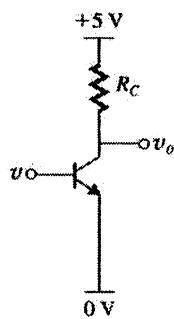

For  $V_o = 2V$ ,  $R_C = 1\text{ k}\Omega$

$$I_C = \frac{5 - 2}{1} = 3 \text{ mA}$$

$$A_V = \frac{-I_C R_C}{V_T} = -120 \text{ V/V}$$

$$\Delta V_o = -120 \times 5 = -600 \text{ mV}$$

$$\Delta V_{BE} = V_T \ln[I_2/I_1]$$

$$\frac{I_2}{I_1} = e^{\Delta V_{BE}/V_T} = e^{5/25}$$

$$(a) I_2 = I_1 e^{5/25} = 3 \times 1.22 = 3.66 \text{ mA}$$

$$\Delta V_o = (I_2 - I_1)R_C = 0.66 \times 1 = 0.660 \text{ V}$$

$$A_V = -660/5 = -132 \text{ V/V}$$

$$(b) I_3 = I_1 e^{-5/25} = 3 \times 0.82 = 2.46 \text{ mA}$$

$$\Delta V_o = (I_3 - I_1)R_C = 0.544 \text{ V}$$

$$A_V = -544/5 = -109 \text{ V/V}$$

$\Delta V_{BE}$	$\Delta V_o$ (exp)	$\Delta V_o$ (linear)
+5 mV	-660 mV	-600 mV
-5 mV	+544 mV	+600 mV

(a) For maximum gain you would bias at the largest current since  $A_V = -I_C R_C / V_T$ . This also means you would bias at the edge of saturation  $A_V = \frac{V_{CE} - V_{CESAT}}{V_T}$

$$= \frac{5 - 0.3}{0.025}$$

$$= \underline{\underline{-188 \text{ V/V}}}$$

However any signal swing at the output would automatically drive it into saturation.

(b) For  $A_V = -100 \text{ V/V}$

$$A_V = \frac{V_{CE} - V_{CG}}{V_T} = \frac{5 - V_{CE}}{V_T} = 100$$

$$V_{CE} = \underline{\underline{2.5 \text{ V}}}$$

(c) For a dc collector current of 0.5mA

$$R_C = \frac{5 - 2.5}{0.5} = \underline{\underline{5 \text{ k}\Omega}}$$


(d)  $I_S = 10^{-15} \text{ A} \Rightarrow$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$0.5 \times 10^{-3} = 10^{-15} e^{V_{BE}/0.025}$$

$$V_{BE} = \underline{\underline{0.673 \text{ V}}}$$

4.61

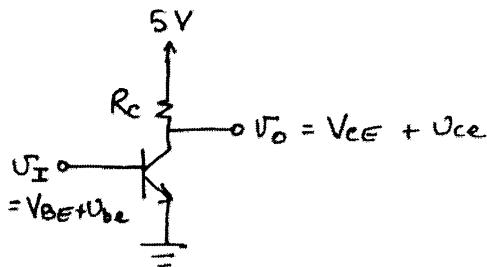

(e) If we assume linear operation we can use  $A_V$  to find the output change for  $U_{be} = 5\text{mV}$

$$\begin{aligned} U_{ce} &= A_V U_{be} = -100 \times 0.005 \\ &= -0.5\text{ V} \sim \text{peak sine wave.} \end{aligned}$$

∴ the output is a 0.5V p sine wave

(f) For  $U_{ce} = 0.5$

$$i_c = \frac{0.5}{5} = \underline{0.1\text{mA peak}}$$


This current is superimposed on  $I_c$ .

$$(g) I_B = I_c / \beta = \frac{0.5}{100} = \underline{0.005\text{mA}}$$


$$i_b = \frac{i_c}{\beta} = \frac{0.1}{100} = \underline{0.001\text{mA p}}$$

$$\begin{aligned} (h) R_{in} &= \frac{U_{be}}{i_b} = \frac{0.005}{0.001 \times 10^{-3}} \\ &= \underline{5\text{k}\Omega} \end{aligned}$$

(i) See sketches that follow:

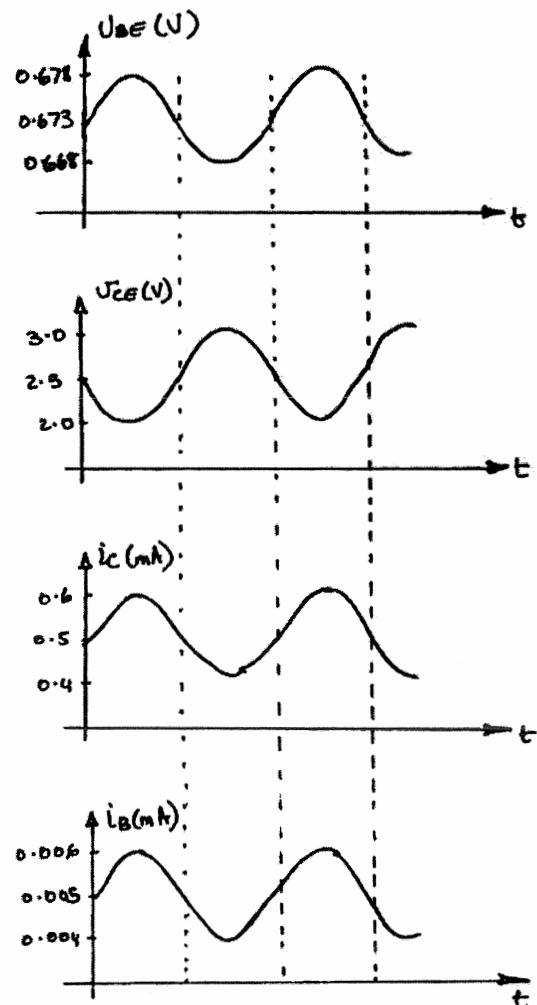

4.62

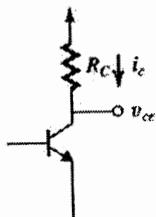

$$A_V = \frac{V_{ce}}{V_{be}} = \frac{-I_C R_C}{V_T}$$

$$\text{But } V_{ce} = -i_C R_C$$

$$\therefore -\frac{i_C R_C}{V_{be}} = -\frac{I_C R_C}{V_T}$$

$$\text{Now } g_m = \frac{\text{Output current}}{\text{Input voltage}} = \frac{i_C}{V_{be}}$$

$$\therefore g_m R_C = \frac{I_C R_C}{V_T}$$


$$g_m = I_C / V_T$$

$$g_m = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ ms}$$

$$\text{for } I_C = 1 \text{ mA}$$

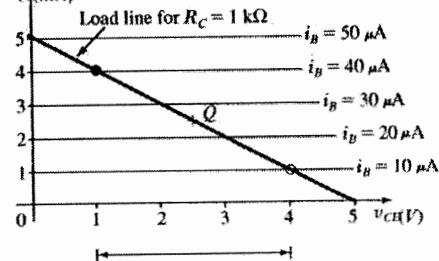4.63

$$I_C (\text{mA}) \quad \text{For } \beta = 100 : \quad I_C = \beta I_B$$



$$\text{Peak-to-peak } V_c \text{ swing} = 4 - 1 = 3 \text{ V}$$

$$\text{For Q point at } V_{CE}/2 = 2.5 \text{ V}$$

$$V_{CE} = 2.5 \text{ V} : \quad I_C = 2.5 \text{ mA}$$

$$I_B = 25 \mu\text{A}$$

$$I_B = \frac{V_{BB} - 0.7}{R_B} = 25 \mu\text{A}$$

$$\Rightarrow V_{BB} = I_B R_B + 0.7 = 2.5 + 0.7 = 3.2 \text{ V}$$

4.63

(a) Using the exponential characteristic :

$$i_C = I_{ce} e^{\frac{V_{be}}{V_T}} - I_C$$

$$\text{giving } \frac{i_C}{I_C} = e^{\frac{V_{be}}{V_T}} - 1$$

(b) Using small-signal approximation :

$$i_C = g_m V_{be} = \frac{I_C}{V_T} \cdot V_{be}$$

$$\text{Thus, } \frac{i_C}{I_C} = \frac{V_{be}}{V_T}$$

See table below


For signals at  $\pm 5 \text{ mV}$ , the error introduced by the small-signal approximation is 10 %

The error increases to above 20% for signals at  $\pm 10 \text{ mV}$ .

$v_{be}$ (mV)	$i_C/I_C$ Expan.	$i_C/I_C$ small signal.	% Error
+1	+0.041	+0.040	-2
-1	-0.03P	-0.040	+2
+2	+0.083	+0.080	-4
-2	-0.077	-0.080	+4
+5	+0.221	+0.200	-9.5
-5	-0.181	-0.200	+10.3

+8	+0.377	+0.320	-15.2
-8	-0.274	-0.320	+16.8
+10	+0.492	+0.400	-18.7
-10	-0.330	-0.400	+21.3
+12	+0.616	+0.480	-22.1
-12	-0.381	-0.480	+25.9

4.65

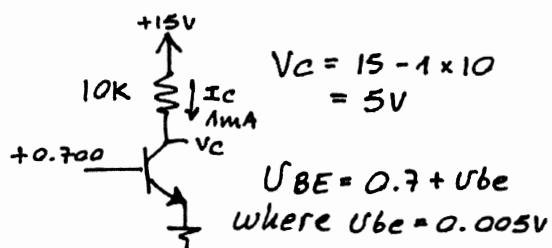

$$I_C \approx I_c (1 + \frac{U_{be}}{V_T}) \quad \text{Eq. (5.83)}$$

$$I_C = I_c + i_c \quad \text{where:}$$

$$i_c = \frac{1m \times 0.005}{25m} = 0.2m$$

$$I_C = 1mA + 0.2mA$$

$$V_C = V_{cc} - I_C R_C \quad \text{Eq. (5.101)}$$

$$\Rightarrow V_C = \underbrace{i_c R_C}_{0.2mA \times 10K}$$

$$V_C = 5V - 2V$$

$$\text{gain} = \frac{-2V}{0.005V} = -400 \text{ V/V}$$

$$\text{while } -g_m \cdot R_C = -\frac{1m}{25m} \cdot 10K = -400 \frac{\text{V}}{\text{V}}$$

$$g_m = \frac{I_C}{V_T} = \frac{1.2mA}{25mV} = \underline{\underline{48mA/V}}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{120}{48 \times 10^3} = \underline{\underline{2.5k\Omega}}$$

$$r_e = \frac{r_\pi}{\beta+1} = \frac{2500}{121} = 20.6\Omega$$

For a bias current of  $120\mu A$   
i.e. 10 times lower:

$$g_m = \frac{48}{10} = 4.8mA/V$$

$$r_\pi = 10 \times 2.5 = 25k\Omega$$

$$r_e = 10 \times 20.6 = 206\Omega$$

4.66

$$I_C = 2mA \Rightarrow g_m = \frac{2mA}{25mV}$$

$$g_m = 80mA/V$$

$$r_e = \frac{V_T}{I_E}, \quad I_E = I_C \frac{(\beta+1)}{\beta}$$

$$I_E = 2mA \times \frac{51}{50} = 2.04mA$$

$$r_e = \frac{25m}{2.04m} = 12.25\Omega$$

$$r_\pi = \frac{\beta}{g_m} = \frac{50}{80 \times 10^{-3}} = 625\Omega$$

gain:  $-g_m \times R_C$

For  $R_C = 5k\Omega$  and  $\hat{U}_{be} = 5mV$

$$\hat{U}_o = -80m \times 5K \times 5mV \\ = -2V$$

4.67

$$g_m = 50 \text{ mA} = \frac{I_c}{V_T}$$

$$\Rightarrow I_c = g_m \times V_T = 50 \text{ mA} \times 25 \text{ mV} = 1.25 \text{ mA}$$

$$r_{\pi} = 2 \text{ k} = \frac{\beta}{g_m} \Rightarrow \beta = 2 \text{ k} \times 50 \text{ mA}$$

$$\beta = \frac{100}{g_m} \rightarrow \alpha = \frac{100}{101} = 0.99$$

$$I_E = \frac{I_c}{\alpha} = \frac{1.25 \text{ mA}}{0.99} = 1.26 \text{ mA}$$

$$i_{c(t)} = I_c + g_m v_{be}(t)$$

$$= 1 + 40 \cdot 10^3 \times 0.005 \sin \omega t = \frac{1 + 0.2 \sin \omega t}{1 + 0.2 \sin \omega t, \text{ mA}}$$

$$v_{c(t)} = 5 - R_C i_{c(t)}$$

$$= \frac{2 - 0.6 \sin \omega t}{1 + 0.2 \sin \omega t, \text{ V}}$$

$$i_{b(t)} = i_{c(t)}/\beta$$

$$= \frac{1 + 0.2 \cdot 0.99 \sin \omega t}{100} = \frac{10 + 2 \sin \omega t}{100}, \text{ mA}$$

$$\text{Voltage gain} = -\frac{0.6}{0.005} = -120 \text{ V/V}$$

4.68

$$g_m \text{ varies from: } 1.2 \times 60 = 72 \text{ mA} \text{ to } 0.8 \times 60 = 48 \text{ mA}$$

$$\beta \text{ varies from } 50 \text{ to } 200$$

$$R_{in/base} = r_{\pi} = \beta/g_m$$

$$\text{Largest value: } r_{\pi} = \frac{\beta_{\max}}{g_{m\min}} = \frac{200}{48 \text{ mA}} = 4.2 \text{ k}\Omega$$

$$\text{Smallest value: } r_{\pi} = \frac{\beta_{\min}}{g_{m\max}} = \frac{50}{72 \text{ mA}} = 694 \text{ }\Omega$$

4.70

$$i_c = I_c + g_m \hat{v}_{be} \sin \omega t$$

$$v_c = v_{cc} - I_c R_C - g_m R_C \hat{v}_{be} \sin \omega t$$

To maintain BJT in active region,  $v_c > v_{be}$ , thus  $v_{cc} - I_c R_C - g_m R_C \hat{v}_{be} > v_{be} + \hat{v}_{be}$

To obtain the largest possible output signal we design such that this constraint is satisfied with the equality sign, that is:

$$v_{cc} - R_C I_c - g_m R_C \hat{v}_{be} = v_{be} + \hat{v}_{be}$$

substituting  $g_m = \frac{I_c}{V_T}$ , gives.

$$v_{cc} - R_C I_c - R_C I_c \frac{\hat{v}_{be}}{V_T} = v_{be} + \hat{v}_{be}$$

$$\Rightarrow R_C I_c \left(1 + \frac{\hat{v}_{be}}{V_T}\right) = v_{cc} - v_{be} - \hat{v}_{be}$$

CONT.

4.69

$$v_c = 2 \text{ V} \Rightarrow I_c = \frac{v_{cc} - v_c}{R_C}$$

$$I_c = \frac{5 - 2}{3 \text{ k}} = 1 \text{ mA}$$

$$g_m = \frac{I_c}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mA/V}$$

$$R_c I_c = \frac{(V_{CC} - V_{BE} - \hat{V}_{be})}{(1 + \frac{\hat{V}_{be}}{V_T})} \quad Q.E.D.$$

$$\begin{aligned} \text{Voltage gain} &= -g_m \cdot R_c \\ &= -\frac{I_C}{V_T} \cdot R_c \\ &= -\frac{V_{CC} - V_{BE} - \hat{V}_{be}}{V_T + \hat{V}_{be}} \end{aligned}$$

For  $V_{CC} = 5V$ ,  $V_{BE} = 0.7V$  and  $\hat{V}_{be} = 5mV$

$$R_c I_c = \frac{5 - 0.7 - 0.005}{1 + \frac{0.005}{0.025}} = 3.6V$$

Thus,

$$V_C = 5 - 3.6 = +1.4V$$

$$\begin{aligned} \text{Amplitude of output signal is} \\ &= 1.4 - (V_{BE} + \hat{V}_{be}) \\ &= 1.4 - 0.7 - 0.005 \\ &= 0.695V \end{aligned}$$

$$\text{Voltage gain} = -\frac{0.695}{0.005} = -139V/V$$

Check

$$\begin{aligned} \text{Voltage gain} &= -\frac{(5 - 0.7 - 0.005)}{0.025 + 0.005} \\ &= -143V/V \end{aligned}$$

The difference is caused by decimal rounding-up of  $R_c I_c$ .

Otherwise:

$$\begin{aligned} \text{Voltage gain} &= -\frac{0.716}{0.005} \\ &= -143V/V \end{aligned}$$

4.71

	a	b	c	d	e	t	s
$\alpha$	1.00 0	0.990	0.98	1	0.890	0.90	0.841
$\beta$	$\infty$	100	50	$\infty$	100	9	16
$I_C$ (mA)	1.00	0.89	1.00	1.00	0.48	4.5	17.5
$I_E$ (mA)	1.00	1.00	1.02	1.00	0.25	5	18.6
$I_B$ (mA)	0	0.010	0.020	0	0.002	0.5	1.10
$g_m$ (mA/V)	40	39.6	40	40	0.01	180	700
$r_e$ ( $\Omega$ )	25	25	24.5	25	100	5	1.34
$r_\pi$ ( $\Omega$ )	00	2.5 k	1.255	00	10.1 k	50	227

4.72



$$I_C = 1mA, \beta = 120, \alpha = 0.992$$

$$g_m = \frac{I_C}{V_T} = \frac{1}{25} = 40mA/V$$

$$r_\pi = \frac{\beta}{g_m} = \frac{120}{40 \times 10^3} = 3k\Omega$$

$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m} = \frac{0.992}{40 \times 10^{-3}} = 24.8\Omega$$

The four equivalent circuit models are:

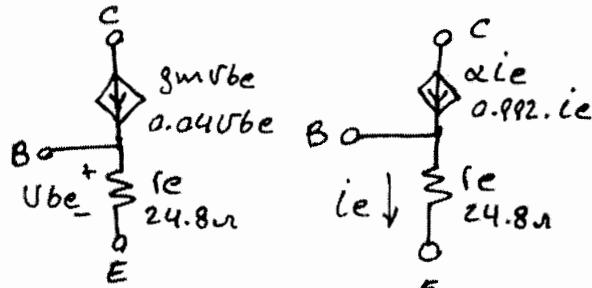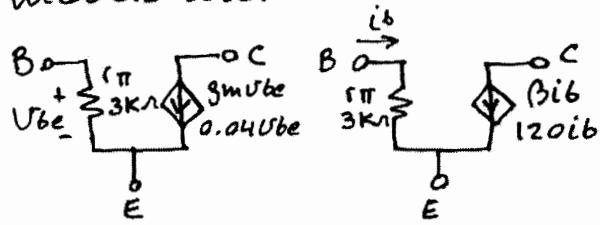


4.73

$\beta$  very high  $\rightarrow \alpha = 1$

$$I_C = I_E = 0.5 \text{ mA}$$

$$V_C = 5 - 7.5 \times 0.5 = + \underline{\underline{1.25 \text{ V}}}$$
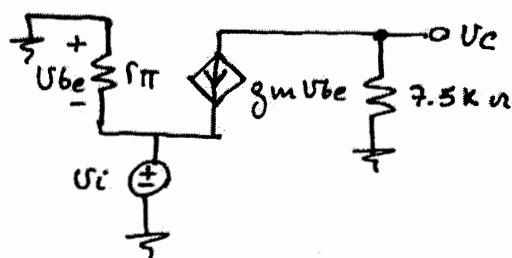
$$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V}$$



Observe that  $U_{be} = -U_i$   
the output voltage  $U_C$  is found from:

$$U_C = -g_m U_{be} \times 7.5 \text{ k}\Omega$$

Thus the voltage gain is

$$\begin{aligned} \frac{U_C}{U_i} &= g_m \times 7.5 \text{ k}\Omega \\ &= 20 \times 7.5 = \underline{\underline{150 \text{ V/V}}} \end{aligned}$$



4.74

$$\begin{aligned} \frac{U_C}{U_{be}} &= -g_m R_C \Rightarrow U_{be} = \frac{1}{50 \times 2} \\ &= \underline{\underline{10 \mu\text{V p-p to p-p}}} \end{aligned}$$

$$I_b = \frac{U_{be}}{r_\pi} = \frac{10 \times 10^{-3}}{\beta/g_m} = \frac{0.01}{100/0.05}$$


$$I_b = \underline{\underline{0.005 \text{ mA p-p to p-p}}}$$

4.75

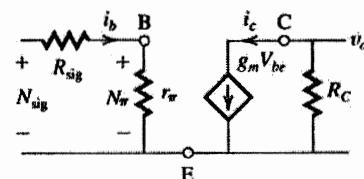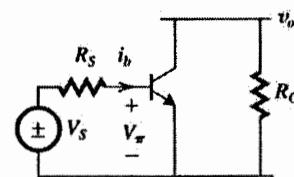

$$\begin{aligned} \frac{v_o}{v_{sig}} &= \frac{v_1}{v_i} = \frac{r_\pi}{r_\pi + R_{sig}} (-) g_m R_C \\ &= \frac{-r_\pi g_m}{r_\pi + R_{sig}} R_C \\ &= \frac{-\beta R_C}{r_\pi + R_{sig}} \end{aligned}$$

4.76

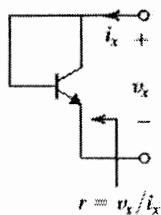


Apply  $V_i$

$$\text{then } v_B = V_x$$

$$i_x = i_b + i_c$$

$$v_x = (i_b + i_c)r_e$$

$$= i_x r_e$$

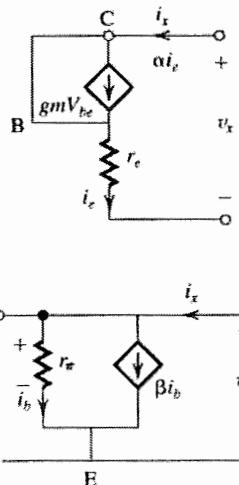

$$\therefore r = \frac{v_t}{i_x} = r_e$$

(or)


$$i_x = \beta i_b + i_b$$

$$= (\beta + 1)i_b$$

$$= (\beta + 1)\frac{v_x}{r_\pi}$$

$$r = \frac{v_x}{i_x} = \frac{r_\pi}{\beta + 1} = r_e$$

4.77

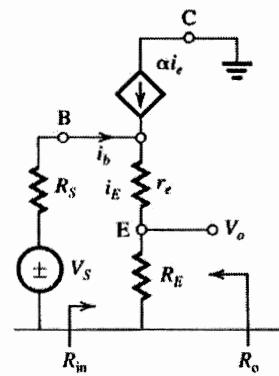

Neglecting  $r_o$

$$R_{IN} = \frac{v_{be}}{i_b}$$

$$= \frac{i_e(r_e + R_E)}{i_e / (\beta + 1)}$$

$$= (\beta + 1)(r_e + R_E)$$

$$v_o = -\alpha i_e R_E$$

$$i_e = \frac{v_{be}}{r_e + R_E}$$

$$\therefore \frac{v_o}{v_{be}} = \alpha \frac{R_E}{r_e + R_E}$$

$$A_V = \frac{v_o}{v_{be}} = -\frac{\alpha}{r_e} \frac{R_E}{1 + R_E/r_e} = -\frac{g_m R_C}{1 + g_m R_E}$$

4.78

$$\beta = 200 \rightarrow \alpha = 0.995$$

$$I_C = \alpha I_E = 0.995 \times 10 \text{ mA} = 9.95 \text{ mA}$$

$$V_C = 9.95 \text{ mV} \times 100 = 0.995 \text{ V}$$


$$I_B \cong \frac{10 \text{ mA}}{200} = 0.05 \text{ mA}$$

$$V_B = 1.5 - 10 \text{ k}\Omega \times 0.05 \text{ mA}$$

$$= 1 \text{ V}$$

$$\Rightarrow V_{BC} = +0.005$$

→ Active region

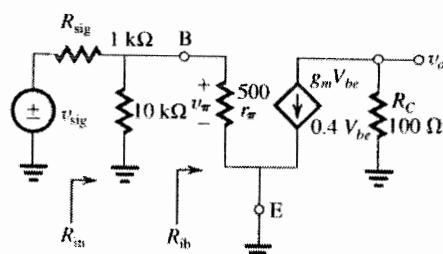

$$g_m = \frac{I_C}{V_T} = \frac{9.95}{25 \text{ m}} = 0.4 \text{ A/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{200}{0.4} = 500 \Omega$$

$$R_{i\delta} = r_\pi = 500 \Omega$$

$$R_{in} = 10 \text{ k}\Omega \parallel r_\pi = 476 \Omega$$

$$v_{be} = v_{sig} \times \frac{R_{in}}{R_{sig} + R_{in}} = v_{sig} \times 0.32$$

also :

$$v_o = -g_m v_{be} \cdot R_C$$

$$= -g_m R_C \times 0.32 v_{sig}$$

$$= -0.4 \times 100 \times 0.32 v_{sig}$$

$$= -12.8 v_{sig}$$


$$\Rightarrow \text{gain } \frac{v_o}{v_s} = -12.8 \approx -13 \frac{v}{V}$$

If  $v_o = \pm 0.4 \text{ V}$

$$\hat{v}_s = \frac{\hat{v}_o}{13} = 30 \text{ mV}$$

$$\hat{v}_{be} = 0.32 \times 30 \text{ m} = 9.8 \text{ mA}$$

4.80

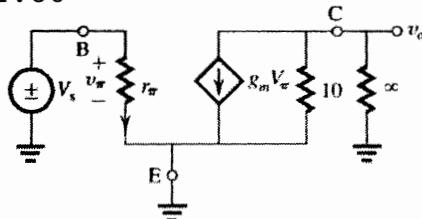

$$V_s = V_\pi \Rightarrow \frac{V_o}{V_s} = -g_m r_\pi$$


$$\text{but: } r_\pi = \frac{V_A}{I_C} = \frac{V_A}{V_T \cdot g_m}$$

$$\Rightarrow \frac{V_o}{V_s} = -\frac{V_A}{V_T}$$

$$\text{if } V_A = 25 \text{ V} \Rightarrow \frac{V_o}{V_s} = -1000 \frac{\text{V}}{\text{V}}$$

$$\text{if } V_A = 250 \text{ V} \Rightarrow \frac{V_o}{V_s} = -10,000 \frac{\text{V}}{\text{V}}$$

4.81

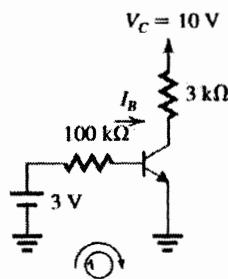

DC Analysis:

$$(1) I_B = \frac{3 - 0.7}{100}$$

$$I_B = 0.023 \text{ mA}$$

Saturation begins to occur when  $V_C \leq 0.7 \text{ V}$

$$\therefore I_C \geq \frac{10 - 0.7}{3} = 3.1 \text{ mA}$$

$$I_C = \beta I_B \rightarrow \beta \geq \frac{3.1}{0.023} = 135$$


$$\beta = 25 :$$

$$r_e = \frac{V_T}{I_E} = \frac{V_T}{(\beta + 1)I_B} = \frac{25 \times 10^{-3}}{26 \times 0.023 \times 10^{-3}}$$

$$r_e = 41.8 \Omega$$

$$g_m = \frac{\alpha}{r_e} = \frac{25 / 26}{41.8} = 23 \frac{\text{mA}}{\text{V}}$$

4.82

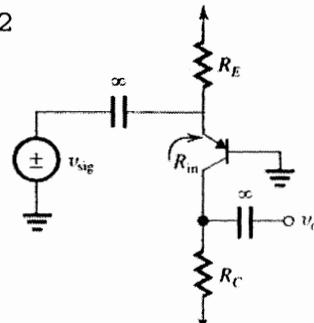

$$R_{in} = r_e \parallel R_E$$

$$\approx r_e$$

$$= 75 \Omega$$

$$I_E = \frac{25 \text{ mV}}{75 \Omega} = (0.33 \text{ mA})$$

$$R_E = \frac{10 - 0.7}{0.33} = 28 \text{ k}\Omega$$

$$n = 2.8$$

$$R_C = 14 \text{ k}\Omega$$

$$\frac{V_o}{V_i} = \frac{\alpha R_C}{r_e} = \frac{14}{0.075} = 187 \text{ V/V}$$


4.83

$$R_{in} = R_E \parallel r_e \quad r_e \approx 100\Omega$$

thus,  $\frac{V_T}{I_E} = 100 \rightarrow I_E = 0.25mA$

$$V_E = 0.7V$$
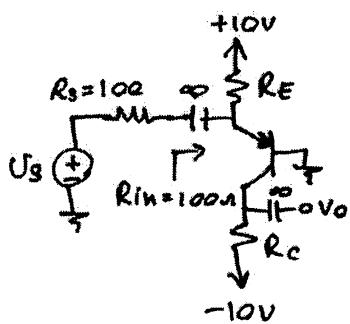
$$R_E = \frac{10 - 0.7}{1m} = \underline{\underline{9.3k\Omega}}$$



Selection of a value for  $R_E$ :

The voltage gain is directly proportional to  $R_C$ ,

$$\begin{aligned} \frac{V_o}{U_s} &= \frac{V_e}{U_s} \cdot \frac{V_o}{V_e} \\ &= \frac{R_{in}}{R_B + R_{in}} \cdot \frac{R_C}{r_e} \\ &\approx \frac{100}{100+100} \cdot \frac{R_C}{0.1} \\ &= 5R_C, \quad R_C \text{ in k}\Omega. \end{aligned}$$

For an emitter-base signal as large as 10mV, the signal at the collector will be  $gm R_C \times 0.010$  volts. Thus the maximum collector

voltage in the positive direction will be:

$$\begin{aligned} |V_{cl}|_{max} &= V_c + 0.01 gm \cdot R_C \\ &= -10 + I_E R_C + 0.01 \times \frac{1}{0.1} \times R_C \\ &= -10 + 0.25 R_C + 0.1 R_C \\ &= -10 + 0.35 R_C \end{aligned}$$

To prevent saturation,  $|V_{cl}|_{max} \leq V_B$  which is 0V. Thus to obtain maximum gain while allowing an emitter-base signal as large as 10mV and at the same time keeping the transistor in the active mode we select  $R_C$  from:  
 $-10 + 0.35 R_C = 0$   
 $\Rightarrow R_C = \underline{\underline{28.6k\Omega}}$

$$\text{Voltage gain} = \frac{V_o}{U_s} = 5 R_C = 143V/V$$

4.84


For large  $\beta$ , the DC base current will be  $\sim 0$ .  
Thus the DC voltage at the base can be found directly using the voltage V-divider rule

$$V_B = 15 \cdot \frac{100}{100+100} = 7.5V$$

$$V_{BE} = 0.7$$

$$V_E = 7.5 - 0.7 = 6.8V$$
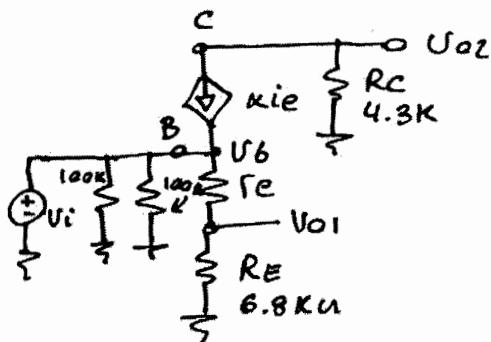
$$\rightarrow I_E = \frac{6.8V}{6.8k\Omega} = 1mA$$



$$U_B = U_i$$

$$\rightarrow \frac{U_{O1}}{U_i} = \frac{R_E}{R_E + r_e} \quad Q.E.D.$$

Also,

$$i_e = \frac{U_B}{r_e + R_E} = \frac{U_i}{r_e + R_E}$$

and,

$$\begin{aligned} U_{O2} &= -\alpha i_e \cdot R_C \\ &= -\frac{\alpha R_C U_i}{r_e + R_E} \end{aligned}$$

Thus,

$$\frac{U_{O2}}{U_i} = -\frac{\alpha R_C}{R_E + r_e} \quad Q.E.D.$$

Substituting  $r_e = \frac{V_T}{I_E} = 25\Omega$   
and  $R_E = 6.8k\Omega$ ,  $R_C = 4.3k\Omega$   
and  $\alpha \approx 1$  gives


$$\frac{U_{O1}}{U_i} = \frac{6.8}{0.025 + 6.8} = \underline{0.996} \text{ V/V}$$

$$\frac{U_{O2}}{U_i} = -\frac{4.3}{6.8 + 0.025} = \underline{0.63} \text{ V/V}$$

If the node labeled  $U_{O2}$  is connected to ground:  
 $R_E = 0$

$$\frac{U_{O2}}{U_i} = -\alpha \frac{R_C}{r_e}$$

4.85

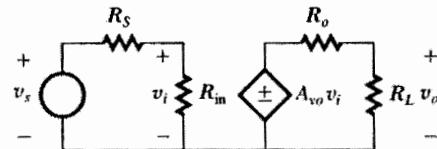

Given :  $R_s = 100 \text{ k}\Omega$   $A_v = 2 \text{ k}\Omega$  &  $R_L = 1 \text{ k}\Omega$

Find :  $R_{in}$ ,  $A_{vo}$ ,  $R_o$

a)  $|V_i(e)| \geq 0.9|v_S(t)|$

$$\theta_{i(t)} = \frac{R_{IN}}{R_{IN} + R_s} v_S(t)$$

$$\left| \frac{R_{IN}}{R_{IN} + R_s} v_S(e) \right| \geq 0.9 |v_S(t)|$$

$$\frac{R_{in}}{R_{IN} + R_s} \geq 0.9$$

b)  $v_o(t) = \frac{R_L}{R_L + R_o} A_{vo} v_i(t)$

$$v_o(t) = \frac{R_o^2}{R_o^2 + R_L} A_{vo} v_i(t)$$

$$|v_o(t)| \geq 0.9 |v_o(t)|$$

$$\frac{R_o}{R_o + R_L} \geq 0.9 \frac{R_L}{R_L + R_o} \Rightarrow$$

$$\begin{aligned} R_o &\leq \frac{R_L R_o}{9R_L + 10R_o} = \frac{(10^3)(2 \times 10^3)}{9(2 \times 10^3) + 10(1 \times 10^3)} \\ &= 250 \Omega \end{aligned}$$


c) Taking the limiting values for  $R_{in}$  &  $R_{out}$

$$10 = A_v \left( \frac{R_{IN}}{R_{IN} + R_s} \right) \left( \frac{R_L}{R_O + R_L} \right)$$

$$A_v \left( \frac{900 \times 10^3}{900 \times 10^3 + 100 \times 10^3} \right) \left( \frac{2 \times 10^3}{250 + 2 \times 10^3} \right)$$


$$A_{VO} = 12.5$$

4.86

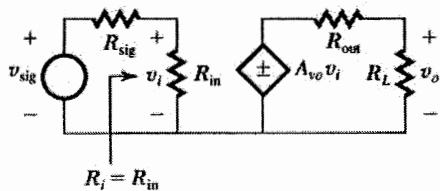

$$v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig} = \frac{R_i}{R_i + R_{sig}} v_{sig}$$

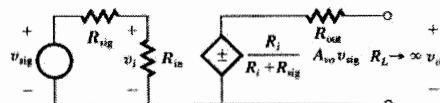
Setting  $R_L \rightarrow \infty$  and substitution for  $v_i$



$$v_o = \frac{R_i}{R_i + R_{sig}} A_{VO} v_{sig} \Rightarrow G_{VO}$$

$$= v_o / v_{sig} = \frac{R_i}{R_i + R_{sig}} A_{VO}$$


Connecting the load

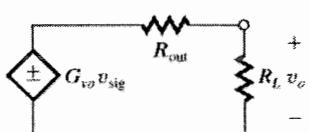


$$v_o = \frac{R_L}{R_L + R_{out}} G_{VO} v_{sig} \Rightarrow G_V = v_o / v_{sig}$$

$$= \frac{R_L}{R_L + R_{out}} G_{VO}$$


4.87

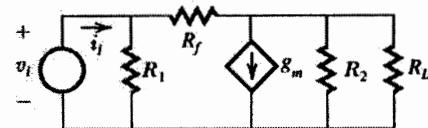

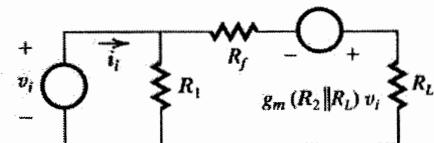
$R_L$  and  $R_L$  are in Parallel. Also do a source transformation



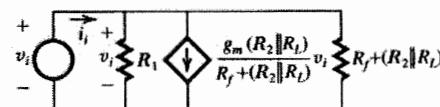Combine  $R_f$  and  $R_2 \parallel R_L$  and do another source transformation



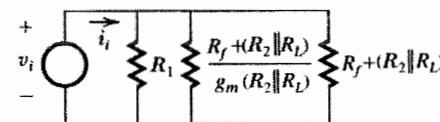The dependent current source is equivalent to a resistor




$$R_{in} = v_i / i_1 = R_1 \parallel \frac{R_f + (R_2 \parallel R_L)}{g_m (R_2 \parallel R_L)} \parallel (R_f + [R_2 \parallel R_L])$$


Consider the form

$$(R/e) \parallel R : \frac{RR}{A/a + R} = \frac{R}{1+a}$$

$$R_{in} = R_1 \parallel \left[ \frac{R_f + (R_2 \parallel R_L)}{1 + g_m (R_2 \parallel R_L)} \right]$$

The circuit for  $A_{vo}$  is

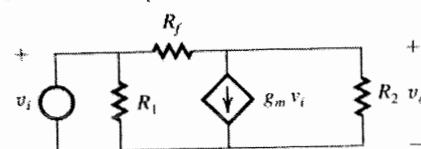

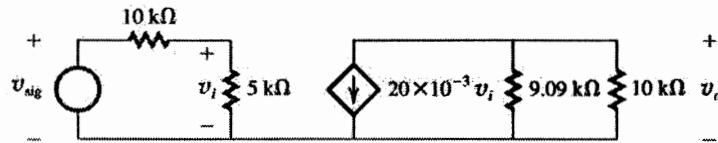


4 . 88

$$\frac{v_o - v_i}{R_f} + g_m v_i + \frac{1}{R_2} v_o$$

$$\left[ \frac{1}{R_f} + \frac{1}{R_2} \right] V_o = \left( \frac{1}{R_f} - g_m \right) v_i$$

$$A_{vo} = v_o / v_i = \frac{1 - g_m R_f}{1 + R_f / R_2}$$

The circuit for  $R_o$

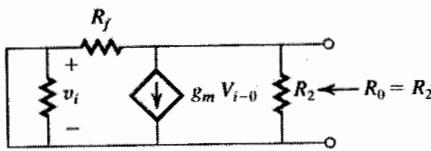

for values given

$$R_{in} = 99.90, A_{vo} = -9.9989, R_o = 100$$

The dependence on  $R_f$  is

$$R_{in} = 100 \frac{1100 R_f + 10^5}{1100 R_f + 1.21 \times 10^6}$$

$$A_{vo} = -10 \left( \frac{R_f - 10}{R_f + 100} \right)$$

If  $R_f$  decreases the gain becomes sensitive to  $R_f$

$$\text{If } R_f \rightarrow \infty, R_{in} = 100, A_{vo} = -10$$

with  $R_f$

$$G_{vo} = \frac{R_{in}}{R_{in} + R_{avg}} A_{vo} = \frac{-99.9}{99.9 + 100} (-9.9989) \\ = -4.997 \text{ V/V}$$

Without  $R_f$

$$G_{vo} = \left( \frac{100}{100 + 100} \right) (-10) = -5$$

$$R_C = 10 \text{ k}\Omega, V_A = 50 \text{ V}, \beta = 100, I_C = 0.5 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.5 \times 10^{-3}}{0.025} = 20 \times 10^{-3} \text{ S}$$

$$r_o = \frac{V_A}{I_A} = \frac{50}{0.5 \times 10^{-3}} = 100 \text{ k}\Omega$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{20 \times 10^{-3}} = 5 \times 10^3 \Omega$$

$$R_o = R_C \parallel r_o = (10 \times 10^3 \parallel 100 \times 10^3) \\ = 9.09 \text{ k}\Omega$$

$$R_{in} = r_\pi = 5 \times 10^3$$

The circuit is now (see figure above)

$$A_v = \frac{v_o}{v_i} = -g_m (R_o \parallel R_L) \\ = -(20 \times 10^{-3}) (9.09 \times 10^3 \parallel 10 \times 10^3) \\ A_v = -95.23$$

$$G_V = v_o / v_{sig} = \frac{R_{in}}{R_{in} + R_{sig}}$$

$$A_V = \left( \frac{5 \times 10^3}{5 \times 10^3 + 10 \times 10^3} \right) (-95.2) = -31.74$$

max signal  $v_{sig}$  is

$$\max \frac{|v_o(t)|}{|G_V|} = \frac{5 \times 10^{-3}}{31.74} = 157.5 \mu\text{V}$$

4 . 89

$$|G_V| = \beta \frac{R_C \parallel R_L \parallel r_o}{R_{sig} + r_\pi}$$

IF  $r_o \rightarrow \infty$  then  $R_C \parallel R_L \parallel r_o \rightarrow R_C \parallel R_L$

Let  $R_L' = R_C \parallel R_L$

$$|G_V| = \beta \frac{R_L'}{R_{sig} + r_\pi}$$

$$|G_V| = \frac{R_L'}{\frac{R_{sig}}{\beta} + \frac{r_\pi}{\beta}}$$

But  $r_\pi/\beta = 1/g_m$

$$|G_V| = \frac{R_L'}{\frac{R_{sig}}{\beta} + \frac{r_\pi}{g_m}}$$

$$R_L' = 10 \text{ k}\Omega; R_{sig} = 10 \text{ k}\Omega; \beta = 100; \\ I_C = 1 \text{ mA}$$

$$g_m = I_c V_p \text{ so} \\ |G_V| = \frac{R_L'}{\frac{R_{sig}}{\beta} + \frac{V_T}{I_c}}$$

$$\text{a) } |G_V| = \frac{10^4}{\frac{10^4}{100} + \frac{0.025}{10^{-3}}} = 80 \text{ V/V}$$

b) If  $\beta$  ranges from 50 → 150

For  $\beta = 50$ :

$$|G_V| = \frac{10^4}{\frac{10^4}{50} + \frac{0.025}{10^{-3}}} = 44.44 \text{ V/V}$$

For  $\beta = 150$ :

$$|G_V| = \frac{10^4}{\frac{10^4}{150} + \frac{0.025}{10^{-3}}} = 109.09 \text{ V/V}$$

c) What is  $\beta$  range if  $|G_V| \leq 96$

at  $|G_V| = 64$ :

$$\frac{10^4}{\frac{10^4}{\beta} + \frac{0.025}{10^{-3}}} = 64 \Rightarrow \beta = 76.19$$

at  $|G_V| = 96$ :

$$\frac{10^4}{\frac{10^4}{\beta} + \frac{0.025}{10^{-3}}} = 96 \Rightarrow \beta = 126.32$$

d) Suppose the nominal  $G_V$  is  $G_{V-nom}$ , and  $I_c$  is variable

$$\beta = 50 \Rightarrow G_V = 0.8 G_{V-nom}$$

$$\beta = 150 \Rightarrow G_V = 1.2 G_{V-nom}$$

Then

$$\frac{10^4}{\frac{10^4}{50} + \frac{0.025}{I_c}} = 0.8 G_{V-nom}$$

$$\frac{10^4}{\frac{10^4}{150} + \frac{0.025}{I_c}} = 1.2 G_{V-nom}$$

Take ratio

$$\frac{\frac{10^4}{\frac{10^4}{50} + \frac{0.025}{I_c}}}{\frac{10^4}{\frac{10^4}{150} + \frac{0.025}{I_c}}} = \frac{0.8}{1.2} \Rightarrow I_c = 0.125 \text{ mA}$$

$$\frac{\frac{10^4}{\frac{10^4}{\beta_{nom}} + \frac{0.025}{I_c}}}{\frac{10^4}{\beta_{nom}} + \frac{0.025}{I_c}} = G_{V-nom} \\ G_{V-nom} = 31.25 \beta_{nom} = 83.33$$

4.90

$$|G_V| = \beta \frac{R_C \parallel R_L \parallel r_o}{R_{sig} + r_\pi} = \beta \frac{(R_C \parallel R_L) \parallel r_o}{R_{sig} + r_\pi}$$

$$r_o = \frac{V_A}{I_c}$$

$$|G_V| = \frac{(R_C \parallel R_L) \parallel \frac{V_A}{I_c}}{\frac{R_{sig}}{\beta} + \frac{r_\pi}{\beta}};$$

$$\frac{r_\pi}{\beta} = \frac{1}{g_m} = \frac{V_T}{I_c}$$

$$\text{thus, } |G_V| = \frac{(R_C \parallel R_L) \parallel \frac{V_A}{I_c}}{\frac{R_{sig}}{\beta} + \frac{V_T}{I_c}}$$

$R_C \parallel R_L = 10 \Omega$ ,  $R_{sig} = 10 \text{ k}\Omega$ ,  $V_A = 25 \text{ V}$ ,  
and  $V_T = 0.025 \text{ V}$

$$|G_V| = \frac{\frac{(10^4) \parallel 25 / I_c}{10^4 + \frac{0.025}{I_c}}}{(10^4 I_c + 25)(10^4 I_c + 2.5)}$$


$I_c (\text{ref})$	$ G_V $
0.1	27.47
0.2	41.15
0.5	55.56
1.0	57.14
1.25	55.55

The values of  $I_c$  that result in  $|G_V| = 50$  are :

$1 \times 0.925 \text{ mA}$  and  $0.324 \text{ mA}$ .

The  $0.324 \text{ mA}$  would be preferred since a lower power is required.

4.91

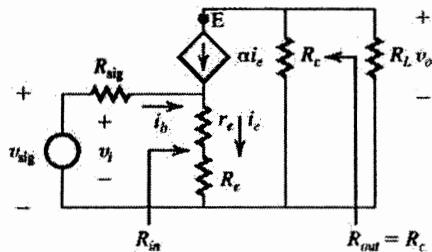

$$i_e = v_i / (r_e + R_e)$$

$$i_b = i_e - \alpha i_e = (1 - \alpha) i_e = (1 - \alpha) \frac{v_i}{r_e + R_e}$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{100 + 1} = 0.99$$

$$i_b = \frac{1}{(\beta + 1)} \frac{v_i}{r_e + R_e}$$

$$R_{in} = v_i / i_b = (\beta + 1)(r_e + R_e)$$

$$r_e = \frac{V_T}{I_E} = \frac{V_T}{I_C / \alpha} = \alpha \frac{V_T}{I_C}$$


$$= (0.99) \left( \frac{0.025}{0.5 \times 10^{-3}} \right) = 49.5 \Omega$$

$$R_{in} = (100 + 1)(49.5 + 150) = 20150 \Omega$$

$$A_{VO} = -\alpha i_e R_C = -\alpha R_C \frac{1}{r_e + R_e}$$

$$A_{VO} = -(0.99)(10 \times 10^3) / (49.5 + 150) = -49.62$$

now model becomes

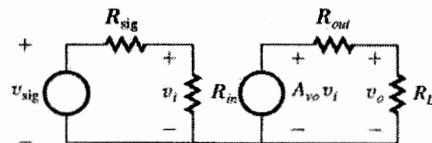

$$v_o = \frac{R_L}{R_L + R_{out}} A_{VO} v_i$$


$$v_o = \frac{R_L}{R_L + R_{out}} A_{VO} \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$$

$$G_V = v_o / v_{sig}$$

$$= \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 10 \text{ k}\Omega} (-49.62) \frac{20150 \Omega}{20150 \Omega + 10000 \Omega}$$

$$= -16.582$$

4.92

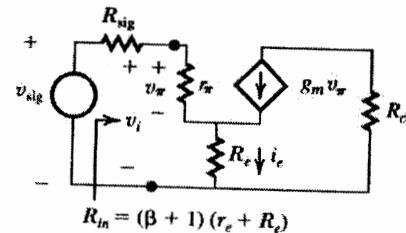

$$R_{in} = (\beta + 1)(r_e + R_e)$$

$$r_e = \frac{V_T}{I_C}$$

$$R_{in} = (\beta + 1) \left( \frac{V_T}{I_C} + R_e \right) \text{ multiply both sides}$$

by  $I_C$  and rearrange :

$$-(\beta + 1)R_e I_C + R_{in} I_C = (\beta + 1)V_T$$

Given  $\beta = 100$ ;  $R_e = 20 \text{ k}\Omega$ ;  $V_T = 0.025 \text{ V}$

Equation becomes

$$-101 R_e I_C + (2 \times 10^4) I_C = (101)(0.025) = 2.525 \text{ (Eq A)}$$

Our unknowns are  $I_C$  &  $R$ . This is one equation.

$$i_e = v_{pi} / r_{pi} + g_m v_{pi} = (1 / r_{pi} + g_m) v_{pi}$$

$$= \left( \frac{1}{\beta} + 1 \right) g_m v_{pi}$$

$$= \left( \frac{1}{\beta} + 1 \right) \frac{I_C}{V_T} v_{pi}$$

$$v_{sig} = R_e i_e + v_{pi} + R_{sig} \frac{v_{pi}}{r_{pi}}$$

$$= R_e \left( \frac{1}{\beta} + 1 \right) \frac{I_C}{V_T} v_{pi} + v_{pi} + \frac{R_{sig}}{\beta} \frac{I_C}{V_T} v_{pi}$$

$$v_{sig} - v_{sig} = \left[ \frac{1}{\beta} + 1 \right] \frac{v_{pi}}{V_T} R_e I_C + \frac{R_{sig} v_{pi}}{\beta V_T} I_C$$

$$0.1 - 0.005 = \left[ \frac{1}{100} + 1 \right] \left[ \frac{5 \times 10^{-3}}{0.025} \right] \bullet$$

$$R_e I_C + \frac{(5000)(5 \times 10^{-3})}{(100)(0.025)} I_C$$

$$0.005 = 0.202 R_e I_C + 10 I_C \text{ (Eq B)}$$

4 . 94

Equations A and B can be solved simultaneously

$$I_c = 1.25 \text{ mA}$$

$$R_e I_C = 0.00064$$

$$\Rightarrow R_e = 0.22264 / 1.25 \times 10^{-3} \\ = 178.11$$

$$G_V = \frac{v_o}{v_{\text{sig}}} = \frac{v_o}{v_\pi} \cdot \frac{v_\pi}{v_{\text{sig}}}$$

$$v_o / v_\pi = -R_C g_m = -R_C \frac{I_C}{V_T}$$

$$= -(5 \times 10^3) \left( \frac{1.25 \times 10^{-3}}{0.025} \right) = -250$$

$$G_V = (-250) \left( \frac{5 \times 10^{-3}}{0.1} \right) = -12.5$$

4 . 93

$$|G_V| = \frac{\beta R_C}{R_{\text{sig}} + (\beta + 1)(r_e + R_e)}$$

$$r_e = \frac{V_T}{I_E}$$

$$|G_V| = \frac{\beta R_C}{R_{\text{sig}} + (\beta + 1)(V_T / I_E + R_e)}$$

$$R_{\text{sig}} = 10 \text{ k}\Omega; R_e = 10 \text{ k}\Omega; \beta = 100;$$

$$V_T = 0.025 \text{ V};$$

$$I = 1 \text{ mA}$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.99$$

$$I_E = I / \alpha = 1.01 \times 10^{-3} \text{ A}$$

$$\text{If } R_e = 0$$

$$|G_V| = \frac{(100)(10 \times 10^3)}{10 \times 10^3 + (101)[0.025 / (1.01 \times 10^{-3})]} = 80$$

Suppose  $|G_V|$  has a nominal value  $G_{V-\text{nom}}$  and

0.8  $G_{V-\text{nom}}$  corresponds to  $\beta = 50$ . Let  $R_e$  be a variable (note that  $\alpha = 0.98$ ):

$$\frac{\beta R_C}{R_{\text{sig}} + (\beta + 1)[0.025 / (1.02 \times 10^{-3}) + R_e]}$$

$$= 0.8 G_{V-\text{nom}}$$

$$\frac{(50)(10^4)}{10^4 + (51)(0.025 / 1.02 \times 10^{-3} + R_e)} = 0.8 G_{V-\text{nom}}$$


$$\text{at } \beta = 150 \quad G_v = 1.2 G_{V-\text{nom}}$$

$$\frac{(150)(10^4)}{10^4 + (151)(0.025 / 1.01 \times 10^{-3} + R_e)} = 1.2 G_{V-\text{nom}}$$

These two equations can be solved simultaneously for  $R_e$  &  $G_{V-\text{nom}}$

$$R_e = 179.3 \text{ V}$$

$$G_{V-\text{nom}} = -30.625$$

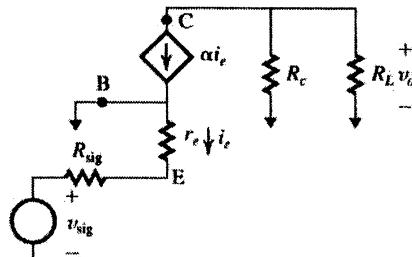

$$v_{be}(t) = r_e i_e$$

$$v_o(t) = -\alpha i_e (R_C \parallel R_L)$$

$$v_{be}(t) = -r_e \frac{v_o(t)}{\alpha (R_C \parallel R_L)}$$

$$|v_o(t)| = \frac{\alpha (R_C \parallel R_L)}{r_e} |v_{be}(t)|$$

$$= \frac{\alpha (R_C \parallel R_L)}{V_T} I_E |v_{be}(t)|$$

Suppose  $\alpha \approx 1$

$$|v_o(t)| = \frac{(10 \text{ k}\Omega) \parallel (10 \text{ k}\Omega)}{0.025} (0.25 \text{ mA})(10 \times 10^{-3})$$

$$|v_o(t)| = 0.5 \text{ V}$$

$$G_V = v_o(t) / v_{\text{sig}(t)} = \alpha \frac{R_C \parallel R_L}{R_{\text{sig}} + r_e} = \alpha \frac{R_C \parallel R_L}{R_{\text{sig}} + V_T / I_E}$$

$$G_V = \frac{(10 \text{ k}\Omega) \parallel (10 \text{ k}\Omega)}{1 \text{ k}\Omega + 0.025 / 10^{-3}} \text{ Since } \alpha \approx 1 \\ = 4.88 \text{ V/V}$$

$$|v_{\text{sig}}(t)| = |v_o(t)| / G_V$$

$$|v_{\text{sig}}(t)| = 0.5 / 4.88 = 0.1025 \text{ V}$$

4 . 95

$$|v_o(t)|_{\text{max}} = (0.5 \text{ V})$$

$$|i_c(t)|_{\text{max}} = \frac{|v_o(t)|_{\text{max}}}{R_L} = \frac{0.5}{2 \times 10^3} = 250 \mu\text{A}$$

$$r_e = \frac{|v_{be}(t)|_{\text{max}}}{|i_c(t)|_{\text{max}}} = \frac{5 \times 10^{-3}}{250 \mu\text{A}} = 20 \Omega$$

$$r_e = \frac{V_T}{I_E} \Rightarrow I_E = \frac{V_T}{r_e} = \frac{0.025}{20} = 1.2 \text{ mA}$$

$$|i_E(t)|_{\text{max}} = I_E + |i_c(t)|_{\text{max}} = 1.5 \text{ mA}$$

$$|i_E(t)|_{\text{max}} = I_E - |i_c(t)|_{\text{max}} = 1 \text{ mA}$$

Suppose  $\beta = 100$

$$G_V = \frac{(\beta + 1) R_L}{(\beta + 1) R_L + (\beta + 1) r_e + R_{\text{sig}}}$$

$$= \frac{(101)(2 \times 10^3)}{(101)(2 \times 10^3) + (101)(20) + 200 \times 10^3} = 0.499$$

$$(G_V = v_o(t) / v_{sig}(t)) \Rightarrow$$

$$v_{sig}(t) = \frac{v_o(t)}{G_V} = \frac{0.5}{0.499}$$

$$|V_{sig}|_{max} = 1.00 \text{ Volt}$$

4 . 96

$$I_C = 1 \text{ mA}; \beta = 100; R_{sig} = 20 \text{ k}\Omega; R_L = 1000 \Omega$$


$$I_E = \frac{\beta + 1}{\beta} I_C = \frac{101}{100} 10^{-3} = 1.01 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{0.025}{1.01 \times 10^{-3}} = 24.752 \Omega$$

$$R_{in} = (\beta + 1)(r_e + R_L) = (101)(24.752 + 1000) = 103.5 \text{ k}\Omega$$

we have:
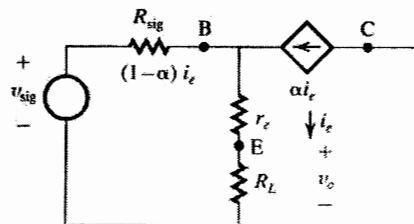
$$\begin{aligned} v_o / v_{sig} &= G_V = \frac{(\beta + 1)R_L}{(\beta + 1)R_L + (\beta + 1)r_e + R_{sig}} \\ &= \frac{(101)(1000)}{(101)(1000) + (101)(24.752) + 20 \times 10^3} = 0.8178 \end{aligned}$$



$$i_C(t) = v_o(t) / R_L = \frac{G_V V_{sig}}{R_L}$$

$$V_{be}(t) = r_e i_e(t) = (r_e / R_L) G_V V_{sig}(t) \Rightarrow$$

$$v_{be}(t) / v_{sig}(t) = (r_e / R_L) G_V$$

$$= (24.752 / 1000)(0.8178) = 0.02024$$

$$v_b(t) = v_o(t) + v_{be}(t) \Rightarrow$$

$$v_b(t) / v_{sig}(t) = G_V + (r_e / R_L) G_V = (1 + r_e / R_L) G_V$$

$$v_b(t) / v_{sig}(t) = (1 + 24.752 / 1000)(0.8178)$$

$$= 0.838056$$

$$\text{b) } v_{be}(t) / v_{sig}(t) = 0.02024$$

$$\Rightarrow |v_{sig}(t)|_{max}$$

$$= |v_{be}(t)|_{max} / 0.02024$$

$$|v_{sig}(t)|_{max} = 10 \times 10^{-3} / 0.02024 = 0.494 V_{old}$$

$$|v_o(t)|_{max} = G_V |v_{sig}(t)|_{max} = (0.494)(0.8178)$$


$$= 0.404 \text{ V}$$

c) If  $R_L$  is removed  $i_e = 0$ , therefore,

$$v_e = v_{ao} \text{ Thus}$$

$$G_m = 1.$$

Now for  $R_{out}$

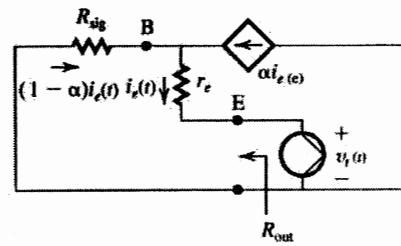

$$R_{out} = -\frac{v_o(t)}{i_C(t)}$$

$$i_e(t) = \frac{v_b(t) - v_e(t)}{r_e} = \frac{v_b(t) - v_i(t)}{r_e}$$

$$v_b(t) = -i_e(t)(1 - \alpha)R_{sig} \Rightarrow$$

$$i_e(t) = \frac{-i_e(t)(1 - \alpha)R_{sig} - v_i(t)}{r_e};$$


$$r_e i_e(t) = -i_e(1 - \alpha)R_{sig} - v_i(t)$$

$$i_e(t) = \frac{-v_i}{r_e + (1 - \alpha)R_{sig}}$$

Substituting into  $R_{out}$  expression

$$\begin{aligned} R_{out} &= r_e + (1 - \alpha) R_{sig} = r_e + \frac{1}{\beta + 1} R_{sig} \\ &= 24.752 + \frac{20 \times 10^3}{101} = 222.772 \end{aligned}$$

now

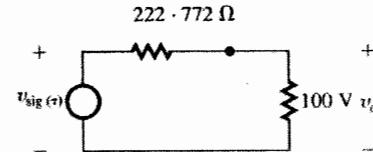

$$v_o(t) / v_{sig}(t) = \frac{1000}{1000 + 222.772} = 0.8178$$

This agrees with  $G_V$ .

4 . 97

$$I_C = 0.25 \text{ mA}; R_{sig} = 10 \text{ k}\Omega; R_L = 1 \text{ k}\Omega; V_T = 0.025$$

$$G_V = \frac{(\beta + 1) R_L}{(\beta + 1) R_L + (\beta + 1) r_e + R_{sig}}$$

$$r_e = \frac{V_T}{I_E} = \frac{\beta V_T}{(\beta + 1) I_C}$$

$$G_V = \frac{(\beta + 1) R_L}{(\beta + 1) R_L + \beta V_T / I_C + R_{sig}}$$


$$R_{out} = r_e + R_{sig} / (\beta + 1)$$

$$= \frac{\beta V_T}{(\beta + 1) I_C} + \frac{R_{sig}}{\beta + 1}$$

for  $\beta = 100$        $\beta = 50$        $\beta = 150$   
 $G_v = 0.8347$      $G_v = 0.7727$      $G_v = 0.85$   
 $R_{out} = 199.01 \Omega$      $R_{out} = 298.0 \Omega$      $R_{out} = 166.0 \Omega$

4.98

Part a) Nodal equations:

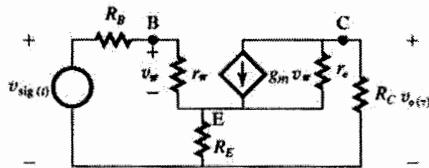

Part a)

$$\frac{v_e}{R_E} + \frac{v_e - v_{sig}}{R_B + r_\pi} - g_m V_\pi + \frac{v_e - v_c}{r_o} = 0$$

$$g_m v_\pi + \frac{v_c - v_e}{r_o} + \frac{v_e}{R_C} = 0$$

$$\frac{v_\pi}{r_\pi} + \frac{v_e + v_\pi - v_{sig}}{R_B} = 0$$


Solving:

$$\frac{v_e(t)}{v_{sig}(t)} = \frac{(g_m r_o r_\pi - R_E) R_C}{(r_\pi R_C + R_E r_\pi + r_o r_\pi + g_m R_E r_o r_\pi + R_C R_B + R_E r_o + r_o R_B + R_E R_C + R_E R_B)}$$

$$\frac{v_e(t)}{v_{sig}(t)} = \frac{R_E (g_m r_o r_\pi + R_C + r_o)}{(r_\pi R_C + R_E r_\pi + r_o r_\pi + g_m R_E r_o r_\pi + R_C R_B + R_E r_o + r_o R_B + R_E R_C + R_E R_B)}$$

$$r_o = \frac{|V_A|}{I_C}$$

Part b) Nodal equations:

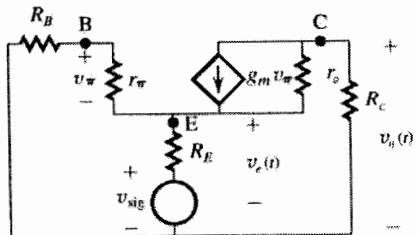

$$\frac{v_e - v_{sig}}{R_E} + \frac{v_e}{R_B + r_\pi} - g_m v_\pi + \frac{v_e - v_c}{r_o} = 0$$

$$g_m v_\pi + \frac{v_c - v_e}{r_o} + \frac{v_e}{R_C} = 0$$

$$\frac{v_\pi}{r_\pi} + \frac{v_e + v_\pi}{R_B} = 0$$

Solutions

$$\frac{V_e(t)}{V_{sig}(t)} = \frac{R_C(g_m r_o r_\pi + R_B + r_\pi)}{(r_\pi R_C + R_E r_\pi + r_o r_\pi + g_m R_E r_o r_\pi + R_C R_B + R_E r_o + r_o R_B + R_E R_C + R_E R_B)}$$

$$\frac{V_e(t)}{V_{sig}(t)} = \frac{(R_C + r_o)(R_B + r_\pi)}{(r_\pi R_C + R_E r_\pi + r_o r_\pi + g_m R_E r_o r_\pi + R_C R_B + R_E r_o + r_o R_B + R_E R_C + R_E R_B)}$$

4.99

$$\begin{aligned} \textcircled{1} \quad & \frac{5}{R_B1 + R_B2} = 0.690 \\ \textcircled{2} \quad & 5 R_B2 = 0.69 R_B1 + 0.69 R_B2 \\ & \rightarrow 4.31 R_B2 = 0.69 R_B1 \\ & \Rightarrow \frac{R_B1}{R_B2} = \underline{\underline{6.24}} \end{aligned}$$

② Since  $V_{BE} = \frac{5 R_B2}{R_B1 + R_B2}$

If both  $R_B2$  &  $R_B1$  are at 0.99 or 1.01 of their nominal value  $\rightarrow V_{BE}$  will not be affected.

We must consider the cases when one resistor is at 0.99 and the other at 1.01 of their nominal value.

$$\begin{aligned} \text{If: } R_B2' &= 1.01 R_B2 \\ R_B1' &= 0.99 R_B1 \end{aligned}$$

$$\Rightarrow V_{BE} = 0.702 \text{ V}$$

$$\begin{aligned} \text{If: } R_B2' &= 0.99 R_B2 \\ R_B1' &= 1.01 R_B1 \end{aligned}$$

$$\Rightarrow V_{BE} = 0.678 \text{ V}$$

thus  $V_{BE}$  ranges from 0.678V to 0.702V

CONT.

For  $I_C$ :  $I_C = I_S e^{V_{BE}/V_T}$   
for  $V_{BE} = 0.690 \rightarrow I_C = 1\text{mA}$   
 $\Rightarrow I_S = 1.032 \times 10^{-15}$

for  $V_{BE} = 0.678 \rightarrow I_C = 0.618\text{mA}$   
 $V_{BE} = 0.702 \rightarrow I_C = 1.62\text{mA}$

$I_C$  ranges from  $0.618\text{mA}$  to  $1.62\text{mA}$ .

③ If  $R_C = 3\text{k}\Omega$

$$V_{CE} = 5 - 3\text{k} \times 0.62\text{mA} = 3.14\text{V}$$

$$V_{CE} = 5 - 3\text{k} \times 1.62\text{mA} = 0.14\text{V}$$

This circuit is too sensitive to parameter variations as shown here for a 1% resistor tolerance.

4.100

$R_B = ? \text{ if } \beta = 100$

$$I_B \times \beta = I_C$$

$$\frac{5 - 0.7}{R_B} = \frac{1\text{mA}}{100}$$

$$\rightarrow R_B = \underline{\underline{430\text{k}\Omega}}$$

$$V_{CE} = 5\text{V} - 3\text{k} \times 1\text{mA} = 2\text{V}$$

If  $\beta = 50$ :  $I_C = \frac{5 - 0.7}{430\text{k}} \times 50$


$$I_C = 0.5\text{mA}$$

$$\Rightarrow V_{CE} = 5 - 3\text{k} \times 0.5\text{mA} = +3.5\text{V}$$

If  $\beta = 150$ :  $I_C = 1.5\text{mA}$   
 $V_{CE} = 0.5\text{V}$

This design is too sensitive to variations of  $\beta$ .

4.101

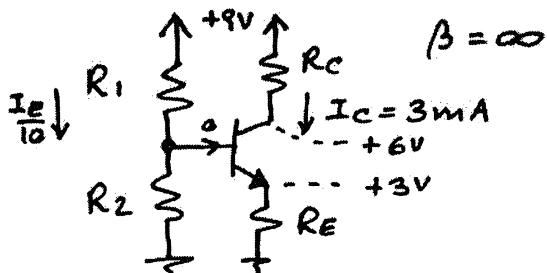

$$R_C = \frac{3\text{V}}{3\text{mA}} = 1\text{k}\Omega$$

$$R_E = \frac{3\text{V}}{3\text{mA}} = 1\text{k}\Omega$$

$$V_b = 0.7 + 3 = 3.7\text{V}$$

$$R_1 = \frac{9 - 3.7}{I_E/10} = 17.7\text{k}\Omega$$

$$9\text{V} = (R_1 + R_2) \frac{I_E}{10} \rightarrow R_2 = 12.3\text{k}\Omega$$

Choose suitable 5% resistors

$$R_1 = 17.7\text{k} \rightarrow 18\text{k}\Omega$$

$$R_2 = 12.3\text{k} \rightarrow 13\text{k}\Omega$$

$$R_1 = R_2 = 1\text{k}$$

$$V_{BB} = \frac{9 \times 13}{18 + 13} = 3.77\text{V}$$

For these values of  $R$  and  $\beta = 90$ :  $R_B = 18/13 = 7.55\text{k}\Omega$

$$I_E = \frac{3.77 - 0.7}{1\text{k} + 7.55\text{k}} = 2.83\text{mA}$$

$$\alpha = 0.989 \Rightarrow I_C = 2.80\text{mA}$$

If  $R_E$  is reduced by  $\sim \frac{7.55\text{k}}{9.1}$

$$\rightarrow R_E = 910\Omega$$

$$\Rightarrow I_E = 3.09\text{mA}$$

$$I_C = 3.05\text{mA}$$

4.102

For  $\beta = \infty$ ,  $I_B = 0$ ,  $I_E = 0.6 \text{ mA}$ 

$$R_c = \frac{3 \text{ V}}{0.6 \text{ mA}} = 5 \text{ k}\Omega = R_E$$

$$V_b = 0.7 + 3 = 3.7$$

$$R_1 = \frac{9 - 3.7}{I_E/2} = \frac{10.6}{.6 \text{ mA}} = 17.7 \text{ k}\Omega$$

$$9 = (R_2 + R_1) \frac{I_E}{2} \Rightarrow R_2 = \frac{18}{I_E} - R_1 = 12.3 \text{ k}\Omega$$

Suitable 5% Resistors:  $R_1 = 17.4 \text{ k}\Omega$ 

$$R_2 = 12.1 \text{ k}\Omega$$

 $\beta = 90$ :

$$R_B = (17.4 \text{ K}) \parallel (12.1 \text{ K}) = \frac{17.4 \text{ K}(12.1 \text{ K})}{29500} = 7.137 \text{ }\Omega$$

$$V_{BB} = \frac{9(12.1 \text{ K})}{12.1 \text{ K} + 17.4 \text{ K}} = 3.7 \text{ V}$$

$$I_E = \frac{3.7 - 0.7}{5 \text{ K} + \frac{7137}{(90+1)}} = \frac{3}{5 \text{ K} + 78.4} = .6 \text{ mA}$$

4.103

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta+1}}$$

(a) For  $\beta = 100$ , varying between 50 and 150 the maximum deviation in  $I_E$  (from the nominal value obtained for  $\beta = 100$ ) occurs at the low end of  $\beta$  values ( $\beta = 50$ ). Thus, to keep

$I_E$  within  $\pm 5\%$  of nominal we must impose the constraint  $I_E(\beta=50) \geq 0.95 I_E(\beta=100)$

$$\text{or, } \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{51}} \geq 0.95 \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{101}}$$

$$\text{or, } R_E + \frac{R_B}{51} \geq 0.95 \left( R_E + \frac{R_B}{101} \right)$$

$$0.05 R_E \geq R_B \left( \frac{0.95}{51} - \frac{1}{101} \right)$$

$$\Rightarrow \frac{R_B}{R_E} \leq 5.73$$

Thus, the largest ratio of  $R_B/R_E$  is 5.73

$$(b) I_E \cdot R_E = V_{CC}/3$$

$$\rightarrow \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta+1}} \cdot R_E = \frac{V_{CC}}{3}$$

$$\frac{V_{BB} - 0.7}{1 + \frac{R_B}{R_E} \cdot \frac{1}{\beta+1}} = \frac{V_{CC}}{3}$$

$$V_{BB} = \frac{1}{3} V_{CC} \left( 1 + \frac{5.73}{101} \right) + 0.7$$

$$\Rightarrow \underline{\underline{V_{BB} = 0.35 V_{CC} + 0.7}}$$

$$(c) V_{CC} = 10 \text{ V}$$

$$V_{BB} = 0.35 \times 10 + 0.7 = 4.2 \text{ V}$$

$$\rightarrow \frac{R_2}{R_1 + R_2} \times 10 = 4.2$$

$$\frac{R_2}{R_1 + R_2} = 0.42 \quad (1)$$

$$I_E \cdot R_E = \frac{1}{3} V_{CC}$$

CONT.

$$2 \times R_E = \frac{1}{3} \times 10$$

$$\Rightarrow R_E = \underline{\underline{1.67 \text{ k}\Omega}}$$


$$R_B = 5.73 \times 1.67 = 9.55 \text{ k}\Omega$$

$$\frac{R_1 \cdot R_2}{R_1 + R_2} = 9.55$$

Substituting from ① gives

$$R_1 = \frac{9.55}{0.42} = \underline{\underline{22.7 \text{ k}\Omega}}$$

4.104

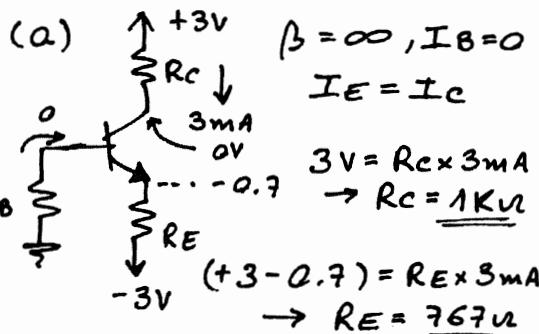

(b)  $\beta = 90$   $\frac{V_{RE}}{10} = V_{RB}$

$$I_B \cdot R_B = \frac{I_E \cdot R_E}{10}$$

$$\rightarrow \frac{I_E}{(\beta+1)} \cdot R_B = \frac{I_E \cdot R_E}{10}$$

$$\rightarrow R_B = \frac{(\beta+1)}{10} R_E \quad \textcircled{1}$$

also,  $0 = V_{RB} + 0.7 + V_{RE} - 3$

$$2.3 = \frac{V_{RE}}{10} + V_{RE}$$

$$\rightarrow V_{RE} = \frac{2.3}{1.1} = 2.09V$$

$$2.09 = I_E \times R_E \quad \textcircled{2}$$

$$\text{but: } I_E = \frac{I_C}{\alpha} = \frac{3 \text{ mA}}{0.989} = 3.033 \text{ mA}$$

Substituting in ②:

$$R_E = 689 \text{ }\mu\Omega$$

from ①:

$$R_B = \underline{\underline{6269 \text{ }\mu\Omega}}$$

(c) Standard 5% values:

$$R_C = 1 \text{ k}\Omega$$

$$R_E = 689 \text{ }\mu\Omega \rightarrow 680 \text{ }\mu\Omega$$

$$R_B = 6269 \text{ }\mu\Omega \rightarrow 6.2 \text{ k}\Omega$$

(d)  $\beta = \infty: I_B = 0$

$$I_C = I_E$$

$$V_B = 0$$

$$V_E = -0.7$$

$$I_E = \frac{3 - 0.7}{R_E} = \frac{3 - 0.7}{680} = \underline{\underline{3.38 \text{ mA}}}$$

$$V_C = 3 - 3.38 \text{ mA} \times 1 \text{ k}\Omega = \underline{\underline{-0.38V}}$$

For  $\beta = 90:$

$$I_E = \frac{2.3}{680 + 6.2 \text{ k}} = \frac{2.3}{91} = \underline{\underline{3.07 \text{ mA}}}$$

$$I_C = \alpha I_E = \underline{\underline{3.04 \text{ mA}}}$$

$$V_B = R_B \cdot I_E = \frac{R_B \cdot I_E}{\beta+1} = -0.209$$

$$V_E = -0.209 - 0.7 = \underline{\underline{0.909V}}$$

$$V_C = 3 - I_C \cdot R_C = 3 - 3.04 \times 1 = \underline{\underline{-0.04V}}$$


4.105

$$V_E = -0.7V$$

To obtain  $I_E = 1 \text{ mA}$

$$R_E = \frac{-0.7 - (-5)}{1} = 4.3 \text{ k}\Omega$$

$$= 4.3 \text{ k}\Omega$$

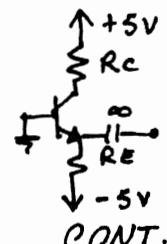

CONT.

To maximize gain while allowing  $\pm 1V$  signal at collector, design for a dc collector voltage of  $+1V$ .

Thus,

$$R_C = \frac{5-1}{I_C} \approx \frac{4}{1} = \underline{\underline{4\text{ k}\Omega}} \quad (\alpha=1)$$

For  $100^\circ\text{C}$  rise in temperature,  $V_{BE}$  decreases by

$2 \times 100 = 200\text{mV}$  and thus  $I_E$  increases by  $\frac{0.2V}{R_E}$

$$= \frac{0.2V}{4.3\text{k}\Omega} = 0.047\text{ mA}$$

i.e. an increase of  $\underline{\underline{4.7\%}}$

The change in  $\beta$  from 50 to 150 causes  $\alpha$  to change from 0.980 to 0.993 which implies an increase in collector current of  $\underline{\underline{1.3\%}}$ . Thus the overall increase in  $I_C$  is  $\underline{\underline{6\%}}$

4.106

To allow a collector voltage swing of  $\pm 1V$ , we design for:

$$V_C = V_B + 1 \\ = 0.7 + 1 = 1.7V$$

$$I_E = 0.5\text{ mA}$$

$$\rightarrow R_C = \frac{5-1.7}{0.5} = \underline{\underline{6.6\text{ k}\Omega}}$$

For  $\beta = 100$ :

$$I_B = \frac{I_E}{\beta+1} = \frac{0.5}{101} \approx 5\mu\text{A}$$

$$I_B \cdot R_B = 1V$$

$$R_B = \frac{1V}{5\mu\text{A}} = \frac{1}{5} \text{ M}\Omega = \underline{\underline{200\text{ k}\Omega}}$$

Now, if the BJT used has  $\beta = 50$ , the emitter current resulting can be found from Eq (5.44)

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + R_B} \cdot \frac{1}{\beta+1} \\ = \frac{5 - 0.7}{6.6 + \frac{200}{51}} = \underline{\underline{0.41\text{ mA}}}$$

$$\text{and } I_B = \frac{0.41}{51} \approx 8\mu\text{A}$$


Thus the collector will be higher than the base by  $8 \times 0.2 = 1.6V$ , allowing for a  $\pm 1.6V$  signal swing at the collector.

For  $\beta = 150$ :

$$I_E = \frac{5 - 0.7}{6.6 + \frac{200}{151}} = 0.54\text{ mA}$$

$$I_B = \frac{0.54}{151} = 36\mu\text{A}$$

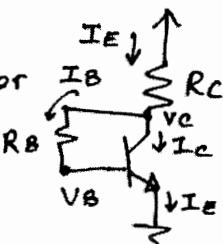Thus the collector voltage will be higher than that of the base by  $3.6 \times 0.2 = 0.72V$  allowing for only  $\pm \underline{\underline{0.72V}}$  signal swing.



4.107

$$I_B = I_C / \beta = 3 \text{ mA} / 90 = 0.033 \text{ mA}$$

$$V_C = R_B \cdot I_B + 0.7$$


$$V_C = 1.5 \text{ V} \rightarrow R_B = \underline{\underline{24.2 \text{ k}\Omega}}$$

$$I_E = \frac{I_C}{\alpha} = \frac{3.03 \text{ mA}}{\alpha}$$


$$I = I_C - I_B \equiv I_E$$

$$I = \underline{\underline{3.03 \text{ mA}}}$$

4.109

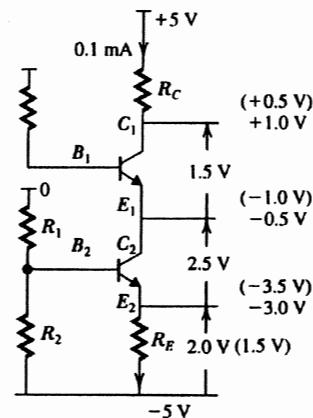

4.108

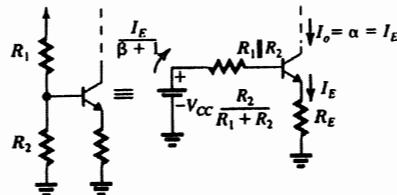

$$V_{CC} \cdot \frac{R_2}{R_1 + R_2} = \frac{I_E}{\beta + 1} (R_1 \parallel R_2) + V_{BE} + I_E R_E$$

$$\Rightarrow I_E = \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE}}{R_E + \frac{(R_1 \parallel R_2)}{\beta + 1}}$$

Thus,

$$I_O = \alpha I_E = \frac{\alpha \cdot \left[ \frac{V_{CC} R_2}{R_1 + R_2} - V_{BE} \right]}{R_E + \frac{(R_1 \parallel R_2)}{\beta + 1}}$$

The constraints imposed cannot be met

$$V_{E1} < -0.7 \text{ V} \text{ for } Q_1 \text{ active.}$$

Change  $V_{RE}$  to 1.5 V then

$$V_{E1} = -3.5 \text{ V}$$

$$V_{C1} = V_{E2} + 2.5 = -1.0 \text{ V}$$

$$V_{G1} = V_{G2} + 1.5 = +0.5 \text{ V}$$

For  $\beta = \infty$

$$R_E = 1.5 \text{ V} / 0.1 \text{ mA} = 15 \text{ k}\Omega$$

$$V_{E1} = -3.5 + 0.7 = -2.8 \text{ V}$$

$$\text{Then } \frac{V_{R1}}{V_{R2}} = \frac{2.8}{2.2} = \frac{R_1}{R_2}$$

$$V_{E1} = 0 \text{ (} I_{B1} = 0 \text{)}$$

$$V_{E1} = -0.7 \text{ V}$$

$$V_{C1} = V_{E1} + 1.5 = +0.8 \text{ V}$$

$$R_{C2} = \frac{V_{CC}}{0.1 \text{ mA}} \cdot 42 \text{ k}\Omega$$

For  $I_{E2}$  ( $\beta = 50$ ) within 5%  $I_{E2}$  ( $\beta = \infty$ )

For  $\beta = 50$

$$I_E = \frac{1.5}{R_E + (R_1 \parallel R_2) / 51}$$

$$\beta = \infty$$

$$I_E = \frac{1.5}{R_E}$$

$$\text{Need } \frac{R_1 \parallel R_2}{51} \leq \frac{5}{100} R_E$$

$$\therefore R_1 \parallel R_2 \leq 51 R_E / 2 = 38.25 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = \frac{R_1}{1 + R_1/R_2} = \frac{R_1}{1 + 28/22} < 38.25 \text{ k}\Omega$$

$$\therefore R_1 < 86.9 \text{ k}\Omega \text{ use } 82 \text{ k}\Omega$$

$$R_2 < 68.3 \text{ k}\Omega \text{ use } 68 \text{ k}\Omega$$

$$R_1 \parallel R_2 = 37 \text{ k}\Omega < 38.25 \text{ k}\Omega$$

For  $\beta = \infty$  and 5% values

$$V_{B2} = \frac{-5 \times R_1}{R_1 + R_2} = -2.73 \text{ V}$$

$$V_{E2} = 2.27 + 0.7 = -1.57 \text{ V}$$

$$I_{E2} = 1.57 / 15 = 0.1046 \text{ mA}$$

For  $\beta = 50$  V determine  $R_s$

$$I_{E2} = \frac{2.27 - 0.7}{37/51 + 15} = 0.0998 \text{ mA}$$

$$I_C = 0.98 \times I_E = 0.098 \text{ mA}$$

$$I_{C1} = 0.98 \times I_{E2} = 0.096 \text{ mA}$$

$$I_B = I_{C1}/50$$

$$V_{BE} = 0.099 \times 15 = 1.47 \text{ V}$$

$$V_{E1} = -5 + V_{BE} = -3.53 \text{ V}$$

For  $V_{CE2} = 2.5 \text{ V}$

$$V_{E1} = V_{C2} = V_E + V_{CE} = -1.03 \text{ V}$$

$$V_{E1} = V_{C1} + 0.7 = -0.33 \text{ V}$$

$$R_B = V_{B1} \times \frac{\beta}{I_{C1}} = 173.7 \text{ k}\Omega \text{ use } 180 \text{ k}\Omega$$

For  $\beta = 50$

$$I_{C1} = 0.096 \text{ mA}$$

$$V_{B1} = -\frac{0.09}{50} \times 180 = -0.35 \text{ V}$$

$$V_{E1} = V_{B1} - 0.7 = -1.05 \text{ V}$$

$$V_{C1} = 5 - 0.096 \times 43 = 0.872 \text{ V}$$

$$V_{CE1} = 1.9 \text{ V}$$

For  $\beta = 100$

$$I_{E2} = \frac{1.57}{37/101 + 15} = 0.102 \text{ mA}$$

$$I_{C1} = 0.99 \times 0.99 \times I_E = 0.10 \text{ mA}$$

$$V_{E1} = 0.7 \text{ V}$$

$$V_{B1} = -\frac{0.10}{101} \times 180 = -0.878 \text{ V}$$

$$V_{E1} = V_{B1} - 0.7 = -0.878 \text{ V}$$

$$V_{CE1} = 0.7 + 0.878 = 1.578 \text{ V}$$

For  $\beta = 200$

$$I_{E2} = \frac{1.57}{37/201 - 15} = 0.103 \text{ mA}$$

$$I_{C1} = 0.995 \times 0.995 \times I_E = 0.102 \text{ mA}$$

$$V_{E1} = 0.615 \text{ V}$$

$$V_{B1} = -\frac{0.102}{201} \times 180 = -0.091 \text{ V}$$

$$V_{E1} = V_{B1} - 0.7 = -0.791 \text{ V}$$

$$V_{CE1} = 1.45 \text{ V}$$

4.110

$$I_O = 2 \text{ mA} = \alpha \times \frac{5 - 0.7}{R} \approx \frac{4.3}{R}$$

$$\Rightarrow R = \underline{\underline{2.15 \text{ k}\Omega}}$$

$$U_{C \min} = \underline{\underline{0 \text{ V}}} \quad (\text{In actual practice, } U_{C \min} \approx 0.4 \text{ V})$$

4.111


$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_B / (\beta + 1)}$$

$$\text{where, } V_{BB} = V_{cc} \cdot \frac{R_2}{R_1 + R_2}$$

$$= 9 \cdot \frac{15}{27+15} = 3.21 \text{ V}$$

$$R_B = R_1 \parallel R_2 = 15/127 = 9.64 \text{ k}\Omega$$
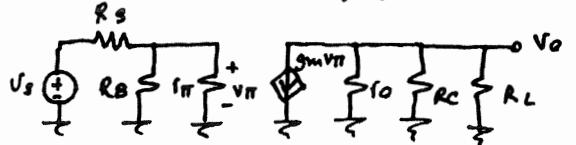
$$\text{Thus, } I_E = \frac{3.21 - 0.7}{1.2 + 9.64} = \underline{\underline{1.94 \text{ mA}}}$$



$$g_m = \frac{I_C}{V_T} = \frac{0.99 \times 1.94}{0.025} = \underline{\underline{76.8 \text{ mA/V}}}$$


$$f_{\pi} = \frac{\beta}{g_m} = \frac{100}{76.8} = 1.3 \text{ k}\Omega$$

$$f_0 = \frac{V_A}{I_C} = \frac{100}{0.99 \times 1.94} = 52.1 \text{ k}\Omega$$

$$R_i = R_B \parallel f_{\pi} = 9.64 \parallel 1.3 = \underline{\underline{1.15 \text{ k}\Omega}}$$

$$G_m = -g_m = -\underline{\underline{76.8 \text{ mA/V}}}$$
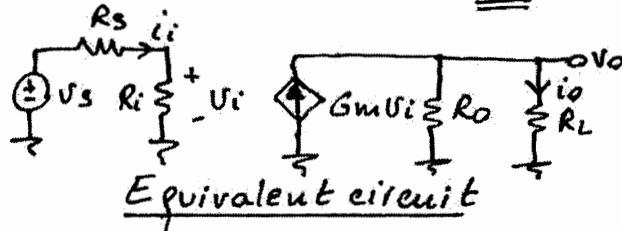
$$R_o = R_c \parallel r_o = 2.2 \parallel 52.1 = \underline{2.11} \text{ k}\Omega$$



$$\begin{aligned} A_v &= \frac{V_o}{V_s} = \frac{V_i}{V_s} \cdot \frac{V_o}{V_i} \\ &= \frac{R_i}{R_s + R_i} \cdot \frac{G_m (R_o \parallel R_L)}{V_i} \\ &= \frac{-1.15}{10+1.15} \times 76.8 \times (2.11 \parallel 2) \\ &= \underline{-8.13} \text{ V/V} \end{aligned}$$

$$A_i = \frac{i_o}{i_i} = \frac{V_o \cdot R_L}{V_s (R_s + R_i)}$$

$$\begin{aligned} \rightarrow A_i &= \frac{V_o}{V_s} \cdot \frac{R_s + R_i}{R_L} \\ &= -8.13 \times \frac{(10 + 1.15)}{2} \\ &= \underline{-45.3} \text{ A/A} \end{aligned}$$

4.112

$$V_{CC} = 9V \quad V_{BB} = \frac{1}{3} V_{CC} = 3V$$

Neglecting the base current,  
 $R_1 + R_2 = \frac{9}{0.2} = 45 \text{ k}\Omega$

$$\frac{R_2}{R_1 + R_2} = \frac{1}{3}$$

$$\begin{aligned} \Rightarrow R_2 &= \underline{15 \text{ k}\Omega}, \quad R_1 = \underline{30 \text{ k}\Omega} \\ R_B &= R_1 \parallel R_2 = \frac{30 \times 15}{45} = 10 \text{ k}\Omega \end{aligned}$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_B}$$

$$2 = \frac{3 - 0.7}{R_E + 10/10} \Rightarrow R_E = \underline{1.05 \text{ k}\Omega}$$

$$\text{Use } R_E = \underline{1 \text{ k}\Omega}$$

The resulting  $I_E$  will be


$$I_E = \frac{3 - 0.7}{1 + 10/10} = 2.09 \text{ mA}$$

$$I_C = \kappa I_E = 0.99 \times 2.09 = 2.07 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{2.07}{0.025} = 82.9 \frac{\text{mA}}{\text{V}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{82.9} = 1.21 \text{ k}\Omega$$
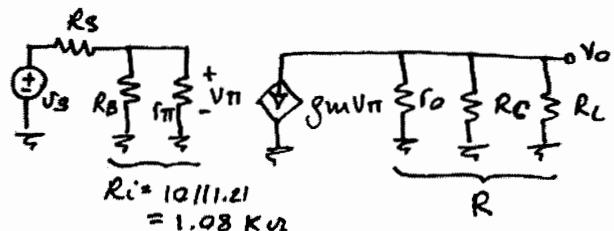
$$r_o = \frac{V_A}{I_C} = \frac{100}{2.07} = 48.3 \text{ k}\Omega$$



$$\begin{aligned} \frac{V_o}{V_s} &= \frac{V_{\pi}}{V_{\pi}} \cdot \frac{V_o}{V_{\pi}} = \frac{R_i}{R_s + R_i} \cdot \frac{-g_m V_{\pi} R}{V_{\pi}} \\ &= \frac{-1.08}{10+1.08} \times 82.9 \times R \end{aligned}$$

To obtain  $\frac{V_o}{V_s} = -8 \frac{\text{V}}{\text{V}}$  we use:

$$R = \frac{8 \times 11.08}{1.08 \times 82.9} = 0.99 \text{ k}\Omega$$

$$\text{Now } R = r_o \parallel R_c \parallel R_L$$

$$0.99 = 48.3 \parallel R_c \parallel 2$$

$$\Rightarrow R_c = 2.04 \text{ k}\Omega$$

$$\text{use } R_c = \underline{2 \text{ k}\Omega}$$

Check:  $V_C = 9 - 2.07 \times 2 = 4.86 \text{ V}$   
 while  $V_B \approx 3 \text{ V}$ . Thus in active mode as assumed.

4.113

$$V_{BB} = 9 \cdot \frac{47}{82+47} = 3.28 \text{ V}$$

$$R_B = 47 \parallel 82 = 29.88 \text{ k}\Omega$$


$$I_E = \frac{3.28 - 0.7}{3.6 + 29.88} = 0.66 \text{ mA}$$

$$I_C = 0.99 \times 0.66 = 0.65 \text{ mA}$$

$$g_m = \frac{0.65}{0.025} = 26 \text{ mA/V}$$

$$\Gamma_{\pi} = \frac{100}{26} = 3.85 \text{ k}\Omega$$
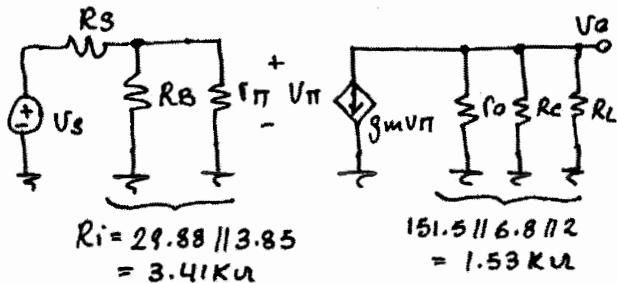
$$r_o = \frac{100}{0.66} = 151.5 \text{ k}\Omega$$



$$A_v = \frac{V_o}{U_s} = \frac{3.41}{10 + 3.41} \times -26 \times 1.53$$

$= -10.1 \text{ V/V}$  Which is about 25% higher than in the original design.


The improvement is not as large as might have been expected because although  $R_i$  increases,  $g_m$  decreases by about the same factor.

Indeed most of the improvement is due to the increase in  $R_C$  and hence in the effective load resistance.

4.114

$$\beta = 100$$

$$f_0 = \infty$$

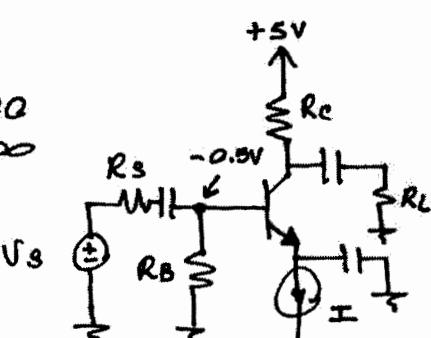

$$R_{in} = 5 \text{ k}\Omega, R_{in} = R_B \parallel \Gamma_{\pi}$$

$$\Rightarrow 5K = \frac{R_B \cdot \Gamma_{\pi}}{R_B + \Gamma_{\pi}}$$

$$5K \Gamma_{\pi} = R_B (\Gamma_{\pi} - 5K)$$

$$\text{but: } \Gamma_{\pi} = \frac{V_T}{I_B} \text{ and } R_B \cdot I_B = 0.5$$

$$\rightarrow 5K \cdot \frac{V_T}{I_B} = 0.5 (\Gamma_{\pi} - 5K)$$

$$\text{thus, } \Gamma_{\pi} = 5250 \text{ }\Omega$$

$$\text{then } R_B = 105 \text{ k}\Omega$$

$$\text{choose } R_B = 100 \text{ k}\Omega$$

$$\text{and } I_B = 4.76 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 101 \times 4.76 \text{ mA}$$

$$I_E = 0.48 \text{ mA}$$

$$I = I_E \rightarrow I \approx 0.5 \text{ mA}$$

To avoid saturation:

$$V_C - V_B \geq -0.5$$

$$V_C = 5V - R_C [I_C + g_m V_{BE}]$$

$$I_C = I \cdot \alpha = 0.5 \text{ mA} \times 100 / 101 = 0.49 \text{ mA}$$

$$g_m = \frac{V_T}{I_C} = \frac{25 \text{ m}}{0.49 \text{ mA}} \approx 50 \text{ mA/V}$$

$$V_{BE} = 0.005 \text{ V}$$

$$\rightarrow V_C = 5 - R_C [0.49 \text{ mA} + 50 \text{ mA} \times 5 \text{ m}] = 5 - 0.74 \times 10^{-3} \times R_C$$

Then:

$$V_C - V_B = (5 - 0.7mV R_E) - (-0.5 + V_{BE}) \\ = 5.495 - 0.7mV R_E > -0.5$$

$$R_E \leq \underline{8.1\text{ k}\Omega}.$$


Base-to-Collector open circuit gain:

$$\frac{V_C}{V_B} = -g_m R_C = -50m \times 8.1\text{ k} \\ = -\underline{405\text{ V/V}}$$

For  $R_S = 10\text{ k}$ ,  $R_L = 10\text{ k}$

$$\frac{V_o}{V_B} = -g_m (R_C \parallel R_L) \\ = -50m \times 4.47\text{ k} \\ = -223\text{ V/V}$$
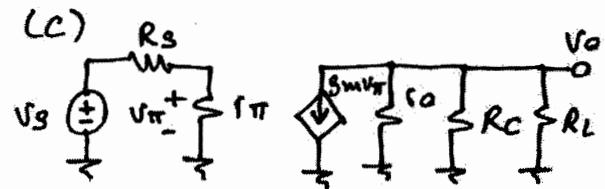
$$\frac{V_C}{V_S} = \frac{V_B}{V_S} \cdot \frac{V_o}{V_B} = \frac{5}{5+10} \times -223 \\ = -\underline{74.3\text{ V/V}}$$



$$R_L = 10\text{ k}\Omega, R_S = 2.5\text{ k}$$

$$f_0 = 200\text{ kHz}$$

$$g_m = \frac{I_C}{V_T} \approx \frac{0.5\text{ mA}}{25\text{ m}} = 20\text{ mA/V}$$

$$f_{\pi} = \frac{\beta}{g_m} = \frac{100}{20} = 5\text{ kHz}$$

$$A_V = \frac{V_o}{V_S} = \frac{f_{\pi} \times V_o}{f_{\pi} + R_S} \\ = \frac{f_{\pi}}{f_{\pi} + R_S} \times -g_m (R_C \parallel R_E \parallel R_L) \\ = -\frac{5}{5+2.5} \times 20 (200 \parallel 20 \parallel 10) \\ = -\underline{86\text{ V/V}}$$

4.115

$$I_E = 0.5\text{ mA}$$

$$(a) I_E = \frac{15 - 0.7}{R_E + R_S} \frac{1}{\beta + 1}$$

$$0.5 = \frac{14.3}{R_E + 2.5} \frac{1}{100}$$

$$\Rightarrow R_E = \underline{28.57\text{ k}\Omega}.$$

$$(b) V_C = 15 - R_C \cdot I_C$$

$$5 = 15 - R_C \times 0.99 \times 0.5\text{ mA} \\ \Rightarrow R_C = 20.2\text{ k}\Omega \\ \approx \underline{20\text{ k}\Omega}$$

4.116

(a) For each transistor

$$V_{BB} = 15 \times \frac{47}{100+47} = 4.8\text{ V}$$


$$R_B = R_1 \parallel R_2 = 100 \parallel 47 = 32\text{ k}\Omega$$

$$I_E = \frac{4.8 - 0.7}{3.9 + \frac{32}{101}} = 0.97\text{ mA}$$

$$I_C = 0.99 \times 0.97 = \underline{0.96\text{ mA}}$$

$$V_C = V_{CC} - I_C \times R_C$$
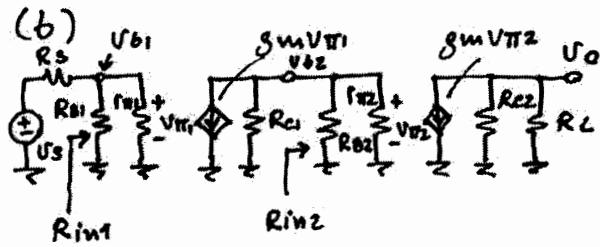
$$= 15 - 0.96 \times 6.8 = \underline{8.5\text{ V}}$$



$$R_{B1} = R_{B2} = R_B = 32 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{0.96}{0.025} = 38.4 \text{ mA/V}$$

$$r_{\pi 1} = r_{\pi 2} = \frac{100}{38.4} = 2.6 \text{ k}\Omega$$

$$R_{c1} = R_{c2} = 6.8 \text{ k}\Omega$$

$$f_{01} = f_{02} = \infty$$

$$(c) R_{in1} = R_{B1} // r_{\pi 1} \\ = 32 // 2.6 = \underline{\underline{2.4}} \text{ k}\Omega$$

$$\frac{U_{61}}{U_s} = \frac{R_{in1}}{R_s + R_{in1}} \\ = \frac{2.4}{5 + 2.4} = \underline{\underline{0.32}} \text{ V/V}$$

$$(d) R_{in2} = R_{B2} // r_{\pi 2} \\ = 32 // 2.6 = \underline{\underline{2.4}} \text{ k}\Omega$$

$$U_{62} = -g_{m1} U_{\pi 1} (R_{c1} // R_{in2}) \\ = -38.4 U_{61} (6.8 // 2.4)$$

$$\frac{U_{62}}{U_{61}} = -\underline{\underline{68.1}} \text{ V/V}$$

$$(e) U_o = -g_{m2} U_{\pi 2} (R_{c2} // R_L) \\ = -38.4 U_{62} (6.8 // 2)$$

$$\frac{U_o}{U_{62}} = -\underline{\underline{59.3}} \text{ V/V}$$

$$(f) \frac{U_o}{U_s} = \frac{U_{61}}{U_s} \times \frac{U_{62}}{U_{61}} \times \frac{U_o}{U_{62}} \\ = 0.32 \times -68.1 \times -59.3 \\ = \underline{\underline{1292}} \text{ V/V}$$

4.119

$$R_{in} = (\beta + 1)(r_e + 250)$$

$$\beta = 100 \quad r_e = \frac{V_T}{I_e} = \frac{0.025}{0.1} = 250 \Omega$$

$$R_{in} = 101 \times (250 + 250) \\ = \underline{\underline{50.5}} \text{ k}\Omega$$

$$\frac{U_6}{U_s} = \frac{R_{in}}{R_s + R_{in}} = \frac{50.5}{20 + 50.5} \\ = 0.72 \text{ V/V}$$

$$\frac{U_o}{U_6} = -\frac{\alpha (20 // 20)}{(r_e + R_E)} \\ = -\frac{0.99 \times 10}{0.250 + 0.250} = -\underline{\underline{19.8}} \text{ V/V}$$

$$\text{Thus, } \frac{U_o}{U_s} = 0.72 \times -19.8 = -\underline{\underline{14.2}} \text{ V/V}$$

For  $U_{be} = 5 \text{ mV}$ ,  $U_e = 5 \text{ mV}$  also  
(since  $r_e = R_E = 250 \Omega$ )

Thus,

$$U_b = 5 + 5 = 10 \text{ mV}$$


$$U_s = \frac{10}{0.72} = \underline{\underline{13.88}} \text{ mV}$$

$$U_o = 13.88 \times 14.2 = \underline{\underline{197.2}} \text{ mV}$$

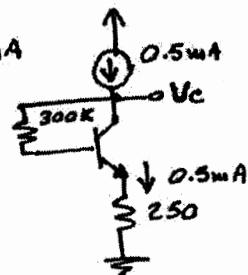4.120

$$(a) I_C = 0.99 \times 0.5 \text{ mA} \\ = 0.495 \text{ mA}$$

$$V_C = I_E R_E + V_{BE} \dots \\ + I_B R_B \\ = 0.5 \times 0.175 + 0.7 \\ + 0.005 \times 300 \\ = \underline{\underline{2.28 \text{ V}}}$$



$$(b) i_e = \frac{V_i}{r_e + R_E}$$

$$r_e = \frac{V_T}{I_E} = 50 \text{ ohm}$$

$$\rightarrow i_e = \frac{V_i}{50 + 250}$$


$$i_e = \frac{V_i}{300}$$

Node equation at C:

$$\frac{V_o - V_i}{300K} + \alpha i_e + \frac{V_o}{30K} = 0$$


$$\frac{V_o - V_i}{300K} + \frac{\alpha V_i}{(250 + 50)} + \frac{V_o}{30K} = 0$$
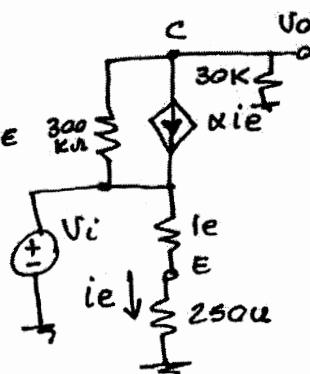
$$\Rightarrow \frac{V_o}{V_i} = \underline{\underline{-90 \text{ V/V}}}$$



4.121

$$\alpha = 1$$

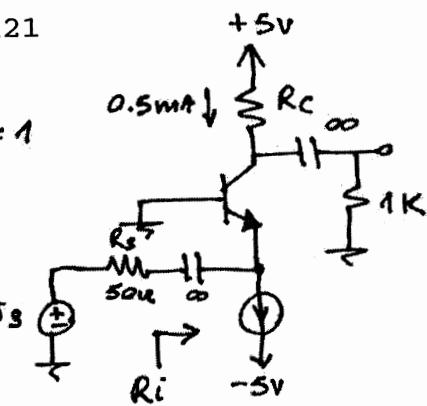

$$R_i = \frac{V_T}{I} = 50 \text{ ohm} \Rightarrow I = \underline{\underline{0.5 \text{ mA}}}$$

$$V_c = 5 - 0.5 \cdot R_c$$

$$V_{cmin} = V_c - 0.01 g_m (R_c \parallel 1K)$$

To prevent saturation  $V_{cmin} = 0$

$$\rightarrow 0 = V_c - 0.01 \times 20 \quad (R_c \parallel 1K) \\ = 5 - 0.5 \frac{R_c}{R_c + 1}$$

$$5R_c + 5 - 0.5R_c^2 - 0.5R_c - 0.2R_c = 0$$

$$0.5R_c^2 - 4.3R_c + 5 = 0$$

$$R_c = \frac{4.3 + \sqrt{4.3^2 + 10}}{1}$$

$$= 9.64 \text{ K}\Omega$$

$$\text{Select } R_c = \underline{\underline{9.1 \text{ K}\Omega}}$$

$$V_c = 0.45 \text{ V}$$

$$\frac{V_o}{V_s} = \frac{R_i}{R_s + R_i} g_m \quad (R_c \parallel 1K)$$

$$= \frac{50}{50+50} \times 20 \times (9.1 \parallel 1)$$

$$= \underline{\underline{9 \text{ V/V}}}$$

For  $U_{BE\max} = 10 \text{ mV}$

$$U_{S\max} = 20 \text{ mV}$$

$$V_{C\max} = 180 \text{ mV}$$

Thus the collector voltage swings from

$$(0.45 - 0.18) \text{ V to } (0.45 + 0.18) \text{ V}$$

i.e. from 0.27 V to 0.63 V

4.122

$$R_i = r_e = \frac{V_T}{I_E} = \frac{V_T}{0.5} = \underline{\underline{50 \Omega}}$$

To find the voltage gain  $\frac{U_o}{U_s}$  first note that

$$\frac{U_e}{U_s} = \frac{R_i}{R_s + R_i} = \frac{50}{50 + 50} = 0.5$$

Then,

$$\begin{aligned} \frac{U_C}{U_e} &= \alpha \times (\text{Total resistance at C}) \\ \frac{U_C}{U_e} &= \frac{r_e}{r_e} \\ &\approx \frac{1 \times (100 \text{ k}\Omega // 1 \text{ k}\Omega)}{50 \Omega} \\ &= 19.8 \text{ V/V} \end{aligned}$$

$$\text{Thus, } \frac{U_o}{U_s} = 19.8 \times 0.5 = \underline{\underline{9.9 \text{ V/V}}}$$

4.123

$$(a) I_E = \frac{9 - 0.7}{1 + 100 // (\beta + 1)}$$

$$\text{for } \beta = 40, I_E = \frac{8.3}{1 + \frac{100}{40}} = \underline{\underline{2.41 \text{ mA}}}$$

$$V_E = 1 \times 2.41 = \underline{\underline{2.41 \text{ V}}}$$

$$V_B = 2.41 + 0.7 = \underline{\underline{3.11 \text{ V}}}$$

$$\text{for } \beta = 200, I_E = \frac{8.3}{1 + \frac{100}{200}} = \underline{\underline{5.54 \text{ mA}}}$$

$$V_E = + \underline{\underline{5.54 \text{ V}}}$$

$$V_B = + \underline{\underline{6.24 \text{ V}}}$$

$$(b) R_i = 100 \text{ k}\Omega // (\beta + 1) [r_e + (1//1)] \\ = 100 // (\beta + 1) [r_e + 0.5]$$

$$\text{For } \beta = 40, I_E = 2.41 \text{ mA}$$

$$\rightarrow r_e = 10.37 \text{ V}$$

$$\text{thus } R_i = 100 // 40 \times (0.01037 + 0.5) \\ = 100 // 21 \\ = \underline{\underline{17.3 \Omega}}$$

$$\text{For } \beta = 200, I_E = 5.54 \text{ mA}$$

$$\rightarrow r_e = 4.51 \text{ V}$$

$$\text{thus } R_i = 100 // 200 \times (0.0045 + 0.5) \\ = 100 // 101.4 \\ = \underline{\underline{50.3 \text{ k}\Omega}}$$

$$(c) \frac{U_o}{U_s} = \frac{U_B}{U_s} \cdot \frac{U_o}{U_B} \\ = \frac{R_i}{R_s + R_i} \cdot \frac{(1//1)}{(1//1) + r_e}$$

$$\text{For } \beta = 40,$$

$$\begin{aligned} \frac{U_o}{U_s} &= \frac{17.3}{10 + 17.3} \times \frac{0.5}{0.5 + 0.01037} \\ &= \underline{\underline{0.621 \text{ V/V}}} \end{aligned}$$

$$\text{For } \beta = 200,$$

$$\begin{aligned} \frac{U_o}{U_s} &= \frac{50.3}{10 + 50.3} \cdot \frac{0.5}{0.5 + 0.0045} \\ &= \underline{\underline{0.827 \text{ V/V}}} \end{aligned}$$

4.124

$$I_E = \frac{5 - 0.7}{3.3 + 100} = 1.00 \text{ mA}$$

$$r_e = \frac{25}{1.00} = 25 \text{ mV}$$

$$R_i = (\beta + 1) [r_e + (3.3 \parallel 1)] \\ = 80.0 \text{ kV}$$

$$\frac{U_o}{U_s} = \frac{U_b}{U_s} \cdot \frac{U_o}{U_b} = \frac{R_i}{R_s + R_i} \frac{(3.3 \parallel 1)}{r_e + (3.3 \parallel 1)}$$

Thus,

$$\frac{U_o}{U_s} = \frac{80}{100 + 80} \cdot \frac{(3.3 \parallel 1)}{0.025 + (3.3 \parallel 1)} \\ = 0.430 \text{ V/V}$$

$$\frac{i_o}{i_i} = \frac{U_o / R_L}{U_s / (R_s + R_i)} \\ = \frac{U_o}{U_s} \cdot \frac{R_s + R_i}{R_L} \\ = 0.43 \times \frac{(100 + 80)}{1} \\ = 77.4 \text{ A/A}$$

$$R_{out} = 3.3 \parallel [r_e + \frac{100}{\beta + 1}]$$


$$= 3.3 \parallel [0.025 + \frac{100}{101}] \\ = 0.776 \text{ kV}$$

4.125

$$(a) I_{E2} = 5 \text{ mA}$$

$$\beta_1 = 50, \quad \beta_2 = 100$$
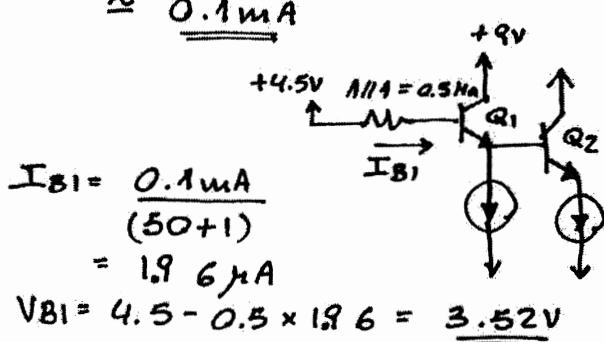
$$I_{E1} = 50 \text{ mA} + I_{B2} \\ = 50 + \frac{I_{E2}}{\beta_2 + 1} = 50 + \frac{5000}{101} \\ \approx 0.1 \text{ mA}$$



$$I_{B1} = \frac{0.1 \text{ mA}}{(50 + 1)} \\ = 1.96 \mu\text{A}$$

$$V_{B1} = 4.5 - 0.5 \times 1.96 = 3.52 \text{ V}$$

$$V_{B2} = 3.52 - 0.7 = 2.82 \text{ V}$$

(b) Refer to Fig. P. 5.148

$$\frac{U_o}{U_{B2}} = \frac{R_L}{R_L + r_{e2}}$$

$$R_L = 1 \text{ kV} \quad r_{e2} = \frac{25}{5} = 5 \text{ mV}$$

$$\frac{U_o}{U_{B2}} = \frac{1}{1 + 0.005} = 0.995 \text{ V/V}$$

$$R_{ib2} = (\beta_2 + 1) (r_{e2} + R_L) \\ = (101) \times (1.005) \\ = 101.5 \text{ kV}$$

$$(c) \frac{U_{e1}}{U_{B1}} = \frac{R_{ib2}}{R_{ib2} + r_{e1}}$$

$$r_{e1} = \frac{V_T}{100 \mu\text{A}} = 250 \text{ mV}$$

$$\rightarrow \frac{U_{e1}}{U_{B1}} = \frac{101.5}{101.5 + 0.25} = 0.997 \text{ V/V}$$

$$R_i = 1 \text{ M}\Omega \parallel 1 \text{ M}\Omega \parallel (\beta_1 + 1)(r_{e1} + R_{ib2}) \\ = 1 \parallel 1 \parallel 51 \times (0.25 + 101.5) \text{ kV} \\ = 1 \parallel 1 \parallel 5.2 \text{ M}\Omega \\ = 0.499 \text{ M}\Omega = 499 \text{ kV}$$

$$(d) \frac{U_{B1}}{U_s} = \frac{R_i}{R_s + R_i} = \frac{499}{100 + 499} = 0.833 \text{ V/V}$$

$$(e) \frac{U_0}{U_S} = \frac{U_{b1}}{U_S} \cdot \frac{U_{e1}}{U_{b1}} \cdot \frac{U_0}{U_{e1}}$$
$$= 0.833 \times 0.997 \times 0.995$$
$$= \underline{\underline{0.826 \text{ V/V}}}$$

## 5.1

The capacitance per unit area is:  $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$

$$\epsilon_{ox} = 3.45 \times 10^{11} \text{ F/m}$$

$$t_{ox} = 5 \text{ nm} \Rightarrow C_{ox} = \frac{3.45 \times 10^{11}}{5 \times 10^{-9}} = 6.9 \text{ fF}/\mu\text{m}^2$$

$$t_{ox} = 20 \text{ nm} \Rightarrow C_{ox} = 0.86 \text{ fF}/\mu\text{m}^2$$

For 1PF capacitance, we require an area A:

$$A = \frac{10^{-12}}{6.9 \times 10^{-15}} = 145 \mu\text{m}^2 \text{ for } t_{ox} = 5 \text{ nm}$$

$$A = \frac{10^{-12}}{0.86 \times 10^{-15}} = 1163 \mu\text{m}^2 \text{ for } t_{ox} = 20 \text{ nm}$$

For a square plate capacitor of 10PF:

$$A = 10 \times 145 = 1450 \mu\text{m}^2 \text{ or } 38 \times 38 \mu\text{m}^2 \text{ square for } t_{ox} = 5 \text{ nm}$$

$$A = 10 \times 1163 = 11630 \mu\text{m}^2 \text{ or } 108 \times 108 \mu\text{m}^2 \text{ square for } t_{ox} = 20 \text{ nm}$$

## 5.2

With  $V_{ds}$  small, compared to  $V_{ov}$ ,

$$r_{DS} = \frac{1}{(\mu_n C_{ox}) \left( \frac{W}{L} \right) (V_{ov})}$$

(a)  $V_{ov}$  is doubled  $\rightarrow r_{DS}$  is halved. factor = 0.5

(b) W is doubled  $\rightarrow r_{DS}$  is halved. factor = 0.5

(c) W and L are doubled  $\rightarrow r_{DS}$  is unchanged. factor = 1.0

(d) If oxide thickness  $t_{ox}$  is halved, and

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$C_{ox}$  is doubled. If W and L are also halved,  $r_{DS}$  is halved, factor = 0.5

## 5.3

The transistor size will be minimized if  $W/L$  is minimized, since  $W/L$  appears in the equations that must be satisfied, we can minimize  $(W/L)$ . Clearly we want to minimize  $L$  by using the smallest feature size.

$$L = 0.18 \mu\text{m}$$

$$r_{DS} = \frac{1}{k_b (W/L) (V_{GS} - V_t)}$$

$$r_{DS} = \frac{1}{k_b' (W/L) V_{ov}}$$

Two conditions need to be met for  $V_{ov}$  and  $r_{DS}$

Condition 1:

$$r_{DS,1} = \frac{1}{400 \times 10^{-6} (W/L) V_{ov,1}} \\ = 200 \Rightarrow (W/L) V_{ov,1} = 12.5$$

Condition 2:

$$r_{DS,2} = \frac{1}{400 \times 10^{-6} (W/L) V_{ov,2}} \\ = 1000 \Rightarrow (W/L) V_{ov,2} = 2.5$$

If condition 1 is met, condition 2 will be met since the over-voltage can always be reduced to satisfy this requirement. For condition 1, we want to decrease  $W/L$  as much as possible (so long as it is greater than or equal to 1), while still meeting all of the other constraints.

This requires our using the largest possible  $v_{GS,1}$  voltage.  $v_{GS,1} = 1.8$  Volts, so  $v_{ov,1} = 1.4$  Volts that

$$W/L = \frac{12.5}{v_{ov,1}} = \frac{12.5}{1.4} \approx 8.93$$

Condition 2 now can be used to find  $v_{GS,2}$

$$v_{ov,2} = \frac{12.5}{W/L} = \frac{2.5}{12.5/1.4} = 0.28$$

$$\Rightarrow v_{GS,2} = 0.68 \text{ Volts} \Rightarrow 0.68 \leq v_{GS} \leq 1.8$$


## 5.4

$$k_n = 5 \text{ mA/V}^2 \quad V_t = 0.5 \text{ V}$$

Small  $v_{DS}$

$$i_D = k_n (v_{GS} - V_t) v_{DS} = k_n v_{ov} v_{DS}$$
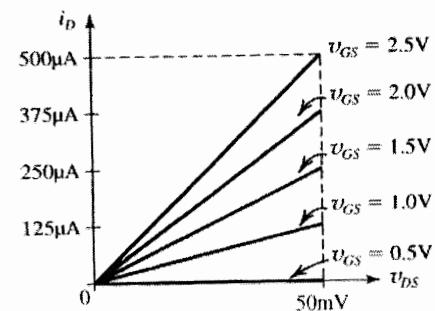
$$g_{DS} = \frac{1}{r_{DS}} = k_n v_{ov}$$



(V)	(V)	(mS)	(Ω)
$V_{GS}$	$V_{OV}$	$g_{DS}$	$r_{DS}$
0.5	0	0	$\infty$
1.0	0.5	2.5	400
1.5	1.0	5.0	200
2.0	1.5	7.5	133
2.5	2.0	10	100

5.5

$$V_{DS\text{ sat}} = V_{OV}$$

$$V_{OV} = V_{GS} - V_t = 2.5 - 1 = 1.5 \text{ V}$$

$$\Rightarrow V_{DS\text{ sat}} = 1.5 \text{ V}$$

In saturation:

$$i_D = \frac{1}{2} K'_n \left(\frac{W}{L}\right) V_{OV}^2 = \frac{1}{2} K_n V_{OV}^2$$

$$i_D = \frac{1}{2} \times \frac{1 \text{ mA}}{\text{V}^2} \times (1.5 \text{ V})^2$$

$$i_D = (1.125 \text{ mA})$$

5.6

$$\text{a)} C_{ox} = \frac{E_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{15 \times 10^{-9}} = 2.3 \text{ fF}/\mu\text{m}^2$$

$$K_n = \mu_n C_{ox} = 550 \times 10^{-4} \times 2.3 \times 10^{-3} = 126.5 \text{ A/V}^2$$

$$\text{b)} i_D = \frac{1}{2} K_n \frac{W}{L} (V_{GS} - V_t)^2 \Rightarrow 100 = \frac{1}{2} \times 126.5 \times \frac{16}{0.8} (V_{GS} - 0.7)^2$$

$$V_{GS} - 0.7 = 0.28 \Rightarrow V_{OV} = 0.28 \text{ V}$$

$$V_{GS} = 0.98 \text{ V}$$

$$V_{DS\text{ min}} = V_{GS} - V_t = 0.28 \text{ V}$$

$$\text{c)} \text{For small } V_{DS} \text{ (triode region)}: i_D = \frac{K_n W}{L} V_{OV} \cdot V_{DS}$$

$$r_{DS} = \frac{V_{DS}}{i_D} = \frac{1}{K_n \frac{W}{L} V_{OV}} = \frac{1}{126.5 \times 10^{-6} \times \frac{16}{0.8} \times 0.28} = 1000$$

$$\Rightarrow V_{OV} = 0.4 \text{ V}$$

$$V_{GS} = V_{OV} + V_t = 0.4 + 0.7 = 1.1 \text{ V}$$

5.7

p-Channel

$$V_{ip} = -0.7 \text{ V.}$$

$$(a) |V_{OV}| = 0.5 \text{ V.}$$

$$V_{GS} = -1.2 \text{ V.} = V_G$$

$$(b) \text{for } V_{GD} = V_{ip}, V_{DS} = V_{GS} - V_{DS} = (-1.2) - (-0.5) = -0.7 \text{ V.}$$

$$V_{DS} = V_D \leq -0.7 \text{ V.}$$

$$(c) i_D = 1 \text{ mA in saturation mode}$$

$$\therefore k_p = \frac{2i_D}{(V_{GS} - V_{ip})^2} = 8 \text{ mA/V}^2$$

For  $V_D = -10 \text{ mV}$ , ohmic mode

$$i_D = k_p \left( V_{GS} - V_{ip} - \frac{1}{2} V_{DS} \right) (V_{DS})$$

$$= 39.6 \text{ } \mu\text{A}$$

For  $V_D = -2 \text{ V}$ , sat mode,  $i_D = 1 \text{ mA}$

5.8

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2 \quad k'_n = \mu_n C_{ox}$$

for equal drain currents :

$$\mu_n C_{ox} \frac{W_n}{L} = \mu_p C_{ox} \frac{W_p}{L} = \frac{W_p}{W_n} = \frac{\mu_n}{\mu_p}$$

$$= \frac{1}{0.4} = 2.5$$

5.9

$$\text{For small } V_{DS} = i_D \approx k'_n \frac{W}{L} (V_{GS} - V_t) \cdot V_{DS}$$

$$r_{DS} = \frac{V_{DS}}{i_D} = \frac{1}{k'_n \frac{W}{L} (V_{GS} - V_t)}$$

$$= \frac{1}{50 \times 10^{-6} \times 20 \times (5 - 0.8)}$$

$$r_{DS} = 238 \Omega \quad V_{DS} = r_{DS} \times i_D = 238 \text{ mV}$$

for the same performance of a p-channel device :

$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} = 2.5 \Rightarrow \frac{W_p}{L} = \frac{W_n}{L} \times 2.5 =$$

$$20 \times 2.5 \Rightarrow \frac{W_p}{L} = 50$$

5.10

$$k'_n = \mu_n C_{ox} = \mu_n \frac{C_{ox}}{t_{ox}} = 6.50 \times 10^{-4} \times \frac{3.45 \times 10^{-11}}{20 \times 10^{-9}} = 112.1 \mu A/V^2$$

a) triode region:  $v_{DS} < v_{GS} - V_t$

$$i_D = k'_n \frac{W}{L} [(v_{GS} - V_t)v_{DS} - \frac{1}{2} v_{DS}^2]$$

$$i_D = 112.1 \times 10^{-6} \times 10 \left[ (5 - 0.8) \times 1 - \frac{1}{2} \times 1^2 \right] = 4.15 \text{ mA}$$

b) edge of saturation region:  $v_{DS} = v_{GS} - V_t$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 = \frac{1}{2} \times 112.1 \times 10^{-6} \times 10 \times (1.2)^2 = 0.8 \text{ mA}$$

c) triode region:  $v_{DS} < v_{GS} - V_t$

$$i_D = 112.1 \times 10^{-6} \times 10 \left[ (5 - 0.8) \times 0.2 - \frac{1}{2} \times 0.2^2 \right] = 0.92 \text{ mA}$$

d) Saturation region:  $v_{DS} > v_{GS} - V_t$

$$i_D = \frac{1}{2} \times 112.1 \times 10^{-6} \times 10 \times (5 - 0.8)^2 = 9.9 \text{ mA}$$

5.11

L (μm)	0.5	0.25	0.18	0.13
$t_{ox}$ (nm)	10	5	3.6	2.6
$C_{ox} \left( \frac{\text{fF}}{\mu\text{m}^2} \right) \epsilon_{ox} = 34.5 \text{ pF/m}$	3.45	6.90	9.58	13.3
$k'_n \left( \frac{\mu\text{A}}{\text{V}^2} \right)$ $\mu_n = 500 \text{ cm}^2/\text{VS}$	173	345	479	664
$k \left( \frac{\text{mA}}{\text{V}^2} \right)$ for $\frac{W}{L} = 10$	1.73	3.45	4.79	6.64
A ( $\mu\text{m}^2$ ) for $\frac{W}{L} = 10$	2.50	0.625	0.324	0.169
$V_{DD}$ (V)	5	2.5	1.8	1.3
$V_t$ (V)	0.7	0.5	0.4	0.4
$I_D$ (mA)				
for $v_{ds} = v_{DD} = V_D$	16	6.90	4.69	2.69
$I_D = \frac{1}{2} k_n (v_{DD} - V_t)^2$				
P (mW)				
$P = V_{DD} I_D$	80	17.3	8.44	3.50
$P \left( \frac{\text{mW}}{\mu\text{m}^2} \right)$	32	27.7	26.1	20.7
devices chip	n	4n	7.72n	14.8n

$$i_D = 191.7 \times 10^{-6} \times 10 [(5 - 0.7) \times 0.2 - \frac{1}{2}(0.2)^2]$$

$$= 1.61 \text{ mA}$$

(d) saturation region:  $V_{ds} > V_{GS} - V_t$

$$i_D = \frac{1}{2} \times 191.7 \times 10^{-6} \times 10 \times (5 - 0.7)^2$$

$$= 17.7 \text{ mA}$$


### 5.12

Sat mode,  $\lambda = 0$

$$\left(\frac{i_D}{k_n}\right) = \frac{1}{2} v_{ov}^2$$


Slope at  $v_{ov} = 1 \text{ V}$ :

$$m = 1 \frac{\text{V}^2}{\text{V}}$$

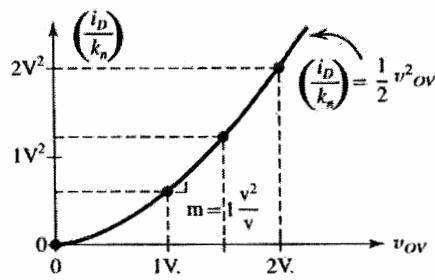

Ohmic mode,  $\lambda = 0$
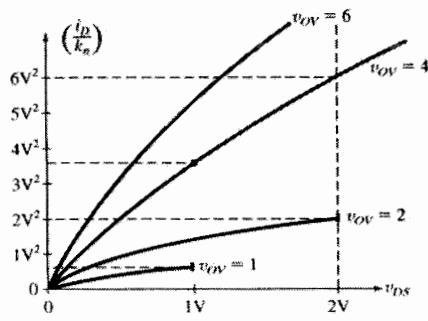
$$\left(\frac{i_D}{k_n}\right) = v_{ov} v_{ds} - \frac{1}{2} v_{ds}^2$$



$$\left. \frac{\partial \frac{i_D}{k_n}}{\partial v_{ds}} \right|_{v_{ds}=0} = v_{ov}$$

For pmos, change

$$v_{ds} \rightarrow v_{sd}$$

$$v_{ov} \rightarrow v_{sg} - |V_{tp}|$$

### 5.13

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 \Rightarrow 0.2 \times 10^{-3} = \frac{1}{2} \times 0.1 \times 10^{-3} (V_{GS} - 1)^2$$

$$V_{GS} - 1 = 2 \Rightarrow V_{GS} = 3 \text{ V}$$

$$V_{DSmin} = V_{GS} - V_t = 3 - 1 = 2 \text{ V}$$

$$\text{For } i_D = 0.8 \text{ mA: } 0.8 = \frac{1}{2} \times 0.1 (V_{GS} - 1)^2$$

$$V_{GS} - 1 = 4 \Rightarrow V_{GS} = 5 \text{ V}$$

$$V_{DSmin} = V_{GS} - V_t = 5 - 1 = 4 \text{ V}$$

### 5.14

$V_{GS} = V_{DS}$  indicates operation in saturation mode:

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2$$

$$4 = \frac{1}{2} k_n' \frac{W}{L} (5 - V_t)^2 \quad \left. \begin{array}{l} \\ \end{array} \right\} \Rightarrow 4 = \frac{(5 - V_t)^2}{(3 - V_t)^2} \Rightarrow$$

$$(5 - V_t) = 2(3 - V_t) \Rightarrow V_t = 1 \text{ V} \quad , \quad k_n' \frac{W}{L} = 0.5 \text{ mA/V}^2$$

### 5.15

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 \Rightarrow 0.8 = \frac{1}{2} \times 50 \times 10^{-3} \frac{W}{L} (5 - 1)^2$$

$$\frac{W}{L} = 2 \Rightarrow W = 2 \times 2 = 4 \mu\text{m}$$

### 5.16

For the channel to remain continuous:

$$V_{DS} \leq V_{GS} - V_t \Rightarrow V_{DSmax} = 1.5 - 0.8 = 0.7 \text{ V}$$

### 5.17

$$r_{os} = \left[ k_n' \frac{W}{L} V_{ov} \right]^{-1}$$

$$= \frac{1}{50 \times \frac{100}{5} (V_{GS} - 1)} \text{ M}\Omega$$

$$r_{ds} = \frac{1}{V_{GS} - 1} \text{ k}\Omega$$

$$V_{GS} = 1.1 \text{ V} \Rightarrow r_{ds} = 10 \text{ k}\Omega$$

$$V_{GS} = 11 \text{ V} \Rightarrow r_{ds} = 100 \Omega$$

$$\Rightarrow 100 \Omega \leq r_{ds} \leq 10 \text{ k}\Omega$$

5.19

a)  $r_{DS} \propto \frac{1}{W}$  so if  $W$  is halved,  $r_{DS}$  is doubled;

$$200 \Omega \leq r_{DS} \leq 20 \text{ k}\Omega$$


b)  $r_{DS} \propto L$  so if  $L$  is halved,  $r_{DS}$  is also halved;

$$50 \Omega \leq r_{DS} \leq 5 \text{ k}\Omega$$

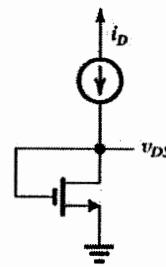c)  $r_{DS} \propto \frac{L}{W}$  so if both  $W$  and  $L$  are halved,  $\frac{W}{L}$


stays unchanged and so does  $r_{DS}$ .

$$100 \Omega \leq r_{DS} \leq 10 \text{ k}\Omega$$




$$v_{DS} = v_{GS}$$

$$i_D = \frac{1}{2}k_n(v_{DS} - V_t)^2$$

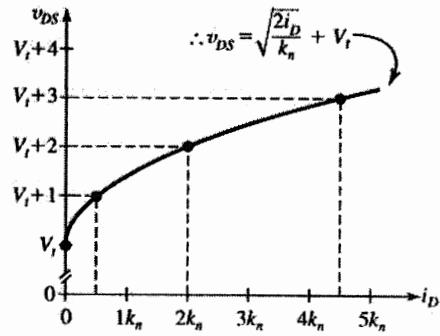

5.18

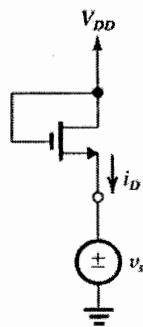

$$v_{GD} = 0 \Rightarrow \text{saturation}$$

$$i_D = \frac{1}{2}k_n(v_{GS} - V_t)^2$$


$$v_{GS} = V_{DD} - v_S$$

$$\therefore i_D = \frac{1}{2}k_n[(V_{DD} - V_t)^2 - 2(V_{DD} - V_t)v_S + v_S^2]$$

$$i_D = \frac{1}{2}k_n[(V_{DD} - V_t)^2 - 2(V_{DD} - V_t)v_S + v_S^2]$$

$$0 \leq v_S \leq (V_{DD} - V_t)$$

$$i_D = 0, v_S \geq (V_{DD} - V_t)$$

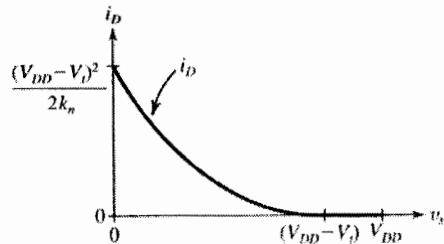

5.20


$$V_{DS} = V_p - V_s \quad V_{GS} = V_g - V_s$$

$V_{OV} = V_{GS} - V_i = V_{GS} - 1.0$  According to Table 5.1, three regions are possible.

Case	$V_s$	$V_g$	$V_D$	$V_{GS}$	$V_{OV}$	$V_{DS}$	Region of Operation
a	+1.0	+1.0	+2.0	0	-1.0	+1.0	cut-off
b	+1.0	+2.5	+2.0	+1.5	+0.5	+1.0	sat.
c	+1.0	+2.5	+1.5	+1.5	+0.5	+0.5	sat.
d	+1.0	+1.5	0	+0.5	-0.5	-1.0	sat.
e	0	+2.5	1.0	+2.5	+1.5	+1.0	triode.
f	+1.0	+1.0	+1.0	0	-1.0	0	cut-off.
g	-1.0	0	0	+1.0	0	+1.0	sat.
h	-1.5	0	0	+1.5	+0.5	+1.5	sat.
i	-1.0	0	+1.0	+1.0	0	+2.0	sat.
j	+0.5	+2.0	+0.5	+1.5	+0.5	0	triode.

\* with  $V_{DS}$  negative, drain and source are reversed to show the device is in the saturation region.

5.21

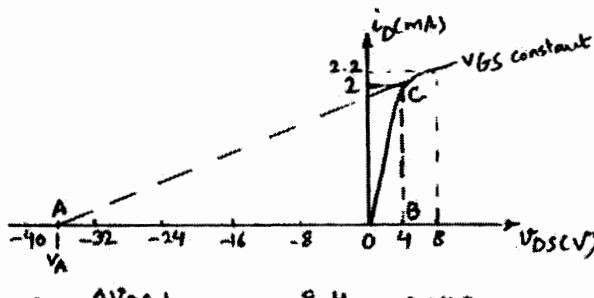

$$r_o = \frac{\Delta V_{DS}}{\Delta i_D} \Big|_{V_{GS}\text{Const}} = \frac{8-4}{2.2-2} = 20\text{k}\Omega$$

To calculate  $V_A$ , consider the ABC triangle:

$$V_A + 4 = 2\text{mA} \times r_o = 2 \times 20 = 40\text{V} \Rightarrow V_A = 36\text{V}$$

$$\lambda = \frac{L}{V_A} = 0.028 \text{ V}^{-1}$$

5.22

$$\lambda = 0.02 \text{ V}^{-1} \Rightarrow V_A = 50\text{V} \text{ for}$$

$$L = 1 \mu\text{m}$$

$$V_A = V_A L \Rightarrow V_A = 50\text{V}$$

$$\text{for } L = 3 \mu\text{m}: V_A = 50 \times 3 = 150\text{V}$$

$$r_o = \frac{V_A}{I_D} = \frac{150}{0.08} = 1875 \text{ k}\Omega$$

$$r_o = \frac{\Delta V_{DS}}{\Delta i_D} \Rightarrow \Delta i_D$$

$$= \frac{\Delta V_{DS}}{r_o} = \frac{5-1}{1875} = 2.13 \mu\text{A}$$

for  $V_{DS}$  raised from 1V to 5V,  $i_o$  increases from 80  $\mu\text{A}$  to 82.13  $\mu\text{A}$ .

$$\frac{\Delta i_D}{i_D} = 2.7 \% \text{ change in } i_o$$

In order to reduce  $\frac{\Delta i_D}{i_D}$  by a factor of 2,  $\Delta i_D$  has

to be halved, or equivalently  $r_o$  has to be doubled. In order to double  $r_o$ ,  $V_A$  has to be doubled and this can be done by doubling the length.  $L = 2 \times 3 = 6 \mu\text{m}$

5.23

original

$$r_o = \left[ \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_t)^2 \right]^{-1}$$

$$= \left[ \frac{1}{2} \lambda k_n \frac{W}{L} (V_{ov})^2 \right]^{-1}$$

$$\text{new } r_o = \left[ \frac{1}{2} \lambda k_n \frac{4W}{4L} \left( \frac{1}{2} V_{ov} \right)^2 \right]^{-1} = 4r_o$$

Note that quadrupling  $W$  and  $L$  had no effect, but decreasing the overdrive voltage by half increased the output resistance by a factor of 4.

5.24

MOS	1	2	3	4
$\lambda(\text{v}')$	0.02	0.01	0.1	0.005
$V_A (\text{V})$	50	100	10	200
$I_D (\text{mA})$	5	3.33	0.1	0.2
$r_o (\text{k}\Omega)$	10	30	100	1000
$r_o = \frac{V_A}{I_D}$	$, \lambda = \frac{L}{V_A}$			

5.25

$$V_{GS} = -3\text{V} \quad V_{SG} = 3\text{V} \quad V_t = -1\text{V}$$

$$V_{DS} = -4\text{V} \quad V_{SD} = 4\text{V} \quad V_A = -50\text{V}$$

$$\lambda = -0.02\text{V}^{-1}$$

$$i_D = \frac{1}{2} k_p \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$3 = \frac{1}{2} k_p \frac{W}{L} (-3 + 1)^2 (1 + 0.02 \times 4)$$

$$= 2.16 k_p \frac{W}{L}$$


$$k_p \frac{W}{L} = 1.39 \text{mA/V}^2$$

5.26

	$V_s$	$V_g$	$V_p$	$V_{sg}$	$ V_{sd} $	$V_{sp}$	Region of Operation
a	+2	+2	0	OV.	OV.	2V.	cutoff
b	+2	+1	0	+1V.	OV.	2V.	cutoff/sat
c	+2	0	0	+2V.	1V.	2V.	Sat
d	+2	0	+1	+2V.	1V.	1V.	Sat/ohmic
e	+2	0	+1.5	+2V.	1V.	0.5V	ohmic
f	+2	0	+2	+2V.	1V.	0V.	ohmic

pmos  $V_g = -1V$ ,

5.27

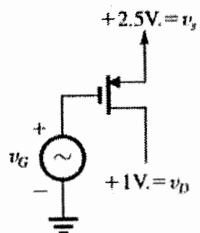

pmos

$$V_{tp} = -0.5V$$


$$V_{sp} = 1.5V$$

$$V_{GS} \geq V_{tp} \Rightarrow \text{Cutoff}$$

$$\therefore V_G \geq 2.0V \Rightarrow \text{Cutoff}$$

$$V_{GD} \leq V_{tp} \Rightarrow \text{ohmic}$$
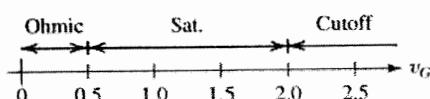
$$\therefore V_{GD} \leq +0.5V \Rightarrow \text{ohmic}$$



5.28

$$\frac{\Delta i_D}{I_D} = \frac{\frac{\partial i_D}{\partial k_n} \Big|_{I_D} \frac{dk_n}{dT} \Delta T + \frac{\partial i_D}{\partial V_t} \Big|_{I_D} \frac{dV_t}{dT} \Delta T}{\left[ \frac{1}{2} k_n \frac{W}{L} (v_{ES} - V_t)^2 \right] \Big|_{I_D}}$$

$$(a) \frac{\Delta i_D}{I_D} = \frac{1}{k_n} \frac{dk_n}{dT} \Delta T + \frac{-2}{(V_{GS} - V_t)} \frac{dV_t}{dT} \Delta T$$

(b)

$$\frac{\left( \frac{\Delta i_D}{I_D} \right)}{\Delta T} = -\frac{0.002}{C^\circ} = \frac{1}{k_n} \frac{dk_n}{dT} - \left( \frac{2}{4V} \right) \left( \frac{-2mV}{C^\circ} \right)$$

for  $V_t = +1V$ ,  $V_{es} = 5V$ ,  $V_{ov} = 4V$ ,

$$\therefore \frac{\left( \frac{dk_n}{dT} \right)}{k_n} = -0.003/C^\circ (-0.3\% C^\circ)$$

5.29

$$a) I_D = \frac{1}{2} K_n \frac{W}{L} (V_{GS} - V_E)^2 \Rightarrow 2 = \frac{1}{2} K_n \frac{W}{L} (3-1)^2 \\ \Rightarrow K_n \frac{W}{L} = 1 \text{ mA}/\sqrt{2}$$

$$V_i = V_{DS} = 3V$$

$$b) V_2 = V_S = V_D - V_{DS} = 1-3 = -2V$$

$$c) V_3 = V_5 = V_D - V_{DS} = 0 - (-3) = 3V$$

$$d) V_4 = V_D = V_S + V_{DS} = 5 + (-3) = 2V$$

In order to calculate  $R_{max}$  that can be inserted in series with the drain,  $V_{DS}$  has to be equal to  $V_{GS} - V_E$ , so that the device is operating on the edge of saturation:

$|V_{DS}| = 3-1 = 2V$ . Note that since  $i_D$  is the same,  $V_{GS}$  stays the same.

$$a) R_{Dmax} = \frac{3-2}{2 \text{ mA}} = 0.5 \text{ k}\Omega$$

$$b) V_2 = -2V \Rightarrow V_D = -2 + 2 = 0 \Rightarrow R_{Dmax} = \frac{1}{2} = 0.5 \text{ k}\Omega$$

Note that  $V_2$  is fixed through  $V_{GS} = 3V$ .

$$c) V_{GS} = -3V \Rightarrow V_S = V_3 = 3V. \text{ Now for } V_{DS} \text{ to be } -2V, V_D \text{ has to be } 1V.$$

$$R_{Dmax} = \frac{1V}{2 \text{ mA}} = 0.5 \text{ k}\Omega$$

$$d) V_{GS} = -3V \Rightarrow V_E = V_4 = 2V. \text{ Adding the resistor between } V_4 \text{ and drain means that } V_D \text{ has to be } 5-2=3V \text{ and this leaves } 1V \text{ voltage drop on the resistor: } R_{Dmax} = \frac{1}{2} = 0.5 \text{ k}\Omega$$

In order to calculate the largest resistor added to the gates, note that since the gate doesn't draw any current, the value of the resistor is immaterial.

Now we calculate  $R_{Smax}$ , assuming that the voltage drop across the current source is at least  $2V$ :

$$a) V_i = 8V \text{ then } V_{GS} = 3V \Rightarrow V_S = 8-3 = 5V$$

$$R_{Smax} = \frac{5}{2} = 2.5 \text{ k}\Omega$$

$$b) V_2 = -9+2 = -7V, V_S = 1 - |V_{GS}| = -2V \\ R_{Smax} = \frac{-2-(-7)}{2} = 2.5 \text{ k}\Omega$$

$$c) V_3 = 10-2 = 8V, V_S = 0 + |V_{GS}| = 3V \\ R_{Smax} = \frac{8-3}{2} = 2.5 \text{ k}\Omega$$

$$d) V_4 = -5+2 = -3V, V_S = -3 + |V_{GS}| = 0V \\ R_{Smax} = \frac{0}{2} = 2.5 \text{ k}\Omega$$

5.30


$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{5-0}{R_D} = 1 \text{ mA} \Rightarrow R_D = 5 \text{ k}\Omega$$

$V_D = V_G \Rightarrow$  saturation

$$\text{therefore: } i_D = \frac{1}{2} K_n \frac{W}{L} (V_{GS} - V_E)^2 \\ = \frac{1}{2} \times 60 \times 10^3 \times \frac{100}{3} (V_{GS} - 1)^2 \\ \Rightarrow V_{GS} = 2V \Rightarrow V_3 = -2V \\ R_S = \frac{-2-(-5)}{1} = 3 \text{ k}\Omega$$

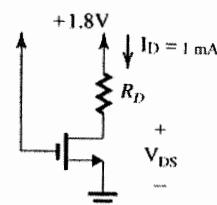5.31

$I_o = 1 \text{ mA}, V_i = 0.5 \text{ V}, V_{DD} = 1.8 \text{ V}$ . To operate at the edge of saturation,  $V_{DS}$  must equal  $V_o$ .



$$V_{GS} = V_G - V_i = 1.8 - 0 = 1.8 \text{ V}$$

$$V_{os} = V_{GS} - V_i = 1.8 - 0.5 = +1.3 \text{ V}$$

with  $V_{os} = V_{oi} = 1.3 \text{ V}$ ,

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{1.8 - 1.3}{1 \text{ mA}} = 500 \Omega$$

5.32

$$R_s = \frac{3.5}{0.115} = 3.04 \text{ k}\Omega$$

$$0.115 = \frac{1}{2} \times 60 \times 10 \times \frac{W_1}{0.8} (-1.5 - (-0.7))^2 \Rightarrow W_1 = 4.8 \mu\text{m}$$

5.33

$$V_{GS1} = 1.5 \text{ V}, 120 \mu\text{A} = \frac{1}{2} \times 120 \times \frac{W_1}{1} (1.5 - 1)^2$$

$$\Rightarrow W_1 = 8 \mu\text{m}$$

$$V_{GS2} = 3.5 - 1.5 = 2 \text{ V}, 120 = \frac{1}{2} \times 120 \times \frac{W_2}{1} (2 - 1)^2$$

$$\Rightarrow W_2 = 2 \mu\text{m}$$

$$R_s = \frac{5 - 3.5}{0.120} = 12.5 \text{ k}\Omega$$

5.34

$$V_{GS1} = 1.5 \text{ V}$$

$$120 \mu\text{A} = \frac{1}{2} \times 120 \times \frac{W_1}{1} (1.5 - 1)^{\frac{1}{2}}$$

$$W_1 = 8 \mu\text{m}$$

$$V_{GS2} = 2 \text{ V}$$

$$120 \mu\text{A} = \frac{1}{2} \times \frac{W_2^2}{1} (2 - 1)$$

$$W_2 = 2 \mu\text{m}$$

$$V_{GS3} = 1.5 \text{ V}$$

$$W_3 = 8 \mu\text{m}$$

5.35

$$V_1 = V_{GS} = 5 \text{ V}, V_o = V_{DS} = 0.05 \text{ V}$$

$$r_{DS} = 50 \Omega = \frac{V_{DS}}{I_D} \Rightarrow I_D = \frac{0.05}{50} = 0.001 \text{ A} = 1 \text{ mA}$$

$$R_s = \frac{V_{DD} - V_o}{I_D} = \frac{5 - 0.05}{1} = 4.95 \text{ k}\Omega$$

$V_{DS} < V_{GS} - V_t \Rightarrow$  triode region

$$I_D = K_n \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$1 = 100 \times 10^{-3} \frac{W}{L} \left[ (5 - 1) \times 0.05 - \frac{0.05^2}{2} \right] \Rightarrow \underline{\underline{W = 50}}$$

5.36

$$\text{In circuit a: } V_2 = 10 - 4 \times 2 = 2 \text{ V}$$

assume saturation:

$$I_D = 2 = \frac{1}{2} \times 1 \times (V_{GS} - 2)^2$$

$$= V_{GS} = 4 \text{ V}$$

$$\Rightarrow V_1 = -4 \text{ V}, V_{DS} = 6 \text{ V} > V_{GS} - V_t$$

so our assumption was correct.

In circuit b:

$$I_D = 1 = \frac{1}{2} \times 1 \times (V_{GS} - 2)^2 \Rightarrow$$

$$V_{GS} = 3.41 \text{ V}, V_3 = 3.41 \text{ V}$$

In circuit c:

$$I_D = 2 \text{ mA} \Rightarrow V_{GS} = -4 \text{ V} \Rightarrow V_S$$

$$= 4 \text{ V} = V_4$$

$$V_S = -10 \times 2.5 \times 2 = -5 \text{ V}$$

In circuit d:

$$I_D = 2 \text{ mA} \Rightarrow V_{GS} = -4 \text{ V} \Rightarrow V_6 = 6 \text{ V}$$

$$\Rightarrow V_7 = V_6 - 4 = 2 \text{ V}$$

If we replace the current source with a resistor in each of those circuits:

In circuit a:

$$R = \frac{-4 - (-10)}{2} \approx 3.01 \text{ k}\Omega$$

(by looking at the table for 1% resistors)

$$\text{now recalculate } I_D: I_D = \frac{1}{2} \times 1 \times (V_{GS} - V_t)^2$$

$$V_{GS} - V_t = 0 - (-10 + 3.01 I_D) = 2$$

$$= 8 - 3.01 I_D \Rightarrow$$

$$2 I_D = (8 - 3.01 I_D)^2 \Rightarrow I_D$$

$$= 1.99 \text{ mA} \Rightarrow V_2 = 2.04 \text{ V}$$

$$V_1 = -4.01 \text{ V}$$

In circuit b:

$$R = \frac{10 - 3.41}{1} = 6.59 \text{ k} \approx 6.65 \text{ k}\Omega$$

then

$$V_{GS} = 10 - 6.65I$$

$$= \frac{1}{2} \times 1(10 - 6.65I - 2)^2 \Rightarrow I = 0.99 \text{ mA}$$

$$V_3 = 10 - 6.65 \times 0.99 = 3.41 \text{ V}$$

In circuit c:

$$R = \frac{10 - 4}{2} \approx 3.01 \text{ k}\Omega,$$

$$V_{GS} = -(10 + 3.01I)$$

$$I = \frac{1}{2} \times 1 \times (-10 + 3.01I + 2)^2$$

$$I_D = 1.99 \text{ mA}$$

$$V_4 = 10 - 3.01 \times 1.99 = 4.01 \text{ V}$$

$$V_5 = -10 + 2.5 \text{ k} \times 1.99 = -5.03 \text{ V}$$

In circuit d:

$$R = \frac{2}{2} = 1\text{k} \text{ so } V_7 \text{ is still } 2 \text{ V.}$$

### 5.37

$$a) V_{GS} = -V_1 \cdot \frac{10 \mu A}{2} = \frac{1}{2} \times 0.4 \times 10^3 (V_{GS} - 1)^2 \Rightarrow$$

$$V_{GS} = 1.22 \text{ V} \Rightarrow V_1 = -1.22 \text{ V}$$

$$b) 100 \mu A = \frac{1}{2} \times 0.4 \times 10^3 (V_{GS} - 1)^2 \Rightarrow V_{GS} = 1.71, V_2 = -1.71 \text{ V}$$

$$c) I = \frac{1}{2} \times 0.4 \times (V_{GS} - 1)^2 \Rightarrow V_{GS} = 3.23 \text{ V} \Rightarrow V_3 = -3.23 \text{ V}$$

$$d) I = \frac{1}{2} \times 0.4 \times 10^3 (V_{GS} - 1)^2 \Rightarrow V_{GS} = 1.22 \text{ V} \Rightarrow V_4 = 1.22 \text{ V}$$

$$e) I = \frac{1}{2} \times 0.4 (V_{GS} - V_t)^2 \Rightarrow V_{GS} = 3.24 \text{ V} \Rightarrow V_5 = 3.24 \text{ V}$$

$$f) I = \frac{1}{2} \times 0.4 \times (5 - 100I - 1)^2 \Rightarrow I = 0.045 \text{ mA}, 0.036 \text{ mA}$$

$$V_6 = 5 - 100 \times 0.036 = 1.4 \text{ V}$$

$$g) I = \frac{1}{2} \times 0.4 \times (5 - 1 \times I - 1)^2 \Rightarrow I = 1.38 \text{ mA}$$

$$V_7 = 5 - 1.38 \times 1 = 3.62 \text{ V}$$

$$h) I = \frac{1}{2} \times 0.4 \times (5 - 100 - I)^2 \Rightarrow I = 0.045 \text{ mA}, 0.036 \text{ mA}$$

$$V_8 = -5 + 100 \times 0.036 = -1.4 \text{ V}$$

Note that  $I = 0.045 \text{ mA}$  in circuits h and f is not acceptable, because it results in  $V_{GS} < V_t$  that is not physically possible.

### 5.38

$$a) V_{GS2} = -V_2, I = \frac{V_2 - (-5)}{1\text{k}} = \frac{1}{2} \times 2 \times (-V_2 - 1)^2$$

$$\Rightarrow V_2 + 5 = V_2^2 + 2V_2 + 1 \Rightarrow V_2^2 + V_2 - 4 = 0 \Rightarrow V_2 = 1.55 \text{ V}$$

$$V_2 = -2.56 \text{ V}$$

$V_2 = 1.55 \text{ V}$  is not acceptable because it results in  $V_{GS} < 0$  that is not possible for an NMOS.

$$\text{Therefore } V_2 = -2.56 \text{ V}$$

$$i_{D1} = i_{D2} \Rightarrow \frac{V_2 - (-5)}{1\text{k}} = \frac{1}{2} \times 2(5 - V_1 - 1)^2 \Rightarrow$$

$$2.44 = (4 - V_1)^2 \Rightarrow 4 - V_1 = \pm 1.56 \Rightarrow V_1 = 2.44 \text{ V}$$

$$V_1 = 5.56 \text{ V X}$$

The second answer results in  $V_{GS} = 5.5 - 5.56 < 0$  which is not acceptable. Therefore  $V_1 = 2.44 \text{ V}$

$$b) \frac{10 - V_3}{1\text{k}} = \frac{V_5}{1\text{k}} = i_D \Rightarrow 10 - V_3 = V_5 \quad (1)$$

$$i_{D1} = \frac{V_5}{1\text{k}} = \frac{1}{2} \times 2 \times (V_3 - V_4 - 1)^2 \Rightarrow V_5 = (V_3 - V_4 - 1)^2 \quad (2)$$

$$i_{D2} = \frac{V_5}{1\text{k}} = \frac{1}{2} \times 2 \times (V_4 - V_5 - 1)^2 \Rightarrow V_5 = (V_4 - V_5 - 1)^2 \quad (3)$$

$$(2), (3) \Rightarrow V_3 - V_4 - 1 = V_4 - V_5 - 1 \Rightarrow V_5 = 2V_4 - V_3 \quad (4)$$

$$(1), (4) \Rightarrow 2V_4 - V_3 = 10 - V_3 \Rightarrow V_4 = 5 \text{ V}$$

$$(3) \Rightarrow V_5 = (4 - V_5)^2 \Rightarrow V_5^2 - 9V_5 + 16 = 0 \Rightarrow V_5 = 6.55 \text{ V}$$

$$V_5 = 2.45 \text{ V}$$

$V_5 = 6.55$  results in  $i_D = 6.55 \text{ mA}, V_3 = 4.45 \text{ V}$  and this is not physically possible. So  $V_5 = 2.45 \text{ V}$

$$V_3 = 10 - 2.45 = 7.55 \text{ V}$$

$$0.5 = [(V_{SG} - 1)(V_{SG} - 3) - \frac{1}{2}(V_{SG} - 3)^2]$$

$$0.5 = 0.5V_{SG}^2 - V_{SG} - 1.5$$

$$\Rightarrow V_{SG}^2 - 2V_{SG} - 4 = 0$$

$$V_{SG} = 3.24V, -1.2V \times$$

$$V_{SD} = 3.24 - 3 = 0.24V$$

$$100k\Omega \Rightarrow IR = 100 \times 0.1$$

= 10 V  $\Rightarrow$  triode region

$$100 = 8 \times 25 \times$$

### 5.39

The PMOS transistor operates in saturation region if

$$V_{SD} \geq V_{SG} - |V_t|$$


or

$$V_{SD} \geq V_{SG} - 1$$

$$\text{Also, } V_{SD} + IR = V_{SG} \Rightarrow V_{SD}$$

$$= V_{SG} - IR$$

$\Rightarrow IR \leq |V_t|$  for PMOS to be in saturation.

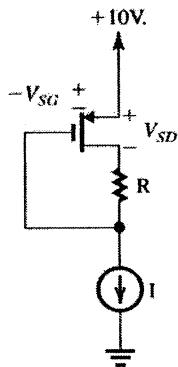

$$\text{a) } R = 0 \Rightarrow IR = 0 < |V_t|$$

saturation:

$$I = 100 = \frac{1}{2} \times 8 \times 2.5$$

$$\times (V_{SG} - |V_t|^2)$$

$$V_{SG} - 1 = \pm 1 \Rightarrow V_{SG} = 2V$$

$$= V_{SD}$$

b)

$$R = 10k\Omega = IR = 10 \times 0.1 = 1V \Rightarrow$$

saturation

$$V_{SG} = 2V \Rightarrow V_{SD} = 2 - 1 = 1V$$

$$\text{c) } R = 30k\Omega \Rightarrow IR = 30 \times 0.1$$

$$= 3V \Rightarrow \text{triode region}$$

$$100 = 8 \times 25$$

$$[(V_{SG} - |V_t|)V_{SD} - \frac{1}{2}V_{SD}^2]$$

### 5.40


a)  $Q_2, Q_1$  operating in Saturation:  $i_{D1} = i_{D2}$

$$\Rightarrow V_{GS1} = V_{GS2}$$

$$3V = V_{GS1} + V_{GS2} \Rightarrow V_{GS1} = V_{GS2} = 1.5V$$

$$V_2 = 1.5V$$
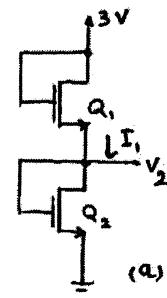
$$I_1 = \frac{1}{2} \times 20 \times \frac{30}{10} (1.5 - 1)^2 = 7.5\mu A$$




b) Both transistors have  $V_D = V_G$  and therefore they are operating in Saturation:  $i_{D1} = i_{D2}$

$$\frac{1}{2} \mu_n C_o \frac{W}{L} (V_4 - 1)^2 = \frac{1}{2} \mu_p C_o \frac{W}{L} (3V - 1)^2$$

$$2.5(V_4 - 1)^2 = (2 - V_4)^2$$

$$1.5V(V_4 - 1) = (2 - V_4) \Rightarrow V_4 = 1.39V \approx 1.4V$$
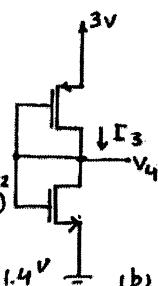
$$I_3 = \frac{1}{2} \times 20 \times \frac{30}{10} (1.39 - 1)^2 = 4.6\mu A$$



$$c) \frac{W_1}{L_1} = \frac{75}{10} = 7.5$$


$$\frac{W_2}{L_2} = \frac{30}{10} = 3 \quad \frac{\frac{W_1}{L_1}}{\frac{W_2}{L_2}} = \frac{7.5}{3} = 2.5$$

$$i_{D1} = i_{D2}$$

$$\text{Since } \mu_n C_o \frac{W_2}{L_2} = \mu_p C_o \frac{W_1}{L_1}$$

$$\Rightarrow V_{GS1} = V_{GS2} = \frac{3}{2} = 1.5V = V_5$$
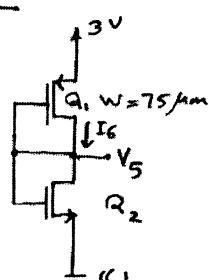
$$I_6 = \frac{1}{2} \times 20 \times \frac{30}{10} (1.5 - 1)^2 = 7.5\mu A$$



### 5.41

Since  $V_{G1} = V_{D1}$  then  $Q_1$  is in saturation. We assume that  $Q_2$  is also in saturation, then because  $I_{D1} = I_{D2}$ ,  $V_{an}$  would be equal to  $V_{GS2}$ .

$$V_{GS1} = V_{GS2} = \frac{5}{2} = 2.5 \text{ V}$$

$$I_1 = \frac{1}{2} \times 50 \times \frac{10}{1}(2.5 - 1)^2 = 562.5 \mu\text{A}$$

$V_{GS3} = V_{GS4} = 2.5 \text{ V}$ . Since  $Q_3$  and  $Q_4$  have the same drain current, then

$V_{GS3} = V_{GS4} = 2.5 \text{ V}$ . This is based on the assumption that  $Q_3$  &  $Q_4$  are saturated:

$$V_{GS3} = V_{GS4} \Rightarrow I_2 = I_{GS3} = I_{GS4}$$

$$= 562.5 \mu\text{A}$$

$$V_2 = 5 - 2.5 = 2.5 \text{ V}$$

Now if  $Q_3$  and  $Q_4$  have  $W = 100 \mu\text{m}$  then:

$$I_2 = \frac{1}{2} \times 50 \times \frac{100}{1}(2.5 - 1)^2 = 5.625 \text{ mA}$$

or

$$\frac{I_{Q3}}{I_{Q1}} = \frac{W_3}{W_1} = \frac{100}{10} \Rightarrow I_{Q3} =$$

$$10 \times 562.5 \mu\text{A} = 5.625 \text{ mA}$$

### 5.42

Part a

Find the  $R_D$  corresponding to point B, which is the saturation-triode boundary with

$$V_{DS,B} = 0.5 \text{ Volts}$$

Also on the boundary

$$i_{D,B} = \frac{\frac{K'}{n} \frac{W}{L} V_{DS,B}^2}{2}$$

$$5 \frac{(0.25 \times 10^{-3})(40)(0.5)^2}{2} = 1.25 \text{ mA}$$

$$R_D = \frac{2.5 - 0.5}{1.25 \times 10^{-3}} = 1600 \Omega$$

Part b

Find  $v_{GS}$  corresponding to point B.

$$V_{DS,B} = 0.5 \Rightarrow V_{GS,B} = V_{GD,B} + V_{DS,B} = V_I + V_{DS,B} = 0.5 + 0.5 = 1.0 \text{ Volts}$$

### Part c

Find  $V_{DS,C}$  corresponding to point C, where  $v_{GS,C} = 2.5 \text{ Volts}$  and the transistor is in the triode region.

$$V_{DS,C} + R_D \left[ k_n \frac{W}{L} \left( (v_{GS,C} - V_I) v_{DS,C} - \frac{v_{DS,C}^2}{2} \right) \right] = V_{DD} \Rightarrow V_{DS,C} + 1600$$

$$\left[ (0.25 \times 10^{-3}) 40 ((2.5 - 0.5) - 0.5 v_{DS,C} - \frac{v_{DS,C}^2}{2}) \right]$$

The roots of this equation are 0.07720 & 4.04778

Clearly the  $v_{GS} \approx 0.07720$  is the choice because the other one is above  $V_{DD}$ .

The current,  $i_D$ , corresponding to point C,  $i_{DS,C}$  is

$$i_{DS,C} = \frac{V_{DD} - V_{DS,C}}{R_D}$$

$$= \frac{2.5 - 0.07720}{1600} = 1.514 \text{ mA}$$

An equivalent resistor value can now be calculated at point C

$$R_{\text{equivalent}} = \frac{V_{DS,C}}{i_{DS,C}} = \frac{0.07720}{1.514 \times 10^{-3}} = 50.98 \Omega$$

This can be compared to the value of  $r_{DS}$ , which is really derived for  $v_{DS} = 0$ .

$$r_{DS} = \frac{1}{k_n \frac{W}{L} (V_{GS} - V_I)}$$

$$= \frac{1}{(0.25 \times 10^{-3})(40)(2.5 - 0.5)} = 50$$

The value is close to the equivalent resistor value, but they are not exactly equal.

Part d

$V_{GS} = 0.8$ , so the transistor is in saturation.

Find  $V_{DS}$ .

$$V_{DS} + R_D \left[ k_n \frac{W}{L} \frac{(v_{GS} - V_I)^2}{2} \right] = V_{DD} \Rightarrow V_{DS}$$

$$+ 1600 \left[ \frac{(0.25 \times 10^{-3}) 40 (0.8 - 0.5)^2}{2} \right] = 2.5$$

$$V_{DS} \approx 1.78 \text{ Volts}$$

The voltage gain is

$$A_V = -k_n \frac{W}{L} (V_{GS} - V_I) R_D = -(0.25 \times 10^{-3})$$

$$(40)(0.8 - 0.5)(1600) = -4.8$$

5.43

a)

$$\text{Point A: } V_{GS} = V_E = 1V, V_{DS} = V_{DD} = 5V$$

For  $V_i < V_E$ , the transistor is not on.  $V_{GS} < V_E$ . Point A is when  $V_{GS} = V_E$  and the transistor turns on. As  $V_i$  increases, the  $i_D$  increases and  $V_o$  decreases.  $V_o$  decreases to the point that it is below  $V_E$  by  $V_t$  Volts. At this point, B, the MOSFET enters the triode region:  $V_{DS} = V_{IB} - V_t$

$$\text{or } V_{DS} = V_{GS} - V_t. \text{ So at point B: } I = \frac{V_{DD} - V_{GS}}{R}$$

$$I = \frac{V_{DD} - (V_{GS} - V_t)}{R} = \frac{1}{2} \times k_n' \frac{W}{L} (V_{GS} - V_t)^2$$

$$\frac{5 - V_{GS} + 1}{24} = \frac{1}{2} \times 1 \times (V_{GS} - 1)^2 \Rightarrow 12V_{GS}^2 - 23V_{GS} + 6 = 0$$

$$V_{GS} = 1.61V \Rightarrow V_I = 1.61V \quad V_o = 1.61 - 1 = 0.61V$$

$$\text{Point B: } V_{OB} = 0.61V \quad V_{IB} = 1.61V$$

$$\text{b) } I_Q = \frac{1}{2} \times 1 \times 0.5^2 = 0.125mA$$

$$V_{OQ} = 5 - 24 \times 0.125 = 2V$$

$$V_{IQ} = V_{GS} = V_{OV} + V_t = 0.5 + 1 = 1.5V$$

Now to calculate the incremental gain

$A_V$  at this bias point, From equation 4.41,

$$\text{we have: } A_V = -2V_{RD}/V_{OV} = \frac{-2(V_{DD} - V_{OQ})}{V_{OV}}$$

$$A_V = \frac{-2(5-2)}{0.5} = -12V/V$$

c)  $V_{IQ} = 1.5V$ ,  $V_t = 1V$ ,  $V_{IB} = 1.61V$ . Thus the largest amplitude of a sine wave that can be applied to the input while the transistor remains in saturation is:  $1.61 - 1.5 = 0.11V$

The amplitude of the output voltage signal that results is approximately equal to  $V_{OQ} - V_{OB} = 2 - 0.61 = 1.39V$ . The gain implied by this amplitudes is:

$$\text{gain} = \frac{1.39}{0.11} = 12.64V/V$$

This gain is 5.3% different from the incremental gain calculated in part(b). This difference is due to the fact that the segment of the voltage transfer curve considered here is not perfectly linear.

5.44

$$R_D = 20k\Omega, V_{RD} = 2V \Rightarrow I_D = 0.1mA$$

$$A_V = -\frac{2V_{RD}}{V_{OV}} \Rightarrow -10 = -\frac{2 \times 2}{V_{OV}} \Rightarrow V_{OV} = 0.4V$$

$$V_{GS} = 1.2V \Rightarrow V_t = 1.2 - 0.4 = 0.8V$$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} V_{OV}^2 \Rightarrow 0.1 = \frac{1}{2} \times 50 \times 10^{-3} \frac{W}{L} \times 0.4^2$$

$$\Rightarrow \frac{W}{L} = 25$$

5.55 the maximum gain achievable is:

$$|A_{vmax}| = \frac{V_{DD}}{(V_{OV}/2)} = \frac{5}{(0.2/2)} = 50 V/V$$

the gain is maximum when  $V_{OV}$  is minimum ( $= 0.2V$ ) and when the drop across  $R_D$  ( $= I_D R_D$ ) is largest possible, which occurs when we operate closest to point B

$$\text{At B: } |V_{DS}| = |V_{GS}|_B - V_t = V_{OV}$$

$$V_{DS}|_B = 0.2$$

to allow for  $\pm 0.5V$  swing

$$V_{DS} = 0.2 + 0.5 = 0.7V$$

$$\rightarrow |A_V| = \frac{(5 - 0.7)}{0.2/2} = 43 V/V$$

$$\Delta V_i \times 43 = \Delta V_O$$

$$\Delta V_i = \frac{\pm 0.5}{43} = \pm 11.6 mV$$

c) If  $I_D = 100 \mu A$ ,

$$k_n' = 100 \mu A/V^2 \Rightarrow \frac{W}{L} = ?$$


$$\text{In saturation: } I_D = \frac{1}{2} k_n' \frac{W}{L} V_{OV}^2 \Rightarrow \frac{W}{L} = \frac{2I_D}{k_n' V_{OV}^2}$$

$$\frac{W}{L} = \frac{2 \times 100 \mu}{100 \mu \times (0.2)^2} = 50$$

$$(d) V_{DD} - I_D R_D = 0.7$$

$$5 - 100 \mu \cdot R_D = 0.7 \Rightarrow R_D = 43 k\Omega$$

5.46

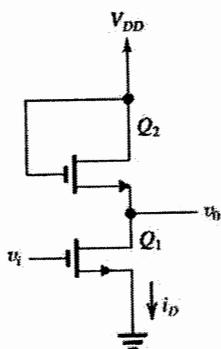

$$\text{given } V_{o1} = V_{o2} = V_o$$

$$\text{for } Q_2 \quad i_D = \frac{1}{2} k_n \left( \frac{W}{L} \right)_2 [V_{DD} - V_o - V_t]^2$$

$$\text{for } Q_1 \quad i_D = \frac{1}{2} k_n \left( \frac{W}{L} \right)_1 [V_t - V_i]^2$$

$$\text{for } V_t \leq V_i \leq V_o + V_t$$

equate  $i_{D1}$  and  $i_{D2}$

$$\left( \frac{W}{L} \right)_2 [V_{DD} - V_o - V_t]^2 = \left( \frac{W}{L} \right)_1 [V_t - V_i]^2$$

$$[V_{DD} - V_o - V_t] = \sqrt{\frac{(W/L)_1}{(W/L)_2}} \cdot [V_t - V_i]$$

$$V_o = V_{DD} - V_t + V_t \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$-V_i \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$\text{for } \sqrt{\frac{(W/L)_1}{(W/L)_2}} = \sqrt{\frac{\left(\frac{50}{0.5}\right)}{\left(\frac{5}{0.5}\right)}} = \sqrt{10}$$

$$A_v = -\sqrt{10} = -3.16$$

5.47

$$I_D = \frac{1}{2} k_n \frac{W}{L} V_{ov}^2 \Rightarrow I_D = \frac{1}{2} \times 2 \times 1^2 = 1 \text{ mA}$$

$$i_D = \frac{1}{2} \times 2 \times (1+0.1)^2 = 1.21 \text{ mA} \quad (V_{gs} = 0.1 \text{ V})$$

$$i_D = 1.21 - 1 = 0.21 \text{ mA}$$

$$\text{If } V_{gs} = -0.1 \text{ V} \Rightarrow i_D = \frac{1}{2} \times 2(1-0.1)^2 = 0.81 \text{ mA}$$

$$i_D = 0.81 - 1 = -0.19 \text{ mA}$$

$$\text{For positive increment: } g_m = \frac{\Delta i_D}{\Delta V_{gs}} = \frac{0.21-1}{0.1} = 2.1 \text{ mA/V}$$

$$\text{For negative increment: } g_m = \frac{0.19}{0.1} = 1.9 \text{ mA/V}$$

$$\text{An estimate of } g_m = \frac{2.1+1.9}{2} = 2 \text{ mA/V}$$


$$g_m = k_n \frac{W}{L} V_{ov} = 2 \times 1 = 2 \text{ mA/V} \text{ (same as estimate)}$$

5.48

$$a) I_D = \frac{1}{2} \times 1 \times (4-2)^2 = 2 \text{ mA}$$

$$V_D = V_{DD} - R_D I_D = 10 - 2 \times 3.6$$

$$V_D = 2.8 \text{ V}$$

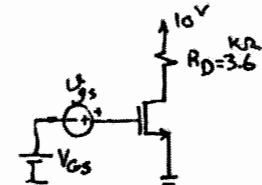

$$b) g_m = k_n \frac{W}{L} V_{ov} = 1 \times (4-2) = 2 \text{ mA/V}$$


$$c) A_v = \frac{V_D}{V_{GS}} = -g_m R_D = -2 \times 3.6 = -7.2 \text{ V/V}$$

$$d) r_o \approx \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 2} = 50 \text{ kΩ}$$

$$A_v = \frac{V_D}{V_{GS}} = g_m (R_D || r_o) = -2(3.6 || 50) = -6.7 \text{ V/V}$$

5.49

$$g_m R_D = 5 \Rightarrow g_m = \frac{5}{50} = 0.1 \text{ mA/V}$$

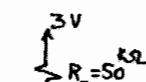

For 0.5V output signal and

$$\text{a gain of } 5 \text{ V/V}, \quad V_{GS} = \frac{0.5}{5} = 0.1 \text{ V}$$

$$\text{So we can write } V_{DS} - 0.5 \geq V_{GS} + 0.1 - V_t$$

$$\text{or } V_{DS} \geq V_{GS} + 0.6 - 0.8 \Rightarrow V_{DS} \geq V_{GS} - 0.2$$

$$\text{Also, from the other side: } V_{DS} + 0.5 \leq V_{DD}$$

$$\text{or } V_{DS} \leq 3 - 0.5 \Rightarrow V_{DS} \leq 2.5 \text{ V}$$

5.50

We design the circuit for lowest possible  $V_{DS}$  that guarantees the device operation in saturation:  $V_{DS} = V_{GS} - 0.2$

$$V_{DS} = V_{DD} - R_D I_D \Rightarrow V_{GS} - 0.2 = 3 - 50 \times I_D$$

$$\Rightarrow I_D = \frac{3 - V_{GS}}{50}$$

Also, From eq. 4.71:  $g_m = \frac{2 I_D}{V_{GS} - V_t} = 0.1$

$$0.1 = \frac{2}{V_{GS} - 0.8} \times \frac{3 - V_{GS}}{50}$$

$$\Rightarrow V_{GS} = 1.49V, I_D = 0.034mA$$

$$V_{DS} = 1.49 - 0.2 = 1.29V \quad V_{OV} = 1.49 - 0.8 = 0.69V$$

$$\frac{W}{L} = \frac{I_D}{\frac{1}{2} K_n V_{OV}^2} = \frac{0.034 \times 10^{-3}}{\frac{1}{2} \times 100 \times 0.69^2} = 1.43$$

$$\underline{\underline{\frac{W}{L} = 1.43}}$$

$$A_V = -g_m R_D, \quad g_m = \frac{2 I_D}{V_{OV}} \quad \text{eq. 4.71} \quad \Rightarrow A_V = -\frac{2 R_D I_D}{V_{OV}} = -\frac{2(V_{DD} - V_t)}{V_{OV}}$$

①

Minimum  $V_{DS}$  for edge of saturation:

$$V_{DS} \geq V_{GS} - V_t \quad \text{or} \quad V_{DSmin} = V_{GSmax} - V_t$$

$$V_{DS} - |A_V| \hat{V}_i = V_{GS} + \hat{V}_i - V_t$$

IF we replace  $A_V$  with ①:

$$V_D - \frac{2(V_{DD} - V_t)}{V_{OV}} \hat{V}_i = V_i + \hat{V}_i$$

$$\Rightarrow V_D \left( 1 + \frac{2 \hat{V}_i}{V_{OV}} \right) = V_{OV} + \hat{V}_i + \frac{2 V_{DD} \hat{V}_i}{V_{OV}}$$

$$V_D = \frac{V_{OV} + \hat{V}_i + 2 V_{DD} (\hat{V}_i / V_{OV})}{1 + 2 (\hat{V}_i / V_{OV})}$$

$$V_{DD} = 3V, \hat{V}_i = 20mV \quad m = 10 = \frac{V_{OV}}{\hat{V}_i} \Rightarrow \frac{V_{OV}}{OV} = 0.2V$$

$$V_D = \frac{0.2 + 0.02 + 2 \times 3 \times 10^{-3}}{1 + 2 \times 0.1} \approx 0.68V$$

$$A_V = \frac{2(3 - 0.68)}{0.2} = -23.2 \frac{V}{V}$$

IF  $I_D = 100 \mu A = 0.1mA$ :

$$A_V = -\frac{2 R_D I_D}{V_{OV}} \Rightarrow 23.2 = \frac{2 \times R_D \times 0.1}{0.2} \Rightarrow$$

$$\underline{\underline{R_D = 23.2 k\Omega}}$$

$$I_D = \frac{1}{2} K_n \frac{W}{L} V_{OV}^2 \Rightarrow 0.1 = \frac{1}{2} \times 100 \times 10^{-3} \frac{W}{L} \times 0.2^2$$

$$\Rightarrow \underline{\underline{\frac{W}{L} = 50}}$$

5.51

Given  $u_n = 500 \text{ cm}^2/\text{Vs}$

$$\mu_p = 250 \text{ cm}^2/\text{Vs} \quad C_{ox} = 0.4 \frac{\text{fF}}{\mu\text{m}^2}$$

$$k'_n = \mu_n C_{ox} = 20 \mu\text{A}/\text{V}^2$$

$$k'_p = 10 \mu\text{A}/\text{V}^2$$

Use equations

$$(5.55) g_m = k' \frac{W}{L} V_{ov}$$

$$(5.56) g_m = \sqrt{2k' \frac{W}{L} I_D}$$

$$(5.57) g_m = \frac{2I_D}{V_{ov}}$$

case type	$I_D$ (mA)	$ V_{os} $	$ V_s $	$ V_a $	$W$ ( $\mu\text{m}$ )	$L$ ( $\mu\text{m}$ )	$\frac{W}{L}$	$k' \frac{W}{L}$ ( $\text{mA}/\text{V}^2$ )	gm(ms)
a(N)	(1)	(3)	(2)	1	100	(1)	100	2	2
b(N)	(1)	1.2	0.7	(0.5)	(50)	0.125	400	8	4
c(N)	(10)	-	-	(2)	250	(1)	250	5	10
d(N)	(0.5)	-	-	(0.5)	-	-	200	4	2
e(N)	(0.1)	-	-	1.41	(10)	(2)	5	0.1	0.141
f(N)	0.1	(1.8)	(0.8)	1	(40)	(4)	10	0.2	0.2
g(P)	(1)	-	-	2	-	-	(25)	*	* See comment
h(P)	1	(3)	(1)	2	-	-	50	(0.5)	1
i(P)	(10)	-	-	1	(4000)	(2)	2000	20	20
j(P)	(10)	-	-	(4)	-	-	125	1.25	5
k(P)	0.05	-	-	(1)	(30)	(3)	10	0.1	0.1
l(P)	(0.1)	-	-	(5)	-	-	0.8	(0.008)	0.04

Note - the circled entries are the givens.


5.52

$$g_m = \sqrt{2k_n' \frac{W}{L} I_D} \Rightarrow \frac{W}{L} = \frac{g_m^2}{2k_n' I_D}$$

$$\frac{W}{L} = \frac{1}{2 \times 50 \times 10^{-3} \times 0.5} \Rightarrow W = 20 \mu m$$

$$g_m = \frac{2 I_D}{V_{ov}} \Rightarrow V_{ov} = \frac{2 \times 0.5}{1} = 1 \Rightarrow V_{GS} = 1 + V_t = 1.7 V$$

5.53

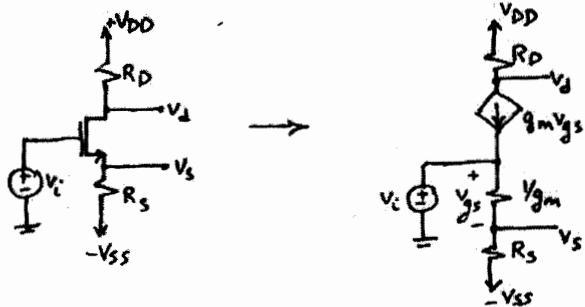

$$\frac{V_d}{V_i} = \frac{R_s}{R_s + \frac{1}{g_m}} = \frac{R_s g_m}{R_s g_m + 1}$$

$$\frac{V_s}{V_i} = \frac{-g_m V_{GS} R_D}{R_s} = -g_m R_D \frac{1/g_m}{1/g_m + R_s} = \frac{-g_m R_D}{1 + g_m R_s}$$

5.54

$$r_0 \approx \frac{V_A}{I_D} = \frac{50}{0.5} = 100 k\Omega$$

$$g_m = \frac{2 I_D}{V_{GS} - V_t} \Rightarrow V_{GS} = V_{DS} = 2 V$$

$$g_m = \frac{2 \times 0.5}{2 - 0.9} = 0.91 \text{ mA/V}$$

$$\frac{V_o}{V_i} = -g_m (r_0 \parallel R_L) = -0.91 (100 k\Omega \parallel 10 k\Omega) = -8.3 V$$

For I=1mA or twice the current:

$$\frac{I_{D1}}{I_{D2}} = \frac{(V_{GS} - V_t)^2}{(V_{GS2} - V_t)^2} \Rightarrow V_{GS2} = V_t + \sqrt{2} (V_{GS1} - V_t)$$

5.55

$$NMOS: g_m = \sqrt{2 k_n' \frac{W}{L} I_D} = \sqrt{2 \times 90 \times 10^{-3} \times \frac{20}{2} \times 0.1} = 0.42 \text{ mA}$$

$$r_o = \frac{|V_A|}{I_D} = \frac{8 \times 2}{0.1} = 160 \text{ k}\Omega$$

$$X = \frac{Y}{2\sqrt{2k_n' + |V_{SB}|}} = \frac{0.5}{2\sqrt{2 \times 0.34 + 1}} = 0.2$$

$$g_{mb} = X g_m = 0.2 \times 0.42 = 0.084 \text{ mA/V}$$

$$g_m = \frac{2 I_D}{V_{ov}} \Rightarrow V_{ov} = \frac{2 \times 0.1}{0.42} = 0.48 V$$

$$PMOS: g_m = \sqrt{2 \times 30 \times 10^{-3} \times \frac{20}{2} \times 0.1} = 0.24 \text{ mA/V}$$

$$r_o = \frac{|V_A|}{I_D} = \frac{12 \times 2}{0.1} = 240 \text{ k}\Omega$$

$$X = 0.2 \Rightarrow g_{mb} = 0.2 \times 0.24 = 0.048 \text{ mA/V}$$

$$V_{ov} = \frac{2 \times 0.1}{0.24} = 0.83 V$$

5.56

$$V_t = 1 V, k_n' = \frac{W}{L} = 2 \text{ mA/V}^2$$

$$(a) \text{ dc analysis } V_G = \frac{5}{15} \times 15 V = 5 V, \text{ assume}$$

$$I_D = 1 \text{ mA}$$


$$V_S = 3 V, V_{GS} = 2 V, V_{ov} = 1 V.$$

$$I_D = \frac{1}{2} k' V_{ov}^2 = 1 \text{ mA} \text{ (check)}$$


$$V_D = V_{DD} - I_D R_D = 7.5 V.$$

$$(b) r_0 = \frac{V_A}{I_D} = \frac{100 V}{1 \text{ mA}} = 100 \text{ k}\Omega$$
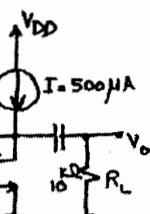
$$g_m = \sqrt{2 k_n' I_D} = 2 \text{ mS}$$



(c)

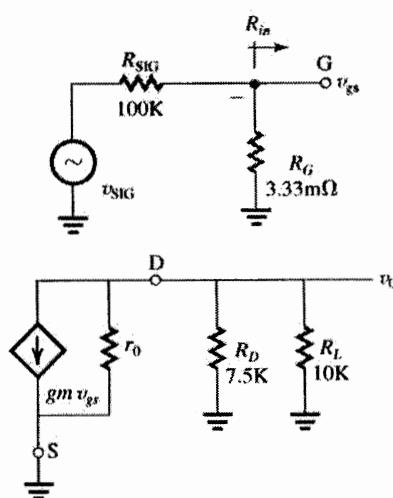


$$(d) R_{in} = R_G = 3.33 \text{ M}\Omega$$

$$\frac{v_{gs}}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} = 0.97$$

$$\frac{v_0}{v_{gs}} = -g_m(r_o \| R_D \| R_L) = -8.2$$

$$\frac{v_0}{v_{sig}} = -8.0$$

5.57

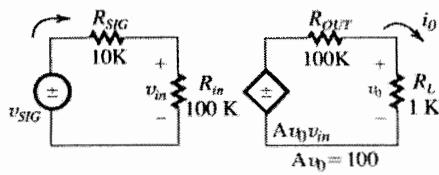


$$G_v = \frac{v_0}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} A_{V0} \frac{R_L}{R_{out} + R_L}$$

$$= 82.6$$

$$A_i = \frac{i_g}{i_i} = \frac{v_0}{v_{sig}} \quad \frac{R_{SIG} + R_{in}}{R_L} = 9090$$


5.58

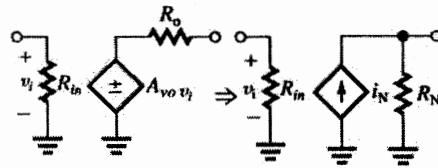

$$\text{Where } i_N = \text{Norton's current source} = \frac{A_{VD} V_I}{R_o}$$


and  $R_N = R_o$  this is equivalent to Fig. P5.82
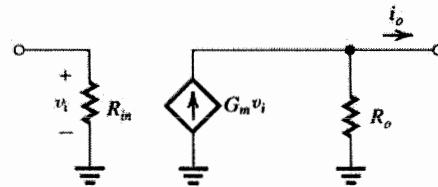
$$\text{where } G_m = \frac{A_{vo}}{R_o}$$



If the output is shorted,  $i_o = G_m V_i$  or

$$G_m = \frac{i_o}{V_i} \Big|_{R_L = 0} \quad \text{with a signal source and load connected,}$$

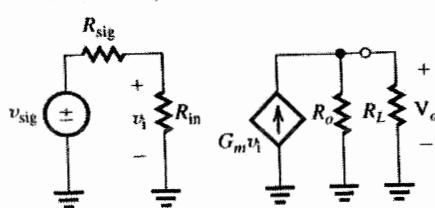


$$\text{by voltage division, } V_i = \frac{V_{sig} R_{in}}{R_{in} + R_{sig}}$$

since  $V_o = G_m V_i (R_o \parallel R_L)$ , substitution for  $V_i$  yields

$$V_o = \frac{V_{sig} R_{in}}{R_{in} + R_{sig}} \cdot G_m (R_o \parallel R_L), \text{ so that}$$

$$G_V = \frac{V_o}{V_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} G_m (R_o \parallel R_L)$$

5.59

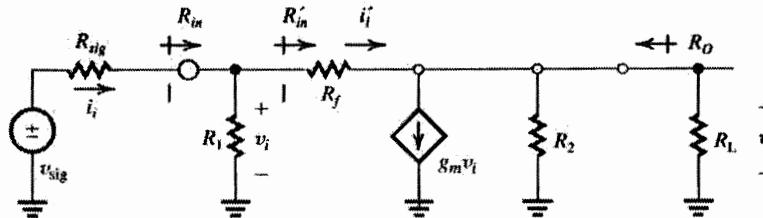

$$\text{note } R_{in} = R_1 \parallel R_{in}'$$

$$R_L' = R_2 \parallel R_L$$

$$\begin{aligned} v_o &= v_i = \frac{R_L'}{R_f + R_L'} - g_m v_i (R_f \parallel R_L') \\ &= v_i \left[ \frac{R_L' - g_m R_f R_L'}{R_f + R_L'} \right] = v_i \frac{R_L' (1 - g_m R_f)}{R_L' + R_f} \\ A_{vo} &= \left| \frac{v_o}{v_i} \right| = \frac{R_2 (1 - g_m R_f)}{R_2 + R_f} = -g_m R_2 \\ &\frac{\left( 1 - \frac{1}{g_m R_f} \right)}{1 + \frac{R_2}{R_f}} \end{aligned}$$

$$i_i' = \frac{v_i - v_o}{R_f} = \frac{v_i}{R_f} \left[ 1 - \frac{R_L' (1 - g_m R_f)}{R_L' + R_f} \right]$$

$$R_L' = R_2 \quad (R_L \rightarrow \infty)$$

$$\begin{aligned} \frac{i_i'}{v_i} &= \frac{1}{R_{in}'} = \frac{1}{R_f} \frac{R_f + R_L' - R_L' + g_m R_f R_L'}{R_f + R_L'} \\ &= \frac{1 + g_m R_L'}{R_f + R_L'} \end{aligned}$$


$$R_{in}' = \frac{R_f + R_L'}{1 + g_m R_L'} = \frac{R_f + R_2 \parallel R_L}{1 + g_m (R_2 \parallel R_L)}$$

$$R_{in} = R_1 \parallel R_{in}' = R_1 \parallel \frac{R_f + R_2 \parallel R_L}{1 + g_m (R_2 \parallel R_L)}$$

Output resistance assuming  $R_{ss} = 0$

$$R_O = R_2 \parallel R_f \approx R_2$$

Output resistance including  $R_{ss}$

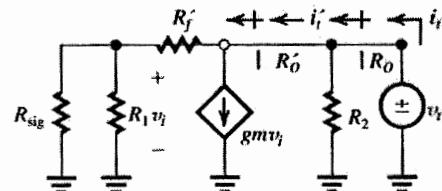

$$R_L' = R_1 \parallel R_{sig}$$

$$i_f' = \frac{v_t}{R_1 + R_f} + g_m v_t \frac{R_1'}{R_1 + R_f}$$

$$v_t = \frac{1 + g_m R_L'}{R_1 + R_f}$$

$$R_O' = \frac{R_1' + R_f}{1 + g_m R_L'}$$

$$R_O = R_2 \parallel R_O' = R_2 \parallel \frac{(R_1 \parallel R_{sig}) + R_f}{1 + g_m (R_1 \parallel R_{sig})}$$

Evaluate for

$$R_1 = 100 \text{ k}\Omega, R_f = 1 \text{ m}\Omega, g_m = 100 \text{ mA/V}$$

$$R_2 = 100 \Omega, R_L = 1 \text{ k}\Omega \quad (R_{sig} \text{ assumed } \phi)$$

$$R_{in} = 49.8 \text{ k}\Omega$$

$$A_{vo} = -10.0$$

$$R_O = 100 \Omega$$

$R_{in}$  is out in half by  $R_f$ .

Given  $R_{sig} = 100 \text{ k}\Omega, R_f \rightarrow \infty$ , and

$$R_f = 1 \text{ m}\Omega$$

$$G_V = \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} \left( -g_m R_L \frac{1 - \frac{1}{g_m R_f}}{1 + \frac{R_L'}{R_f}} \right)$$

$$G_V = -4.55 \quad (R_f \rightarrow \infty), G_V = -3.02$$

$$(R_f = 1 \text{ m}\Omega)$$

5.60

$R_{in}$  = depends on biasing

$$\begin{aligned} A_{vo} &= -g_m(r_o \parallel R_D) \\ &= -0.4 \frac{\text{mA}}{V} (50 \text{ k}\Omega \parallel 6 \text{ k}\Omega) \\ &= -2.14 \text{ V/V} \\ r_o &= \frac{V_A}{I_D} = \frac{10\text{V}}{0.2 \text{ mA}} = 50 \text{ k}\Omega \end{aligned}$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = 0.4 \text{ mA/V}$$

$$R_o = r_o || R_D = 50 \text{ k}\Omega || 6 \text{ k}\Omega = 5.36 \text{ k}\Omega$$


WITH  $R_L=10 \text{ k}\Omega$  and assuming losses due to source impedance are negligible

$$\begin{aligned} G_v &= A_v = -g_m(r_o \parallel R_D \parallel R_L) \\ &= -0.4 \frac{\text{mA}}{V} (5.36 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = -1.40 \text{ V/V} \end{aligned}$$

For a 0.2V peak output, the input must be

$$\frac{0.2\text{V}}{1.4} = 0.143 \text{ V peak}$$

5.61

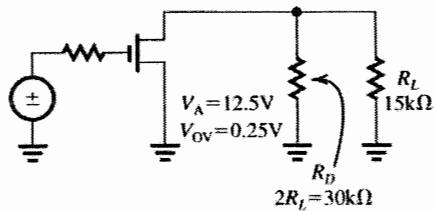

$$\text{a)} g_m r_o = ? \quad g_m = \frac{2I_D}{V_{ov}} \text{ and } r_o = \frac{V_A}{I_D}$$

$$g_m r_o =$$

$$\frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} = \frac{2V_A}{V_{ov}} = \frac{2 \cdot 12.5}{0.25} = 100$$

b) If  $Gv = -10 \text{ V/V}$ ,

$$R_L = 15 \text{ k}\Omega, R_D = 2R_L = 30 \text{ k}\Omega.$$

what is gm?

$$Gv = A_v = -g_m(R_D \parallel \infty \parallel R_L)$$

$$-10 \text{ V/V} = -g_m(30 \text{ k} \parallel 15 \text{ k}) = -g_m \cdot 10 \text{ k}$$

$$gm = \frac{1 \text{ mA}}{\text{V}}$$

therefore:

$$I_D = \frac{V_{ov}}{2} \cdot gm = \frac{0.25 \text{ V} \cdot 1 \text{ mA/V}}{2} = 0.125 \text{ mA.}$$

c) If  $R_D = R_L$

$$\Rightarrow Gv = -g_m \cdot \frac{R_L}{2} = \frac{-1 \text{ mA}}{V} \cdot 7.5 \text{ K}$$

$$Gv = -7.5 \text{ V/V}$$

5.62

$$Gv = Av = -g_m(R_D \parallel R_L \parallel r_o)$$

$$\text{if } R_D \parallel R_L = \infty \Rightarrow Gv = -g_m r_o$$

$$\text{since } g_m = \frac{2I_D}{V_{ov}} \text{ and } r_o = \frac{V_A}{I_D}$$

$$Gv = \frac{-2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} = \frac{-2V_A}{V_{ov}}$$

5.63

$$g_m = 5 \text{ mS}$$

$$i_d = g_m v_{gs} = \frac{g_m}{1 + g_m R_s} v_g$$

$$\frac{g_m}{1 + g_m R_s} = 1 \text{ mS}$$

$$\therefore R_s = \frac{4}{g_m} = 800 \Omega$$

5.64

$$R_s = 1 \text{ k}\Omega$$

$$\frac{-g_m R'_L}{1 + g_m R_s} = -15$$

$$-g_m R'_L = -30$$

$$\therefore g_m = \frac{1}{R_s} = 1 \text{ ms}$$


$$\text{for } A_v = -10, \text{ let } R_s = \frac{2}{g_m} = 2 \text{ k}\Omega$$

5.65


$$R_{in} = \frac{1}{g_m} = 250\Omega$$

$$Gv = \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} g_m (R_D \parallel R_L) = +3.3$$

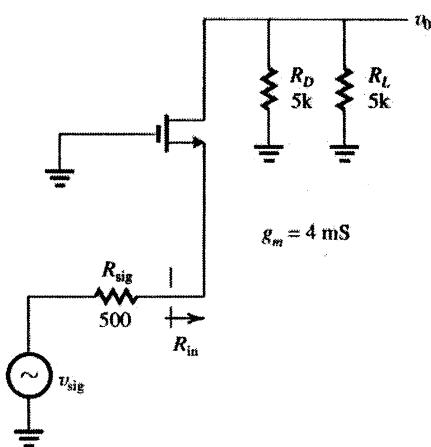$g_m = \sqrt{2k_n I_D}$ , so for  $\frac{1}{g_m} = R_{sig} g_m$  must decrease to 1/2, and  $I_D$  must decrease to 1/4



5.66

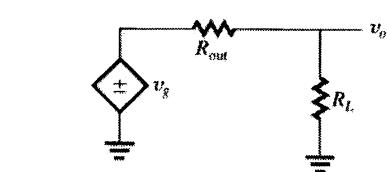

$$1K < R_L < 3K$$

$$R_{L, nom} = 2K$$

for  $R_{L, min}$

$$\frac{R_{L, min}}{R_{L, min} + R_{out}} \geq (0.80) \frac{R_{L, nom}}{R_{L, nom} + R_{out}}$$

$$\frac{1K}{1K + R_{out}} \geq \frac{1.6K}{2K + R_{out}}$$

$$2K^2 + 1KR_{out} \geq 1.6K^2 + 1.6KR_{out}$$

$$400 \geq 0.6R_{out}$$

$$R_{out} \leq 667\Omega$$

for  $R_{L, max}$

$$\frac{R_{L, max}}{R_{L, max} + R_{out}} \leq (1.20) \frac{R_{L, nom}}{R_{L, nom} + R_{out}}$$

$$\frac{3K}{3K + R_{out}} \leq \frac{2.4K}{2K + R_{out}}$$

$$R_{out} \leq 2 k\Omega$$

Therefore  $R_{L, min}$  is the ruling case and

$$R_{out} \leq 667\Omega$$

$$g_m = \sqrt{2k_n I_D} \geq \frac{1}{667\Omega}$$

$$k_n = 16mA/V^2$$

$$\therefore I_D \geq 70 \mu A$$

$$V_{ov} = \frac{2I_D}{g_m} = 0.093V.$$

5.67

Source Follower

$$|v_{gs}| \leq 50mV$$

$$|v_o| \leq 0.5V$$

$$R_L = 2k\Omega$$

$$v_o = g_m v_{gs} R_L \Rightarrow g_m \geq \frac{500mV}{50mV} \frac{1}{2k\Omega} = 5mS$$

For low distortion, keep

$$|v_{gs}| < 0.2 V_{ov} \Rightarrow V_{ov} = 0.25V.$$

$$\therefore I_D \geq \frac{g_m V_{ov}}{2} = 0.625mA$$

$$i_{D, peak} = \frac{500mVpk}{2k\Omega} = 250\mu Apeak$$

$$i_{D, max} = 0.625 mA + 250 \mu A = 0.875 mA$$

$$i_{D, min} = 0.625 mA - 250 \mu A = 0.375 mA$$

$$v_{sig} = v_{gs} + v_o = 550mVpk$$

5.68

$$I_D = 2 \text{ mA} = \frac{1}{2} \times 80 \times 10^{-3} \times \frac{2.4}{8} \times (V_{GS} - 1.2)^2 \Rightarrow$$

$$V_{GS} = 2.32 \text{ V}$$

$$R_D I_D = \frac{15}{3} = 5 \text{ V} \Rightarrow R_D = \frac{5}{2.2} = 2.5 \text{ k}\Omega$$

$$R_S I_D = 5 \text{ V} \Rightarrow R_S = \frac{5}{2} = 2.5 \text{ k}\Omega$$

$$V_G = 5 + V_{GS} = 7.32 \text{ V}$$

$$\frac{15}{R_{G1} + R_{G2}} \times R_{G2} = 7.32 \quad R_{G1} = 22 \text{ M}\Omega \Rightarrow R_{G2} = 20.97 \text{ k}\Omega$$

$$V_{DS} = 5 \text{ V}$$

at the edge of saturation  $V_{DS} = V_{GS} - V_t$  or

$$V_{DS} = 2.32 - 1.2 = 1.12 \text{ V}. \text{ So } V_{DS} \text{ is } 5 - 1.12 = 3.88 \text{ V}$$

away from the edge of saturation.

5.69

$$I_D = 2 \text{ mA} = \frac{1}{2} K_n \frac{W}{L} V_{OV}^2 \Rightarrow 2 = \frac{1}{2} \times 50 \times 10^{-3} \times \frac{200}{4} V_{OV}^2$$

$$V_{OV} = 1.26 \text{ V}$$

$$V_{DS} = V_{OV} \text{ edge of triode}$$

Midway of cutoff ( $V_{DS} = V_{DD}$ ) and beginning of triode operation ( $V_{DS} = V_{OV}$ ) is when  $V_{DS} = \frac{30 + 1.26}{2}$

$$V_{DS} = 15.63 \text{ V}$$

$$V_{GS} = 2.32 \text{ V} \Rightarrow V_S = -2.32 \text{ V} \Rightarrow R_S = \frac{-2.32 + 15}{2}$$

$$R_S = 6.34 \text{ k}\Omega$$

$$V_D = V_S + V_{DS} = -2.32 + 15.63 = 13.31 \text{ V} \Rightarrow R_D = \frac{15 - 13.31}{2}$$

$$R_D = 0.85 \text{ k}\Omega$$

5.70

$$V_G = 12 \times \frac{2.2}{2.2 + 5.6} = 3.4 \text{ V}$$

$$K_n \frac{W}{L} = 220 \text{ to } 380 \text{ mA/V}^2$$

$$V_t = 1.3 \text{ to } 2.4 \text{ V}$$

$$I_D = \frac{1}{2} \times K_n \frac{W}{L} (3.4 - V_t)^2$$

$$I_{Dmin} = \frac{1}{2} \times 220 (3.4 - 2.4)^2 = 110 \text{ mA}$$

$$I_{Dmax} = \frac{1}{2} \times 380 (3.4 - 1.3)^2 = 838 \text{ mA}$$

to limit  $I_{Dmax}$  to 150 mA:

$$150 = \frac{1}{2} \times 380 (3.4 - 0.15 R_S - 1.3)^2$$

$$R_S = 8.1 \text{ k}\Omega$$

Select  $R_S = 8.2 \text{ k}\Omega$

$$I_{Dmax} = \frac{1}{2} \times 380 \times (3.4 - I_{Dmax} \times 8.2 - 1.3)^2$$

$$I_{Dmax} = 0.15 \text{ mA} \text{ or } 0.94 \text{ mA}$$

The second answer results in negative  $V_{GS}$

and therefore it is not acceptable.

$$I_{Dmin} = \frac{1}{2} \times 0.22 \times (3.4 - 8.2 I_{Dmin} - 2.4)^2$$

$$I_{Dmin} = 0.04 \text{ mA}$$

5.71

$$V_t = 2 \text{ V}, K_n \frac{W}{L} = 2 \text{ mA/V}^2$$

$$I_D = \frac{1}{2} \times 2 \times (4 - I_D \times 1 - 2)^2$$

$$I_D = 4 + I_D^2 - 4I_D \Rightarrow I_D = 1 \text{ mA}, 4 \text{ mA}$$


$$I_D = 4 \text{ mA} \text{ results in } V_{GS} = 0 \text{ which}$$

is not acceptable, therefore  $I_D = 1 \text{ mA}$ .

For  $K_n \frac{W}{L}$  50% larger, i.e.  $K_n \frac{W}{L} = 3 \text{ mA/V}^2$

$$I_D = \frac{1}{2} \times 3 (4 - I_D \times 1 - 2)^2 \Rightarrow I_D = 1.13 \text{ mA}$$

$I_D$  increases by 13%.

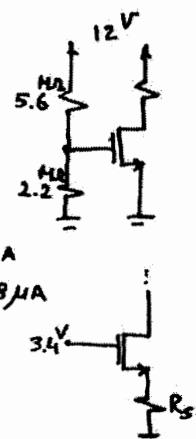

5.72

$$V_{GS} = 5 - 2 = 3V \Rightarrow I_D = \frac{V_S}{R_S} = \frac{2}{1} = 2mA$$

$$I_D = 2 = \frac{1}{2} \times 2 \times (3 - V_t)^2 \Rightarrow 1.41 = 3 - V_t \Rightarrow V_t = 1.59V$$

For a device with  $V_t = 1.59 - 0.5 = 1.09V$ :

$$I_D = \frac{1}{2} \times 2 \times (5 - I_D \times 1 - 1.09)^2 \Rightarrow I_D = 2.37mA$$

$$V_S = 2.37V$$

$$\frac{\partial I_D}{\partial K} = \frac{I_D}{K} - 2R_S \sqrt{\frac{I_D}{K}} K \frac{\partial I_D}{\partial k}$$

$$\frac{\partial I_D}{\partial K}(1 + 2\sqrt{KI_D} R_S) = \frac{I_D}{K} \Rightarrow$$

$$S_k^{I_D} = \frac{\partial I_D}{\partial K} \frac{K}{I_D} = \frac{1}{1 + 2\sqrt{KI_D} R_S}$$

$$b) K = 100 \mu A/V^2, \frac{\Delta K}{K} = \pm 10\%,$$

5.73

To maximize gain, we design for the lowest possible  $V_D$  constant with allowing a 2V p-p signal swing.  $V_{Dmin} = V_D - 1$

$$V_{Dmin} = V_G - V_t = 0 - 2$$

$$V_D - 1 = -2 \Rightarrow V_D = -1V \Rightarrow R_D = \frac{10 - (-1)}{1mA} = 11k\Omega$$


$$I_D = \frac{1}{2} \times 2 [0 - (-1 + 1 \times R_S) - 2]^2 = 1 \Rightarrow 1 = (8 - R_S)^2$$

$$R_S = 7k\Omega$$



5.74

$$k = \frac{1}{2} k' \frac{W}{L}$$

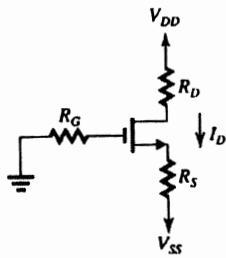

$$a) I_D = \frac{1}{2} k' \frac{W}{L} (V_{GS} - V_t)^2$$

$$I_D = K(0 + V_{SS} - R_S I_D - V_t)^2$$

$$\frac{\partial I_D}{\partial K} = (V_{SS} - R_S I_D - V_t)^2 +$$

$$+ 2K(V_{SS} - R_S I_D - V_t)(-R_S) \frac{\partial I_D}{\partial k}$$

$$V_t = 1V, I_D = 100 \mu A$$

$$\frac{\Delta I_D}{I_D} = \pm 1\%$$

$$S_k^{I_D} = \frac{\partial I_D}{\partial k} \frac{K}{I_D} = \frac{1}{10} = 0.1$$

$$= \frac{1}{1 + 2\sqrt{100 \times 10^{-6} \times 100 \times 10^{-6} \times R_S}}$$

$$\Rightarrow R_S = 45 k\Omega$$

Now find  $V_{GS}$  and  $V_{SS}$  when  $I_D = 100 \mu A$  and  $K = 100 \mu A/V^2$ :  $100 = 100(V_{GS} - 1)^2$

$$\Rightarrow V_{GS} = 2V$$

$$\text{Also } V_{GS} = V_{SS} - I_D R_S$$

$$2 = V_{SS} - 100 \times 10^{-6} \times 45 \times 10^3$$

$$\Rightarrow V_{SS} = 6.5V$$

C. For  $V_{SS} = 5V$

$$R_S = \frac{-V_{GS} + V_{SS}}{I_D}$$

$$= \frac{-2 + 5}{100 \times 10^{-6}} = 30 k\Omega$$

$$S_k^{I_D} = \frac{1}{1 + 2\sqrt{100 \times 10^{-6} \times 100 \times 10^{-6} \times R_S}} \\ = 0.14$$

$$\therefore \text{For } \frac{\Delta K}{K} = \pm 10\%, \frac{\Delta I_D}{I_D} = \pm 1.4\%$$

5.75

Both cases are in saturation region, because

$$V_{DG} > V_E.$$

$$V_D = 10 - 5 \times 1 = 5 \text{ V}$$

$$\text{a) } I = \frac{1}{2} \times 0.5 \times (V_{GS} - 1)^2 \Rightarrow V_{GS} = 3 \text{ V}, V_S = -3 \text{ V}$$

$$V_{DS} = 8 \text{ V}$$

$$\text{b) } I = \frac{1}{2} \times 1.25 \times (V_{GS} - 2)^2 \Rightarrow V_{GS} = 3.3 \text{ V}, V_S = -3.3 \text{ V}$$


$$V_{DS} = 8.3 \text{ V}$$

5.76

$$V_D = V_G = V_{GS}$$

$$V_{DS} \geq V_{GS} - V_t \Rightarrow V_{DG} \geq -V_t$$

$$V_{DG} = 0$$

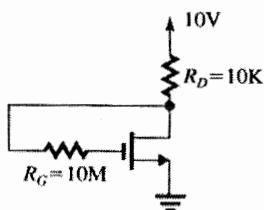

$$\text{a) } \frac{10 - V_D}{10} = \frac{1}{2} \times 0.5 \times (V_D - 1)^2$$

$$\Rightarrow V_D = 2.7 \text{ V}$$

$$V_G = 2.7 \text{ V}$$

$$\text{b) } \frac{10 - V_D}{10} = \frac{1}{2} \times 1.25 \times (V_D - 2)^2$$

$$\Rightarrow V_D = 3.05 \text{ V}$$

$$V_G = 3.05 \text{ V}$$

For a given  $V_D$ ,  $I_D$  is constant.

5.77

For  $I_D = 0.2 \text{ mA}$ :


$$0.2 = \frac{1}{2} \times 0.4 \times (V_{GS} - 1)^2$$

$$V_{GS} = 2 \text{ V}, V_D = V_G = V_{GS} = 2 \text{ V}$$

$$R_D = \frac{9-2}{0.2} = 35 \text{ k}\Omega$$

$$\text{Select } R_D = 36 \text{ k}\Omega \Rightarrow \frac{9-V_D}{R_D} = \frac{1}{2} \times 0.4(V_D - 1)^2$$
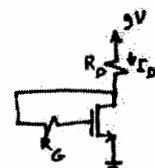
$$\frac{9-V_D}{36} = 0.2(V_D - 1)^2 \Rightarrow V_D = 2 \text{ V}, I_D = 0.21 \text{ mA.}$$



5.78

$$I_D = 2 = \frac{1}{2} \times 3.2 \times (V_{GS} - 1.2)^2$$

$$V_{GS} - 1.2 = 1.12 \Rightarrow V_{GS} = 2.32 \text{ V}$$

$$V_G = 2.32 \text{ V}$$


$$V_{DS\min} = V_{GS} - V_t = 1.12 \text{ V}$$

$$V_{DS} = V_{DS\min} + 2 = 3.12 \text{ V}$$

$$R_{G2} = 22 \text{ M}\Omega \Rightarrow I = \frac{2.32}{22} = 0.11 \mu\text{A}$$

$$R_{G1} = \frac{3.12 - 2.32}{0.11} = 7.58 \text{ M}\Omega$$
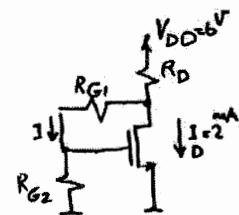
$$R_D = \frac{6 - 3.12}{2 + 0.11 \times 2} = 1.44 \text{ k}\Omega$$



5.79

a)

$$A_{vo} = -2 \frac{(V_{DD} - V_D)}{V_{OV}} = -2 \frac{(10 - 2.5)}{1} = -15 \text{ V/V}$$

b) if  $V_{OV}$  is halved ( $V_{OV} = 0.5$ ) then  $I_D$  is divided

$$\text{by 4, i.e. } I_D = \frac{0.5}{4} = 0.125 \text{ mA}$$

Since  $V_D$  is kept unchanged at 2.5 V then:

$$R_D = \frac{10 - 2.5}{0.25} = 60 \text{ k}\Omega,$$

$$g_m = \frac{2I_D}{V_{OV}} = 0.5 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} \Rightarrow r_o = 4 \times r_{o1} = 4 \times \frac{75}{0.5} = 600 \text{ k}\Omega$$

$$A_{vo} = -15 \times 2 = -30 \text{ V/V (without } r_o)$$

c) If we take  $r_o$  into account :

$$A_{vo} = -g_m(r_o \parallel R_D) = -0.5(600^k \parallel 60^k) \\ = -27.3 \text{ V/V}$$

$$R_{out} = R_D \parallel r_o = 600^k \parallel 60^k = 54.5 \text{ k}\Omega$$

d)  $R_{in} = R_G = 4.7 \text{ M}\Omega$

$$R_o = 54.5 \text{ k}\Omega$$

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_L}{R_L + R_o} \\ = \frac{4.7}{4.7 + 0.1} \times 27.3 \times \frac{15}{15 + 54.5}$$

$$G_v = 5.77 \text{ V/V}$$


e) As we can see by reducing  $V_{OV}$  to half of its value or equivalently multiplying drain current by 4,  $A_{vo}$  is almost doubled, while  $R_{out}$  is multiplied by 4.

As a result  $G_v$ , which is proportional to both

$A_{vo}$  and  $\frac{1}{R_{out}}$  is only slightly reduced.

( $G_v$  was -7 V/V before and it is 5.8 V/V now)

5.80

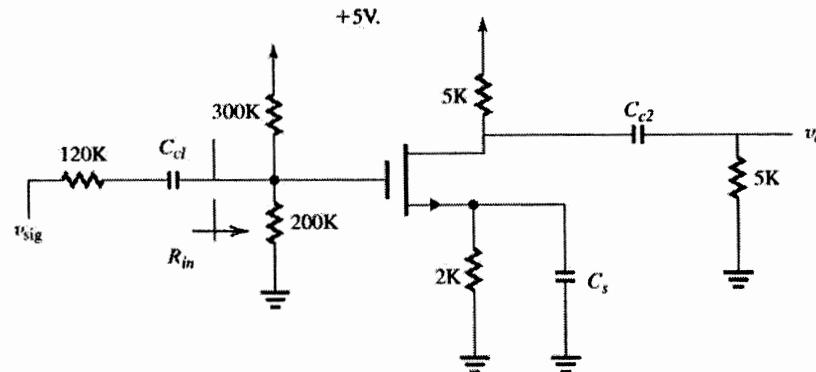

$$V_{gd} + V_{GD} = \hat{v}_o + \frac{\hat{v}_0}{8.12} - 0.5$$

$$\leq V_t = 0.7 \text{ V.}$$

$$\hat{v}_o \text{ max} = 1.07 \text{ V}_{\text{pk}}$$

$$\therefore \hat{v}_g \text{ max} = \frac{\hat{v}_o \text{ max}}{8.12} = 132 \text{ mV}_{\text{pk}}$$

$$\hat{v}_{sig, \text{ max}} = \frac{\hat{v}_o \text{ max}}{4.1} = 261 \text{ mV}_{\text{pk}}$$

$$\text{d) Add } R_S = \frac{I}{g_m} = 300 \Omega,$$

$$\text{then } v_{gs} = \frac{v_g}{1 + g_m R_s} = \frac{v_g}{2}$$

$$\frac{g_m R'_L}{1 + g_m R_S} = \left| \frac{v_o}{v_g} \right| = 4.06$$

$$\hat{v}_o + \frac{\hat{v}}{4.06} - 0.5 \leq 0.7 \text{ V.}$$

$$\Rightarrow \hat{v}_o \text{ max} = 0.96 \text{ V.}$$

$$V_t = 0.7 \text{ V.}$$

$$V_A = 50 \text{ V.}$$

$$\text{a) with } I_D = 0.5 \text{ mA}$$

$$V_G = +2 \text{ V} - V_S + 1 \text{ V.} \quad V_{GS} = +1 \text{ V.}$$

$$V_{ov} = 0.3 \text{ V}$$

$$0.5 \text{ mA} = \frac{1}{2} k_n V_{ov}^2 \Rightarrow k_n = 11.1 \frac{\text{mA}}{\text{V}^2}$$

$$V_D = 5 - (5 \text{ K})(0.5 \text{ mA}) = +2.5 \text{ V.}$$

$$V_{GD} = -0.5 \text{ V} < V_t \therefore \text{Saturation}$$

$$\text{b) } R_{in} = 200 \text{ K} \parallel 300 \text{ K} = 120 \text{ k}\Omega$$

$$G_V = \frac{v_2}{v_{sig}} = -\frac{R_{in}}{120 \text{ K} + R_{in}} g_m$$

$$(5 \text{ K} \parallel r_o \parallel 5 \text{ K})$$

$$g_m = \frac{2I_D}{V_{ov}} = 3.33 \text{ mS}$$


$$r_o = \frac{V_A}{I_D} = 100 \text{ k}\Omega$$

$$G_V = -4.1$$

$$\text{c) } v_{sig} = \hat{v}_{sig} \sin \omega t$$

$$g_m(5 \text{ K} \parallel 5 \text{ K} \parallel 100 \text{ K}) = 8.12$$

5.81

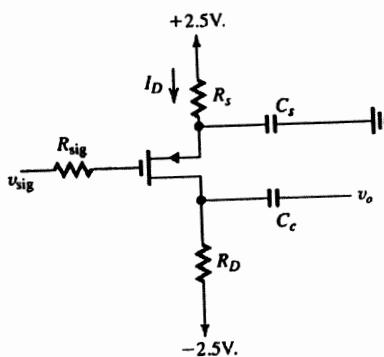

$$V_{ip} = -0.7V, \quad V_A \rightarrow \infty$$

$$\text{a) for } I_D = 0.3 \text{ mA, } |V_{ov}| = 0.3 \text{ V.}$$

$$V_{SG} = 1.0 \text{ V.}, \quad V_G = 0$$

$$V_S = 2.5 - I_D R_S = 1.0 \text{ V.}$$

$$\therefore R_S = 5.0 \text{ k}\Omega$$

$$\text{b) } g_m = \frac{2I_D}{V_{ov}} = 2 \text{ mS}$$

$$G_V = \frac{v_o}{v_{sig}} = -g_m R_D = -10$$

$$\therefore R_D = 5.0 \text{ k}\Omega$$

$$\text{c) } v_{gd} + V_{GD} \geq V_{ip} = -0.7$$

$$-\left| \hat{v}_o + \frac{\hat{v}_o}{10} \right| + 1 \text{ V.} \geq -0.7$$

$$\hat{v}_o \leq 1.55 \text{ V}_{pk}$$

$$\hat{v}_{sig} \leq \frac{\hat{v}_o \max}{10} = 0.155 \text{ V}_{pk}$$

$$\text{d) for } \hat{v}_{sig} = 50 \text{ mV, changed } R_D$$

$$-\left| \hat{v}_o + \frac{\hat{v}_o}{g_m R_D} \right| + (2.5 - I_D R_D) \geq -0.7$$

$$\text{for } g_m = 2 \text{ mS, } I_D = 0.3 \text{ mA}$$

$$-\left| \frac{1 + g_m R_D}{g_m R_D} \right| g_m R_D \hat{v}_{sig} + 2.5 - I_D R_D \geq -0.7$$

$$R_D \leq 7.88 \text{ k}\Omega \quad (\hat{v}_{sig} = 50 \text{ mV})$$

$$G_V = -g_m R_D = -15.8$$

5.82

$$\text{a) } I_D = 0.1 = \frac{1}{2} \times 0.8 \times V_{ov}^2 \Rightarrow V_{ov} = 0.5 \text{ V}$$

$$\Rightarrow V_{GS} = 0.5 + 1 = 1.5 \text{ V}$$

$$V_G = 0 \Rightarrow V_S = -1.5 \text{ V}$$

$$R_S = \frac{-1.5 - (-5)}{0.1} = 35 \text{ k}\Omega$$


$$V_{DS} = 5 - R_D \times 0.1$$

Largest possible  $R_D$  is achieved for  $V_{DSmin}$

$$V_{DS} \geq V_{GS} - V_t \Rightarrow V_{DSmin} = V_{ov} \Rightarrow V_{DS} - 1 = V_{ov}$$

$$\Rightarrow V_{DS} = 1 + 0.5 = 1.5 \text{ V} \Rightarrow R_D = \frac{5 - 1.5}{0.1} = 35 \text{ k}\Omega$$

$$R_G = 10 \text{ M}\Omega$$

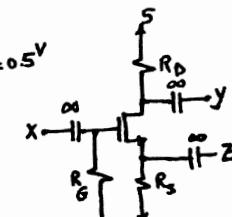

$$\text{b) } g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.1}{0.5} = 0.4 \text{ mS/V}$$

$$r_o = \frac{V_{ov}}{I_D} = \frac{0.5}{0.1} = 5 \text{ k}\Omega$$

c) IF z is grounded then the circuit becomes a common-source configuration. The voltage gain according to Eq. 4.82:

$$G_V = -\frac{R_L}{R_G + R_S} g_m (r_o \parallel r_D \parallel R_L)$$

$$G_V = \frac{10 \text{ M}}{10 \text{ M} + 1 \text{ M}} \times 0.4 \times (400 \text{ k} \parallel 35 \text{ k} \parallel 40 \text{ k}) = 6.5 \text{ V/V}$$

$$G_V = 6.5 \text{ V/V}$$

d) IF y is grounded, then the circuit becomes a source follower configuration.

$$\text{Eq. 4.103: } A_{V_o} = \frac{r_o}{r_o + \frac{1}{g_m}} = \frac{400}{400 + \frac{1}{0.4}} = 0.99 \text{ V/V}$$

$$R_{out} = \frac{1}{g_m} \parallel r_o = \frac{1}{0.4} \parallel 400 \text{ k} = 2.33 \text{ k}\Omega$$

$$R_{out} = 2.48 \text{ k}\Omega$$

e) If x is grounded, the circuit becomes a common-gate configuration.

$$R_{in} = \frac{1}{g_m} \parallel R_S = 35 \text{ k} \parallel \frac{1}{0.4} = 2.33 \text{ k}\Omega$$

$$\text{Eq. 4.98: } i_c = i_{sig} \frac{R_S g_m}{R_{sig} + R_{in}}$$

$$i_c = 10 \text{ mA} \frac{100 \text{ k}}{100 \text{ k} + 2.33 \text{ k}} = 9.77 \text{ mA}$$

$$V_y = R_D \times i_c = 35 \times 9.77 \text{ mA} = 0.34 \text{ V}$$

5 . 83

a) \_\_\_\_\_ is a source Follower:

$$A_{vo} = \frac{r_o}{r_o + \frac{1}{g_m}},$$

$$r_o \gg \frac{1}{g_m} \Rightarrow A_{vo} \approx 1 \text{ V/V}$$

$$R_{out} = \frac{1}{g_m} = \frac{1}{5} = 0.2 \text{ k}\Omega$$

b) \_\_\_\_\_ is a common - gate configuration:

$$R_{in} = \frac{1}{g_m} = \frac{1}{5} = 0.2 \text{ k}\Omega$$

$$A_v = g_m(R_D || R_L) = 5(5\text{K} || 2\text{K}) = 7.1 \text{ V/V}$$

c) If we connect both stages together, then: for the

$$\text{first stage: } A_v = A_{vo} \frac{R_L}{R_L + R_{out}}$$

where  $R_L$  is fact  $R_{in}$  of the second stage.


$$\text{Therefore: } A_{v_1} = 1 \times \frac{0.2\text{K}}{0.2 + 0.2} = 0.5 \text{ V/V}$$

For the second stage :  $A_{v_2} = 7.1 \text{ V/V}$

overall gain

$$A_v = A_{v_1} A_{v_2} = 7.1 \times 0.5 = 3.55 \text{ V/V}$$

5 . 84

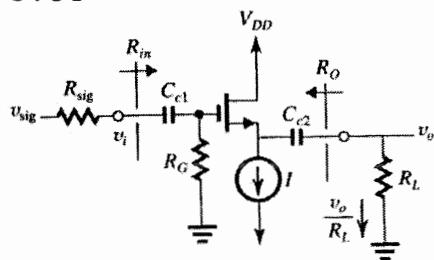

5 . 85

$$V_t = 1.0 \text{ V.}$$

$$r = 0.5 \text{ V.}^{1/2}$$

$$2\phi_f = 0.6 \text{ V.}$$

$$0 < V_{sg} < 4 \text{ V.}$$

$$V_t = V_{to} + r[\sqrt{2\phi_f + V_{sg}} - \sqrt{2\phi_f}]$$

$$\text{for } 0 < V_{sg} < 4 \text{ V.}, \quad V_{to} < V_t < V_{to} + 0.685 \text{ V.}$$

$$\text{so } 1 \text{ V.} < V_t < 1.68 \text{ V.}$$

$$\text{Since } r = \sqrt{\frac{2qN_A\epsilon_S}{C_{ox}}}, \text{ an increase of 4x in } t_{ox}$$

makes  $C_{ox}$  4x lower, and  $V_t$  becomes

$$1 \text{ V.} < V_t < 3.74 \text{ V.}$$

5 . 86

The test for region of operation for a depletion mode MOSFET is the same as for a enhancement mode MOSFET. The threshold voltage is negative; however.

$$V_t = -3 \text{ Volts}, V_{ds} = 0, V_g = 0 \text{ P}V_{ds} = 0$$


$$\text{a) } V_b = 0.1 \text{ Volts } P V_{ds} = 0.1 \text{ and } V_{ds} - V_t = 3 \text{ P}V_{ds} - V_t, \text{ so transistor is in the triode region}$$

$$\text{b) } V_b = 1 \text{ Volts } P V_{ds} = 1 \text{ and } V_{ds} - V_t = 3 \text{ P}V_{ds} < V_{ds} - V_t, \text{ so transistor is in the triode region.}$$

$$\text{c) } V_b = 3 \text{ Volts } P V_{ds} = 3 \text{ and } V_{ds} - V_t = 3 \text{ P}V_{ds} = V_{ds} - V_t, \text{ so transistor is at triode-saturation boundary.}$$

$$\text{d) } V_b = 5 \text{ Volts } P V_{ds} = 51 \text{ and } V_{ds} - V_t = 3 \text{ P}V_{ds} > V_{ds} - V_t, \text{ so transistor is in the saturation region.}$$

5 . 87

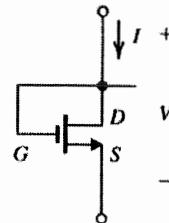

$$V_{GS} = V_{DS} = V - V_t \text{ is negative so}$$

$$V_{DS} < V_{GS} - V_t \text{ (always)}$$

First, when  $V = V_{GS} > V_t$

- From TABLE 5.1, this is triode region

$$I_D = k_n' \left( \frac{W}{L} \right) [ (V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2 ]$$


$$= k_n' \left( \frac{W}{L} \right) [ (V - V_t)V - \frac{1}{2}V^2 ]$$

$$= k_n' \left( \frac{W}{L} \right) [ \frac{1}{2}V^2 - V_tV ]$$

$$= \frac{1}{2}k_n' \left( \frac{W}{L} \right) [ V^2 - 2V_tV ]$$

Note that when  $V < 0$ ,  $I = I_D$  is negative.

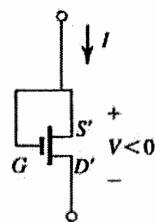- When  $V = V_{GS} < V_t$ , AND assuming the device can operate symmetrically with  $D$  acting as the source and  $S$  acting as the drain, the circuit can be modeled as below. In this configuration,



$$V_{GS'} = 0 > V_t \quad V_{DS'} = -V$$

( $V_{DS'}$  is therefore positive)

Since  $V_{GD'} = V < V_t$ , this is saturation region  
(see Table 5.1)

so

$$I = -i_D = -\frac{1}{2}k_n'\left(\frac{W}{L}\right)(V_{GS'} - V_t)^2$$

$$= -\frac{1}{2}k_n'\left(\frac{W}{L}\right)(0 - V_t)^2$$

$$= -\frac{1}{2}k_n'\left(\frac{W}{L}\right)V_t^2$$

$$V_t = -2 \text{ V}, k_n'\left(\frac{W}{L}\right) = 2 \text{ mA/V}^2$$


$$I = -\frac{1}{2}k_n'\left(\frac{W}{L}\right)(V^2 - 2V_tV) \quad V \geq V_t$$

$$= 1 \text{ mA/V}^2(V^2 + 4 \text{ V/V})$$

$$I = -\frac{1}{2}k_n'\left(\frac{W}{L}\right)V_t^2 \quad V \leq V_t$$

$$= -\frac{1}{2}(2 \text{ mA/V}^2)(-2 \text{ V})^2$$

$$= -4 \text{ mA}$$

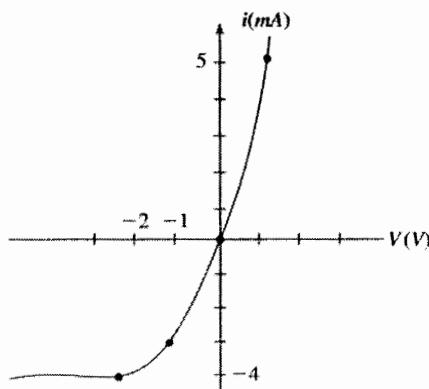

### 6.1

For  $I = 10 \mu\text{A}$ :

$$g_m = \frac{I}{V_T} = \frac{10 \mu\text{A}}{25 \text{ mV}} = 0.4 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.4 \text{ mA/V}} = 250 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I} = \frac{10 \text{ V}}{10 \mu\text{A}} = 1 \text{ M}\Omega$$

$$A_o = g_m r_o = \frac{V_A}{V_T} = \frac{10 \text{ V}}{0.025 \text{ V}} = 400 \text{ V/V}$$


For  $I = 100 \mu\text{A}$ :

$$g_m = \frac{100 \mu\text{A}}{25 \text{ mV}} = 4 \text{ mA/V}$$

$$r_\pi = \frac{100}{4 \text{ mA/V}} = 25 \text{ k}\Omega$$

$$r_o = \frac{10 \text{ V}}{100 \mu\text{A}} = 100 \text{ k}\Omega$$
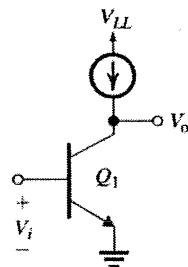
$$A_o = 4 \text{ mA/V}(100 \text{ k}\Omega) = 400$$



For  $I = 1 \text{ mA}$ :

$$g_m = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mA/V}$$

$$r_\pi = \frac{100}{40 \text{ mA/V}} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{10 \text{ V}}{1 \text{ mA}} = 10 \text{ k}\Omega$$

$$A_o = 40 \text{ mA/V} (10 \text{ K}) = 400$$

$I$	$g_m$	$r_\pi$	$r_o$	$A_o$
$10 \mu\text{A}$	$0.4 \text{ mA/V}$	$250 \text{ k}\Omega$	$1 \text{ M}\Omega$	400
$100 \mu\text{A}$	$4.0 \text{ mA/V}$	$25 \text{ k}\Omega$	$100 \text{ k}\Omega$	400
$1 \text{ mA}$	$40 \text{ mA/V}$	$2.5 \text{ k}\Omega$	$10 \text{ k}\Omega$	400

### 6.2

$$g_m = \frac{I_D}{V_{OV}}, \text{ so}$$

$$I_D = \frac{g_m V_{OV}}{2} = \frac{2 \text{ mA/V}(0.25 \text{ V})}{2} = 0.25 \text{ mA}$$

From chapt. 5,  $k'_n = \mu_n C_{ox}$

since  $g_m = \sqrt{2\mu_n C_{ox}(W/L)} \sqrt{I_D}$ ,

$$2 \text{ mA/V} = \sqrt{2(200 \mu\text{A/V}^2)(W/L)(250 \mu\text{A})}$$

yielding

$$W/L = 40$$

so that

$$W = 40(0.5 \mu\text{m}) = 20 \mu\text{m}$$

### 6.3

Assuming that the MOSFET is operating above  $V_D$ ,

$$A_o = \frac{V_A' \sqrt{2(\mu_n C_{ox})(WL)}}{\sqrt{I_D}}$$

If  $I_D$  is decreased to  $25 \mu\text{A}$ ,

$$A_o \text{ is increased by } \frac{1}{\sqrt{1/4}} = 2$$

$$g_m = \sqrt{2(\mu_n C_{ox})(W/L)} \cdot \sqrt{I_D}$$


so,  $g_m$  is decreased by

$$\sqrt{1/4} = 1/2$$

If  $I_D$  is increased to  $400 \mu\text{A}$ ,

$$A_o \text{ is decreased by } \frac{1}{\sqrt{4}} = \frac{1}{2}$$

$g_m$  increases by  $\sqrt{4} = 2$

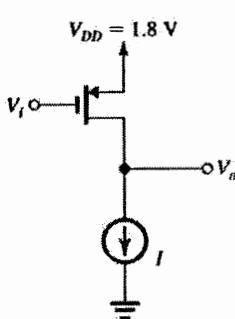

The edge of the Saturation region is defined as when  $|V_{DS}| = |V_{GS}| - |V_t| = |V_{ov}|$   
 $\therefore$  The highest instantaneous output voltage is  $V_{DD} - |V_{ov}| = 1.8 - 0.3 = 1.5 \text{ V}$

#### 6 . 4

$$L = 2(0.18 \mu\text{m}) = 0.36 \mu\text{m}$$

$$\text{a) } g_m = \frac{I_D}{V_{ov}} = \frac{10 \mu\text{A}}{0.25} = 80 \frac{\mu\text{A}}{\text{V}}$$

$$V_A' = 5 \text{ V}/\mu\text{m}$$

so,

$$r_o = \frac{V_A' L}{I_D} = \frac{5 \text{ V}/\mu\text{m} (2)(0.18 \mu\text{m})}{10 \mu\text{A}} = 180 \text{ k}\Omega$$

$$A_o = \frac{2V_A' L}{V_{ov}} = \frac{2(5 \text{ V}/\mu\text{m})(0.36 \mu\text{m})}{0.25 \text{ V}} = 14.4 \text{ V/V}$$

b) with  $I_D = 10 \mu\text{A}$

$$k_n = \frac{2I_D}{V_{ov}^2} = \frac{2(10 \mu\text{A})}{(0.25 \text{ V})^2} = 320 \frac{\mu\text{V}/\text{A}^2}{\text{V}^2}$$

Solving for  $V_{ov}$  with  $I_D = 100 \mu\text{A}$ :

$$V_{ov} = \frac{2I_D}{k_n} \rightarrow$$

$$V_{ov} = \sqrt{\frac{2(100 \mu\text{A})}{320 \frac{\mu\text{V}/\text{A}^2}{\text{V}^2}}} = 0.79 \text{ Volts}$$

$$g_m = \frac{I_D}{V_{ov}/2} = \frac{100 \mu\text{A}}{0.79 \text{ V}/2} = 253 \frac{\mu\text{A}}{\text{V}}$$

$$r_o = \frac{V_A' L}{I_D} = \frac{5 \text{ V}/\mu\text{m} (0.36 \mu\text{m})}{100 \mu\text{A}} = 18 \text{ k}\Omega$$

$$A_o = g_m r_o = 253 \frac{\mu\text{A}}{\text{V}} (18 \text{ k}\Omega) = 4.56 \text{ V/V}$$

c) Now, with a new  $W$  and  $V_{ov} = 0.25 \text{ V}$ ,

$$I_D = 100 \mu\text{A},$$

$$g_m = \frac{I_D}{V_{ov}/2} = \frac{100 \mu\text{A}}{0.25 \text{ V}/2} = 800 \frac{\mu\text{A}}{\text{V}}$$

$$r_o = \frac{V_A' L}{I_D} = \frac{5 \text{ V}/\mu\text{m}(0.36 \mu\text{m})}{100 \mu\text{A}} = 18 \text{ k}\Omega$$

$$A_o = \frac{2V_A' L}{V_{ov}} = \frac{(2)(5 \text{ V}/\mu\text{m})(0.36 \mu\text{m})}{0.25 \text{ V}} = 14.4 \text{ V/V}$$

d)  $I_D$  is now  $10 \mu\text{A}$ , first, find  $k_n$ :

$$k_n = \frac{2I_D}{V_{ov}^2} = \frac{2(10 \mu\text{A})}{(0.25 \text{ V})^2} = 3 \text{ mA/V}^2$$

so, now with  $I_D = 10 \mu\text{A}$ ,

$$V_{ov} = \sqrt{\frac{2I_D}{k_n}} = \sqrt{\frac{2(10 \mu\text{A})}{3 \text{ mA/V}^2}} = 0.079 \text{ V}$$

$$g_m = \frac{I_D}{V_{ov}/2} = \frac{10 \mu\text{A}}{0.079/2 \text{ V}} = 253 \frac{\mu\text{A}}{\text{V}}$$

$$r_o = \frac{V_A' L}{I_D} = \frac{(5 \text{ V}/\mu\text{m})(0.36 \mu\text{m})}{10 \mu\text{A}} = 180 \text{ k}\Omega$$

$$A_o = \frac{2V_A' L}{V_{ov}} = \frac{2(5 \text{ V}/\mu\text{m})(0.36 \mu\text{m})}{0.079 \text{ V}} = 45.6 \text{ V/V}$$

e) The lowest  $A_o$  is  $4.56 \text{ V/V}$

when  $V_{ov} = 0.79 \text{ V}$ ,  $I_D = 100 \mu\text{A}$ ,

$$L = 0.36 \mu\text{m}$$

The highest  $A_o$  is  $45.6 \text{ V/V}$

with  $I_D = 10 \mu\text{A}$ ,  $V_{ov} = 0.079 \text{ V}$

If  $W/L$  is held constant, and  $L$  is increased 10 times,

since  $A_o = \frac{2V_A' L}{V_{ov}}$  (or since  $g_m$  remains

constant, and  $r_o$  is increased by  $L$ )

Each gain is increased by a factor of 10:

Low  $A_o = 45.6 \text{ V/V}$

High  $A_o = 456 \text{ V/V}$

6.5

$$I_D = \frac{1}{2} k_n \left( \frac{W}{L} \right) V_{ov}^2$$

$$\frac{W}{L} = \frac{2I_D}{k'_n V_{ov}^2} = \frac{2(100 \mu\text{A})}{200 \mu\text{A/V}^2 (0.25 \text{ V})^2} = 16$$

$$\text{so, } W = 16(0.4 \mu\text{m}) = 6.4 \mu\text{m}$$

$$g_m = \frac{I_D}{V_{ov}/2} = \frac{100 \mu\text{A}}{\left(\frac{0.25 \text{ V}}{2}\right)} = 800 \mu\text{A/V}$$

$$r_o = \frac{V_A L}{I_D} = \frac{20 \text{ V}/\mu\text{m}(0.4 \mu\text{m})}{100 \mu\text{A}} = 80 \text{ k}\Omega$$


$$\text{If } L = 0.8 \mu\text{m},$$

$$W = 0.8 \mu\text{m}(16) = 12.8 \mu\text{m}$$

$$g_m = \frac{100 \mu\text{A}}{\left(\frac{0.25 \text{ V}}{2}\right)} = 800 \mu\text{A/V}$$

$$r_o = \frac{V_A L}{I_D} = \frac{20 \text{ V}/\mu\text{m}(0.8 \mu\text{m})}{100 \mu\text{A}} = 160 \text{ k}\Omega$$

6.6

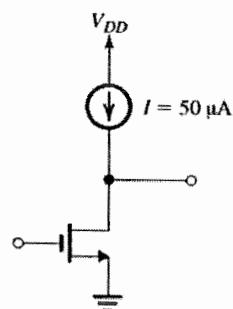

Since  $A_{\theta} = \frac{2V_A L}{V_{ov}}$ , and the current source is ideal,


$$L = \frac{A_{\theta} V_{ov}}{2V'_A} = \frac{100(0.2 \text{ V})}{2(20 \text{ V}/\mu\text{m})} = 0.5 \mu\text{m}$$

Since  $I_D = \frac{1}{2} (\mu_n C_{ox}) \left( \frac{W}{L} \right) V_{ov}^2$ ,

$$\frac{W}{L} = \frac{2I_D}{(\mu_n C_{ox}) V_{ov}^2}$$

$$= \frac{2 (50 \mu\text{A})}{(200 \mu\text{A/V}^2)(0.2 \text{ V})^2} = 12.5$$

6.7

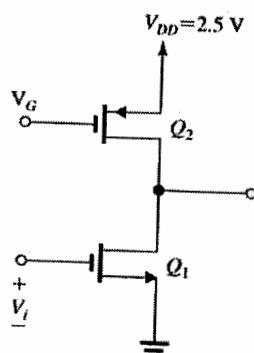

$$\begin{aligned} V_G &= V_{DD} - V_{SD2} \\ &= V_{DD} - |V_{tp}| - |V_{ov}| \\ &= 2.5 - 0.5 - 0.3 = 1.7 \text{ V} \end{aligned}$$

$$\text{Since } I_{D1} = \frac{1}{2} (\mu_n C_{ox}) \left( \frac{W}{L} \right)_1 V_{ov}^2$$

$$\left( \frac{W}{L} \right)_1 = \frac{2I_{D1}}{(\mu_n C_{ox}) V_{ov}^2}$$

$$= \frac{2(100 \mu\text{A})}{(200 \mu\text{A/V}^2)(0.3 \text{ V})^2} = 11.1$$

$$\begin{aligned} \text{for } Q_2, \left( \frac{W}{L} \right)_2 &= \frac{2I_{D2}}{(\mu_p C_{ox}) |V_{ov}|^2} \\ &= \frac{2 (100 \mu\text{A})}{(100 \mu\text{A/V}^2)(0.3)^2} = 22.2 \end{aligned}$$

$$\text{Since } V_{An} = \left| V_{Ap} \right| = 20 \text{ V}/\mu\text{m}$$

$$r_{o1} = r_{o2} = r_o = \frac{V_A L}{I} = \frac{20 \text{ V}/\mu\text{m} (0.5 \mu\text{m})}{100 \mu\text{A}} = 100 \text{ k}\Omega$$


$$g_m = \frac{I_{D1}}{\frac{V_{ov}}{2}} = \frac{100 \mu\text{A}}{0.3/2 \text{ V}} = 667 \mu\text{A/V}$$

$$r_o = 100 \text{ k}\Omega$$

so,

$$\begin{aligned} A_V &= \frac{1}{2} g_m r_o = -\frac{1}{2} (667 \mu\text{A/V})(100 \text{ k}\Omega) \\ &= -33.3 \text{ V/V} \end{aligned}$$

6 . 8

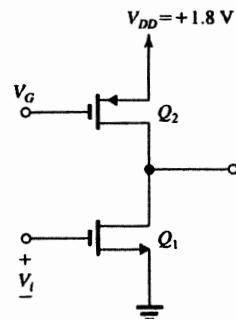

$$V_G = V_{DD} - |V_{tp}| - |V_{ov}| \\ = 1.8 - 0.5 - 0.2 = 1.1 \text{ V}$$

$$g_m = \frac{I_D}{V_{ov}/2} = \frac{100 \mu\text{A}}{0.2 \text{V}/2} = 1 \text{ mA/V}$$

$A_v = -g_m(r_{o1} \parallel r_{o2})$  so we must find

$r_{o1}$  and  $r_{o2}$

$$r_{o1} \parallel r_{o2} = \frac{A_v}{-g_m} = \frac{-40}{-1 \text{ mA/V}} = 40 \text{ k}\Omega$$

$$\text{since } r_{o1} = \frac{|V_{tp}|}{I_D} \text{ and } r_{o2} = \frac{|V_{tp}|L}{I_D}$$

$$r_{o1} = \frac{5 \text{ V}/\mu\text{m}}{100 \mu\text{A}} \cdot L = \frac{50 \text{ K}}{\mu\text{m}} \cdot L$$

$$r_{o2} = \frac{6 \text{ V}/\mu\text{m}}{100 \mu\text{A}} \cdot L = \frac{60 \text{ K}}{\mu\text{m}} \cdot L$$

so,

$$40 \text{ k}\Omega = \frac{50 \text{ k}\Omega/\mu\text{m}(60 \text{ k}\Omega/\mu\text{m}) \cdot L^2}{50 \text{ k}\Omega/\mu\text{m} \cdot L + 60 \text{ k}\Omega/\mu\text{m} \cdot L}$$

or  $L = 1.47 \mu\text{m}$

$$\text{since } I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) V_{ov}^2$$

$$\left( \frac{W}{L} \right)_1 = \frac{2I_{D1}}{\mu_n C_{ox} V_{ov}^2}$$


$$= \frac{2(100 \mu\text{A})}{387 \mu\text{A/V}^2 (0.2 \text{ V})^2} = 12.9$$

similarly,

$$\left( \frac{W}{L} \right)_2 = \frac{2I_{D2}}{\mu_p C_{ox} |V_{ov}|^2}$$

$$= \frac{2(100 \mu\text{A})}{86 \mu\text{A/V}^2 (0.2 \text{ V})^2} = 58.1$$

6 . 9

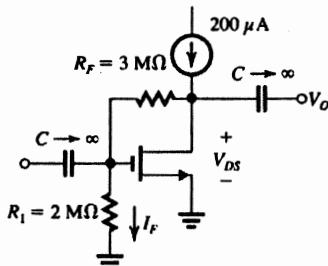

(a) If we neglect the current through  $R_F$ ,

$$I_D = 200 \mu\text{A} = \frac{1}{2} k_n (W/L) V_{ov}^2$$

$$V_{ov} = \sqrt{\frac{2I_D}{k_n(W/L)}} = \sqrt{\frac{2(200 \mu\text{A})}{2 \text{ mA/V}^2}} = 0.45 \text{ V}$$

$$V_{GS} = V_i + V_{ov} = 0.5 + 0.45 = 0.95 \text{ V}$$

The current through the feedback network is

$$I_F = \frac{V_G}{R_I} = \frac{0.95 \text{ V}}{2 \text{ M}\Omega} = 0.475 \mu\text{A}$$


This is  $\ll 200 \mu\text{A}$ , so this assumption is justified.

$$V_{DS} \approx$$

$$I_F (R_F + R_I) = 0.475 \mu\text{A} (3 \text{ M}\Omega + 2 \text{ M}\Omega)$$

$$= 2.38 \text{ V} \approx 2.4 \text{ V}$$

(b) small-signal model:

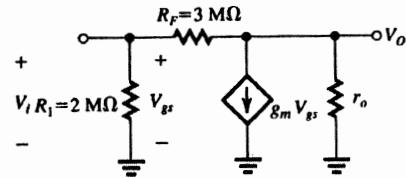

KCL at the output node yields

$$\frac{V_o}{r_o} + g_m V_{gs} + \frac{V_o - V_i}{R_F} = 0$$

$$\text{since } V_{gs} = V_i$$

$$\frac{V_o}{r_o} + g_m V_i + \frac{V_o}{R_F} - \frac{V_i}{R_F} = 0 \text{ or}$$

$$\frac{V_o}{V_i} = \frac{\left( \frac{1}{R_F} - g_m \right)}{\left( \frac{1}{r_o} + \frac{1}{R_F} \right)}$$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2(200 \mu A)}{0.45 V} = 0.89 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{20 V}{200 \mu A} = 100 \text{ k}\Omega$$

so,

$$\frac{V_D}{V_i} = \frac{\frac{1}{3000 \text{ K}} - 0.89 \text{ mA/V}}{\frac{1}{100 \text{ K}} + \frac{1}{3000 \text{ K}}} = -86.1 \text{ V/V}$$


To find the peak of the maximum sinewave output possible, we note that the current source is assumed to be ideal. Therefore, sinewave amplitude will be limited by the negative excursion. Since this happens when

$$V_{DS} = V_{ov} = 0.45 \text{ V},$$

the maximum peak amplitude will be

$$2.4 - 0.45 = 1.95 \text{ V}$$

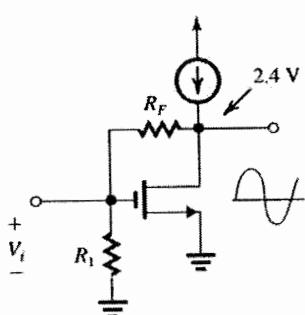
(That is, the output will vary between 0.45V and  $2.4 + 1.95 = 4.35 \text{ V}.$ )



The corresponding input voltage is

$$V_{i_{\text{peak}}} = \frac{V_{o_{\text{peak}}}}{|A_V|} = \frac{1.95 \text{ V}}{86.1 \text{ V/V}} = 23 \text{ mV}_{\text{peak}}$$

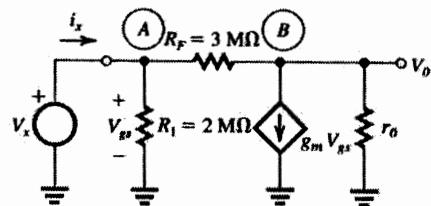(c) To find  $R_{in}$ , we apply a test voltage  $V_x$  to the input



KCL at node A:

$$i_x = \frac{V_x}{R_1} + \frac{V_x - V_o}{R_F}$$

KCL at node B:

$$\frac{V_x - V_o}{R_F} = \frac{V_o}{r_o} + g_m V_x$$

$$\Rightarrow V_o = \frac{V_x \left( \frac{1}{R_F} - g_m \right)}{\frac{1}{r_o} + \frac{1}{R_F}}$$

Substituting into the first equation, we get

$$i_x = \frac{V_x}{R_1} + \frac{V_x - V_o}{R_F} \frac{\left( \frac{1}{R_F} - g_m \right)}{\left( \frac{1}{r_o} + \frac{1}{R_F} \right)}$$

so that

$$R_{in} = \frac{V_x}{i_x} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_F} - \frac{1}{1/r_o + 1/R_F} + \frac{g_m/R_F}{r_o + R_F}}$$

$$R_{in} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_F} - \frac{1}{(R_F)^2 + R_F} + \frac{g_m}{r_o + R_F}}$$

$$R_{in} = \frac{1}{\frac{1}{2 \text{ m}\Omega} + \frac{1}{3 \text{ m}\Omega} - \frac{1}{(3 \text{ m}\Omega)^2 + 3 \text{ m}\Omega} + \frac{0.89 \text{ mA/V}}{0.1 \text{ m}\Omega + 1}}$$

$$R_{in} = 33.9 \text{ k}\Omega$$

### 6.10

the transfer characteristic of the amplifier over the region labeled as segment III, is quite linear.

$V_{OA} = V_{DD} - V_{OV3} = 5 - 0.53 = 4.47 \text{ V}$   
Now to Find the linear equation for segment III, we can write  $i_{D1} = i_{D2}$ :

$$\begin{aligned} & \frac{1}{2} k_n \left( \frac{W}{L} \right)_1 (v_t - v_{in})^2 \left( 1 + \frac{v_o}{V_{AP}} \right) \\ &= \frac{1}{2} k_n \left( \frac{W}{L} \right)_2 (v_t - |v_{ip}|)^2 \left( 1 + \frac{V_{DD} - v_o}{V_{AP}} \right) \\ &\Rightarrow 200(V_t - 0.6)^2 \left( 1 + \frac{v_o}{20} \right) \\ &= 65 \times 0.53^2 \times \left( 1 + \frac{V_{DD} - v_o}{10} \right) \\ &(V_{S6} - |V_{ip}|)^2 \left( 1 + \frac{V_{DD} - v_o}{V_{AP}} \right) \\ &\frac{200}{65 \times 0.53^2} (V_t - 0.6)^2 = \frac{1.5 - v_o / 10}{1 + \frac{v_o}{20}} \\ &7.3(V_t - 0.6)^2 = \frac{1 - v_o / 15}{1 + \frac{v_o}{20}} \\ &= \frac{1 - 0.067 v_o}{1 + 0.05 v_o} \approx 1 - 0.117 v_o \\ &\Rightarrow v_o = 8.57 - 62.57(V_t - 0.6)^2 \end{aligned}$$

If we substitute for  $v_{OA} = 4.47 \text{ V}$ , then  
 $V_{IA} = 0.86 \text{ V}$

To determine coordinates of B, note that  
 $V_{IB} - V_m = V_{OB}$  or  $V_{IB} - 0.6 = V_{OB}$   
Substitute in 1:

$$V_{OB} = 8.57 - 62.57v_{OB} \Rightarrow V_{OB} = 0.36 \text{ V}$$


$$V_{IB} = 0.6 + 0.36 = 0.96 \text{ V}$$

Therefore the linear region is :

$$0.86 \text{ V} \leq V_t \leq 0.96 \text{ V} \text{ or}$$

$$0.36 \text{ V} \leq V_o \leq 4.47 \text{ V}$$


### 6.11

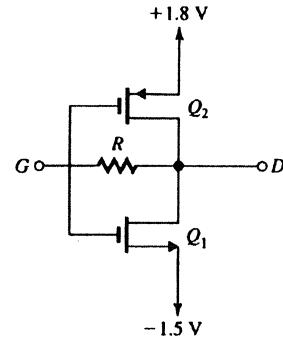

(a) If  $G$  and  $D$  are open, and no current flows to either gate,

$$\begin{aligned} V_D &= V_G \text{ and } I_{D1} = I_{D2} \\ I_{D1} &= \frac{1}{2} k_n (W/L)_1 (V_G - V_S - V_i)^2 \\ &= I_{D2} = \frac{1}{2} k_n (W/L)_2 (V_{DD} - V_G - |V_i|)^2 \\ \text{or, } (V_G - (-1.5V) - 0.5V)^2 &= (1.5V - V_G - 0.2V)^2 \\ (V_G + 1)^2 &= (1 - V_G)^2 \Rightarrow V_G = 0 \text{ so,} \\ I_{D2} &= I_{D1} = \frac{1}{2} (1 \text{ mA/V}^2)(0 + 1)^2 \\ &= 0.5 \text{ mA} \end{aligned}$$

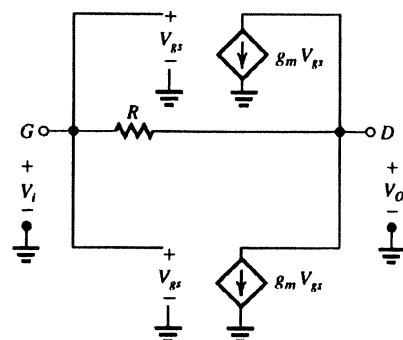(b) For  $r_o = \infty$ , the small-signal model becomes:



$$V_o = V_i - 2(g_m V_{gs})R$$

$$V_{gs} = V_i \text{ so}$$

$$V_o = V_i - 2 g_m R V_i$$

$$Av = \frac{V_o}{V_i} = 1 - 2 g_m R$$



Total resistance at the collector of  $Q_1$  is equal to  $r_{o1} \parallel r_{o2}$ , thus:

$$r_{tot} = 100 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 50 \text{ k}\Omega$$

$$r_{tot} = 50 \text{ k}\Omega$$

$$\text{c) } g_m = \frac{I_{C1}}{V_T} = \frac{0.5}{0.025} = 20 \text{ mA/V}$$


$$r_{\pi1} = \frac{B}{g_m} = \frac{50}{20} = 2.5 \text{ k}\Omega$$

$$\text{d) } R_{in} = r_{\pi1} = 2.5 \text{ k}\Omega$$

$$R_O = r_{o1} \parallel r_{o2} = 100 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 50 \text{ k}\Omega$$

$$A_V = -g_m R_O = -20 \times 50 = -1000 \text{ V/V}$$

### 6.13

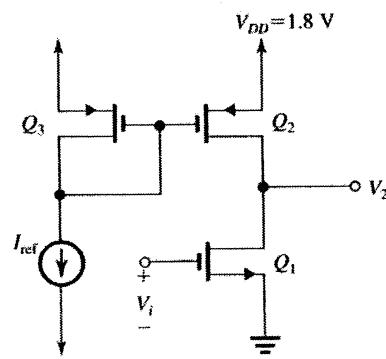

For an output of 1.6 V,

$$V_{SD2,\min} = |V_{ov}| = 1.8 - 1.6 = 0.2 \text{ V},$$

$$V_{SD1,\min} = 0.2 \text{ V}$$

Since  $I_{D2} = I_{D3} = I_{D1} = 50 \mu\text{A}$ ,

$$\text{and } I_D = \frac{1}{2}(\mu_p C_{ox})(W/L)V_{ov}^2$$

$$\begin{aligned} \left(\frac{W}{L}\right)_2 &= \left(\frac{W}{L}\right)_3 = \frac{2I_{D2}}{(\mu_p C_{ox})(V_{ov})^2} \\ &= \frac{2(50 \mu\text{A})}{(86 \mu\text{A/V}^2)(0.2 \text{ V})^2} = 29.1 \end{aligned}$$

For  $Q_1$ ,

$$\left(\frac{W}{L}\right)_1 = \frac{2(50 \mu\text{A})}{(387 \mu\text{A/V}^2)(0.2 \text{ V})^2} = 6.46$$

$A_V$  must be at least  $-10 \text{ V/V}$ ,

and  $A_V = -g_m(r_{o1} \parallel r_{o2})$

If we want to make  $r_{o1}$  and  $r_{o2}$  equal,

$$A_V = -\frac{1}{2}g_m r_o$$

$$\text{so, } r_o = \frac{A_V}{-1/2 g_m}$$

$$g_m \cdot \frac{I_{D1}}{V_{ov12}} = \frac{50 \mu\text{A}(2)}{0.2 \text{ V}} = 0.5 \text{ mA/V}$$

$$r_o = \frac{-10 \text{ V/V}}{-(1/2)(0.5 \text{ mA/V})} = 40 \text{ k}\Omega$$

$$r_o = \frac{|V_A|L}{|I_D|} \text{ so,}$$

$$\text{for } Q_1, L_1 = \frac{40 \text{ k}\Omega(0.05 \mu\text{A})}{5 \text{ V}/\mu\text{m}} = 0.4 \mu\text{m}$$

for  $Q_2$  and  $Q_3$ ,

$$L_2 = L_3 = \frac{40 \text{ k}\Omega(0.05 \mu\text{A})}{6 \text{ V}/\mu\text{m}} = 0.33 \mu\text{m}$$

Since we want  $L_1 = L_2 = L_3$  and  $L$  be an integer multiple of  $0.18 \mu\text{m}$ , we choose

$$L = 3(0.18 \mu\text{m}) = 0.54 \mu\text{m}$$

(Note: Choosing  $0.36 \mu\text{m}$  results in slightly less than  $-10 \text{ V/V}$ .)

checking,

$$r_{o1} = \frac{|V_A|L}{|I_D|} = \frac{5 \text{ V}/\mu\text{m}(0.54 \mu\text{m})}{0.05 \text{ mA}} = 54 \text{ k}\Omega$$

$$\begin{aligned} r_{o2} &= r_{o3} = \frac{6 \text{ V}/\mu\text{m}(0.54 \mu\text{m})}{0.05 \text{ mA}} \\ &= 64.8 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} A_V &= -g_m(r_{o1} \parallel r_{o2}) \\ &= -0.5 \text{ mA/V}(54 \text{ K1164.8 K}) \\ &= -14.7 \text{ V/V} \end{aligned}$$

If the gain is to be doubled, and the  $\frac{W}{L}$  ratios kept

the same,  $r_{o1} \parallel r_{o2}$  must double.

If  $r_{o1}$  and  $r_{o2}$  had been equal, this would have meant doubling  $L$  and  $W$ , making the area 4 times greater.

For a gain of  $-20 \text{ V/V}$ ,

$$L_1 = 0.8 \mu\text{m}$$

$$L_2 = 0.67 \mu\text{m}$$

The closest integer multiple that satisfies our requirement is  $(0.18 \mu\text{m})(5) = 0.9 \mu\text{m}$ .

so, with  $L_1 = L_2 = L_3$ ,

$$r_{o1} = \frac{5 \text{ V}/\mu\text{m}(0.9 \mu\text{m})}{0.05 \text{ mA}} = 90 \text{ k}\Omega$$

$$r_{o2} = \frac{6 \text{ V}/\mu\text{m}(0.9 \mu\text{m})}{0.05 \text{ mA}} = 133 \text{ k}\Omega$$

This results in a gain of

$$A_V = -(0.5 \text{ mA/V})(90 \text{ k}\Omega \parallel 133 \text{ k}\Omega)$$

$$A_V = -26.8 \text{ V/V}$$

This represents an increase in area of

$$\left(\frac{0.9}{0.54}\right)^2 = 2.78 \text{ (instead of 4)}$$

6.14

$$K = 40 = g_m r_{o2} = \frac{V_A}{V_{ov/2}}$$

so that

$$V_A = \frac{KV_{ov}}{2} = \frac{40(0.2V)}{2} = 4 \text{ V}$$

If  $V_A' = 5 \text{ V}/\mu\text{m}$ ,

$$L = \frac{V_A'}{V_A} = \frac{4 \text{ V}}{5 \text{ V}/\mu\text{m}} = 0.8 \mu\text{m}$$

$$2WL = 2(0.18 \mu\text{m})(0.18 \mu\text{m})n = 0.065 \text{ n}$$

Assuming that the driving NMOS transistors have similar  $g_m$  and  $R_O$ ,

$$A_V = -\frac{1}{2}g_m R_O$$

$$A_V = -\frac{1}{2}(0.1 \text{ mA/V})(810 \text{ K}) = -40.5 \text{ V/V}$$

For  $L = 0.36 \mu\text{m}$ :


$$IR_O = \frac{2(5 \text{ V}/\mu\text{m})^2(0.36 \mu\text{m})^2}{(0.2 \text{ V})} = 32.4 \text{ V}$$

$$R_O = \frac{32.4 \text{ V}}{0.01 \text{ mA}} = 3240 \text{ k}\Omega$$

$g_m$  remains unchanged

$$A_V = -\frac{1}{2}(0.1 \text{ mA/V})(3240 \text{ K}) = -162 \text{ V/V}$$

6.15

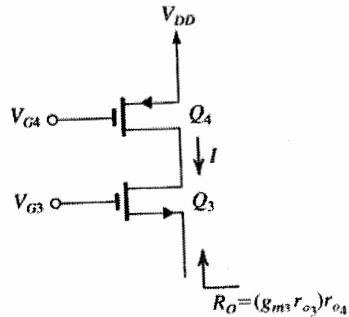

$$V_{ov3} = V_{ov4} = V_{ov}$$

$$L_4 = L_3 = L$$

$$V_{A3} = V_{A4} = V_A'$$

$$g_m r_{o3} = A_{o3} = \frac{|V_A'|L}{|V_{ov/2}|}$$

$$V_{o4} = \frac{|V_A'|L}{I}$$

so that

$$R_O \approx \frac{2|V_A'|L}{|V_{ov}|} \cdot \frac{|V_A'|L}{I}$$

$$\text{Finally, } IR_O = \frac{2|V_A'|^2 L^2}{|V_{ov}|}$$

$$\text{Now, } |V_A'| = 5 \text{ V}/\mu\text{m}, |V_{ov}| = 0.2 \text{ V}$$

For  $L = 0.18 \mu\text{m}$ :

$$IR_O = \frac{2(5 \text{ V}/\mu\text{m})^2(0.18 \mu\text{m})^2}{(0.2 \text{ V})} = 8.1 \text{ V}$$

$$R_O = \frac{IR_O}{I} = \frac{8.1 \text{ V}}{0.01 \text{ mA}} = 810 \text{ k}\Omega$$

$$g_m = \frac{|I|}{|V_{ov}|/2} = \frac{0.01 \text{ mA}}{(0.2 \text{ V}/2)} = 0.1 \text{ mA/V}$$

$$\text{Area} = 2WL = (0.36 \mu\text{m})^2n(2) = 0.26 \text{ n}\mu\text{m}^2$$

For  $L = 0.54 \mu\text{m}$ :

$$IR_O = \frac{2(5 \text{ V}/\mu\text{m})^2(0.54 \mu\text{m})^2}{(0.2 \text{ V})} = 72.9 \text{ V}$$

$$R_O = \frac{72.9 \text{ V}}{0.01 \text{ mA}} = 7290 \text{ k}\Omega$$

$$A_V = -\frac{1}{2}(0.1 \text{ mA/V})(7290 \text{ k}\Omega) \\ = -364.5 \text{ V/V}$$

$$\text{Area} = 2(0.54 \text{ n})(0.54) = 0.58 \text{ n}\mu\text{m}^2$$

Now, use  $I = 0.1 \text{ mA}$ :

$$L = 0.18 \mu\text{m}$$

$$\text{Since } I_D = \frac{1}{2}k_p(W/L)V_{ov}^2,$$

$W/L$  will be ten times larger ( $10n$ )

$$g_m = \frac{(0.1 \text{ mA})(2)}{(0.2 \text{ V})} = 1 \text{ mA/V}$$

$$R_O = \frac{IR_O}{I} = \frac{8.1 \text{ V}}{0.1 \text{ mA}} = 81 \text{ k}\Omega$$

$$A_V = -\frac{1}{2}(1 \text{ mA/V})(81 \text{ K}) = -40.5 \text{ V/V}$$

$$\text{Area} = 2WL = 2(10 \text{ n})(0.18 \mu\text{m})^2 \\ = 0.65 \text{ n}\mu\text{m}^2$$

For  $L = 0.36 \mu\text{m}$ :

$$R_O = \frac{32.4 \text{ V}}{0.1 \text{ mA}} = 324 \text{ k}\Omega$$

$$A_V = \frac{1}{2}(1 \text{ mA/V})(324 \text{ K}) = -162 \text{ V/V}$$

$$\text{Area} = 2WL = 2(10 \text{ n})(0.36 \mu\text{m})^2 \\ = 2.59 \text{ n}\mu\text{m}^2$$

For  $L = 0.54 \mu\text{m}$ :

$$R_O = \frac{72.9 \text{ V}}{0.1 \text{ mA}} = 729 \text{ k}\Omega$$

	$L = L_{\min} = 0.18 \mu\text{m}$ $IR_O = 8.1 \text{ V}$				$L = 2L_{\min} = 0.36 \mu\text{m}$ $IR_O = 32.4 \text{ V}$				$L = 3L_{\min} = 0.54 \mu\text{m}$ $IR_O = 72.9 \text{ V}$			
	$g_m$	$R_O$	$A_{vo}$	2WL	$g_m$	$R_O$	$A_{vo}$	2WL	$g_m$	$R_O$	$A_{vo}$	2WL
	mA/V	kΩ	V/V	μm²	mA/V	kΩ	V/V	μm²	mA/V	kΩ	V/V	μm²
$I=0.01 \text{ mA}$ $W/L = n$	0.1	810	-40.5	0.065 n	0.1	3,240	-162	0.26 n	0.1	7,290	-364, 5	0.58 n
$I=0.01 \text{ mA}$ $W/L = 10 \text{ n}$	1.0	81	-40.5	0.65 n	1.0	324	-162	2.6 n	1.0	729	-364, 5	5.8 n
$I=0.01 \text{ mA}$ $W/L = 100 \text{ n}$	10.0	8.1	-40.5	6.5 n	10.0	32.4	-162	26 n	10.0	72.9	-364, 5	58 n

$$A_v = -\frac{1}{2}(1 \text{ mA/V})(729 \text{ K}) = -364.5 \text{ V/V}$$

$$\begin{aligned} \text{Area} &= 2 \text{ WL} = (2)(10 \text{ n})(0.54 \mu\text{m})^2 \\ &= 5.8 \text{ n } \mu\text{m}^2 \end{aligned}$$

Now, for  $I = 1.0 \text{ mA}$ ,

For  $L = 0.18 \mu\text{m}$ :

$$\frac{W}{L} = 100 \text{ n}$$

$$g_m = \frac{1 \text{ mA}(2)}{(0.2 \text{ V})} = 10 \text{ mA/V}$$

$$R_O = \frac{8.1 \text{ V}}{1 \text{ mA}} = 8.1 \text{ k}\Omega$$

$$\begin{aligned} A_V &= -\frac{1}{2}(10 \text{ mA/V})(8.1 \text{ k}) \\ &= -40.5 \text{ V/V} \end{aligned}$$

$$\begin{aligned} \text{Area} &= 2 \text{ WL} = 2(100 \text{ n})(0.18 \mu\text{m})^2 \\ &= 6.5 \text{ n } \mu\text{m}^2 \end{aligned}$$

For  $L = 0.36 \mu\text{m}$ :

$$R_O = \frac{32.4 \text{ V}}{1 \text{ mA}} = 32.4 \text{ k}\Omega$$

$$A_V = -\frac{1}{2}(10 \text{ mA/V})(32.4 \text{ k}) = -162 \text{ V/V}$$

$$\begin{aligned} \text{Area} &= 2 \text{ WL} = 2(100 \text{ n})(0.36 \mu\text{m})^2 \\ &= 26 \text{ n } \mu\text{m}^2 \end{aligned}$$

For  $L = 0.54 \mu\text{m}$ :

$$R_O = \frac{72.9 \text{ V}}{1 \text{ mA}} = 72.9 \text{ k}\Omega$$

$$\begin{aligned} A_V &= -\frac{1}{2}(10 \text{ mA/V})(72.9 \text{ k}) \\ &= -364.5 \text{ V/V} \end{aligned}$$

$$\text{Area} = 2 \text{ WL} = 2(100 \text{ n})(0.54 \mu\text{m})^2$$

$$= 58 \text{ n } \mu\text{m}^2$$

The table summarizes the calculations.

Comments:

(a)  $R_O$  and  $A_V$  are increased but at the cost of larger device area. As  $L$  increases by a factor of  $X$ ,  $A_V$  and  $R_O$  increase by a factor of  $X^2$ . The device area increases at this same rate.

(b)  $g_m$  increases with  $|I|$ , but  $R_O$  decreases with

$$\frac{1}{|I|}.$$

The device area increases with  $|I|$ .

(c) Smallest area = 0.065 n  $\mu\text{m}^2$

Largest area = 58 n  $\mu\text{m}^2$  Gain and  $g_m$  have been increased, but at the expense of increased device area.

6.16

$$g_{m1} = \frac{2I_D}{V_{ov}}, \text{ so,}$$

$$I_D = \frac{g_{m1}V_{ov}}{2} = \frac{1 \text{ mA/V}(0.2 \text{ V})}{2} = 100 \mu\text{A}$$


$$R_O = (g_{m2}r_{o2})r_{o1}$$

However, if we make  $g_{m1} = g_{m2} = g_m$  and  $r_{o1} = r_{o2} = r_o$ , we can say that  $400 \text{ k}\Omega = 1 \text{ mA/V} \cdot r_o^2$

$$r_o^2 = \frac{400 \text{ k}\Omega}{1 \text{ mA/V}} \Rightarrow r_o = 20 \text{ k}\Omega$$

since  $r_o = \frac{V_A L}{I_D}$ ,
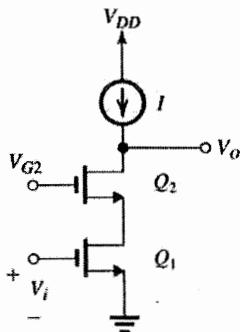
$$L = \frac{I_D r_o}{V_A} = \frac{100 \mu\text{A}(20 \text{ k}\Omega)}{5 \text{ V}/\mu\text{m}} = 0.4 \mu\text{m}$$



$$g_m = \sqrt{2 \mu_n C_{ox} (W/L) \cdot \sqrt{I_D}} \text{ so that}$$

$$\frac{W}{L} = \frac{g_m^2}{2 \mu_n C_{ox} I_D}$$

$$= \frac{(1000 \mu\text{A/V})^2}{2(400 \mu\text{A/V}^2)(100 \mu\text{A})} = 12.5$$

For maximum negative excursion at the output, we want the MOSFETs to be biased so that each transistor can reach  $V_{DS} = V_{ov} = 0.2 \text{ V}$ .

$$\therefore \text{Set } V_{g2} = V_{in} + V_{ov} + V_{ov}$$

$$= 0.5 + 0.2 + 0.2 = 0.9 \text{ V}$$

minimum output voltage will be

$$2 V_{ov} = 0.4 \text{ V}$$

6.17

$$g_{m1} = \frac{I_{D1}}{\frac{V_{ov}}{2}} = \frac{100 \mu\text{A}}{(0.25 \text{ V})/2} = 800 \mu\text{A/V}$$

Since all devices have the same  $V_A$  and  $I_D$ ,

$$r_{o1} = r_{o2} = r_{o3} = r_{o4}$$

$$= \frac{|V_A|}{I_D} = \frac{4 \text{ V}}{0.1 \text{ mA}} = 40 \text{ k}\Omega$$

$$R_{on} = g_m r_o^2 = (0.8 \text{ mA/V})(40 \text{ k}\Omega)^2$$

$$= 1.28 \text{ M}\Omega$$

$$R_{op} = g_m r_o^2 = 1.28 \text{ M}\Omega$$

$$R_O = R_{on} \parallel R_{op} = 640 \text{ k}\Omega$$

$$A_V = -g_{m1} R_O$$

$$= -800 \mu\text{A/V} (640 \text{ k}\Omega)$$

$$= -512 \text{ V/V}$$

6.18

Since  $A_V = -g_{m1} R_O$

$$R_O = \frac{A_V}{-g_{m1}} = \frac{-200}{-2 \text{ mA/V}} = 100 \text{ k}\Omega$$

If all have the same  $I_D$  and  $V_A$ , and since  $R_O = R_{on} \parallel R_{op}$ , and

$$g_{m1} = g_{m2} = g_{m3} = g_{m4} = g_m,$$

$$R_O = (g_m r_o^2) \parallel (g_m r_o^2) = \frac{1}{2} g_m r_o^2$$

solving for  $r_o$ , we get

$$r_o = \sqrt{\frac{2R_O}{g_m}} = \sqrt{\frac{2(100 \text{ k}\Omega)}{2 \text{ mA/V}}} = 10 \text{ k}\Omega$$

$$I = \frac{g_m |V_{ov}|}{2} = \frac{2 \text{ mA/V}(0.2 \text{ V})}{2}$$

$$= 0.2 \text{ mA} = 200 \mu\text{A}$$

Since  $r_o = \frac{|V_A| L}{I_D}$ ,

$$L = \frac{r_o I}{|V_A|} = \frac{10 \text{ k}\Omega(0.2 \text{ mA})}{5 \text{ V}/\mu\text{m}} = 0.4 \mu\text{m}$$

Since  $g_m = \sqrt{2 \mu_n C_{ox}}(W/L) \cdot \sqrt{I_D}$

$$\begin{aligned} \left(\frac{W}{L}\right)_1 &= \left(\frac{W}{L}\right)_2 = \frac{g_m^2}{2 \mu_n C_{ox} I_D} \\ &= \frac{(2 \text{ mA/V})^2}{2 (400 \mu\text{A/V}^2)(200 \mu\text{A})} = 25 \end{aligned}$$

Similarly,

$$\begin{aligned} \left(\frac{W}{L}\right)_3 &= \left(\frac{W}{L}\right)_4 \\ &= \frac{(2 \text{ mA/V})^2}{2 (100 \mu\text{A/V}^2)(200 \mu\text{A})} = 100 \end{aligned}$$

### 6.19

a)  $I = \frac{1}{2} k_s \frac{W}{L} V_{ov}^2$

$$\Rightarrow \text{For same } I: \frac{V_{ovb}^2}{V_{ova}^2} = \frac{\left(\frac{W}{L}\right)_a}{\left(\frac{W}{L}\right)_b}$$

For same  $I$ , if  $\frac{W}{L}$  is divided by 4,

then  $V_{ov}^2$  is multiplied by 4, or equivalently

$V_{ov}$  is doubled  $g_m = \mu_n C_{ox} \frac{W}{L} V_{ov}$  Thus  $g_m$  for circuit (b) is half of the one for circuit(a).

$$A_O = g_m r_o = \frac{2I_D}{V_{ov}} \times \frac{V_A}{I_D} = \frac{2V_A L}{V_{ov}}. \text{ Thus, if}$$

$L$  is multiplied by 4, and  $V_{ov}$  is halved, then  $A_O$  is doubled for circuit(b).

In summary, for circuit (b),  $V_{ov}$  is doubled,  $g_m$  is halved,  $A_O$  is doubled.

(b) Each transistor in circuit (c) has the same  $V_{ov}$  as the one in circuit (a).

$$A_{vo} = -A_O^2 = -(g_m r_o)^2$$

$$G_m \approx g_{m1} = g_m \text{ (same as circuit (a))}$$

Note that for the transistor in (c), the  $g_m$  and  $r_o$  are the same as those in circuit (a). In summary, for circuit(b),  $V_{ov}$  is doubled,  $g_m$  is halved  $A_o$  is doubled.

(b) Each transistor in circuit (c) has the same  $V_{ov}$  as the one in circuit (a).

$$A_{vo} = -A_O^2 = -(g_m r_o)^2$$

$$G_m \approx g_{m1} = g_m \text{ (same as circuit (a))}$$

Note that for the transistor in (c), the  $g_m$  and  $r_o$  are the same as those in circuit (a).

Thus, the intrinsic gain for circuit (c),  $A_{vo} = -A_o^2$  where  $A_o$  is the intrinsic gain for circuit (a).

In general, circuit (c) has a higher output resistance, and for the same  $V_{ov}$  of transistors it has lower output swing. The output swing is limited to  $2 V_{ov}$  on the low side for circuits (b) and (c), but limited to only  $V_{ov}$  in circuit (a)

### 6.20

For  $Q_1$ ,

$$V_{ov} = V_i - V_{in} = 0.8 - 0.5 = 0.3 \text{ V}$$

Since all transistors are identical, and

$$k_{n1} = k_{n2} = k_{p3} = k_{p4}$$

with  $I_{D1} = I_{D2} = I_{D3} = I_{D4}$ ,

$$|V_{ov}| = 0.3 \text{ V} \text{ (since } I_D = \frac{1}{2} k |V_{ov}|^2 \text{.)}$$

with  $V_{G2}$  and  $V_{G3}$  fixed,

$$V_{S2} = V_{G2} - V_{GS2}$$

$$= 1.2 - 0.5 - 0.3 = 0.4 \text{ V}$$

$$V_{S3} = V_{G3} + V_{GS3}$$

$$= 1.3 + 0.5 + 0.3 = 2.1 \text{ V}$$


The lowest  $V_O$  is

$$V_{S2} + V_{OV2} = 0.4 + 0.3 = 0.7 \text{ V}$$


The highest  $V_O$  is

$$V_{S3} - V_{OV3} = 2.1 - 0.3 = 1.8 \text{ V}$$

so the output range is 0.7 V to 1.8 V

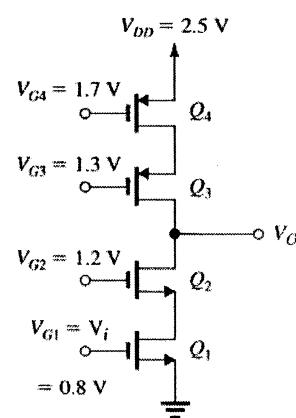

6.21

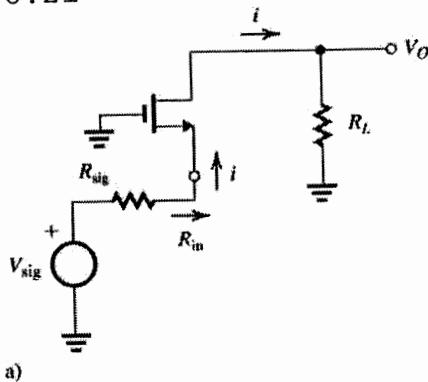

a)

$$R_{in} = \frac{R_L + r_o}{1 + g_m r_o} = \frac{R_L}{g_m r_o} + \frac{1}{g_m}$$

(b)  $V_O = i R_L$  and

$$i = \frac{V_{sig}}{R_{sig} + R_{in}} = \frac{V_{sig}}{R_{sig} + \frac{R_L + r_o}{1 + g_m r_o}}$$

multiplying and dividing by  $V_{sig}$ , we get

$$\frac{V_O}{V_{sig}} = \frac{R_L}{R_{sig} + \frac{R_L + r_o}{1 + g_m r_o}} \approx \frac{R_L}{R_{sig} + \frac{R_L}{g_m r_o} + \frac{1}{g_m}}$$


c) If  $R_L = r_o = 10 \text{ k}\Omega$ ,  $A_o = 20$ ,

$$R_{sig} = 1\text{K}, g_m = \frac{A_o}{r_o} = \frac{20}{10\text{k}\Omega} = 2\text{mA/V}$$

$$R_{in} = \frac{10\text{k}\Omega}{20} + \frac{1}{2\text{mA/V}} = 1\text{k}\Omega$$


$$\frac{V_O}{V_{sig}} = \frac{R_L}{R_{sig} + R_{in}} = \frac{10\text{k}\Omega}{1\text{k}\Omega + 1\text{k}\Omega} = 5\text{V/V}$$

6.22

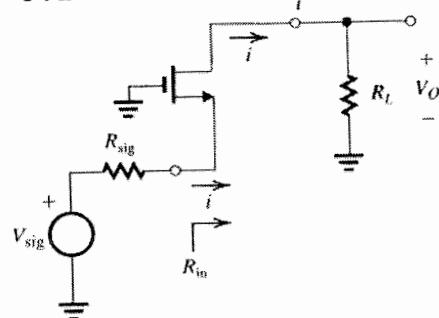

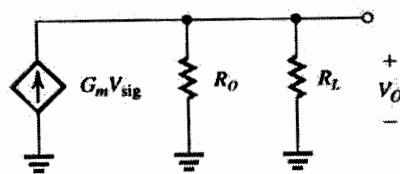a) If d is shorted to ground, the current flowing through the short is

$$i = \frac{V_{sig}}{R_{sig} + R_{in}} = \frac{V_{sig}}{R_{sig} + \frac{1}{g_m}}$$



$$G_m = \frac{i}{V_{sig}} = \frac{1}{R_{sig} + \frac{1}{g_m}}$$

From Fig. 7.13,

$$R_o = r_o + R_{sig} + (g_m r_o) R_{sig}$$

b) If  $r_o = 10 \text{ k}\Omega$ , and

$$g_m = \frac{A_o}{r_o} = \frac{20}{10\text{k}\Omega} = 2 \text{ mA/V},$$

$$G_m = \frac{1}{R_{sig} + \frac{1}{g_m}} = \frac{1}{1\text{k}\Omega + \frac{1\text{V}}{2\text{mA}}} = 0.67 \text{ mA/V}$$

$$R_o + 10\text{k}\Omega + 1\text{k}\Omega + (20)(1\text{k}\Omega) = 31\text{k}\Omega$$


Using the new model,

$$V_O = G_m V_{sig} (R_o \parallel R_L)$$

$$\frac{V_O}{V_{sig}} = G_m (R_o \parallel R_L)$$

$$= 0.67 \text{ mA/V} (31\text{k}\Omega \parallel 10\text{k}\Omega) = 5.04 \text{ V/V}$$

6.23

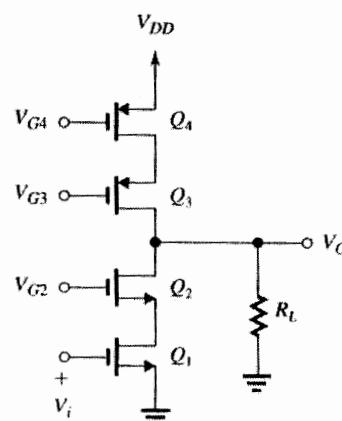

$$\text{If } |V_{Ap}| = |V_{An}|,$$

$$r_{o1} = r_{o2} = r_{o3} = r_o = \frac{V_L}{I_D}$$

$$= \frac{(5 \text{ V}/\mu\text{m})(0.36 \mu\text{m})}{200 \mu\text{A}}$$

$$r_o = 9 \text{ k}\Omega$$

$$I_D = \frac{1}{2} k' \left( \frac{W}{L} \right) V_{ov1}^2$$

$$V_{ov1} = \sqrt{\frac{2I_D}{k' \left( \frac{W}{L} \right)}}$$

$$= \sqrt{\frac{2(200 \mu\text{A})}{400 \mu\text{A/V}^2 \left( \frac{5.4}{0.36} \right)}} = 0.26 \text{ V}$$

$$g_{m1} = \frac{I_{D1}}{V_{ov1}} = \frac{200 \mu\text{A}}{0.26/2} = 1.54 \text{ mA/V}$$

$$V_{ov3} = V_{ov4} = \sqrt{\frac{2(200 \mu\text{A})}{100 \mu\text{A/V}^2 \left( \frac{5.4}{0.36} \right)}}$$

$$= 0.52 \text{ V}$$

$$g_{m3} = g_{m4} = \frac{200 \mu\text{A}}{(0.52 \text{ V})/2} = 769 \mu\text{A/V}$$

$$R_{op} = (g_{m3}r_{o3})r_{o4} \\ = (1.54 \text{ mA/V})(9 \text{ k}\Omega)^2 = 125 \text{ k}\Omega$$

$$R_{op} = (g_{m3}r_{o3})r_{o4} \\ = (0.769 \text{ mA/V})(9 \text{ k}\Omega)^2 = 62.3 \text{ k}\Omega$$


$$R_o = R_{op} \parallel R_{on} \\ = 62.3 \text{ k}\Omega \parallel 125 \text{ k}\Omega = 41.6 \text{ k}\Omega$$

The value of  $R_o \parallel R_L$  needed is

$$R_o \parallel R_L = \frac{A_V}{-g_{m1}} = \frac{-100}{1.54 \text{ mA/V}} = 64.9 \text{ k}\Omega$$

This is greater than  $R_o$ !

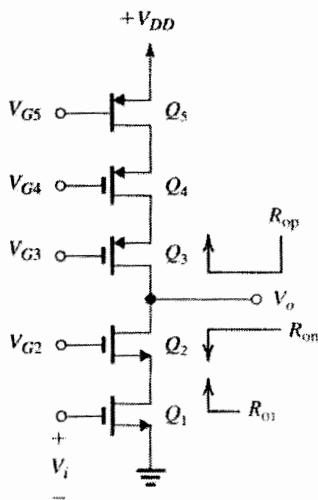This can't be done with the present design.  
One thing we could do is double cascode the current source to raise  $R_{op}$ :



This raises  $R_{op}$  to

$$R_{op} = (g_{m3}r_{o3})(g_{m4}r_{o4})r_{o5} \\ = (0.769 \text{ mA/V})^2(9 \text{ k}\Omega)^3 = 431 \text{ k}\Omega$$

We can now find an  $R_L$  that will allow a gain of -100 V/V. Since

$$431 \text{ k}\Omega \parallel 125 \text{ k}\Omega = 96.9 \text{ k}\Omega$$

Setting  $\frac{R_L(96.9)}{R_L + (96.9)} = 65 \text{ k}\Omega$ , we get

$$R_L = 197 \text{ k}\Omega$$

To find the gain of the CS amplifier, we calculate  $R_{o1}$ :

$$R_{o1} = (R_{op} \parallel R_L)(g_{m3}r_{o3}) \parallel r_{o1}$$

$$R_{o1} = [(431 \text{ k}\Omega \parallel 197 \text{ k}\Omega)(1.5 \text{ mA/V}) \\ (9 \text{ k}\Omega)] \parallel (9 \text{ k}\Omega)$$

$$R_{o1} = 9 \text{ k}\Omega$$

$$\text{so, } A_{V1} = -g_{m1}R_{o1} = (1.54 \text{ mA/V})(9 \text{ k}\Omega) \\ = -13.9 \text{ V/V}$$

## 6.24

$$R_1 = r_o$$

$$R_2 = g_m r_o^2$$

$$R_3 = \frac{1}{g_m} + \frac{g_m r_o^2}{g_m r_o}$$

$$R_3 = \frac{1}{g_m} + r_o$$

$$\text{b) } i_1 = V_i g_m$$

By current division,

$$i_2 = \frac{i_1 R_3}{r_o + R_3} = \frac{V_i g_m \left( \frac{1}{g_m} + r_o \right)}{r_o + \frac{1}{g_m} + r_o} \\ = \frac{V_i (1 + g_m r_o)}{\frac{1}{g_m} + 2r_o}$$

also,

$$i_3 = \frac{i_1 r_o}{r_o + R_3} = \frac{V_i g_m r_o}{r_o + \frac{1}{g_m} + r_o} = \frac{V_i g_m r_o}{\frac{1}{g_m} + 2r_o}$$

$$i_4 = i_5 = i_7 = i_3 = \frac{V_i g_m r_o}{\frac{1}{g_m} + 2r_o}$$

c)

$$V_1 = -V_i g_m (r_o \parallel R_3)$$

$$= \frac{-V_i g_m (r_o) \left( \frac{1}{g_m} + r_o \right)}{r_o + \frac{1}{g_m} + r_o}$$

$$V_1 = \frac{-V_i g_m r_o}{1 + \frac{r_o}{\frac{1}{g_m} + r_o}}$$

$$= \frac{-V_i g_m r_o}{1 + \frac{1}{\frac{1}{g_m} + r_o}} \approx \frac{-1}{2} V_i g_m r_o$$

$$V_2 = V_i g_m [(g_m r_o^2) \parallel (g_m \parallel r_o^2)]$$

$$= \frac{1}{2} (g_m r_o)^2$$

$$V_3 = \frac{-V_i g_m r_o}{\frac{1}{g_m} + 2r_o} r_o = \frac{-V_i g_m r_o}{\frac{1}{g_m r_o} + 2}$$

$$\approx -\frac{1}{2} V_i g_m r_o$$

$$\text{d)} V_1(t) \approx -\frac{1}{2} V_i g_m r_o$$

with  $V_{i\text{peak}} = 5 \text{ mV}$ ,





$$V_{1\text{peak}} = -\frac{1}{2}(5 \text{ mV})(20) = -50 \text{ mV}_{\text{peak}}$$

$$V_2(t) = -\frac{1}{2} V_i (g_m r_o)^2$$

$$V_{2\text{peak}} = -\frac{1}{2}(5 \text{ mV})(20)^2 = -1 \text{ V}_{\text{peak}}$$

$$V_3(t) \approx -\frac{1}{2} V_i (g_m r_o)$$
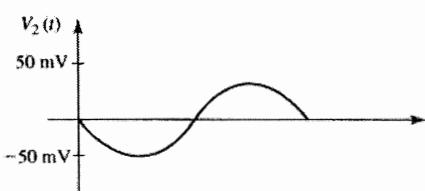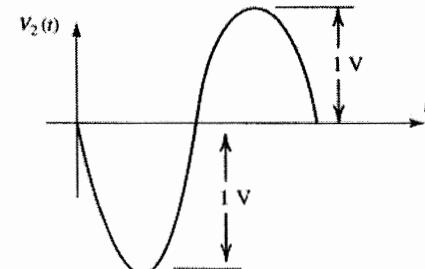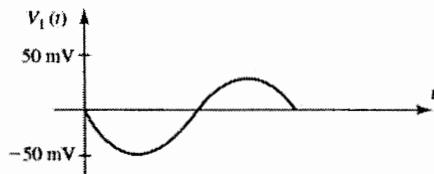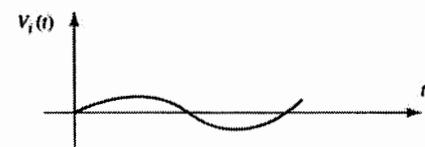
$$V_{3\text{peak}} = -\frac{1}{2}(5 \text{ mV})(20) = -50 \text{ mV}_{\text{peak}}$$



### 6.25

$$\text{Since } I_D = \frac{1}{2} (\mu_p C_{ox}) \left( \frac{W}{L} \right) |V_{ov}|^2,$$

$$\begin{aligned} \frac{W}{L} &= \frac{2I_D}{(\mu_p C_{ox}) |V_{ov}|^2} \\ &= \frac{2(100 \mu\text{A})}{(100 \mu\text{A}/\text{V}^2)(0.2 \text{ V})^2} \end{aligned}$$

$$\frac{W}{L} = 50$$

(for all transistors)

$$r_o = \frac{|V_A| L}{I_D} = \frac{(6 \text{ V}/\mu\text{m})(0.18 \mu\text{m})}{100 \mu\text{A}}$$

$$= 10.8 \text{ k}\Omega$$

To permit the maximum swing, each  $V_{DS\text{min}}$  should equal  $|V_{ov}|$ . So,

$$\begin{aligned}
 V_{G1} &= V_{DD} - |V_{op}| - |V_{ov}| \\
 &= 1.8 - 0.5 - 0.2 = 1.1 \text{ V} \\
 V_{G2} &= V_{D1_{max}} - |V_{op}| - |V_{ov}| \\
 &= (1.8 - 0.2) - 0.5 - 0.2 = 0.9 \text{ V} \\
 V_{G3} &= V_{D2_{max}} - |V_{op}| - |V_{ov}| \\
 &= (1.8 - 0.2 - 0.2) - 0.5 - 0.2 = 0.7 \text{ V} \\
 R_O &\geq r_{o1}(g_{m2}r_{o2})(g_{m3}r_{o3}) \\
 &\approx g_m^2 r_o^3 = (1 \text{ mA/V})^2 (10.8 \text{ k}\Omega)^3 = 1.26 \text{ M}\Omega
 \end{aligned}$$

### 6.26

a) Assuming that all transistors have the same  $g_m$  and  $r_o$ ,

$$\begin{aligned}
 R_{o1} &= r_o \\
 R_{o2} &= r_o \\
 R_{o3} &= (g_{m3} r_{o3}).
 \end{aligned}$$

$$R_{o1} \parallel R_{o2} = g_m r_o \left( \frac{1}{2} r_o \right) = \frac{1}{2} g_m r_o^2$$

$$R_{o3} \geq (g_{m3} r_{o4}) \quad r_{o5} = g_m r_o^2$$

$$R_{o3} = \frac{1}{g_m} + \frac{R_{o4}}{g_m r_o} = \frac{1}{g_m} + \frac{g_m r_o^2}{g_m r_o} = \frac{1}{g_m} + r_o$$


$$\text{b) } R_o = R_{o3} \parallel R_{o4} = \left( \frac{1}{2} g_m r_o^2 \right) \parallel (g_m r_o^2)$$

$$\begin{aligned}
 R_o &= \frac{\frac{1}{2} g_m^2 r_o^4}{\frac{1}{2} g_m r_o^2 + g_m r_o^2} \\
 &= \frac{1}{3} g_m r_o^2
 \end{aligned}$$

c) If  $V_a$  is shorted to ground,

$$R_{in3} = \frac{1}{g_m} + \frac{0}{g_m r_o} = \frac{1}{g_m}$$

Using current division,

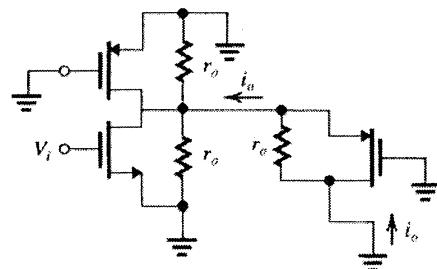

$$i_o = g_{m1} V_i \frac{\frac{1}{2} r_o}{\frac{1}{2} r_o + \frac{1}{g_m}} = \frac{g_{m1} V_i}{1 + \frac{2}{g_m r_o}}$$

$$G_m = \frac{i_o}{V_i} = \frac{g_{m1}}{1 + \frac{2}{g_m r_o}} = g_{m1}$$

d) If  $R_t = R_{o4}$ ,

$$R_{in3} = \frac{1}{g_m} + r_o$$

$$i_o = \frac{V_i g_m \left( \frac{r_o}{2} \right)}{r_o / 2 + \frac{1}{g_m} + r_o} = \frac{V_i g_m r_o}{3r_o + \frac{2}{g_m}}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{g_m r_o (g_m r_o^2)}{3r_o + \frac{2}{g_m}}$$


$$\text{Calculating: } r_o = \frac{A_o}{g_m} = \frac{20}{2 \text{ mA/V}} = 10 \text{ k}\Omega$$

$$\begin{aligned}
 \frac{V_o}{V_i} &= \frac{-(g_m r_o)^2 r_o}{3r_o + 2/g_m} = -\frac{(20)^2 10 \text{ k}\Omega}{3(10 \text{ k}\Omega) + \frac{2}{2 \text{ mA/V}}} \\
 &= -129 \text{ V/V}
 \end{aligned}$$
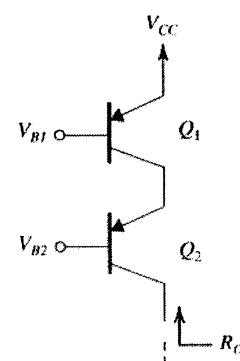
### 6.27

$$\beta = 50, V_A = 5 \text{ V}, I_c = 0.5 \text{ mA}$$

If the base currents are ignored, we can use the same  $r_o$  and  $g_m$  for each transistor.



$$g_m = \frac{I_c}{V_i} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{50}{20 \text{ mA/V}} = 2.5 \text{ k}\Omega$$


$$r_o = \frac{|V_A|}{I_c} = \frac{5 \text{ V}}{0.5 \text{ mA}} = 10 \text{ k}\Omega$$

$$R_o = (g_{m2} r_{o2})(r_{o4} \parallel r_{\pi3})$$

$$R_o = \left( \frac{20 \text{ mA}}{5 \text{ V}} \right) (10 \text{ k}\Omega) (10 \text{ k}\Omega \parallel 2.5 \text{ k}\Omega)$$

$$R_o = 400 \text{ k}\Omega$$

6.28

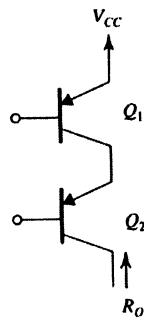

If the transistors are identical,

$$r_{o1} = r_{o2} = r_o = \frac{|V_A|}{I_c}$$

$$g_{m1} = g_{m2} = g_m = \frac{|I_c|}{V_T}$$

$$r_{\pi1} = r_{\pi2} = r_\pi = \frac{\beta}{g_m} = \frac{\beta V_T}{|I_c|}$$

$$R_o = (g_{m2}r_{o2})(r_{o1} \parallel r_{\pi2})$$

$$R_o = \left( \frac{|I_c|}{V_T} \cdot \frac{|V_A|}{|I_c|} \right) \left( \frac{|V_A|}{|I_c|} \parallel \frac{\beta V_T}{|I_c|} \right)$$

$$R_o = \frac{|V_A|}{V_T} \cdot \left[ \frac{\frac{|V_A|}{|I_c|} \cdot \frac{\beta V_T}{|I_c|}}{\frac{|V_A|}{|I_c|} + \frac{\beta V_T}{|I_c|}} \right] \text{ with } I_c = I$$

$$IR_o = \frac{|V_A|}{V_T} \left[ \frac{|V_A| \cdot \beta V_T}{|V_A| + \beta V_T} \right]$$

$$IR_o = \frac{|V_A|}{V_T} \cdot \frac{\beta V_T}{1 + \frac{\beta V_T}{|V_A|}} = \frac{|V_A|}{V_T} \cdot \frac{1}{\frac{1}{\beta V_T} + \frac{1}{|V_A|}}$$

$$IR_o = \frac{|V_A|}{(V_T/|V_A|) + (1/\beta)}$$

For  $|V_A| = 5 \text{ V}$ ,  $\beta = 50$

If  $I = 0.1 \text{ mA}$ ,

$$R_o = \frac{5 \text{ V}}{\frac{0.025 \text{ V}}{5 \text{ V}} + \frac{1}{50}} \cdot \frac{1}{0.1 \text{ mA}} = 2 \text{ M}\Omega$$


If  $I = 0.5 \text{ mA}$ ,

$$R_o = 2 \text{ M}\Omega \left( \frac{0.1 \text{ mA}}{0.5 \text{ mA}} \right) = 400 \text{ k}\Omega$$

If  $I = 1.0 \text{ mA}$ ,

$$R_o = 2 \text{ M}\Omega \left( \frac{0.1 \text{ mA}}{1 \text{ mA}} \right) = 200 \text{ k}\Omega$$

6.29

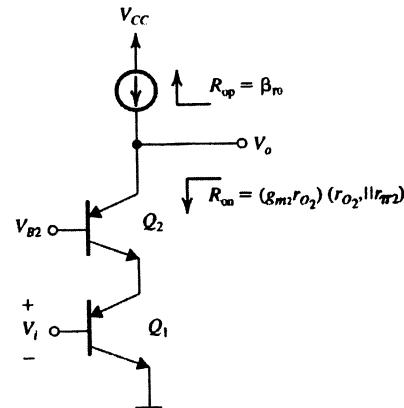

$$r_{o1} = r_{o2} = r_o = \frac{|V_A|}{I} = \frac{100 \text{ V}}{0.1 \text{ mA}} = 1 \text{ M}\Omega$$

$$g_{m1} = g_{m2} = g_m = \frac{|I_c|}{V_T} = \frac{0.1 \text{ mA}}{25 \text{ mV}}$$

$$= 4 \text{ mA/V}$$

$$r_{\pi1} = r_{\pi2} = r_\pi = \frac{\beta}{g_m} = \frac{100}{4 \text{ mA/V}} = 25 \text{ k}\Omega$$

$$A_V = -g_m \cdot (R_{on} \parallel R_{op})$$

$$R_{op} = \beta r_o = 100(1 \text{ M}\Omega) = 100 \text{ M}\Omega$$

$$R_{on} = (g_{m2}r_{o2})(r_{o1} \parallel r_{\pi2})$$

$$= (4 \text{ mA/V} \cdot 1 \text{ M}\Omega)(1 \text{ M}\Omega \parallel 25 \text{ k}\Omega)$$

$$R_{on} = 100 \text{ M}\Omega$$

$$\text{so, } A_V = -4 \text{ mA/V} (100 \text{ M} \parallel 100 \text{ M})$$

$$= 200,000 \text{ V/V}$$

6.30

$$R_o \approx r_o [1 + g_m (R_e \parallel r_\pi)]$$

$$g_m = \frac{|I_c|}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 0.02 \text{ A/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.02 \text{ A/V}} = 5 \text{ k}\Omega$$

when  $R_e = 0$ ,  $R_o = r_o$

a) For  $R_o = 5 \cdot r_o$ ,

$$5 = [1 + g_m (R_e \parallel r_\pi)]$$

$$5 = 1 + 0.02 \text{ A/V} (R_e \parallel 5 \text{ k}\Omega)$$

$$R_e \parallel 5 \text{ k}\Omega = \frac{4}{0.02 \text{ A/V}} = 0.2 \text{ k}\Omega$$

$$\text{Solving, } \frac{R_e \cdot 5 \text{ k}\Omega}{R_e + 5 \text{ k}\Omega} = 0.2 \text{ k}\Omega$$

$$R_e = \frac{5 \text{ k}\Omega(0.2 \text{ k}\Omega)}{4.8 \text{ k}\Omega} = 208 \Omega$$

b) For  $R_o = 10 \cdot r_\pi$ ,

$$10 = 1 + (0.02 \text{ A/V}) \cdot (R_e \parallel 5\text{k})$$

$$\text{So that } \frac{R_e \cdot 5 \text{ k}\Omega}{R_e + 5 \text{ k}\Omega} = \frac{9}{0.02 \text{ A/V}} = 450 \Omega$$

Solving,  $R_e = 495 \Omega$

c) For  $R_o = 50 \cdot r_\pi$ ,


$$50 = 1 + 0.02 \text{ A/V}(R_e \parallel 5 \text{ k}\Omega)$$

$$\frac{R_e \cdot 5 \text{ k}\Omega}{R_e + 5 \text{ k}\Omega} = \frac{49}{0.02 \text{ A/V}} = 2.45 \text{ k}\Omega$$

$$R_e = 4.8 \text{ k}\Omega$$
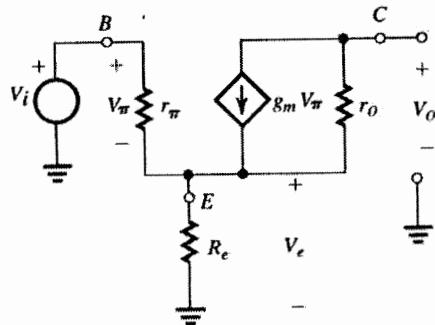
### 6.31

With the output unloaded, the small-signal model can be drawn as follows:



Since no current flows out the collector,

$$V_o = -g_m V_{\pi} r_o + V_e \text{ By voltage division,}$$

$$V_e = \frac{V_i R_e}{r_\pi + R_e} \text{ and } V_\pi = \frac{V_i r_\pi}{r_\pi + R_e}$$

substituting, we get

$$A_{VO} = \frac{V_o}{V_i} = \frac{-g_m r_o r_\pi + R_e}{r_\pi + R_e}$$

$$A_{VO} = -g_m r_o = \frac{r_\pi - R_e}{r_\pi + R_e}$$

dividing by  $r_\pi$ ,

$$A_{VO} = -g_m r_o \cdot \frac{1 - \frac{R_e}{g_m r_\pi r_o}}{1 + \frac{R_e}{r_\pi}}$$


since  $g_m r_\pi = \beta$ ,

$$A_{VO} = -g_m r_o \cdot \frac{1 - \frac{R_e}{\beta r_o}}{1 + \frac{R_e}{r_\pi}}$$

There are several ways to derive the equation for  $G_m$ .

Method 1:

Take the basic small-signal model:

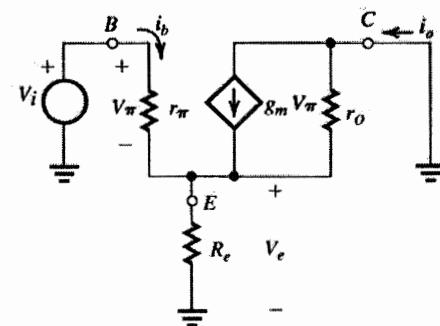

Note that  $V_\pi = V_i - V_e$

$$i_o = \frac{0 - V_e}{r_o} + g_m V_\pi$$

$$i_o = -\frac{V_e}{r_o} + g_m(V_i - V_e)$$

Assuming that  $i_o \gg i_b$

$V_e \approx i_o R_e$ . Then,

$$i_o = \frac{-i_o R_e}{r_o} + g_m V_i + i_o R_e g_m$$

$$i_o \left( 1 + \frac{R_e}{r_o} + R_e g_m \right) = g_m V_i \text{ so that,}$$


$$G_m = \frac{i_o}{V_i} \approx \frac{g_m}{1 + \frac{R_e}{r_o} + g_m R_e}$$

since  $\frac{R_e}{r_o} \ll 1$  usually,

$$G_m = \frac{i_o}{V_i} \approx \frac{g_m}{1 + g_m R_e}$$

**Method 2:**

Consider the model

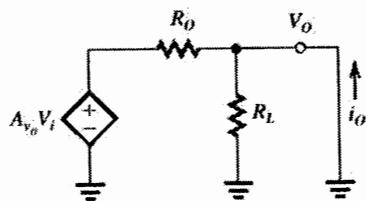

$$R_o = r_o + (R_e \parallel r_\pi) + (g_m r_o)(R_e \parallel r_\pi)$$

or

$$R_o \approx r_o [1 + g_m (R_e \parallel r_\pi)]$$

Shorting the output removes  $R_L$  from the CKT.

$$-A_{vo} = \frac{g_m r_o r_\pi - R_e}{r_\pi + R_e} \quad (\text{from part 1 above})$$

$$G_m = \frac{i_o}{V_i} = \frac{-A_{vo}}{R_o} = \frac{\frac{g_m r_o r_\pi - R_e}{r_\pi + R_e}}{r_o + g_m r_o \frac{R_e r_\pi}{r_\pi + R_e}}$$

$$G_m = \frac{g_m r_o r_\pi - R_e}{r_o(r_\pi + R_e) + g_m r_o R_e r_\pi}$$

Dividing by  $r_o r_\pi$ , we get

$$G_m = \frac{\frac{g_m - \frac{R_e}{r_o r_\pi}}{r_o(r_\pi + R_e)}}{+ g_m R_e}$$

$$\text{since } \frac{r_\pi + R_e}{r_\pi} \approx 1 \text{ and } \frac{R_e}{r_o r_\pi} \ll g_m,$$

$$G_m \approx \frac{g_m}{1 + g_m R_e}$$

with  $\beta = 100$ ,  $r_o = 100 \text{ k}\Omega$ ,

$I_C = 0.2 \text{ mA}$ , and  $R_e = 250 \text{ }\Omega$ ,

$$g_m = \frac{|I_C|}{V_T} = \frac{0.2 \text{ mA}}{25 \text{ mV}} = 8 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{8 \text{ mA}} = 12.5 \text{ k}\Omega$$

$$R_o \approx r_o + (R_e \parallel r_\pi)(1 + g_m)$$

$$\approx r_o + r_o g_m (R_e \parallel r_\pi)$$

$$R_o \approx 100 \text{ k}\Omega + (0.25 \text{ k}\Omega \parallel 12.5 \text{ k}\Omega)$$

$$(100 \text{ k}\Omega) \left( 8 \frac{\text{mA}}{\text{V}} \right)$$

$$= 296 \text{ k}\Omega$$


$$A_{vo} = -g_m r_o \frac{1 - \frac{R_e}{\beta r_o}}{1 + \frac{R_e}{r_\pi}}$$

$$= -(8 \text{ mA/V})(100 \text{ k}\Omega) \cdot \frac{1 - \frac{0.25 \text{ k}\Omega}{100(100 \text{ k}\Omega)}}{1 + \frac{0.25 \text{ k}\Omega}{12.5 \text{ k}\Omega}}$$

$$A_{vo} = -784 \text{ V/V}$$

$$G_m \approx \frac{g_m}{1 + g_m R_e} = \frac{8 \text{ mA/V}}{1 + 8 \text{ mA/V}(12.5 \text{ k}\Omega)}$$

$$= 2.67 \text{ mA/V}$$

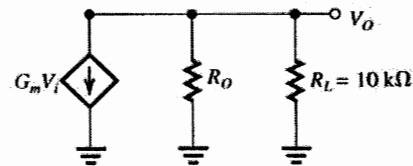


$$A_V = \frac{V_o}{V_i} = -G_m (R_o \parallel R_L)$$

$$= -2.67 \text{ mA/V} (296 \text{ k}\Omega \parallel 10 \text{ k}\Omega)$$

$$A_V = -25.9 \text{ V/V}$$

Note: Depending upon the approximations taken, the values of  $A_V$  may vary slightly.

6.32

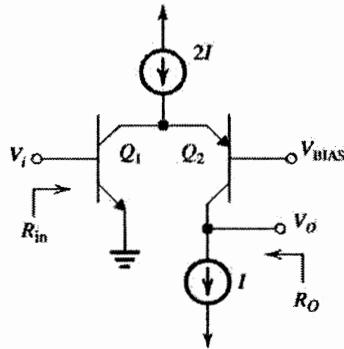

$$g_{m1} = g_{m2} = \frac{|I_{D1}|}{V_T} = \frac{0.1 \text{ mA}}{25 \text{ mV}} = 4 \text{ mA/V}$$

$$r_{\pi 1} = r_{\pi 2} = \frac{\beta}{g_m} = \frac{100}{4 \text{ mA/V}} = 25 \text{ k}\Omega$$

$$r_{o1} = r_{o2} = \frac{|V_A|}{I} = \frac{5 \text{ V}}{0.1 \text{ mA}} = 50 \text{ k}\Omega$$

$$R_{in} = r_{\pi 1} = 25 \text{ k}\Omega$$


$$R_o \approx (g_{m2}r_{o2})(r_{o1} \parallel r_{\pi 2})$$

$$R_o \approx (4 \text{ mA/V})(50 \text{ k}\Omega)(50 \text{ k}\Omega \parallel 25 \text{ k}\Omega) \\ = 3.33 \text{ M}\Omega$$

$$A_{VO} = -G_m R_o \approx -g_{m1} R_o$$

$$= -(4 \text{ mA/V})(3.33 \text{ M}\Omega) = -13.3 \times 10^3 \text{ V/V}$$
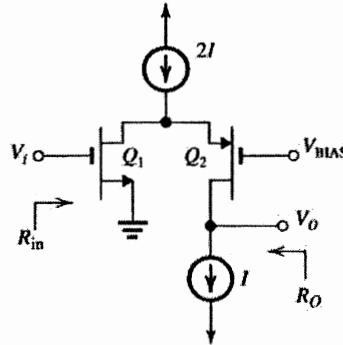
$$A_{VO} = -G_m R_o \approx -g_{m1} R_o \\ = -(4 \text{ mA/V})(2.5 \text{ M}\Omega) = -10 \times 10^3 \text{ V/V}$$



From part (b),

$$g_{m1} = g_{m2} = 1 \text{ mA/V}$$



$$R_{in} = \infty$$

$$R_o = (g_{m2}r_{o2})r_{o1}$$

$$R_o = (1 \text{ mA/V})(50 \text{ k}\Omega)^2 = 2.5 \text{ M}\Omega$$

$$A_{VO} = -G_m R_o = -g_{m1} R_o$$
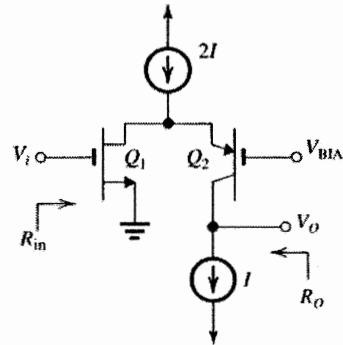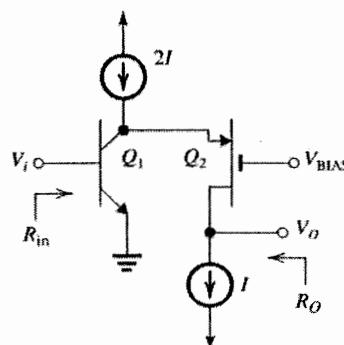
$$A_{VO} = -(1 \text{ mA/V})(2.5 \text{ M}\Omega) = -2,500 \text{ V/V}$$



From above,

$$g_{m1} = 1 \text{ mA/V}$$

$$g_{m2} = 4 \text{ mA/V}, \quad r_{\pi 2} = 25 \text{ k}\Omega$$

$$R_{in} = \infty$$

$$R_o = (g_{m2}r_{o2})(r_{o1} \parallel r_{\pi 2})$$

$$R_o = (4 \text{ mA/V})(50 \text{ k}\Omega)(50 \text{ k}\Omega \parallel 25 \text{ k}\Omega) \\ = 3.33 \text{ M}\Omega$$

$$A_{VO} = -G_m R_o$$

$$A_{VO} \approx -g_{m1} R_o = -1 \text{ mA/V}(3.33 \text{ M}\Omega) \\ = 3.33 \times 10^3 \text{ V/V}$$

$$g_{m1} = 4 \text{ mA/V}$$

$$g_{m2} = \frac{|I_{D2}|}{\frac{|V_{ov}|}{2}} = \frac{0.1 \text{ mA}}{0.2 \text{ V}/2} = 1 \text{ mA/V}$$

$$\text{Again, } R_{in} = r_{\pi 1} = 25 \text{ k}\Omega$$

$$R_o = (g_{m2}r_{o2})r_{o1} = (1 \text{ mA/V})(50 \text{ k}\Omega)^2 \\ = 2.5 \text{ M}\Omega$$

Comments:

(1) A MOSFET for  $Q_1$   
makes  $R_{in} \rightarrow \infty$ .(2) The output resistance when  $Q_2$  is a BJT is limited by  $r_{\pi 2}$ . In cases (a) and (d),  $R_o$  was higher due to the value of  $r_O$  and  $g_{m2}$ .(3) In these four cases,  $A_{VO}$  was highest with two BJTs  $A_{VO}$  was lowest with two MOSFETs.  
These results could be changed with different biasing.

6.33

$$I_D = I_{REF} = 50 \mu A, L = 0.5 \mu m, W = 5 \mu m, V_t = 0.5 V$$

$$I_D = I_D = \frac{1}{2} \mu_n \frac{W}{L} V_D^2$$

$$K_n = 250 \mu A/V^2$$

$$50 = \frac{1}{2} \times 250 \times \frac{5}{0.5} (V_{GS} - 0.5)^2 \Rightarrow V_{GS} = 0.7 V, 0.3 V$$

$$V_{GS} = 0.3 V < V_t \text{ is not acceptable, therefore}$$

$$V_{GS} = 0.7 V$$

$$I_D = I_{RE} = \frac{V_{DD} - V_{GS}}{R} \Rightarrow \frac{1.8 - 0.7}{R} = 0.050 \Rightarrow R = 22 k\Omega$$

$Q_1$  and  $Q_2$  have the same  $V_{GS}$ . The lowest value of  $V_o$  or  $V_{DS2}$  is when  $V_{DS} = V_{GS} - V_t = 0.7 - 0.5 = 0.2 V$

$$\text{hence } V_{o\min} = 0.2 V$$

$$r_o = \frac{V_A}{I_D} = \frac{V_{AL}}{I_D} = \frac{20 \times 0.5}{0.05} = 200 k\Omega$$

$$\Delta I_D \ll \frac{\Delta V_o}{r_o} = \frac{1}{200} = 5 \mu A \Rightarrow \Delta I_D = 5 \mu A$$

6.34

$$\mu_n C_{ox} = 250 \mu A/V^2 \Rightarrow V_A = 20 \mu m, V_t = 0.6 V$$

$$\frac{\Delta I_D}{I_D} = 5 \Rightarrow \Delta I_D = 5 \mu A \text{ for } \Delta V_o = 1.8 - 0.25 = 1.55 V$$

$$r_o = \frac{\Delta V_o}{\Delta I_D} = \frac{1.55}{5 \mu A} = 310 k\Omega$$

$$r_o = \frac{V_{AL}}{I_D} \Rightarrow L = I_D \times \frac{r_o}{V_A} = 0.1 \times \frac{310}{20} = 1.55 \mu m$$

$$V_{o\min} = V_{GS} - V_t = 0.25 \Rightarrow V_{GS} = 0.25 + 0.6 = 0.85 V$$

$$R = \frac{V_{DD} - V_{GS}}{I_D} = \frac{1.8 - 0.85}{0.1} = 9.5 k\Omega$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 \Rightarrow W = \frac{2L I_D}{\mu_n C_{ox} (V_{GS} - V_t)^2}$$

$$\Rightarrow W = \frac{2 \times 1.55 \times 100}{250 (0.85 - 0.6)^2} = 19.84 \mu m$$

6.35

$$V_{DD} = 1.8 V, |V_t| = 0.6 V, \mu_p C_{ox} = 100 \mu A/V$$

$$I_{REF} = 80 \mu A, V_{max} = 1.6 V$$

$$V_{DS} \leq V_{GS} - V_t$$

$$V_{max} = V_{DSmax} = V_{GS} - V_t \Rightarrow I_{REF}$$

$$1.6 - 1.8 = V_{GS} + 0.6 \Rightarrow V_{GS} = -0.8 V$$

$$\Rightarrow V_G = 1.8 - 0.8 = 1 V$$

$$R = \frac{V_G}{I_D} = \frac{1}{0.080} = 12.5 k\Omega$$

$$I_D = \frac{1}{2} \mu_p C_{ox} (V_{GS} - V_t)^2 \frac{W}{L} \Rightarrow W = \frac{2 L I_D}{\mu_p C_{ox} (V_{GS} - V_t)^2}$$

$$W = \frac{2 \times 80}{100 (-0.8 + 0.6)^2} = 40$$

6.36

$$W_2 = 4W_1, L_1 = L_2, V_{ov} = 0.3 V, I_{REF} = 20 \mu A$$

$$I_D = I_{REF} \frac{(W/L)_2}{(W/L)_1} = 20 \times 4 = 80 \mu A$$

$$V_{o\min} = V_{ov} = 0.3 V$$

$$V_t = 0.5 V. \text{ According to Eq. 6.11 } I = \frac{(W/L)_2}{(W/L)_1} I_{REF} \left( 1 + \frac{V_o - V_{GS}}{V_{A2}} \right)$$

$$V_{ov} = V_{GS} - V_t \Rightarrow V_{GS} = 0.3 + 0.5 = 0.8 V$$

$$1 + \frac{V_o - V_{GS}}{25} = 1 \Rightarrow V_o = 0.8 V$$

Or we could simply say  $V_{DS1} = V_{DS2} = V_o$  and

$$\text{Since } V_{DS1} = V_{DS2} = 0.8 V \Rightarrow V_o = 0.8 V$$

$$r_{o2} = \frac{V_A}{I_{D2}} = \frac{2.5}{0.08} = 312.5 k\Omega$$

$$r_{o2} = \frac{\Delta V_o}{\Delta I_D} = \frac{1}{\Delta I_D} \Rightarrow \Delta I_D = \frac{1}{312.5} = 3.2 \mu A$$

6.37

$V_{GS1} = V_{GS2}$  so that  $\frac{I_{D2}}{I_{D1}} = \frac{(W/L)_2}{(W/L)_1}$  and

$$I_{D2} = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$

$$I_{D2} = I_{D3}$$

$V_{GS3} = V_{GS4}$  so that  $\frac{(W/L)_3}{(W/L)_4} = \frac{I_{D3}}{I_{D4}} = \frac{I_{D2}}{I_{D4}}$

$$I_0 = I_{D4} = I_{REF} \frac{(W/L)_2 (W/L)_4}{(W/L)_1 (W/L)_3}$$

6.38

IF the transistor with  $w=10$  is diode-connected,

$$\text{then: } I_2 = 100 \times \frac{10}{10} = 100 \mu\text{A}$$

$$I_3 = 100 \times \frac{40}{10} = 400 \mu\text{A}$$

IF the transistor with  $w=20$  is diode-connected

$$\text{then: } I_2 = 100 \times \frac{10}{20} = 50 \mu\text{A}$$

$$I_3 = 100 \times \frac{40}{20} = 200 \mu\text{A}$$

IF the transistor with  $w=40$  is diode-connected,

$$\text{then: } I_2 = 100 \times \frac{10}{40} = 25 \mu\text{A}$$

$$I_3 = 100 \times \frac{20}{40} = 50 \mu\text{A}$$

So for cases that only one transistor is diode connected, 4 different output currents are possible (depending on the configuration we choose).

IF 2 transistors are diode-connected; then they act as an equivalent transistor whose width is the sum of the widths of each transistor:

IF  $W_{eff} = 10+20$  then  $I_0 = 100 \times \frac{40}{30} = 133 \mu\text{A}$

IF  $W_{eff} = 20+40$  then  $I_0 = 100 \times \frac{60}{60} = 16.7 \mu\text{A}$

IF  $W_{eff} = 40+10$  then  $I_0 = 100 \times \frac{20}{50} = 40 \mu\text{A}$


So 3 different output currents are possible depending on which two transistors are diode-connected. Now we calculate  $V_{SG}$ :

$100 = \frac{1}{2} \times 80 \times \frac{30}{1} (V_{SG} - 0.7)^2 \Rightarrow V_{SG} = 1^V$  for  $W_{eff} = 30$  all have the same  $V_{SG}$  for any given configuration.

For  $W_{eff} = 60 \Rightarrow 100 = \frac{1}{2} \times 80 \times \frac{60}{1} (V_{SG} - 0.7)^2 \Rightarrow V_{SG} = 0.9V$

for  $W_{eff} = 50 \Rightarrow 100 = \frac{1}{2} \times 80 \times \frac{50}{1} (V_{SG} - 0.7)^2 \Rightarrow V_{SG} = 0.93V$

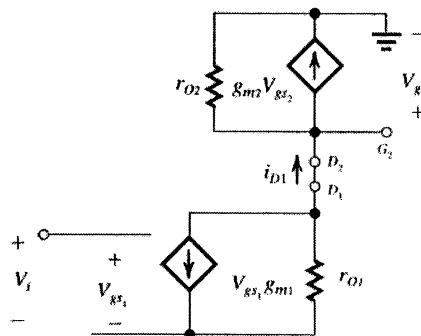6.39 , the small-signal model can be drawn as follows:



$$(1) V_o = -gm_3(r_{o3} \parallel R_L)V_{gs2}$$

$$V_{gs2} = (i_{D1} - g_{m2} V_{gs2}) r_{o2}$$

$$(2) V_{gs2} = i_{D1} r_{o2} - g_{m3} V_{gs2} r_{o2}$$

$$(3) i_{D1} = -V_{gs1} g_{m1} - \frac{V_{gs2}}{r_{o1}}$$

substituting (3) into (2), we get

$$V_{gs2} = -V_{gs1} g_{m1} r_{o2} - \frac{V_{gs2} r_{o2}}{r_{o1}} - g_{m2} V_{gs2} r_{o2}$$

$$(4) V_{gs2} = \frac{-V_{gs1} g_{m1} r_{o2}}{\left(1 + \frac{r_{o2}}{r_{o1}} + g_{m2} r_{o2}\right)}$$

substituting (4) into (1), we get

$$V_o = -g_{m3}(r_{o3} \parallel R_L) \left[ \frac{-V_{gs1} g_{m1} r_{o2}}{\left( 1 + \frac{r_{o2}}{r_{o1}} + g_{m2} r_{o2} \right)} \right]$$

since  $V_{gs1} = V_i$

$$\frac{V_o}{V_i} = g_{m3}(r_{o3} \parallel R_L) \left[ \frac{g_{m1} r_{o2}}{\left( 1 + \frac{r_{o2}}{r_{o1}} + g_{m2} r_{o2} \right)} \right]$$

divide out  $r_o$ :

$$\frac{V_o}{V_i} = \frac{g_{m1} g_{m3} (r_{o3} \parallel R_L)}{\left( \frac{1}{r_{o2}} + \frac{1}{r_{o1}} + g_{m2} \right)}$$


Assuming all  $r_o$  values are  $\gg 1$ ,

$$\frac{V_o}{V_i} = \frac{g_{m1} g_{m3} R_L}{g_{m2}}$$

Since  $I_D = \frac{1}{2} k_p \left( \frac{W}{L} \right) V_{ov}^2$  and  $V_{GS2} = V_{GS3}$ ,

$$V_{ov2} = V_{ov3}, \text{ Also, } g_m = \frac{I_D}{V_{ov}/2}$$

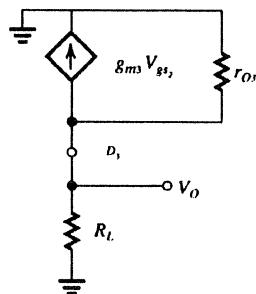
making  $g_m \propto I_D$  which is  $\propto \frac{W}{L}$



Here,  $L_2 = L_3$ , so we could also express the gain as

$$\frac{V_o}{V_i} = g_{m1} R_L \left( \frac{W_3}{W_2} \right)$$

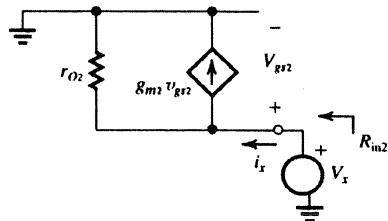Now, to find the resistance looking into the diode-connected drain of  $Q_2$ , we apply a test voltage  $V_x$ :



$$i_x = \frac{V_x}{V_{o2}} + g_{m2} V_{gs2}$$

$$\text{since } V_{gs2} = V_x, \quad i_x = \frac{V_x}{r_{o2}} + g_{m2} V_x$$

$$\frac{i_x}{V_x} = \frac{1}{r_{o2}} + g_{m2}$$

$$R_{in2} = \frac{V_x}{i_x} = r_{o2} \parallel \frac{1}{g_{m2}}$$

The CS gain is

$$\frac{V_{d1}}{V_i} = -g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{o1} \right)$$

## 6.40

$$I_s = 10^{-15} \text{ A}$$

$$a) I_{REF} = I_s e^{V_{BE}/V_T} \Rightarrow V_{BE} = V_T \ln \frac{I_{REF}}{I_s}$$

$$I_{REF} = 10 \mu\text{A} \Rightarrow V_{BE} = 0.025 \ln \frac{10 \times 10^{-6}}{10^{-15}} = 0.576 \text{ V}$$

$$I_{REF} = 10 \text{ mA} \Rightarrow V_{BE} = 0.025 \ln \frac{10^{-15}}{10 \times 10^{-6}} = 0.748 \text{ V}$$

Therefore:

$$10 \mu\text{A} \leq I_{REF} \leq 10 \text{ mA} \Rightarrow 0.576 \leq V_{BE} \leq 0.748 \text{ V}$$

Since  $\beta$  is very high,  $I_B$  is negligible and hence  $I_o \approx I_{REF}$  :  $10 \mu\text{A} \leq I_o \leq 10 \text{ mA}$

$$b) I_o = I_{REF} \frac{1}{1 + 2/\beta}$$

For  $0.1 \leq I_c \leq 5 \text{ mA}$ ,  $\beta$  remains constant at 100.

$$I_{REF} = 10 \text{ mA} \Rightarrow I_o = \frac{10}{1 + \frac{2}{100}} = 9.72 \text{ mA}$$

$$I_{REF} = 0.1 \text{ mA} \Rightarrow I_o = \frac{0.1}{1 + \frac{2}{100}} = 0.098 \text{ mA}$$

$$I_{REF} = 1 \text{ mA} \Rightarrow I_o = \frac{1}{1 + \frac{2}{100}} = 0.98 \text{ mA}$$

$$I_{REF} = 10 \mu\text{A} \Rightarrow$$

6.41

$$I_{S2} = I_{S1} \times m, \quad I_c = I_c \\ I_{REF} = I_c + \frac{I_c}{\beta} + \frac{I_o}{\beta} \quad ①$$

$$V_{BE1} = V_{BE2} \Rightarrow \\ V_T \ln \frac{I_c}{I_{S1}} = V_T \ln \frac{I_o}{I_{S2}}$$

$$\Rightarrow \frac{I_o}{I_c} = \frac{I_{S2}}{I_{S1}} = m \Rightarrow I_c = I_o/m$$


by substituting for  $I_c$  in ①:

$$I_{REF} = \frac{I_o}{m} + \frac{I_o}{m\beta} + \frac{I_o}{\beta} \Rightarrow \frac{I_o}{I_{REF}} = \frac{m}{1 + \frac{1}{\beta} + \frac{m}{\beta}}$$

$$\frac{I_o}{I_{REF}} = \frac{m}{1 + \frac{1+m}{\beta}}$$

This result is the same as Eq. 6.22.

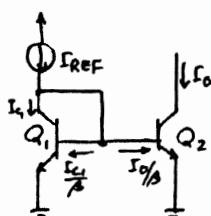For large  $\beta$ ,  $\frac{I_o}{I_{REF}} = m$ , with finite  $\beta$  this ratio drops to  $\frac{I_o}{I_{REF}} = \frac{m}{1 + \frac{1+m}{\beta}}$ . To keep the introduced error within 5%:  $0.95m = \frac{m}{1 + \frac{1+m}{\beta}}$   
 $\beta_{min} = 80 \Rightarrow 0.95 = \frac{1}{1 + \frac{1+m}{80}} \Rightarrow m = 3.21$



6.43


$$I_{c1} = I_{c2} = I_{R1}$$

$$V_{B1} = 10 - 0.7 = 9.3V, V_{B2} = -10 + 0.7 = -9.3V, I_{R1} = \frac{9.3 + 9.3}{10} \\ \Rightarrow I_{R1} = 1.86mA = I_{c1} = I_{c2} = I_{c3} = I_{c4} = I_{c5} = I_{c6}$$

$$V_{c3} = 1.86 \times 2^k = 3.72V \Rightarrow V_{c5} = 0.7V$$

$$V_{c6} = 5 - 1.86 \times 1 = 3.14V \Rightarrow I_{c9} = I_{c8} = I_{c7} = I_{c2} = 1.86mA$$
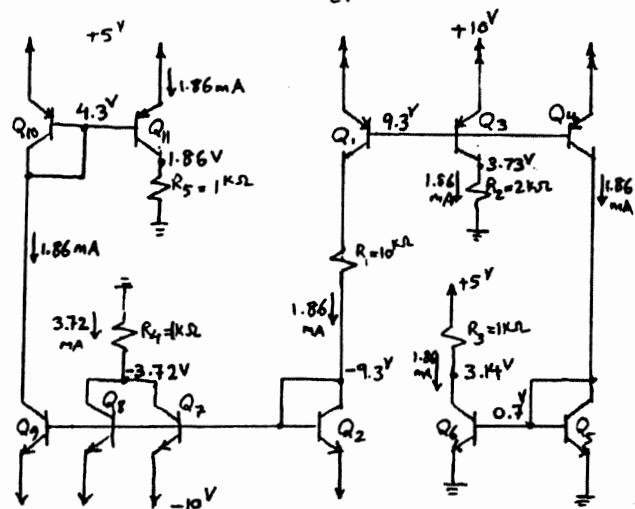
$$I_{R4} = 2 \times 1.86 = 3.72mA \Rightarrow V_{c7} = -3.72 \times 1 = -3.72V$$




$$I_{c10} = I_{c9} = 1.86mA$$

$$V_{c9} = V_{c10} = V_{B10} = 5 - 0.7 = 4.3V$$

$$I_{c11} = I_{c10} = 1.86mA$$

$$V_{c11} = 1.86 \times 1 = 1.86V$$

6.42

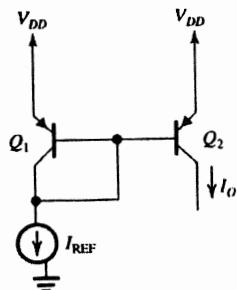

For identical transistors, the transfer ratio is the same as eq. (7.69):

$$\frac{I_o}{I_{REF}} = \frac{1}{1 + 2/\beta} = \frac{1}{1 + \frac{2}{20}} = 0.91$$

6.44

a)

$$R = 10 \text{ k}\Omega$$

$$V_1 = -0.7 \text{ V} \Rightarrow I_{C_1} = \frac{-0.7 - (-10.7)}{10 \text{ k}} = 1 \text{ mA}$$

$$\underline{I_{C_1} = 1 \text{ mA}}$$

$$V_2 = 5.7 - 0.7 = 5 \text{ V}$$

$$I = I_{C_3} + I_{C_4}, \quad I_{C_3} = I_{C_4} = I_{C_1} \Rightarrow I = 2 \times 1 = 2 \text{ mA}$$

$$V_3 = 0 + 0.7 = 0.7 \text{ V}$$

$$V_4 = -10.7 + 1 \times 10 \text{ k} = -0.7 \text{ V}$$

$$V_5 = -10.7 + 1 \times \frac{10 \text{ k}}{2} = -5.7 \text{ V}$$

b)  $R = 100 \text{ k}\Omega$

$$V_1 = -0.7 \text{ V} \Rightarrow I_{C_1} = \frac{-0.7 + 10.7}{100 \text{ k}} = 0.1 \text{ mA}$$


$$I = 2 I_{C_1} = 0.2 \text{ mA}$$

$$V_3 = 0.7 \text{ V}, \quad V_2 = 5.7 - 0.7 = 5 \text{ V}$$


$$V_4 = -10.7 + 1 \times 100 = -0.7 \text{ V}$$

$$V_5 = -10.7 + 0.1 \times \frac{100}{2} = -5.7 \text{ V}$$

6.45

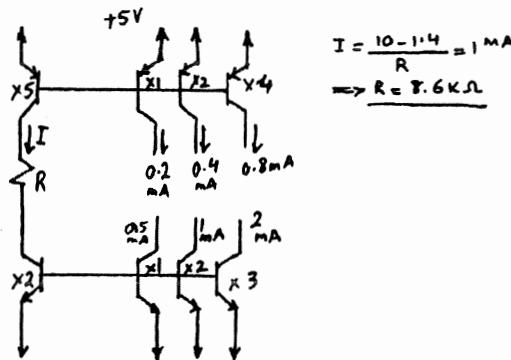

6.46

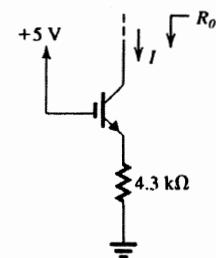

$$I_E = \frac{5 - V_{BE}}{4.3 \text{ k}\Omega} = \frac{5 - 0.7}{4.3 \text{ k}\Omega} = 1 \text{ mA}$$

since  $\beta \gg 1$ ,  $I = I_C \approx I_E \approx 1 \text{ mA}$

To find the output resistance, we can use eq. (7.50) or since  $g_m r_o \gg 1$ ,

$$R_o \approx r_o + g_m r_o (R_e \parallel r_\pi)$$

In this case,

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 0.04 \text{ A/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.04} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{1 \text{ mA}} = 100 \text{ k}\Omega$$

$$R_o = 100 \text{ k}\Omega + (0.04 \text{ A/V})(100 \text{ k}\Omega)$$

$$(4.3 \text{ k}\Omega \parallel 2.5 \text{ k}\Omega)$$

$$R_o = 6.42 \text{ M}\Omega$$

If the collector voltage changes by 10 V,

$$\Delta I = \frac{\Delta V}{R_o} = \frac{10 \text{ V}}{6.42 \text{ M}\Omega} = 1.56 \mu\text{A}$$

6.47

All the transistors in this problem are operating at a bias current of 0.5mA and thus have:

$$r_e = 50\Omega, g_m = 20 \text{ mA/V}, r_{\pi} = 5 \text{ k}\Omega$$

$$C_{N1} + C_{M1} = \frac{20 \text{ pF}}{2\pi \times 400 \text{ Hz}} = 8 \text{ pF}$$

$$\text{Since } C_M = 2 \text{ pF} \Rightarrow C_{N1} = 6 \text{ pF} \Rightarrow r_o = \infty, r_K = 0$$

a) Common-Emitter amplifier:

$$R_{S1} = 10 \text{ k}\Omega, R_C = 10 \text{ k}\Omega$$

$$A_H = -\frac{r_{\pi}}{R_{S1} r_{\pi}} g_m R_C = -\frac{5}{10+5} \cdot 20 \times 10 = -66.7 \text{ V/V}$$

$$f_H = \frac{1}{2\pi (R_{S1} || r_{\pi}) [C_{N1} + (1+g_m R_C) C_{M1}]} \Rightarrow$$

$$f_H = \frac{1}{2\pi (10 || 5) [6 + (1+20 \times 10) 2]} = 117 \text{ kHz}$$

b) Cascode:

$$A_H = -\frac{\beta_1 \alpha_2 R_C}{R_{S1} g_m + r_{\pi}} = -\frac{100 \times 0.99 \times 10}{10+5} = -66 \text{ V/V}$$

$$\text{Input pole: } f_{P1} = \frac{1}{2\pi (R_{S1} || r_{\pi}) (C_{N1} + 2C_{M1})}$$

$$f_{P1} = \frac{1}{2\pi (10 || 5) (6+4)^2} = 4.77 \text{ MHz}$$

$$\text{Output pole: } f_{P3} = \frac{1}{2\pi C_{M2} R_C} = \frac{1}{2\pi \times 2 \times 10} = 7.96 \text{ MHz}$$

Pole at midband node:

$$f_{P2} = \frac{1}{2\pi C_{M2} r_{e2}} = \frac{1}{2\pi \times 6 \times 50} = 530.5 \text{ MHz}$$

Very high

$$f_H = \sqrt{\frac{1}{(\frac{1}{f_{P1}})^2 + (\frac{1}{f_{P2}})^2}} = 4.1 \text{ MHz}$$

c) CC-CB Cascade (Modified diff. amplifier)

$$A_H = \frac{\beta R_C}{R_{S1} g_m + 2r_{\pi}} = \frac{100 \times 10}{10+10} = 50 \text{ V/V}$$

$$\text{Input pole: } f_{P1} = \frac{1}{2\pi (R_{S1} || 2r_{\pi}) (C_{N1/2} + C_{M1})}$$

$$f_{P1} = \frac{1}{2\pi (10 || 10) (3+2)^2} = 6.4 \text{ MHz}$$

$$\text{Output pole: } f_{P2} = \frac{1}{2\pi C_{M2} R_C} = \frac{1}{2\pi \times 2 \times 10} = 7.96 \text{ MHz}$$

$$\text{Thus: } f_H = \frac{1}{\sqrt{(\frac{1}{f_{P1}})^2 + (\frac{1}{f_{P2}})^2}} = 5 \text{ MHz}$$

d) CC-CE Cascade:

$$A_H = -\frac{(\beta_1 + 1)\beta_2 R_C}{R_{S1} g_m + r_{\pi} + (\beta_1 + 1)r_{\pi 2}} = -\frac{101 \times 100 \times 10}{10+5+101 \times 5} = -194 \text{ V/V}$$

Refer to Example 6.13 in :

$$R_{M1} = (R_{S1} g_m || r_{\pi}) = 10^2 || (\beta_1 + 1) [r_{e1} + r_{\pi 2}]$$

$$R_{M1} = 10^2 || 101 \times [0.05 + 5] = 9.81 \text{ k}\Omega$$

$$R_{\pi 1} = r_{\pi 1} || \frac{R_{S1} r_{\pi 2}}{1 + g_m r_{\pi 2}} = 5 || \frac{10 + 5}{1 + 20 \times 5} = 144 \text{ }\Omega$$

$$R_T = r_{\pi 2} || \frac{r_{\pi 1} + R_{S1} g_m}{\beta_1 + 1} = 5 || \frac{5 + 10}{101} = 144 \text{ }\Omega$$

$$\text{where } C_T = C_{\pi 2} + C_{M2} (1 + g_m R_C) = 6 + 2(1+200) \\ C_T = 408 \text{ pF}$$

$$R_{M2} = R_C = 10 \text{ k}\Omega$$

$$C_T = C_{\pi 2} R_{\pi 1} + C_{\pi 1} R_{\pi 2} + C_T R_T + C_{M2} R_{M2}$$

$$T_A = 2 \times 9.81 + 6 \times 0.144 + 408 \times 0.144 + 2 \times 10$$

$$T_A = 19.62 + 0.86 + 58.75 + 20 = 99.2 \text{ ns}$$

$$f_H = \frac{1}{2\pi T_A} = \frac{1}{2\pi \times 99.2 \text{ ns}} = 1.6 \text{ MHz}$$

e) Folded Cascode:

$$A_H = -\frac{\beta_1 \alpha_2 R_C}{R_{S1} g_m + r_{\pi 1}} = -\frac{100 \times 0.99 \times 10}{10+5} = -66 \text{ V/V}$$

Input pole:

$$f_{P1} = \frac{1}{2\pi (R_{S1} g_m || r_{\pi 1}) (C_{N1} + 2C_{M1})} = \frac{1}{2\pi (10 || 5) (6+4)}$$

$$f_{P1} = 4.77 \text{ MHz}$$

$$\text{At middle: } f_{P2} = \frac{1}{2\pi C_{M2} r_{e2}} = \frac{1}{2\pi \times 6 \times 0.05} = 530 \text{ MHz}$$

$$\text{At output: } f_{P3} = \frac{1}{2\pi C_{M2} R_C} = \frac{1}{2\pi \times 2 \times 10} \Rightarrow \text{very high!}$$

$$f_{P3} = 7.96 \text{ MHz}$$

$$\text{Thus: } f_H = \frac{1}{\sqrt{\frac{1}{f_{P1}}^2 + \frac{1}{f_{P2}}^2}} = 4.1 \text{ MHz}$$

f) CC-CB Cascade:

$$A_M = \frac{(g_m + 1)\alpha_s R_o}{R_{sig} + (g_m + 1)2r_e} = \frac{10 \times 0.99 \times 10}{10 + 10 \times 0.1} \approx 50 \text{ V/V}$$

$$\text{Input pole: } f_{p1} = \frac{1}{2\pi(R_{sig} \parallel 2r_e)(C_{T/2} + S_L)} \\ f_{p1} = \frac{1}{2\pi(10^k \parallel 10^k)(3^P + 2^P)} = 6.4 \text{ MHz}$$

$$\text{Output pole: } f_{p2} = \frac{1}{2\pi R_o C_L} = \frac{1}{2\pi \times 10^k \times 2^P} = 7.96 \text{ MHz}$$

$$f_H \approx \frac{1}{\sqrt{\frac{1}{6.4^2} + \frac{1}{2.96^2}}} = 5 \text{ MHz}$$

Summary of results:

Configuration	$A_M (\text{V/V})$	$f_H (\text{MHz})$	G.B.
a) CE	-66.7	0.117	7.8
b) Cascode	-66	4.1	271
c) CC-CB cascade	+50	5.0	250
d) CC-CE cascade	-194	1.6	310
e) Folded cascode	-66	4.1	271
f) CC-CB cascade	+50	5.0	250

## 6.48

$$I_{REF} = 80 \mu A = I_4 = I_1 = I_2 = I_3$$

All transistors have the same  $g_m$ ,  $r_o$ ,  $V_{ov}$  values.

$$I = \frac{1}{2} k_n' \frac{W}{L} V_{ov}^2 \Rightarrow 0.08 = \frac{1}{2} \times 4 \times V_{ov}^2 \Rightarrow V_{ov} = 0.2 \text{ V}$$

$$V_{GS} = V_{ov} + V_t = 0.2 + 0.5 = 0.7 \text{ V}$$

$$V_{G1} = V_{GS} = 0.7 \text{ V} = V_{S4} \Rightarrow V_{G4} = 0.7 + V_{GS4} = 1.4 \text{ V}$$

$$\Rightarrow V_{G3} = 1.4 \text{ V} \Rightarrow V_{S3} = 1.4 - V_{GS} = 0.7 \text{ V}$$

$$\Rightarrow V_{G2} = V_{GS} = V_{S3} + V_{ov} = 0.9 \text{ V}$$

As explained, the voltage at the gate of  $Q_3$

is  $2V_{GS}$  which implies voltage of  $V_{GS} = V_{ov} + V_t$  at the source of  $Q_3$ . For minimum allowable voltage at the output,  $V_{DS} = V_{ov}$  or equivalently  $V_{min} = V_{ov} + V_{GS}$

$$V_{min} = V_{ov} + V_{ov} + V_t = 2V_{ov} + V_t$$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.08}{0.2} = 0.8 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{8}{0.08} = 100 \text{ k}\Omega$$

Using Eq. 6.189:  $R_o = r_{o3} + [1 + (g_{m3} + g_{mb3})r_{o3}]r_{o2}$

$$R_o = 100 \text{ k} + [1 + 0.8 \times 100] \times 100 = 8.2 \text{ M}\Omega$$

## 6.49

$$I_{REF} = 25 \mu A,$$

$$I_4 = 25 \mu A = I_1 = W_1 = W_4 = 2 \mu m$$

$$W_2 = W_3 = 40 \mu m$$

$$I_1 = \frac{1}{2} k_n' \frac{W_1}{L_1} V_{ov1}^2 \Rightarrow 25$$

$$= \frac{1}{2} \times 200 \times \frac{2}{1} V_{ov1}^2 \Rightarrow V_{ov1} = 0.354 \text{ V}$$

$$V_{ov1} = V_{ov2} \Rightarrow \frac{I_2}{I_1} = \frac{(W/L)^2}{(W/L)_1}$$

$$\Rightarrow I_2 = 25 \times \frac{40}{2} = 500 \mu A$$

$$I_2 = 0.5 \text{ mA} = I_3$$

$$I_O = 0.5 \text{ mA}$$

$$V_{GS1} = V_{ov1} + V_t = 0.354 + 0.6 = 0.954 \text{ V}$$

$$V_{G1} = 0.954 \text{ V}$$

$$V_{G4} = V_{GS1} + V_{GS4},$$

Since  $I_1 = I_4$  and  $W_1 = W_4$  then

$$V_{GS1} = V_{GS4} \Rightarrow V_{G4} = 2V_{GS1}$$

$$= 1.91 \text{ V} = V_{G3}$$

The lowest possible voltage for the output is when  $Q_3$  has  $V_{DS3} = V_{ov3}$  or

$$V_{O \min} = V_{G3} - V_{GS3} + V_{ov3}$$

since  $V_{GS1} = V_{GS2}$  and  $I_2 = I_3$  then

$$V_{GS3} = V_{GS1}$$

$$\Rightarrow V_{O \min} = 1.91 - 0.954 + 0.354 = 1.31 \text{ V}$$

$$g_{m2} = g_{m3} = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.5}{0.354}$$

$$= 2.82 \text{ mA/V}$$

6.50


$$r_{o2} = r_{o3} = \frac{V_A}{I_D} = \frac{20}{0.5} = 40 \text{ k}\Omega$$

Eq. 6.189:

$$R_O = r_{o3} + [1 + (g_{m3} + g_{mb3})r_{o3}]r_{o2}$$

$$R_O = 40 \text{ k}\Omega + [1 + 2.82 \text{ k}\Omega \times 40 \text{ k}\Omega \times 40 \text{ k}\Omega] \times 40 \text{ k}\Omega = 4.6 \text{ M}\Omega$$

6.51

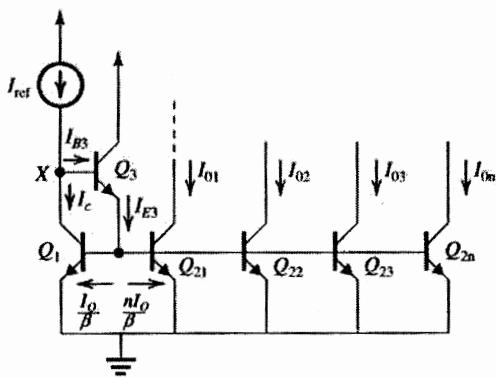

$$I_{01} = I_{02} = I_{03} = \dots = I_{0n} = I_0$$

The emitter of  $Q_3$  supplies the base currents for all transistors so

$$I_{E3} = \frac{(n+1)I_0}{\beta}$$

$$I_{REF} = I_{B3} rI_0 = \frac{(n+1)I_0}{\beta(\beta+1)} + I_0$$

$$\frac{I_0}{I_{REF}} = \frac{1}{1 + \frac{(n+1)}{\beta(\beta+1)}}$$

for deviation of .1% from unity:

$$\frac{99.9}{100} = \frac{1}{1 + \frac{(n+1)}{100(101)}} \Rightarrow n \approx 9$$

6.52

Since  $Q_{21}, Q_{22}, \dots, Q_{2n}$  are all matched to  $Q_1$ :

$$I_{01} = I_{02} = \dots = I_{0n} = I_0$$


The emitter of  $Q_3$  supplies the basecurrent for all transistors, so  $I_{c3} = \frac{(n+1)I_0}{\beta}$

A node equation at the base of  $Q_3$  yields:

$$I_{REF} = I_0 + \frac{(n+1)I_0}{\beta(\beta+1)}, \text{ Thus: } \frac{I_0}{I_{REF}} = \frac{1}{1 + \frac{n+1}{\beta^2}}$$

For a deviation from unity of less than 0.1%:  $\frac{99.9}{100} = \frac{1}{1 + \frac{n+1}{\beta^2}} \Rightarrow \frac{n+1}{\beta^2} = \frac{1}{999}$
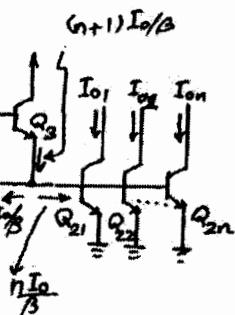
$$\Rightarrow n = \frac{\beta^2}{999} - 1 \Rightarrow n \leq 9$$




6.53


$$I_{REF} = 0.1 \text{ mA} = \frac{5 - 0.7 - 0.7 - (-5)}{R}$$

$$\Rightarrow R = 86 \text{ k}\Omega$$

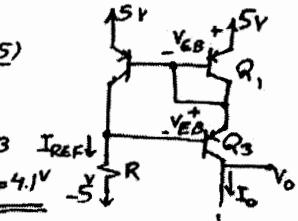$V_{max}$  is obtained when  $Q_3$  is saturated:  $V_{max} = 5 - 0.7 - 0.2 = 4.1 \text{ V}$



6.54

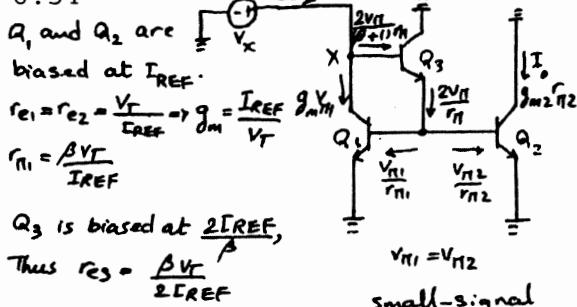

Refer to the small-circuit analysis performed directly on the circuit. Since the current in the emitter of  $Q_3$  is  $\frac{2V_{n1}}{r_{n1}}$ , the voltage  $V_{n3}$  will be:  $V_{n3} = \frac{2V_{n1}}{r_{n1}} \times r_{e3}$ .

$$V_x = V_{n2} + V_{n1} = \frac{2V_{n1} \cdot r_{e3}}{r_{n1}} + V_{n1} = V_{n1} \left(1 + 2 \frac{r_{e3}}{r_{n1}}\right)$$

$$V_x = V_{n1} \left(1 + 2 \frac{\beta V_T}{2I_{REF}} \times \frac{I_{REF}}{\beta V_T}\right) = 2V_{n1}$$

$$\text{and } i_x \approx g_{m1} V_{n1}. \text{ Thus: } R_{in} = \frac{V_x}{i_x} = \frac{2}{g_{m1}} = \frac{2V_T}{I_{REF}}$$


$$\text{For } I_{REF} = 100 \mu A \Rightarrow R_{in} = \frac{2 \times 0.025}{0.1} = 0.5 k\Omega$$

6.55

All the output currents are equal to  $I_o$ , then we have:  $I_{REF} = 2I_o + \frac{I_o}{\beta} \Rightarrow I_o = \frac{1}{2 + 1/\beta}$   
 $I_o$  is ideally  $I_{REF}/2$ , For 5% lower  $I_o$ :

$$0.95 \times \frac{I_{REF}/2}{I_{REF}} = \frac{1}{2 + 1/\beta} \Rightarrow \beta = 104.5 \approx 105$$

$\beta = 105$

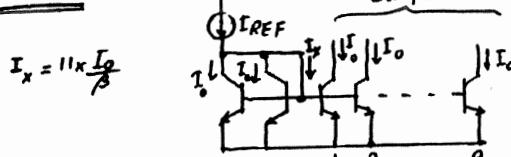

6.56

a) See the analysis on the circuit.

$$I_{REF} = I + \frac{\beta + 2}{\beta(\beta + 1)} I = I \frac{\beta^2 + 2\beta + 2}{\beta(\beta + 1)}$$

$$I_{o1} = I_{o2} = \frac{1}{2} \frac{\beta + 2}{\beta + 1} I$$

$$\frac{I_{o1}}{I_{REF}} = \frac{I_{o2}}{I_{REF}} = \frac{1}{2} \frac{\beta(\beta + 2)}{\beta^2 + 2\beta + 2} = \frac{1}{2} \times \frac{1}{1 + 2/(\beta^2/2\beta)}$$

$$\frac{I_{o1}}{I_{REF}} = \frac{1}{2} \frac{1}{1 + 2/\beta^2}$$

Observe that the deviation factor  $\frac{1}{1 + 2/\beta^2}$  is independent of the number of outputs or the value of each output, i.e.:


The current  $I_{REF}$  can be split into any number of outputs through an appropriate combinations of parallel-connected transistors. ( $Q_3$  and  $Q_4$  in this case) The reason the error factor remains unchanged at  $\frac{1}{1 + 2/\beta^2}$  is that the base current


that need to be supplied by  $I_{REF}$  (subtract from  $I_{REF}$ ) remains unchanged.

b) The  $I$  mA reference current can be used to generate three output currents of 1, 2, 4 mA by using 3 transistors in parallel having relative area ratios of 1, 2, 4 as shown:

$$\frac{I_{o1}}{I_{REF}} = \frac{1}{7} \frac{1}{1 + 2/\beta^2} \Rightarrow I_{o1}$$

$$= 0.998 \text{ mA (1 mA ideally)}$$

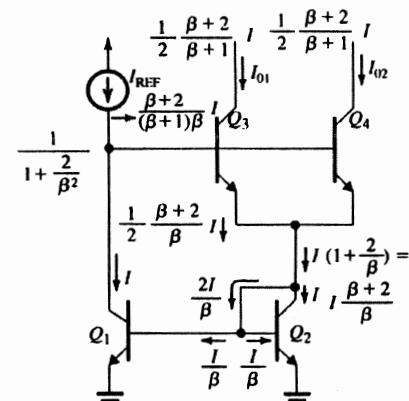

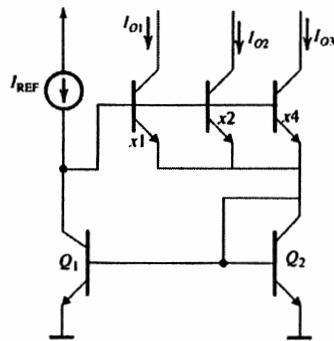


$$\frac{I_{O2}}{I_{REF}} = \frac{2}{7} \frac{1}{1 + 2/\beta^2} \Rightarrow I_{O2}$$

= (1.996) mA (2 mA ideally)

$$\frac{I_{O3}}{I_{REF}} = \frac{4}{7} \frac{1}{1 + 2/\beta^2} \Rightarrow I_{O3}$$

= 3.992 mA (4 mA ideally)

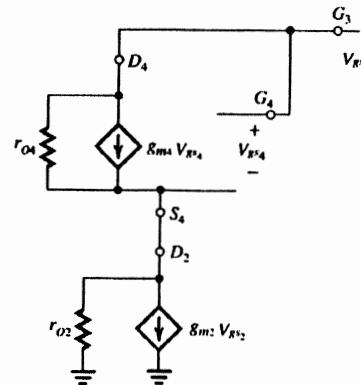(e) If a small-signal model is added to account for  $Q_i$ , the circuit is changed to



Since  $V_{D24} = V_{GS4} = -g_m4 V_{R34} r_{o4}$   
(no current into gate 3)

$V_{GS4} = V_{DS4} = 0$  so that  $V_{D2} = V_G$  and  
there is no effect.

$$R_o \approx (g_{m3} r_{o3}) r_{o2}$$

$$g_m = \frac{I_D}{V_{ov}/2} = \frac{0.1 \text{ mA}}{0.2 \text{ V}/2} = 1 \text{ mA/V}$$

$$R_o \approx (1 \text{ mA/V})(200 \text{ k}\Omega)^2 = 40 \text{ M}\Omega$$

6.57  $V_{ov} = \sqrt{\frac{2 I_D}{\mu_n C_{ox} (W/L)}}$

$$V_{ov} = \sqrt{\frac{2(100 \mu\text{A})}{(400 \mu\text{A/V})(12.5)}} = 0.2 \text{ V}$$

since no value is given for  $V_m$ , we have to estimate  
this with  $\mu_n C_{ox} = 400 \mu\text{A/V}^2$ .

this fabrication process is similar to  
the 0.18  $\mu\text{m}$  technology. We will therefore  
approximate  $V_m$  as approximately 0.5 V.

$$V_{GS} = V_{in} + V_{ov} = 0.5 \text{ V} + 0.2 \text{ V} = 0.7 \text{ V}$$

(b)  $V_{DS2} = V_{GS1} + V_{GS3} = 1.4 \text{ V}$ , which is  
 $\approx (2 \cdot V_{ov})$

$$r_o = \frac{V_A}{I} = \frac{20 \text{ V}}{0.1 \text{ mA}} = 200 \text{ k}\Omega$$

$$\Delta I = \frac{\Delta V_{ov}}{r_o} = \frac{1.4 - 0.7}{200 \text{ k}\Omega} = 0.35 \mu\text{A}$$

$$I_o \approx I_{REF} - \Delta I$$


so that,

$$I_o \approx 100 - 3.5 = 96.5 \mu\text{A}$$

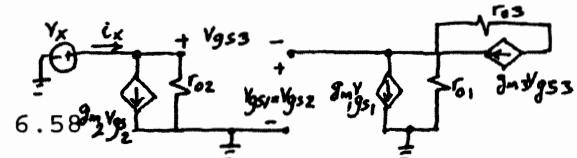(c)  $I_o \approx I_{REF}$

$$(d) V_{v_{min}} = V_{in} + 2 V_{ov}$$

$$= 0.5 + 2(0.2 \text{ V}) = 0.9 \text{ V}$$



$$i_x = g_{m2} v_{gs2} \quad (1)$$

$$v_{gs2} + v_{gs3} = V_x$$

Since  $Q_2$  and  $Q_3$  have the same parameters  
and same current, therefore  $v_{gs2} = v_{gs3}$

$$V_x = 2v_{gs2} \Rightarrow v_{gs2} = \frac{V_x}{2}$$

Substitute for  $v_{gs2}$  in (1):

$$i_x = g_{m2} \times \frac{V_x}{2}$$

$$R_{in} = \frac{V_x}{i_x} = \frac{2}{g_{m2}}$$



6.63

$$I = 2mA \Rightarrow g_m = \frac{2}{0.025} = 80mA/V \Rightarrow r_n = \frac{\beta}{g_m} = 1.25^{k\Omega}$$

$$r_e = \frac{r_T}{\beta+1} = 12.4\Omega$$

$$f_T = \frac{g_m}{2\pi(C_n + C_A)} \Rightarrow C_n + C_A = \frac{80^m}{2\pi \times 400 \times 10^6} = 31.85 \text{ pF}$$

$$\Rightarrow C_n = 31.85 - 2 = 29.85 \text{ pF}$$

$$A_M = \frac{R_L}{\frac{R_{sig} + R_L}{\beta+1} + R_L} = \frac{1}{\frac{R_{sig}}{101} + \frac{0.0124}{101} + 1} = \frac{1}{1.0124 + \frac{R_{sig}}{101}}$$

$$R'_L = R_L = 1k\Omega \quad , \quad R'_{sig} = R_{sig} + r_x = R_{sig}$$

$$R_{\mu} = R_{sig} \parallel [r_n + (\beta+1)R'_L] \quad (\text{Eq. 6.179})$$

$$R_{\mu} = R_{sig} \parallel (1.25 + 101 \times 1) = R_{sig} \parallel 102.25^k$$

$$R_H = \frac{R_{sig} + R'_L}{1 + \frac{R_{sig}}{r_n} + \frac{R'_L}{r_C}} \quad (\text{Eq. 6.180})$$

$$R_H = \frac{R_{sig} + 1k}{1 + 0.8R_{sig} + 80} = \frac{R_{sig} + 1}{0.8R_{sig} + 81}$$

$$f_H = \frac{1}{2\pi(R_n C_n + R_H C_H)} = \frac{1}{2\pi(29.85 R_H + 2 R_{\mu})}$$

a)  $R_{sig} = 1^{k\Omega}$ :  $A_M = 0.978 V/V$

$$R_{\mu} = 0.99^{k\Omega}, R_H = 24.4\Omega \Rightarrow f_H = 58.8 \text{ MHz}$$

b)  $R_{sig} = 10k\Omega$ :  $A_M = 0.9 V/V$

$$R_{\mu} = 9.11 k\Omega, R_H = 124\Omega \Rightarrow f_H = 7.27 \text{ MHz}$$

c)  $R_{sig} = 100k\Omega$ :  $A_M = 0.499 V/V$

$$R_{\mu} = 50.6 k\Omega, R_H = 627\Omega \Rightarrow f_H = 1.34 \text{ MHz}$$

6.64

Each of the transistors is operating at a bias current of approximately  $100\mu A$ . Thus:

$$g_m = \frac{0.1}{0.025} = 4mA/V \quad \Rightarrow r_{\pi} = \frac{100}{4} = 25k\Omega$$

$$r_e \approx 250\Omega \quad \Rightarrow r_o = \frac{100}{0.1} = 1M\Omega$$

$$C_{\pi} + C_{\mu} = \frac{g_m}{2\pi f_p} = \frac{4}{2\pi \times 4000} = 1.39pF \Rightarrow C_{\pi} = 1.39pF$$

a)  $R_{in} = (\beta+1) [r_{\pi 1} + (r_{\pi 2} || r_o)]$

$$R_{in} = 101 [250k \times 10^{-3} + 25k || 1M] \approx 2.5k\Omega$$

$$A_M = - \frac{R_{in}}{R_{in} + R_{sig}} \times \frac{r_{\pi 2} || r_o}{r_{\pi 1} + (r_{\pi 2} || r_o)} \times g_{m2} r_o$$

$$A_M = - \frac{2.5}{2.5 + 0.01} \times \frac{25k || 1M}{0.25 + (25k || 1M)} \times 4 \times 1M$$

$$A_M = -3943.6 V/V$$


b) To calculate  $f_H$ , refer to

$$R_{H1} = R_{sig} || R_{in} = 10^k || 2.5^M = 10k\Omega$$

$$R_{in2} = r_{\pi 2} || r_o$$


$$R_{in2} = 25k || 1M$$

$$R_{in2} = 24.4k\Omega$$

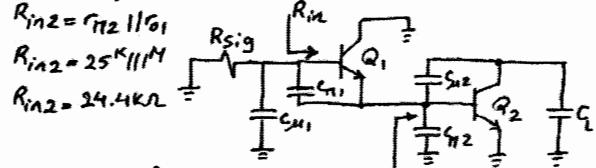


$$R_{pi1} = \frac{R_{sig} + R_{in2}}{1 + \frac{R_{sig}}{R_{pi1}} + \frac{R_{in2}}{r_{\pi 1}}}$$
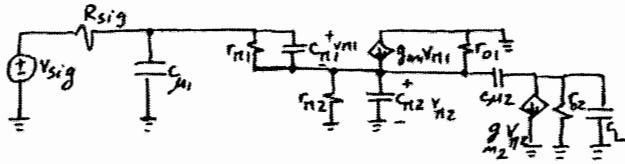
$$R_{pi1} = \frac{10 + 24.4}{1 + \frac{10}{25} + \frac{24.4}{0.25}} = 0.35k\Omega$$



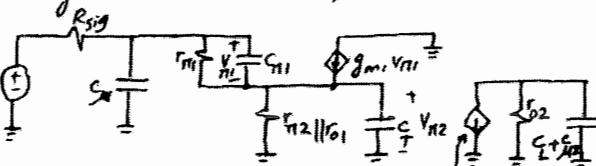Using Miller's Theorem for  $C_{\mu 2}$ :



$$C_T = C_{\pi 2} + C_{\mu 2} (1 + g_{m2} r_o)$$

$$C_T = 1.39 + 0.2(1 + 4 \times 1000) = 801.6 pF$$

$$R_T = r_{\pi 2} || r_o || \frac{r_{\pi 1} + R_{sig}}{\beta + 1} = 25k || 1000k || \frac{25 + 10}{101}$$

$$R_T = 342\Omega$$

$$R_{\mu 2} = r_o = 1000k$$

$$C_T = C_{\pi 1} R_{\pi 1} + C_{\pi 2} R_{\pi 2} + C_T R_T + (C_{\mu 2} + C_L) R_{\mu 2}$$

$$C_T = 0.2 \times 10 + 1.39 \times 0.35 + 801.6 \times 0.342 + (0.2 + 1) \times 1000$$

$$C_T = 2 + 0.49 + 274.15 + 1200 \text{ nS}$$

Thus  $(C_{\mu 2} + C_L) R_{\mu 2}$  is the dominating term. The second most significant term is  $C_T R_T$ .

So  $(C_{\mu 2} + C_L) R_{\mu 2}$  dominates and then  $C_T$  or equivalently  $C_{\mu 2}$ .

$$f_H = \frac{1}{2\pi C_T} = \frac{1}{2\pi \times 1476.6} = 107.8 \text{ MHz}$$

c) Increasing the bias currents by a factor of 10:

$$g_m = 40mA/V \quad \Rightarrow r_{\pi} = 2.5k\Omega$$

$$r_e \approx 25\Omega \quad \Rightarrow r_o = 100k\Omega$$

$$C_{\pi} = C_{je} + C_{de} \times 10 = 0.8 + 0.59 \times 10 = 6.7pF$$

$$C_{\mu} = 0.2pF$$

$$R_{in} = 101 [0.025 + (2.5 || 100)] = 249k\Omega$$

$R_{in}$  is almost decreased by a factor of 10.

$$A_M = - \frac{249}{249 + 10} \times \frac{2.5 || 100}{0.025 + (2.5 || 100)} \times 4000$$

$$A_M = -3807 V/V$$

$A_M$  remains almost constant.

$$C_T = 6.7 + 0.2(1 + 40 \times 100) = 806.9 \text{ (almost constant)}$$

$$R_{H1} = R_{sig} || R_{in} = 10^k || 249k = 9.61k\Omega$$

$R_{H1}$  stays almost the same.

$$R_T = 2.5k || 10^k || \frac{2.5 + 10}{101} = 117.8\Omega$$

$R_T$  is almost reduced by a factor of 3.

$$R_{in2} = r_{\pi 2} || r_o = 2.44k\Omega$$

$$R_{pi1} = \frac{10k + 2.44}{1 + \frac{10}{2.5} + \frac{2.44}{0.025}} = 120\Omega$$

$R_{pi1}$  is almost decreased by a factor of 3.

$$R_{\mu 2} = r_o = 100k\Omega \quad (\text{decreased by a factor of 10})$$

$$C_T = 0.2 \times 9.61 + 6.7 \times 0.120 + 806.9 \times 0.118 + 1.2 \times 100$$

$$C_T = 1.92 + 0.8 + 95.2 + 120 = 217.92 \text{ nS}$$

Thus the dominant effect, that of the output pole, is reduced by a factor of 10.

This occurs because  $(C_{\mu 2} + C_L)$  remains constant while  $r_o$  decreases by a factor of 10. The second most significant factor (that due to  $C_T$  or  $C_{\mu 2}$  with Miller effect) also decreases, but only by a factor of 3. The overall result is an increase in  $f_H$ .

Cont.



	0.5 μm		0.25 μm		0.18 μm		0.13 μm	
	NMOS	PMOS	NMOS	PMOS	NMOS	PMOS	NMOS	PMOS
$V_{ov}$ (V)	0.32	-0.54	0.27	-0.46	0.23	-0.48	0.2	-0.42
$V_{os}$ (V)	1.02	-1.34	0.7	-1.08	0.71	-0.93	0.6	-0.82

	0.5 μm		0.25 μm		0.18 μm		0.13 μm	
	NMOS	PMOS	NMOS	PMOS	NMOS	PMOS	NMOS	PMOS
$g_m$ (mA / V)	0.62	0.37	0.73	0.43	0.88	0.41	1.02	0.48

6.69 If the area of the emitter-base junction is changed by a factor of 10, then  $I_s$  is changed by the same factor. If  $V_{BE}$  is kept constant, then  $I_C$  is also changed by the same factor:

$$I_C = I_s e^{\frac{V_{BE}}{V_T}}$$

$$I_s \propto A, I_C \propto I_s \Rightarrow I_C \propto A$$

$$A_2 = 10 A_1 \Rightarrow I_{C2} = 10 I_{C1}$$

If  $I_C$  is kept constant, then  $V_{BE}$  changes:

$$I_{S2} = 10 I_{S1} \Rightarrow I_s e^{\frac{V_{BE2}}{V_T}}$$

$$e^{\frac{V_{BE1} - V_{BE2}}{V_T}} = 10 \Rightarrow V_{BE1} - V_{BE2}$$

$$= V_T \ln 10 = 0.058 \text{ V or } 58 \text{ mV}$$

$$= \frac{2 \times 100}{267 \times 0.25^2} = 11.98 \approx 12$$

For PMOS:

$$k' = 93 \frac{\mu\text{A}}{\text{V}^2} \Rightarrow \left(\frac{W}{L}\right)_p$$

$$= \frac{2 \times 100}{93 \times 0.25^2} = 34.4 \approx 34$$

6.72

$$i_{Dn} = i_{Dp} \Rightarrow \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n V_{ovn}^2$$

$$= \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p V_{ovp}^2 \quad (1)$$

we also have  $g_{mn} = g_{mp}$

$$g_m = \frac{2I_D}{V_{ov}} \Rightarrow V_{ovn} = V_{ovp} \quad (2)$$

$$\textcircled{1}, \textcircled{2} \Rightarrow \frac{\left(\frac{W}{L}\right)_p}{\left(\frac{W}{L}\right)_n} = \frac{\mu_n}{\mu_p} = \frac{460}{160} = 2.88$$

6.70  $\frac{W}{L} = 10, I_D = 100 \mu\text{A}$ ,

$$I_D = \frac{1}{2} k' \frac{W}{L} V_{ov}^2$$

$$V_{ov} = \sqrt{\frac{2I_D}{k' \frac{W}{L}}} = \sqrt{\frac{2 \times 100}{k' \frac{10}{1}}} = \sqrt{\frac{20}{k'}}$$

$$V_{GS} = V_i + V_{ov}$$

6.71

$$|V_{ov}| = 0.25 \text{ V}, I_D = 100 \mu\text{A}$$

$$I_D = \frac{1}{2} k' \frac{W}{L} V_{ov}^2 \Rightarrow \frac{W}{L} = \frac{2I_D}{k' V_{ov}^2}$$

For NMOS:

$$k' = 267 \frac{\mu\text{A}}{\text{V}^2} \Rightarrow \left(\frac{W}{L}\right)_n$$

### 6.73

$$V_{ov} = 0.25 \text{ V}$$

for an npn transistor:

$$g_m = \frac{I_C}{V_T} = \frac{0.1}{0.025} = 4 \text{ mA/V}$$

For an NMOS with the same  $g_m$ , i.e.

$$g_m = 4 \text{ mA/V}$$

we will have :

$$g_m = \frac{2I_D}{V_{ov}} \Rightarrow I_D = g_m \times \frac{V_{ov}}{2} = 0.5 \text{ mA}$$

$$I_D = 0.5 \text{ mA}$$

### 6.74

Assuming large  $r_o$  For both transistors, for

$$\text{case (a) we have } r = \frac{1}{g_m} = \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}}$$

$$r = \frac{10^3}{\sqrt{2 \times 200 \times 10 \times 0.1 \times 10^3}} = 1.58 \text{ k}\Omega$$

For case (b) we have

$$r = r_\pi \parallel \frac{1}{g_m} = \frac{\beta}{(\beta + 1)g_m}$$

$$r = \frac{\beta V_T}{(\beta + 1)I_C} \approx \frac{V_T}{I_c} = \frac{0.025}{0.1} = 0.25 \text{ k}\Omega$$

$$r = 250 \text{ }\Omega$$

### 6.75

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 100 \times 10^{-3}}{0.5} = 0.4 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{V_A}{I_c} = \frac{25 \times 1}{0.1} = 250 \text{ k}\Omega$$

$$A_\phi = g_m r_o = 0.4 \times 250 = 100 \text{ V/V}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{ov} \Rightarrow$$

$$W = \frac{g_m \times L}{\mu_n C_{ox} V_{ov}} = \frac{0.4 \times 1}{127 \times 10^{-3} \times 0.5}$$

$$W = 6.3 \text{ }\mu\text{m}$$

### 6.76

$$L = 0.3 \text{ }\mu\text{m}, I_D = 100 \text{ }\mu\text{A},$$

$$V_{ov} = 0.2 \text{ V}$$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 100 \times 10^{-3}}{0.2} = 1 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{V_A \times L}{I_D} = \frac{5 \times 0.3}{0.1} = 15 \text{ k}\Omega$$

$$A_\phi = g_m r_o = 1 \times 15 = 15 \text{ V/V}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{ov} \Rightarrow$$

$$W = \frac{g_m \times L}{\mu_n C_{ox} V_{ov}} = \frac{1 \times 0.3}{387 \times 10^{-3} \times 0.2}$$

$$W = 3.88 \text{ }\mu\text{m}$$

### 6.77

$$L = 0.3 \text{ }\mu\text{m}, W = 6 \text{ }\mu\text{m}$$

$$V_{ov} = 0.2 \text{ V}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2$$

$$= \frac{1}{2} \times 387 \times \frac{6}{0.3} \times 0.2^2 = 155 \text{ }\mu\text{A}$$

$$I_D = 0.155 \text{ mA}$$

$$g_m = \frac{2I_D}{V_{ov}} = 1.55 \text{ mA/V}$$

$$C_{gs} = \frac{2}{3} \frac{W}{L} C_{ox} + C_{ov} = \frac{2}{3} WLC_{ox}$$

$$+ WL_{ov} C_{ox}$$

$$C_{gs} = \frac{2}{3} \times 6 \times 0.3 \times 8.6 + 6 \times 0.37 \\ = 12.54 \text{ fF}$$

$$C_{gd} = C_{ov} W = 0.37 \times 6 = 2.22 \text{ fF}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} \\ = \frac{1.55 \times 10^{-3}}{2\pi(12.54 + 2.22) \times 10^{-15}} = 16.7 \text{ GHz}$$

If we use the approximation formula:

$$f_T \approx \frac{1.5 \mu_n V_{ov}}{2\pi L^2} \text{ when}$$

$$C_{gs} \gg C_{gd}, C_{gs} \approx \frac{2}{3} \frac{W}{L} C_{ox}$$

$$f_T \approx \frac{1.5 \times 450 \times 10^{-4} \times 0.2}{2 \times \pi \times 0.3^2 \times 10^{-12}} = 23.9 \text{ GHz}$$

The approximation formula over estimates  $f_T$  because it ignores  $WL_{ov} C_{ox}$  or  $C_{ov}$  in  $C_{gs}$  and  $C_{gd}$  calculation.

### 6.78

$I_C = 10 \mu\text{A}$ , High-voltage process:

$$g_m = \frac{I_C}{V_T} = \frac{10 \times 10^{-3}}{0.025} = 0.4 \text{ mA/V}$$

$$C_{de} = \tau_F g_m = 0.35 \times 10^{-9} \times 0.4 \times 10^{-3}$$

$$= 140 \times 10^{-15} \text{ F} = 140 \text{ fF}$$

$$C_{je} = 2C_{j_{eo}} = 2 \times 1 = 2 \text{ pF} = 2000 \text{ fF}$$

$$C_\pi = C_{de} + C_{je} = 2140 \text{ fF}$$

$$C_\mu = C_{\mu_o} = 0.3 \text{ pF} = 300 \text{ fF}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$= \frac{0.4 \times 10^{-3}}{2\pi(2140 + 300 \times 10^{-15})} = 26.1 \text{ MHz}$$

$I_C = 100 \mu\text{A}$ , High-voltage process:

$$g_m = 10 \times 0.4 = 4 \text{ mA/V},$$

$$C_{de} = 10 \times 140 = 1400 \text{ fF}$$

$$C_\pi = 3400 \text{ fF} \Rightarrow$$

$$f_T = \frac{4 \times 10^{-3}}{2\pi(3400 + 300) \times 10^{-15}} = 172.1 \text{ MHz}$$

$I_C = 10 \mu\text{A}$ , Low-voltage process

$$g_m = \frac{10 \times 10^{-3}}{0.025} = 0.4 \text{ mA/V}$$

$$C_{de} = 10 \times 10^{-12} \times 0.4 \times 10^{-3} = 4 \text{ fF}$$

$$C_{je} = 2 \times 5 \text{ fF} = 10 \text{ fF}$$

$$C_\pi = C_{de} + C_{je} = 14 \text{ fF}$$

$$C_\mu \approx C_{\mu_o} = 5 \text{ fF}$$

$$f_T = \frac{g_m}{2\pi(C_\mu + C_\pi)} = \frac{0.4 \times 10^{-3}}{2\pi(5 + 14) \times 10^{-15}} = 3.35 \text{ GHz}$$

$I_C = 100 \mu\text{A}$ , Low-voltage process

$$g_m = \frac{100 \times 10^{-3}}{0.025} = 4 \text{ mA/V}$$

$$C_{de} = 10 \times 4 = 40 \text{ fF}$$

$$C_\pi = 40 + 10 = 50 \text{ fF}, C_\mu = 5 \text{ fF}$$

$$f_T = \frac{4 \times 10^{-3}}{2\pi(50 + 5) \times 10^{-15}} = 11.6 \text{ GHz}$$

In Summary:

	Standard High-Voltage npn		Standard low-Voltage npn	
$I_C =$	$I_C =$		$I_C =$	$I_C =$
$10 \mu\text{A}$	$100 \mu\text{A}$		$10 \mu\text{A}$	$100 \mu\text{A}$

$f_T$	26.1 MHz	172.1 MHz	3.35 GHz	11.6 MHz
-------	----------	-----------	----------	----------

### 6.79

$$I_C = 1 \text{ mA} \Rightarrow g_m = \frac{I_C}{V_T} = 40 \text{ mA/V}$$

For pnp:

$$C_{de} = \tau_F g_m = 30 \times 10^{-9} \times 40 \text{ mA/V} = 1200 \text{ pF}$$

$$C_{je} = 2C_{j_{eo}} = 2 \times 0.3 = 0.6 \text{ pF}$$

$$C_\pi = 1200.6 \text{ pF}$$

$$C_\mu \approx 1 \text{ pF}$$

$$\Rightarrow f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} = \frac{40 \text{ mA/V}}{2\pi(1200.6 + 1) \text{ pF}}$$

$$f_T = 5.3 \text{ MHz}$$

For npn:

$$C_{de} = \tau_F g_m = 0.35 \text{ ns} \times 40 \text{ mA/V} = 14 \text{ pF}$$

$$C_{je} = 2 \times 1 = 2 \text{ pF}$$

$$C_\mu \approx 0.3 \text{ pF}$$

$$C_\pi = 14 + 2 = 16 \text{ pF}$$

$$\Rightarrow f_T = \frac{40 \text{ mA/V}}{2\pi(16 + 0.3) \text{ pF}} = 391 \text{ MHz}$$

### 6.80

$$A_O = g_m r_O = \frac{2I_D}{V_{OV}} \times \frac{V_A}{I_D} = \frac{2V_A}{V_{OV}} = \frac{2V_A L}{V_{OV}}$$

Therefore  $A_O$  is only determined by setting values for  $L$  and  $V_{OV}$ .

$$f_T = \frac{g_m}{2\pi(C_{rs} + C_{rd})}$$

$$= \frac{2I_D/V_{OV}}{2\pi\left(\frac{2}{3}WLC_{ox} + C_{ov} + C_{ov}\right)}$$

If we assume that  $C_{ov}$  is very small or equivalently  $C_{rs} \gg C_{rd}$  and  $C_{rs} = \frac{2}{3}WLC_{ox}$ :

(replace  $I_D$  with  $\frac{1}{2}k_n \frac{W}{L} V_{OV}^2$ )

$$f_T \approx \frac{k_n W/L V_{OV}}{2\pi \times \frac{2}{3}WLC_{ox}} = \frac{3\mu_n}{4\pi} V_{OV} / L^2$$

$$= \frac{3}{4\pi} \mu_n \frac{V_{OV}}{L^2}$$

As we can see  $f_T$  can be determined after knowing  $V_{OV}$  and  $L$ , it is not dependent on either  $I_D$  or  $W$ .

### 6.81

$V_{OV} = 0.2 \text{ V}$ ,  $L = 0.2 \mu\text{m}$ ,  $0.3 \mu\text{m}$ ,  $0.4 \mu\text{m}$

$$A_o = g_m r_o = \frac{2V_A L}{V_{OV}} = \frac{2 \times 5 \times L}{0.2} = 50 \text{ LV/V}$$

$$f_T \approx \frac{1.5 \mu_n V_{OV}}{2\pi L^2} = \frac{1.5 \times 450 \times 10^{-4} \times 0.2}{2 \times 3.14 \times L^2 \times 10^{-2}} = \frac{2.15}{L^2} \text{ GHz}$$

$L(\mu\text{m})$	0.2	0.3	0.4
$A_o (\text{V/V})$	10	15	20
$f_T (\text{GHz})$	53.75	23.9	13.4

### 6.82

$L = 0.5 \mu\text{m}$ ,  $V_{OV} = 0.3 \text{ V}$ ,  $C_L = 1 \text{ pF}$ ,  
 $f_T = 100 \text{ MHz}$

$$f_T = \frac{g_m}{2\pi C_L} \Rightarrow g_m = 2\pi C_L f_T = 2\pi \times 1 \text{ pF} \times 100 \text{ MHz} = 628 \text{ } \mu\text{A/V}$$

$$g_m = \frac{2I_D}{V_{OV}} \Rightarrow I_D = g_m \times V_{OV}/2 = 6.28 \times \frac{0.3}{2} = 94.2 \text{ } \mu\text{A}$$

$$I_D = \frac{1}{2} k_n \frac{W}{L} V_{OV}^2 \Rightarrow W = \frac{2LI_D}{k_n V_{OV}^2} = \frac{2 \times 0.5 \times 94.2}{190 \times 0.3^2} = 5.51 \text{ } \mu\text{m}$$

$$W = 5.51 \text{ } \mu\text{m}$$

$$r_o = \frac{V_A}{I_D} = \frac{V_A L}{I_D} = \frac{20 \times 0.5}{94.2 \times 10^{-3}} = 106.2 \text{ k}\Omega$$

$$A_o = g_m r_o = \frac{628}{1000} \times 106.2 = 66.7 \text{ V/V}$$

$$f_{1db} = \frac{1}{2\pi C_L r_o} = \frac{1}{2\pi \times 1 \text{ pF} \times 106.2 \text{ k}\Omega} = 1.5 \text{ MHz}$$

$$(e) V_{CMX} = V_t + V_{DD} - \frac{I}{2} R_D \\ = 0.7 + 2.5 - 0.1 \times 2.5 = + \underline{\underline{2.95V}}$$

7.1


$$V_{DD} = V_{SS} = 2.5V$$

$$K_n' \frac{W}{L} = 3 \frac{mA}{V^2}; V_{tN} = 0.7V$$

$$I = 0.2mA; R_D = 5k\Omega$$

$$(a) V_{ov} = \sqrt{I / K_n' W/L} \\ = \sqrt{0.2 / 3} = \underline{\underline{0.26V}}$$
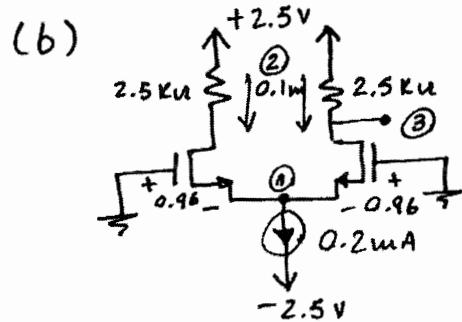
$$V_{GS} = V_{ov} + V_t = 0.26 + 0.7 \\ = \underline{\underline{0.96V}}$$



$$\textcircled{1} \quad V_{S1} = V_{S2} = V_{CM} - V_{GS} \\ = 0 - 0.96 = - \underline{\underline{0.96V}}$$

$$\textcircled{2} \quad I_{D1} = I_{D2} = \frac{I}{2} = 0.1mA$$

$$\textcircled{3} \quad V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} \times R_D \\ = +2.5 - 0.1 \times 2.5 = \underline{\underline{2.25V}}$$

$$(c) \text{ If } V_{CM} = +1V$$

$$V_{S1} = V_{S2} = +1 - 0.96 = \underline{\underline{0.04V}}$$

$$I_{D1} = I_{D2} = \underline{\underline{0.1mA}}$$

$$V_{D1} = V_{D2} = \underline{\underline{2.25V}}$$

$$(d) \text{ If } V_{CM} = -1V$$

$$V_{S1} = V_{S2} = -1 - 0.96 = - \underline{\underline{1.96V}}$$

$$I_{D1} = I_{D2} = \underline{\underline{0.1mA}}$$

$$V_{D1} = V_{D2} = \underline{\underline{2.25V}}$$

$$(f) V_{CMIN} = -V_{SS} + V_{GS} + V_t + V_{ov} \\ = -2.5 + 0.3 + 0.7 + 0.26 \\ = - \underline{\underline{1.24V}}$$

$$V_{Smin} = V_{CMIN} - V_{GS} \\ = -1.24 - 0.96 = - \underline{\underline{2.2V}}$$

7.2

$$(a) V_{ov} = - \sqrt{I / K_p' (W/L)} \\ = - \sqrt{0.7 / 3.5} = - \underline{\underline{0.45V}} \\ V_{GS} = V_{ov} + V_t = -0.45 - 0.8 \\ = - \underline{\underline{1.25V}} \\ U_{S1} = U_{S2} = U_G - V_{GS} \\ = 0 + 1.25 = + \underline{\underline{1.25V}} \\ V_{D1} = V_{D2} = \frac{I}{2} \times R_D - V_{DD} \\ = \frac{0.7}{2} \times 2 - 2.5 = - \underline{\underline{1.8V}}$$

(b) For Q<sub>1</sub> and Q<sub>2</sub> to remain in saturation:


$$V_{DS} \leq V_{GS} - V_t \\ \rightarrow V_{CM} \geq \left( \frac{I}{2} R_D - V_{DD} \right) + V_t$$

$$V_{CMmin} = \frac{0.7}{2} \times 2 - 2.5 - 0.8 \\ = - \underline{\underline{2.6V}}$$

To allow sufficient voltage for the current source to operate properly:

$$V_{CM} \leq V_{SS} - V_{GS} + (V_{tN} + V_{ov}) \\ \rightarrow V_{CMmax} = 2.5 - 0.5 - 1.25 \\ = 0.75V //$$

7.3

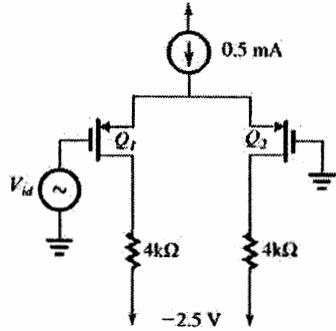

$$V_{G2} = 0$$

$$V_{GE} = v_{id}$$

When all the current is on  $Q_1$ :

$$I = \frac{1}{2} \left( k_p \frac{w}{L} \right) (V_{GS1} - V_t)^2$$

$$\Rightarrow V_{GS1} = V_t + \sqrt{\frac{2I}{k_p w / L}}$$

$$= V_t + \sqrt{2} V_{ov}$$

and  $V_{GS}$  is reduced to  $V_t$ , thus  $V_s = -V_t$ .

$$\text{Then } v_{id} = v_{GS1} + v_s$$

$$= V_t + \sqrt{2} V_{ov} - V_t = \sqrt{2} V_{ov}$$

In a similar manner as for the NMOS Differential Amplifier, as  $v_i$  reaches  $-\sqrt{2} V_{ov}$ ,  $Q_1$  turns off and  $Q_2$  on. Thus the steering range is

$$\sqrt{2} V_{ov} \leq V_t \leq -\sqrt{2} V_{ov}$$

For this particular case

$$V_{ov} = \sqrt{\frac{0.25 \text{ mA}}{4 \text{ mA/V}^2}} = 0.25 \text{ V}$$

$$\sqrt{2} \times -0.25 \leq v_{id} \leq \sqrt{2} \times 0.25$$

$$-0.35 \leq v_{id} \leq 0.35$$

when  $V_{id} = -0.35 \text{ V}$ ,

$$i_{D1} = 0.5 \text{ mA}, i_{D2} = 0$$

$$V_s = -V_{D2} = +0.8 \text{ V}$$

$$V_{D1} = 4 \text{ k}\Omega \times 0.5 \text{ mA} - 2.5 = -0.5 \text{ V}$$

$$V_{D2} = 0 - 2.5 \text{ V} = -2.5 \text{ V}$$

when  $v_{id} = +0.35 \text{ V}$ ,

$$i_{D1} = 0 : i_{D2} = 0.5 \text{ mA}$$

$$V_s = v_{id} - v_{GS1} = v_{id} - V_t$$

$$= 0.35 \text{ V} + 0.8 \text{ V} = 1.15 \text{ V}$$

$$V_{D1} = -2.5 \text{ V}$$

$$V_{D2} = -0.5 \text{ V}$$

7.4

$$V_{G1} = v_{id} i_{D1} = 0.11 \text{ mA}$$

$$V_{G2} = 0 : i_{D2} = 0.09 \text{ mA}$$

$$I_D = \frac{1}{2} k' \frac{W}{n} (V_{GS} - V_t)^2$$

For  $Q_1$ :

$$0.11 \text{ mA} = \frac{1}{2} 5 \text{ m} (V_{GS1} - 0.5)^2$$

$$\rightarrow V_{GS1} = 0.71 \text{ V}$$

For  $Q_2$ :

$$0.09 \text{ mA} = \frac{1}{2} 5 \text{ m} (V_{GS2} - 0.5)^2$$

$$\rightarrow V_{GS2} = 0.69 \text{ V}$$

$$V_s = -V_{GS2} = -0.69 \text{ V}$$

$$v_{id} = V_s + V_{GS1} = -0.69 + 0.71 \\ = 0.02 \text{ V}$$

$$V_{D2} - V_{D1} = 10 \text{ k}\Omega (i_{D1} - i_{D2})$$

$$= 10 \text{ kV} (0.11 - 0.09) \text{ mA}$$

$$= 0.2 \text{ V}$$

thus

$$\frac{V_{D2} - V_{D1}}{v_{id}} = \frac{0.2}{0.02} = 10$$

when  $i_{D1} = 0.09 \text{ mA}$  and

$$i_{D2} = 0.11 \text{ mA}$$

is the reverse condition from the case we just studied, thus  $v_{id} = -0.02 \text{ V}$

7.5

$$V_{GS} = V_m + V_{ov} = 0.5 \text{ V} + 0.2 \text{ V} = 0.7 \text{ V}$$

$$V_{D4} = V_{G4} = -V_{SS} + V_{GS} = -1.2 \text{ V} + 0.7 \text{ V} \\ = -0.5 \text{ V}$$

$$R = \frac{V_{DD} - V_{D4}}{0.1 \text{ mA}} = \frac{1.2 \text{ V} - (-0.5 \text{ V})}{0.1 \text{ mA}} = 17 \text{ k}\Omega$$

$$R_D = \frac{V_{DD} - V_{D1}}{0.4 \text{ mA}/2} = \frac{1.2 \text{ V} - 0.2 \text{ V}}{0.2 \text{ mA}} = 5 \text{ k}\Omega$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \frac{0.4 \text{ mA}}{2} \left[ k' \frac{V}{n} \right]^2$$

$$= 0.2 \text{ mA} [(0.25 \text{ mA/V}^2)(0.2 \text{ V})]^2 = 20$$

$$\left(\frac{W}{L}\right)_3 = 0.4 \text{ mA} [0.01 \text{ mA}]^{-1} = 40$$

$$\left(\frac{W}{L}\right)_4 = 0.1 \text{ mA} [0.01 \text{ mA}]^{-1} = 10$$

$$V_{cm(max)} = V_m + V_{DD} - (I/2)R_D$$

$$= 0.5 \text{ V} + 1.2 \text{ V} - (0.2 \text{ mA})(5 \text{ k}\Omega) = 0.7 \text{ V}$$

$$V_{cm(min)} = -V_{SS} + V_{ov3} + V_m + V_{ov1}$$

$$= -1.2 \text{ V} + 0.2 \text{ V} + 0.5 \text{ V} + 0.2 \text{ V} = -0.3 \text{ V}$$

7.6

We Know that there is a linear relationship between  $V_{ov}$  &  $V_{id}$  since:

$$V_{ov} = V_{id}/2$$

$$\sqrt{0.1}$$

Then from the data in table 7.3 we can tell that for  $V_{imax} = 150\text{mV}$

$$V_{ov} = 0.2 \times \frac{150}{126} = 0.238\text{V}$$

$$\text{For } w/L: \frac{w}{L} = \frac{1}{(V_{ov})^2} \cdot \frac{I}{K}$$

where I and K are constant  
thus, for  $w/L$ :

$$\left(\frac{W}{L}\right)_2 = \frac{50}{\left(\frac{150}{126}\right)^2} = 35.3$$

For  $g_m$ :  $g_m = \frac{I}{V_{ov}}$  where I is constant

$$\rightarrow g_{m2} = \frac{g_{m1}}{\left(\frac{150}{126}\right)} = \frac{2}{\frac{150}{126}} = \frac{1.68}{\frac{m}{V}}$$

7.7

$$\left(\frac{v_{idmax}/2}{V_{ov}}\right)^2 = K$$

$$\Rightarrow 2V_{ov}\sqrt{K} = v_{idmax}$$

Q.E.D.

$$i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{ov}}\right) \frac{v_{id}}{2} \sqrt{1 - K}$$

$$i_{D1} = \frac{I}{2} \pm \frac{I}{V_{ov}} \cdot \frac{2}{2} V_{ov}\sqrt{K} \cdot \sqrt{1 - K}$$

$$\rightarrow i_{D1} = \frac{I}{2} \pm I\sqrt{K(1 - K)}$$

$$\text{thus } \Delta I = 2I\sqrt{K(1 - K)}$$

Q.E.D.

$$\text{For } K = 0.01$$

$$\Delta I = 2I\sqrt{0.01(1 - 0.01)} \\ = 0.198 \times I$$

$$V_{idmax} = 2V_{ov}\sqrt{0.01} = 0.2V_{ov}$$

$$\text{For } K = 0.1$$

$$\Delta I = 2I\sqrt{0.1(1 - 0.1)} = 0.8I$$

$$V_{idmax} = 2V_{ov}\sqrt{0.1} \\ = 0.894 \cdot V_{ov}$$

7.8

$$I_D = \frac{1}{2} \mu_C \alpha \times \frac{W}{L} (V_{GS} - V_T)^2$$

$$\frac{200}{2} = \frac{1}{2} \times 90 \times \frac{100}{1.6} (V_{GS} - 0.8)^2 \\ \Rightarrow V_{GS} = \underline{1.19V}$$

$$g_m = \frac{2I_D}{V_{GS} - V_T} = \frac{2 \times 100}{(1.19 - 1)} = \underline{1.06 \frac{mA}{V}}$$

$$V_{id} \Big|_{\substack{\text{full current} \\ \text{switching}}} = \sqrt{2} (V_{GS} - V_T) \\ = \underline{0.27V}$$

To double this value,  $V_{GS} - V_T$  must be doubled which means that  $I_D$  should be quadrupled. i.e. I changed to:

$$\underline{800mA}$$

7.9

$$g_m = \frac{2I_0}{V_{ov}} \rightarrow 1m = \frac{I}{0.2}$$

$$\rightarrow I = 0.2mA$$

$$I_0 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2$$

$$100 = \frac{1}{2} \times 90 \times \frac{W}{L} \times (0.2)^2$$

$$\Rightarrow \frac{W}{L} = 55.6$$

7.10

$$i_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$50 = \frac{1}{2} \times 400 (V_{GS} - 1)^2$$

$$\Rightarrow V_{GS} = 1.5 V$$

For  $V_{G1} = V_{G2} = 0$ ,  $v_s = -1.5 V$

For  $V_{G1} = V_{G2} = 2 V$ ,  $v_s = +0.5 V$

The drain currents are equal in both cases.

For  $V_{G2} = 0$ :

To reduce  $i_{D2}$  by 10%:

$$i_{D2} = 0.9 \times 50 = 45 \mu A$$

$$i_{D1} = 55 \mu A$$

$$v_{GS2} = \sqrt{\frac{2i_{D2}}{400}} + 1 = 1.47 V$$

$$v_{GS1} = \sqrt{\frac{2 \times 55}{400}} + 1 = 1.52 V$$

$$\text{Thus, } V_{G1} = v_{GS1} - v_{GS2} = 0.05 V$$

To increase  $i_{D2}$  by 10%

$$i_{D2} = 55 \mu A$$

$$i_{D1} = 45 \mu A$$

$$v_{GS2} = 1.52 V$$

$$v_{GS1} = 1.47 V$$

$$\Rightarrow V_{G1} = -0.05 V$$

$i_{D2}/i_{D1}$	$i_{D2}$ ( $\mu A$ )	$i_{D1}$ ( $\mu A$ )	$V_{GS2}$ (V)	$V_{GS1}$ (V)	$V_G - V_{G1}$ (V)
1	50	50	1.5	1.5	0
0.5	33.3	66.7	1.408	1.577	-0.17
0.8	47.4	52.6	1.487	1.513	-0.026
0.99	47.75	50.25	1.4886	1.5012	-0.013

For  $i_{D1}/i_{D2} = 20 \Rightarrow i_{D2} = 4.76 \mu A$

$$i_{D1} = 95.24 \mu A$$

$$V_{GS2} = 1.154 V, V_{GS1} = 1.690$$

$$\text{Thus } V_{G1} - V_{G2} = 0.536 V$$

7.11

$$(a) V_{od} = V_{D2} - V_{D1} = (V_{DD} - i_{D2}R_D) - (V_{DD} - i_{D1}R_D) = (i_{D1} - i_{D2})R_D$$

$$V_{od} = \left[ \left( \frac{I}{V_{ov}} \right) \left( \frac{V_{id}}{2} \right) \sqrt{1 - \left( \frac{V_{id}/2}{V_{ov}} \right)^2} + \left( \frac{I}{V_{ov}} \right) \left( \frac{V_{id}}{2} \right) \sqrt{1 - \left( \frac{V_{id}/2}{V_{ov}} \right)^2} \right] R_D$$

$$= IR_D \frac{V_{id}}{V_{ov}} \sqrt{1 - \left( \frac{V_{id}/2}{V_{ov}} \right)^2}$$

(b) see plot

slope of linear portion

$$= \frac{d}{dV_{id}} \left( \frac{IR_D}{V_{ov}} \cdot V_{id} \right) = IR_D / V_{ov}$$

(c) see plot

when the bias current is doubled,  $V_{ov}$  so

$$V_{od}/V_{id} = \frac{2IR_D}{\sqrt{2} V_{ov}} \sqrt{1 - \left( \frac{V_{id}/2}{\sqrt{2} V_{ov}} \right)^2}$$

increases by a factor of  $\sqrt{2}$  the slope of the linear part has increased by a factor of  $\sqrt{2}$

(d) see plot

If W/L is doubled,  $V_{ov}$  reduces by a factor at  $\sqrt{2}$

$$\text{so } V_{od}/V_{id} = \frac{2IR_D}{\sqrt{2} V_{ov}} \sqrt{1 - \left( \frac{V_{id}/\sqrt{2}}{V_{ov}} \right)^2}$$

The slope of the linear part has increased by factor of  $\sqrt{2}$  compared to (b)

7.12

$$V_{ov} = \sqrt{\frac{I}{K_n' w}} = \sqrt{\frac{0.5}{L}} = \underline{0.2V}$$

$$g_m = \frac{I}{V_{ov}} = \frac{0.5 \text{ mA}}{0.2V} = \underline{2.5 \text{ mA/V}}$$

$$f_0 = \frac{V_A}{I_D} = \frac{10}{(0.5 \text{ mA}/2)} = \underline{40 \text{ KHz}}$$

$$\begin{aligned} A_d &= g_m \times (R_D \parallel f_0) \\ &= 2.5 \frac{\text{mA}}{V} (4 \text{ KHz} \parallel 40 \text{ KHz}) \\ &= \underline{9.09 \text{ V/V}} \end{aligned}$$

7.13

$$\left( \frac{V_{id}/2}{V_{ov}} \right)^2 = 0.1 \rightarrow \left( \frac{0.2/2}{V_{ov}} \right)^2 = 0.1$$

$$\rightarrow V_{ov} = \sqrt{0.1} = \underline{0.316V}$$

$$\begin{aligned} g_m &= \frac{I}{V_{ov}} \rightarrow 3 \frac{\text{mA}}{V} = \frac{I}{0.316} \\ \rightarrow I &= \underline{0.95 \text{ mA}} \end{aligned}$$

$$\begin{aligned} \text{also: } V_{ov} &= \sqrt{\frac{I}{K_n' w/L}} \\ \Rightarrow (0.316)^2 &= \frac{0.95 \text{ mA}}{0.1 \text{ mA} \times \left(\frac{w}{L}\right)} \\ \rightarrow \frac{w}{L} &= \underline{95} \end{aligned}$$

If  $R_D = 5 \text{ K}\Omega \Rightarrow$

$$A_d = g_m R_D = 3 \frac{\text{mA}}{V} \times 5 \text{ K}\Omega = \underline{15 \text{ V/V}}$$

$$\begin{aligned} \text{if } V_{id} = 0.2 \Rightarrow Nod &= V_{id} \times A_d \\ &= 0.2 \times 15 = \underline{3V} \end{aligned}$$

7.14

$$(a) g_m = \frac{A_d}{R_D} = \frac{20}{47 \text{ k}\Omega} = 0.426 \text{ mA/V}$$

$$(b) I = g_m V_{ov} = (0.426 \text{ mA/V})(0.2V) = 85 \mu\text{A}$$

$$(c) V_{RD} = \frac{I}{2} R_D = (85 \mu\text{A}/2)(47 \text{ k}\Omega) = 2 \text{ V}$$

$$(d) V_{id(MAX)} = V_{CM} + 10 \text{ mV} = 0.51 \text{ V}$$

$$\begin{aligned} V_{DD} &\geq V_{id(MAX)} - V_i + I_D R_D \\ &= 0.51 \text{ V} - V_i + (85 \mu\text{A}/2)(47 \text{ k}\Omega) \\ &= 2.51 \text{ V} - V_i \end{aligned}$$

7.15

For a CS amplifier  $A_r = -g_m R_D$


For a differential amplifier  $A_d = g_m R_D$  with  $I = 2I_D$

So the differential pair requires twice the bias current as the CS amplifier.

The power dissipation at the diff amp is also twice as high.

7.16

HALF-CIRCUIT

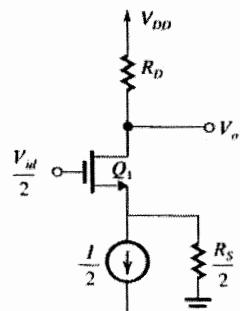

small-signal analysis

$$V_{gs} = \frac{V_{id}}{2} - g_m V_{gs} \frac{R_s}{2}$$

$$V_{gs} = \frac{V_{id}/2}{1 + g_m \frac{R_s}{2}}$$

$$V_{o1} = -g_m V_{gs} R_D = -g_m \left[ \frac{V_{id}/2}{1 + g_m R_s/2} \right] R_D$$

$$A_d = \frac{V_{od}}{V_{id}} = \frac{g_m R_D}{1 + g_m R_s / 2}$$

when  $R_s = 0$   $A_d = g_m R_D$  (agrees with Eqn. 8.35)

when  $R_s = \frac{2}{g_m}$  the differential gain is reduced

by half

### 7.17

$$(a) V_{G1} = V_{G2} = OV$$

$V_{S1} = V_{S2}$  assuming matching components

$$\begin{aligned} V_{S1} &= V_{G1} - V_{GS1} = OV - (V_i + V_{ov}) \\ &= -(V_i + V_{ov}) \end{aligned}$$

(b) zero current flows through  $Q_3$

$$\begin{aligned} V_{ov3} &= V_C - V_{S1} - V_i = V_C - (-(V_i + V_{ov})) - V_i \\ &= V_C + V_i \\ &= V_C + V_{ov} \end{aligned}$$

$$(c) V_{G1} = -V_{G2} = V_{id}/2$$

$V_{S1}$  is now more negative than in (a) and  $V_{S2}$  is now less negative than in (a) so there is a voltage across  $Q_3$ . If this voltage is small and if  $V_C$  is such that  $V_{GS3} > V_i$  then  $Q_3$  will operate in triode.

$$r_{DS3} = \left[ k_n \frac{W}{L} V_{ov3} \right]^{-1}$$

$$g_{m1} = g_{m2} = \frac{1/2 k_n \frac{W}{L} V_{ov}^2}{V_{ov}} = 1/2 k_n \frac{W}{L} V_{ov}$$

$$\text{so } r_{DS3} = \left[ g_{m1} \frac{V_{ov3}}{V_{ov}} \right]^{-1} = \frac{V_{ov}}{V_{ov3} g_{m1}}$$

$$(d) r_{DS3} = \frac{V_{ov}}{V_{ov3}} \cdot \frac{1}{g_{m1}}$$

$$(i) R_s = \frac{1}{g_{m1}} \therefore V_{ov3} = V_{ov}$$

From (b)  $V_{ov3} = V_C + V_{ov}$  so  $V_C = 0V$

$$(ii) R_s = \frac{1}{2 g_{m1}} \therefore V_{ov3} = 2 V_{ov}$$

so  $V_C = V_{ov}$

### 7.18

$$(a) V_{G1} = V_{G2} = 0V$$

$$V_{S1} = V_{S2} = -(V_i + V_{ov})$$

Zero current flows through  $Q_3$  and  $Q_4$

$Q_3$  and  $Q_4$  have the same overdrive voltage as  $Q_1$  and  $Q_2$

$$r_{DS3} = r_{DS4} = \left[ k_n \left( \frac{W}{L} \right)_{3,4} V_{ov3,4} \right]^{-1}$$

$$= \left[ k_n \left( \frac{W}{L} \right)_{3,4} V_{ov1,2} \right]^{-1}$$

$$g_{m1,2} = \frac{1}{2} k_n \left( \frac{W}{L} \right)_{1,2} V_{ov1,2}$$

$$V_{ov1,2} = g_{m1,2} \left[ \frac{1}{2} k_n \left( \frac{W}{L} \right)_{1,2} \right]^{-1}$$

$$r_{DS3} = r_{DS4} = r_{DS3,4}$$

$$= \left[ k_n \left( \frac{W}{L} \right)_{3,4} g_{m1,2} \left[ \frac{1}{2} k_n \left( \frac{W}{L} \right)_{1,2} \right]^{-1} \right]^{-1}$$

$$= \left[ 2 g_{m1,2} \left( \frac{W}{L} \right)_{3,4} / \left( \frac{W}{L} \right)_{1,2} \right]^{-1}$$

$$= \frac{\left( \frac{W}{L} \right)_{1,2}}{\left( \frac{W}{L} \right)_{3,4} \cdot 2 \cdot g_{m1,2}}$$

$$R_s = 2 r_{DS3,4} = \frac{\left( \frac{W}{L} \right)_{1,2}}{g_{m1,2} \left( \frac{W}{L} \right)_{3,4}}$$


$$(b) A_d = V_{od} / V_{id} = \frac{g_m R_D}{1 + g_m R_s / 2}$$

(See solution to 8.21)

$$= \frac{g_{m1,2} R_D}{1 + g_{m1,2} \left[ \frac{\left( \frac{W}{L} \right)_{1,2}}{\left( \frac{W}{L} \right)_{3,4} \cdot 2 \cdot g_{m1,2}} \right]}$$

$$= \frac{g_{m1,2} R_D}{1 + \frac{\left( \frac{W}{L} \right)_{1,2}}{2 \left( \frac{W}{L} \right)_{3,4}}}$$

7.19

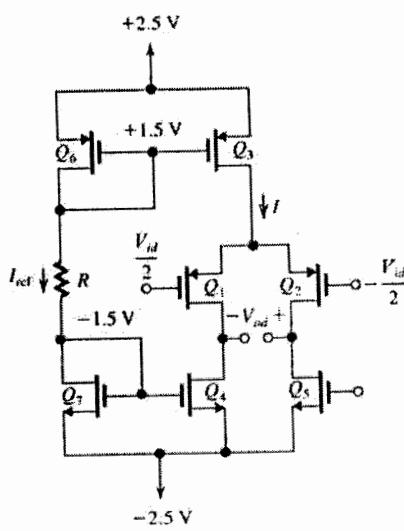

For  $I_{REF} = 100 \mu\text{A}$ ,

$$R = \frac{V_{D6} - V_{D7}}{I_{REF}} = \frac{1.5 - (-1.5)}{0.1 \text{ mA}} = 30 \text{ k}\Omega$$

$$V_{GS1} = V_{GS4} = V_{GS} = -1.5 - (-2.5) = 1 \text{ V}$$

$$V_{OV1} = V_{OV4} = V_{OV} = V_{GS} - V_{th} = 1 - 0.7 = 0.3 \text{ V}$$

$$V_{GS2} = V_{GS3} = 1.5 - 2.5 = -1 \text{ V}$$

$$V_{OV2} = V_{OV3} = V_{GS} - V_{th} = -1 - (-0.7) = -0.3 \text{ V}$$

From section 8.23, we know that

$$A_d = g_m(r_{o1} \parallel r_{o4})$$

Since  $Q_1$  and  $Q_2$  circuits are symmetrical

With  $I = I_{REF} = 100 \mu\text{A}$

$$I_D = \frac{1}{2} = 50 \mu\text{A}$$

$$r_{o1} = r_{o2} = r_{o4} = r_{o5} = \frac{|V_A|}{I_D} = \frac{20 \text{ V}}{50 \mu\text{A}} = 400 \text{ k}\Omega$$

So,

$$80 \text{ V/V} = g_m(400 \text{ K} \parallel 400 \text{ K})$$

and

$$g_m = 400 \mu\text{A/V}$$

$$\text{Since } g_m = \frac{|I_D|}{|V_{OV}|/2},$$

$$|V_{OVI}| = |V_{OVI}| = |V_{OVA}| = |V_{OVS}| = \frac{2 I_D}{g_m}$$

$$= \frac{2(50 \mu\text{A})}{400 \mu\text{A/V}} = 0.25 \text{ V}$$

so,

$$V_{GS1} = V_{GS2} = V_{OV} + V_{th} = -0.25 + 0.7 \\ = -0.95 \text{ V}$$

For  $\left(\frac{W}{L}\right)$  ratios

$$I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{OV})^2$$

So that

$$\frac{W}{L} = \frac{2 I_D}{\mu C_{ox} V_{OV}^2}$$

For  $Q_7$ ,

$$\left(\frac{W}{L}\right)_7 = \frac{2(100 \mu\text{A})}{90 \mu\text{A/V}^2 (0.3 \text{ V})^2} = 24.7$$

For  $Q_4$  and  $Q_5$ ,

$$\left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_5 = \frac{2(50 \mu\text{A})}{90 \mu\text{A/V}^2 (0.3 \text{ V})^2} = 12.3$$

For  $Q_1$  and  $Q_2$ ,

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \frac{2(50 \mu\text{A})}{30 \mu\text{A/V}^2 (0.25 \text{ V})^2} = 53.3$$

For  $Q_6$  and  $Q_3$ ,

$$\left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_3 = \frac{2(100 \mu\text{A})}{30 \mu\text{A/V}^2 (0.3 \text{ V})^2} = 74.1$$

In summary, the results are as follows:

	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$	
$\mu C_{ox}$	30	30	30	90	90	30	90	$\mu\text{A/V}^2$
$I_D$	50	50	100	50	50	100	100	$\mu\text{A}$
$V_{OV}$	-0.25	-0.25	-0.3	0.3	0.3	-0.3	0.3	V
$\frac{W}{L}$	53.3	53.3	74.1	12.3	12.3	74.1	24.7	
$V_{GS}$	-0.95	-0.95	-1	1	1	-1	1	V

7.20

$$(a) I_{D1} = \frac{1}{2} k_n \frac{W}{L} (V_{GS1} - V_i)^2$$

$$I_{D2} = \frac{1}{2} k_n \left(2 \times \frac{W}{L}\right) (V_{GS2} - V_i)^2$$

Since  $V_{GS} - V_i$  is equal for both transistors :

$$\Rightarrow \frac{I_{D1}}{I_{D2}} = \frac{1}{2}; I_{D2} = 2 I_{D1}$$

$$\text{but } I = I_{D1} + I_{D2} = 3 I_{D1}$$

$$I_{D1} = I/3$$

$$I_{D2} = 2I/3$$

$$(b) V_{ov} = V_{GS} - V_i$$

$$V_{ov1} = V_{ov2} = V_{ov}$$

$$\text{For Q1: } \frac{I}{3} = \frac{1}{2} k_n \left( \frac{W}{L} \right) V_{ov}^2$$

$$\Rightarrow V_{ov} = \sqrt{\frac{2}{3k_n W/L} I}$$

$$(c) g_m = \frac{2I_D}{V_{ov}} \rightarrow g_{m1} = \frac{2I}{3V_{ov}}$$

$$g_{m2} = \frac{4}{3} \frac{I}{V_{ov}}$$

$$v_{o1} = -g_{m1} \times \frac{v_{id}}{2} \cdot R_D$$

$$= -\frac{2}{3} \frac{I}{V_{ov}} \cdot R_D \cdot v_{id}$$

$$v_{o2} = +g_{m2} \times \frac{v_{id}}{2} \cdot R_D$$

$$= \frac{4}{3} \frac{I}{V_{ov}} \cdot R_D \cdot v_{id}$$

$$\Rightarrow \frac{v_{o2} - v_{o1}}{v_{id}} = \left( \frac{4}{3} + \frac{2}{3} \right) \frac{1}{V_{ov}} \cdot R_D$$

$$= 2 \times \frac{I}{V_{ov}} \cdot R_D$$

7.21

$$A_d = g_{m1}(R_{in} \parallel R_{op})$$

$$= g_{m1}[(g_{m3}r_{os})r_{o1} \parallel (g_{m3}r_{os})r_{o2}]$$

If all transistors have the same channel length and the

$$\text{same } |V_{ov}| \text{ and } |V_A| \text{ Since } g_m = \frac{2I_D}{V_{ov}}$$

$$r_o = \frac{V_A}{I_D} \text{ and with } g_m \text{ and } r_o \text{ the same for all devices,}$$

$$A_d = \frac{2I_D}{V_{ov}} \left[ \left( \frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} \right) \parallel \left( \left( \frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} \right) \frac{V_A}{I_D} \right) \right]$$

$$= \frac{2I_D}{V_{ov}} \left[ \frac{2V_A^2}{V_{ov} I_D} \parallel \frac{2V_A^2}{V_{ov} I_D} \right]$$

$$= \left( \frac{2I_D}{V_{ov}} \cdot \frac{V_A^2}{V_{ov} I_D} \right)$$

$$= \frac{2V_A^2}{V_{ov}^2} = 2 \left( \frac{|V_A|}{|V_{ov}|} \right)^2$$

For  $A_d = 1000 \text{ V/V}$  and  $|V_{ov}| = 0.2 \text{ V}$

$$1000 = 2 \frac{|V_A|^2}{|V_{ov}|^2}$$

$$V_A = \sqrt{500} \cdot 0.2 \text{ V} = 4.47 \text{ V}$$

$$\text{If } |V_A| = 10 \text{ V/}\mu\text{A}$$

$$L = \frac{4.47 \text{ V}}{10 \text{ V/}\mu\text{A}} = 0.447 \mu\text{m}$$

For high  $g_m$  the bias current should be high, but with  $\pm 0.9 \text{ V}$  Supplies the bias current must not exceed  $\frac{1 \text{ mW}}{1.8 \text{ V}} = 0.556 \text{ mA}$  to keep power dissipation at 1 mW

7.22

$$V_{ov} = \sqrt{\frac{I}{Ku'w/L}} = \sqrt{\frac{0.2}{3}} = 0.26 \text{ V}$$

$$g_m = \frac{I}{V_{ov}} = \frac{0.2 \text{ mA}}{0.26 \text{ V}} = 0.77 \frac{\text{mA}}{\text{V}}$$

(a) Single-ended output:

$$|Ad| = \frac{1}{2} g_m \times R_D = \frac{0.77}{2} \times 10 = \underline{\underline{3.85 \text{ V/V}}}$$

$$|A_{cm}| = \frac{R_D}{2R_{ss}} = \frac{10}{2 \times 100} = \underline{\underline{0.05 \text{ V/V}}}$$

$$CMRR = \left| \frac{Ad}{A_{cm}} \right| = \frac{3.85}{0.05} = 77 \\ i.e \underline{\underline{37.7 \text{ dB}}}$$

(b) Differential output, and 1% mismatch in  $R_D$ 's:

$$|Ad| = g_m R_D \\ = 0.77 \times 10 = \underline{\underline{7.7}} \text{ V/V}$$

$$|A_{cm}| = \frac{R_D}{2R_{SS}} \times \left( \frac{\Delta R_D}{R_D} \right)$$

$$= \frac{10}{2 \times 100} \times 0.01 = \underline{\underline{0.5 \mu \text{V/V}}}$$

$$CMRR = \left| \frac{Ad}{A_{cm}} \right| = \frac{7.7}{0.5 \times 10^3} = 15,400$$

$$\text{i.e. } \underline{\underline{83.7 \text{ dB}}}$$

7.23

$$V_{OV} = -\sqrt{\frac{I}{K_p' w/L}} = -\sqrt{\frac{0.7 \mu A}{3.5 \frac{\mu A}{V^2}}} \\ = \underline{\underline{-0.45V}}$$

$$g_m = \frac{I}{|V_{OV}|} = \frac{0.7 \mu A}{0.45V} = 1.56 \frac{\mu A}{V}$$

$$|Ad| = g_m R_D = 1.56 \times 2 = \underline{\underline{3.12 \text{ V/V}}}$$

$$|A_{cm}| = \frac{R_D}{2R_{SS}} \cdot \left( \frac{\Delta R_D}{R_D} \right) = \frac{2}{2 \times 30} \times 0.02 \\ = \underline{\underline{6.7 \times 10^{-4}}}$$

$$CMRR = \frac{3.12}{6.7 \times 10^{-4}} = 4680 \rightarrow \underline{\underline{73.4 \text{ dB}}}$$

7.24

$$(a) R_{D1} = R_D + \frac{\Delta R_D}{2}, R_{D2} = R_D - \frac{\Delta R_D}{2}$$

$$g_{m1} = g_m + \frac{\Delta g_m}{2}, g_{m2} = g_m - \frac{\Delta g_m}{2}$$

$$i_{d1} = \frac{g_{m1} V_{icm}}{g_m R_{SS}}, i_{d2} = \frac{g_{m2} V_{icm}}{2g_m R_{SS}}$$

$$i_{d1} - i_{d2} = (g_{m1} - g_{m2}) \frac{V_{icm}}{2g_m R_{SS}}$$

$$= \Delta g_m \frac{V_{icm}}{2g_m R_{SS}} \quad (1)$$

$$i_{d1} + i_{d2} = (g_{m1} + g_{m2}) \frac{V_{icm}}{2g_m R_{SS}}$$

$$= (2g_m) \frac{V_{icm}}{2g_m R_{SS}} = \frac{V_{icm}}{R_{SS}} \quad (2)$$

$$V_{od} = V_{O2} - V_{O1} = -i_{d2} R_{D2} + i_{d1} R_{D1}$$

$$= -i_{d2} \left( R_D - \frac{\Delta R_D}{2} \right) + i_{d1} \left( R_D + \frac{\Delta R_D}{2} \right)$$

$$V_{od} = R_D (i_{d1} - i_{d2}) + \frac{\Delta R_D}{2} (i_{d2} + i_{d1})$$

Now substitute (1) and (2)

$$V_{od} = R_D \left( \Delta g_m \frac{V_{icm}}{2g_m R_{SS}} \right) + \frac{\Delta R_D}{2} \left( \frac{V_{icm}}{R_{SS}} \right)$$

$$A_{cm} = \frac{V_{od}}{V_{icm}} = \frac{R_D}{R_{SS}} \cdot \frac{\Delta g_m}{2g_m} + \frac{\Delta R_D}{2R_{SS}}$$

$$= \frac{R_D}{2R_{SS}} \left[ \frac{\Delta g_m}{g_m} + \frac{\Delta R_D}{R_D} \right]$$

$$(b) R_D = 5 \text{ k}\Omega, R_{SS} = 25 \text{ k}\Omega$$

If  $A_{cm} = 0.002 \text{ V/V}$ , use the result of (a)

$$A_{cm} = 0.002 = \frac{R_D}{2R_{SS}} \left[ \frac{\Delta g_m}{g_m} + \frac{\Delta R_D}{R_D} \right]$$

So,  $\Delta R_D$  can compensate for  $\Delta g_m$

$$0.002 = \frac{5 \text{ k}\Omega}{2.25 \text{ k}\Omega} \cdot \frac{\Delta R_D}{5 \text{ k}\Omega}$$

$$\Delta R_D = 0.002(50 \text{ k}\Omega) = 100 \text{ }\Omega$$

so a 100 ohm compensation in  $R_D$  (a 2% adjustment) is sufficient.

7.25

If  $A_O = 100$  (40dB),  $R_{SS}$  and therefore CMRR will increase by 40 dB.

$$A_O = \frac{V_A}{V_{OV}/2}$$

$$V_A = 100 \cdot \frac{V_{OV}}{2} = 100 \left( \frac{0.2 \text{ V}}{2} \right) = 10 \text{ V}$$

$$\text{for } V_A = \frac{10 \text{ V}}{\mu \text{m}}, L = 1 \mu \text{m}$$

7.26

$$U_{BE} = 0.7 \text{ V at } i_c = 1 \text{ mA}$$

$$\rightarrow \text{at } i_c = 0.5 \text{ mA } V_{BE} = -2 \text{ V}$$

$$U_{BE} = 0.7 + 25 \text{ mV} \ln\left(\frac{0.5}{1}\right)$$

$$= 0.683 \text{ V}$$

Thus,

$$\begin{aligned} U_E &= U_{CM} - U_{BE} \\ &= -2 - 0.683 = -2.683 \text{ V} \end{aligned}$$

$$I_{C1} = I_{C2} = \alpha \times 0.5 = \frac{100}{101} \times 0.5$$

$$= 0.495 \text{ mA}$$

$$V_{C1} = V_{C2} = V_{CC} - i_c R_C$$

$$= 5 - 0.495 \times 3$$

$$= +3.515 \text{ V}$$

7.27

$$I = 0.5 \text{ mA So } I_{C1} = I_{C2} = 0.25 \text{ mA}$$

$$V_E = V_B - V_{BE} \quad V_{BE} = 0.7 + 0.025 \cdot \ln\left(\frac{i_t}{1}\right)$$

$$\text{for } i_t = 0.5 \text{ mA, } V_{BE} = 0.683 \text{ V}$$

$$\text{if } V_{B1} = 0.5 \text{ V and } V_{B2} = 0 \text{ V, } V_{id} = 0.5 \text{ V}$$

$$i_{t1} = \frac{I}{1 + e^{-V_{id}/V_T}} = \frac{0.5 \text{ mA}}{1 + e^{-0.5 \text{ V} / 0.025 \text{ V}}}$$

$$= \frac{0.5 \text{ mA}}{1 + e^{-20}} = 0.5 \text{ mA}$$


$$i_{t2} = \frac{I}{1 + e^{V_{id}/V_T}} = \frac{0.5 \text{ mA}}{1 + e^{0.5 / 0.025}}$$

$$= \frac{0.5 \text{ mA}}{1 + e^{20}} \approx 1 \times 10^{-12} \text{ A}$$

$$i_{C1} = \frac{100}{101} \times 0.5 \text{ mA} = 0.495 \text{ mA}$$

$$V_{C1} = 2.5 \text{ V} - (0.495 \text{ mA})(8 \text{ k}\Omega)$$

$$= -1.46 \text{ V}$$

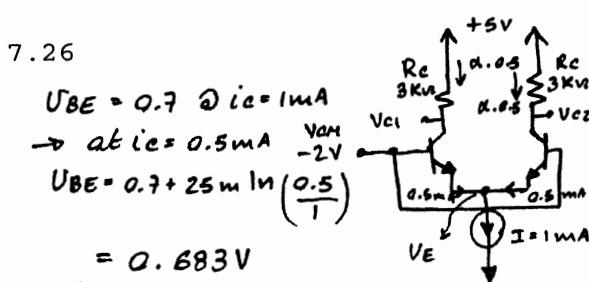

$$i_{C2} \approx 0 \quad V_{C2} = 2.5 \text{ V}$$

$$V_t = 0.5 \text{ V} - 0.683 \text{ V} = -0.183 \text{ V}$$

$$\text{if } V_{B1} = -0.5 \text{ V and } V_{B2} = 0 \text{ V}$$

$$V_{id} = -0.5 \text{ V } i_{t1} \approx 0 \quad i_{t2} \approx 0.5 \text{ mA}$$

(Same equations as above)

$$V_{C1} = 2.5 \text{ V } V_{C2} = -1.46 \text{ V}$$

$$V_t = 0 - 0.683 \text{ V} = -0.683 \text{ V}$$

7.28

$$V_{CM\max} = V_{CC} - \alpha \frac{I}{2} R_C + 0.4 \text{ V}$$

$$= 2.5 \text{ V} - \frac{100}{101} \left( \frac{0.5 \text{ mA}}{2} \right) 8 \text{ k}\Omega + 0.4 \text{ V} = 0.92 \text{ V}$$


$$\begin{aligned} V_{CM\min} &= -V_{EE} + V_{CS} + V_{BE} \\ &= -2.5 \text{ V} + 0.3 \text{ V} + V_{BE} \end{aligned}$$

$$V_{BE} = 0.7 \text{ V} + 0.025 \ln\left(\frac{0.25 \text{ mA}}{1 \text{ mA}}\right) = 0.665 \text{ V}$$

$$V_{CM\min} = -2.2 \text{ V} + 0.665 \text{ V} = -1.53 \text{ V}$$

So  $-1.53 \text{ V} < V_{CM} < 0.92 \text{ V}$

7.29

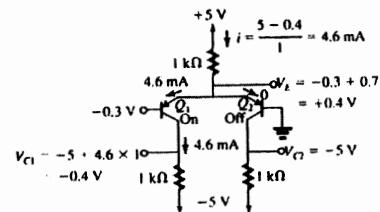

7.30

$$V_{BE} = 690 \text{ mV at } i_C = 1 \text{ mA } \beta = 50$$

$$V_{CE(SAT)} = 0.3 \text{ V}$$

$$R_C = 82 \text{ k}\Omega \quad V_{CC} = -V_{EE} = 1.2 \text{ V}$$

$$I = 20 \mu\text{A}$$

(a)

$$V_{RE} = 690 \text{ mV} + 25 \text{ mV} \ln\left(\frac{10 \mu\text{A}}{1000 \mu\text{A}}\right) = 575 \text{ mV}$$

$$V_E = V_B - V_{BE} = -575 \text{ mV}$$

$$V_{C1} = V_{C2} = 1.2 \text{ V} - (10 \mu\text{A})(82 \text{ k}\Omega) = 0.38 \text{ V}$$

(b)

$$V_{CM\ MAX} = V_{CC} - \alpha \frac{I}{2} R_C + 0.4 \text{ V}$$

$$= 1.2 \text{ V} - \frac{50}{51} 10 \mu\text{A} \cdot 82 \text{ k}\Omega + 0.4 \text{ V}$$

$$= 0.8 \text{ V}$$

$$V_{CM\ MIN} = V_{EE} + V_{CS} + V_{BE}$$

$$= -1.2 \text{ V} + 0.3 \text{ V} + 0.575 \text{ V} = -0.325 \text{ V}$$

So  $-0.325 \text{ V} \leq V_{CM} \leq 0.80 \text{ V}$

(c)

$$i_{E1} = I \left( \frac{I}{2} \right) = \frac{1}{e^{-V_{id}/V_T} - 1} \cdot \frac{1}{0.55} = 1 + e^{-V_{id}/V_T}$$

$$0.82 = e^{-V_{id}/V_T}$$

$$-V_T \ln(0.82) = V_{id} = 5 \text{ mV}$$

if  $V_{B2} = 0, V_{B1} = +5 \text{ mV}$

$$(c) V_{CM\ MAX} = 3 = 5 - \frac{I}{2} R_C$$

$$\Rightarrow I R_C = \underline{\underline{4V}}$$

$$(d) \frac{I/2}{\beta+1} \leq 2 \mu\text{A}$$

$$\Rightarrow I \leq 4(\beta+1) \mu\text{A}$$

$$\text{Thus, } I = 4 \times 10 \mu\text{A} = 0.404 \mu\text{A}$$

$$\text{Select } I = \underline{\underline{0.4 \mu\text{A}}}$$

$$R_C = \frac{4V}{I} = \frac{4V}{0.4 \mu\text{A}} = \underline{\underline{10 \text{ k}\Omega}}$$

### 7.31

With only common-mode at the inputs

$$V_{C1} = V_{C2} = V_{CC} - \alpha \frac{I}{2} R_C + V_r$$

therefore the ripple voltage directly appears at the single-ended output  $V_{C1}$  and  $V_{C2}$

However, because the differential output

$V_{od} = V_{C2} - V_{C1}$  does not include the common-mode output, the ripple voltage does not appear on the differential output.

This is an advantage of using the differential output compared to using the single ended output.

### 7.33

$$i_{E1} = \frac{I}{e^{-V_d/V_T} - 1}, v_d = v_{B1} - v_{B2}$$

$$\frac{\Delta i_{E1}}{I} = \frac{i_{E1} - I/2}{I} = \frac{I_{E1}}{I} - 0.5$$

Define normalized Gain

$$G_n = \frac{\Delta i_{E1} I}{v_d}$$

$v_d (\text{mV})$	5	10	20	30	40
$G_n$	9.97	9.87	9.50	8.95	8.30

Observe that the gain stays relatively constant upto  $V_d$  nearly 20 mV. Then it decreases significantly with the increase in signal level. Whenever gain depends on signal level, nonlinear distortion occurs.

### 7.32

$$(a) V_{CM\ MAX} = V_{C1,2} = V_{CC} - \underline{\underline{\frac{I}{2} \cdot R_C}}$$

(b) If the current is steered to  $Q_1$ , then

$V_{C1} = V_{CC} - I R_C$ , a change of:  $\underline{\underline{-\frac{I}{2} R_C}}$

$V_{C2} = V_{CC} + \underline{\underline{\frac{I}{2} R_C}}$

7.34

With:

$$V_{B1} - V_{B2} = 10 \text{ mV}$$

$$i_{E1} = \frac{I}{1 + e^{-10/25}} = 0.598 I$$

Since  $i_{E1} + i_{E2} = I$   
 $i_{E2} = 0.402 I$

For a collector resistance  $R_C$

$$V_o = V_{c1} - V_{c2} = (V_{cc} - i_{c1} R_C) - (V_{cc} - i_{c2} R_C)$$

$$= -(i_{c2} - i_{c1}) R_C$$

$$= -\alpha (i_{E2} - i_{E1}) R_C$$

$$\approx -0.196 I R_C$$

Thus, for

$$V_o = 1V; 0.196 I R_C = 1$$

$$I R_C = 5.102$$

Now  $I = 2 \text{ mA}$ , thus

$$R_C = \underline{\underline{2.5 \text{ k}\Omega}}$$

DC (bias) voltage at each collector

$$= V_{cc} - \frac{I}{2} R_C = 10 - 1 \times 2.5 = 7.5V$$

For a -1V output swing, the minimum voltage at each collector is:

$$7.5 - 0.5 = 7.0V$$

$$\text{Thus, } V_{icm|_{max}} = \underline{\underline{7V}}$$

7.35

$$i_{E1} = \frac{I}{1 + e^{-V_{id}/V_T}} \text{ and } i_{E2} = \frac{I}{1 + e^{V_{id}/V_T}}$$

$$\text{with } V_{id} = v_{B1} - v_{B2} = 5 \text{ mV, and } \alpha = 1,$$

$$i_{c1} \approx i_{E1} = \frac{I}{1 + e^{-5 \text{ mV}/25 \text{ mV}}} = 0.55 I$$

$$i_{c2} \approx i_{E2} = \frac{I}{1 + e^{5 \text{ mV}/25 \text{ mV}}} = 0.45 I$$

$$V_{c2} - V_{c1} = (V_{cc} - i_{c2} R_C) - (V_{cc} - i_{c1} R_C)$$

$$= -0.45 I R_C + 0.55 I R_C = 0.1 I R_C$$

$$A_v = \frac{v_o}{V_{id}} = \frac{(0.1) I R_C}{0.005 \text{ V}} = (20 I R_C) \text{ V/V}$$

(b) Each collector is biased at  $V_{cc} - \frac{I}{2} R_C$

If we want to maintain the same differential input, each collector should be allowed to fall by

$$\frac{0.1 I R_C}{2} \text{ below its bias value.}$$

so,

$$V_{c(min)} = V_{cc} - 0.5 I R_C - 0.05 I R_C$$

$$= V_{cc} - 0.55 I R_C$$

If this is permitted until  $v_{cb} = 0$ ,

$$V_{ICM(max)} = V_{c(min)} = V_{cc} - 0.55 I R_C$$

If the gain is  $20 I R_C$ ,

$$I R_C = \frac{A_v}{20} \text{ so that}$$

$$V_{ICM(max)} = V_{cc} - \frac{0.55 A_v}{20} = V_{cc} - 0.0275 A_v$$

so, for a given  $V_{cc}$ ,  $A_v$  reduces the maximum allowed  $V_{ICM}$ .

$A_v (\text{V/V})$	100	200	300	400
$V_{ICM(max)}$ (V)	$V_{cc} - 2.75$	$V_{cc} - 5.5$	$V_{cc} - 8.25$	$V_{cc} - 11$
$I R_C (\text{V})$	5	10	15	20
$R_C (\text{k}\Omega)$	5	10	15	20

For example, if  $V_{cc} = 10 \text{ V}$ , a gain of 200 can be achieved by increasing  $R_C$  to  $10 \text{ k}\Omega$ , the maximum common-mode input voltage would be  $V_{cc} - 5.5 = 4.5 \text{ V}$ . If a gain of 300 is required, if can be achieved by changing  $R_C$  to  $15 \text{ k}\Omega$ . However this means that  $V_{ICM(max)} = V_{cc} - 8.25 = 1.75 \text{ V}$ .

7.36

$$I = 6 \text{ mA}$$

The current will divide between the two transistors in proportion to their emitter areas. Thus with no input,

$$I_{E1} = 1.5 I_{E2}$$

$$I_{E1} + I_{E2} = 2.5 I_{E2} = 6 \text{ mA}$$

$$I_{E2} = 2.4 \text{ mA}$$

$$I_{E1} = 3.6 \text{ mA}$$

For  $\alpha \approx 1$

$$I_{C1} = 3.6 \text{ mA}$$

$$I_{C2} = 2.4 \text{ mA}$$

To equalize the collector currents we apply a difference signal  $V_d = V_{B2} - V_{B1}$  whose value can be determined as follows :

$$I_{E1} = I_{SE1} e^{((V_{B1} - V_E)/VT)}$$

$$I_{E2} = I_{SE2} e^{((V_{B2} - V_E)/VT)}$$

$$\text{where } I_{SE1}/I_{SE2} = 1.5$$

Now,  $I_{E1} = I_{E2}$  when

$$1 = 1.5 e^{(V_{B1} - V_{B2})/VT}$$

$$V_d = V_{B2} - V_{B1} = VT \ln 1.5 = 10.1 \text{ mV}$$

7.37

(a)

$$V_{BE} = 690 \text{ mV} + 25 \text{ mV} \ln \left( \frac{0.2/2}{1} \right) = 632 \text{ mV}$$

$$R_e = 0, V_{id} = 0$$

(b) Eqn 8.73

$$i_{C1} = \alpha i_{E1} \approx i_{E1} = \frac{200 \mu\text{A}}{1 + e^{-20/25}} = 138 \mu\text{A}$$

$$i_{C2} = \alpha i_{E2} \approx i_{E2} = \frac{200 \mu\text{A}}{1 + e^{-20/25}} = 62 \mu\text{A}$$

$$R_e = 0, V_{id} = 20 \text{ mV}$$

(c)

$$V_{BE1} = 690 \text{ mV} + 25 \text{ mV} \ln \left( \frac{138}{1} \right) = 640 \text{ mV}$$

$$V_{BE2} = 690 \text{ mV} + 25 \text{ mV} \ln \left( \frac{62}{1} \right) = 620 \text{ mV}$$

$$V_{BE1} - V_{BE2} = 20 \text{ mV}$$

$$200 \text{ mV} = V_{id} = V_{B1} - V_{B2}$$


$$= (V_{BE1} + 138 \mu\text{A} R_E + V_E)$$

$$- (V_{BE2} + 62 \mu\text{A} R_E + V_E)$$

$$200 \text{ mV} = V_{B1} - V_{B2} + (138 \mu\text{A} - 62 \mu\text{A}) R_E$$

$$180 \text{ mA} = 76 \mu\text{A} \cdot R_E$$

$$R_E = 2.37 \text{ k}\Omega$$

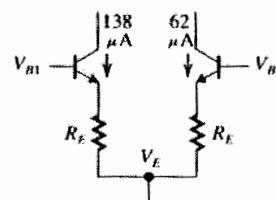

(d) Without  $R_E$ , a  $V_{id}$  of 20 mV causes a differential current of 76 μA

$$G_m = \frac{76 \mu\text{A}}{20 \text{ mV}} = 3.8 \text{ mA/V} = (263 \Omega)^{-1}$$

with  $R_E = 2.37 \text{ k}\Omega$ , a  $V_{id}$  of 200 mV causes a differential current of 76 μA

$$G_m = \frac{76 \mu\text{A}}{200 \text{ mV}} = 0.38 \text{ mA/V} = (2.63 \text{ k}\Omega)^{-1}$$

So  $G_m$  has been reduced by a factor of 10. This is the same factor by which  $V_{id}$  increased. So we have traded differential gain for a wider usable input range.

7.38

Each device is operating at a current of  $150 \mu\text{A} = 0.15 \text{ mA}$ . Thus,

$$g_m = \frac{0.15 \text{ mA}}{25 \text{ mV}} = \frac{6 \text{ mA}}{\text{V}}$$

$$R_{id} = 2(\beta + 1) r_e = 2 \text{ f}\pi$$

$$= 2 \times \frac{150}{4} = \underline{\underline{75 \text{ k}\Omega}}$$

7.39

$$R_{id} > 10K\Omega ; A_d = 200 \text{ V/V}$$

$$\beta > 100 ; V_{ce} = 10V$$

$$R_{id} = 10^4 + 2\pi = 2 \times \frac{100}{8m} = 25\Omega$$

$$\Rightarrow g_m = 20 \text{ mA/V}$$

Thus each device is operating at  $0.5 \text{ mA}$  and  $I = \underline{\underline{1 \text{ mA}}}$

$$\text{Voltage gain} = g_m \cdot R_c$$

$$200 = 20 R_c$$

$$\Rightarrow R_c = \underline{\underline{10K\Omega}}$$


7.40

$$r_e = \frac{5 \text{ mV}}{I/2} = \frac{25 \text{ mV}}{50 \text{ mA}} = \underline{\underline{500 \Omega}}$$

$$\text{Half-circuit gain} = \frac{\alpha R_c}{r_e} = \frac{R_c}{r_e} = \frac{10K}{500} = \underline{\underline{20 \text{ V/V}}}$$

At one collector we expect a signal of (+100mV) and at the other a signal of (-100mV)

7.41

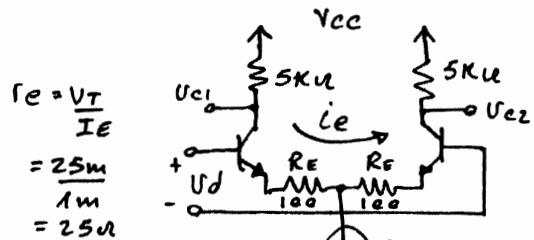


$$(a) i_e = \frac{U_d}{2(r_e + R_E)} = \frac{0.1 \text{ V}}{2(25 + 100) \Omega} = \underline{\underline{0.4 \text{ mA}}}$$

$$(b) i_{E1} = I + 0.4 = \underline{\underline{1.4 \text{ mA}}} \\ i_{E2} = I - 0.4 = \underline{\underline{0.6 \text{ mA}}}$$

$$(c) U_{c1} = -i_e R_C \approx -0.4 \times 5 = \underline{\underline{-2V}} \\ U_{c2} = +\underline{\underline{2V}}$$

$$(d) U_{od} = 4V \\ A_d = U_{od} / U_{id} = \frac{4}{0.1} = \underline{\underline{40 \text{ V/V}}}$$

7.42

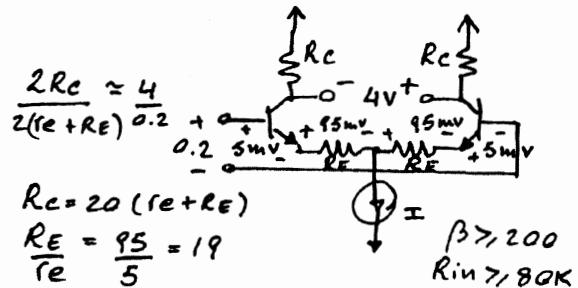

$$\frac{2R_C}{2(r_e + R_E)} \approx \frac{4}{0.2} = 20$$

$$R_E = \frac{95}{5} = 19$$

$$\beta > 200 \\ R_{in} > 80K$$

$$\begin{aligned}
 R_{in} &= 2(\beta+1)(r_e + R_E) \\
 &= 2 \times 201 \times 20 \text{ mV} = 80 \text{ k}\Omega \\
 \Rightarrow r_e &\approx \frac{80000}{8000} = 10 \text{ mV}
 \end{aligned}$$

Thus each device is operating at a current of  $\frac{25 \text{ mV}}{10 \mu\text{A}} = 2.5 \text{ mA}$

$$\Rightarrow I = 5 \text{ mA}$$

$$\begin{aligned}
 R_E &= 19 \times 10 = 190 \text{ mV} \\
 R_C &= 20 \times 200 = 4 \text{ k}\Omega
 \end{aligned}$$

### 7.43

$$(a) V_{BC} \leq 0.4 \text{ V}$$

$$V_B - V_C \leq 0.4 \text{ V}$$

$$(V_{CM} + V_{id}/2) - (V_{CC} - i_{C1}R_C) \leq 0.4 \text{ V}$$

$$\begin{aligned}
 \text{So } V_{CM \max} &= V_{CC} + 0.4 \text{ V} - \frac{\hat{V}_{id}}{2} - i_{C1}R_C \\
 &= V_{CC} + 0.4 \text{ V} - \frac{\hat{V}_{id}}{2} - \left( I_C + g_m \frac{\hat{V}_{id}}{2} \right) R_C \\
 A_d &= g_m R_C \text{ and } g_m = \frac{I_C}{V_T}
 \end{aligned}$$

$$I_C = g_m V_T$$

$$\begin{aligned}
 V_{CM \max} &= V_{CC} + 0.4 \text{ V} - \frac{\hat{V}_{id}}{2} \\
 &- \left[ (g_m V_T R_C) + \left( g_m \frac{\hat{V}_{id}}{2} R_C \right) \right] \\
 &= V_{CC} + 0.4 \text{ V} - \frac{\hat{V}_{id}}{2} - \left[ A_d V_T + A_d \frac{\hat{V}_{id}}{2} \right] \\
 &= V_{CC} + 0.4 \text{ V} - \frac{\hat{V}_{id}}{2} - A_d \left[ V_T + \frac{\hat{V}_{id}}{2} \right]
 \end{aligned}$$

$$\begin{aligned}
 (b) \quad V_{CM \max} &= V_{CC} + 0.4 \text{ V} - \frac{\hat{V}_{id}}{2} - A_d \left( V_T + \frac{\hat{V}_{id}}{2} \right) \\
 &= 5 \text{ V} + 0.4 \text{ V} - \frac{10 \text{ mV}}{2} - 100 \left( 25 \text{ mV} + \frac{10 \text{ mV}}{2} \right) \\
 &= 5 \text{ V} + 0.4 \text{ V} - 5 \text{ mV} - 100 (30 \text{ mV}) \\
 &= 2.395 \text{ V}
 \end{aligned}$$

$$\hat{V}_{id} = A_d \cdot \hat{V}_{id} = 100 \cdot 10 \text{ mV} = 1 \text{ V}$$

$$I_{RC} = 2I_C R_C \quad \text{Eqn 8.80} \quad g_m = \frac{I_C}{V_T}$$

$$I_C = g_m V_T \quad I_{RC} = 2(g_m V_T) R_C \quad \text{Eqn 8.93}$$

$$A_d = g_m R_C$$

$$I_{RC} = 2V_T A_d = (2)(25 \text{ mV})(100) = 5 \text{ V}$$

$$I = \frac{\text{quiescent power}}{V_{CC} - (-V_{EE})} = \frac{5 \text{ mW}}{10 \text{ V}} = 0.5 \text{ mA}$$

$$R_C = \frac{5 \text{ V}}{1} = 10 \text{ k}\Omega$$

(c) For  $V_{CM \max} = 0 \text{ V}$

$$= 5 \text{ V} + 0.4 \text{ V} - \frac{\hat{V}_{id}}{2} - A_d \left( 25 \text{ mV} + \frac{\hat{V}_{id}}{2} \right)$$

$$0 \text{ V} = 5.4 \text{ V} - 5 \text{ mV} - A_d (30 \text{ mV})$$


$$A_d = \frac{5.395 \text{ V}}{30 \text{ mV}} = 180 \text{ V/V}$$

(for  $\hat{V}_{id} = 10 \text{ mV}$ )
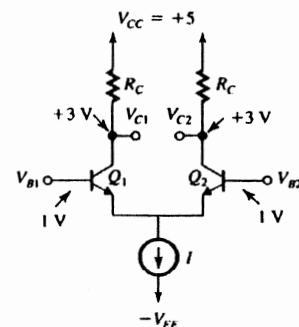
### 7.44

with  $I_{RC} = 4 \text{ V}$ , and assuming that  $\alpha = 1$ ,

$$\begin{aligned}
 V_{C1} &= V_{C2} = V_{CC} - \frac{1}{2} \cdot R_C \\
 &= 5 - 2 = 3 \text{ V}
 \end{aligned}$$



$$(a) v_{B1} = 1 + 0.005 \sin(\omega t)$$

$$v_{B2} = 1 - 0.005 \sin(\omega t)$$

we see

$$\text{that since } \frac{V_{id}}{V_T} = \frac{10.0 \text{ mV}}{25 \text{ mV}} = 0.4,$$

the output will be fairly linear. With the information given,

$$\text{since } i_C = I_E$$

$$i_{C1} \approx \frac{I}{1 + e^{-(V_{id}/V_T)}} \text{ and } i_{C2} \approx \frac{I}{1 + e^{(V_{id}/V_T)}}$$

$$v_{od} = v_{C2} - v_{C1}$$

$$= (V_{CC} - i_{C2}R_C) - (V_{CC} - i_{C1}R_C)$$


or

$$V_{od} = \frac{IR_C}{1 + e^{-V_{id}/V_T}} - \frac{IR_C}{1 + e^{V_{id}/V_T}}$$

with  $I_{RC} = 4 \text{ V}$  and  $|V_{id}| = 10 \text{ mV}$ ,

$$v_{od\max} = 5 \text{ V} \left( \frac{1}{1 + e^{-10/25}} - \frac{1}{1 + e^{10/25}} \right) \\ = 989 \text{ mV}$$
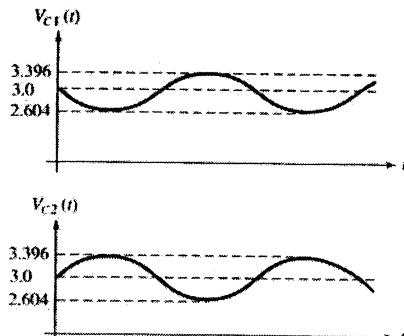
$$\text{so, } A_d = \frac{V_{od\max}}{V_{id\max}} = \frac{989 \text{ mV}}{10 \text{ mV}} = 98.9$$



$$(b) v_{B1} = 1 + 0.1 \sin(\omega t)$$

$$v_{B2} = 1 - 0.1 \sin(\omega t)$$

$$\text{Here, } \frac{V_{id}}{V_T} = \frac{200 \text{ mV}}{25 \text{ mV}} = 8$$

see that this will clearly represent large-signal operation with significant distortion.



Using the same equation,

$$v_{od\max} = 4 \text{ V} \left( \frac{1}{1 + e^{-200/25}} - \frac{1}{1 + e^{200/25}} \right)$$


$$\approx 4.0 \text{ V}$$

$$A_d = \frac{V_{od}}{V_{id}} = \frac{5 \text{ V}}{0.2 \text{ V}} = 25$$

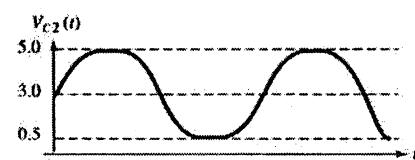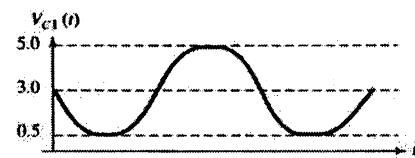waveform is distorted; upper excursions are limited to 5 V.



### 7.45

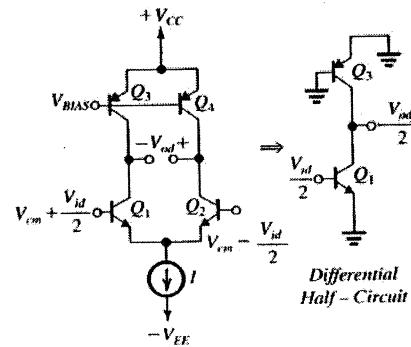

$$|A_d| = \frac{V_{od}}{V_{id}} = g_m(r_{o1} \parallel r_{o2}) \text{ Assuming that}$$

$$I_C = I_E = \frac{I}{2},$$

$$r_{o1} = r_{o2} = \frac{|V_A|}{I_C} = \frac{10 \text{ V}}{I_C} \text{ and}$$

$$g_m = \frac{|V_A|}{V_T} = \frac{I_C}{25 \text{ mV}}$$

$$A_d = \frac{I_C}{25 \text{ mV}} \left( \frac{1}{2} \right) \left( \frac{10 \text{ V}}{I_C} \right) = \frac{5 \text{ V}}{25 \text{ mV}} = 200$$

### 7.46

$$-\frac{V_{od}}{2} = i_b \beta R_C$$



$$i_b = \frac{\frac{V_{id}}{2}}{r_\pi + (\beta + 1)R_e}$$

So,

$$-\frac{V_{od}}{2} = \frac{\frac{V_{id}}{2} \beta R_C}{r_\pi + (\beta + 1)R_e}$$

$$\frac{V_{od}}{V_{id}} = \frac{-R_C}{\frac{r_\pi}{\beta} + \frac{\beta + 1}{\beta} R_e} \text{ If } \alpha \approx 1 \text{ and}$$

(a)

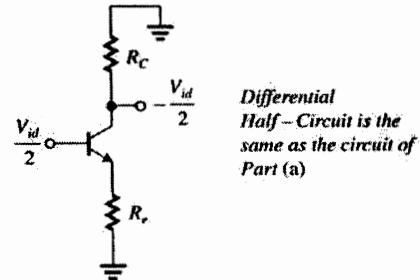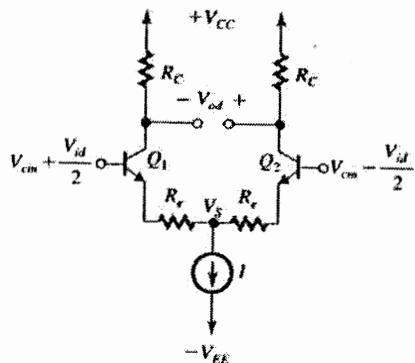

Differential Half-Circuit is the same as the circuit of Part (a)


So, using the same derivation,

$$|A_d| = \left| \frac{V_{od}}{V_{id}} \right| \approx \frac{R_C}{r_e + R_e}$$

$$R_{id} = 2r\pi + 2(\beta + 1)R_e = (\beta + 1)(2r_e + 2R_e)$$

$$V_{Cm} = V_{BE} + V_S$$

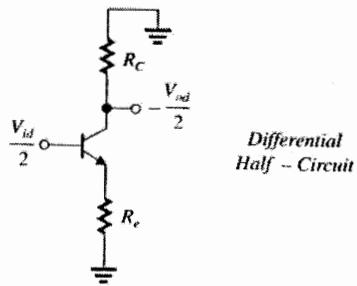Since the quiescent emitter currents do not pass through the  $2R_e$  resistance, there is no drop so that  $V_{Cm}$  can be lower in case (b) than case (a)



noting

$$r_e = \frac{V_T}{I_E},$$

$$|A_d| = \left| \frac{V_{od}}{V_{id}} \right| \approx \frac{R_C}{r_e + R_e} \text{ which is identical to}$$

The half circuit has

$$R_i = r\pi + (\beta + 1)R_e$$


$$R_{id} = 2r\pi + (\beta + 1)(2R_e)$$

This is equivalent to


$$R_{id} = (\beta + 1)(2r_e + 2R_e)$$

$$V_{Cm} = V_{BE} + \frac{I}{2} R_e + V_S$$

(b)

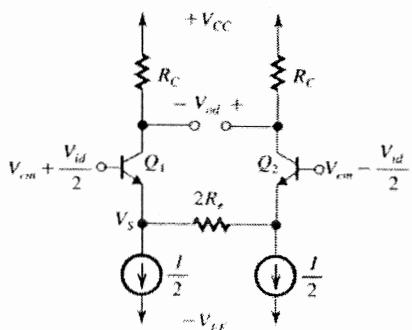

7.47

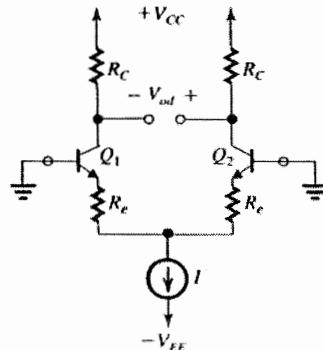

$$V_{RE} = 4V_T \quad V_{RC} = 40V_T$$

From Eq. (8.94),

$$A_d \approx \frac{R_C}{r_e + R_e} = \frac{\frac{40V_T}{I_C}}{\frac{V_T}{I_E} + \frac{4V_T}{I_E}} = \frac{40V_T}{I_E + 4V_T}$$

If  $\alpha \approx 1$ ,  $I_C \approx I_E$ , and


$$A_d = \frac{40V_T}{5V_T} = 8$$

7.48

$$2M\Omega$$

$$\frac{U_o}{U_{icm}} \approx \frac{R_c}{2R} = \frac{20K\Omega}{2M\Omega}$$

$$= \underline{\underline{0.01}} V/V$$

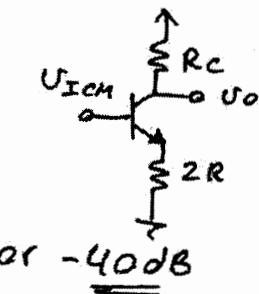


Since  $R_i \gg r_e$ ,

$$\left| \frac{V_o}{V_{id}} \right| \approx \frac{1}{2} \cdot \frac{\alpha R_c}{r_e} \text{ if } \alpha \approx 1,$$

$$\left| \frac{V_o}{V_{id}} \right| \approx \frac{R_c}{2r_e} = \frac{2K}{2(50)} = 20 \text{ V/V}$$
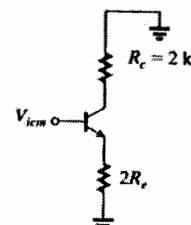
$$(b) A_{ow} \approx \frac{\alpha R_c}{2R_e + r_e}$$



7.49

$$\frac{U_o}{U_i} = \frac{\alpha \times 20K\Omega}{(2r_e + 2 \times 200)\mu}$$

$$\text{Where } r_e = \frac{V_T}{0.5/2} = \frac{0.05V}{0.5mA} = 100\Omega$$

$$\frac{U_o}{U_i} \approx \frac{20000}{600} = \underline{\underline{33.3V/V}}$$

$$R_i = (\beta + 1)(2r_e + 2 \times 200)$$

$$= 101 \times 2 \times 300 \approx \underline{\underline{60K\Omega}}$$

common-mode half circuit

If  $\alpha = 1$ ,

$$A_{ow} \approx \frac{2K}{2(4.3K) + 50} = 0.23$$

(c) CMRR (dB) =  $20 \log_{10}$

$$\left| \frac{V_o / V_{id}}{A_{cm}} \right| = 20 \log_{10} \left| \frac{20}{0.23} \right| = 38.8 \text{ dB}$$

(d)

$$V_{B1} = 0.1 \sin 2\pi \times 60t + 0.005 \sin 2\pi \times 1000t$$

$$V_{B2} = 0.1 \sin 2\pi \times 60t - 0.005 \sin 2\pi \times 1000t$$

$$V_\omega = 0.01 \sin 2\pi \times 1000t$$

$$V_{be} = 0.1 \sin 2\pi \times 60t$$

so that

$$V_o = \left| \frac{V_o}{V_{id}} \right| \cdot V_{id} + A_{cm} \cdot V_{icm}$$

$$V_o(t) = 20 [0.01 \sin 2\pi \times 1000t] + 0.23$$

$$[0.1 \sin 2\pi \times 60t]$$

$$V_o(t) = 0.2 \sin 2\pi \times 1000t + 0.023 \sin 2\pi \times 60t$$

7.50

Each transistor is operating at  $I_E = 1mA$ , thus

$$r_e = 25\Omega \text{ and } r_{it} = 101 \times 25$$

$$= 2525\Omega$$

$$\frac{U_o}{U_i} = \frac{\alpha \times 7.5K\Omega}{(2r_e + 200)\mu} \approx \frac{7500}{250} = \underline{\underline{30V/V}}$$

$$R_i = (\beta + 1)(r_e + 200 + r_e) \approx \underline{\underline{25K\Omega}}$$

7.51

with  $V_{ce} = 0$ ,  $V_b \approx -0.7V$

$$(a) I = \frac{V_T - V_{BE}}{R_E} = \frac{-0.7 - (-0.5)}{4.3K} = 1mA$$

$$r_e = \frac{V_T}{I_E} = \frac{25mV}{1mA/2} = 50\Omega$$

7.52

Each transistor is biased at  $50\Omega$ . Thus,  
 $r_e = 25\Omega$ ,  $g_m = 40mA/V$ ,  
 $r_o = 100/1 = 100K\Omega$

$\sum R_L = 5K\Omega$

$\sum R_E = 100\Omega$

The differential half-circuit is

$$Ad = \frac{U_o}{U_i} = \alpha \left[ R_C \parallel (R_L/2) \right]$$

$$\approx \frac{10/15}{0.025 + 0.100} = \underline{\underline{26.7}} \text{ V/V}$$

$$R_{id} = 2 [R_B \parallel (\beta+1)(r_e + R_E/2)] \\ = 2 [30 \parallel 101 (0.025 + 0.100)] \\ = \underline{\underline{17.8}} \text{ k}\Omega$$


The common-mode half circuit

$$A_{cm} = \frac{U_o}{U_{icm}} \approx \frac{10}{300}$$

$$= \frac{1}{30} = \underline{\underline{0.033}} \text{ V/V}$$

$$2R_{icm} = 30k \parallel 7.5k\Omega \\ = 30k\Omega$$
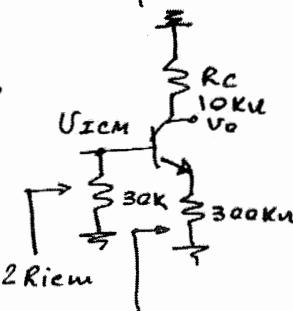
$$R_{icm} = \underline{\underline{15k\Omega}}$$



$$\text{Without the } R_B \quad \approx 30 \parallel 10 = 7.5 \text{ k}\Omega$$

$$\text{resistors } R_{icm} = \underline{\underline{3.75}} \text{ k}\Omega$$

7.53

$$(a) Ad \mid_{\substack{\text{single-ended} \\ \text{output}}} = \alpha \frac{(R_C \parallel r_o)}{2r_e}$$

$$\text{where } r_e = \frac{0.025V}{0.25mA} = 100\Omega$$

$$r_o = \frac{200V}{0.25mA} = 800k\Omega$$

$$Ad \mid_{\substack{\text{single} \\ \text{ended}}} \approx \frac{20}{2 \times 0.1} = \underline{\underline{100}} \text{ V/V}$$

$$(b) Ad \mid_{\substack{\text{differ} \\ \text{output}}} = 2 \times Ad \mid_{\substack{\text{single} \\ \text{ended}}} \\ = \underline{\underline{200}} \text{ V/V}$$

$$(c) R_{id} = 2f\pi = 2 \times 20 \times 100 \\ = \underline{\underline{40.2}} \text{ k}\Omega$$

$$(d) A_{cm} \mid_{\substack{\text{single-ended} \\ \text{output}}} = \frac{R_C}{2R} \\ = \frac{20}{2000} = \underline{\underline{0.1}} \text{ V/V}$$

$$(e) A_{cm} \mid_{\substack{\text{diff out}}} = 0$$

7.54

$$I = 100 \mu\text{A}, \beta = 50, V_A = 20 \text{ V}$$

For Q<sub>o</sub>,

$$R_{EE} = r_{o3} = \frac{V_A}{I} = \frac{20 \text{ V}}{0.1 \text{ mA}} = 200 \text{ k}\Omega$$

$$r_o = r_{o1} = r_{o2} = \frac{V_A}{I/2} = \frac{20 \text{ V}}{0.05 \text{ mA}} = 400 \text{ k}\Omega$$

Using Eq. (8.103),


$$R_{icm} \approx \beta R_{EE} \frac{1 + \frac{R_C}{\beta r_o}}{1 + \frac{R_C + 2R_{EE}}{r_o}} \\ R_{icm} \approx 50(200 \text{ k}) \cdot \frac{1 + \frac{R_C}{(50)(400 \text{ k})}}{1 + \frac{R_C + 2(200 \text{ k})}{400 \text{ k}}}$$

If  $R_C \ll R_{EE}$

and  $R_C \ll r_o$



$$R_{icm} \approx 50(200 \text{ k}) \cdot 5 = 5 \text{ M}\Omega$$

This figure is for 7.54

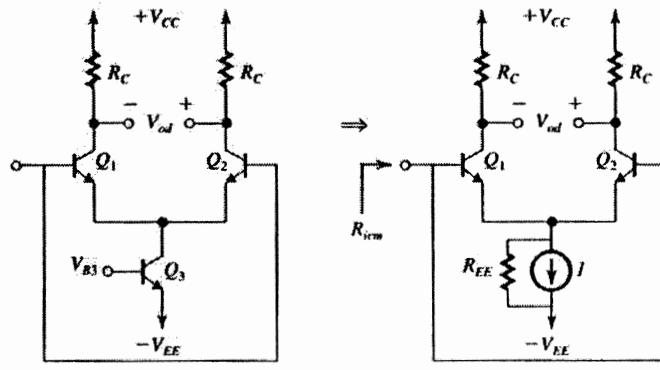

(c)

7.55

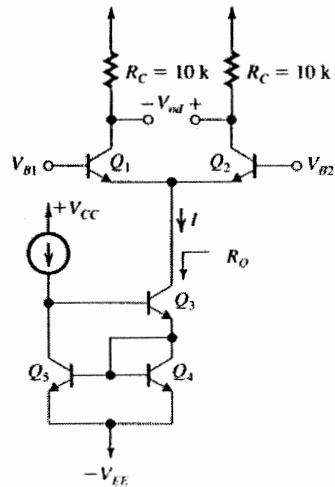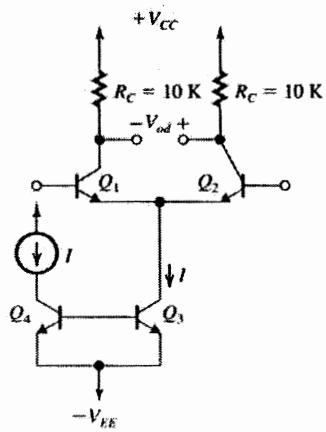

Equivalent

$$R_{EE} = r_{o3} = \frac{V_A}{I} = \frac{10 \text{ V}}{0.5 \text{ mA}} = 20 \text{ k}\Omega$$

$$r_{e2} = r_{e3} = r_e = \frac{V_T}{I/2} = \frac{25 \text{ mV}}{0.5 \text{ mA}/2} = 100 \Omega$$

$$\text{Since } \alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 1,$$

$$A_d \approx \frac{R_C}{r_e} = \frac{10 \text{ k}}{0.1 \text{ k}} = 100 \text{ V/V}$$

$$(b) A_{cm} = \frac{\alpha \Delta R_C}{2R_{EE} + r_e} = \frac{(0.02)(10 \text{ k})}{2(20 \text{ k}) + 0.1 \text{ k}} \\ = 0.00499 \text{ V/V}$$

$$\text{CMRR(dB)} = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right| = 20 \log_{10} \left| \frac{100}{0.00499} \right| \\ = 86 \text{ dB}$$

From Eq. (7.88)

$$R_o \approx \frac{1}{2} \beta_3 r_{o3}$$


$$R_o \approx \frac{1}{2} (100)(20 \text{ k}) = 1 \text{ M}\Omega$$

$$A_{cm} \approx \frac{\Delta R_C}{2R_o + r_o} \approx$$

$$\frac{(0.02)(10 \text{ k})}{2(1 \text{ M}) + 0.1 \text{ k}} = 0.0001 \text{ V/V}$$

$$\text{CMRR(dB)} = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right| = 20 \log_{10} \left| \frac{100}{0.0001} \right| \\ = 120 \text{ dB}$$

7.56

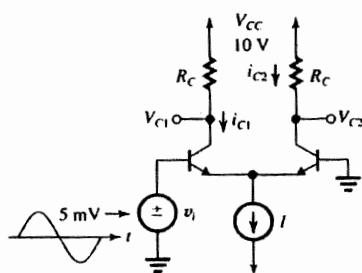

$$i_{c1} = \frac{I}{2} + \left(\frac{I/2}{V_T}\right) \left(\frac{5}{2}\right) \sin \omega t$$

$$i_{c2} = \frac{I}{2} - \left(\frac{I/2}{V_T}\right) \left(\frac{5}{2}\right) \sin \omega t$$

$$v_{c1} = V_{cc} - \frac{I}{2} R_c - \frac{I/2}{V_T} R_c \frac{5}{2} \sin \omega t$$

$$v_{c2} = V_{cc} - \frac{I}{2} R_c - \frac{I/2}{V_T} R_c \frac{5}{2} \sin \omega t$$

$$V_{c1}, V_{c2} \geq 0$$

$$\Rightarrow 10 - 5I - 0.5I = 0$$


$$I = 1.8 \text{ mA}$$

$$V_{c1} = V_{c2} = 1 \text{ V}$$

$$A_d = \frac{20 \text{ k}\Omega}{2r_e}, \text{ where } r_e = \frac{25}{0.9} = 27.8 \Omega$$

Thus,  $A_d = 360 \text{ V/V}$
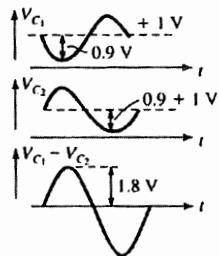
$$v_{c2} - v_{c1} = 1.8 \sin \omega t, \text{ V}$$



7.57

$$\text{Taken single-endedly } A_{cm_s} = \frac{\alpha R_C}{2R_o}$$

Let collector resistors be  $R_c$  &  $R_c + \Delta R_c$ , then

$$A_{cm} = \frac{\alpha}{2R_o} (R_c + \Delta R_c - R_c)$$

$$= \frac{\alpha \Delta R_c}{2R_o}$$

Which can be written as

$$A_{cm_d} = \frac{\alpha R_C}{2R_o} \cdot \frac{\Delta R_C}{R_C} = A_{cm_s} \frac{\Delta R_C}{R_C}$$

$$\text{CMRR} = \frac{A_d}{A_{cm_d}} = \frac{2 \cdot A_s}{A_{cm_s} \frac{\Delta R_C}{R_C}}$$

$$= \frac{A_d}{A_{cm_s}} \cdot \frac{2}{\frac{\Delta R_C}{R_C}}$$

$$\text{Thus, } 20 \log \frac{2}{\frac{\Delta R_C}{R_C}} = 40 \text{ dB}$$

$$\rightarrow \Delta R_C / R_C = 2\%$$


7.58

The bias current will split between the two transistors according to their area ratio. Thus the large-area device will carry twice the current of the other device.

That is, the bias currents will be  $2I/3$  and  $I/3$ .

Now with  $V_{icm}$  applied, the CM signal current will  $\rightarrow V_{icm}/R$

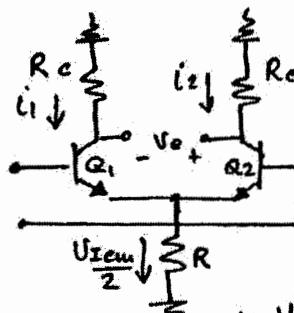split between  $Q_1$  and  $Q_2$  in the same ratio. This is



because their  $r_e$  values will be related in the same way. Thus, if  $Q_1$  is the large device ( $i_1$ )

will be half the value of  $r_{e2}$ .

The result will be that

$$i_1 = \frac{2}{3} \frac{U_{icm}}{R} \text{ and } i_2 = \frac{1}{3} \frac{U_{icm}}{R}$$

Thus the differential output voltage  $V_o$  will be

$$\begin{aligned} V_o &= (-i_2 R_c) - (-i_1 R_c) = (i_1 - i_2) R_c \\ &= \frac{1}{3} \frac{U_{icm}}{R} \cdot R_c \end{aligned}$$

$$A_{cm} = \frac{1}{3} \frac{R_c}{R} = \frac{1}{3} \times \frac{12}{1000} = \underline{\underline{0.004 \text{ V}}}$$

7.59

For  $I = 200 \mu\text{A}$ :

$$\begin{aligned} g_m &= \sqrt{2 K_n W_L I_D} = \sqrt{2 \times 4 \times 0.1} \\ &= 0.89 \text{ mA/V} \end{aligned}$$

$$R_D = 10 \text{ k}\Omega$$

$$\text{Thus, } A_d = g_m R_D = 10 \times 0.89 = \underline{\underline{8.9 \text{ V/V}}}$$

$$V_{os} = \frac{(V_{GS} - V_t)}{2} \cdot \frac{\Delta R_D}{R_D}$$

$$\text{where } \frac{\Delta R_D}{R_D} = 0.02 \text{ (worst case)}$$

$$\begin{aligned} \text{and } V_{GS} - V_t &= \sqrt{\frac{2 I_D}{K_n W_L}} = \sqrt{\frac{2 \times 0.1}{4}} \\ &= \underline{\underline{0.223 \text{ V}}} \end{aligned}$$

$$\begin{aligned} \text{Thus, } V_{os} &= \frac{1}{2} \times 0.223 \times 0.02 \\ &= \underline{\underline{2.23 \text{ mV}}} \end{aligned}$$

For  $I = 400 \mu\text{A}$ :

$$\begin{aligned} g_m &= \sqrt{2 \times 4 \times 0.2} = 1.265 \text{ mA/V} \\ A_d &= \underline{\underline{12.65 \text{ V/V}}} \end{aligned}$$

$$V_{ov} = V_{GS} - V_t = 0.316 \text{ V}$$

$$V_{os} = \frac{1}{2} \times 0.316 \times 0.02 = \underline{\underline{3.16 \text{ mV}}}$$

Thus both  $A_d$  and  $V_{os}$  increase by the same ratio since both are proportional to  $\sqrt{I}$ .

7.60

Worst cases:  $\Delta V_t = 10 \text{ mV}$

$$\frac{\Delta R_D}{R_D} = 0.04; \frac{\Delta (W/L)}{(W/L)} = 0.04$$

$$\begin{aligned} V_{os} (\text{due to } \Delta R_D) &= \frac{V_{ov}}{2} \frac{\Delta R_D}{R_D} = \frac{0.3}{2} \times 0.04 \\ &= \underline{\underline{6 \text{ mV}}} \end{aligned}$$

$$V_{os2} (\text{due to } \Delta w_{IL}) = \frac{V_{ov}}{2} \frac{\Delta w_{IL}}{w_{IL}} = \frac{0.3}{2} \times 0.04 \\ = 6 \text{ mV} //$$

$$V_{os3} (\text{due to } \Delta V_t) = \Delta V_t = \underline{10 \text{ mV}}$$

Since these offsets are not correlated

$$V_{os} = \sqrt{V_{os1}^2 + V_{os2}^2 + V_{os3}^2}$$

$$V_{os} = \sqrt{6^2 + 6^2 + 10^2} = \underline{13.11 \text{ mV}}$$

The major contribution is due to the threshold mismatch  $\Delta V_t$ .

To find the required mismatch  $\Delta R_D$  that can correct for  $V_{os}$

$$13.11 \text{ mV} = \frac{V_{ov}}{2} \cdot \frac{\Delta R_D}{R_D}$$

$$\Rightarrow \frac{\Delta R_D}{R_D} = \frac{2 \times 13.11 \text{ mV}}{0.3 \text{ V}} \\ = 0.087 \text{ or } \underline{8.7\%}$$

If  $\Delta V_t$  is reduced by a factor of 10 to 1 mV,  $V_{os}$  reduces to:

$$\sqrt{6^2 + 6^2 + 1^2} = 8.54 \text{ mV}$$

$$\text{and } \frac{\Delta R_D}{R_D} = \frac{2 \times 8.54 \text{ mV}}{0.3 \text{ V}} = \underline{5.69\%}$$

7.61

$$V_{ov} = \sqrt{\frac{I}{k_n w_{IL}}} = \sqrt{\frac{100}{100 \times 20}} = 0.223 \text{ V}$$

we obtain

$V_{os}$  due to  $\Delta R_D / R_D$  as:

$$V_{os} = \frac{V_{ov}}{2} \frac{\Delta R_D}{R_D} = \frac{0.223}{2} \times \frac{0.05}{2} \\ = 5.57 \text{ mV}$$

From Eqn. (7.117),  $V_{os}$  due to  $\Delta w_{IL} / w_{IL}$  is:

$$V_{os} = \left( \frac{V_{ov}}{2} \right) \frac{\Delta w_{IL}}{w_{IL}} = \frac{0.223}{2} \times 0.05 \\ = \underline{5.57 \text{ mV}}$$

The offset arising from  $\Delta V_t$  is

$$V_{os} = \Delta V_t = \underline{5 \text{ mV}}$$

Worst case offset is:

$$5.57 + 5.57 + 5 = 16.15 \text{ mV}$$

Applying the root-sum-of-squares

$$V_{os} = \sqrt{2(5.57)^2 + 5^2} = \underline{9.33 \text{ mV}}$$

7.62

$$\Delta V_C = \Delta R_C \cdot \frac{I}{2}$$

$$A_d = \frac{R_C}{R_E} = \frac{R_C}{V_T / \frac{I}{2}} = \frac{I R_C}{2 V_T}$$

$$\Rightarrow V_{os} = \frac{\Delta V_C}{A_d} = \frac{\Delta R_C}{R_C} \cdot V_T$$

$$= 0.1 \times 25 = \underline{2.5 \text{ mV}}$$

$$7.63 \quad V_{OS} = V_T \cdot \frac{\Delta I_S}{I_S}$$

$$= 25 \times 0.1 = \underline{\underline{2.5 \mu V}}$$

$$I_{C2} = I_C \left(1 + \frac{V_{CE}}{V_{A2}}\right)$$

Where  $I_C$  can be determined from

$$I_{C1} + I_{C2} = I$$

$$\Rightarrow I_C = \frac{I}{2 + \frac{V_{CE}}{V_{A1}} + \frac{V_{CE}}{V_{A2}}}$$

Note that for  $V_{CE} \ll V_{A1}, V_{A2}$ ,  $I_C \approx \frac{I}{2}$ . Thus, the differential gain  $A_d$  can still be written as

$$A_d \approx \frac{R_C}{r_e} = \frac{I R_C}{2 V_T}$$

The offset voltage at the output can be found from

$$\Delta V_C = v_{C2} - v_{C1} = (I_{C1} - I_{C2})R_e$$

$$= I_C R_C \left( \frac{V_{CE}}{V_{A1}} - \frac{V_{CE}}{V_{A2}} \right)$$

$$= \frac{I}{2} R_C \left( \frac{V_{CE}}{V_{A1}} - \frac{V_{CE}}{V_{A2}} \right)$$

$$\text{Thus, } V_{OS} = \frac{\Delta V_C}{A_d}$$

$$V_{OS} = V_T \left( \frac{V_{CE}}{V_{A1}} - \frac{V_{CE}}{V_{A2}} \right)$$

For

$$V_{CE} = 10 \text{ V}, V_{A1} = 100 \text{ V} \text{ and}$$

$$V_{A2} = 300 \text{ V}$$

$$V_{OS} = 25 \left( \frac{10}{100} - \frac{10}{300} \right)$$

$$= 1.7 \text{ mV}$$

7.64

$$\Delta v_{EE} = \Delta R_C \frac{I}{2}$$

$$A_d = \frac{R_C}{r_e + R_e} = \frac{R_C}{2 V_T + R_E} = \frac{I R_C}{2 V_T + I R_E}$$

$$V_{OS} = \frac{\Delta v_C}{A_d} = \frac{\Delta R_C}{R_C} \left( V_T + \frac{I R_E}{2} \right)$$

7.65

CASE 1: BJT Diff. Amp.

From Eq. (8.121)

$$|V_{OS}| = V_T \left( \frac{\Delta R_C}{R_C} \right) = 25 \text{ mV} (0.04) = 1 \text{ mV}$$

CASE 2: MOSFET Diff. Amp.

$$V_{OS} = \left( \frac{V_{OV}}{2} \right) \left( \frac{\Delta R_D}{R_D} \right) = \frac{300 \text{ mV}}{2} (0.04) = 6 \text{ mV}$$

If the MOSFET widths are increased by a factor of 4, and since  $I_D$  must remain constant, we see that since

$$I_D = \frac{1}{2} K_n \left( \frac{W}{L} \right) V_{OV}^2,$$

$$\text{The new } V_{OV} = \sqrt{\frac{2I_D}{(4)K_n \left( \frac{W}{L} \right)}} \text{ which is } \sqrt{\frac{1}{4}} \text{ or } \frac{1}{2}$$

of its original value.

So, the new offset voltage is

$$V_{OS} = \left( \frac{150 \text{ mV}}{2} \right) (0.04) = 3 \text{ mV}$$

7.66


Since the two transistors are matched except for their  $V_A$  value, we can express the collector currents when the input terminals are grounded as,

$$I_{C1} = I_C \left( 1 + \frac{V_{CE}}{V_{A1}} \right)$$

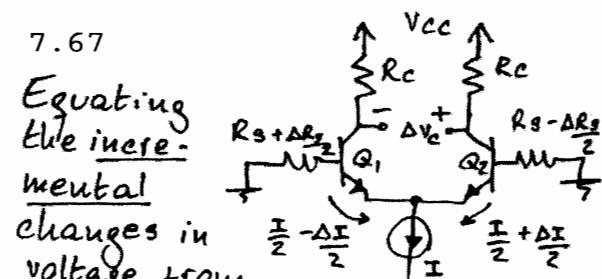7.67

Equating the incremental changes in

voltage from ground to emitter on both sides of the pair (and neglecting second-order terms i.e.  $\Delta x \Delta$  terms):



$$\frac{I}{2(\beta+1)} \cdot \frac{\Delta R_s}{2} - \frac{\Delta I}{2(\beta+1)} \cdot R_s - \frac{\Delta I}{2} \cdot r_e$$

$$\simeq -\frac{I}{2(\beta+1)} \frac{\Delta R_s}{2} + \frac{\Delta I}{2(\beta+1)} R_s + \frac{\Delta I}{2} r_e$$

$$\Delta I \left[ r_e + \frac{R_s}{\beta+1} \right] = \frac{I}{2(\beta+1)} \cdot \Delta R_s$$

$$\Delta I = \frac{I \Delta R_s}{2(\beta+1)} \cdot \frac{1}{r_e + \frac{R_s}{\beta+1}}$$

$$\Delta V_c = -\Delta I \cdot R_c \\ = -\frac{I R_c \Delta R_s}{2(\beta+1)} \cdot \frac{1}{r_e + R_s / (\beta+1)}$$

$$A_d = R_c / r_e$$

$$\text{Thus, } V_{os} = \Delta V_c / A_d$$

$$= -\frac{I \Delta R_s}{2(\beta+1)} \cdot \frac{r_e}{r_e + \frac{R_s}{\beta+1}}$$

For  $\frac{R_s}{\beta+1} \ll r_e$  and  $\beta \gg 1$ ,

$$|V_{os}| \simeq \frac{I}{2\beta} (\Delta R_s) \quad Q.E.D.$$

7.68

$$(a) R_{c1} = 5 \times 1.05 = 5.25 \text{ k}\Omega$$

$$R_{c2} = 5 \times 0.95 = 4.75 \text{ k}\Omega$$

Perfect offset nulling will be achieved when  $x$  is such that

$$R_{c1} + (x \times 1 \text{ k}\Omega) = R_{c2} + (1-x) \times 1 \text{ k}\Omega$$

$$\Rightarrow 5.25 + x = 4.75 + 1 - x$$

$$\Rightarrow x = \underline{\underline{0.25}}$$

$$(b) I_{c1} = 1.05 \text{ mA} \\ I_{c2} = 0.95 \text{ mA}$$

Offset nulling is achieved when  $x$  is such that

$$1.05(x+5) = 0.95(1-x)+5 \\ x = \underline{\underline{0.225}}$$

7.69

$$I_{B\max} = \frac{I/2}{\beta_{\min}+1} = \frac{300}{80+1} = \underline{\underline{3.7}} \text{ mA}$$

$$I_{B\min} = \frac{I/2}{\beta_{\max}+1} = \frac{300}{200+1} = \underline{\underline{1.5}} \text{ mA}$$

$$I_{os} = I_{B\max} - I_{B\min} = \underline{\underline{2.2}} \text{ mA}$$

7.70

$$I_{E1} = \frac{2}{3} I \text{ and } I_{E2} = \frac{1}{3} I$$

(Q<sub>1</sub> twice the area of Q<sub>2</sub>)

$$\Delta V_c = V_{c2} - V_{c1} \simeq \frac{1}{3} I R_c$$

Nominally,

$$A_d = \frac{V_{c2}}{r_e} = \frac{I R_c}{2 V_T}$$

$$V_{os} = \frac{\Delta V_c}{A_d} = \frac{2}{3} V_T = \underline{\underline{16.7}} \text{ mV}$$

Thus, small-signal analysis predicts that a 16.7 mV DC

voltage applied as  $V_{B2} - V_{B1} = 16.7\text{V}$  would restore the current balance in the pair and reduce  $\Delta V_c$  to zero.

Using large-signal analysis:

$$i_{E1} = I_{S1} \cdot e^{\frac{V_{B1}-V_E}{V_T}}$$

$$i_{E2} = I_{S2} \cdot e^{\frac{V_{B2}-V_E}{V_T}}$$

Thus,

$$\frac{i_{E1}}{i_{E2}} = \frac{I_{S1}}{I_{S2}} \cdot e^{\frac{V_{B1}-V_{B2}}{V_T}}$$

To restore balance,  $i_{E1} = i_{E2}$ , thus

$$1 = 2 e^{\frac{V_{B1}-V_{B2}}{V_T}}$$

$$\Rightarrow V_{B1} - V_{B2} = -V_T \ln 2$$

$$V_{B2} - V_{B1} = \underline{\underline{17.3\text{mV}}}$$

Nominally

$$I_B = \frac{I/2}{\beta + 1} \approx \frac{100}{2 \times 100} = \underline{\underline{0.5\text{mA}}}$$

But with the imbalance,

$$I_{B1} \approx \frac{2I/3}{\beta} = \frac{2 \times 100}{300} = \underline{\underline{0.67\text{mA}}}$$

$$I_{B2} = \frac{I/3}{\beta} = \frac{100}{300} = \underline{\underline{0.33\text{mA}}}$$

$$I_B = \frac{I_{B1} + I_{B2}}{2} = \underline{\underline{0.5\text{mA}}}$$

$$I_{OS} = |I_{B1} - I_{B2}| = \underline{\underline{0.34\text{mA}}}$$

7.71

$$R_C = 20\text{K}\Omega ; A_d = 90\text{V/V}$$

$$V_{OS} = \pm 3\text{mV}$$

Worst case  $|V_{OS}|$  is 3mV


$$|V_{OS}| = V_T \left( \frac{\Delta R_C}{R_C} \right) \quad |V_{OS}| = 3\text{mV}$$

$$\Rightarrow \frac{3\text{mV} \times 20\text{K}}{25\text{mV}} = 2.4\text{K}, \Delta R_C = 2.4\text{K}\Omega$$

This is the maximum mismatch that occurs in  $R_C$ .

Thus, if the lowest collector resistor is adjusted from  $R_{Cmin} + \Delta R$  with  $\Delta R$  varying between zero and  $2.4\text{K}\Omega$ , then the offset would be eliminated!

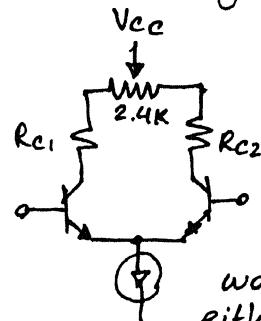This can be achieved with the following circuit:



When  $R_{C1} \times R_{C2}$  are equal the potentiometer is tuned to the middle point. In the worst case, when either  $R_C$  is higher

by  $2.4\text{K}\Omega$ , the potentiometer is adjusted to one extreme such as to increase the lowest  $R_C$  by  $2.4\text{K}\Omega$ . In all other cases, when  $\Delta R_C$  is distributed between  $R_{C1}$  and  $R_{C2}$  the potentiometer is adjusted

7.72

For each transistor  $I_D = I/2$ .

$$\text{for } r_{o2} = r_{o4} = r_o$$

$$A_d = \frac{1}{2} g_m r_o$$

$$\text{but } g_m = \frac{2I_D}{V_{ov}} \text{ and } r_o = \frac{V_A}{I_D}$$

$$\Rightarrow A_d = \frac{1}{2} \left( \frac{2I_D}{V_{ov}} \right) \frac{V_A}{I_D} = \frac{V_A}{V_{ov}}$$

$$\rightarrow 80 \text{ V/V} = 20 \text{ V/V}_{ov}$$

$$\rightarrow V_{ov} = 20/80 = 0.25 \text{ V}$$

Finally,

$$\begin{aligned} I &= 2I_D = K_w \frac{V_{ov}^2}{L} \\ &= 3.2 \frac{\mu\text{A}}{\text{V}^2} (0.25 \text{ V})^2 = \underline{\underline{0.2 \mu\text{A}}} \end{aligned}$$

$$= \frac{200 \mu\text{A}}{2} = 100 \mu\text{A}$$

$$I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) V_{ov}^2$$

so,

$$\left( \frac{W}{L} \right)_{1-2} = \frac{2I_D}{\mu_n C_{ox} V_{ov}^2} = \frac{2(100 \mu\text{A})}{400 \mu\text{A/V} (0.2 \text{ V})^2} = 12.5$$

For  $Q_3$  and  $Q_4$ ,

$$\left( \frac{W}{L} \right)_{3-4} = \frac{2I_D}{\mu_p C_{ox} V_{ov}^2} = \frac{2(100 \mu\text{A})}{100 \mu\text{A/V}^2 (0.2 \text{ V})^2} = 50$$

(b)

$$A_d = \frac{V_o}{V_{id}} = g_m (r_{o2} \parallel r_{o4})$$

$$\text{Since } r_{o2} = r_{o4} = r_o, A_d = \frac{1}{2} g_m r_o$$

$$\begin{aligned} g_{m1} &= g_{m2} = g_{m3} = g_{m4} = g_m = \frac{I_D}{V_{ov}/2} \\ &= \frac{100 \mu\text{A}}{0.2 \text{ V}/2} = 1 \text{ mA/V} \end{aligned}$$

The value of  $r_o$  needed is

$$r_o = \frac{2A_d}{g_m} = \frac{(2)(50 \text{ V/V})}{1 \text{ mA/V}} = 100 \text{ k}\Omega$$

$$\text{Since } r_o = \frac{|V_A'|}{I_D} \cdot L,$$

$$L = \frac{r_o I_D}{|V_A'|} = \frac{100 \text{ k}(0.1 \text{ mA})}{20 \text{ V}/\mu\text{m}} = 0.5 \text{ }\mu\text{m}$$

(c) If  $V_{ov} = 0$ , the maximum  $V_o$  is  $V_{DD} - V_{ov} = 1 - 0.2 = +0.8 \text{ V}$  with a single-NMOS current transistor, the lowest  $V_o$  should go is  $V_{SS} + 2V_{ov} = -1 + 2(0.2 \text{ V}) = -0.6 \text{ V}$  so, the range of  $V_o$  is  $-0.6 \text{ V}$  to  $+0.8 \text{ V}$

(d)  $Q_5$  delivers  $I = 200 \mu\text{A}$ , and  $L = 0.5 \mu\text{m}$ ,  $V_{ov} = 0.2 \text{ V}$ . So,

$$r_{os} = \frac{|V_A'|}{I} = \frac{(20 \text{ V}/\mu\text{m})(0.5 \mu\text{m})}{0.2 \text{ mA}} = 50 \text{ k}\Omega$$

$$r_{oi} = r_{os} = r_o = 100 \text{ k}\Omega$$


$$A_{cm} = \frac{v_o}{v_{icm}} \approx -\frac{r_{os}}{2R_{ss}} \cdot \frac{1}{1 + g_{m3} r_{os}}$$

$$A_{cm} = -\frac{100 \text{ k}}{2(50 \text{ k})} \cdot \frac{1}{1 + (1 \text{ mA/V})(100 \text{ k})} = -0.01$$

$$CMRR(\text{dB}) = 20 \log_{10} \frac{|A_d|}{|A_{cm}|}$$

$$= 20 \log_{10} \left( \frac{50}{0.01} \right) = 74 \text{ dB}$$

7.73

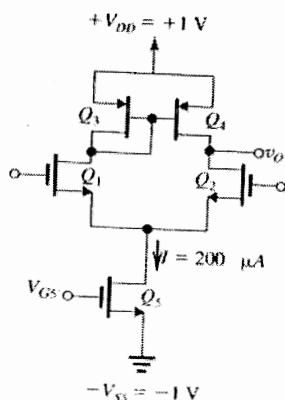

$$(a) I_{D5} = I = 200 \mu\text{A}$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = \frac{I}{2}$$

7.74

$$\text{CMRR} = (g_m r_o)(g_m R_{in})$$

(a) For a simple current mirror

$$R_{ss} = r_{os} \Rightarrow (\text{for } I_D = 1/2)$$

$$\text{CMRR} = (g_m r_o)(g_m r_{in})$$

$$= \left( \frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} \right) \cdot \left( \frac{2I_D}{V_{ov}} \cdot \frac{V_A}{2I_D} \right)$$

$$= 2 \cdot \frac{V_A}{V_{ov}} \cdot \frac{V_A}{V_{ov}}$$

$$= 2 \left( \frac{V_A}{V_{ov}} \right)^2 \quad \text{Q.E.D.}$$

(b) for the modified Wilson current source of

$$RSS = g_m r_o \cdot r_{os}$$

$$\Rightarrow \text{CMRR} = (g_m r_o)(g_m \cdot g_m r_o \cdot r_{os})$$

For  $Q_{5,6,7,8}$ :

$$V_{ovs} = \sqrt{\frac{2I}{k' W/L}}$$

while for  $Q_{1,2,3,4}$ :

$$V_{ov} = \sqrt{\frac{I}{k' W/L}}$$

$$\Rightarrow V_{ovs} = \sqrt{2} V_{ov}$$

Thus, (for  $I = 2I_D$ )

$$\begin{aligned} \text{CMRR} &= \frac{I}{V_{ov}} \cdot \frac{V_A}{(I/2)} \cdot \frac{I}{V_{ov}} \cdot \frac{2I}{\sqrt{2}V_{ov}} \cdot \frac{V_A}{I} \cdot \frac{V_A}{I} \\ &= \frac{4}{\sqrt{2}} \frac{V_A^3}{V_{ov}^3} = 2 \cdot \sqrt{2} \frac{V_A^3}{V_{ov}^3} \end{aligned}$$

For  $k' W/L = 10 \text{ mA/V}^2$

$$I = 1 \text{ mA}$$

$$|V_A| = 10 \text{ V}$$

$$V_{ov} = \sqrt{\frac{1 \text{ mA}}{10 \text{ mA/V}^2}} = 0.316 \text{ V}$$

$\Rightarrow$  For the simple current mirror case:

$$\text{CMRR} = 2 \left( \frac{10}{0.316} \right)^2 = 2000$$


$$\rightarrow 66 \text{ dB}$$

For the Wilson source:

$$\text{CMRR} = 2\sqrt{2} \frac{(10)^3}{(0.316)^3} = 89442$$

$$\rightarrow 99 \text{ dB}$$

7.75

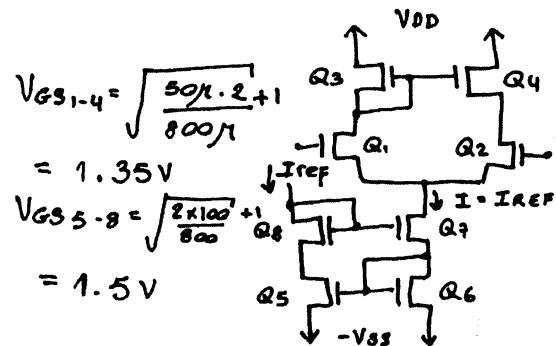


$$\text{For } V_{DS} = V_{GS}$$

$$-V_{SS} + 2V_{GS5-8} + 2V_{GS1-4} = V_{DD}$$

Thus,

$$\begin{aligned} V_{DD} + V_{SS} &= 2(1.5) + 2(1.35) \\ &= \underline{\underline{5.7 \text{ V}}} \end{aligned}$$

7.76

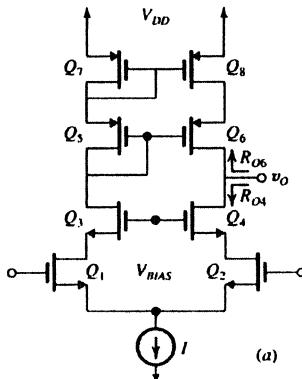

$$(b) R_{O4} = (g_m r_{o4})r_{o2}$$

$$= g_m r_o^2$$

$$R_{O6} = (g_m r_{o6})r_{o8}$$

$$= g_m r_o^2$$

$$A_d = g_m (R_{O4} \parallel R_{O6})$$

$$= g_m \cdot \frac{1}{2} g_m^2 r_o^2$$

$$g_m = \frac{2I_D}{V_{ov}} \quad r_o = \frac{V_A}{I_D}$$

$$\text{thus, } g_m r_o = 2V_A / V_{ov} \\ \Rightarrow A_d = 2(V_A / V_{ov})^2$$

Q.E.D.  
For  $V_{ov} = 0.25 \text{ V}$  &  $V_A = 20 \text{ V}$   
 $A_d = 2(20 / 0.25)^2 = 12800 \text{ V/V}$

7.77

$$i_1 = \frac{V_o}{r_o} = \frac{\frac{1}{2}(g_m r_o) v_{id}}{r_o} = \frac{1}{2} g_m v_{id}$$

$$i_2 = g_{m4} v_{g4} = \frac{g_m v_{id}}{4}$$

$$i_3 = i_1 - i_2 = \frac{g_m v_{id}}{2} - g_m \frac{v_{id}}{4} = \frac{g_m v_{id}}{4}$$

$$i_4 = -g_{m2} v_{g2} = -g_m \left[ -\frac{v_{id}}{2} - \frac{v_{id}}{4} \right] \\ = \frac{3}{4} g_m v_{id}$$

$$i_5 = i_4 = \frac{3}{4} g_m v_{id}$$

$$i_6 = i_4 - i_3 = \frac{3}{4} g_m v_{id} - \frac{1}{4} g_m v_{id} = \frac{1}{2} g_m v_{id}$$

However, if we use KVL,

$$i_6 = \frac{v_o - v_s}{r_o} = \frac{\frac{1}{2} g_m r_o v_{id} - \frac{V_{id}}{4}}{r_o} \\ = \frac{1}{2} g_m V_{id} - \frac{V_{id}}{4 r_o} \text{ inconsistent}$$

$$i_7 = i_5 - i_6 = \frac{3}{4} g_m V_{id} - \frac{g_m V_{id}}{2} = \frac{g_m V_{id}}{4}$$

(which is the same as  $i_3$ )

$$i_8 = g_m v_{g31} = g_m \left( \frac{V_{id}}{2} - \frac{V_{id}}{4} \right) = \frac{1}{4} g_m v_{id}$$

$$i_9 = i_8 = \frac{1}{4} g_m V_{id}$$

$$i_{10} = i_8 - i_7 = \frac{g_m V_{id}}{4} - \frac{g_m V_{id}}{4} = 0$$

$$i_{11} + i_{10} = i_9 \text{ or}$$

$$i_{11} = i_9 - i_{10} = i_9 = \frac{g_m V_{id}}{4}$$

(which is the same as  $i_7$ )

$$i_{12} = g_m v_{g33} = \frac{1}{4} g_m V_{id}$$

$$i_{13} = i_{11} - i_{12} = \frac{1}{4} g_m V_{id} - \frac{1}{4} g_m V_{id} = 0$$

Note, through, that this is inconsistent with KVL.

If  $i_{13} = 0$ ,  $V_{D3} = 0$ , but  $V_{D3} = V_{G3} = -V_{id}/4$ .

If  $i_{10} = 0$ ,  $V_{D1} = \frac{V_{id}}{4}$ , but this conflicts with  $V_{D3}$

being  $-\frac{V_{id}}{4}$ .

It appears that the approximations for  $V_{gs}$  and  $v_s$  prevent a clean solution. If these were more exact, all current and voltage relationships should be consistent.

7.78

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = \frac{I}{2} = \frac{100 \mu\text{A}}{2} = 50 \mu\text{A}$$

$$g_{m1} = g_{m2} = \frac{I_D}{V_{ov}/2} = \frac{50 \mu\text{A}}{0.2 \text{ V}/2} = 0.5 \text{ mA/V}$$

$$G_m = g_{m1} = 0.5 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \frac{V_{Ae}}{I_D} = \frac{20 \text{ V}}{0.05 \text{ mA}} = 400 \text{ k}\Omega$$

$$r_{o3} = r_{o4} = \frac{|V_{Ap}|}{I_D} = \frac{12 \text{ V}}{0.05 \text{ mA}} = 240 \text{ k}\Omega$$

$$R_o = r_{o2} \parallel r_{o4} = 400 \text{ k} \parallel 240 \text{ k} = 150 \text{ k}\Omega$$

$$A_d = G_m R_o = (0.5 \text{ mA/V})(150 \text{ k}) = 75 \text{ V/V}$$

Gain will be reduced by a factor of 2 if

$$R_L = R_o = 150 \text{ k}\Omega$$

7.79

$$R_{id} = (\beta + 1) 2f_e ; f_e = \frac{25 \mu\text{V}}{50 \mu\text{A}}$$

$$\rightarrow R_{id} = 101 \times 1000 = 101 \text{ k}\Omega$$

$$R_o = f_{o4} \parallel f_{o2} = \frac{f_o}{2} ; f_o = \frac{V_A}{I_C}$$

$$\rightarrow f_o = \frac{160 \text{ V}}{50 \mu\text{A}} = 3.2 \text{ M}\Omega$$

$$\text{Thus, } R_o = \underline{1.6 \text{ M}\Omega}$$

$$G_m = g_{m1} = g_{m2} = \frac{50 \mu\text{A}}{25 \mu\text{V}} = \underline{2 \text{ mA/V}}$$

$$A_d = G_m R_o = 2 \times 1600 = \underline{3200} \text{ V/V}$$

With a subsequent stage having a  $100\text{K}\Omega$  input resistance,


$$A_d = G_m (R_{in} \parallel 100\text{K}\Omega) \\ = \underline{188.2} \text{ V/V}$$

$$U_{ICM\max} = U_{C1} + 0.4V \\ = 5 - 0.7 + 0.4 = \underline{4.7V}$$

$$U_{ICM\min} = V_{BS} - 0.4 + 0.7 \\ = -5 - 0.4 + 0.7 \\ = -4V$$

Thus, the input common-mode range is  $-4\text{V}$  to  $+4.7\text{V}$   
(where we have assumed that a transistor remains active)

7.80

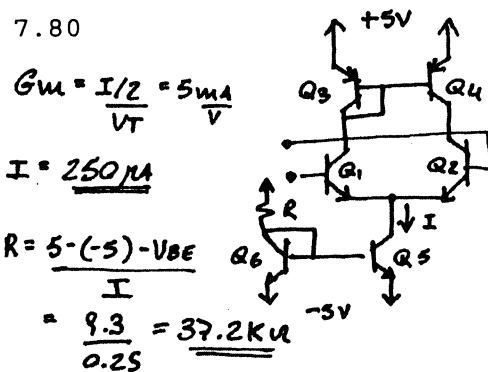

$$G_m = \frac{I}{V_T} = 5 \text{ mA/V}$$

$$I = \underline{250 \mu A}$$

$$R = \frac{5 - (-5) - V_{BE}}{I} \\ = \frac{9.3}{0.25} = \underline{37.2 \text{ K}\Omega}$$

$$R_{id} = (\beta + 1) 2r_e \text{ where,}$$

$$r_e = \frac{V_T}{I/2} = \frac{25 \text{ mV}}{0.125 \text{ mA}} = 200 \text{ }\mu\text{V}$$

$$\rightarrow R_{id} = 151 \times 2 \times 0.2 = \underline{60.4 \text{ K}\Omega}$$

$$r_o = \frac{V_A}{I_c} = \frac{100}{0.125} = 800 \text{ K}\Omega$$

$$R_o = \frac{r_o}{2} = \underline{400 \text{ K}\Omega}$$

$$A_d = g_m R_o = 5 \times 400 = \underline{2000} \text{ V/V}$$

$$I_B = \frac{I/2}{\beta + 1} = \frac{125}{151} = \underline{0.83 \mu A}$$

7.81

$$R_{id} = (\beta + 1) 2(r_e + R_E)$$

$$G_m \text{ is still equal to: } g_m = 5 \text{ mA/V}$$

$$\rightarrow I = \underline{250 \mu A}$$

(from Problem 7.68 above)

$$\text{and } r_e = \frac{V_T}{I/2} = 200 \text{ }\mu\text{V}, r_o = 800 \text{ K}\Omega$$



If  $R_{id} = 100 \text{ K}\Omega \Rightarrow$

$$100 \text{ K} = 151 \times 2 \times (200 + R_E)$$

$$\rightarrow R_E = 131 \text{ }\mu\text{V}$$

To obtain  $A_d$ :

$$A_d = G_m \cdot R_o \quad (\text{Eqn. 7.165})$$

As in the derivation of  $R_{o2}$  in Eqn. (7.162),  $R_{o2}$  can be found using Eqn. (6.159), but this time noting that  $r_e$  at the emitter of  $Q_2$  is:

$$r_{e1} + 2R_E$$

Thus,

$$R_{O2} = r_{o2} \left[ 1 + g_m ((r_{e1} + 2R_E) \parallel r_{T2}) \right]$$

$$R_{O2} = 800K \left[ 1 + 5m \left( (200 + 2 \times 131) \parallel 30.2K \right) \right] \quad (\beta+1)r_{o2}$$

$$R_{O2} = 2620Ku$$

$$R_O = R_{O2} \parallel r_{o4}$$

$$= (2620 \parallel 800)K = 613Ku$$

$$\Rightarrow A_d = 5m \times 613K = \underline{\underline{3065}} V/V$$

7.82

$$G_m = g_m = \frac{I/2}{V_T} = 0.5m/2$$

$$g_m = \underline{\underline{10mA/V}}$$

$$R_O = r_{o2} \parallel r_{o4} = \frac{V_A}{I_{C2}} \parallel \frac{V_A}{I_{C4}} = \frac{1}{2} \frac{V_A}{I/2} \\ = \frac{120}{0.5m} = \underline{\underline{240Ku}}$$

$$A_d = G_m R_O = 10 \times 240 = \underline{\underline{2400V/V}}$$

$$R_{id} = 2\pi \approx 2 \frac{V_T}{I/2} \beta = \frac{25m \times 150}{0.5m}$$

$$R_{id} = \underline{\underline{7.5Ku}}$$

For a simple current mirror

the output resistance (thus REE) is  $r_o$

$$\Rightarrow REE = \frac{V_A}{I} = \frac{120}{0.5m} = \underline{\underline{240Ku}}$$

$$A_{cm} = \frac{-r_{o4}}{\beta_3 R_{EE}} = \frac{-(2 \times 240K)}{150 \times 240K}$$

$$= -13.3 mV/V$$

$$\text{and, CMRR} = \frac{2400}{-13.3m} = 180,451$$

$$\text{i.e. } \underline{\underline{105 dB}}$$

$$\frac{U_L}{U_S} = \frac{R_{id}}{R_{id} + R_S} = \frac{7.5K}{7.5K + 10K} = 0.43V/V$$

$\Rightarrow$  Overall gain A:

$$A = \frac{U_L}{U_S} \frac{U_o}{U_L} = 0.43 \times 2400 \\ = \underline{\underline{1032 V/V}}$$

7.83

(a) If  $R_{o1}$  and  $R_{o2}$  can be ignored,

$$i_i = G_{mem} V_{icm}$$

$$v_o \approx [A_m i_i - G_{mem} V_{icm}] R_{om}$$

substituting in for  $i_i$ ,

$$v_o = [A_m G_{mem} V_{icm} - G_{mem} V_{icm}] R_{om}$$

$$A_{cm} = \frac{v_o}{V_{icm}} = G_{mem} R_{om} (A_m - 1)$$

(b),  $i_i = i_{o3} + A_m i_i$

$$A_m = \frac{i_i - i_{o3}}{i_i} = 1 - \frac{i_{o3}}{i_i} = 1 - \frac{V_{sg3}}{r_{o3} i_i}$$

$g_m + V_{sg3} = A_m i_i$  so,

$$A_m = 1 - \frac{A_m i_i}{g_m r_{o3} i_i} \text{ since } g_{m4} = g_{m3},$$

$$A_m = \frac{1}{1 + \frac{1}{g_m r_{o3}}}$$

Continuing, we can substitute this into the equation of part (a):

$$A_{cm} = G_{mem} R_{om} \left( \frac{1}{1 + \frac{1}{g_m r_{o3}}} - 1 \right)$$


Since  $V_{icm}G_{mem} = \frac{V_{icm}}{2R_{ss}}$ ,  $G_{mem} = \frac{1}{2R_{ss}}$   
substituting,

$$A_{cm} = \left( \frac{R_{om}}{2R_{ss}} \right) \left[ \frac{1 - \left( 1 + \frac{1}{g_m r_{o3}} \right)}{1 + \frac{1}{g_m r_{o3}}} \right]$$

since  $R_{om} = r_{o4}$ ,

$$A_{cm} = \frac{-r_{o4}}{2R_{ss}} \left( \frac{1}{g_m r_{o3} + 1} \right)$$

(c)

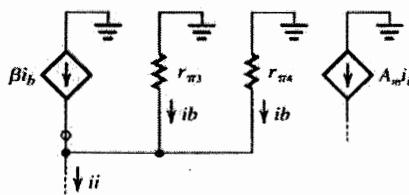

$$i_i = \beta i_b + 2i_b \Rightarrow i_b = \frac{i_i}{\beta + 2}$$

$$A_m i_i = i_b \beta$$

$$A_m i_i = \left( \frac{i_i}{\beta + 2} \right) \beta$$

$$A_m = \left( \frac{\beta}{\beta + 2} \right) = \frac{1}{1 + 2/\beta}$$

Now, substituting into the resulting equation of part (a),

$$A_{cm} = G_{mem} R_{om} (A_m - 1)$$

$$A_{cm} = G_{mem} r_{o4} \left( \frac{\beta}{\beta + 2} - 1 \right) \text{ and since}$$

$$G_{mem} = \frac{1}{2R_{ss}},$$

$$A_{cm} = \frac{r_{o4}}{2R_{ss}} \cdot \left( \frac{\beta - \beta - 2}{\beta + 2} \right) = \frac{-r_{o4}}{2R_{ss}} \cdot \left( \frac{2}{\beta + 2} \right)$$

since  $\beta \gg 2$ ,

$$A_m \approx \frac{-r_{o4}}{\beta_p R_{ss}}$$

### 7.84

for a wilson current mirror,

$$\frac{I_O}{I_{REF}} = \frac{1}{1 + \frac{2}{\beta(\beta + 2)}}$$

As an active load, this means that one collector current will be  $\frac{\alpha I}{2}$ , while the other is

$$\frac{\alpha I}{2} \left( 1 + \frac{2}{\beta(\beta + 2)} \right)$$

$$|\Delta i| = \frac{\alpha I}{2} \left( 1 + \frac{2}{\beta(\beta + 2)} - 1 \right) = \alpha I \left[ \frac{1}{\beta(\beta + 2)} \right]$$


$$G_m = g_m = \frac{2}{V_T} = \frac{\alpha I}{2V_T}$$

$$|V_{os}| = \frac{\Delta i}{G_m} = \frac{\alpha I}{\beta(\beta + 2)} = \frac{2V_T}{\beta(\beta + 2)}$$

For  $\beta_p = 50$ ,

$$|V_{os}| = \frac{2(25 \text{ mV})}{50(50 + 2)} = 19.2 \mu\text{V}$$

### 7.85

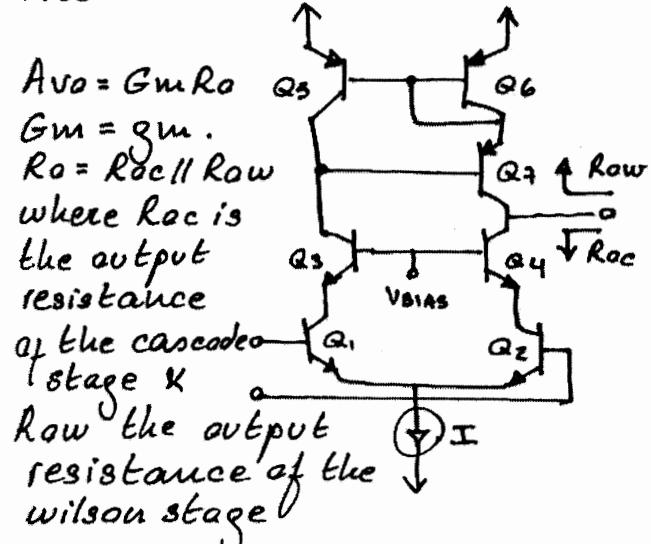

$$R_{OC} = \beta r_O \quad \& \quad R_{OW} = \frac{\beta r_O}{2}$$

$$\Rightarrow R_O = \frac{\beta r_O}{Z} \parallel \frac{\beta r_O}{Z} = \frac{\beta r_O \cdot \beta r_O}{Z^2} = \frac{\beta r_O (1 + \frac{1}{2})}{Z^2} = \frac{\beta r_O}{2 \times \frac{3}{2}} = \frac{\beta r_O}{3}$$

$$\Rightarrow A_{VO} = G_m R_O = g_m \frac{\beta r_O}{3} \quad Q.E.D.$$

For:  $I = 0.4 \text{ mA}$ ,  $\beta = 100$ ,  $V_A = 120 \text{ V}$

$$A_{VO} = \frac{I/2}{V_T} \cdot \frac{\beta}{3} \cdot \frac{V_A}{I/2} = \frac{\beta}{3} \frac{V_A}{V_T}$$

$$= \frac{100}{3} \times \frac{120 \text{ V}}{25 \text{ mV}} = \underline{\underline{160000}}$$

i.e. 104 dB

7.86

To obtain maximum positive swing  $V_{bias}$  must be as low as possible.

To keep the top current sources out of saturation:

$$V_{CC} - 0.2 - 0.7 = V_{bias \max}$$

$$V_{bias \max} = 4.1 \text{ V}$$

$$\text{And: } V_O - V_{bias \min} = +0.4 \text{ V}$$

$$\text{Since } V_O \sim 0 \Rightarrow V_{bias \min} = -0.4 \text{ V}$$

Range of  $V_{bias}$  is:

$$(-0.4 < V_{bias} \leq 4.1) \text{ V}$$

For:  $I = 0.4 \text{ mA}$ ,  $\beta_p = 50$ ,  $\beta_n = 150$  &

$$V_A = 120$$

$$G_m = g_{m1} = \frac{0.2 \text{ mA}}{25 \text{ mV}} = 8 \frac{\text{mA}}{\text{V}}$$

For the folded cascode:  $R_{O4} = \beta_4 r_{O4}$

For the Wilson mirror:  $R_{O5} = \beta_5 \frac{r_{O5}}{2}$

$$\Rightarrow R_O = [\beta_4 \cdot r_{O4} \parallel \beta_5 \cdot \frac{r_{O5}}{2}]$$

$$r_{O4} = r_{O5} = 120/0.2 \text{ mA} = 600 \text{ k}\Omega$$

$$\Rightarrow R_O = [50 \times 600 \text{ k} \parallel 150 \times \frac{600 \text{ k}}{2}]$$

$$= [30 \text{ M} \parallel 45 \text{ M}]$$

$$= 18 \text{ M}\Omega$$


$$A_d = G_m R_O = 8 \frac{\text{mA}}{\text{V}} \times 18 \text{ M}\Omega = 144000$$

7.87

$$Kp'W/L = 6.4 \text{ mA/V}^2$$

$$|V_{AP}| = 10 \text{ V}$$

$$V_{ANPN} = 120 \text{ V}$$

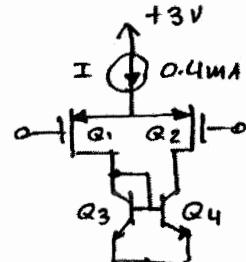

$$R_O = r_{O2} \parallel r_{O4} = \frac{V_{AP}}{I/2} \parallel \frac{120}{I/2} = \frac{V_{AP}}{I/2} = \frac{10}{0.4} = 25 \text{ k}\Omega$$

$$R_O = (10/0.2 \text{ mA}) \parallel (120/0.2 \text{ mA}) = \underline{\underline{46 \text{ k}\Omega}}$$

$$G_m = g_{m1} = \sqrt{I \times Kp'W/L}$$

$$= \sqrt{0.4 \text{ mA} \times 6.4 \text{ mA/V}^2}$$

$$\Rightarrow G_m = \frac{1.6 \text{ mA}}{\text{V}}$$

$$A_d = G_m \times R_O = \frac{1.6 \text{ mA}}{\text{V}} \times 46 \text{ k}\Omega$$

$$\Rightarrow A_d = \underline{\underline{73.6 \text{ V/V}}}$$

7.88

$$I_{D5} = I_{D8} = I_{D1} = I_{D6} = I = I_{REF} = 225 \mu A$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = \frac{I}{2} = \frac{225 \mu A}{2}$$

$$= 112.5 \mu A$$

From Eq. (8.180), systemic balance will occur in this circuit when

$$\left(\frac{W}{L}\right)_6 = 2 \left(\frac{W}{L}\right)_7$$

$$\left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_5$$

$$\left(\frac{W}{L}\right)_6 = 2 \left(\frac{W}{L}\right)_7 \cdot \left(\frac{W}{L}\right)_4 = (2) \frac{\left(\frac{60}{0.5}\right)}{\left(\frac{60}{0.5}\right)} \cdot \frac{\left(\frac{10}{0.5}\right)}{\left(\frac{10}{0.5}\right)}$$

$$= \frac{20}{0.5}$$

$$\text{so, } W_6 = 20$$

$$\text{To find } |V_{ov}|, \text{ we use } I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) V_{ov}^2$$

$$|V_{ov}|_{1,2} = \sqrt{\frac{2(I_{D1})}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{1,2}}} = \sqrt{\frac{225 \mu A}{60 \mu A/V^2 \left(\frac{30}{0.5}\right)}} = 0.25 V$$

$$|V_{ov}|_{3,4} = \sqrt{\frac{2I_{D3}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{3,4}}} = \sqrt{\frac{2(112.5 \mu A)}{180 \mu A/V^2 \left(\frac{10}{0.5}\right)}} = 0.25 V$$

$$|V_{ov}|_{5,7,8} = \sqrt{\frac{2I}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{5,7,8}}} = \sqrt{\frac{2(225 \mu A)}{60 \mu A/V^2 \left(\frac{60}{0.5}\right)}} = 0.25 V$$

$$|V_{GS}| = |V_i| + |V_{ov}|, \text{ so all are}$$

$$|V_{GS}| = 0.75 + 0.25 = 1.0 V$$

$$g_{m1..4} = \frac{I/2}{1 V_{ov} 1/2} = \frac{225 \mu A}{0.25 V} = 0.9 mA/V$$

$$g_{m5..8} = \frac{I}{1 V_{ov} 1/V} = \frac{2(225 \mu A)}{0.25 V} = 1.8 mA/V$$

$$r_{o1..4} = \frac{|V_A|}{I/2} = \frac{9 V}{0.225 mA} = 80 k\Omega$$

$$r_{o5..8} = \frac{|V_A|}{I/2} = \frac{9 V}{0.1125 mA} = 40 k\Omega$$

$$A_1 = -g_{m1}(r_{o2} \parallel r_{o4}) \\ = -(0.9 mA/V)(80 k \parallel 80 k) = -36 V/V$$

$$A_2 = -g_{m6}(r_{o5} \parallel r_{o7}) \\ = -(1.8 mA/V)(40 k \parallel 40 k) = -36 V/V$$

$$A_O = A_1 \times A_2 = (-36)(-36) = 1296 V/V \\ = 20 \log_{10}(1296) = 62.25 dB$$

The input common-mode range is determined as follows:

The lower limit is when the input is such that  $Q_1$  and  $Q_2$  leave the saturation region:

$$V_{D1} = -V_{SS} + V_{GS1} = -1.5 + 1 = 0.5 V$$

with  $|V_{DS}| = |V_{ov}|$ , this would be when

$$V_{S1} = -0.5 + 0.25 = -0.25 V$$

$$V_{in\min} = V_{S1} - V_{SG} = -0.25 - 1 = -1.25 V$$

The upper limit is when  $Q_3$  leaves saturation:

$$V_{DS_{max}} = V_{DD} - |V_{ov}| = 1.5 - 0.25 = 1.25 V$$

$$V_{in\max} = V_{S1\max} - V_{SG} = 1.25 - 1.0 = +0.25 V$$

so, range is (-1.25 V to +0.25 V)

For the output range,  $V_{Omax}$  is

$$V_{Omax} = V_{DD} - |V_{ov}| = 1.5 - 0.25 = 1.25 V$$

$$V_{Omin} = -V_{SS} + |V_{ov}| = -1.5 + 0.25$$

$$= -1.25 V$$

so the output range is (-1.25 V to +1.25 V.)

	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$	$Q_8$
$I_D(\mu A)$	112.5	112.5	112.5	112.5	225	225	225	225
$ V_{ov} (V)$	0.25	0.25	0.25	0.25	0.25	0.25	0.25	0.25
$ V_{GS} (V)$	1.0	1.0	1.0	1.0	1.0	1.0	1.0	1.0
$g_m \left(\frac{mA}{V}\right)$	0.9	0.9	0.9	0.9	1.8	1.8	1.8	1.8
$r_o(k\Omega)$	80	80	80	80	40	40	40	40

7.89

$$I_{D6} = I_{D1-4} = I_{REF} = 200 \mu\text{A}$$

$$I_{DS} = 2I_{D1} = 400 \mu\text{A}$$

No requirements are given for  $Q_6$  and  $Q_7$ , so choose

$$\star I_{D6} = I_{D7} = 2I_{REF} = 400 \mu\text{A}$$

	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$	$Q_8$
$\left(\frac{W}{L}\right)$	25	25	100	100	50	200	50	25

$$I_D = \frac{1}{2}k'(W/L)V_{OV}^2 \text{ so,}$$

$$\left(\frac{W}{L}\right)_{1,2,8} = \frac{2I_{REF}}{k_n(V_{OV})^2} = \frac{2(200 \mu\text{A})}{400 \mu\text{A}/\text{V}^2(0.2 \text{ V})^2} = 25$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{2I_{REF}}{k_p(V_{OV})^2} = \frac{2(200 \mu\text{A})}{400 \mu\text{A}/\text{V}^2(0.2 \text{ V})^2} = 100$$

$$\left(\frac{W}{L}\right)_{5,7} = \frac{2(2I_{REF})}{k_n(V_{OV})^2} = \frac{2(400 \mu\text{A})}{400 \mu\text{A}/\text{V}^2(0.2 \text{ V})^2} = 50$$

$$\left(\frac{W}{L}\right)_C = \frac{4I_{REF}}{k_p(V_{OV})^2} = \frac{4(200 \mu\text{A})}{100 \mu\text{A}/\text{V}^2(0.2 \text{ V})^2} = 200$$

Ideally,  $V_o(dc) = 0$

(b) For the common-mode input range:

The lower limit is when  $Q_5$  is leaving saturation.

$$V_{DS} = -V_{SS} + |V_{OS}| = -1 \text{ V} + 0.2 \text{ V} = -0.8 \text{ V}$$

$$V_{in(min)} = V_{GS1} + V_{DS} = V_{in} + V_{OV} + V_{DS}$$

$$= 0.4 + 0.2 - 0.8 = -0.2 \text{ V}$$

The upper input limit is when  $Q_1$  and  $Q_2$  leave the saturation region:

$$V_{D1} = V_{DD} - V_{SD3} = 1 - (0.4 + 0.2) = 0.4 \text{ V}$$

$$V_{DS1} = |V_{OV}| = 0.2 \text{ V}, \text{ so}$$

$$V_{in(max)} = V_{D1} - V_{OV} + V_{GS1}$$

$$= V_{D1} + V_{in} = 0.4 \text{ V} = 0.8 \text{ V}$$

so, the range of input voltage is

(-0.2 V to +0.8 V)

(c) The maximum output voltage is

$$V_{O_{max}} = V_{DD} - |V_{OV}| = 1 - 0.2 = +0.8 \text{ V}$$

$$V_{O_{min}} = -V_{SS} + |V_{OV}| = -1 + 0.2$$

$$= -0.8 \text{ V}$$

so range is (-0.8 V to +0.8 V)

$$(d) r_{o2} = r_{o4} = \frac{|V_A|}{I_{D2}} = \frac{5 \text{ V}}{0.2 \text{ mA}} = 25 \text{ k}\Omega$$

$$r_{o6} = r_{o7} = \frac{|V_A|}{I_{D6}} = \frac{5 \text{ V}}{0.4 \text{ mA}} = 12.5 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{|I_D|}{V_{OV}/2} = \frac{0.2 \text{ mA}}{0.2 \text{ V}/2} = 2 \text{ mA/V}$$

$$g_{m6} = \frac{|I_D|}{V_{OV}/2} = \frac{0.4 \text{ mA}}{0.2 \text{ V}/2} = 4 \text{ mA/V}$$

$$A_1 = g_{m1}(r_{o2} \parallel r_{o4}) = (2 \text{ mA/V})(25 \text{ k} \parallel 25 \text{ k}) = 25 \text{ V/V}$$

$$A_2 = -g_{m2}(r_{o6} \parallel r_{o7}) = -4 \text{ mA/V}(12.5 \text{ k} \parallel 12.5 \text{ k}) = -25 \text{ V/V}$$

$$A_O = A_1 \cdot A_2 = 25(-25) = -625 \text{ V/V}$$

7.90

$$I = \frac{1}{2}k V_{OV}^2$$

$$(a) V_{OV} = \sqrt{\frac{2I}{k}}$$

If K increases by 4  $\rightarrow V_{OV}$  decreases by 1/2

$$g_m = 2I/V_{OV} = k \cdot V_{OV}$$

$\rightarrow$  if k increases by 4

gm increases by  $\times 2$

$$(b) A_1 = g_m R_{O1}$$

$\rightarrow A_1$  increases  $\times 2$  as does  $A_O$

(c) Offsets due to  $V_i$  mismatch are unaffected.

Others reduced  $\times \frac{1}{2}$  since  $A_O$  increases  $\times 2$

7.91

$$I_{D7} = \frac{W_7}{W_8} I_{REF} = \frac{50}{40} \times 90 \mu\text{A} = 112.5 \mu\text{A}$$

Output offset current  $= I_{D7} - I_{D6}$

$$= 112.5 - 90 = 22.5 \mu\text{A}$$

$$\Rightarrow V_o = 22.5 \mu\text{A} (111 \text{ k} \parallel 88.9 \text{ k})$$

$$r_{o7} = \frac{10}{112.5 \mu\text{A}} = 88.9 \text{ k}\Omega$$

$$\Rightarrow V_o = 22.5 \mu\text{A} (111 \text{ k} \parallel 88.9 \text{ k})$$

$$= 1.11 \text{ V}$$

$$V_{os} = \frac{V_o}{A_o} = \frac{1.11 \text{ V}}{1109} = 1 \text{ mV}$$

7.92

$$\begin{aligned}
 \text{Offset current} &= I_{D2} - I_{D4} \\
 &= I_{D3} - I_{D4} \\
 I_{D3} &= \frac{K}{2} (V_{GS} - V_t)^2 \\
 I_{D4} &= \frac{K}{2} (V_{GS} - (V_t + \Delta V_t))^2 \\
 I_o &= I_{D3} - I_{D4} \\
 &= \frac{K}{2} [(V_{GS} - V_t - V_{GS} + V_t + \Delta V_t) \times \\
 &\quad (V_{GS} - V_t + V_{GS} - V_t - \Delta V_t)] \\
 &= \Delta V_t \cdot \frac{K}{2} (2V_{GS} - 2V_t - \Delta V_t) \\
 &\approx K (V_{GS} - V_t) \cdot \Delta V_t \\
 I_o &= \underline{\underline{g_{m3} \Delta V_t}}
 \end{aligned}$$

$$\begin{aligned}
 \text{Recall } I_o &= G_{m1} \cdot V_{os} \\
 \text{and } G_{m1} &= g_{m1} \\
 \Rightarrow V_{os} &= \underline{\underline{g_{m3}} \cdot \Delta V_t} \quad \text{from } g_{m1}
 \end{aligned}$$

$$\begin{aligned}
 \text{For } \Delta V_t &= 2\text{mV} \\
 V_{os} &= \frac{0.3\text{m}}{0.3\text{m}} \times 2\text{m} = \underline{\underline{2\text{mV}}}
 \end{aligned}$$

7.93

$$(a) \underline{\underline{I_{E1} = I_{E2} = 0.1\text{mA}}} \approx I_{E3}, I_{E4}$$

$$\begin{aligned}
 \underline{\underline{I_{E5} \approx 1\text{mA}}} \quad \text{and since the} \\
 \text{output is held at } 0\text{V} \\
 \underline{\underline{I_{E6} = 2\text{mA}}}
 \end{aligned}$$

$$\begin{aligned}
 (b) \quad &I_{e1} = I_{e2} = \frac{25\text{mV}}{0.1\text{mA}} = 250\text{uA} \\
 &I_{e3} = \frac{25\text{mV}}{1\text{mA}} = 25\text{uA} \\
 &I_{e6} = \frac{25\text{mV}}{2\text{mA}} = 12.5\text{uA}
 \end{aligned}$$

For the active loaded differential pair; Recall from Eqn.  
(7.161)  $G_{m1} = g_{m1}$

$$\begin{aligned}
 &\approx \frac{1}{I_{e1}} = \frac{1}{250} = 4\text{mA/V} \\
 R_{o1} &= (\beta + 1) R_{es} \quad \text{Since all } r_o's = \infty \\
 R_{o1} &= 101 \times 25 = 2525\text{uA} \\
 \Rightarrow A_1 &= G_{m1} R_{o1} = \frac{4\text{mA}}{V} \times 2525\text{uA} \\
 &= 10.1 \text{V/V}
 \end{aligned}$$

For the common-emitter:

$$\begin{aligned}
 A_5 &= -g_{m5} R_{es} \\
 &\approx -\frac{\beta R_L}{R_{es}} = -\frac{100 \times 10\text{K}}{25} \\
 &= -40,000 \text{V/V}
 \end{aligned}$$

For the emitter follower:  
 $A_6 \approx 1$

$$A_{2\text{nd-stage}} = A_5 \cdot A_6 = -40,000 \text{V/V}$$

$$\begin{aligned}
 A &= A_1 \cdot A_{2\text{nd-stage}} = 10.1 \times -40,000 \\
 &= -\underline{\underline{404,000 \text{V/V}}}
 \end{aligned}$$

(c) Since the dominant low-frequency pole is set by  $C_C$  &  
 $f_{\pi 3}$

$$\begin{aligned}
 f_p &= \frac{1}{2\pi \cdot R_{o1} \underbrace{(A_5 + 1) C_C}_{\text{by Miller effect}}} = 100\text{Hz} \\
 \Rightarrow C &\approx 1 / (2\pi \times 2525 \times 40\text{K} \times 100) \\
 &= \underline{\underline{15.76\text{pF}}}
 \end{aligned}$$

7.94

$$I_B = 225 \mu A$$

$$\mu_n C_{ox} = 180 \mu A/V^2$$

$$\mu_p C_{ox} = 60 \mu A/V^2$$

For  $Q_8$  &  $Q_9$ :  $W/L = 60/0.5$

$$\Rightarrow |V_{ov}| = \frac{2I_D}{\sqrt{k_p(W/L)}}$$

$$|V_{ov}|_{h,9} = \frac{2 \times 225 \mu}{\sqrt{60 \mu \times 120}} = 0.25 V$$

$$\text{then } g_m,9 = \frac{2I_D}{|V_{ov}|} = \frac{2 \times 225 \mu}{0.25 V}$$

= 1.8 mA/V

Since  $g_m$  of  $Q_{10}$ ,  $Q_{11}$  &  $Q_{13}$  are identical to  $g_m$  of  $Q_8$  &  $Q_9$  then  $V_{ov,13} = 0.25 V$

Thus for  $Q_{13}$

$$(0.25)^2 = \frac{2 \times 225 \mu}{180 \mu \times (W/L)_{13}}$$

$$\rightarrow (W/L)_{13} = 40 \text{ i.e., } (20/0.5)$$

Since  $Q_{12}$  is 4 times as wide as  $Q_{13}$ , then

$$(W/L)_{12} = \frac{4 \times 20}{0.5} = 80/0.5$$

$$R_B = \frac{2}{\sqrt{2 k_n (W/L)_{12} I_B}} \cdot \left( \sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$= \frac{2}{\sqrt{2 \times 180 \mu \times \frac{80}{0.5} \times 225 \mu}} \cdot \left( \sqrt{\frac{80/0.5}{420/0.5}} - 1 \right)$$

$$\rightarrow R_B = 555.6 \Omega$$

The voltage drop on  $R_B$  is :

$$555.6 \times 225 \mu = 0.125 V$$

To obtain the gate voltages: (assume  $|V_{ov}| = |V_{gp}| = 0.7 V$ )

$$V_{ov,12} = \frac{2 \times 225 \mu}{\sqrt{180 \mu \times \frac{80}{0.5}}} = 0.125 V$$

$$V_{OV12} = V_{GS12} - V_{in}$$

$$\rightarrow V_{GS12} = 0.125 + 0.7 = 0.825 V$$

thus,

$$V_{G12,13} = V_{GS12} + I_B R_B - V_{SS}$$

$$= 0.825 + 0.125 - 1.5$$

$$= -0.55 V$$

$$V_{ov,11} = |V_{ovs}| = 0.25 V$$

$$\Rightarrow V_{GS11} = 0.25 + 0.7 = 0.95 V$$

$$V_{G11} = -0.55 + 0.95$$

$$V_{G11} = V_{G10} = 0.4 V$$

$$V_{GS} = V_{DD} - V_{SG11} = 1.5 + (-0.25 - 0.7)$$

$$= +0.55 V$$

Finally from the results above:


$$(W/L)_{10} = 20/0.5$$

$$(W/L)_{11} = 20/0.5$$

$$(W/L)_{12} = 80/0.5$$

$$(W/L)_{13} = 20/0.5$$

7.95

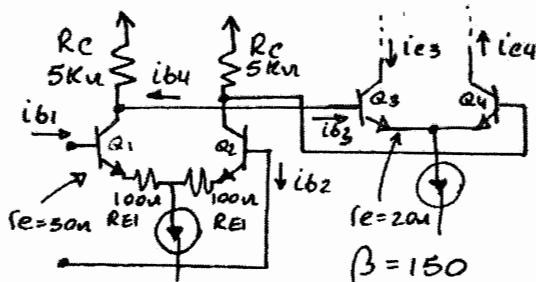

$$A_1 = \frac{2R_C \parallel R_{id2}}{2(R_{EI} + r_{e1})}$$

$$R_{id2} = (\beta + 1)(2r_{e2}) = 6.04 k\Omega$$

$$\Rightarrow A_1 = 12.5 V/V$$

$$A_i = \frac{i_{E4}}{i_{B1}} = \beta_1 \cdot \frac{2R_C}{R_{id2} + 2R_C} \beta_4$$

$$= 1.4 \times 10^4 \text{ A/A}$$

7.96

$$R_O \approx \frac{R_S}{\beta + 1} + r_{es} = R_C$$

Thus  $R_S$  affects  $R_O$ . We want  $R_O \parallel 3 k \Omega = 76$

$$\Rightarrow R_O = 78 \Omega$$

$$\Rightarrow R_S = (78 - r_{es})(\beta + 1)$$

$$= 7.34 k\Omega$$

$$A_3 = \frac{-R_3 \parallel R_{i4}}{r_{e4} + R_4} ; \quad R_{i4} \approx 304 \text{ k}\Omega$$

and  $A_3 = -3.09 \text{ V/V}$

$$\text{and } A = 8513 \cdot \frac{3.09}{6.42} = 4104 \text{ V/V}$$

The gain has been reduced by a factor of 2.07 and can be restored by reducing  $R_4$  by this same factor to increase  $A_3$ . Thus  $R_4 = 1.11 \text{ k}\Omega$   
(Note that this is a first order approximation).

7.97

$$(a) A_3 = \frac{-R_{i4}}{2.325 \text{ k}\Omega} = \frac{-303.5}{2.325}$$

$= -130.5 \text{ V/V}$

$$\text{i.e. } A_3 \text{ is increased by } \frac{130.5}{6.42}$$

$= 20.33$


$$\Rightarrow A = 8513 \times 20.33$$

$$= 173.1 \times 10^3 \text{ V/V}$$

(b) Let the output resistance of the current source

$$\text{be } R \rightarrow \infty \quad R_O = 3 \text{ k} \parallel \left( \frac{R}{\beta + 1} + r_e \right) = 3 \text{ k}\Omega$$

The amplifier can be modelled as shown:

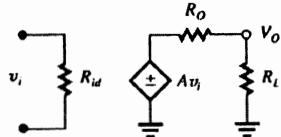

Thus,

$$A_{LOAD} = \frac{A \cdot R_L}{R_L + R_O}$$


$$= 173.1 \times 10^3 \frac{100}{100 + 3000}$$

$$= 5583 \text{ V/V}$$

For the original amplifier:

$$A_{LOAD} = 8513 \times \frac{100}{100 + 152} = 3378 \frac{\text{V}}{\text{V}}$$

7.98

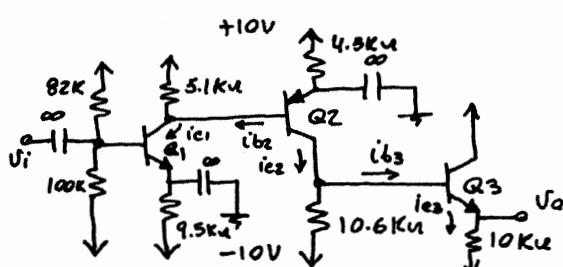

$$(a) I_{E1} = \frac{20\text{V} \times 100\text{k}}{82\text{k} + 100\text{k}} - 0.7$$

$$= \frac{9.5\text{k} + (82\text{k} \parallel 100\text{k})}{\beta + 1}$$

$$\beta = 100 \Rightarrow I_{E1} = 1.03 \text{ mA}$$

$$\alpha = \frac{100}{101} \Rightarrow I_{C1} = \underline{1.02 \text{ mA}}$$

$$V_{C1} \approx 10\text{V} - 1.02 \text{ mA} \times 5.1\text{k}\Omega = 4.8\text{V}$$

$$I_{E2} = \frac{(10 - 0.7 - 4.8)\text{V}}{4.5\text{k}\Omega} = 1 \text{ mA}$$

$$\rightarrow I_{C2} = \underline{0.99 \text{ mA}}$$

$$V_{C2} \approx 0.99 \text{ mA} \times 10.6\text{k} - 10 = 0.5\text{V}$$

$$\Rightarrow U_{Odc} = 0.5 - 0.7 = \underline{-0.2 \text{ V}}$$

$$I_{E3} = \frac{-0.2 - (-10)}{10\text{k}} = 0.98 \text{ mA}$$

$$\rightarrow I_{C3} = \underline{0.97 \text{ mA}}$$

Thus all transistors are operating at  $I_c \approx \underline{1 \text{ mA}}$

$$(b) R_{in} = 82K \parallel 100K \parallel r_{\pi 1}$$

where  $r_{\pi 1} = \frac{B}{g_{m1}} = \frac{100}{40m} = 2.5K\Omega$

$$\Rightarrow R_{in} = (82 \parallel 100 \parallel 2.5)K = \underline{\underline{2.37K\Omega}}$$

$$\Rightarrow f_{p2} = \frac{1}{2\pi \times 852p \times 10.5K} = \underline{\underline{17.8 \text{ KHz}}}$$

$$R_{out} = 10K \parallel \left[ r_{e3} + \frac{10.6K}{\beta+1} \right]$$

$$= 10K \parallel \left[ 25 + \frac{10.6K}{101} \right]$$

$$= \underline{\underline{128\Omega}}$$

7.99

$$(a) I_{D1-5,7} = \frac{I}{2}$$

$$I_{D6,8} = 2\left(\frac{I}{2}\right) = I$$

$$g_m = \frac{|I_D|}{|V_{ov}|} \text{ So that}$$

$$g_{m1-5,7} = \frac{I/2}{|V_{ov}/2|} = \frac{I}{|V_{ov}|}$$

$$g_{m6,8} = \frac{I}{|V_{ov}|} = \frac{2I}{|V_{ov}|}$$

$$r_D = \frac{|V_A|}{|I_D|} \text{ So that}$$

$$r_{D1-5,7} = \frac{2|V_A|}{I}$$

$$r_{D6,8} = \frac{|V_A|}{I}$$

In Summary,

$$(c) \frac{i_{c1}}{V_i} = g_{m1} = 40m\text{A/V}$$

$$\frac{i_{b2}}{i_{c1}} = \frac{5.1K}{5.1K + r_{\pi 2}} = \frac{5.1}{5.1 + 2.5} = 0.671 \text{ A/A}$$

$$\frac{i_{e2}}{i_{b2}} = \beta_2 = 100 \text{ A/A}$$

$$i_{b2}$$

$$\frac{i_{b3}}{i_{c2}} = \frac{10.6K}{10.6K + (\beta+1)(r_{e3} + 10K)} = 0.01036 \text{ A/A}$$

$$\frac{i_{e3}}{i_{b3}} = \beta_3 + 1 = 101$$

$$i_{b3}$$

$$V_o = i_{e3} \times 10K$$

Thus,

$$\frac{V_o}{V_i} = 10 \times 101 \times 0.01036 \times 100 \times 0.671 \times 40 \\ = \underline{\underline{2.81 \times 10^4 \text{ V/V}}}$$

$$(d) f_{p2} = 1 / (2\pi C_2 \cdot R_2)$$

$$\text{where: } R_2 = 5.1K \parallel r_{\pi 2}$$

$$= 5.1K \parallel 2.5K = 1.68K\Omega$$

$$C_2 = C_{\pi 2} + C_{f2}(1 + g_{m2} R_{L2})$$

with:

$$R_{L2} = 10.6K \parallel ((\beta+1)(r_{e3} + 10K)) \\ = 10.6K \parallel 101 \times (25 + 10K) \\ = 10.5K\Omega.$$

$$\Rightarrow C_2 = 10p + 2p(1 + 40m \times 10.5K) \\ = 852 \text{ pF}$$

	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$	$Q_8$
$I_D$	$I/2$	$I/2$	$I/2$	$I/2$	$I/2$	$I$	$I/2$	$I$
$g_m$	$\frac{I}{ V_{ov} }$	$\frac{2I}{ V_{ov} }$	$\frac{I}{ V_{ov} }$	$\frac{2I}{ V_{ov} }$				
$r_D$	$\frac{2 V_A }{I}$	$\frac{ V_A }{I}$	$\frac{2 V_A }{I}$	$\frac{ V_A }{I}$				

(b) To find the differential gain, apply  $-\frac{V_{id}}{2}$  to  $Q_1$

and  $V_{id}/2$  to  $Q_2$

$$V_{x5} = g_{m1} \left( r_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right) V_{id}/2$$

since  $\frac{1}{g_{m3}} \ll r_{o1} \parallel r_{o3}$

$$V_{x5} = g_{m1} \left( \frac{1}{g_{m3}} \right) \cdot \frac{V_{id}}{2}$$

$$i_{d5} = -V_{x5} g_{m5} = -g_{m1} \left( \frac{1}{g_{m3}} \right) (g_{m5}) \frac{V_{id}}{2}$$

$$V_{x8} = V_{x7} = i_{d5} \left( r_{o5} \parallel r_{o7} \parallel \frac{1}{g_{m7}} \right) = i_{d5} \left( \frac{1}{g_{m7}} \right)$$

since  $g_{m8} = g_{m7}$

$$V_{x8} = -g_{m1} \left( \frac{1}{g_{m7}} \right) \frac{V_{id}}{2}$$

since  $g_{m8} = 2 g_{m7}$

$$i_{d8} = +g_{m1} \left( \frac{1}{g_{m7}} \right) (2g_{m7}) \cdot \frac{V_{id}}{2} = +g_{m1} V_{id}$$

with  $+\frac{V_{id}}{2}$  applied to  $Q_2$ ,

$$V_{x4} = -g_{m2} \left( r_{o2} \parallel r_{o4} \parallel \frac{1}{g_{m4}} \right)$$

$$V_{x6} = V_{x4} = -g_{m1} \left( \frac{1}{g_{m4}} \right) \cdot \frac{V_{id}}{2}$$

since  $g_{m6} = g_{m4} \times 2$ ,

$$i_{d6} = -g_{m4}(2) (-g_{m1}) \left( \frac{1}{g_{m4}} \right) \frac{V_{id}}{2}$$

$$i_{dp} = g_{m1} V_{id}$$

$$i_O = g_{m1} V_{id} + g_{m1} V_{id} = 2 g_{m1} V_{id}$$

$$\frac{A_d}{V_{id}} = \frac{i_O R_O}{V_{id}} = 2 g_{m1} (r_{o6} \parallel r_{O8})$$

$$g_{m1} = \frac{I}{|V_{ov}|} \quad r_{o6} = r_{O8} = \frac{|V_A|}{I}$$

$$\frac{A_d}{V_{id}} = 2 \frac{I}{|V_{ov}|} \left( \frac{1}{2} \right) \frac{|V_A|}{I} = \frac{V_A}{V_{ov}}$$

(c) If each input transistor ( $Q_1$  and  $Q_2$ ) is replaced with a current source of  $\frac{V_{icm}}{2R_{ss}}$ ,

From  $Q_2$ , with a transfer ratio of  $\left(1 - \frac{1}{g_m r_{o3}}\right)$ ,

$$i_{D6} = -\frac{V_{icm}}{2R_{ss}} \left(1 - \frac{1}{g_m r_{o3}}\right) (2)$$

From

$$Q_1, i_{D8} = \frac{V_{icm}}{2R_{ss}} \left(1 - \frac{1}{g_m r_{o3}}\right) \left(1 - \frac{1}{g_m r_{o7}}\right) (2)$$

$$i_o = i_{D8} + i_{D6}$$

$$i_o = \frac{V_{icm}}{R_{ss}} \left[ -1 + \frac{1}{g_m r_{o4}} + \left(1 - \frac{1}{g_m r_{o3}}\right) \left(1 - \frac{1}{g_m r_{o7}}\right) \right]$$

Since  $g_m 3 = g_m 4$  and  $r_{o3} = r_{o4}$ ,

$$i_o = \frac{V_{icm}}{R_{ss}} \left[ \left(1 - \frac{1}{g_m r_{o3}}\right) \left(1 - \frac{1}{g_m r_{o7}}\right) \right]$$

$$V_o = i_o (r_{o6} \parallel r_{o8}) \text{ and Since } \frac{1}{g_m r_{o3}} \gg 1$$

$$v_o \approx \frac{-V_{icm}}{R_{ss}} \left( \frac{1}{g_m r_{o7}} \right) (r_{o6} \parallel r_{o8})$$

$$|A_{CM}| = \left| \frac{V_o}{V_{icm}} \right| = \frac{(r_{o6} \parallel r_{o8})}{R_{ss}} = \frac{1}{g_m r_{o7}}$$

(d) If the current source is fabricated as a simple

$$\text{current mirror, } R_{ss} = \frac{V_A}{I}$$

$$r_{o6} = r_{o8} = \frac{V_A}{I} \text{ so, } r_{o6} \parallel r_{o8} = \frac{V_A}{2I}$$

$$g_m 7 = \frac{I}{V_{ov}/2} = \frac{2I}{V_{ov}}$$

$$CMRR = \frac{|A_d|}{|A_{CM}|} = \frac{V_A/V_{ov}}{\frac{r_{o6} \parallel r_{o8}}{R_{ss}} \cdot \frac{1}{g_m r_{o7}}} \\ = \frac{V_A/V_{ov}}{\frac{V_A/2I}{V_A/I} \cdot \frac{1}{2I} \cdot \frac{V_A}{I}} \\ = \frac{V_A/V_{ov}}{\frac{1}{2} \left( \frac{V_{ov}}{V_A} \right)}$$

(e) To find the input common-mode range, consider both upper and lower limits: Lower limit is when the current source begins to leave the saturation region at  $V_{DS} = V_{ov}$

So,

$$V_{I(min)} = V_{GS1} + V_{ov} + V_{SS} = V_t + 2V_{ov} - V_{DD}$$

The maximum limit occurs when  $Q_1$  or  $Q_2$  begins to leave the saturated region: For example, when

$$V_{S1} = V_{DD} - V_{GS1} - V_{ov}$$

$$V_{I(max)} = V_t + V_{ov} + V_{S1}$$

$$V_{I(max)} = V_t + V_{ov} + V_{DD} - V_t + 2V_{ov}$$


$$V_t(max) = V_{DD} - V_{ov}$$

So the range is

$$(-V_{DD} + V_t + 2V_{ov} \leq V_{ICM} \leq V_{DD} - V_{ov})$$

7.100

(a)

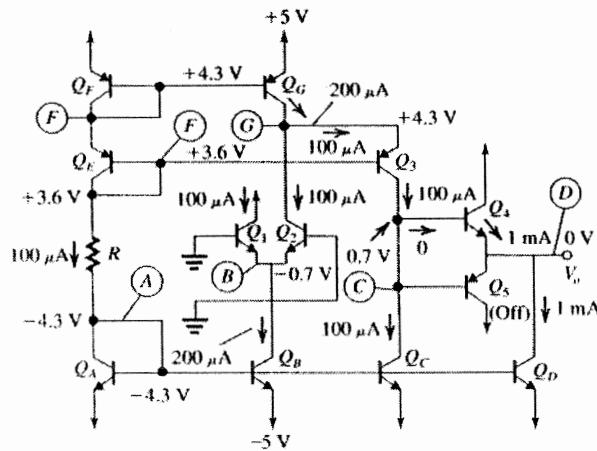

**DC Analysis**

$$R = \frac{3.6 - (-4.3)}{100 \mu\text{A}} = 79 \text{ k}\Omega$$

Node voltages:

$$\begin{aligned} V_A &= -4.3 \text{ V} & V_B &= -0.7 \text{ V} \\ V_C &= +0.7 \text{ V} & V_D &= 0 \text{ V} \\ V_E &= +3.6 \text{ V} & V_F &= +4.3 \text{ V} \\ V_G &= +4.3 \text{ V} \end{aligned}$$

$$\frac{v_{C3}}{v_i} = + g_m \times \frac{1}{2} \times 1.65 \times 10^3 = 3300 \frac{\text{V}}{\text{V}}$$

$$\frac{v_O}{v_{C3}} \approx 1$$

$$\text{Thus, } \frac{v_O}{v_i} \approx 3300 \text{ V/V (Polarity correct)}$$

$$(d) R_{in} = 2 r_{in}$$



$$= 2 \times \frac{100}{4} = 50 \text{ k}\Omega$$

(b)

Transistor	$I_C(\text{mA})$	$g_m(\text{mA/V})$	$r_s(\text{m}\Omega)$
$Q_1$	0.1	4	2
$Q_2$	0.1	4	2
$Q_3$	0.1	4	2
$Q_4$	1.0	40	0.2
$Q_5$	0	0	$\infty$
$Q_A$	0.1		
$Q_B$	0.2		
$Q_C$	0.1	.....	2
$Q_D$	1.0	.....	0.2
$Q_E$	0.1		
$Q_F$	0.1		
$Q_G$	0.2	.....	1

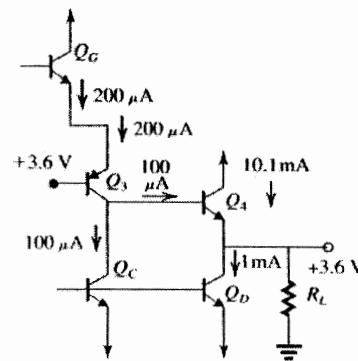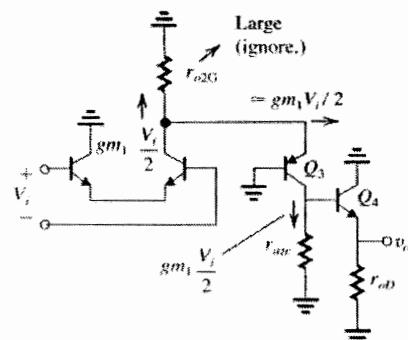(c) Total resistance at collector  $Q_3$  is

$$\begin{aligned} &\approx \beta_3 r_{o3} \parallel r_{od} \parallel (\beta_4 + 1)(r_{o4} \parallel r_{od}) \\ &= 100 \times 2 \parallel 2 \parallel 101(0.2 \parallel 0.2) \\ &= 1.65 \text{ M}\Omega \end{aligned}$$




i.e.  $v_O = +3.3 \text{ V}$  and  $Q_2$  just cut off

$$R_L = \frac{3.3 \text{ V}}{9.1 \text{ mA}}$$

(this is the minimum allowed  $R_L$  for +3.3 V output)

At the negative limit of  $v_O$  i.e.  $v_O = -3.3$  V and  $Q_1$  has cut-off.  $Q_3$  will also be cut-off, and  $Q_4$  will cut-off.

Thus,

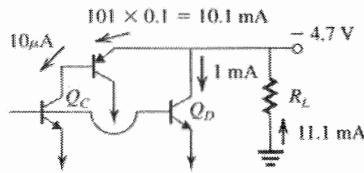

$R_L = \frac{4.7}{11.1 \text{ mA}} = 423 \Omega$  This is the minimum allowed  $R_L$  for a -4.7 V output.

7.101

## DC analysis

$$(a) I_{REF} = 10 \mu A = \frac{1}{2} \times 40 \times \frac{5}{5} (V_{GS_A} - V_t)^2$$

$$\Rightarrow V_{GS_A} = 1.71 \text{ V} = 1.7 \text{ V}$$

$$10 = \frac{1}{2} \times 20 \times \frac{5}{5} (V_{GS_E,F} - 1)^2$$

$$\Rightarrow V_{GS_{EF}} \approx 2\text{ V}$$

$$R = \frac{3 - (-3.3)}{10 \mu\text{A}} = 660 \text{ k}\Omega$$

(b) See figure above

$$V_{GS1} = V_{GS2} = V_{GSA} = 1.7 \text{ V}$$

$$V_{GS3} = \sqrt{\frac{2 \times 10}{20 \times \frac{10}{3}}} + 1 = 1.71 \text{ V} \approx 1.7 \text{ V}$$

$$V_{GSS} = V_{GS3} = 1.7 \text{ V}$$

$$\text{For } Q_6 : 50 = \frac{1}{2} \times 40 \times \frac{50}{5} (V_{GS6} - V_i)^2$$

$$\Rightarrow V_{GSS} = 1.50 \text{ V}$$

$$V_A \approx -3.3 \text{ V} \quad V_B \approx -1.7 \text{ V}$$


$$V_C = +1.5 \text{ V} \quad V_D = 0 \text{ V}$$

$$V_E = +1\text{ V} \quad V_F = +3\text{ V}$$


$$V_G = +3.3 \text{ V} \quad V_H = +2.7 \text{ V}$$

(c) Transistor	$I_D$ ( $\mu\text{A}$ )	$V_{GS}$ (V)	$gm$ ( $\text{mA/V}$ )	$r_O$ ( $\text{M}\Omega$ )
$Q_1$	10	1.7	28.3	5
$Q_2$	10	1.7	28.3	5
$Q_3$	10	1.7	28.3	5
$Q_4$	20	1.7	56.6	2.5
$Q_5$	10	1.7	28.3	5
$Q_6$	50	1.5	200	1
$Q_7$	0	-1.5*	0	$\infty$
$Q_A$	10	1.7	28.3	5
$Q_B$	20	1.7	56.6	2.5
$Q_C$	10	1.7	28.3	5
$Q_D$	50	1.7	141.4	1
$Q_E$	10	2	20	5
$Q_F$	10	2	20	5

\* Cut-off

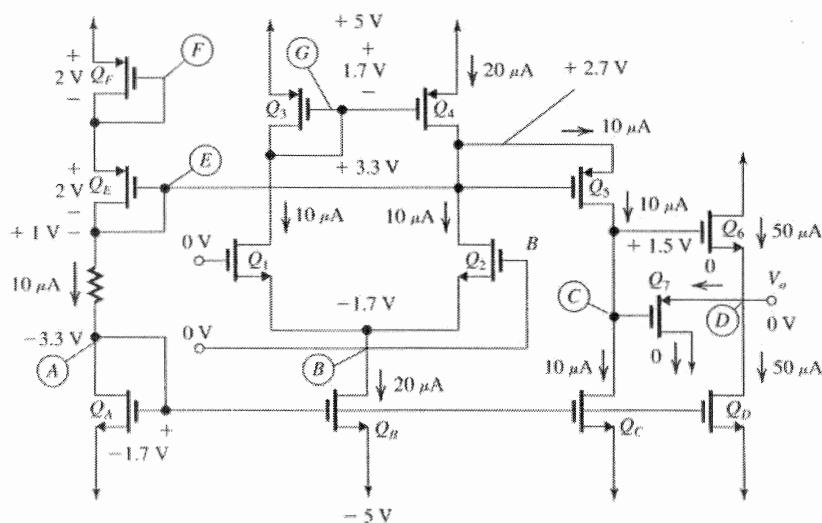

(d)

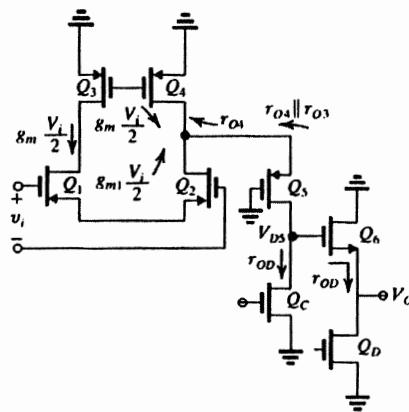

Total resistance at the drain of  $Q_5$ ,  $R$  is:

$$R = (g_m r_{O5})(r_{O4} \parallel r_{O2}) \parallel r_{OC}$$

$$= [(28.3 \times 5)(2.5 \parallel 2)] \parallel 5$$

$$= 4.9 \text{ M}\Omega$$

$$\text{Thus, } \frac{v_{ds}}{v_i} = g_m R$$

$$= 28.3 \times 4.9 = 138.7 \text{ V/V}$$

$$\text{and } \frac{v_o}{v_{ds}} = \frac{(r_{OD} \parallel r_{O6})}{(r_{OD} \parallel r_{O6}) + \frac{1}{g_{m6}}}$$

$$= \frac{(1 \parallel 1)}{(1 \parallel 1) + \frac{1}{200}} \approx 1$$

$$\frac{v_o}{v_i} = 138.7 \text{ V/V}$$

$$R_{in} = \infty$$

$$R_{out} = r_{OD} \parallel r_{O6} \parallel 1/g_{m6}$$

$$= 1 \parallel 1 \parallel 1/200 \text{ M}\Omega$$

$$\approx 5 \text{ k}\Omega$$

$$(c) v_{ICM|max} = V_G + V_t$$

$$= +4.3 \text{ V}$$

$$v_{ICM|min} = V_{GS1} + V_{B|min}$$

$$= V_{GS1} + V_A - V_t$$

$$= 1.7 - 3.3 - 1 = -2.6 \text{ V}$$

$$(f) v_{o|max} = V_C|_{max} - V_{GS6}$$

$$= V_E + |V_t| - V_{GS6}$$

$$= +1 + 1 - 1.5 = +0.5 \text{ V}$$


$$v_{o|min} = V_A - V_t = -3.3 - 1 = -4.3 \text{ V}$$

(g)  $Q_6$  cuts off

thus,


$$\frac{1V}{R_L} = 50 \mu\text{A}$$
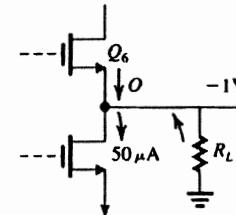
$$R_L = \frac{1V}{50 \mu\text{A}} = 20 \text{ k}\Omega$$



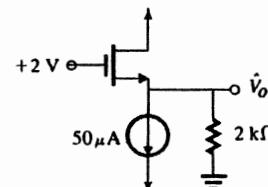(h) Maximum possible voltage at drain of  $Q_5$  is +2V. At this value we have:


$$I_D = 50 \mu\text{A} + \frac{\hat{V}_o}{2} \text{ mA}$$



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (2 - V_o - V_t)^2$$

$$\Rightarrow V_o \approx 0.17 \text{ V}$$

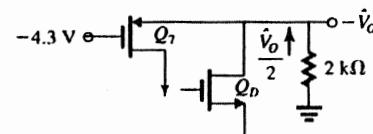For the lowest possible output, the circuit becomes



Where:

$Q_6$  cuts off and  $Q_7$  conducts

$$I_D = \frac{V_o}{2} - 0.05 \text{ mA}$$

$$= \frac{1}{2} \mu_p C_{ox} \left( \frac{100}{5} \right) (-\hat{V}_o + 4.3 - 1)^2$$

$$\Rightarrow \hat{V}_o = 1.45 \text{ V}$$

That is, the range of  $v_o$  is

$$-1.45 \text{ V to } +0.17 \text{ V}$$

8.1


$$I_D = 1 \text{ mA}, g_m = 1 \text{ mA/V}$$

Using eq. 4.89 we have:

$$A_M = \frac{-g_m R_D}{1 + g_m R_S} = -\frac{1 \times 10}{1 + 1 \times 6} \\ A_M = 1.43 \text{ V/V}$$

$$f_L = \frac{1}{2\pi(\frac{1}{g_m} || R_S) C_S} = 10 \text{ Hz}$$
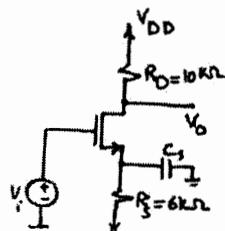
$$C_S = \frac{1}{2\pi \times 10 (1/16 \text{ K})} = 18.57 \mu\text{F}$$



8.2

$$f_{C_2} = \frac{1}{2\pi C_2 (R_L + R_D || r_o)} \leq 10 \text{ Hz}$$

$$\Rightarrow C_{C_2} > \frac{1}{10 \times 2\pi \times (10^4 + 15/1150)} \Rightarrow C_{C_2} > 0.67 \mu\text{F}$$

$$\Rightarrow C_{C_2} = 0.7 \mu\text{F} \Rightarrow f_{C_{C_2}} = 9.62 \text{ Hz}$$

IF  $I_D$  is doubled with both  $r_o$  and  $R_D$  halved:

$$f_{C_{C_2}} = \frac{1}{2\pi \times 0.7 \times (10^4 + 15/2 || 150/2)} = 13.5 \text{ Hz}$$

8.3

$$g_m = 1 \text{ mA/V}$$

$$A_M = -\frac{R_G}{R_G + R_{S\text{sig}}} g_m (R_D || R_L) \text{ where } R_G = 10 \text{ M} \parallel 47 \text{ M} \\ R_G = 8.25 \text{ M}\Omega$$

$$A_M = -\frac{8.25}{8.25 + 0.1} \times 1 \times (4.7 \parallel 10^4) = -3.16 \text{ V/V}$$

$$f_{P_1} = \frac{1}{2\pi C_{C_1} (R_G + R_{S\text{sig}})} \quad (\text{Eq. 4.134})$$

$$f_{P_1} = \frac{1}{2\pi \times 0.01 \times 10^{-6} \times (8.25 + 0.1) \times 10^6} = 1.9 \text{ Hz}$$

$$f_{P_2} = \frac{1}{2\pi C_S (R_S || \frac{L}{g_m})} = \frac{1}{2\pi \times 10 \times 10^{-6} \times (2 \parallel 1)} = 23.9 \text{ Hz}$$

$$f_{P_3} = \frac{1}{2\pi C_{C_2} (R_D + R_L)} = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times (4.7 + 10) \times 10^3} = 108.3 \text{ Hz}$$

$$f_L \approx 108.3 \text{ Hz}$$

8.4

$$C_{TOT} = C_S + C_{C1} + C_{C2} = 3 \mu\text{F}$$

$$R_G = 10 \text{ M}\Omega, R_{S\text{sig}} = 100 \text{ k}\Omega, g_m = 2 \frac{\text{mA}}{\text{V}}$$

$$R_D = R_L = 10 \text{ k}\Omega$$

$$f_{P_2} = \frac{g_m}{2\pi \cdot C_S} \Rightarrow C_S = \frac{2 \times 10^{-3}}{2\pi} \cdot \frac{1}{f_{P_2}} \\ = \frac{3.18 \times 10^{-4}}{f_{P_2}}$$

$$f_{P_1} = \frac{1}{2\pi \cdot C_{C1} \cdot (R_G + R_{S\text{sig}})} \\ \Rightarrow C_{C1} = \frac{1.57 \times 10^{-8}}{f_{P_1}}$$

$$f_{P_3} = \frac{1}{2\pi \cdot C_{C2} \cdot (R_D + R_L)} \\ \Rightarrow C_{C2} = \frac{7.95 \times 10^{-6}}{f_{P_3}}$$

If we choose:  $f_{P_2} = f_L, f_{P_1} = f_L/25, f_{P_3} = f_L/5$   
 $C_{TOT} = 3 \mu\text{F} = C_S + C_{C1} + C_{C2}$

$$3 \mu\text{F} = \frac{3.18 \times 10^{-4}}{f_L} + \frac{1.57 \times 10^{-8}}{f_L/25} \\ + \frac{7.95 \times 10^{-6}}{f_L/5}$$

$\Rightarrow f_L = 120 \text{ Hz}$  and  $C_S = 2.65 \mu\text{F}$ ,  
 $C_{C1} = 3.3 \text{ nF}, C_{C2} = 0.33 \mu\text{F}$

If we choose:  $f_{P_2} = f_L, f_{P_1} = \frac{f_L}{5}, f_{P_3} = \frac{f_L}{25}$   
 $C_{TOT} = 3 \mu\text{F} = C_S + C_{C1} + C_{C2}$

$$3 \mu\text{F} = \frac{3.18 \times 10^{-4}}{f_L} + \frac{1.57 \times 10^{-8}}{f_L/5} \\ + \frac{7.95 \times 10^{-6}}{f_L/25}$$

$\Rightarrow f_L = 172.3 \text{ Hz}, C_S = 1.8 \mu\text{F}$ ,  
 $C_{C1} = 455 \text{ pF}, C_{C2} = 1.15 \mu\text{F}$

8.5

$$R_E = 72 \Omega,$$

$$R_{C1} = 7.44 \text{ k}\Omega, R_{C2} = 13 \text{ k}\Omega$$

If  $C_E = 50 \mu\text{F}$ ,  $C_{C1} = C_{C2} = 2 \mu\text{F}$

$$f_{P_1} = \frac{1}{2\pi \cdot C_{C1} \cdot R_{C1}} \\ = \frac{1}{2\pi \times 2 \times 10^{-6} \times 7.44 \times 10^3} = 10.7 \text{ Hz}$$

$$f_{P_2} = \frac{1}{2\pi \cdot C_E \cdot R_E}$$

### 8.6

$$f_{p3} = \frac{1}{2\pi C_{C2} R_{C2}} = 44.2 \text{ Hz}$$

$$f_{p3} = \frac{1}{2\pi \times 50 \times 10^{-6} \times 72} = 44.2 \text{ Hz}$$

$$f_{p3} = \frac{1}{2\pi \times 2 \times 10^{-6} \times 13 \times 10^3} = 6.1 \text{ Hz}$$

From Eq 9.19

$$f_L = f_{p1} + f_{p2} + f_{p3} = 61 \text{ Hz}$$

$$g_m = 40 \text{ mA/V}, r_\pi = 2.5 \text{ k}\Omega \text{ and}$$

$$r_e = 25 \text{ }\Omega$$

If  $I_C$  is reduced by half, since

$$g_m = \frac{I_C}{V_T} \rightarrow g_m = 20 \frac{\text{mA}}{\text{V}}$$

$$r_\pi = \frac{\beta}{g_m} \rightarrow r_\pi = 5 \text{ k}\Omega \text{ and}$$

$$r_e = \frac{\alpha}{g_m} \rightarrow r_e = 50 \text{ }\Omega$$

Then:

$$R_{C1} = (R_B \parallel r_\pi) + R_{sig}$$

$$= (100 \text{ K} \parallel 5 \text{ K}) + 5 \text{ K} = 9.76 \text{ k}\Omega$$

$$R_E = r_e + \frac{R_B \parallel R_{sig}}{\beta + 1} = 50 + \frac{100 \text{ K} \parallel 5 \text{ K}}{101}$$

$$= 97 \text{ }\Omega$$

$$R_{C2} = R_C + R_L = 13 \text{ k}\Omega$$

For  $C_E$  to contribute 80% of  $f_L$

$$0.8 \times 2\pi \times 100 = \frac{1}{C_E \cdot 97} \rightarrow C_E = 20.51 \mu\text{F}$$

For  $C_{C1}$  and  $C_{C2}$  to contribute 10% of  $f_L$  each

$$0.1 \times 2\pi \times 100 = \frac{1}{C_{C1} \cdot 9.76 \times 10^3}$$

$$\rightarrow C_{C1} = 1.64 \mu\text{F}$$

$$0.1 \times 2\pi \times 100 = \frac{1}{C_{C2} \cdot 13 \times 10^3}$$

$$\rightarrow C_{C2} = 1.23 \mu\text{F}$$

To verify the value of  $f_L$  that results,

$$f_L = \frac{1}{2\pi} \left( \frac{1}{97 \times 20.51 \mu} + \frac{1}{9.76 \text{ K} \times 1.64 \mu} \right)$$

$$+ \frac{1}{13 \text{ K} \times 1.23 \mu}$$

$$f_L = 99.89 \text{ Hz}$$

### 8.7

$$R_{sig} = 20 \text{ k}\Omega, R_C = 20 \text{ k}\Omega,$$

$$R_B = 200 \text{ k}\Omega, R_L = 10 \text{ k}\Omega,$$

$$\beta = 100, I_C \approx 100 \mu\text{A}$$

$$g_m = \frac{I_C}{V_T} \approx \frac{100 \mu\text{A}}{25 \text{ mV}} = 4 \frac{\text{mA}}{\text{V}}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{4 \times 10^{-3}} = 25 \text{ k}\Omega$$

$$r_e = \frac{\alpha}{g_m} = \frac{0.99}{4 \times 10^{-3}} = 247.5 \text{ }\Omega$$

Then,

$$R_{C1} = (R_B \parallel r_\pi) + R_{sig}$$

$$= (200 \text{ K} \parallel 25 \text{ K}) + 20 \text{ K}$$

$$R_{C1} = 42.22 \text{ k}\Omega$$

$$R_E = r_e + \frac{R_B \parallel R_{sig}}{\beta + 1}$$

$$= 247.5 + \frac{(200 \text{ K} \parallel 20 \text{ K})}{101} = 427.52 \text{ }\Omega$$

$$R_{C2} = R_C + R_L = 20 \text{ K} + 10 \text{ K} = 30 \text{ K}$$

If we choose  $f_L = 100 \text{ Hz}$  and

$$f_{p2} = 0.9 \times f_L$$

$$C_E = \frac{1}{2\pi(0.9 \times f_L) \times R_E}$$

$$= \frac{1}{2\pi \times 90 \times 427.52} = 4.2 \mu\text{F}$$

Selecting  $C_{C1}$  and  $C_{C2}$  such as they contribute

5% of  $f_L$  each we have:

$$C_{C1} = \frac{1}{2\pi(0.05 \times 100) \times (42.22 \text{ K})} = 0.8 \mu\text{F}$$

$$C_{C2} = \frac{1}{2\pi(0.05 \times 100) \times (30 \text{ K})} = 1 \mu\text{F}$$

The resulting  $f_L$  is:

$$f_L = \frac{1}{2\pi} \left\{ \frac{1}{4.2 \mu \times (427.52)} \right.$$

$$+ \frac{1}{0.8 \mu \times 42.22 \text{ K}} \left. + \frac{1}{1 \mu \times 30 \text{ K}} \right\}$$

$$f_L = 98.65 \text{ Hz}$$

The total capacitance is:

$$C_I = 0.8 \mu + 1 \mu + 4.2 \mu = 6 \mu\text{F}$$

8.8

$$R_{in} = R_1 \parallel R_2 \parallel (f_x + f_\pi)$$

where  $R_1 = 33\text{ k}\Omega$ ,  $R_2 = 22\text{ k}\Omega$

$f_x = 50$  and,

$$f_\pi = \frac{\beta_0}{g_m} = \frac{120}{0.3 \times 40} = \frac{120}{12} = 10\text{ k}\Omega$$

$$R_{in} = 33 \parallel 22 \parallel 10.05 = \underline{\underline{5.7\text{ k}\Omega}}$$

$$\begin{aligned} A_M &= - \frac{R_{in}}{R_{in} + R_S} \cdot \frac{f_\pi}{f_\pi + f_x} \cdot g_m (R_C \parallel R_L \parallel r_o) \\ &= - \frac{5.7}{5.7 + 5} \cdot \frac{10}{10 + 0.05} \cdot 12 (4.7 \parallel 5.6 \parallel 300) \\ &= \underline{\underline{-16.11 \text{ V/V}}} \end{aligned}$$

$$\begin{aligned} R'_\text{sig} &= f_\pi \parallel [f_x + (R_1 \parallel R_2 \parallel R_\text{sig})] \\ &= 10\text{ k} \parallel [50 + (33 \parallel 22 \parallel 5)\text{ k}] \\ &= \underline{\underline{2.69\text{ k}\Omega}} \end{aligned}$$

$$\begin{aligned} R'_L &= r_o \parallel R_C \parallel R_L = 300 \parallel 4.7 \parallel 5.6(\text{k}\Omega) \\ &= \underline{\underline{2.53\text{ k}\Omega}} \end{aligned}$$

$$C_{\pi} + C_R = \frac{g_m}{2\pi \cdot f_T} = \frac{12 \cdot 10^{-3}}{2\pi \times 700 \cdot 10^6} = 2.73 \text{ pF}$$

$$C_\pi = (2.73 - 1) \text{ pF} = 1.73 \text{ pF}$$

$$\begin{aligned} C_{in} &= C_\pi + C_R (1 + g_m R'_L) \\ &= 1.73 \text{ p} + 1 \text{ p} (1 + 12 \times 2.53) \\ &= \underline{\underline{33 \text{ pF}}} \end{aligned}$$

$$\begin{aligned} f_H &= 1/2\pi C_{in} \cdot R'_\text{sig} \\ &= 1/2\pi \times 33 \cdot 10^{-12} \times 2.69 \cdot 10^3 \\ &= \underline{\underline{1.79 \text{ MHz}}} \end{aligned}$$

8.9

To select  $C_E$  so that it contributes 90% of the value of  $f_L$

$$\frac{1}{2\pi C_E \cdot R_E} = 0.9 \times 100 \quad R_E = 110.8 \Omega$$

(From problem 9.11)

$$\Rightarrow C_E = 15.9 \mu\text{F}$$

To select  $C_{c1}$  so that it contributes 5% of  $f_L$ :

$$R_{C1} = 10.7 \text{ k}\Omega$$

$$\Rightarrow C_{c1} = \frac{1}{2\pi \cdot 10.7 \times 10^3 \times 0.05 \times 100} = 2.97 \mu\text{F}$$

To select  $C_{C2}$  so that it contributes 5% of  $f_L$ :  $R_{C2} = 10.3 \text{ k}\Omega$

$$\Rightarrow C_{C2} = \frac{1}{2\pi \cdot 10.3 \times 10^3 \times 0.05 \times 100} = 3.1 \mu\text{F}$$

8.10

$$\begin{aligned} R_{C1} &= R_S + [R_B \parallel (f_x + f_\pi)] \\ &= 10 + [10 \parallel (0.1 + 1)] \\ &= 10.99 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} R_E' &= R_E \parallel \frac{f_\pi + f_x + (R_B \parallel R_S)}{(\beta_0 + 1)} \\ &\simeq 1 \parallel \frac{1 + 0.1 + (10 \parallel 10)}{100 + 1} \\ &= 57\text{V} \end{aligned}$$

For  $C_E$  and  $C_{c1}$  to contribute equally to the determination of  $f_L$ ,

$$\begin{aligned} C_E R_E' &= C_{c1} R_{C1} \\ \Rightarrow \frac{C_E}{C_{c1}} &= \frac{R_{C1}}{R_E'} = \frac{10.99}{0.057} = \underline{\underline{193}} \end{aligned}$$

### 8.11

$$a) I_b = \frac{V_s}{R_s + r_\pi} \quad I_C = \beta \cdot I_b = \frac{\beta \cdot V_s}{R_s + r_\pi}$$

$$V_o = -I_C (R_C \parallel R_L) = -\beta \cdot \frac{(R_C \parallel R_L)}{R_s + r_\pi} \cdot V_s$$

$$A_M = \frac{V_o}{V_s} = -\beta \frac{(R_C \parallel R_L)}{R_s + r_\pi}$$

$$b) \text{Pole due to } C_E: \omega_{PE} = \frac{1}{C_E \left( r_e + \frac{R_s}{\beta + 1} \right)}$$

$$\text{Pole due to } C_C: \omega_{PC} = \frac{1}{C_C (R_C + R_L)}$$

zeros are both at  $s = 0$

$$c) A(s) = A_M \cdot \frac{s^2}{(s + \omega_{PE})(s + \omega_{PC})}$$

$$A(s) = \frac{-\beta (R_C \parallel R_L)}{R_s + r_\pi}$$

$$\frac{s^2}{\left[ s + \frac{1}{C_E \left( R_e + \frac{R_s}{\beta + 1} \right)} \right] \times \left[ s + \frac{1}{C_C (R_C + R_L)} \right]}$$

$$d) A_M = \frac{-100(10 \parallel 10)}{10 + \frac{100}{40}} = -40 \text{ V/V}$$


e) Since the resistance that forms the pole  $\omega_{PE}$  is very small, we choose to make  $\omega_{PE}$  the dominant pole, thus :

$$f_{PE} = f_L = 100 = \frac{1}{2\pi C_E \left( 25 + \frac{10 \text{ K}}{101} \right)}$$

$$\Rightarrow C_E = \frac{1}{2\pi \cdot 100 \cdot (0.025 + 0.100) \times 10^3} = 12.7 \mu\text{F}$$

$$f_{PC} = 10 \text{ Hz} \Rightarrow 10 \text{ Hz} = \frac{1}{2\pi C_C (R_L + R_C)}$$
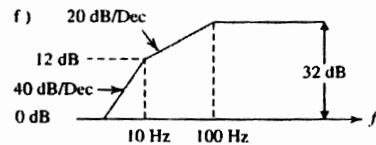
$$\Rightarrow C_C = \frac{1}{2\pi \times 10(10 + 10) \cdot 10^3} = 0.8 \mu\text{F}$$



Unity-gain frequency must be an octave lower than 10 Hz i.e. at 5 Hz


$$g) A(j\omega) = -A_M \cdot \frac{\omega^2}{(\omega_{PE} + j\omega)(\omega_{PC} + j\omega)} \\ = +40 \cdot \frac{\omega^2}{(\omega_{PE} + j\omega)(\omega_{PC} + j\omega)}$$

$$\text{Thus } \phi = \tan^{-1} \left( \frac{\omega}{\omega_{PE}} \right) - \tan^{-1} \left( \frac{\omega}{\omega_{PC}} \right)$$

$$= - \left[ \tan^{-1} \frac{f}{f_{PE}} + \tan^{-1} \frac{f}{f_{PC}} \right]$$

$$= - \left[ \tan^{-1} \frac{f}{100} + \tan^{-1} \frac{f}{10} \right]$$
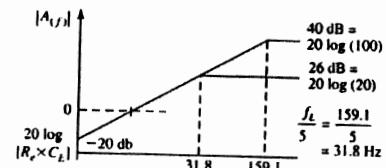
$$\text{Thus at } f = 100 \text{ Hz } \phi = -[\tan^{-1} 1 + \tan^{-1} 10] \\ \approx 129.3^\circ$$



### 8.12

$$(a) I_e = \frac{V_s}{r_e + R_e + \frac{1}{sC_e}}$$

$$I_c \approx I_e$$

$$V_o = -R_C I_c = \frac{-R_C}{r_e + R_e + \frac{1}{sC_e}} \cdot V_s$$

$$A(s) \equiv \frac{V_o}{V_s} = \frac{-R_C}{r_e + R_e + \frac{1}{sC_e}}$$

$$= \frac{-R_C}{r_e + R_e} \cdot \frac{s}{s + \frac{1}{C_e(r_e + R_e)}}$$

$$\text{Thus, } A_M = \frac{-R_C}{r_e + R_e}$$

$$WL = \frac{1}{C_e(r_e + R_e)}$$

(b)  $A_m$  is reduced by the factor  $\frac{1 + R_e}{R_e}$

$$= 1 + \frac{R_e}{R_e}$$

(c)  $W_L$  is reduced by the factor  $(1 + \frac{R_e}{R_e})$

which is the same as the gain reduction factor. Thus, the value of  $R_e$  can be used as the parameter for exercising the gain-bandwidth trade off.

(d)  $R_e = 0$ :

$$|A_m| = \frac{R_c}{R_e} = \frac{10,000}{25} = \underline{\underline{400}} \text{ V/V}$$

$$f_L = \frac{1}{2\pi C_E R_e} = \frac{1}{2\pi \times 100 \times 10^{-6} \times 25} \\ = \underline{\underline{63.7}} \text{ Hz}$$

To lower  $f_L$  by a factor of 5 use:

$R_e = 4R_e = \underline{\underline{100}}$ . The gain is also lowered by a factor of 5 to  $\underline{\underline{80}}$  V/V

8.13

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{8 \times 10^{-9}} \\ = 4.3 \times 10^{-3} \text{ F/m}^2 = 4.3 \text{ fF}/\mu\text{m}^2$$

$$k_n = \mu_n C_{ox} = 450 \times 10^{-4} \times 4.3 \times 10^{-3} \\ = 193.5 \mu\text{A/V}^2$$

$$I_D = 100 \mu\text{A} = \frac{1}{2} \times 193.5 \times \frac{20}{1} V_{ov}^2 \\ \Rightarrow V_{ov} = 0.23 \text{ V}$$

$V_{DS} = 1.5 \text{ V} > V_{ov} \Rightarrow \text{Saturation}$

$$g_m = \frac{2I_D}{V_{ov}} = 880 \mu\text{A/V},$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.05 \times 0.1} = 200 \text{ k}\Omega$$

$$X = \frac{r}{2\sqrt{2} \mu_f + V_{SB}} = \frac{0.5}{2\sqrt{0.65 + 1}} = 0.19$$

$$g_m b = X g_m = 167.2 \mu\text{A/V}$$

$$C_{ov} = W L_{ov} C_{ox} = 20 \times 0.05 \times 4.3 \\ = 4.3 \text{ fF}$$

$$C_{gs} = \frac{2}{3} W L C_{ox} + C_{ov} \\ = \frac{2}{3} \times 20 \times 1 \times 4.3 + 4.3 = 61.6 \text{ fF}$$

$$C_{gd} = C_{ov} = 4.3 \text{ fF}$$

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}} = \frac{15}{\sqrt{1 + \frac{1}{0.7}}} = 9.6 \text{ fF}$$

$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{db}}{V_o}}} = \frac{15}{\sqrt{1 + \frac{(1 + 1.5)}{0.7}}} = 7 \text{ fF}$$

8.14

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.1}{0.25} = 0.8 \text{ mA/V}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} = \frac{0.8 \times 10^{-3}}{2\pi(20 + 5) \times 10^{15}} = 5.1 \text{ GHz}$$

### 8.15

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$g_m = \sqrt{2 \cdot \mu_n \cdot C_{ov} \frac{W}{L} \cdot I_D}$$

Also  $C_{gs} \approx \frac{2}{3}WL \cdot C_{ox}$ , if  $C_{gs} \gg C_{gd}$  then we can ignore  $C_{gd}$ . If we replace for  $g_m$  and  $C_{gs}$ , then we have :

$$f_T = \frac{\sqrt{2\mu_n \cdot C_{ox}(W/L)I_D}}{2 \cdot \pi \cdot \frac{2}{3}W \cdot L \cdot C_{ox}}$$

$$= \frac{1.5}{\pi \cdot L} \sqrt{\frac{\mu_n \cdot I_D}{2C_{ox} \cdot WL}}$$

Therefore we can see that the higher the current  $I_D$  then the higher is  $f_T$ . Also the frequency is inversely proportional to the size of the device, i.e. higher frequencies are achievable for smaller devices.

### 8.16

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} \quad (1)$$

For  $C_{gs} \gg C_{gd}$  and the over lap capacitance of  $C_{gs}$  negligibly small :  $C_{gs} \approx \frac{2}{3}WL C_{ox}$

$$\text{Also } g_m = \frac{2I_D}{V_{ov}} = k_n \frac{W}{L} V_{ov}$$

If we substitute  $g_m$  and  $C_{gs}$  in (1) from the above

$$\text{formulas : } f_T = k_n \frac{W}{L} V_{ov} \frac{1}{2\pi \times \frac{2}{3}WL C_{ox}}$$

$$\Rightarrow f_T = \frac{3\mu_n V_{ov}}{4\pi L^2}$$

Therefore, for a given device  $f_T$  is proportional to  $V_{ov} \cdot f_T \propto V_{ov}$

For  $L = 1 \mu\text{m}$ ,  $V_{ov} = 0.25$ :

$$f_T = \frac{3 \times 450 \times 10^{-4} \times 0.25}{4 \times \pi \times 1 \times 10^{-12}} = 2.7 \text{ GHz}$$

$$\text{For } V_{ov} = 0.5 \text{ V} : \frac{f_{T1}}{f_{T2}} = \frac{V_{ov1}}{V_{ov2}}$$

$$\Rightarrow f_{T2} = 2.7 \times \frac{0.5}{0.25}$$

$$f_T = 5.4 \text{ GHz}$$

### 8.17

The intrinsic gain  $A_O$  is

$$= g_m \cdot r_o = \left( \frac{2I_D}{V_{ov}} \right) \cdot \left( \frac{V_A}{I_D} \right) = \frac{2V_A}{V_{ov}}$$

$$V_A = V_A \cdot L = 5 \text{ V}/\mu\text{m} \times L$$

$$A_O = \frac{2 \times 5[\text{V}/\mu\text{m}] \cdot L}{0.2[\text{V}]} = 50 \times L \text{ V/V with}$$

$L$  in mm.

\* From problem 9.19

$$f_T = \frac{3\mu_n V_{ov}}{4\pi \cdot L^2} = \frac{3 \times 450 \left[ \frac{\text{cm}^2}{\text{V} \cdot \text{s}} \right] \cdot 0.2[\text{V}]}{4\pi L^2}$$

$$= \frac{2.15 \times 10^{-3}}{L^2}$$

$$L_{min} = 0.18 \times 10^{-6} \text{ m}$$

	$1 L_{min}$	$2 L_{min}$	$3 L_{min}$	$4 L_{min}$	$5 L_{min}$
$A_O [\text{V/V}]$	9	18	27	36	45
$f_T [\text{GHz}]$	66.35	16.59	7.37	4.14	2.65

### 8.18

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$


$$= \frac{80 \times 10^{-3}}{2\pi(10+1) \times 10^{-12}}$$

$$= \underline{\underline{4.24 \text{ GHz}}}$$

$$f_B = f_T / \beta_0 = (4.24 / 150) \times 10^9$$

$$= \underline{\underline{28.26 \text{ MHz}}}$$

8.19

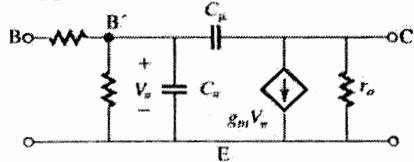

$$r_x = 100 \Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V}$$

$$r_\pi = \frac{\beta_0}{g_m} = \frac{100}{20} = 5 \text{ k}\Omega$$

$$r_O = \frac{V_A}{I_C} = \frac{50 \text{ V}}{0.5 \text{ mA}} = 100 \text{ k}\Omega$$

$$C_\mu = \frac{C_{\mu n}}{\left(1 + \frac{V_{ce}}{V_{oc}}\right)^{0.5}} = \frac{30}{\left(1 + \frac{2}{0.75}\right)^{0.5}}$$

$$= 15.7 \text{ fF}$$

$$C_\pi \leq 2C_{ne} = 2 \times 20 = 40 \text{ fF}$$

$$C_{de} = \tau_F g_m = 30 \times 10^{-12} \times 20 \times 10^{-3}$$

$$= 600 \text{ fF}$$

$$C_\pi = C_{je} + C_{de} = 0.640 \text{ pF}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$= \frac{20 \times 10^{-3}}{2\pi(0.64 + 0.016) \times 10^{-12}} = 4.85 \text{ GHz}$$

8.20

$$|h_{fe}| \approx f_T/f$$

• At  $I_C = 0.2 \text{ mA}$ ,  $|h_{fe}| = 2.5$   
at  $f = 500 \text{ MHz}$ , thus:

$$f_T = 2.5 \times 500 = \underline{\underline{1.25 \text{ GHz}}}$$

• At  $I_C = 1.0 \text{ mA}$ ,  $|h_{fe}| = 11.6$

at  $f = 500 \text{ MHz}$ , thus:

$$f_T = 11.6 \times 500 = \underline{\underline{5.8 \text{ GHz}}}$$

$$f_T = \frac{g_m}{2\pi(C\pi + C_\mu)}$$

$$C\pi + C_\mu = \frac{g_m}{2\pi f_T} \rightarrow C\pi = \frac{g_m}{2\pi f_T} - C_\mu$$

$$C\pi (I_C = 0.2 \text{ mA}) = \frac{8 \times 10^{-3} - 0.05 \times 10^{-12}}{2\pi \times 1.25 \times 10^9}$$

$$= 0.9686 \text{ pF}$$

$$C\pi (I_C = 1.0 \text{ mA}) = \frac{40 \times 10^{-3} - 0.05 \times 10^{-12}}{2\pi \times 5.8 \times 10^9}$$

$$= 1.0476 \text{ pF}$$

Since  $C\pi = C_{je} + \gamma_F g_m$ ,

$$C_{je} + 8 \times 10^{-3} \gamma_F = 0.9686 \times 10^{-12} \quad (1)$$

$$C_{je} + 40 \times 10^{-3} \gamma_F = 1.0476 \times 10^{-12} \quad (2)$$

Solving Eqn. (1) and (2)  
together yields,

$$C_{je} = \underline{\underline{0.95 \text{ pF}}}, \gamma_F = \underline{\underline{247 \text{ ps}}}$$

8.21

$$\omega_T = g_m / (C\pi + C_\mu)$$

$$2\pi \times 5 \times 10^9 = \frac{20 \times 10^{-3}}{C\pi + 0.1}$$

$$C\pi + 0.1 = \frac{(C\pi + 0.1) \times 10^{-12}}{20} = 0.64 \text{ pF}$$

$$C\pi = \underline{\underline{0.54 \text{ pF}}}$$

$$g_m = \underline{\underline{20 \text{ mA/V}}}$$

$$f_T = \beta/g_m = 150/20 = \underline{\underline{7.5 \text{ kHz}}}$$

$$f_\beta = f_T/\beta = \frac{5 \times 10^9}{150} = \underline{\underline{33.3 \text{ MHz}}}$$

8.22

$f_{T/20}$  becomes 20 at:

$$f_{T/20} = \frac{1 \times 10^9}{20} = 50 \text{ MHz}$$

$$f_B = f_{T/\beta_0} = \frac{1000 \text{ MHz}}{200} = 5 \text{ MHz}$$

8.23

$$Z = r_x + \frac{1}{\frac{r_\pi}{r_\pi} + j\omega c\pi}$$

$$= r_x + \frac{r_\pi}{1 + j\omega c\pi r_\pi}$$

$$Z = r_x + \frac{r_\pi}{1 + j(\omega/\omega_\beta)}$$

$$= r_x + r_\pi \left( 1 - j\omega/\omega_\beta \right)$$

$$= r_x + \frac{r_\pi}{1 + (\frac{\omega}{\omega_\beta})^2} - j \cdot \frac{r_\pi (\omega/\omega_\beta)}{1 + (\frac{\omega}{\omega_\beta})^2}$$

$$\operatorname{Re}[Z] = r_x + \frac{r_\pi}{1 + (\frac{\omega}{\omega_\beta})^2}$$

For  $\operatorname{Re}[Z]$  to be an estimate of  $r_x$  good to within 10% we must keep

$$\frac{r_\pi}{1 + (\frac{\omega}{\omega_\beta})^2} \leq \frac{r_x}{10}$$

But  $r_x \leq r_\pi/10$

Thus,

$$\frac{r_\pi}{1 + (\frac{\omega}{\omega_\beta})^2} \leq \frac{r_\pi}{100}$$

$$1 + (\frac{\omega}{\omega_\beta})^2 \geq 100$$

or  $\omega \geq 10 \omega_\beta$  (approx.)

8.24

	$I_E$ (mA)	$r_e$ ( $\Omega$ )	$g_m$ (mA/V)	$r_\pi$ (k $\Omega$ )	$\beta_0$
(a)	1	25	40	2.5	100
(b)	1	25	40	3.13	125.3
(c)	0.99	25.3	39.6	2.525	100
(d)	10	2.5	400	0.25	100
(e)	0.1	250	4	25	100
(f)	1.0	25	40	0.25	10
(g)	1.25	20	50	0.20	10

CONT.	$f_T$ (MHz)	$C_s$ (pF)	$C_m$ (pF)	$f_B$ (MHz)
(a)	400	2	13.9	4
(b)	501.3	2	10.7	4
(c)	400	2	13.8	4
(d)	400	2	157	4
(e)	100	2	4.4	1
(f)	400	2	13.9	40
(g)	800	1	9	80

8.25

$$C_{in} = C_{gs} + C_{eq}$$

$$= C_{gs} + C_{gd} (1 + g_m R_L)$$

$$= 0.5 + 0.1(1 + 29) = 3.5 \text{ pF}$$

Neglecting  $R_G$ :

$$f_H = \frac{1}{2\pi \cdot C_{in} \cdot R_{sig}}$$

i.e.  $R_G$  is very large if

$$f_H > 10 \text{ MHz} \Rightarrow \frac{1}{2\pi \cdot 3.5 \times 10^{-12} \times 10^6} > R_{sig}$$

$$\Rightarrow R_{sig} < 4.55 \text{ k}\Omega$$

### 8.26

Since  $R_G$  is very large:

$$f_H = \frac{1}{2\pi \cdot C_{in} \cdot R_{sig}}$$

$$\text{if } f_H \geq 10 \text{ MHz} \Rightarrow 10 \times 10^6 \leq \frac{1}{2\pi \cdot C_{in} \cdot R_{sig}}$$

$$C_{in} \leq \frac{1}{2\pi \times 10 \times 10^6 \times 1 \times 10^3}$$

$$C_{in} \leq 15.91 \text{ pF}$$

$$\Rightarrow C_{gs} + C_{gd}(1 + g_m R_L) \leq 15.91 \text{ pF}$$

$$5 \times 10^{-12} + 1 \times 10^{-12}(1 + 5 \times 10^{-3} \cdot R_L)$$

$$\leq 15.91 \text{ pF} \Rightarrow R_L \leq 1982 \Omega$$

Since  $R_G$  is very large:  $A_M = -g_m \cdot R_L$

$$A_M \geq -5 \times 10^{-3} \cdot 1982 \Rightarrow A_M \geq -9.91 \text{ V/V}$$

Gain - bandwidth product :  $\text{GB} = |\Delta_M| \cdot \text{BW}$

$$\text{GB} \geq 9.1 \times 10 \times 10^6 \text{ GB} \geq 91 \text{ MHz}$$

$$\text{If } f_H \geq \frac{10}{3} \text{ MHz}$$

$$\text{then: } R_L \leq 8349 \Omega$$

$$A_M \geq -47.75 \text{ V/V}$$

$$\text{GB} \geq 139.2 \text{ MHz}$$

### 8.27

$$g_m = 1 \frac{\text{mA}}{\text{V}}; C_{gs} = 1 \text{ pF}; C_{gd} = 0.4 \text{ pF};$$

$$C_{in} = 4.26 \text{ pF}; A_M = -7 \frac{\text{V}}{\text{V}}; f_H = 382 \text{ KHz}$$

$$\Rightarrow \text{GB} = 7 \times 382 \cdot 10^3 = 2.67 \text{ MHz}$$

We also Know that:

$$C_{gs} = \frac{2}{3} W \cdot C_{ox} + WL_{ov} \cdot C_{ox}$$

$$= WC_{ox} \left( \frac{2}{3} + L_{ov} \right)$$

$$C_{gd} = WL_{ov} C_{ox}$$

$\Rightarrow$  if  $W$  is reduced by half so are  $C_{gs}$  and  $C_{gd}$

$$\Rightarrow C_{gs2} = 0.5 \text{ pF} \quad C_{gd2} = 0.2 \text{ pF}$$

In saturation:

$$I_D = \frac{1}{2} k_n \frac{W}{L} (V_{ov})^2 \Rightarrow \text{For } I_D \text{ to remain}$$

unchanged while  $\omega$  is halved

$$\Rightarrow (V_{ov})^2 \text{ is doubled}$$

$$\text{thus } V_{ov2} = \sqrt{2} V_{ov}$$

$$\text{but } g_m = \frac{2I_D}{V_{ov}} = g_{m2} = \frac{1}{\sqrt{2}} g_m$$

$$= 0.707 \text{ mA/V}$$

we can now calculate the new values of  $A_M$ ,  $C_{in}$ ,  $f_H$  and  $\text{GB}$

$$A_{M2} = \frac{-R_G}{R_G + R_{sig}} \cdot g_m R_L = -\frac{7}{\sqrt{2}} \cdot \text{V/V}$$

$$= -4.9 \text{ V/V}$$

$$C_{eq2} = (1 + 0.707 + 7.14) \cdot 0.2 \times 10^{-12}$$

$$= 1.21 \text{ pF}$$

$$\Rightarrow C_{in2} = 0.5 + 1.21 = 1.71 \text{ pF}$$

$$f_{H2} = \frac{1}{2\pi \cdot 1.71 \times 10^{-12} \cdot (0.1 \parallel 4.7) \times 10^6}$$

$$= 950 \text{ KHz}$$

$$GB_2 = 4.9 \times 950 \cdot 10^3 = 4.65 \text{ MHz}$$

The ratios of new vs old values are:

$\frac{W_2}{W}$	$\frac{V_{ov2}}{V_{ov}}$	$\frac{g_{m2}}{g_m}$	$\frac{C_{eq2}}{C_{eq}}$	$\frac{C_{gd2}}{C_{gd}}$	$\frac{C_{in2}}{C_{in}}$	$\frac{\Delta M_2}{\Delta M}$
$\frac{1}{2}$	$\sqrt{2}$	$\frac{1}{\sqrt{2}}$	$\frac{1}{2}$	$\frac{1}{2}$	0.4	0.7

$\frac{f_{H2}}{f_H}$	$\frac{GB_2}{GB}$
2.49	1.74

8.28

$$R_{sig} = 100\text{ k}\Omega, R_{in} = 100\text{ k}\Omega, C_{gs} = 1\text{ pF}, C_{gd} = 0.2\text{ pF}$$

$$A_M = -\frac{R_G}{R_G + R_{sig}} g_m (r_0 \parallel R_D \parallel R_L)$$

$$\text{Also } R_{in} = 100\text{ k}\Omega = R_G$$

$$A_M = \frac{-100}{100+100} 3(50^k \parallel 8k \parallel 10^k) = -6.1 \text{ V/V}$$

$$f_H = \frac{1}{2\pi C_{in} R'_{sig}} \quad (\text{Eq. 4.132})$$

$$R'_{sig} = R_{sig} \parallel R_G = 100 \parallel 100 = 50\text{ k}\Omega$$

$$C_{in} = C_{gs} + C_{gd}(1 + g_m R'_L)$$

$$R'_L = r_0 \parallel R_D \parallel R_L = 4.1\text{ k}\Omega$$

$$C_{in} = 1 + 0.2(1 + 3 \times 4.1) = 3.66\text{ pF}$$

Now we can calculate  $f_H$ :

$$f_H = \frac{1}{2\pi \times 3.66 \times 10^{-12} \times 50 \times 10^3} = 870 \text{ kHz}$$

In order to double  $f_H$ , we have to either decrease  $C_{in}$  (by reducing  $R_{out}$ ) or reduce  $R'_{sig}$  by reducing  $R_{in}$ .

If we reduce  $R_{out} = R_0 \parallel r_0$ :

$$\frac{f_{H2}}{f_{H1}} = \frac{C_{in1}}{C_{in2}} \Rightarrow 2 = \frac{3.66 \text{ pF}}{1 + 0.2(1 + 3 \times R'_L)}$$

$$\Rightarrow R'_L = 1.27\text{ k}\Omega \quad R'_L = R_{out} \parallel R_L = R_{out} \parallel 10^k$$

$$\Rightarrow R_{out} = 1.45\text{ k}\Omega$$

Therefore in order to double  $f_H$  to  $870 \times 2 = 1.74 \text{ MHz}$ , we have to reduce  $R_{out} = r_0 \parallel R_D$  to  $1.45\text{ k}\Omega$  or equivalently reducing  $R_D$  to  $1.5\text{ k}\Omega$ . The new midband gain would be:

$$\frac{A_{M2}}{A_{M1}} = \frac{R'_L}{R'_L} = \Rightarrow A_{M2} = 6.1 \times \frac{1.27}{4.1} = 1.9 \text{ V/V}$$

Gain is almost reduced by a factor of 3.

If we reduce  $R_{in} = R_G$ :

$$\frac{f_{H2}}{f_{H1}} = \frac{R'_{sig1}}{R'_{sig2}} \Rightarrow 2 = \frac{50^k}{R'_{sig2}} \Rightarrow R'_{sig2} = 25\text{ k}\Omega$$

$$\Rightarrow 25\text{ k}\Omega = 100\text{ k}\Omega \parallel R_G \Rightarrow R_G = 33\text{ k}\Omega = R_{in}$$

Therefore in order to double  $f_H$ ,  $R_{in}$  is reduced by a factor of 3, from  $100\text{ k}\Omega$  to  $33\text{ k}\Omega$ .

The new midband gain would be:

$$\frac{A_{M2}}{A_{M1}} = \frac{R_G}{R_G + R_{sig}} \frac{R_{in} + R_{sig}}{R_{in} + R_{sig}} \Rightarrow A_{M2} = 6.1 \times \frac{1}{3} \frac{100 + 100}{33 + 100}$$

$$A_{M2} = 3.06 \text{ V/V}$$

Gain is almost reduced by a factor of 2.

8.29

$$R_{in} = 2\text{ M}\Omega, g_m = 4\text{ mA/V}, r_0 = 100\text{ k}\Omega, R_D = 10\text{ k}\Omega$$

$$C_{gs} = 2\text{ pF}, C_{gd} = 0.5\text{ pF}, R_{sig} = 500\text{ k}\Omega, R_L = 10\text{ k}\Omega$$

noting that  $R_G = R_{in}$ ,

we have:

$$\frac{A_M}{A_M} = \frac{R_G}{R_G + R_{sig}} g_m (r_0 \parallel R_D \parallel R_L) = -\frac{2 \times 4}{2 + 0.5} (100^k \parallel 10 \parallel 10^k)$$

$$\therefore f_H = \frac{1}{2\pi C_{in} R'_{sig}} \quad \text{where} \\ C_{in} = C_{gs} + C_{gd}(1 + g_m (r_0 \parallel R_D \parallel R_L)), R'_{sig} = R_{sig} \parallel R_G \\ C_{in} = 2 + 0.5(1 + 4 \times (100^k \parallel 10^k \parallel 10^k)) = 12.02\text{ pF} \\ R'_{sig} = 0.5\text{ M}\Omega \parallel 2\text{ M}\Omega = 0.4\text{ M}\Omega = 400\text{ k}\Omega$$


$$f_H = \frac{1}{2\pi \times 12.02 \times 10^{-12} \times 400 \times 10^3} = 33.1 \text{ kHz}$$

8.30

If we write KCL

at node D:
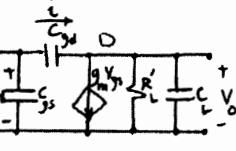
$$i = g_m v_{gs} + \frac{v_o}{R'_L} + v_o c_s$$



$$\text{then: } v_{sig} = i \times \frac{1}{c_{gs}s} + v_o$$

$$v_{sig} = (g_m v_{gs} + \frac{v_o}{R'_L} + v_o c_s) \frac{1}{c_{gs}s} + v_o, \quad v_{sig} = v_{gs}$$

$$v_{sig} (1 - \frac{g_m}{c_{gs}s}) = v_o (1 + \frac{1}{R'_L c_{gs}s} + \frac{c_s s}{c_{gs}s})$$

$$\frac{v_o}{v_{sig}} = -g_m \frac{R'_L (1 - s(c_s/g_m))}{R'_L c_{gs}s + 1 + R'_L c_s}$$

$$\frac{v_o}{v_{sig}} = -g_m \frac{R'_L \frac{1 - s(c_s/g_m)}{1 + s(c_s + c_{gs})R'_L}}$$

$$SF(g_m/c_{gs}) \gg \omega \Rightarrow \frac{v_o}{v_{sig}} = \frac{-g_m R'_L}{1 + s(c_s + c_{gs})R'_L}$$

For \$c\_{gs} = 0.5 \text{ pF}\$, \$c\_s = 2 \text{ pF}\$, \$g\_m = 4 \text{ mA/V}\$, \$R'\_L = 5 \text{ k}\Omega

$$\frac{v_o}{v_{sig}} = \frac{A_M}{1 + s/\omega_H} \Rightarrow \left\{ A_M = -g_m R'_L = -4 \times 5 = -20 \text{ V/V} \right.$$

$$\Rightarrow f_H = \frac{10^2}{2\pi(2+0.5) \times 5 \times 10^3}$$

$$f_H = 12.7 \text{ MHz}$$

$$g_m/c_{gs} = \frac{4}{0.5} = 8 \text{ rad/s} \gg \omega$$

8.31

If \$g\_m = 1 \frac{\text{mA}}{\text{V}}\$ and \$r\_o = 100 \text{ k}\Omega\$:

$$A_M = \frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L) \text{ where}$$

$$R_G = 10 \text{ M} \parallel 47 \text{ M}$$

$$R_G = 8.25 \text{ M}\Omega$$

$$A_M = -\frac{8.25}{8.25 + 0.1} |(100 \text{ K} \parallel 4.7 \text{ K} \parallel 10 \text{ K})|$$

$$= -3.06 \text{ V/V}$$

$$f_H = \frac{1}{2\pi C_{in} R'_{sig}} \text{ where}$$

$$R'_{sig} = R_{sig} \parallel R_G = 0.1 \text{ M} \parallel 8.25 \text{ M}\Omega$$

$$R'_{sig} \approx 0.1 \text{ M}\Omega$$

$$C_{in} = C_{gs} + C_{gd}(1 + g_m (r_o \parallel R_D \parallel R_L))$$

$$C_{in} = 1 + 0.2(1 + 1(100 \text{ K} \parallel 4.7 \text{ K} \parallel 10 \text{ K}))$$

$$= 1.82 \text{ pF}$$

$$f_H = \frac{1}{2\pi \times 1.82 \times 10^{-12} \times 0.1 \times 10^6}$$

$$= 875 \text{ kHz}$$

8.32

$$I = 2 \text{ mA}, \beta = 100, f_T = 800 \text{ MHz}$$

$$R_B = 50 \text{ k}\Omega, R_C = 4 \text{ k}\Omega, r_x = 50 \text{ }\Omega$$

$$V_A = 100, C_\mu = 1 \text{ pF}, R_{sig} = 5 \text{ k}\Omega$$

$$R_L = 5 \text{ k}\Omega$$

$$g_m = \frac{2 \text{ mA}}{25 \text{ mV}} = 80 \text{ mA/V}$$

$$r_\pi = \frac{B_O}{g_m} = \frac{100}{80 \text{ mA}} = 1250 \text{ }\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{2 \text{ mA}} = 50 \text{ k}\Omega$$

$$C_\pi + C_\mu = \frac{g_m}{\omega_T} = \frac{80 \times 10^{-3}}{2\pi \times 800 \times 10^6} = 16 \text{ pF}$$

$$C_\mu = 1 \text{ pF} \Rightarrow C_\pi = 15 \text{ pF}$$

$$A_M = \frac{-R_B}{R_B + R_{sig}} \cdot \frac{r_\pi \times g_m R'_L}{(r_\pi + r_x + (R_B \parallel R_{sig}))}$$

$$\text{where } R'_L = r_o \parallel R_C \parallel R_L$$

$$= (50 \parallel 4 \parallel 5) \text{ k}\Omega$$

$$= 2.1 \text{ k}\Omega$$

$$A_M = -\frac{50}{50+5} \cdot \frac{1250 \times 168}{1250 + 50 + (50 \parallel 5) \text{ k}\Omega}$$

$$\text{where } 168 = g_m \times R'_L$$

$$= 80 \times 10^{-3} \times 2.1(10^3)$$

$$\text{Then: } A_M = -32.6$$

$$20 \log |A_M| = 30.3 \text{ dB}$$

$$C_{in} = C_\pi + C_\mu (1 + g_m R'_L)$$

$$= 15 + 1(1 + 168) = 184 \text{ pF}$$

$$R'_{sig} = r_\pi \parallel [r_x + (R_B \parallel R_{sig})]$$

$$= 1250 \parallel [50 + (50 \text{ K} \parallel 5 \text{ K})] = 983 \text{ }\Omega$$

$$f_H = \frac{1}{2\pi C_{in} R'_{sig}} = \frac{1}{2\pi \times 184 \times 10^{-12} \times 983}$$

$$= 880 \text{ kHz}$$

Gain-bandwidth product

$$GB = |A_M| \times f_H = 32.6 \times 880 \times 10^3$$

$$= 29 \times 10^6$$

Previously,


$$GB = 39 \times 754 \times 10^3 = 29 \times 10^6$$

Thus, the designer traded gain for bandwidth by increasing \$I\$. However, by doubling \$I\$ the dissipation increased by a factor of 2, since:

$$\text{Power} = \frac{I}{2I'} \times \text{Vs supply}$$

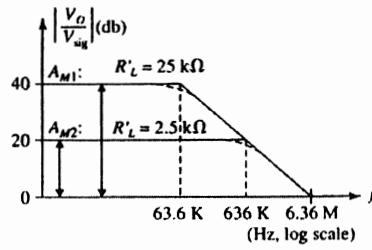8.33

$$\begin{aligned}
 R_B &>> R_{sig}, r_X \ll R_{sig} \\
 R_{sig} &>> r_\pi, g_m R_L >> 1, \\
 g_m R_L C_\mu &>> C\pi \\
 f_H &= \frac{1}{2\pi \times 10^{-12} \times 100 \times 2.5(10^3)} \\
 f_H &= 636 \text{ KHz}
 \end{aligned}$$



$$GP = 6.36 \times 10^6 = A_M \times f_H$$

when  $A_M = 1 \Rightarrow f_H = 6.36 \cdot 10^6 \text{ Hz}$

$$R_L' = \frac{1}{2\pi(6.36 \times 10^6)C_\mu \times \beta}$$

$$C_\mu = 1 \times 10^{-12}$$

$$\beta = 100$$

$$R_L' = 250 \Omega$$

8.34

$$R_{in} = R_1 \parallel R_2 \parallel r_\pi$$

$$\text{where } r_\pi = \frac{\beta}{g_m} \text{ and } g_m = \frac{I_C}{V_T}$$

$$g_m = \frac{0.8}{0.025} = 32 \text{ mA/V}$$

$$r_\pi = \frac{200}{32} = 6.25 \text{ k}\Omega$$

$$R_{in} = 68 \parallel 27 \parallel 6.25 = 4.72 \text{ k}\Omega$$

$$R_L = R_C \parallel R_L = 4.7 \parallel 10 = 3.2 \text{ k}\Omega$$

$$\begin{aligned}
 A_M &= \frac{R_{in}}{R_S + R_{in}} \times -g_m R_L \\
 &= \frac{-4.72}{10 + 4.72} \times 32 \times 3.2 \\
 &= -32.8 \text{ V/V}
 \end{aligned}$$

$$C_T = C\pi + C\mu (1 + g_m R_L)$$

$$\begin{aligned}
 \text{where } C\pi + C\mu &= \frac{g_m}{2\pi f_T} = \frac{32 \times 10^{-3}}{2\pi \times 10^3} \\
 &= 5.1 \text{ pF}
 \end{aligned}$$

$$C\pi = 5.1 - 0.8 = 4.3 \text{ pF}$$

$$C_T = 4.3 + 0.8 (1 + 32 \times 3.2)$$

$$= 87 \text{ pF}$$

The resistance seen by  $C_T$  is  $R_T$ .

$$\begin{aligned}
 R_T &= r_\pi \parallel R_1 \parallel R_2 \parallel R_3 \\
 &= 6.25 \parallel 68 \parallel 27 \parallel 10 = 3.2 \text{ k}\Omega
 \end{aligned}$$

Thus

$$\begin{aligned}
 f_H &\equiv \frac{1}{2\pi C_T R_T} \\
 &= \frac{1}{2\pi \times 87 \times 10^{-12} \times 3.2 \times 10^3} \\
 &= 572 \text{ KHz}
 \end{aligned}$$

8.35

$$I_C \approx 2 \text{ mA}, f_T = 2 \text{ GHz}, C\mu = 1 \text{ pF},$$

$$r_X = 100 \Omega, \beta_O = 120, R_{sig} = 0$$

$$g_m = \frac{I_C}{V_T} = \frac{2}{25} = 80 \text{ mA/V}$$

$$r_\pi = \frac{\beta_O}{g_m} = \frac{120}{0.08} = 1.5 \text{ k}\Omega$$

$$f_H = \frac{g_m}{2\pi(C_\pi + C\mu)} \Rightarrow 2 \times 10^9$$

$$= \frac{0.08 \times 10^{12}}{2\pi(C_\pi + 1)} \Rightarrow C_\pi = 5.4 \text{ pF}$$

a) If  $A_M = -10 \text{ V/V}$

$$\text{If } R_{sig} = 0: A_M = \frac{-r_\pi}{r_\pi + r_A} \cdot g_m \cdot R_L$$

$$-10 = \frac{-1.5}{1.5 + 0.1} \cdot 0.08 \times R_L = 133.3 \Omega.$$

$$\begin{aligned}
 C_{in} &= C_\pi + C\mu(1 + g_m R_L) \\
 &= 5.4 + 1(1 + 0.08 \times 133.3) \\
 &= 17 \text{ pF}
 \end{aligned}$$

$$\text{Thus } f_H = \frac{1}{2\pi \cdot C_{in} (R_L)}$$

$$= \frac{1}{2\pi \cdot 17 \times 10^{-12} \times 133.3} = 70.2 \text{ MHz}$$

b)  $A_M = (-1 \text{ V/V})$

$$\Rightarrow R_L = 13.3 \Omega$$

$$C_{in} = 7.5 \text{ pF}$$

$$f_H = 1.6 \text{ GHz}$$

$$g_m = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V}$$

$$r_\pi = \frac{\beta_O}{g_m} = \frac{100}{20 \text{ mA/V}} = 5 \text{ k}\Omega$$

$$8.36 \frac{V_A}{I_C} = \frac{100 \text{ V}}{0.5 \text{ mA}} = 200 \text{ k}\Omega$$

$$C\pi + C\mu = \frac{g_m}{\omega_T} = \frac{20 \times 10^{-3}}{2\pi \times 800 \times 10^6} = 4 \text{ pF}$$

Since  $C\mu = 1 \text{ pF} \rightarrow C\pi = 3 \text{ pF}$

The midband voltage gain is:

$$A_M = \frac{-R_B}{R_B + R_{sig}}$$

$$\frac{r_\pi}{r_\pi + r_e + (R_B \parallel R_{sig})} \cdot g_m \cdot R_L$$

$$\text{with } R_L' = r_o \parallel R_e \parallel R_L$$

$$= (200 \parallel 8 \parallel 5) \text{ k}\Omega = 3 \text{ k}\Omega$$

$$\text{Then } g_m R_L' = 20 \times 3 = 60 \text{ V/V}$$

$$\begin{aligned} A_M &= \frac{-100}{100+5} \cdot \frac{5}{5+0.05+(100 \parallel 5)} \times 60 \\ &= -29.1 \text{ V/V or } 29.3 \text{ dB} \end{aligned}$$

To determine  $f_H$ :

$$C_{in} = C_\pi + C\mu (1 + g_m R_L')$$

$$= 4 + 1 \cdot (1 + 60) = 65 \text{ pF}$$

$$R'_{sig} = r_\pi \parallel [r_e + (R_B \parallel R_{sig})]$$

$$= 5 \parallel [0.05 + (100 \parallel 5)] = 2.45 \text{ k}\Omega$$

$$\text{Thus, } f_H = \frac{1}{2\pi \cdot C_{in} \cdot R'_{sig}}$$

$$= \frac{1}{2\pi \times 65 \times 10^{-12} \times 2.45 \times 10^3} = 999 \text{ KHz}$$

$$GB = 29.1 \times 999 \times 10^3 = 29.1 \text{ MHz}$$

$$\text{In example 9.4: } A_M = -39 \text{ V/V,}$$

$$f_H = 754 \text{ KHz} \rightarrow GB = 29.4 \text{ MHz}$$

Notice how operation at lower supply voltage, thus  $I_C$  reduced the mid-band gain, increased the  $f_H$  while keeping the gain-band width product constant.

$$Z_i = \frac{1}{\left(g_m + \frac{1}{r_\pi}\right) + sC\pi}$$

$$= \frac{1}{\frac{1}{re} + sC\pi} = \frac{re}{1 + sC\pi r_e}$$

$$f_T = \frac{g_m}{2\pi(C\pi + C\mu)}$$

Since  $C\pi$  contains a component that is proportional to the bias current, it follows that at high currents  $C\pi \gg C\mu$ , and

$$f_T \approx \frac{g_m}{2\pi C\pi} = \frac{1}{2\pi \cdot C\pi \cdot r_e}$$

Thus,

$$Z_i = \frac{re}{1 + s/\omega_T} \text{ (at high currents)}$$

The phase angle will be  $-45^\circ$  at  $\omega = \omega_T$ , or

$$f = f_T = 400 \text{ MHz}$$

For a lower bias current so that  $C\pi = C\mu$ ,


$$f_T = \frac{1}{4\pi C\pi r_e} \text{ and } Z_i = \frac{r_e}{1 + \frac{s}{2\omega_T}}$$

$-45^\circ$  angle is obtained at  $\omega = 2\omega_T$  or

$$f = 2f_T = 800 \text{ MHz}$$

(Assuming  $f_T$  remains constant which is not necessarily true)


8.37

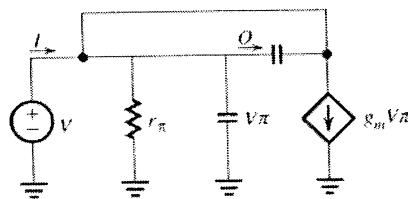

$$I = \frac{V}{r_\pi} + sC\pi V_\pi + g_m V_\pi$$

$$Y_{in} = \left( g_m + \frac{1}{r_\pi} \right) + sC\pi$$

This figure is for 8.38

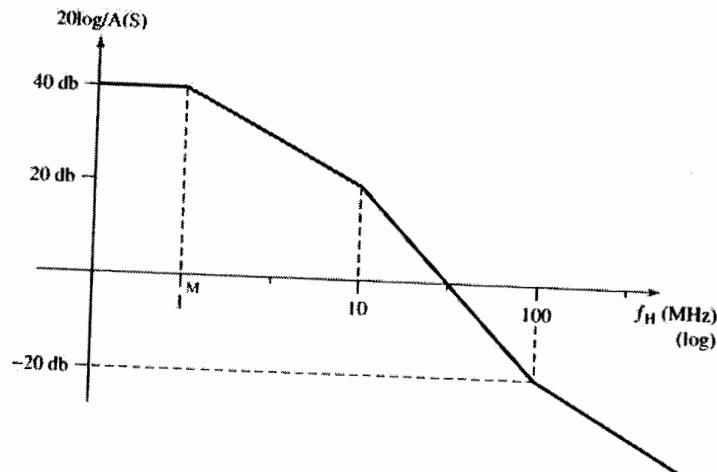

### 8.38

$$40 \text{ dB} = 20 \log A_o \Rightarrow A_o = 100 \text{ V/V}$$

$$A(s) = +100 \frac{(1+s/100 \times 10^6 \times 2\pi)}{\left(1+\frac{s}{2\pi \times 10^7}\right)\left(1+\frac{s}{2\pi \times 10^6}\right)}$$

$$A(s) = +100 \frac{\left(1+\frac{s}{2\pi \times 10^8}\right)}{\left(1+\frac{s}{2\pi \times 10^7}\right)\left(1+\frac{s}{2\pi \times 10^6}\right)}$$

$$\omega_B = \frac{1}{\sqrt{\left(\frac{1}{2\pi \times 10^7}\right)^2 + \left(\frac{1}{2\pi \times 10^6}\right)^2 - 2\left(\frac{1}{2\pi \times 10^8}\right)^2}}$$


$$f_H = 0.995 \text{ MHz}$$

### 8.39

a) Gain  $A = 60 \text{ dB} = 1000$

$$A(s) = \frac{1000}{\left(1+\frac{1}{2\pi \times 10 \times 10^3}\right)} = \frac{1000}{\left(1+\frac{1}{2\pi \times 10^4}\right)}$$


(b)

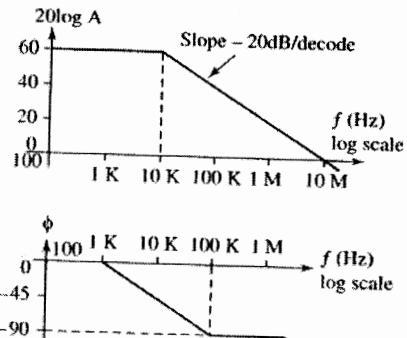

(c) Gain-bandwidth product  $= 1000 \times 10 \text{ K} \approx 10 \text{ MHz}$

(d) From the gain plot, unity gain frequency  $= 10 \text{ MHz}$

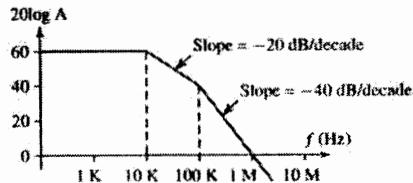(e) From the plot unity gain frequency  $= 1 \text{ MHz}$



8.40

$$f_H(s) = \frac{1}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$\omega_{p1} < \omega_{p2}$$

$$\text{using dominant-pole approximator: } \omega_H \approx \omega_{p1}$$

$$\text{using the root sum of squares formula:}$$

$$\omega_H = \frac{1}{\sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2}}} = \frac{\omega_{p1}}{\sqrt{1 + \left(\frac{\omega_{p1}}{\omega_{p2}}\right)^2}}$$

The difference between the two estimates for  $\omega_H$  is:

$$\Delta\omega_H = \omega_{p1} - \frac{\omega_{p1}}{\sqrt{1 + \left(\frac{\omega_{p1}}{\omega_{p2}}\right)^2}}$$

$$\text{If } n = \frac{\omega_{p2}}{\omega_{p1}}, \frac{\Delta\omega_H}{\omega_{p1}} = 1 - \frac{1}{\sqrt{1 + \frac{1}{n^2}}}$$

$$\text{for } \frac{\Delta\omega_H}{\omega_{p1}} = 10\% = 0.1 \Rightarrow n = 2.07$$

$$\text{for } \frac{\Delta\omega_H}{\omega_{p1}} = 1\% = 0.01 \Rightarrow n = 7.02$$

8.41

$$A(s) = -100 \frac{1 + 5/10^6}{(1 + 5/10^5)(1 + 5/10^7)}$$

$$\text{a) } \omega_H \approx 10^5 \text{ rad/s}$$

$$\text{b) } \omega_H \approx \frac{1}{\sqrt{\left(\frac{1}{10^5}\right)^2 + \left(\frac{1}{10^3}\right)^2 - 2\left(\frac{1}{10^5}\right)^2}} = 101 \text{ Krad/s}$$

If the pole at  $10^6 \text{ rad/s}$  is lowered to  $10^5 \text{ rad/s}$ , the transfer function becomes:

$$A(s) = \frac{-100}{1 + 5/10^2} \Rightarrow f_H = \frac{10^7}{2\pi} \text{ Hz}$$

8.42

$$30^\circ = 3 \tan^{-1} \frac{\omega}{\omega_p} = 3 \tan^{-1} \frac{10^6}{\omega_p} \Rightarrow \omega_p = 5.67 \times 10^6 \text{ rad/s}$$

8.43

$$\omega_H \approx \frac{1}{\tau_{gs} + \tau_{gd}} = \frac{1}{C_{gs} R_{gs} + C_{gd} R_{gd}}$$

$$\omega_H \approx \frac{1}{C_{gs} R' + C_{gd} (R' + R_L' + g_m R_L' R')} \quad (\text{From Example 6.6})$$

$$\text{For } C_{gs} = C_{gd} = 1 \text{ PF}, R_L' = 3.33 \text{ k}\Omega, g_m = 4 \text{ mA/V}$$

$$\omega_H = \frac{1}{10^{12} R' + 10^{12} (R' + 3.33 \times 10^3 + 4 \times 3.33 \times R')}$$

$$\text{To obtain } \omega_H = 2\pi \times 150 \times 10^3$$

$$2\pi \times 150 \times 10^3 = \frac{10^{12}}{3.33 \times 10^3 + 15.32 R'} \Rightarrow R' = 69.04 \text{ k}\Omega$$

$$R' = R // R_{in} = R // 4.20^K = 69.04 \Rightarrow R = 82.6 \text{ k}\Omega$$

8.44

$$\tau_H = \tau_{gs} + \tau_{gd}$$

$$\text{where: } \tau_{gs} = C_{gs} \cdot R_{gs} = C_{gs} (R_G \parallel R_{sig})$$

$$\tau_{gd} = C_{gd} \cdot R_{gd} = C_{gd} (R_{sig} + R_L + g_m R_L \cdot R_{sig})$$

$$\text{since } R_{sig} = R_G \parallel R_{sig}$$

$$\tau_{gs} = C_{gs} \cdot (R_G \parallel R_{sig})$$

$$\left[ 1 + \frac{R_L}{(R_G \parallel R_{sig})} + g_m R_L \right].$$

$$\Rightarrow \tau_H = (R_G \parallel R_{sig})$$

$$\left[ C_{gs} + C_{gd} \left[ 1 + g_m R_L + \frac{R_L}{R_G \parallel R_{sig}} \right] \right]$$

$$\tau_H = \frac{R_G \cdot R_{sig}}{R_G + R_{sig}}$$

$$\left[ C_{gs} + C_{gd} \left[ 1 + g_m R_L + R_L \frac{(R_G + R_{sig})}{R_G \cdot R_{sig}} \right] \right]$$

b)  $\tau = C_{in} \cdot R_{sig}$  where  $R_{sig} = R_G \parallel R_{sig}$  and  $C_{in} = C_{gs} + C_{eq}$  where  $C_{eq}$  is the result of applying miller's theorem to reflect  $C_{gd}$  to the gate-ground nodes.

From Eq 9.76:

$$Z_{eq} = \frac{Z}{1 - K} = \frac{1/s C_{gd}}{1 - (-g_m R_L)} \\ = \frac{1}{s C_{gd} (1 + g_m R_L)}$$

$$\Rightarrow C_{eq} = C_{gd} (1 + g_m R_L)$$

$$\text{Thus } \tau = (C_{gs} + C_{eq}(1 + g_m R_L)) \cdot \frac{R_G \cdot R_{sig}}{R_G + R_{sig}}$$

Evaluating for:  $R_G = 420 \text{ k}\Omega$

$$C_{gs} = C_{gd} = 1 \text{ pF} \quad R_L = 3.33 \text{ k}\Omega$$

$$R_{sig} = 100 \text{ k}\Omega \quad g_m = 4 \text{ mA/V}$$

(1) For the complete expression found in part a)

$$\tau_H = 1.230 \mu\text{s} \rightarrow \omega_H = 813 \text{ K rad/s}$$

(2) For the approximate expression found in part b)

$$\tau = 1.228 \mu\text{s} \rightarrow \omega_H = 814 \text{ K rad/s}$$

$$(\tau_H - \tau) \times 100/\tau = 0.163 \%$$

### 8.45

If a capacitor  $C_L$  is connected in parallel

$$\text{with } R_L \text{ then } \omega_H \cong \frac{1}{\tau_{gs} + \tau_{gd} + R_L \cdot C_L}$$

the values of  $\tau_{gs}$  and  $\tau_{gd}$  remain unaffected since

each is derived by setting the other capacitors to zero. When considering the resistances seen by  $C_L$ ,

$C_{gs} = C_{gd} = 0$  and  $V_{gs} = 0 \Rightarrow$  the open-circuit

time constant of  $C_L$  is:  $R_L \cdot C_L$

$$\Rightarrow \omega_H = \frac{1}{(80.8 + 1160) \times 10^{-9} + 3.33 \times 10^3 \cdot 20 \times 10^{-12}} \\ \omega_H = 765 \text{ K rad/s}$$

$$f_H = \omega_H / 2\pi = 121.7 \text{ MHz}$$

### 8.46

$$A_H = \frac{V_o}{V_i} = - \frac{R_{in}}{R_{in} + R} g_m R'_L = - \frac{1.2}{1.2 + 0.1} (2 \times 12) \\ A_H = - 22.2 V/V$$

$$R_{gs} = R_{in} \parallel R = 1.2 \parallel 0.1 = 92.3 \text{ k}\Omega$$

$$\tau_{gs} = R_{gs} C_{gs} = 1 \times 10^{-12} \times 92.3 \times 10^3 = 92.3 \text{ ns}$$

$$R_{gd} = R' + R'_L + g_m R'_L R' \text{ where } R' = R_{in} \parallel R = 92.3 \text{ k}\Omega$$

$$R_{gd} = 92.3 + 12 + 2 \times 12 \times 92.3 = 2.32 \text{ M}\Omega$$

$$\tau_{gd} = C_{gd} R_{gd} = 1 \times 10^{-12} \times 2.32 \times 10^6 = 2320 \text{ ns}$$

$$\omega_H = \frac{1}{\tau_{gs} + \tau_{gd}} = \frac{1}{(92.3 + 2320) \times 10^{-9}} = 414.5 \text{ Krad/s}$$


$$f_H = 66 \text{ kHz}$$

### 8.47

$$\text{a) } V_o = -g_m R_L V_{gs} \quad (1)$$

$$V_{gs} = V_{sig} - R_S \times g_m V_{gs}$$

$$V_{gs} (1 + g_m R_S) = V_{sig}$$

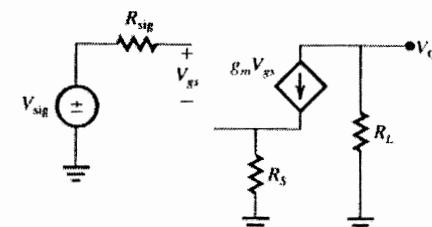

$$(1) \Rightarrow v_o = \frac{-g_m R_L}{1 + g_m R_S} v_{sig} \Rightarrow \frac{v_o}{v_{sig}} = \frac{-g_m R_L}{1 + g_m R_S}$$


$$\text{b) } V_S = (g_m V_X - i_X) R_S$$

$$V_G = V_S + V_X = (g_m V_X - i_X) R_S + V_X$$

$$\Rightarrow i_X = \frac{V_G}{R} = \frac{(1 + g_m R_S)}{R} V_X - i_X \frac{R_S}{R}$$

$$R_{gs} = \frac{V_X}{i_X} = \frac{1 + R_S/R}{1 + g_m R_S} = \frac{R + R_S}{1 + g_m R_S}$$

(R is  $R_{sig}$ )

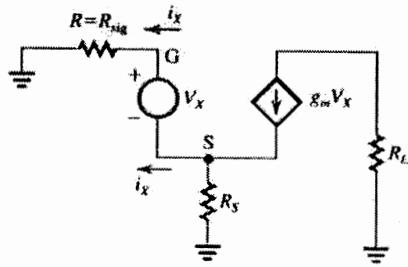


to calculate  $R_{gs}$ :

$$V_G = -Ri_X$$

$$\begin{aligned} V_S &= -Ri_X - V_{gs} \\ V_S &= R_S \times g_m V_{gs} \end{aligned}$$
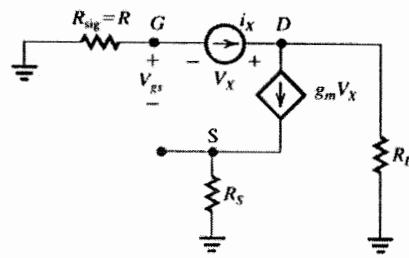
$$R_S g_m V_{gs} = -Ri_X - V_{gs} \Rightarrow V_{gs} = \frac{-Ri_X}{1 + g_m R_S}$$



$$\text{At } D: i_X = g_m V_{gs} + \frac{V_x - R_L i_X}{R_L}$$

$$\text{substitute } V_{gs}: i_X = -\frac{g_m R i_X}{1 + g_m R_S} + \frac{V_x - R_L i_X}{R_L}$$

$$i_X \left[ 1 + \frac{g_m R}{1 + g_m R_S} + \frac{R}{R_L} \right] = \frac{V_x}{R_L}$$

$$R_{gd} = \frac{V_x}{i_X} = R_L + R + \frac{g_m R R_L}{1 + g_m R_S} \quad (R \text{ is } R_{sig})$$

c)  $R_S = 0$ :

$$\frac{v_o}{v_{sig}} = \frac{-4 \times 5 \text{ K}}{1 + 4 \times 0} = -20 \text{ V/V}$$

$$R_{gs} = R_{sig} = 100 \text{ k}\Omega$$

$$R_{gs} = 5 \text{ K} + 100 \text{ K} + 4 \times 5 \times 100 = 2105 \text{ k}\Omega$$

$$\omega_H \approx \frac{1}{C_{gs} R_{gs} + C_{gd} R_{gd}}$$

$$\approx \frac{1}{10^{-12} \times 100 \times 10^3 + 10^{-12} \times 2105 \times 10^3}$$

$$\omega_H \approx 453.5 \text{ K rad/s}$$

$$|\text{Gain|} \times \text{Bandwidth} = 20 \times 453.5$$

$$= 9.07 \text{ M rad/s}$$

$$R_S = 100 \text{ }\Omega:$$

$$\frac{v_o}{v_{sig}} = \frac{-4 \times 5}{1 + 4 \times 0.1} = -14.3 \text{ V/V}$$

$$R_{gs} = \frac{100 + 0.1}{1 + 4 \times 0.1} = 71.5 \text{ k}\Omega$$

$$R_{gd} = 5 + 100 + \frac{4 \times 5 \times 100}{1 + 4 \times 0.1} = 1533.6 \text{ k}\Omega$$

$$\omega_H = \frac{1}{10^{-12} \times 71.5 \times 10^3 + 10^{-12} \times 1533.6 \times 10^3} = 623 \text{ K rad/s}$$

$$|\text{Gain|} \times \text{Bandwidth}$$

$$= 14.3 \times 623 \text{ K} = 8.91 \text{ M rad/s}$$

$$R_S = 250 \text{ }\Omega:$$

$$\frac{v_o}{v_{sig}} = \frac{-4 \times 5}{1 + 4 \times 0.25} = -10 \text{ V/V}$$

$$R_{gs} = \frac{100 + 0.25}{1 + 4 \times 0.25} = 50.1 \text{ k}\Omega$$

$$R_{gd} = 5 + 100 + \frac{4 \times 5 \times 100}{1 + 4 \times 0.25} = 1105 \text{ k}\Omega$$

$$\omega_H = \frac{1}{10^{-12} \times 50.1 \times 10^3 + 10^{-12} \times 1105 \times 10^3} = 865.7 \text{ K rad/s}$$

$$|\text{gain|} \times \text{Bandwidth} = 10 \times 865.7 \text{ K}$$

$$= 8.66 \text{ M rad/s}$$

Summary table:

$R_S(\Omega)$	Gain (V/v)	W (K rad/s)	Gain.BW product (M rad/s)
0	-20	453.5	9.07
100	-14.3	623.0	8.91
250	-10	865.7	8.66

The Gain  $\times$  Bandwidth is approximately constant.

8.48

$$A_M = \frac{V_o}{V_{S, g}} = -\frac{R_{in}}{R_{in} + R_{sig}} (g_m R'_L) = -\frac{5}{5+1} (0.3 \times 10^6)$$

$A_M = 25 V/V$  Now refer to Example 6.6.

$$R_{gs} = R_{in} \parallel R_{sig} = 5 M\Omega \parallel 1 M\Omega = 0.83 M\Omega$$

$$T_{gs} = R_{gs} C_{gs} = 0.2 \times 10^{-12} \times 0.83 \times 10^6 = 166.7 \text{ ns}$$

$$\begin{aligned} R_{gd} &= R' + R'_L + g_m R'_L R' \\ R' &= R_{in} \parallel R_{sig} = 0.83 M\Omega \end{aligned} \Rightarrow R_{gd} = 0.83 + 0.1 + 0.83 \times 0.3 \times 100$$

$$R_{gd} = 25.92 M\Omega$$

$$T_{gd} = C_{gd} R_{gd} = 25.92 \times 10^6 \times 0.1 \times 10^{-12} = 2592 \text{ ns}$$

$$\omega_H = \frac{1}{T_{gs} + T_{gd}} = \frac{1}{(166.7 + 2592) \times 10^{-9}} = 362.5 \text{ rad/s}$$

$$f_H = 57.7 \text{ kHz}$$

8.49

IF we assume that capacitors are perfect open circuits for midband, then:

$$A_M = \frac{V_o}{V_{S, g}} = \frac{-R_{in}}{R_{in} + R_{sig}} (g_m R'_L) = \frac{-650}{650 + 150} (5 \times 10) = 40.6 V/V$$

$$C_{gs} = C_{gs} R_{gs} = C_{gs} (R_{in} \parallel R_{sig}) = 2 \mu F \times (150 \parallel 1650 \text{ k}\Omega)$$

$$T_{gs} = 243.75 \text{ ns}$$

$$T_{gd} = C_{gd} R_{gd} , \text{ Refer to Example 6.6}$$

$$\begin{aligned} R_{gd} &= R' + R'_L + g_m R'_L R' \\ R' &= 150 \text{ k}\Omega \parallel 1650 \text{ k}\Omega = 121.9 \text{ k}\Omega \end{aligned} \Rightarrow R_{gd} = 121.9 + 10 + 5 \times 10 \times 121.9$$

$$R_{gd} = 6.2 \text{ M}\Omega$$

$$T_{gd} = C_{gd} R_{gd} = 0.5 \mu F \times 6.2 \text{ M}\Omega = 3100 \text{ ns}$$

$$T_L = R'_L C_L = 10 \text{ k}\Omega \times 3 \mu F = 30 \text{ ns}$$

$$\omega_H = \frac{1}{T_{gs} + T_{gd} + T_L} = \frac{1}{30 + 3100 + 243.75} = 296.4 \text{ rad/s}$$

$$f_H = 47.2 \text{ kHz}$$

8.50

$$R_{in} = \frac{R}{1-Gain} = \frac{100}{1-0.95} = 2000 \text{ k}\Omega, 2 \text{ MHz}$$


$$8.51 \quad Z_I = Z/I_K \Rightarrow C_I = 0.1 \times (1 - (-1000))$$

$$\Rightarrow C_I = 100.1 \text{ pF}$$

$$C_0 = 0.1 \times \left(\frac{-1}{1000} + 1\right)$$

$$C_0 = 99.9 \text{ pF}$$

(using Miller's Theorem)

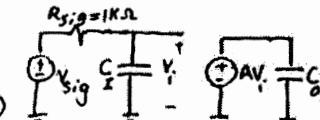

$$V_0 = AV_I = A \times V_{S, sig} \frac{1/C_{I,S}}{R_{S, sig} + 1/C_{I,S}} \Rightarrow \frac{V_0}{V_{S, sig}} = \frac{A}{1 + C_I R_{S, sig}}$$

$$\omega_H = \frac{1}{C_I R_{S, sig}} = \frac{1}{100.1 \times 10^3 \times 1000} = 9.99 \text{ rad/s} \Rightarrow f_H = 1.59 \text{ MHz}$$

To calculate unity gain frequency :

$$|Gain| = 1$$

$$\frac{V_0}{V_I} = \frac{A}{1 + C_I R_{S, sig} S} = \frac{-1000}{1 + 100.1 \times 10^3 S} \quad (S = j\omega)$$

$$\frac{1000}{\sqrt{1 + (100.1 \times 10^3 \times \omega)^2}} = 1 \Rightarrow \omega = 10 \text{ rad/s}$$

$$\text{As we can see } f_T \approx f_H \times A$$

### 8.52

Using Miller's Theorem, in each case the capacitance at the input is  $C(1-A)$  and the capacitance at the output is  $C\left(1 - \frac{1}{A}\right)$ .

Thus :

- a)  $A = -1000 \text{ V/v}$  and  $C = 1 \text{ pF}$   
 $C_i = 1.001 \text{ nF}$  and  $C_o = 1.001 \text{ pF}$
- b)  $A = -10 \text{ V/v}$  and  $C = 10 \text{ pF}$   
 $C_i = 110 \text{ pF}$  and  $C_o = 11 \text{ pF}$
- c)  $A = -1 \text{ V/v}$  and  $C = 10 \text{ pF}$   
 $C_i = 20 \text{ pF}$  and  $C_o = 20 \text{ pF}$
- d)  $A = 1 \text{ V/v}$  and  $C = 10 \text{ pF}$   
 $C_i = 0 \text{ pF}$  and  $C_o = 0 \text{ pF}$
- e)  $A = 10 \text{ V/v}$  and  $C = 10 \text{ pF}$   
 $C_i = -90 \text{ pF}$  and  $C_o = 9 \text{ pF}$

In (e) the negative capacitance at the input can be used to cancel the effect of the input capacitance of the amplifier.


### 8.53

$$\text{a) } R_{in} = \frac{R}{1-A} = \frac{R}{1-2} = -R$$

(Miller's theorem)

$$\text{b) } I_N = \frac{V_{sig}}{R_{sig}}$$

$$R_N = R_{sig} \parallel R_{in}$$

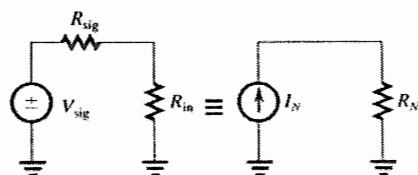


If  $R_{sig} = R$  then :

$$R_N = R \parallel (-R) = \infty \Rightarrow I_L = I_N$$

$$= \frac{V_{sig}}{R_{sig}} = \frac{V_{sig}}{R}$$

c)

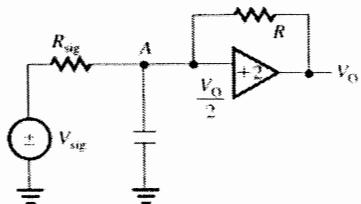

KCL at A:

$$\frac{V_O - V_{sig}}{R_{sig}} + \frac{v_O}{2} \times C_S + \frac{-v_O}{2R} = 0$$

$$\text{If } R_{sig} = R \Rightarrow \frac{v_O - V_{sig}}{R} = \frac{v_O}{2} C_S \Rightarrow \frac{v_O}{v_{sig}} = \frac{2}{RC_S}$$

### 8.54

$$A_M = -g_m R'_L = -5 \times 20 = -100 \text{ V/V}$$

$$C_{in} = C_{gs} + C_{gd}(1+g_m R'_L) \quad (\text{Eq. 6.55})$$

$$C_{in} = 2 + 0.1(1+5 \times 20) = 12.1 \text{ pF}$$

$$f_H \leq \frac{1}{2\pi C_{in} R_{sig}} \quad (\text{Eq. 6.54})$$

$$f_H \leq \frac{1}{2\pi \times 12.1 \times 10^{-12} \times 20k} = 658 \text{ kHz}$$

### 8.55

$$T_H = C_{gs} R_{gs} + C_{gd} R_{gd} + C_L R_{CL}$$

$$T_H = C_{gs} R_{sig} + C_{gd}[R_{sig}(1+g_m R'_L) + R'_L] + C_L R'_L$$

$$T_H = 2^P \times 20^k + 0.1[20^k(1+5 \times 20) + 20] + 1^P \times 20^k$$

$$T_H = 264 \text{ ns}$$

$$f_H \leq \frac{1}{2\pi T_H} = 603 \text{ kHz}$$

$$A_M = -g_m R'_L = -5 \times 20 = -100 \text{ V/V}$$

$$C_{gs} : 15.1\%$$

$$C_{gd} : 77.3\% \quad \text{Contribution of each time-constant to the overall } T_H.$$

$$C_L : 7.6\%$$

If we compare  $f_H$  to the one obtained in Problem 6.66, we notice that Problem 6.66 has a larger  $f_H$  due to neglecting the time constants of  $C_L$  and  $C_{gs}$ .

8.56

$$\Rightarrow f_2 = \frac{g_m}{2\pi C_{gd}} = \frac{5m}{2\pi \times 0.1^p} = 7.96 \text{ GHz}$$

$f_{p_1}$  and  $f_{p_2}$  are the poles of the transfer function of equation (6.60), whose denominator is a quadratic polynomial with coefficient of  $s$ :

$$\begin{aligned} &= [C_{gs} + C_{gd}(1+g_m R'_L)] R_{sig} + (C_L + C_{gd}) R'_L \\ &= [2 + 0.1(1+5 \times 20)] 20 + (1+0.1) \times 20 \\ &= 264 \text{ ns} = 264 \times 10^{-9} \text{ sec} \end{aligned}$$

Coefficient of  $s^2$ :

$$\begin{aligned} &= [(C_L + C_{gd}) C_{gs} + C_L C_{gd}] R_{sig} R'_L \\ &= [(1+0.1) 2 + 1 \times 0.1] 20 \times 20 = \\ &= 920 \times 10^{-18} (\text{sec})^2 \end{aligned}$$

Therefore the quadratic equation is:

$$1 + 264 \times 10^{-9} s + 920 \times 10^{-18} s^2 = 0$$

Denoting the frequencies of the roots of this equation with  $\omega_{p_1}$  and  $\omega_{p_2}$ , we have:

$$\begin{aligned} \omega_{p_1} = 3.84 \times 10^6 \text{ rad/s} &\rightarrow f_{p_1} = \frac{\omega_{p_1}}{2\pi} = 611.15 \text{ kHz} \\ \omega_{p_2} = 283.12 \times 10^6 \text{ rad/s} &\rightarrow f_{p_2} = \frac{\omega_{p_2}}{2\pi} = 45.06 \text{ MHz} \end{aligned}$$

Since  $f_{p_1} \ll f_{p_2}$  and  $f_{p_1} \ll f_2$ , a good estimate for  $f_H$  is  $f_{p_1}$ :

$$f_H \approx f_{p_1} = 611.15 \text{ kHz}$$

Approximate value of  $f_{p_1}$  obtained using (Eq. 6.66) is:

$$\begin{aligned} f_{p_1} &= \frac{1}{2\pi [(C_{gs} + C_{gd}(1+g_m R'_L)) R_{sig} + (C_L + C_{gd}) R'_L]} \\ f_{p_1} &= 603.16 \text{ kHz} \end{aligned}$$

Approximate value of  $f_{p_2}$  obtained using (Eq. 6.67) is:

$$\begin{aligned} f_{p_2} &= \frac{[C_{gs} + C_{gd}(1+g_m R'_L)] R_{sig} + (C_L + C_{gd}) R'_L}{2\pi [(C_L + C_{gd}) C_{gs} + C_L C_{gd}] R'_L R_{sig}} \\ f_{p_2} &= 45.67 \text{ MHz} \end{aligned}$$

The estimate of  $f_{p_1}$  using Eq. 6.66 is 1.3% lower than the exact value, while the estimate of  $f_{p_2}$  is about 1.3% higher than its exact value.

8.57

$$\begin{aligned} R'_L &= 5 \text{ k}\Omega \\ A_H &= -g_m R'_L = -5 \times 5 = -25 \text{ V/V} \end{aligned}$$

$$\begin{aligned} f_{p_1} &= \frac{1}{2\pi [C_{gs} + C_{gd}(1+g_m R'_L) R_{sig} + (C_L + C_{gd}) R'_L]} \\ f_{p_1} &= \frac{1}{2\pi [(2 + 0.1 \times (1+5 \times 5)) 20 + (1+0.1) \times 5]} \\ f_{p_1} &= 1.63 \text{ MHz} \end{aligned}$$

$$\begin{aligned} f_{p_2} &= \frac{[C_{gs} + C_{gd}(1+g_m R'_L)] R_{sig} + (C_L + C_{gd}) R'_L}{2\pi [(C_L + C_{gd}) C_{gs} + C_L C_{gd}] R'_L R_{sig} \times 2\pi} \\ f_{p_2} &= \frac{(2 + 0.1 \times (1+5 \times 5)) 20 + (1+0.1) 5}{((1+0.1) \times 2 + 1 \times 0.1) 5 \times 20 \times 2\pi} \end{aligned}$$

$$f_{p_2} = 67.5 \text{ MHz}$$

$$S_R = \frac{g_m}{C_{gd}} \Rightarrow f_2 = \frac{g_m}{2\pi C_{gd}} = \frac{5m}{2\pi \times 0.1^p} = 7.96 \text{ GHz}$$

$f_{p_1} \ll f_{p_2}$  and  $f_{p_1} \ll f_2 \Rightarrow f_{p_1}$  is the dominant pole.

$$f_H = f_{p_1} = 1.63 \text{ MHz}$$

$$\text{Gain} \times \text{Bandwidth} = 25 \times 1.63 = 40.75 \text{ MHz}$$

$$f_L = |A_M|/f_H = 40.75 \text{ MHz}$$

Since  $f_{p_1} \ll f_{p_2}$  and  $f_{p_1} \ll f_z$ , a dominant pole exists.

$$R'_L = 10 \text{ k}\Omega$$

$$A_M = -5 \times 10 = -50 \text{ V/V}$$

$$f_{p_1} = \frac{1}{2\pi[(2+0.1(1+5 \times 10))20 + (1+0.1) \times 10]} = 1.04 \text{ MHz}$$

$$f_{p_2} = \frac{(2+0.1(1+5 \times 10))20 + (1+0.1) \times 10}{[(1+0.1)2 + 1 \times 0.1]10 \times 20 \times 2\pi} = 52.96 \text{ MHz}$$

$$f_z = \frac{5}{2\pi \times 0.1} = 7.96 \text{ GHz}$$

$f_{p_1} \ll f_{p_2}$  and  $f_{p_1} \ll f_z$   $\Rightarrow f_{p_1}$  is the dominant pole and therefore  $f_H \approx f_{p_1} = 1.04 \text{ MHz}$

$$|A_M| \cdot f_H = 50 \times 1.04 = 52 \text{ MHz}$$

Since  $f_{p_2}$  is still slightly greater than  $|A_M| \cdot f_H$ , therefore:

$$R'_L = 20 \text{ k}\Omega$$

$$A_M = -5 \times 20 = -100 \text{ V/V} , \text{ from Problem 6.68 we have}$$

$$f_{p_1} = 603.16 \text{ kHz}$$

$$f_{p_2} = 45.67 \text{ MHz}$$

$$f_z = 7.96 \text{ GHz}$$

Again  $f_{p_1} \ll f_{p_2}$  and  $f_{p_1} \ll f_z$ , therefore  $f_{p_1}$  is the dominant pole and  $f_H$  can be approximated by  $f_{p_1}$ .  $f_H \approx f_{p_1} = 603.16 \text{ kHz}$

$$|A_M| \cdot f_H = 60.32 \text{ MHz}$$

Since  $f_{p_2} < |A_M| \cdot f_H$ , therefore  $f_T$  is smaller than  $|A_M| \cdot f_H$

The results are summarized in this table:

$R'_L$	$5 \text{ k}\Omega$	$10 \text{ k}\Omega$	$20 \text{ k}\Omega$
$A_M (\text{V/V})$	-25	-50	-100
$f_{p_1} (\text{MHz})$	1.63	1.04	0.60
$ A_M  \cdot f_H (\text{MHz})$	40.75	52.00	60.32

$$8.58 \quad A_M = -\frac{r_\pi}{R_{\text{sig}} + r_x + r_\pi} (g_m R'_L)$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{20} = 5 \text{ k}\Omega \Rightarrow A_M = -\frac{5}{1 + 0.2 + 5} (20 \times 5)$$

$$A_M = 80.65 \text{ V/V}$$

Using Miller's Theorem and Eq. 6.71:

$$C_{in} = C_\pi + C_\mu (1 + g_m R'_L) = 10 + 0.5(1 + 20 \times 5) = 60.5 \text{ pF}$$

$$\text{Eq. 6.69: } R'_{sig} = r_\pi \parallel (R_{\text{sig}} + r_x) = 5 \parallel (1 \parallel 0.2)$$

$$R'_{sig} = 0.97 \text{ k}\Omega$$

$$\text{Eq. 6.72: } f_H = \frac{1}{2\pi C_{in} R'_{sig}} = \frac{1}{2\pi \times 60.5 \times 0.97} \Rightarrow$$

$$f_H = 2.71 \text{ MHz}$$

8.59

$$A_u = -139 \text{ V/V}$$

Using the method of open-circuit time constants, from equation 9.100:

$$r_H = C_\pi \cdot R'_{sig} + C_\mu [(1 + g_m R'_L) \cdot R'_{sig} + R'_L] + C_L \cdot R'_L$$

$$R'_{sig} = r_\pi \parallel (R_{\text{sig}} + r_x)$$

$$= 2.5 \text{ k}\Omega \parallel (1 \text{ k}\Omega + 0.1 \text{ k}\Omega) = 764 \Omega$$

$$r_H = (10 \text{ p} \times 764) + 0.3 \text{ p} [(1 + 40 \times 5) \cdot 764 + 5 \text{ K}] + 3 \text{ p} \times 5 \text{ K}$$

$$\tau_H = 7.64 \text{ ns} + 47.57 \text{ ns} + 15 \text{ ns} = 70.21 \text{ ns}$$

$$f_H = \frac{1}{2\pi\tau_H} \approx 2.27 \text{ MHz}$$

The % contributions to  $\tau_H$  of each capacitance are:

$C_\pi$ : 10.8%,  $C_\mu$ : 67.8%,  $C_L$ : 21.4%

$f_H$  is 10.6% higher than the  $f_H$  obtained in this problem

8.60

$$A_H = -80.65 V/V, R'_{sig} = 0.97 k\Omega$$

$$f_2 = \frac{2m}{2\pi f_L} = \frac{20 m}{2\pi \times 0.5 P} = 6.37 \text{ GHz}$$

$$f_{P1} \approx \frac{1}{2\pi [(C_{\pi 1} + C_{\mu 1}(1 + g_m R'_L)) R'_{sig} + (C_{\pi 2} + C_{\mu 2}) R'_L]}$$

$$f_{P1} \approx \frac{1}{2\pi [(10 + 0.5(1 + 20 \times 5)) / 0.97 + 2.5 \times 5]}$$

$$f_{P1} = 2.24 \text{ MHz}$$

$$f_{P2} = \frac{(C_{\pi 1} + C_{\mu 1}(1 + g_m R'_L)) R'_{sig} + (C_{\pi 2} + C_{\mu 2}) R'_L}{2\pi [C_{\pi 1} C_{\pi 2} + C_{\mu 1} C_{\mu 2}] R'_{sig} R'_L}$$


$$f_{P2} = \frac{(10 + 0.5(1 + 20 \times 5)) / 0.97 + 2.5 \times 5}{2\pi [(10(2 + 0.5) + 2 \times 0.5) / 0.97 \times 5]}$$

$$f_{P2} = 89.89 \text{ MHz}$$

Since  $f_{P1} \ll f_{P2}$  and  $f_{P1} \ll f_2$ , we can approximate  $f_H$  by  $f_{P1}$ :  $f_H \approx f_{P1} = 2.24 \text{ MHz}$

If we compare  $f_H$  to the results obtained from applying Miller's Theorem, then our results are 17% lower.

8.61

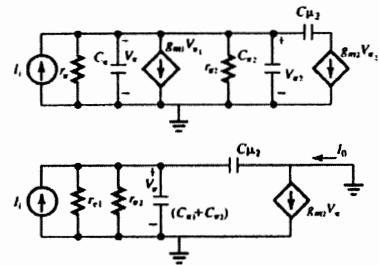

$$V_{\pi} = \frac{I_i}{\left(\frac{1}{r_{\pi 1}} + \frac{1}{r_{\pi 2}}\right) + s(C_{\pi 1} + C_{\pi 2} + C_{\mu 2})}$$

$$I_o = g_{m2} V_{\pi} - C_{\mu 2} V_{\pi} \\ = \frac{(g_{m2} - C_{\mu 2} s) I_i}{\left(\frac{1}{r_{\pi 1}} + \frac{1}{r_{\pi 2}}\right) + s(C_{\pi 1} + C_{\pi 2} + C_{\mu 2})}$$

$$\frac{I_o}{I_i} = \frac{g_{m2} - C_{\mu 2} s}{\left(\frac{1}{r_{\pi 1}} + \frac{1}{r_{\pi 2}}\right) + s(C_{\pi 1} + C_{\pi 2} + C_{\mu 2})}$$

$$I_{C1} = I_{C2} \Rightarrow r_{\pi 1} = r_{\pi 2},$$

$$g_{m1} = g_{m2}, C_{\pi 1} = C_{\pi 2}$$

$$\frac{I_o}{I_i} = \frac{g_m - C_{\mu} s}{\left(\frac{1}{r_e} + \frac{1}{r_{\pi}}\right) + (C_{\mu} + 2C_{\pi})s}$$

$$= \frac{1 - \frac{C_{\mu} s}{g_m}}{\left(\frac{1}{g_m r_e} + \frac{1}{g_m r_{\pi}}\right) + s \frac{C_{\mu} + 2C_{\pi}}{g_m}}$$

$$g_m r_e = \frac{I_C V_T}{V_T I_E} = \alpha = \frac{\beta}{\beta + 1}$$

$$g_m r_{\pi} = \beta$$

$$\Rightarrow \frac{I_o}{I_i} = \frac{1 - \frac{C_{\mu} s}{g_m}}{1 + \frac{1}{\beta} + \frac{1}{\beta} + s(2C_{\pi} + C_{\mu})/g_m}$$

$$\frac{I_o}{I_i} = \frac{1 - \frac{C_{\mu} s}{g_m}}{\frac{1}{1 + \frac{2}{\beta}} \frac{1 - \frac{C_{\mu} s}{g_m}}{1 + s \frac{(2C_{\pi} + C_{\mu})}{g_m (1 + \frac{2}{\beta})}}}$$

If the circuit is biased at 1 mA and  $\beta = \infty$ ,  $f_t = 400 \text{ MHz}$  and  $C_{\pi} = 2 \text{ pF}$ :

8 . 63

$$g_m = \frac{1}{0.025} = 40 \text{ mA/v}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} \Rightarrow C_\pi + C_\mu \\ = \frac{40 \text{ m}}{2\pi \times 400 \text{ M}} = 15.9 \text{ pF}$$

$$C_\pi = 15.9 - 2 = 13.9 \text{ pF}$$


Pole frequency :

$$f_P = \frac{g_m}{2\pi(2C_\pi + C_\mu)} = \frac{40 \times 10^{-3}}{2\pi(2 \times 13.9 + 2) \text{ pF}}$$

$$f_P = 213.74 \text{ MHz}$$

Zero frequency:
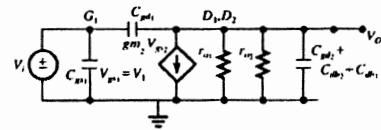
$$f_Z = \frac{g_m}{2\pi C_\mu} = \frac{40 \text{ m}}{2\pi \times 2 \text{ p}} = 3.18 \text{ GHz}$$



$$g_m = \sqrt{2\mu_n C_{Ox} \frac{W}{L} I_D} = \sqrt{2 \times 90 \times \frac{100}{1.6}}$$

$$= 1060 \text{ } \mu\text{A/v}$$

$$g_m = 1.06 \text{ mA/v}$$

$$r_{o1} = \frac{V_{A1}}{I_{D1}} = \frac{12.8}{0.1} = 128 \text{ k}\Omega$$

$$r_{o2} = \frac{|V_{A2}|}{|I_{D2}|} = \frac{19.2}{0.1} = 192 \text{ k}\Omega$$

$$\text{DC-gain} = -g_m (r_{o1} \parallel r_{o2})$$

$$= -1.06 \times (128 \parallel 192)$$

$$= -81.4 \text{ V/V}$$

Total capacitance between output node and ground

$$= C_{sd1} + C_{db1} + C_{db2} = 0.015 + 0.020 + 0.036$$

$$C_L = 0.071 \text{ pF}$$

Write a KCL at output:

$$sC_{sd1}(v_i - v_o) = g_m v_i + \frac{v_o}{r_{o1}} + \frac{v_o}{r_{o2}} + v_o sC_L$$

$$\frac{v_o}{v_i} = \frac{g_m - sC_{sd1}}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + (C_L + C_{sd1})s}$$

Thus:

$$f_Z = \frac{g_m}{2\pi C_{sd1}} = \frac{1.06 \text{ m}}{2\pi \times 0.015 \text{ p}} = 11.3 \text{ GHz}$$

$$f_P = \frac{\frac{1}{r_{o1}} + \frac{1}{r_{o2}}}{2\pi C_L \times C_{sd1}} = \frac{\frac{1}{128 \text{ k}\Omega} + \frac{1}{192 \text{ k}\Omega}}{2\pi(0.071 + 0.015) \text{ p}}$$

$$f_P = 24.1 \text{ MHz}$$

8 . 62

$$A_M = -g_m R'_L = -5 \times 20 = -100 \text{ V/V}$$

$$f_H = \frac{1}{2\pi(C_L + C_{jd})R'_L} = \frac{1}{2\pi(1+0.1) \times 20} = 7.23 \text{ MHz.}$$


(Note that in this case there is no Rsig and we used Eq. 6.79)

$$f_{3dB} = f_H = 7.23 \text{ MHz}$$


$$f_E | A_M |, f_H = 7.23 \text{ MHz}$$

8.64

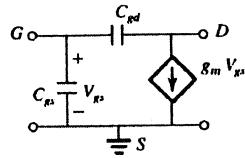
a) For small  $C_{gs}$  and low gain from G to D, we can neglect the Miller effect and  $C_{ss}$ .


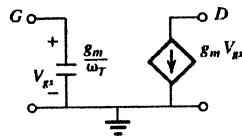
$$\omega_T = \frac{g_m}{C_{gs} + C_{ss}} \approx \frac{g_m}{C_{gs}} \text{ Thus } C_{ss} \approx \frac{g_m}{\omega_T}$$



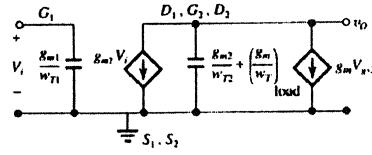b) replace the controlled source  $g_m v_{ds}$  with a resistance  $\frac{1}{g_m}$ . (source absorption theory)



$$V_o = -g_m v_i \frac{1}{g_{m2} + s \left( \frac{g_{m2}}{\omega_{T2}} + \frac{g_{mload}}{\omega_{Tload}} \right)}$$

Since the load device is identical to  $Q_1$ ,

$$g_{mload} = g_{m1} \text{ and } \omega_{Tload} = \omega_{T1} = \omega_T$$

Thus :

$$\frac{v_o}{v_i} = \frac{-g_{m1}/g_{m2}}{1 + \frac{s}{\omega_T} \left( 1 - \frac{g_{m1}}{g_{m2}} \right)}$$

$$\frac{g_{m1}}{g_{m2}} = \frac{\mu_n C_{ox} \left( \frac{W}{L} \right)_1 V_{ov}}{\mu_n C_{ox} \left( \frac{W}{L} \right)_2 V_{ov}} = \frac{W_1}{W_2}$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{-A_o}{1 + \frac{s}{\omega_T} (1 + A_o)}$$

$$\text{where } A_o = \frac{w_1}{w_2} = \frac{g_{m1}}{g_{m2}}$$

$$c) A_o = 3v/v, w_2 = 25\mu m$$

$$A_o = \frac{w_1}{w_2} \Rightarrow w_1 = 3 \times 25 = 75\mu m$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{w_1}{L_1} (V_{GS} - V_t)^2 = \frac{1}{2} \times 200\mu \times \frac{75}{0.5} \times 0.3^2$$

$$I_{D1} = 1.35mA$$


$$I_{D2} = \frac{1}{2} \times 200\mu \times \frac{25}{0.5} \times 0.3^2 = 0.45mA$$

Thus:

$$I = I_{D1} + I_{D2} = 1.35 + 0.45 = 1.8mA$$

$$f_{3db} = \frac{f_r}{1 + A_o} = \frac{12 \times 10^9}{1 + 3} = 3GHz$$

8.65

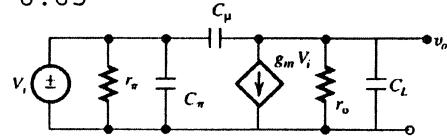

Writing a node equation at the output yields:

$$sC_\mu(v_i - v_o) = g_m \cdot v_i + \frac{v_o}{r_o} + v_o \cdot C_L \cdot s$$

$$\frac{v_o}{v_i} = \frac{C_\mu \cdot s - g_m}{\frac{1}{r_o} + (C_L + C_\mu)s}$$

$$= -g_m \cdot r_o \left[ \frac{1 - sC_\mu/g_m}{1 + s(C_L + C_\mu)r_o} \right]$$

For  $I_c = 200\mu A$ ,  $V_A = 100V$ :

$$g_m = \frac{200\mu}{0.025} = \frac{8mA}{V} \text{ and}$$

$$r_o = \frac{100}{200\mu} = 0.5M\Omega$$

Thus the DC-gain =  $-g_m \cdot r_o$

$$= -8 \times 0.5 \times 10^3 = -4000 V/V$$

For  $C_L = 1pF$ ,  $C_\mu = 0.2pF$

$$\omega_{3dB} = \frac{1}{(C_L + C_\mu)r_o} = \frac{1}{(1 + 0.2)p \times 0.5M}$$


$$= 1.67 \text{ M rad/s}$$

$$f_{\text{ss}} = f_H = 265.4 \text{ kHz}$$

$$f_Z = \frac{g_m}{2\pi \cdot C_{\mu}} = \frac{8 \text{ mA}}{2\pi \times 0.2 \text{ p}} = 6.4 \text{ GHz}$$

$$f_T = |A_0| \cdot f_H = 4000 \times 265.4 = 1.06 \text{ GHz}$$

Bode plot for  $|A|$ :  
 $4000 \text{ V/V} = 720 \text{ dB}$

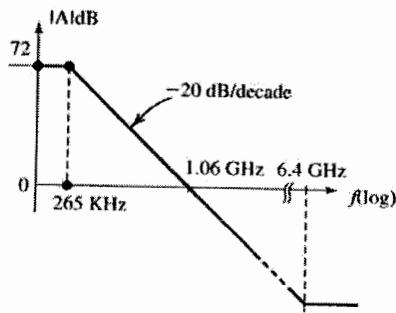

8.66

$$f_T = \frac{g_m}{2\pi(C_L + C_{gd})} \rightarrow g_m = 1 \text{ mA/V}, f_T = 26 \text{ Hz}$$

$$\Rightarrow C_L + C_{gd} = \frac{1 \times 10^3}{2\pi \times 2 \times 10^9} = 79.61 \text{ fF}$$

To have  $f_{T2} = 1 \text{ GHz}$ , we need:

$$C_L + C_{gd} = \frac{1 \times 10^3}{2\pi \times 1 \times 10^9} = 159.23 \text{ fF}$$

Thus we need an additional capacitance of

$$159.23 - 79.61 = \underline{\underline{79.61 \text{ fF}}}$$

8.67

$$f_H \approx f_{pi} = \frac{1}{2\pi C_{in} R_{sig}}, \text{ where}$$

$$R_{sig} = \frac{r_o}{2} = \frac{20 \text{ k}\Omega}{2} = 10 \text{ k}\Omega$$

$$C_{in} = C_{gs} + C_{gd}(1 + g_m R_L), \text{ where}$$

$$R_L = r_o \parallel r_o = \frac{r_o}{2} = 10 \text{ k}\Omega$$

$$\Rightarrow C_{in} = 0.1 \text{ p} + 0.1 \text{ p}(1 + 2 \times 10) = 2.2 \text{ pF}$$

$$\Rightarrow f_H = \frac{1}{2\pi \times 2.2 \text{ p} \times 10 \text{ K}} = 7.23 \text{ MHz}$$

i) If the bias current  $I$  is reduced by a factor of 4:

Since  $I_D \propto V_{ov}^2 \Rightarrow$  For  $I_D$  to reduce by 1/4,  $V_{ov}$  is reduced by 1/2

$$g_{mi} = \frac{2(I_D/4)}{(V_{ov}/2)} = \frac{1}{2} \left( \frac{2I_D}{V_{ov}} \right) = \frac{1}{2} \cdot 2 \text{ mA/V}$$

$$= 1 \frac{\text{mA}}{\text{V}}$$

$$r_{oi} = \frac{V_A}{I_D/4} = 4 \times \frac{V_A}{I_D} = 4 \times 20 \text{ k}\Omega = 80 \text{ k}\Omega$$

8.68

then:  $R_{sig} = R_L = \frac{r_o}{2} = \frac{80 \text{ k}\Omega}{2} = 40 \text{ k}\Omega$

$$C_{in} = 0.1 \text{ p} + 0.1 \text{ p}(1 + 1 \times 40) = 4.2 \text{ pF}$$

$$\Rightarrow f_H = \frac{1}{2\pi \times 4.2 \text{ p} \times 40 \text{ K}} = 0.95 \text{ MHz}$$

ii) if the bias current is increased by  $\times 4$ :

$\rightarrow V_{ov}$  is increased by a factor of 2.

$$g_{mi} = \frac{2(4 \times I_D)}{(2 \times V_{ov})} = 2 \left( \frac{2I_D}{V_{ov}} \right)$$

$$= 2 \times 2 \frac{\text{mA}}{\text{V}} = 4 \frac{\text{mA}}{\text{V}}$$

$$r_{oi} = \frac{V_A}{4 \times I_D} = \frac{1}{4} \left( \frac{V_A}{I_D} \right) = \frac{1}{4} \times 20 \text{ k}\Omega = 5 \text{ k}\Omega$$

then  $R_{sig} = R_L = r_{oi}/2 = 2.5 \text{ k}\Omega$

$$C_{in} = 0.1 \text{ p} + 0.1 \text{ p}(1 + 4 \times 2.5) = 1.2 \text{ pF}$$

$$f_H = \frac{1}{2\pi \times 1.2 \text{ p} \times 2.5 \text{ K}} = 53 \text{ MHz}$$

$$\tau_H = C_{gs} R_{gs} + C_{gd} R_{gd} + C_L \cdot R_{CL}$$

$$= C_{gs} \cdot R_{sig} + C_{gd} \cdot [R_{sig}(1 + g_m R_L) + R_L] + C_L \cdot R_L$$

Where  $R_{sig} = 100 \text{ k}\Omega$

$$R_L = 20 \text{ k}\Omega \parallel 12 \text{ k}\Omega = 7.5 \text{ k}\Omega$$

$$\Rightarrow \tau_H = 0.2 \text{ p} \times 100 \text{ K}$$

$$+ 0.2 \text{ p} [100 \text{ K}(1 + 1.5 \times 7.5) + 7.5 \text{ K}]$$

$$+ C_L \cdot R_L = 20 \text{ ns} + 246 \text{ ns} + C_L \cdot (7.5 \text{ K})$$

$$= 266 \text{ ns} + C_L \cdot (7.5 \text{ K})$$

8.70

$$\text{a) If } C_L = 0 \Rightarrow \tau_H = 266 \text{ ns} \rightarrow f_H = \frac{1}{2\pi\tau_H}$$

$$= 598 \text{ MHz}$$

$$\text{b) } C_L = 10 \text{ pF} \Rightarrow \tau_H = 341 \text{ ns} \rightarrow f_H = 467 \text{ MHz}$$

$$\text{c) } C_L = 50 \text{ pF} \Rightarrow \tau_H = 641 \text{ ns} \rightarrow f_H = 248 \text{ MHz}$$

Using the Miller approximation : Eq 9.80, 9.82

$$C_{in} = C_{gs} + C_{gd}(1 + g_m R_L)$$

$$= 0.2 \text{ p} + 0.2 \text{ p}$$


$$(1 + 1.5 \times 7.5) = 2.65 \text{ pF}$$

$$f_H = \frac{1}{2\pi \cdot C_{in} \cdot R_{sig}} = \frac{1}{2\pi \times 2.65 \text{ p} \times 100 \text{ K}}$$

$$= 600 \text{ MHz}$$

Notice how this result is close to case a) where  $C_L = 0$

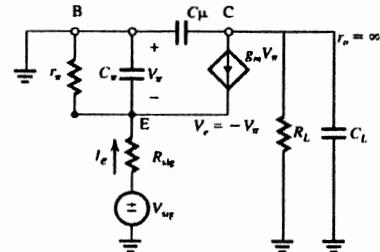and diverges further with increasing value of  $C_L$ , showing the importance of  $C_L$  in determining  $f_H$



We observe that  $V_r$ , voltage at the emitter, is equal to  $-V_u$ . We can write a node equation at the emitter:



$$I_e = -V_u \left( \frac{1}{r_\pi} + sC_\pi \right) - g_m \cdot V_u$$

$$= V_u \left( \frac{1}{r_\pi} + g_m + sC_\pi \right)$$

Thus, the input admittance looking into the emitter is:

$$\frac{I_e}{V_r} = \frac{1}{r_\pi} + g_m + sC_\pi = \frac{1}{r_\pi} + sC_\pi$$

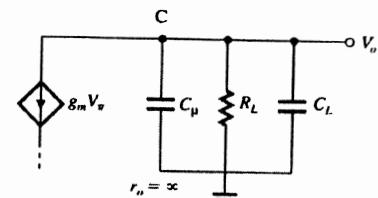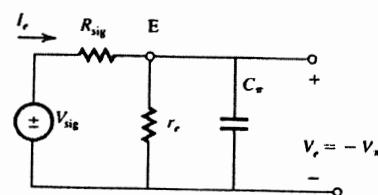Therefore we can replace the transistor at the input of the circuit by this admittance as shown below



a) As we can see above, the circuit can be separated into two parts, each with its own pole:

$$f_{p1} = \frac{1}{2\pi \cdot C_\pi (R_{sig} \parallel r_\pi)} \text{ (input side)}$$

$$f_{p2} = \frac{1}{2\pi (C_\mu + C_L) R_L} \text{ (output side)}$$

If we compare the poles for MOSFETs, we observe that these equations are their bipolar counterparts:

$$f_{P1} = \frac{1}{2\pi \cdot C_s \left( R_{sig} \parallel \frac{1}{g_m} \right)} = 9.108$$

$$f_{P2} = \frac{1}{2\pi(C_{sd} + C_L)R_L} = 9.109$$

b) For  $C\pi = 14 \text{ pF}$ ,  $C_\mu = 2 \text{ pF}$ ,  $C_L = 1 \text{ pF}$ ,  $I_c = 1 \text{ mA}$

$$R_{sig} = 1 \text{ k}\Omega, R_L = 10 \text{ k}\Omega \Rightarrow g_m = \frac{1}{0.025} = 40 \frac{\text{mA}}{\text{V}}$$

Assuming  $\beta = 100$

$$f_{P1} = \frac{1}{2\pi \times 14 \text{ p} \left( 1 \text{ K} \parallel \frac{100}{4} \right)} = 15.9 \text{ MHz}$$

$$f_{P2} = \frac{1}{2\pi \times (2 \text{ p} + 1 \text{ p}) 10 \text{ K}} = 5.3 \text{ MHz}$$

$$f_T = \frac{g_m}{2\pi(C\pi + C_\mu)} = \frac{40 \text{ m}}{2\pi(14 \text{ p} + 2 \text{ p})} = 398.1 \text{ MHz}$$

$f_T \gg f_{P1}$  and  $f_T \gg f_{P2}$ .

### 8.71

$$\text{If } f_H = 300 \text{ MHz} \Rightarrow \tau_H = \frac{1}{2\pi f_H} = 530.5 \text{ ps}$$

$$\tau_H = C_{gs}R_{gs} + (C_{sd} + C_L)R_{sd}$$

From Example 9.12

$$C_{gs} = 20 \text{ fF}, R_{gs} = 1.38 \text{ k}\Omega, C_{sd} = 5 \text{ fF}, R_{sd} = 18.7 \text{ k}\Omega$$

$$\Rightarrow 530.5 \text{ p} = 20 \text{ f} \times 1.38 \text{ K} + (5 \text{ p} + C_L) \times 18.7 \text{ K}$$

Thus  $C_L = 21.9 \text{ fF}$

Since the original  $C_L$  in Eq. 12 was 15 fF

$\Rightarrow$  We must add  $(21.9 - 15) = 6.9 \text{ fF}$  at the output to reduce  $f_H$  from 396 MHz to 300 MHz

### 8.72

$$R_O = 2r_O + (g_m r_O) r_O = 2 \times 50 \text{ k}\Omega + (1 \times 50) \times 50 \text{ k}\Omega = 2.6 \text{ M}\Omega$$

$$A_V = -g_m (R_O \parallel R_L) = -1 \text{ m} (2.6 \text{ M} \parallel 2 \text{ M}) = -1130 \frac{\text{V}}{\text{V}}$$

$$A_V = -1130 \frac{\text{V}}{\text{V}}$$

$$R_{in2} = \frac{r_O + R_L}{g_m r_O} = \frac{50 \text{ k}\Omega + 2 \text{ M}\Omega}{1 \times 50} = 41 \text{ k}\Omega$$

$$R_{d1} = r_O \parallel R_{in2} = 50 \text{ k}\Omega \parallel 41 \text{ k}\Omega = 22.5 \text{ k}\Omega$$

$$\tau_H = R_{sig} [C_{gs} + C_{sd}(1 + g_m R_{d1})] + R_{d1} (C_{sd} + C_{db} + C_{gs}) + (R_L \parallel R_o)(C_L + C_{db} + C_{sd})$$

$$\tau_H = 100 \text{ K} \times [30 \text{ f} + 10 \text{ f}(1 + 1 \times 22.5)] + 22.5 \text{ K} \times [10 \text{ f} + 10 \text{ f} + 30 \text{ f}] + (2 \text{ M} \parallel 2.6 \text{ M}) \times [40 \text{ f} + 10 \text{ f} + 10 \text{ f}]$$

$$\tau_H = 26.5 \text{ ns} + 1.125 \text{ ns} + 67.8 \text{ ns} = 95.42 \text{ ns}$$

$$f_H = \frac{1}{2\pi\tau_H} = 1.67 \text{ MHz}$$

### 8.73

$$a) A_M = -g_m R'_L = -5 \times (20^K \parallel 20^K) = -50 \frac{\text{V}}{\text{V}}$$

$$R_{gs} = R_{sig} = 20 \text{ k}\Omega$$

$$R_{gd} = R_{sig} (1 + g_m R'_L) + R'_L = 20^K (1 + 5 \times 20^K \parallel 20^K) + 20^K \parallel 20^K$$

$$R_{gd} = 10.30 \text{ k}\Omega = 1.03 \text{ M}\Omega$$

We use Eq. 6.57 :

$$\tau_H = C_{gs} R_{gs} + C_{gd} R_{gd} + C_L R'_L$$

$$\tau_H = 2^P \times 20^K + 0.2^P \times 10.30^K + 1^P \times (20^K \parallel 20^K) = 256 \text{ ns}$$

$$f_H = \frac{1}{2\pi\tau_H} = 62.2 \text{ kHz}$$

$$|A_M| \cdot f_H = 31.1 \text{ MHz}$$

b) For the cascode amplifier :

$$A_{v1} = g_m r_o = 5 \times 20 = 100 \text{ V/V}$$

$$A_{v2} = 1 + (g_{m2} + g_{mb2}) r_o = 1 + (5 + 0.2 \times 5) \times 20^k$$

$$A_{v2} = 121 \text{ V/V}$$

$$R_{out} = r_o + A_{v2} r_o = 20^k + (121 \times 20^k) = 2.44 \text{ M}\Omega$$

$$A_{vT} = A_{v2} \frac{R_L}{R_L + R_{out}} = -121 \times 100 \times \frac{20}{20 + 2.44 \times 10^6} = 98.4 \text{ V/V}$$

Using Eq. 6.137,

$$\tau_H = R_S \cdot g_m [C_{GS1} + C_{GD1}(1 + g_{m1} R_{d1})] + R_{d1} (C_{GD1} + C_{DS1} + C_{GS2}) + (R_L \parallel R_{out})(C_L + C_{GD2})$$

$$R_{d1} = r_o \parallel \left( \frac{1}{g_{m2} + g_{mb2}} + \frac{R_L}{A_{v2} r_o} \right)$$

$$R_{d1} = 20^k \parallel \left( \frac{1}{5 + 0.2 \times 5} + \frac{20}{121} \right) = 0.327 \text{ k}\Omega$$

$$\tau_H = 20^k [2 + 0.2(1 + 5 \times 0.327)] + 0.327 (0.2 + 0.2 + 1) + (20 \parallel 2.44 \text{ M})(1 + 0.2)$$

$$\tau_H = 75.1 \text{ ns}$$

$$f_H = \frac{1}{2\pi \tau_H} = 2.12 \text{ MHz}$$

$$|A_{vT}| \cdot f_H = 208.61 \text{ MHz}$$

### 8.74

$$A_V = 6.6 \text{ dB} = 1995 \text{ V/V}$$

$$A_{v1} = A_{v2} \frac{R_L}{R_L + R_{out}} \quad \text{and} \quad R_L = R_{out} \Rightarrow A_{v1} = A_{v2} = \frac{1}{2}$$

$$A_{v2} = (1 + g_{m2} r_o) g_m r_o \approx g_m^2 \approx \left( \frac{2ID}{V_{ov}} \cdot \frac{VA}{ID} \right) = \left( \frac{2VA}{V_{ov}} \right)^2$$

$$\Rightarrow 1995 = \frac{1}{2} \times \left( \frac{2 \times 10}{V_{ov}} \right)^2 \Rightarrow V_{ov} = 0.317 \text{ V}$$

$$\Rightarrow I_D = \frac{1}{2} g_m W \frac{V^2}{L} = \frac{1}{2} \times 200 \times 10^{-3} \times 10 \times 0.317^2 = 0.1 \text{ mA}$$

Since  $R_{sig}$  is small :

$$\tau_H \approx (C_L + C_{GD}) (R_L \parallel R_{out})$$

$$r_o = \frac{VA}{ID} = \frac{10}{0.1} = 100 \text{ k}\Omega \Rightarrow g_m = \frac{2ID}{V_{ov}} = 0.631 \text{ mA/V}$$

$$R_{out} = A_{v2} r_o + r_o = (1 + g_m r_o) r_o + r_o$$

$$R_{out} = 6510 \text{ k}\Omega = 6.5 \text{ M}\Omega \quad , \quad R_L = R_{out} .$$

$$\tau_H \approx (1 \text{ pF} + 0.1 \text{ pF}) \left( \frac{6510}{2} \right) = 3580.5 \text{ ns}$$

$$f_H = 44.5 \text{ kHz}$$

$$f_T \approx |A_{vT}| \cdot f_H = 1995 \times 44.5 = 88.8 \text{ MHz}$$

If the cascode transistor is removed, then we have a common-source configuration.

$$A_H = -g_m (r_o \parallel R_L) = -0.637 (100^k \parallel 6510^k)$$

$$A_H = -62.74 \text{ V/V}$$

$$f_H = \frac{1}{2\pi (C_L + C_{GD}) R_L'} = \frac{1}{2\pi (1 + 0.1)(100^k \parallel 6510^k)} = 1.47 \text{ MHz}$$

$$f_H = 1.47 \text{ MHz}$$

$$|A_H| \cdot f_H = 92.2 \text{ MHz} = f_T$$

Note that the unity-gain stays nearly unchanged. The result is the same as

### 8.75

$$R_{sig} = 4 \text{ k}\Omega, R_L = 2.4 \text{ k}\Omega,$$

$$I = 1 \text{ mA}, \beta = 100, r_o = 100 \text{ k}\Omega$$

$$A_M = -\frac{r_x}{r_x + r_s + R_{sig}} \times g_m (\beta r_o \parallel R_L)$$

$$r_x = \frac{\beta}{g_m} = \frac{100}{1/0.025} = 2.5 \text{ k}\Omega$$

$$g_m = \frac{I_C}{V_r} = 40 \text{ mA/V}$$

$$A_M = \frac{2.5}{2.5 + 0.05 + 4} \times 40 \times (100 \times 100 \parallel 2.4 \text{ K})$$

$$A_M = -36.6 \text{ V/V}$$

$$R_{sig} = r_x \parallel (r_s + R_{sig}) = 2.5 \text{ K} \parallel (0.05 + 4 \text{ K})$$

$$R_{sig} = 1.55 \text{ k}\Omega = R_{x1}$$

$$R_{\mu 1} = R_{sig} = (1 + g_m R_{x1}) + R_{x1}$$

$$R_{x1} = r_{o1} \parallel r_{o2} \left( \frac{r_o + R_L}{r_o + R_L / \beta + 1} \right)$$

$$= 100 \text{ K} \parallel \frac{100 \text{ K}}{101} \left( \frac{100 + 2.4}{100 + \frac{2.4}{101}} \right)$$

$$R_{x1} = 1 \text{ k}\Omega$$

$$R_{\mu 1} = 1.55(1 + 40 \times 1) + 1 = 64.55 \text{ k}\Omega$$

$$R_{out} = \beta \cdot r_o = 10 \text{ M}\Omega$$

$$\tau_H = C_{x1} R_{x1} + C_{\mu 1} R_{\mu 1} + (C_{CS1} + C_{x2}) R_{x1} + (C_L + C_{CS2} + C_{\mu 2})(R_L \parallel R_{out})$$

$$= 14 \times 1.55 + 2 \times 64.55 + (0 + 14)$$

$$\times 1 + (0 + 2)(2.4 \text{ K} \parallel 10 \text{ M})$$

$$\tau_H = 169.6 \text{ ns} \quad f_H = 939 \text{ kHz}$$

8.76

a) If we employ Miller's theorem to  $C_{\mu 1}$ :

$$\frac{1}{C_{\mu 1} S} \cdot \frac{1}{1-A} = \frac{1}{C_{\mu 1} S} \cdot \frac{1}{1-(-1)} = \frac{1}{2C_{\mu 1} S}$$

or  $2C_{\mu 1}$  appears in parallel with  $C_H$ . Thus the time constant due to  $(C_H + 2C_{\mu 1})$  is:

$R'_{sig}(C_H + 2C_{\mu 1})$  which results in:

$$f_{p1} = \frac{1}{2\pi R'_{sig}(C_H + 2C_{\mu 1})}$$

If we refer to Fig. 6.42, we'll see that the output pole is:  $f_{p2} = \frac{1}{2\pi(C_L + C_{c22} + C_{H2})R_L}$

$$b) R_{sig} = 1 \text{ k}\Omega \Rightarrow R'_{sig} = r_\pi || R_{sig} = \frac{100}{1/0.025} || 1 \text{ k}$$

$$\Rightarrow R'_{sig} = 0.714 \text{ k}\Omega$$

$$f_{p1} = \frac{1}{2\pi \times 0.714(5+2 \times 1)^2} = 31.85 \text{ MHz}$$

$$f_{p2} = \frac{1}{2\pi(0.714+1) \times 10} = 15.9 \text{ MHz}$$

(Assume  $R_L = 10 \text{ k}\Omega$ )

$$f_H = \frac{1}{\sqrt{(f_{p1})^2 + (f_{p2})^2}} = 14.2 \text{ MHz}$$

IF  $R_{sig} = 10 \text{ k}\Omega$ :

$$R'_{sig} = 2.5 \text{ k} \parallel 10 \text{ k} = 2 \text{ k}\Omega$$

$$f_{p1} = \frac{1}{2\pi(5+2)^2} = 11.4 \text{ MHz}$$

$f_{p2}$  is the same:  $f_{p2} = 15.9 \text{ MHz}$

$$f_H = 9.26 \text{ MHz}$$

$$f_H = 14.2 \text{ MHz}$$

8.77

$$g_m = \frac{I_C}{V_T} = \frac{0.1 \text{ mA}}{25 \text{ mV}} = \frac{4 \text{ mA}}{\text{V}}$$

$$r_\pi = \frac{B}{g_m} = \frac{100}{4} = 25 \text{ k}\Omega$$

$$R_{sig} = r_\pi = 25 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{0.1 \text{ mA}} = 1 \text{ M}\Omega$$

$$R_L = \beta \cdot r_o = 100 \text{ M}\Omega$$

$$f_T = \frac{1}{2\pi} \cdot \frac{g_m}{(C_\mu + C_\pi)} \Rightarrow C_\mu + C_\pi = \frac{g_m}{2\pi \cdot f_T}$$

$$\rightarrow C_\pi = \frac{4 \times 10^{-3}}{2\pi \times 10^9} - 0.1 \times 10^{-12} = 0.54 \text{ pF}$$

To obtain the DC-gain  $A_M$ :

$$A_M = \frac{-r_\pi}{r_\pi + R_{sig}} \cdot g_m (\beta r_o \parallel R_L)$$

$$R_{sig} = r_\pi R_L = \beta r_o$$

assuming  $r_\pi = 0$

$$A_M = \frac{-1}{2} \cdot g_m \times \frac{\beta r_o}{2}$$

$$= \frac{-1}{4} \times 4 \times 10^{-3} \times 100 \times 1 \times 10^6$$

$$A_M = -100 \text{ KV/V}$$

$$R_{sig} = r_\pi \parallel R_{sig} = \frac{r_\pi}{2} = 12.5 \text{ k}\Omega$$

$$R_{\pi 1} = R_{sig} = 12.5 \text{ k}\Omega$$

$$r_{e2} = r_e = \frac{r_\pi}{\beta + 1} = \frac{25 \text{ k}\Omega}{101} = 247 \text{ }\Omega$$

$$R_{C1} = r_o \parallel r_e \left( \frac{r_o + R_L}{r_o + \frac{R_L}{\beta + 1}} \right)$$

$$= 1 \text{ M} \parallel 247 \times \left( \frac{1 \text{ M} + 100 \text{ M}}{1 \text{ M} + \frac{100 \text{ M}}{101}} \right)$$

$$R_{C1} = 12.4 \text{ k}\Omega$$

$$R_{\mu 1} = R_{sig} (1 + g_m R_{C1}) + R_{C1}$$

$$= 12.5 \text{ K} (1 + 4 \times 12.4) + 12.4 \text{ k}\Omega$$

$$R_{\mu 1} = 645 \text{ k}\Omega$$

$$\Rightarrow \tau_H = C_{\pi 1} R_{\pi 1} + C_{\mu 1} R_{\mu 1} + C_{\pi 2} R_{C1}$$

$$+ C_{\mu 2} (R_L \parallel R_o)$$

where

$$R_o = \beta_2 \cdot r_{o2} = 100 \times 1 \text{ M}\Omega = 100 \text{ M}\Omega$$

$$\tau_H = 0.54 \text{ p} \times 12.5 \text{ K} + 0.1 \text{ p} \times 645 \text{ K} + 0.54 \text{ p}$$

$$\times 12.4 \text{ K} + 0.1 \text{ p} (100 \text{ M} \parallel 100 \text{ M})$$

$$\tau_H = 5.08 \text{ }\mu\text{s}$$

$$f_H = \frac{1}{2\pi\tau_H} = 31.3 \text{ KHz}$$

$$f_T = |A_M| \times f_H = 3.13 \text{ GHz}$$

8.78

$$a) I = \frac{1}{2} K' \frac{V_o^2}{R_L} = \frac{1}{2} \times 160 \times 100 \times (0.5)^2 = 2 \text{ mA}$$

$$b) g_m = \frac{2I_D}{V_{DS}} = 2 \times \frac{2}{0.5} = 8 \text{ mA/V}$$

$$g_{mb} = K g_m = 0.2 \times 8 = 1.6 \text{ mA/V}$$

$$r_0 = \frac{1}{\lambda I_D} = \frac{1}{0.05 \times 2} = 10 \text{ k}\Omega$$

$$A_{VO} = \frac{g_m r_0}{1 + g_m r_0 + g_{mb} r_0}$$

$$A_{VO} = \frac{8 \times 10}{1 + (8 + 1.6) \times 10} = 0.82 \text{ V/V}$$

If we use the approximation formula

$$A_{VO} = \frac{1}{1 + X} = 0.83 \text{ V/V}$$

$$R_0 = \frac{1}{g_m + g_{mb}} \parallel r_0 = \frac{1}{8 + 1.6} \parallel 10^4 = 103 \text{ }\Omega$$

c) with  $R_L = 1 \text{ k}\Omega$


$$A_{VO} = \frac{g_m R'_L}{1 + g_m R'_L}$$

$$R'_L = R_L \parallel r_0 \parallel \frac{1}{g_{mb}} = 1^4 \parallel 10^4 \parallel \frac{1}{1.6} = 370 \text{ }\Omega$$

$$A_{VO} = \frac{8 \times 370 \times 10^{-3}}{1 + 8 \times 0.370} = 0.75 \text{ V/V}$$

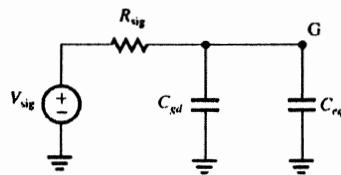8.79

Using the Miller approximation, the resulting input equivalent circuit is:



where  $C_{eq} = C_{ss} (1 - K)$

$$\text{and } K = \frac{g_m R_L}{1 + g_m R_L}$$

$$\Rightarrow C_{eq} = C_{ss} \left[ 1 - \frac{g_m R_L}{1 + g_m R_L} \right] \\ = C_{ss} \left[ \frac{1}{1 + g_m R_L} \right]$$

$$C_{in} = C_{rd} \parallel C_{eq} = C_{rd} + C_{eq} \left[ \frac{1}{1 + g_m R_L} \right]$$

$$\tau_H = R_{sig} \cdot C_{in} \Rightarrow f_H$$

$$= \frac{1}{2\pi \cdot R_{sig} \left( C_{rd} + \frac{C_{eq}}{1 + g_m R_L} \right)}$$

Notice that this is the same result as obtained in problem 9.86. This estimate is higher than that obtained from the method of open-time constants since it neglects the contribution of  $C_s$  to  $\tau_H$  and reduces the contribution of  $C_p$  from:

$$C_{ss} \cdot \frac{(R_{sig} + R_L)}{1 + g_m R_L} \text{ to } \frac{C_{ss} \cdot R_{sig}}{1 + g_m R_L}, \text{ thus}$$

effectively reducing the value of  $\tau_H$ , and therefore increasing  $f_H$

$$g_m = \frac{I_C}{V_r} = \frac{1}{0.025} = 40 \text{ mA/V},$$

$$8.80 \quad r_e = \frac{\beta}{(\beta + 1)g_m} = 25 \text{ }\Omega$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} = 2 \text{ GHz}$$

$$\Rightarrow C_\pi + C_\mu = 3.18 \text{ pF}$$

$$C_\mu = 0.1 \text{ pF} \Rightarrow C_\pi = 3.08 \text{ pF}$$

$$r_\pi = \frac{\beta}{g_m} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{20}{1} = 20 \text{ k}\Omega$$

$r_o$  is in effect parallel to  $R_L$ , so  $R_L' = R_L \parallel r_o$

$$R_L' = 1 \text{ k}\Omega \parallel 20 \text{ k}\Omega = 0.95 \text{ k}\Omega.$$

$$A_M = \frac{R_L'}{R_{sig} + r_\pi + r_\chi + R_L'} \\ = \frac{0.95}{1 + 2.5 + 0.1 + 0.95} = 0.964 \text{ V/V}$$

$$R_\mu = R_{sig} \parallel (r_\pi + (\beta + 1)R_L)$$

$$R_{sig} = R_{sig} + r_\chi = 1 + 0.1 = 1.1 \text{ k}\Omega$$

$$R_\mu = 1.1 \text{ k}\Omega \parallel (2.5 \text{ k}\Omega + 101 \times 0.95) \\ = 1.08 \text{ k}\Omega$$

8.81

$$K_u'(W/L) = \frac{128}{V^2} A \times 25 = 3.2 \text{ mA/V}^2$$

$$(a) V_{ov} = \sqrt{\frac{I}{K_u' W L}} = \sqrt{\frac{0.2}{3.2}} = 0.25 \text{ V}$$

$$g_m = \frac{I}{V_{ov}} = \frac{0.2 \text{ mA}}{0.25 \text{ V}} = 0.8 \text{ mA/V}$$

$$(b) Ad = g_m (R_O || R_o)$$

$$\text{where } R_o = \frac{V_A}{I/2} = \frac{20}{0.2/2} = 200 \text{ k}\Omega$$

$$\Rightarrow Ad = 0.8 \text{ mA} \times (20 \text{ k}\Omega || 200 \text{ k}\Omega) \\ = 14.54 \text{ V/V}$$

(c) For a CS amplifier when  $R_{sig}$  is low:

$$f_H = \frac{1}{2\pi(C_L + C_{gd})R_L'} \\ \text{where } R_L' = R_O || R_o \\ = 20 \text{ k}\Omega || 200 \text{ k}\Omega \\ = 18.18 \text{ k}\Omega$$

$$\text{and } C_L' = C_L + C_{db}$$

Since for a grounded source terminal  $C_{db}$  is in parallel with the load.

$$\rightarrow C_L' = 90 + 5 = 95 \text{ fF}$$

thus,

$$f_H = \frac{1}{2\pi(95+5)10^{-15} \times 18.18 \text{ k}\Omega} \\ = 87.54 \text{ MHz}$$

(d) Using the open-circuit time-constants method for  $R_s = 20 \text{ k}\Omega$

$$f_H = \frac{1}{2\pi\gamma_H}$$

$$\text{where } \gamma_H = C_{gs} \cdot R_s$$

$$+ C_{gd} [R_s(1 + g_m R_L') + R_L'] \\ + C_L \cdot R_L'$$

thus,

$$\gamma_H = 30 \text{ f} \times 20 \text{ k} \\ + 5_f [20 \text{ k}(1 + 0.8 \times 18.18) + 18.18 \text{ k}] \\ + (90_f + 5_f) \times 18.18 \text{ k}$$

$$\gamma_H = 0.6 \text{ ns}$$

$$+ 1.64 \text{ ns}$$

$$+ 1.72 \text{ ns} = 3.96 \text{ ns}$$

$$\Rightarrow f_H = \frac{1}{2\pi 3.96 \text{ ns}} = 40.2 \text{ MHz}$$

8.82

$$f_Z = \frac{1}{2\pi C_{ss} R_{ss}} = \frac{1}{2\pi(0.2\mu\text{A})(100\text{k}\Omega)} = 7.95 \text{ MHz}$$

8.83

$$f_Z = \frac{1}{2\pi C_{ss} R_{ss}}$$

$R_{ss}$  is the output resistance of the current source, which for the single-transistor current source is:

$$R_{ss} = r_o = \frac{V_A}{I_D} = \frac{30 \text{ V}}{100 \mu\text{A}} = 300 \text{ k}\Omega$$

$$\Rightarrow f_Z = \frac{1}{2\pi \cdot 100 \text{ f} \cdot 300 \text{ k}\Omega} = 5.3 \text{ MHz}$$

If  $V_{ov}$  is reduced from 0.5 V to 0.2 V while  $I$  is unchanged.

For the current-source transistor: when  $V_{ov} = 0.5 \text{ V}$

$$I = I_D = \frac{1}{2} k_n \left(\frac{W}{L}\right) V_{ov}^2 \rightarrow 100 \mu\text{A}$$

$$= \left[\frac{1}{2} k_n \frac{W_1}{L_1}\right] \times (0.5)^2$$

$$\rightarrow \frac{1}{2} k_n \frac{W_1}{L_1} = 400 \frac{\mu\text{A}}{\text{V}^2}$$

when  $V_{ov} = 0.2 \text{ V}$ :

$$100 \mu\text{A} = \left[\frac{1}{2} k_n \frac{W_2}{L_2}\right] \times (0.2)^2$$

$$\rightarrow \frac{1}{2} k_n \frac{W_2}{L_2} = 2500 \frac{\mu\text{A}}{\text{V}^2}$$

Assuming that  $L_1 = L_2$ , (the length of the transistor is unchanged)

$$\Rightarrow \frac{W_2}{W_1} = \frac{2500}{400} \rightarrow W_2 = 6.25 W_1$$

The width of the current-source transistor is made 6.25 times larger to operate at  $V_{ov} = 0.2 \text{ V}$ ,  $I_D = 100 \mu\text{A}$

If  $C_{ss}$  is directly proportional to  $W$ :

$$C_{ss2} = 6.25 \times 100 \text{ f}$$

$$f_{Z2} = \frac{f_{Z1}}{6.25} = 848 \text{ kHz}$$

8.84

$$\begin{aligned}
 \text{(a)} V_{ov} &= \sqrt{\frac{1}{(W/L)k_n}} \\
 &= \sqrt{\frac{80 \mu}{100 \times 0.2 \frac{\text{mA}}{\text{V}^2}}} = 63.2 \text{ mV} \\
 g_m &= \frac{2(I/2)}{V_{ov}} = \frac{80 \mu}{63.2 \text{ m}} = 1.27 \frac{\text{mA}}{\text{V}}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} A_d &= g_m(R_D \parallel r_o); \\
 r_o &= \frac{V_A}{(I/2)} = \frac{20 \text{ V}}{40 \mu} = 500 \text{ k}\Omega \\
 \Rightarrow A_d &= 1.27 \text{ mA}(20 \text{ k}\Omega \parallel 500 \text{ k}\Omega) = 24.4 \text{ V/V}
 \end{aligned}$$

$$\begin{aligned}
 \text{(c)} f_H &= \frac{1}{2\pi(C_L + C_{gd})R_L} \\
 R_L &= R_D \parallel r_o = 20 \text{ k}\Omega \parallel 500 \text{ k}\Omega = 19.23 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 C_L &= 100 \text{ fF} + C_{db} = 110 \text{ fF} \\
 \Rightarrow f_H &= \frac{1}{2\pi(110 \text{ fF} + 10 \text{ fF}) \times 19.23 \text{ K}} \\
 &= 69 \text{ MHz}
 \end{aligned}$$

(d) Using the open-circuit time-constants method

$$\text{for } R_{sig} = 100 \text{ k}\Omega \left( R_S = \frac{100 \text{ k}\Omega}{2} = 50 \text{ k}\Omega \right)$$

$$\begin{aligned}
 \tau_H &= C_{gs} \cdot R_S \\
 &+ C_{gd}[R_S(1 + g_m R_L) + R_L] \\
 &+ C_L \cdot R_L
 \end{aligned}$$


$$\begin{aligned}
 \tau_H &= 50 \text{ f} \times 50 \text{ K} \\
 &+ 10 \text{ f}[50 \text{ K}(1 + 1.27 \times 19.23) + 19.23 \text{ K}] \\
 &+ (100 \text{ f} + 10 \text{ f}) \times 19.23 \text{ K}
 \end{aligned}$$

$$\begin{aligned}
 \tau_H &= 2.5 \text{ ns} \\
 &+ 12.9 \text{ ns} \\
 &+ 2.11 \text{ ns} = 17.51 \text{ ns}
 \end{aligned}$$


$$f_H = \frac{1}{2\pi\tau_H} = \frac{1}{2\pi \times 17.51 \text{ ns}} = 9.1 \text{ MHz}$$

8.85

(a) Differential half-circuit:

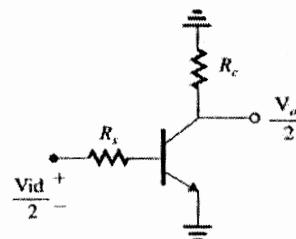

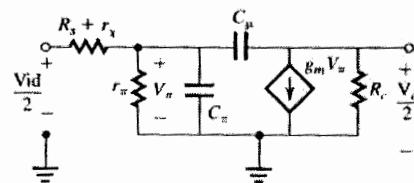High-frequency equivalent circuit ( $r_o$  is very large)



$$(b) I = 0.5 \text{ mA} \rightarrow g_m = \frac{0.5}{25} = 20 \frac{\text{mA}}{\text{V}}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{20 \text{ mA}} = 5 \text{ k}\Omega$$

$$C_\pi + C_\mu = \frac{20 \text{ m}}{2\pi \times 600} = 5.3 \text{ pF},$$

if  $C_\mu = 0.5 \text{ pF} \Rightarrow C_\pi = 4.8 \text{ pF}$

$$R_S = 10 \text{ k}\Omega, R_C = 10 \text{ k}\Omega, r_X = 100 \Omega$$


(Notice that  $R_H = \infty$ ,

$$r_O = \infty)$$

$$\begin{aligned}
 A_M &= \frac{-r_\pi}{r_\pi + R_S + r_X} \cdot g_m \cdot R_C \\
 &\approx \frac{-5 \text{ K}}{5 \text{ K} + (10 \text{ K} + 100)} \cdot 20 \text{ mA} \times 10 \text{ K} \\
 A_M &= -66.22 \text{ V/V}
 \end{aligned}$$

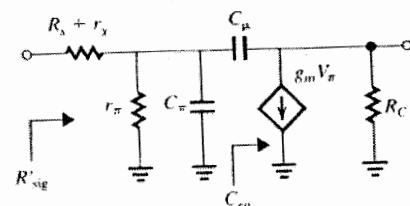(c)  $\Gamma$

$$f_H = \frac{1}{2\pi C_{in} \cdot R_{sig}}$$



where:

$$C_{in} = C_\pi + C_{eq}$$

using Miller's approximation:

$$C_{eq} = C_\mu (1 + g_m R_C)$$

$$\text{and } R_{sig} = (R_S + r_x) \parallel r_\pi$$

Thus,

$$f_H = \frac{1}{2\pi[(R_S + r_x) \parallel r_\pi] \cdot [C_\pi + C_\mu(1 + g_m R_C)]}$$

$$= \frac{1}{2\pi[(10K + 100) \parallel 5K] \cdot [4.8p + 0.5p(1 + 20 \times 10)]}$$

$$= 452 \text{ KHz}$$

$$GBW = 66.22 \times 452 \text{ K} = 30 \text{ MHz}$$

8.86

The CMRR will have..

poles at 500 KHz and at

$$\frac{1}{2\pi \times 10^6 \times 10 \times 10^{-12}} = 15.9 \text{ KHz}$$

The low frequency differential gain is:

$$A_d = g_{m1,2} (f_{o2} \parallel f_{o4})$$

$$= 2 \frac{mA}{V} (30K \parallel 30K) = \underline{\underline{30V}}$$

$$f_{p1} = 1/(2\pi C_L R_o)$$

$$\text{where } R_o = f_{o2} \parallel f_{o4} = 15K\Omega$$

$$f_{p1} = \frac{1}{2\pi \times 0.2p \times 15K} = \underline{\underline{53MHz}}$$

$$(7.193) f_{p2} = \frac{g_{m3}}{2\pi C_m} = \frac{1.2mA/V}{2\pi \times 0.1pF} = \underline{\underline{1.9GHz}}$$

$$(7.194) f_2 = \frac{2g_{m3}}{2\pi C_m} = \frac{2 \times 1.2m}{2\pi \times 0.1p} = \underline{\underline{3.8GHz}}$$

8.87

$$I = 0.6mA$$


$$V_{ovn} = 0.3V$$

$$V_{ovp} = 0.5V$$

$$VA_n = |VA_p| = 9V$$

$$C_m = 0.1pF$$

$$C_L = 0.2pF$$

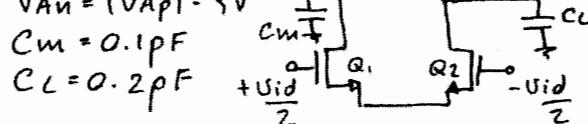


All  $f_o$ 's are identical:

$$f_o = \frac{VA}{ID} = \frac{9}{0.3m} = 30K\Omega$$

$$g_m = \frac{2ID}{V_{ov}} \Rightarrow g_{m1,2} = \frac{0.6m}{0.3} = 2mA/V$$

$$g_{m3,4} = \frac{0.6m}{0.5} = 1.2mA/V$$

This figure is for 8.88

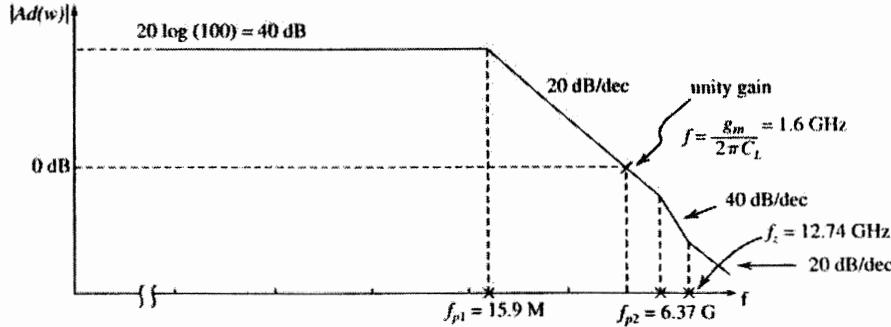

### 8.88

All  $V_{ov}$ 's are the same, all  $V_A$ 's are the same  
 $\Rightarrow$  All  $r_o$ 's are identical, and all  $g_m$ 's are identical

$$Ad(s) = g_m R_o \left[ \frac{1 + \frac{s \cdot C_m}{2g_m}}{1 + \frac{s \cdot C_m}{g_m}} \right] \cdot \left( \frac{1}{1 + sC_L R_o} \right)$$

where we know that the frequencies of the zero  $f_z$  and the pole  $f_p$ , occur at very high frequencies. Thus we can assume that the pole  $f_{p1} = 1/(2\pi C_L R_o)$  dominates the response of  $A_d(s)$  passed the unity gain

Thus:

$$A_d(\omega) \approx g_m R_o \left( \frac{1}{1 + j\omega C_L R_o} \right)$$

At unity gain:  $|A_d(\omega_1)| = 1$

$$\Rightarrow 1 = \frac{g_m R_o}{\sqrt{1 + (\omega_1 C_L R_o)^2}}$$

$$\Rightarrow \omega_1^2 = \frac{(g_m R_o)^2 - 1}{(C_L R_o)^2}$$

Since  $g_m R_o = g_m \frac{r_o}{2} \gg 1 \Rightarrow \omega_1 \approx g_m / C_L$

$$\Rightarrow f_1 \approx \frac{g_m}{2\pi \cdot C_L}$$

For:  $V_A = 20$  V,  $V_{ov} = 0.2$  V,  
 $I = 0.2$  mA,  $C_L = 100$  fF,  $C_m = 25$  fF

All  $r_o$ 's are identical:

$$r_o = \frac{V_A}{I_D} = \frac{20 \text{ V}}{(0.2 \text{ m}/2)} = 200 \text{ k}\Omega. \text{ All } g_m \text{'s}$$

$$\text{are identical: } g_m = \frac{2I_D}{V_{ov}} = \frac{0.2 \text{ m}}{0.2} = \frac{1 \text{ mA}}{\text{V}}$$

The low-frequency differential gain is:

$$A_{DDC} = g_m \times \frac{r_o}{2} = 1 \text{ m} \times 100 \text{ k}\Omega = 100 \text{ V/V}$$

$$f_{p1} = \frac{1}{2\pi C_L \cdot R_o} \quad R_o = \frac{r_o}{2} = 100 \text{ k}\Omega$$

$$f_{p1} = \frac{1}{2\pi \times 100 \text{ fF} \times 100 \text{ K}} = 15.9 \text{ MHz}$$

$$f_{p2} = \frac{g_m}{2\pi C_m} = \frac{1 \text{ m}}{2\pi \times 25 \text{ fF}} = 6.37 \text{ GHz}$$

$$f_z = \frac{2g_m}{2\pi C_m} = 2 \times f_{p2} = 12.74 \text{ GHz.}$$

Notice in the Bode plot the location of the unity-gain frequency.

8.89

$$a) A_M = -A_O \cdot \frac{R_L}{R_L + R_{out}} = -g_m r_o \cdot \frac{R_L}{R_L + r_o}$$

$$A_M = -5 \times 40 \times \frac{40}{40+40} = -100 \text{ V/V}$$

$$R'_L = R_L \parallel R_{out} = R_L \parallel r_o = 20 \text{ k}\Omega$$

$$R_{gd} = R_{sig} (1 + G_m R'_L) \quad \text{where } G_m = g_m$$

$$\Rightarrow R_{gd} = 20 \text{ K} (1 + 5 \times 20) = 2020 \text{ k}\Omega = 2.02 \text{ M}\Omega$$

$$R_{gd} = 2.02 \text{ M}\Omega$$

$$R_S = 0 \Rightarrow R_{gs} = R_{sig} = 20 \text{ k}\Omega$$

$$R_{C_L} = R'_L = 20 \text{ k}\Omega$$

$$T_H = C_{gs} R_{gs} + C_{gd} R_{gd} + C_L R'_L$$

$$T_H = 2 \times 20 \text{ K} + 0.1 \times 2.02 \text{ M} + 1 \times 20 \text{ K} = 262 \text{ ns}$$

$$f_H = \frac{1}{2\pi T_H} = 607.8 \text{ kHz}$$

$$|A_M| \cdot f_H = +100 \times 607.8 = 60.78 \times 10^3 \text{ Hz} = 60.78 \text{ MHz}$$

$$b) R_S = 500 \text{ }\Omega$$

$$R_{out} = r_o [1 + (g_m + g_{mb}) R_S] = 40 [1 + (5 + 1) 0.5] = 160 \text{ k}\Omega$$

$$A_M = -g_m r_o \frac{R_L}{R_L + R_{out}} = -5 \times 40 \times \frac{40}{40 + 160} = -40 \text{ V/V}$$

$$R'_L = R_L \parallel R_{out} = 40 \text{ K} \parallel 160 \text{ K} = 32 \text{ k}\Omega$$

$$R_{gd} = R_{sig} (1 + G_m R'_L)$$

$$G_m = \frac{g_m r_o}{r_o [1 + (g_m + g_{mb}) R_S]}$$

$$G_m = \frac{5 \times 40}{40 [1 + (5 + 1) 0.5]} = 1.25 \text{ mA/V}$$

$$R_{gd} = 20 \text{ K} (1 + 1.25 \times 32 \text{ k}\Omega) = 820 \text{ k}\Omega$$

$$R_{gs} = \frac{R_{sig} + R_S}{1 + (g_m + g_{mb}) R_S} \frac{r_o}{r_o + R_L}$$

$$R_{gs} = \frac{20 \text{ K} + 0.5 \text{ K}}{1 + (5 + 1) 0.5} \frac{40}{40 + 40} = 8.2 \text{ k}\Omega$$

$$R_{C_L} = R_L \parallel R_{out} = R'_L = 32 \text{ k}\Omega$$

$$T_H = C_{gs} R_{gs} + C_{gd} R_{gd} + C_L R'_L = 2 \times 8.2 + 0.1 \times 820 + 32 \times 1$$

$$T_H = 130.4 \text{ ns}$$

$$f_H = \frac{1}{2\pi T_H} = 1.22 \text{ MHz}$$

$$|A_M| \cdot f_H = 48.8 \text{ MHz}$$

8.90

$$f_T = |A_M| \cdot f_H = \frac{1}{2\pi C_{xd} \times R_{sig}}$$

for  $C_{xd} = 0.1 \text{ pF}$  and  $R_{sig} = 10 \text{ k}\Omega$

$$f_T = 159.2 \text{ MHz}$$

(b) If  $|A_M| = 20 \text{ V/V} \Rightarrow f_T = 159.2 \text{ MHz}$

$$\text{and } f_H = \frac{159.2 \text{ MHz}}{20} = 7.96 \text{ MHz}$$

(c)

$$g_m = 5 \frac{\text{mA}}{\text{V}}, A_O = 100 \text{ V/V}, R_L = 20 \text{ k}\Omega$$

$$A_O = g_m \cdot r_o \Rightarrow r_o = \frac{100}{5} = 20 \text{ k}\Omega$$

$$R_L = r_o = 20 \text{ k}\Omega$$

we can rewrite

$$A_M = -G_m (R_O \parallel R_L) \text{ as}$$

$$A_M = -(g_m r_o) \cdot \frac{R_L}{R_L + R_O}$$

$$\Rightarrow 20 = 100 \times \frac{20}{R_O + 20} \Rightarrow R_O = 80 \text{ k}\Omega$$

Since

$$R_O = r_o [1 + g_m R_S] = 20 \text{ K} [1 + 5 \text{ m} \times R_S]$$

$$= 80 \text{ K} \Rightarrow R_S = 600 \Omega$$

8.91

$$R_{gs} = \frac{R_{sig} + R_S}{1 + (g_m + g_{mb}) R_S} \frac{r_o}{r_o + R_L}$$

IF we define:

$$K = (g_m + g_{mb}) R_S \quad \text{and} \quad R_{sig} \gg R_S$$

$$\text{then: } R_{gs} \approx \frac{R_{sig}}{1 + K \frac{r_o}{r_o + R_L}} = \frac{R_{sig}}{1 + K/2}$$

$$G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_S} = g_m / (K + 1)$$

$$R'_L = R_L || R_{out}$$

$$R_{out} = r_o [1 + (g_m + g_{mb}) R_S] = r_o (1 + K)$$

$$R'_L = r_o || r_o (1 + K) = r_o \frac{(1 + K)}{2 + K}$$

Using Eq. 6.148:

$$R_{gd} = R_S \cdot g_d (1 + g_m R'_L) + R'_L$$

$$R_{gd} = R_S \cdot g_d (1 + \frac{g_m}{1 + K} \times r_o \frac{1 + K}{2 + K}) + r_o \frac{1 + K}{2 + K}$$

$$R_{gd} = R_S \cdot g_d (1 + \frac{A_o}{2 + K}) + r_o \frac{1 + K}{2 + K}$$

$$R_{C_2} = R'_L = r_o \frac{1 + K}{2 + K}$$

$$T_H = R_S C_{gs} + R_{gd} C_{gd} + R_{C_2} C_2$$

$$T_H = \frac{R_S \cdot g_d}{1 + K/2} C_{gs} + R_S \cdot g_d (1 + \frac{A_o}{2 + K}) C_{gd} + (C_L + C_{gd}) r_o \frac{1 + K}{2 + K}$$

8.92

$$R_{out} = r_o [1 + (g_m + g_{mb}) R_S] = r_o (1 + K)$$

$$R_{out} = 40(1 + K)$$

$$A_H = -g_m r_o \frac{R_L}{R_L + R_{out}} = -5 \times 40 \times \frac{40}{40 + 40(1 + K)}$$

$$A_H = -\frac{200}{2 + K}$$

$$T_H = \frac{C_{gs} R_S \cdot g_d}{1 + K/2} + C_{gd} R_S \cdot g_d (1 + \frac{A_o}{2 + K}) + (C_L + C_{gd}) r_o \frac{1 + K}{2 + K}$$

(From problem 6.111)

$$T_H = \frac{2 \times 20 K}{1 + K/2} + 0.1 \times 20 K (1 + \frac{5 \times 40}{2 + K}) + (1 + 0.1) 40 \frac{1 + K}{2 + K}$$

$$T_H = \frac{80}{2 + K} + 2(1 + \frac{200}{2 + K}) + 44 \frac{1 + K}{2 + K}$$

$$T_H = 528 + 46K \text{ nS}$$

$$f_H = \frac{1}{2\pi T_H} = \frac{(2 + K) \times 10^3}{2\pi(528 + 46K)} \text{ MHz}$$

$$f_T = |A_H| \cdot f_H$$

$$\begin{array}{|c|c|c|c|} \hline K & A_H (\text{V/V}) & f_H (\text{MHz}) & |A_H| \cdot f_H (\text{MHz}) \\ \hline \end{array}$$

0	-100	0.603	60.3
1	-66.67	0.832	55.47
2	-50.00	1.027	51.35
3	-40.00	1.195	47.8
4	-33.33	1.342	44.73
5	-28.57	1.471	42.03
6	-25.00	1.584	39.6
7	-22.22	1.686	37.46
8	-20.00	1.777	35.54
9	-18.18	1.859	33.8
10	-16.67	1.934	32.24
11	-15.38	2.002	30.79

K	A_H (V/V)	f_H (MHz)	A_H  f_H
12	-14.28	2.064	29.47
13	-13.33	2.121	28.27
14	-12.5	2.174	26.75
15	-11.76	2.223	26.14




IF  $f_H = 2 \text{ MHz}$ , then by looking at the table,

$K = 11$ . Therefore:  $K = 11 = g_m + g_{mb} R_S \Rightarrow$

$$R_S = \frac{11}{5+1} = 1.83 \text{ k}\Omega$$


From the table:  $A_H = -15.38$

8.93

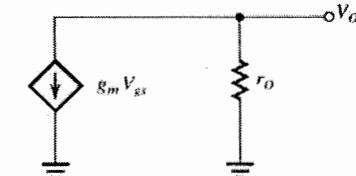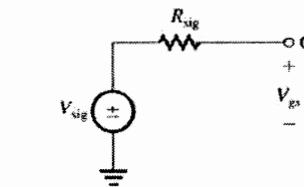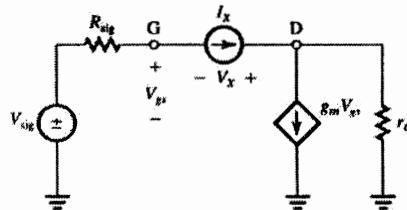

$$\text{then } \frac{V_o}{V_{\text{sig}}} = A_M = -g_m r_o$$

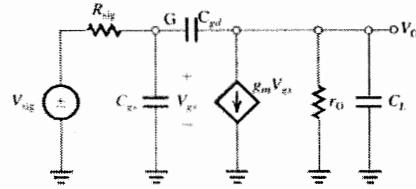The high-frequency small-signal circuit is:



Using the open-circuit time constants method:

$$\tau_H = R_{gs} \times C_{gs} + R_{gd} \times C_{gd} + R_L \times C_L$$

Setting  $C_{gd} = C_L = 0$  we can see that

$$R_{gs} = R_{sig}$$

Setting  $C_{gs} = C_{gd} = 0$  we can see that

$$R_L = r_o$$

To obtain  $R_{gd}$  set  $C_{gs} = C_L = 0$  and consider the following circuit:

$$R_{gd} = R_X = \frac{V_X}{I_X}$$

$$\text{At node G: } V_{gs} = -I_X \cdot R_{sig} \text{ Eq 1.}$$

$$\text{At node D: } I_X = g_m V_{gs} + \frac{V_X + V_{gs}}{r_o} \text{ Eq 2.}$$

Substituting  $V_{gs}$  in Eq 2 by Eq 1 and re-arranging:

$$\frac{V_X}{I_X} = R_X = R_{sig} [1 + g_m r_o] + r_o$$

Thus,

$$\tau_H = C_{gs} \cdot R_{sig} + C_{gd} [R_{sig} [1 + g_m r_o] + r_o] + C_L r_o$$

$$\text{If } g_m = 1 \frac{\text{mA}}{\text{V}}, r_o = 20 \text{ k}\Omega, R_{sig} = 20 \text{ k}\Omega$$

$$C_{gs} = 20 \text{ fF}, C_{gd} = 5 \text{ fF}, C_L = 10 \text{ fF}$$


$$A_M = -g_m \cdot r_o = -1 \times 20 = -20 \text{ V/V}$$

$$\begin{aligned} \tau_H &= 20 \text{ f} \times 20 \text{ K} + 5 \text{ f} [20 \text{ K} (1 + 1 \times 20) + 20 \text{ K}] \\ &+ 10 \text{ f} \times 20 \text{ K} \\ &= 2.8 \text{ ns} \end{aligned}$$

$$f_H = \frac{1}{2\pi \tau_H} = 56.8 \text{ MHz}$$

$$|A_M| \cdot f_H = 20 \times 56.8 \text{ M} = 1.14 \text{ GHz}$$

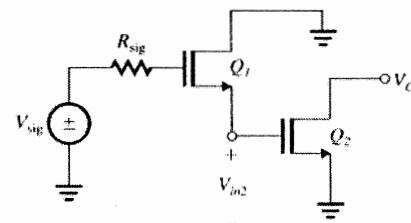(b) For the low-frequency analysis of the CD-CS consider the following circuit



or the CS:

$$V_O = V_{in2}(-g_m r_{O2}) \quad (\text{Eq. 1})$$

For a CD amplifier:

$$A_M = \frac{(R_L \parallel r_O)}{(R_L \parallel r_O) + (1/g_m)}$$


which adapted to our circuit provides:

$$V_{in2} = V_{sig} \frac{r_{O1}}{r_{O1} + 1/g_m} \quad (\text{Eq. 2})$$

Combining Eq. 1 and Eq. 2:

$$\frac{V_O}{V_{sig}} = A_M = \frac{-r_{O1}(g_m r_{O2})}{\frac{1}{g_m} + r_{O1}}$$

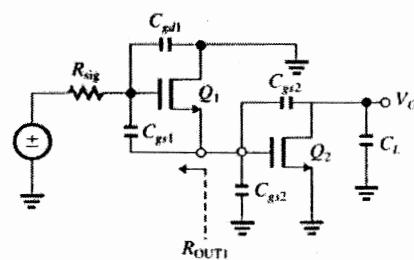For the high-frequency analysis of the CD-CS consider the following circuit



$$\begin{aligned} \tau_H &= C_{gd1} \times R_{gd1} + C_{gs1} \times R_{gs1} + C_{gs1} \\ &\quad \times R_{gs2} + C_{gd2} R_{gd2} + C_L \cdot R_{CL} \end{aligned}$$

To obtain the value of the resistors we must determine the corresponding equivalent circuits when all other capacitances are set to zero.

For  $C_{gd1}$ : Due to the ground connection on the drain of  $Q_1$   $C_{gd1}$  sees  $R_{gd1} = R_{sig}$

For  $C_{gs1}$ :

$$\begin{aligned} I_X &= \frac{V_X(1 + g_m r_O)}{R_{sig} + r_O} \\ \Rightarrow R_{gs1} &= R_X = (R_{sig} + r_O)/(1 + g_m r_O) \end{aligned}$$

For  $C_{gs2}$ :  $C_{gs2}$  sees  $R_{OUT1}$  which for a CD amplifier is:

$$R_{OUT1} = R_{gs2} = \frac{1}{g_m} \parallel r_{O1}$$

For  $C_{gd2}$ : Referring to the analysis of the CS amplifier

$$R_{gd} = R_{sig}(1 + g_m R_L) + R_L$$

which adapted to our circuit becomes:

$$R_L = r_{O2} \text{ and}$$

$$R_{sig} = R_{OUT1} = \frac{1}{g_m} \parallel r_{O1}$$

$$\Rightarrow R_{gd2} = \left( \frac{1}{g_m} \parallel r_{O1} \right) \cdot (1 + g_m r_{O2}) + r_{O2}$$

For  $C_L$ :  $C_L$  sees  $r_{O2} \Rightarrow R_{CL} = r_{O2}$ .

Therefore:

$$\tau_H = C_{gd1} \cdot R_{sig} + C_{gs1} \left( \frac{R_{sig} + r_{O1}}{1 + g_m r_{O1}} \right)$$

$$+ C_{gs2} \left( \frac{1}{g_m} \parallel r_{O1} \right)$$

$$+ C_{gd2} \left[ \left( \frac{1}{g_m} \parallel r_{O1} \right) (1 + g_m r_{O2}) + r_{O2} \right]$$

$$+ C_L \cdot r_{O2}$$

For the circuit parameters of part (a):  $r_{O1} = r_{O2}$

$$g_m = g_m$$

$$A_M = -\frac{20 \text{ K}}{\frac{1}{1 \text{ m}} + 20 \text{ K}} \cdot (1 \times 20) = -19 \text{ V/V}$$

$$C_{gd1} \cdot R_{sig} = 5 \text{ f} \times 20 \text{ K} = 100 \text{ ps}$$

$$\begin{aligned} C_{gs1} \cdot \frac{R_{sig} + r_{O1}}{1 + g_m r_{O1}} &= 20 \text{ f} \times \frac{(20 \text{ K} + 20 \text{ K})}{(1 + 1 \times 20)} \\ &= 38.1 \text{ ps} \end{aligned}$$

$$C_{gs2} \left( \frac{1}{g_m} \parallel r_{O1} \right) = 20 \text{ f} (1 \text{ K} \parallel 20 \text{ K}) = 19.0 \text{ ps}$$

$$C_{gd2} \left[ \left( \frac{1}{g_m} \parallel r_{O1} \right) \cdot (1 + g_m r_{O2}) + r_{O2} \right] = 5 \text{ f} \times \{ (1 \text{ K} \parallel 20 \text{ K})(1 + 20) + 20 \text{ K} \} = 200 \text{ ps}$$


$$C_L \cdot r_{O2} = 10 \text{ f} \times 20 \text{ K} = 200 \text{ ps}$$

$$\tau_H = 100 + 38.1 + 19 + 200 + 200 = 557.1 \text{ ps}$$

$$\Rightarrow f_H = \frac{1}{2\pi \tau_H} = 285.7 \text{ MHz}$$

$$|A_M| \cdot f_H = 19 \times 285.7 \text{ M} = 5.4 \text{ GHz}$$

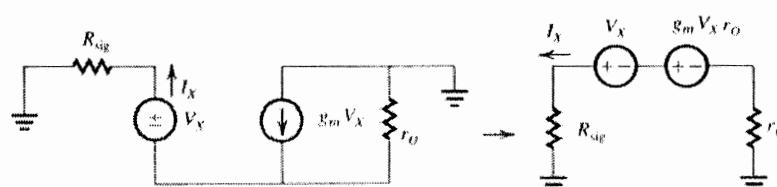Comparing with the stand-alone CS amplifier of part (a) we can see how  $A_M$  is approx. the same, while  $f_H$  and thus the gain-bandwidth product have increased by a factor of 5.



8.94

Each of the transistors is operating at a bias current of approximately 100  $\mu\text{A}$ . Thus:

$$g_m = \frac{0.1}{0.025} = 4 \text{ mA/V},$$

$$r_\pi = \frac{100}{4} = 25 \text{ k}\Omega$$

$$r_e \approx 250 \Omega, r_o = \frac{100}{0.1} = 1 \text{ M}\Omega$$

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{4 \text{ m}}{2\pi \times 400 \text{ M}} = 1.59 \text{ pF}$$

$$\Rightarrow C_\pi = 1.39 \text{ pF}$$

$$\text{a) } R_{in} = (\beta + 1)[r_{e1} + (r_{\pi 2} \parallel r_{o1})]$$

$$R_{in} = 101[250 \times 10^{-3} + 25 \text{ k}\Omega \parallel 1 \text{ M}\Omega] \\ \approx 2.5 \text{ M}\Omega$$


Using Miller's Theorem for  $C_{\mu 2}$ :

$$A_M = -\frac{R_{in}}{R_{in} + R_{sig}} \times \frac{r_{\pi 2} \parallel r_{o1}}{r_{e1} + (r_{\pi 2} \parallel r_{o1})} \\ \times g_{m2} r_{o2}$$

$$A_M = -\frac{2.5 \text{ M}}{2.5 \text{ M} + 0.01} \times \frac{25 \text{ K} \parallel 1 \text{ M}}{0.25 + (25 \text{ K} \parallel 1 \text{ M})} \\ \times 4 \times 1 \text{ M}$$

$$A_M = -3943.6 \text{ V/V}$$

b) To calculate  $f_H$ ,

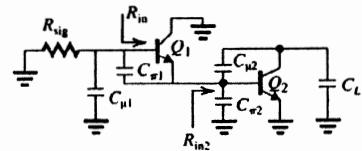

$$R_{\mu 1} = R_{sig} \parallel R_{in} = 10 \text{ k}\Omega \parallel 2.5 \text{ M}\Omega = 10 \text{ k}\Omega$$

$$R_{in2} = r_{\pi 2} \parallel r_{o1}$$

$$R_{in2} = 25 \text{ k}\Omega \parallel 1 \text{ M}\Omega$$

$$R_{in2} = 24.4 \text{ k}\Omega$$

$$R_{\pi 1} = \frac{R_{sig} + R_{in2}}{1 + \frac{R_{sig}}{r_{\pi 1}} + \frac{R_{in2}}{r_{\pi 1}}}$$



$$R_{\pi 1} = \frac{10 + 24.4}{1 + \frac{10}{25} + \frac{24.4}{0.25}} = 0.35 \text{ k}\Omega$$

$$C_T = C_{\pi 2} + C_{\mu 2}(1 + g_{m2} r_{o2})$$

$$C_T = 1.39 + 0.2(1 + 4 \times 1000) = 801.6 \text{ pF}$$

$$R_T = r_{\pi 2} \parallel r_{o1} \parallel \frac{r_{\pi 1} + R_{sig}}{\beta + 1} \\ = 25 \text{ K} \parallel 1000 \text{ K} \parallel \frac{25 + 10}{101}$$

$$R_I = 342 \Omega$$

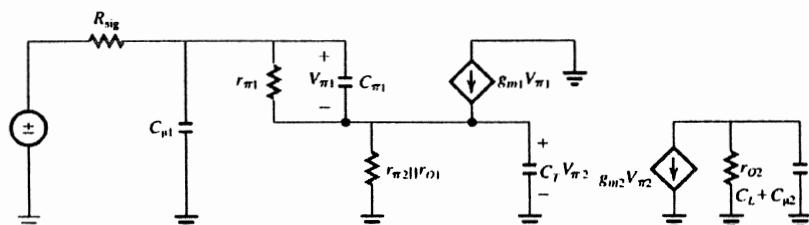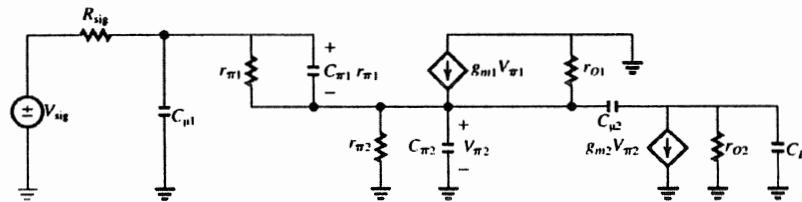




$$R_{gd} = R'_{sig} = 100 \text{ K} \parallel 495 \text{ K} = 83.2 \text{ k}\Omega$$

$$R_{gs} = \frac{R'_{sig} + (6.8 \text{ K} \parallel 5 \text{ K})}{1 + g_m(6.8 \text{ K} \parallel 5 \text{ K})} = \frac{83.2 + 2.88}{1 + 0.63 \times 2.88} = 30.6 \text{ k}\Omega$$
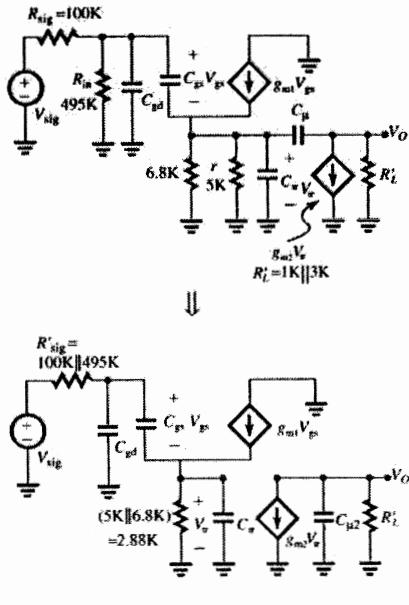
$$R_T = 6.8 \parallel 5 \parallel \frac{1}{g_m} = 1 \text{ k}\Omega$$



$$R'_{L} = 0.75 \text{ k}\Omega$$


$$\tau_H = C_{pd} R_{st} + C_{ps} R_{st} + C_s R_s + C_b R'_L$$

$$\tau_H = 1 \times 83.2 + 1 \times 30.6 + 34.6 \times 1 + 0.8 \times 0.75 = 149 \text{ nS}$$

$$f_H \approx \frac{1}{2\pi\tau_H} = 1.07 \text{ MHz}$$

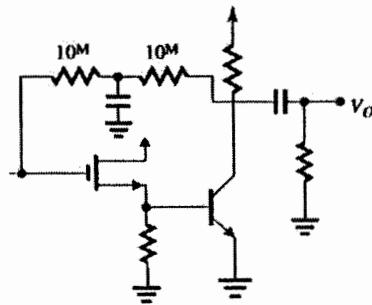f) There will no longer be a signal feedback. The lefthand side  $10 \text{ M}\Omega$  Resistor will in effect appear between the input terminal and ground. Thus:  $R_{st} = 10 \text{ M}\Omega$  (a factor of 20 increase) and correspondingly  $A_H$  becomes:

$$A_H = \frac{10}{10.1} \times (-19.2) = -19.2 \text{ V/V}$$



(an increase from  $-16 \text{ V/V}$ ) Now  $R'_{st}$  becomes approximately  $100 \text{ k}\Omega$ , as compared to  $83.2 \text{ k}\Omega$ , and correspondingly  $R_{st}$  becomes  $100 \text{ k}\Omega$ , and  $R_{gs}$  becomes  $30.6 \text{ k}\Omega$  while  $R_s$  and  $R'_L$  remain practically unchanged. Thus  $\tau_H$  becomes  $172.5 \text{ nS}$  and  $f_H$  decreases from  $1.07 \text{ MHz}$  to  $0.92 \text{ MHz}$ .

8.96

$$V_{G1} = V_S \cdot \frac{2/gm}{2/gm + R_S} \quad I = \frac{V_{G1}}{2/gm}$$

$$V_O = I R_D = \frac{V_{G1} \times R_D}{2/gm}$$

$$= \frac{V_S \times \frac{2/gm}{2/gm + R_S}}{2/gm + R_S} \cdot \frac{R_D}{2/gm}$$


$$= \frac{V_S \cdot R_D}{2/gm + R_S}$$

$$\Rightarrow A_o = \frac{V_O}{V_S} = \frac{gm R_D}{2 + gm R_S}$$

$$gm = \frac{200 \mu A}{0.25V} = 0.8 \text{ mA/V}$$

$$\Rightarrow A_o = \frac{0.8 \times 50}{2 + 0.8 \times 200} = 0.24 \text{ V/V}$$

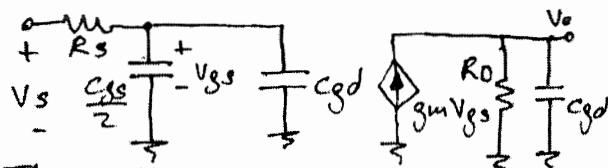The high-frequency equivalent circuit is:



Thus, the pole at the input has a frequency  $f_{pi}$ :

CONT.

$$f_{p1} = \frac{1}{2\pi R_3 \times \left( \frac{C_{gs}}{2} + C_{gd} \right)}$$

$$= \frac{1}{2\pi \times 200K \times (1/2 + 1) p}$$

$$= \underline{530 \text{ KHz}}$$

and the pole at the output has a frequency  $f_{p2}$ :

$$f_{p2} = \frac{1}{2\pi R_O C_{gd}} = \frac{1}{2\pi \times 50K \times 1p}$$


$$= \underline{3.18 \text{ MHz}}$$

Thus  $f_H \approx \frac{1}{\sqrt{\left(\frac{1}{530 \text{ KHz}}\right)^2 + \left(\frac{1}{3.18 \text{ MHz}}\right)^2}}$

$$= \underline{523 \text{ KHz}}$$

Notice that this low value of  $f_H$  is due to the large value of  $R_3$ .

8.97

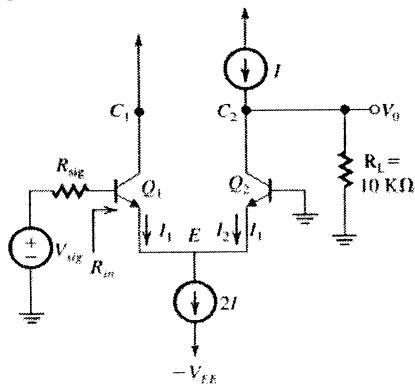

$$I_1 = I_2 = I = 1 \text{ mA}$$

$$g_m = \frac{I}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mA/V}$$

$$\gamma_e = \frac{V_T}{I_E} = 25 \Omega$$

$$\gamma_\pi = (\beta + 1)\gamma_e \approx 3 \text{ k}\Omega$$

$$2\pi f_T = \frac{g_m}{C_\pi + C_\mu}$$

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{40 \times 10^{-3}}{2\pi \times 700 \times 10^6} \approx 9.1 \text{ pF}$$

$$C_\pi = 9.1 - C_\mu = 8.6 \text{ pF}$$

$$R_{in} = (\beta + 1)(2\gamma_e) = 2\gamma_\pi = 6 \text{ k}\Omega$$

$$A_M = \frac{1}{2} \left( \frac{R_{in}}{R_{in} + R_{sig}} \right) \times g_m R_L$$

$$= \frac{1}{2} \left( \frac{6}{6 + 20} \right) \times 40 \times 10$$

$$A_M = 46.15 \text{ V/V}$$

The pole at the input side is

$$f_{p1} = \frac{1}{2\pi \left( \frac{C_\pi}{2} + C_\mu \right) (R_{sig} \parallel 2\gamma_\pi)}$$

$$= \frac{1}{2\pi \left( \frac{8.6}{2} + 0.5 \right) \times 10^{-12} \times (20 \text{ K} \parallel 6 \text{ K})}$$

$$= 7.18 \text{ MHz}$$

$$f_{p2} = \frac{1}{2\pi C_\mu R_L} = \frac{1}{2\pi \times 0.5 \times 10^{-12} \times 10 \text{ K}}$$

$$= 31.8 \text{ MHz}$$

$$f_H = \frac{1}{\sqrt{\left(\frac{1}{f_{p1}}\right)^2 + \left(\frac{1}{f_{p2}}\right)^2}}$$

$$\approx 7 \text{ MHz}$$

8.98

$$I_1 = I_2 = I = 1mA \Rightarrow g_m = 40 \text{ mA/V}, r_H = \frac{120}{40} = 3\text{ k}\Omega$$

$$r_e = \frac{3}{121} \approx 25\text{ }\mu\Omega \Rightarrow C_{in} + C_M = \frac{2m}{2\pi f_T} = \frac{40m}{2\pi \times 700M} = 9.1\text{ pF}$$

Using Eq. 6.185:

$$A_M = \frac{V_o}{V_{sig}} = \frac{1}{2} \left( \frac{R_{in}}{R_{in} + R_{sig}} \right) g_m R_L \quad C_{in} = 8.6\text{ pF}$$

$$R_{in} = 2r_H = 2 \times 3\text{ k}\Omega = 6\text{ k}\Omega$$

$$A_M = \frac{1}{2} \times \frac{6}{6+20} \times 40 \times 10^3 = 46.15 \text{ V/V}$$

$$f_{p1} = \frac{1}{2\pi(C_{in} + C_M)(R_{sig} || 2r_H)} = \frac{1}{2\pi(\frac{8.6}{2} + 0.5)(20 || 6k)}$$

$$f_{p1} = 7.19\text{ MHz}$$

$$f_{p2} = \frac{1}{2\pi C_M R_L} = \frac{1}{2\pi \times 0.5 \times 10^6} = 31.8\text{ MHz}$$

$$f_H = \frac{1}{\sqrt{\left(\frac{C_M}{f_{p1}}\right)^2 + \left(\frac{1}{f_{p2}}\right)^2}} = 7.01\text{ MHz}$$

### 8.99

All the transistors in this problem are operating at a bias current of 0.5 mA and thus have :

$$r_e = 50\Omega, g_m = 20 \text{ mA/V}, r_\pi = 5 \text{ k}\Omega$$

$$C_\pi + C_\mu = \frac{20 \text{ m}}{2\pi \times 400 \text{ m}} = 8 \text{ pF}$$

since  $C_\mu = 2 \text{ pF} \Rightarrow C_\pi = 6 \text{ pF}, r_o = \infty, r_s = 0$

a) Common-Emitter amplifier:

$$R_{sig} = 10 \text{ k}\Omega, R_C = 10 \text{ k}\Omega$$

$$A_M = -\frac{r_\pi}{R_{sig} + r_\pi} g_m R_C = -\frac{5}{10+5} 20 \times 10 = -66.7 \text{ V/V}$$

$$f_H = \frac{1}{2\pi(R_{sig} \parallel r_\pi)(C_\pi + (1 + g_m R_C)C_\mu)} \Rightarrow \\ f_H = \frac{1}{2\pi(10^k \parallel 5^k)[6^p + (1 + 20 \times 10)^2]} = 117 \text{ KHz}$$

b) Cascode :

$$A_M = -\frac{\beta_1 \alpha_2 R_C}{R_{sig} + r_\pi} = -\frac{100 \times 0.99 \times 10}{10+5} = -66 \text{ V/V}$$

Input pole

$$= f_{p1} = \frac{1}{2\pi(R_{sig} \parallel r_{M1})(C_{\pi1} + 2C_{\mu1})}$$

$$f_{p1} = \frac{1}{2\pi(10^k \parallel 5^k)(6+4)^p} = 4.77 \text{ MHz}$$

output pole :

$$f_{p3} = \frac{1}{2\pi C_{\mu2} R_C} = \frac{1}{2\pi \times 2^p \times 10^k} = 7.96 \text{ MHz}$$

pole at midband node :

$$f_{p2} = \frac{1}{2\pi C_{\pi2} r_{e2}} = \frac{1}{2\pi \times 6^p \times 50} = 530.5 \text{ MHz}$$

very high

$$f_H = \sqrt{\frac{1}{\left(\frac{1}{f_{p1}}\right)^2 + \left(\frac{1}{f_{p2}}\right)^2}} = 4.1 \text{ MHz}$$

c) CC-CB Cascade (modified diff. amplifier)

$$A_M = \frac{\beta R_C}{R_{sig} + 2r_\pi} = \frac{100 \times 10}{10+10} = 50 \text{ V/V}$$

Input pole

$$f_{p1} = \frac{1}{2\pi(R_{sig} \parallel 2r_\pi)(C_{\pi12}/2 + C_\mu)}$$

$$f_{p1} = \frac{1}{2\pi(10^k \parallel 10^k)(3+2)^p} = 6.4 \text{ MHz}$$

Output pole:

$$f_{p2} = \frac{1}{2\pi C_{\mu2} R_C} = \frac{1}{2\pi \times 2^p \times 10^k} = 7.96 \text{ MHz}$$

$$\text{Thus: } f_H = \frac{1}{\sqrt{\left(\frac{1}{f_{p1}}\right)^2 + \left(\frac{1}{f_{p2}}\right)^2}} = 5 \text{ MHz}$$

d) CC-CE Cascade :

$$A_M = -\frac{(\beta_1 + 1)\beta_2 R_C}{R_{sig} + r_{\pi1} + (\beta_1 + 1)r_{\pi2}} \\ = -\frac{101 \times 100 \times 10}{10 + 5 + 101 \times 5} = -194 \text{ V/V}$$

Refer to Example 6.13 in :

$$R_{\mu1} = (R_{sig} \parallel R_{in}) = 10^k \parallel (\beta + 1)[r_{e1} + r_{\pi2}]$$

$$R_{\mu1} = 10^k \parallel 101 \times [0.05 + 5] = 9.81 \text{ k}\Omega$$

$$R_{\pi1} = r_{\pi1} \parallel \frac{R_s + r_{\pi2}}{1 + g_{m1}r_{\pi2}} = 5 \parallel \frac{10 + 5}{1 + 20 \times 5} = 144 \text{ }\Omega$$

$$R_T = r_{\pi2} \parallel \frac{r_{\pi1} + R_{sig}}{\beta + 1} = 5^k \parallel \frac{5 + 10}{101} = 144 \text{ }\Omega$$

where

$$C_T = C_{\pi2} + C_{\mu2}(1 + g_{m2}R_C) = 6 + 2(1 + 200)$$

$$C_T J = 408 \text{ pF}$$

$$R_{\mu2} = R_C = 10 \text{ k}\Omega$$

$$\tau_H = C_{\mu1} R_{\mu1} + C_{\pi1} R_{\pi1} + C_T R_T + C_{\mu2} R_{\mu2}$$

$$\tau_H = 2 \times 9.81 + 6 \times 0.144 + 408 \times 0.144 + 2 \times 10$$

$$\tau_H = 19.62 + 0.86 + 58.75 + 20 = 99.2 \text{ ns}$$

$$f_H = \frac{1}{2\pi\tau_H} = \frac{1}{2\pi \times 99.2^n} = 1.6 \text{ MHz}$$

e) Folded Cascode :

$$A_M = -\frac{\beta_1 \alpha_2 R_C}{R_{sig} + r_{\pi1}} = -\frac{100 \times 0.99 \times 10}{10+5} = -66 \text{ (V)/V}$$

Input pole :

$$f_{p1} = \frac{1}{2\pi(R_{sig} \parallel r_{\pi1})(C_{\pi1} + 2C_{\mu1})}$$

$$= \frac{1}{2\pi(10 \parallel 5)(6+4)}$$

$$f_{p1} = 4.77 \text{ MHz}$$

At middle:

$$f_{p2} = \frac{1}{2\pi C_{\pi2} r_{e2}} = \frac{1}{2\pi \times 6^p \times 0.05} = 530 \text{ MHz very high!}$$

At output:

$$f_{p3} = \frac{1}{2\pi C_{\mu2} R_C} = \frac{1}{2\pi \times 2^p \times 10}$$

$$f_{p3} = 7.96 \text{ MHz}$$

$$\text{Thus: } f_H \approx \frac{1}{\sqrt{\frac{1}{4.77^2} + \frac{1}{7.96^2}}} = 4.1 \text{ MHz}$$

f) CC-CB Cascade :

$$A_M = \frac{(\beta_1 + 1)\alpha_2 R_C}{R_{sig} + (\beta_1 + 1)2r_e} = \frac{101 \times 0.99 \times 10}{10 + 101 \times 0.1} \approx 50 \text{ V/V}$$

$$\text{Input pole : } f_{p1} = \frac{1}{2\pi(R_{sig} \parallel 2r_e)(C_{w/2} + C_\mu)}$$

$$f_{p1} = \frac{1}{2\pi(10^k \parallel 10^k)(3^p + 2^p)} = 6.4 \text{ MHz}$$

Output pole:

$$f_{p2} = \frac{1}{2\pi R_C C_\mu} = \frac{1}{2\pi \times 10^k \times 2^p} = 7.96 \text{ MHz}$$

$$f_H = \frac{1}{\sqrt{\frac{1}{6.4^2} + \frac{1}{7.96^2}}} = 5 \text{ MHz}$$

Summary of results :

ConFiguration	$A_M$ (V/V)	$f_H$ (MHz)	G.B (MHz)
a)CE	-66.7	0.117	7.8
b) Cascode	-66	4.1	271
c) CC_CB Cascade	+50	5.0	250
d)CC_CE Cascade	-194	1.6	310
e) Folded Cascode	-66	4.1	271
f) CC_CB Cascade	+50	5.0	250

DC-gain =  $(G_{m1}R_1) \times (G_{m2}R_2)$

$$= (1 \times 100) \times (2 \times 50) = 10 \text{ K V/V} \rightarrow 80 \text{ dB}$$

(b) From Eq (9.175) if  $C_C$  is not connected:

$$\omega_{p1} = \frac{1}{C_1 \cdot R_1 + C_2 \cdot R_2}$$

$$= \frac{1}{0.1 \text{ p} \times 100 \text{ K} + 2 \text{ p} \times 50 \text{ K}}$$

$$= 9.1 \text{ M rad/s}$$

$$\Rightarrow f_{p1} = 1.45 \text{ MHz}$$

To obtain  $\omega_{p2}$  we equate the coefficients of  $s^2$  in Eq (9.171) to  $1/(\omega_{p1}, \omega_{p2})$


Thus, for  $C_C$  not connected.

$$C_1 C_2 R_1 R_2 = \frac{1}{\omega_{p1} \cdot \omega_{p2}}$$

$$\Rightarrow \omega_{p2} = \frac{C_1 R_1 + C_2 R_2}{C_1 C_2 \cdot R_1 \cdot R_2}$$

$$\omega_{p2} = \frac{0.1 \text{ p} \times 100 \text{ K} + 2 \text{ p} \times 50 \text{ K}}{0.1 \text{ p} \times 2 \text{ p} \times 100 \text{ K} \times 50 \text{ K}} = 110 \text{ MHz} \Rightarrow f_{p2} = 17.5 \text{ MHz}$$

The Bode plot for the gain magnitude is

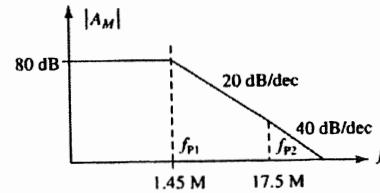

(c) Since  $(C_1 = 0.1 \text{ pF}) \ll (C_2 = 2 \text{ pF})$  and if  $C_1 \ll C_C$  then from Eq (9.177)

$$\omega_{p2} \approx \frac{G_{m2}}{C_2} \rightarrow \omega_{p2} \approx \frac{2 \text{ m}}{2 \text{ p}} \approx 1 \text{ G rad/s}$$

$$\rightarrow f_{p2} = 159 \text{ MHz}$$


two octaves below are  $= \omega_{p2}/4 = 250 \text{ M rad/s} \rightarrow 40 \text{ MHz}$  then, from Eq 9.178:

$$250 \text{ M} \leq \frac{G_{m1}}{C_C} \Rightarrow C_C \leq \frac{1 \text{ m}}{250 \text{ M}} \Rightarrow C_C \leq 4 \text{ pF}$$

For  $C_C = 4 \text{ pF}$  and Eq (9.176)

$$\omega_{p1} \approx \frac{1}{R_1 C_C G_{m2} R_2}$$
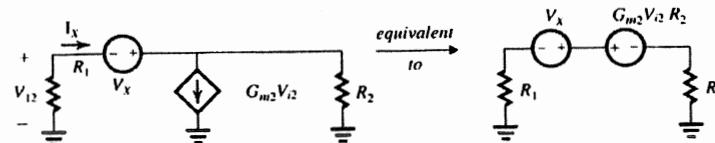
$$\approx \frac{1}{100 \text{ K} \times 4 \text{ p} \times 2 \text{ m} \times 50 \text{ K}} = 25 \text{ K rad/s}$$




$$\Rightarrow f_{P1} = 3.9 \text{ KHz}$$

From Eq (9.173):

$$\omega_L = \frac{G_{m2}}{C_C} = \frac{2 \text{ m}}{4 \text{ p}} = 500 \text{ M rad/s}$$

$$\Rightarrow f_L = 79.6 \text{ MHz} \approx 80 \text{ MHz}$$

The Bode plot for the gain magnitude is

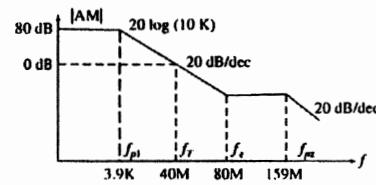

### 8 . 101

$G_{m1} = g_{m1} = g_m$ ; transconductance of input stage.

$G_{m2} = g_{m2}$ ; transconductance of second stage.

$C_1 = C$  at node  $D_2 = 0.2 \text{ pF}$

$C_2 = C$  at node  $D_6 = 3 \text{ pF}$

$$\text{For } f_T = 50 \text{ MHz}, \frac{G_{m1}}{2\pi \times C_C}$$

$$\Rightarrow C_C = \frac{1 \text{ m}}{2\pi \times 50 \mu} = 3.2 \text{ pF}$$

$$f_2 = \frac{G_{m2}}{2\pi C_C} = \frac{3 \text{ m}}{2\pi \times 3.2 \text{ pF}} \approx 149 \text{ MHz}$$

$$f_2 = \frac{G_{m2}}{2\pi C_2} = \frac{3 \text{ m}}{2\pi \times 3 \text{ pF}} \approx 159 \text{ MHz}$$

$$f_T(50 \text{ MHz}) < f_2(149 \text{ MHz}) < f_2(159 \text{ MHz})$$

### 8 . 102

For both transistors:

$V_{ov} = 0.2 \text{ V}$   $C_{gs} = 20 \text{ fF}$

$I = 0.1 \text{ mA}$   $C_{gd} = 5 \text{ fF}$

$|V_A| = 10 \text{ V}$   $C_{ab} = 5 \text{ fF}$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 0.1 \text{ mA}}{0.2 \text{ V}} = 1 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{10}{0.1 \text{ mA}} = 100 \text{ k}\Omega$$

(a) DC - Voltage gain

$$V_o = -g_{m2}r_{o2} \times V_{gs2} \text{ and}$$

$$V_{gs2} = -g_{m1}r_{o1} V_{sig} \Rightarrow A_M = \frac{V_o}{V_{sig}}$$

$$= (g_m r_o)^2 = (1 \times 100)^2 = 10 \text{ KV/V}$$

(b) Using the Miller approximation at node  $G1$

$$C_{eq} = C_{gd1}(1 + g_{m1}R_L) \text{ Eq (9.46)}$$

$$\Rightarrow C_{eq1} = C_{gd1}(1 + g_{m1}r_{o1})$$

$$= 5 \text{ f} (1 + 100) = 50 \text{ fF}$$

$$C_{in1} = C_{gs1} + C_{eq1} = 20 \text{ f} + 505 \text{ f} = 525 \text{ fF}$$

$$(c) R_{sig} = 10 \text{ k}\Omega$$

The pole caused by  $C_{in1}$  at node  $G_1$  is

$$f_{P1} = \frac{1}{2\pi \cdot R_{sig} \cdot C_{in1}} = \frac{1}{2\pi \times 10 \text{ k} \times 525 \text{ f}} = 30.3 \text{ MHz}$$

(d) Using the Miller approximation at node  $G_2$

$$C_{eq2} = C_{gd2}(1 + g_{m2}r_{o2}) = 505 \text{ fF}$$

$$C_{in2} = C_{db1} + C_{gs2} + C_{eq2} = 5 \text{ f} + 20 \text{ f} + 505 \text{ f} = 530 \text{ fF}$$

(e) At node  $G_2$  a pole is caused by  $C_{in2}$  and  $r_{o1}$

$$f_{P2} = \frac{1}{2\pi \times 530 \text{ f} \times 100 \text{ K}} = 3 \text{ MHz}$$

(f) The total capacitance at the output node is

$$C_{out} = C_{db2} + C_2$$

where, using the Miller theorem,  $C_2$  is

$$C_2 = C_{gd2} \left( 1 + \frac{1}{g_{m2}r_{o2}} \right) = 5 \text{ f} \left( 1 + \frac{1}{100} \right) = 5.05 \text{ fF}$$

$$\Rightarrow C_{out} = 5 \text{ f} + 5.05 \text{ f} = 10.05 \text{ fF}$$

Thus a third pole is caused by  $C_{out}$  and  $r_{o2}$


$$f_{P3} = \frac{1}{2\pi C_{out} \cdot r_{o2}} = \frac{1}{2\pi \times 10.05 \text{ f} \times 100 \text{ K}} = 158.4 \text{ MHz}$$

From the 3 poles:  $f_{P1} = 30.3 \text{ MHz}$ ,  $f_{P2} = 3 \text{ MHz}$ ,

$f_{P3} = 158.4 \text{ MHz}$ .  $f_{P2}$ , the pole formed at the

interface of  $Q_1$  and  $Q_2$  is dominant.

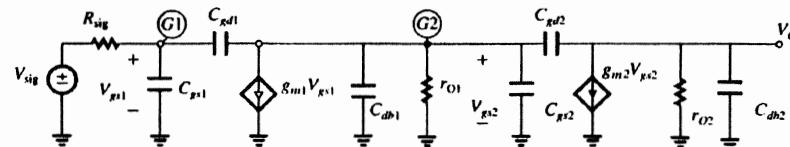(g) The pole formed at the interface of  $Q_1$  and  $Q_2$  is dominant pole. It is at the frequency of 3 MHz.



$$9.1 \quad A_f = \frac{A}{1+A\beta} = 100$$

$$A\beta = \frac{10^5}{100} - 1 = 999$$


$$\Rightarrow \beta = \frac{999}{10^5} = 9.99 \times 10^{-3}$$

$$A = 10^3, \quad A_f = \frac{10^3}{1 + 10^3(9.99 \times 10^{-3})} = 90.99$$

$$\frac{\Delta A_f}{A_f} = \frac{90.99 - 100}{100} \Rightarrow -9\%$$

9.2

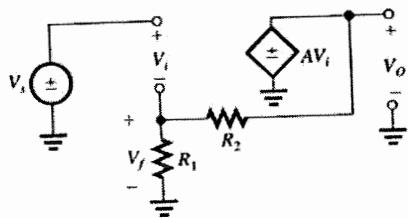(a) Replacing the op-amp with its equivalent circuit model:



$$V_f = \beta V_o = \frac{R_1}{R_1 + R_2} \cdot V_o$$

$$\Rightarrow \beta = \frac{R_1}{R_1 + R_2}$$

(b)  $R_1 = 10 \text{ k}\Omega, A_f = 10 \text{ V/V}$ , what is  $R_2$  if:

(i)  $A = 1000 \text{ V/V}$

$$A_f = \frac{A}{1 + \beta A} \Rightarrow \beta = \frac{1}{A_f} - \frac{1}{A}$$

$$= \frac{1}{10} - \frac{1}{10^3} = 0.099$$

$$\beta = \frac{R_1}{R_1 + R_2} \Rightarrow R_2 = R_1 \left( \frac{1 - \beta}{\beta} \right)$$

$$= 10 \text{ K} \frac{(1 - 0.099)}{0.099} = 91.01 \text{ k}\Omega$$

(ii)  $A = 100 \text{ V/V}$

$$\beta = \frac{1}{10} - \frac{1}{100} = 0.09;$$

$$R_2 = 10 \text{ K} \frac{(1 - 0.09)}{0.09} = 101.11 \text{ K}$$

(iii)  $A = 12$

$$\beta = \frac{1}{10} - \frac{1}{12} = 0.0167;$$

$$R_2 = 10 \text{ K} \frac{(1 - 0.0167)}{0.0167} = 588.8 \text{ k}\Omega$$

(c) if  $A$  decreases by 20%

$$(i) A = 0.8 \times 1000 = 800 \text{ V/V}$$

$$A_f = \frac{800}{1 + (0.099)(800)} = 9.975$$

$$\frac{\Delta A_f}{A} = \frac{9.975 - 10}{10} = -0.25\%$$

$$(ii) A = 0.8 \times 100 = 80 \text{ V/V}$$

$$A_f = \frac{80}{1 + (0.09)(80)} = 9.756$$

$$\frac{\Delta A_f}{A} = \frac{9.756 - 10}{10} = -2.44\%$$

$$(iii) A = 0.8 \times 12 = 9.6 \text{ V/V}$$

$$A_f = 9.6 / (1 + (0.0167)(9.6)) = 8.27$$

$$\frac{\Delta A_f}{A} = \frac{8.27 - 10}{10} = -17.26\%$$

9.3

All output voltage is fed back  $\therefore \beta = 1$

$$A_f = \frac{100}{1 + 100 \times 1} = 0.99$$

$$1 + A\beta = 1 + 100 \times 1 = 101 \equiv 40.1 \text{ dB}$$

$$V_o = 0.99 V_s = 0.99 V$$

$$V_i = V_s - V_o \beta = 1 - 0.99 = 10 \text{ mV}$$

$$A = 90 \Rightarrow A_f = \frac{90}{1 + 90 \times 1} \approx 0.989$$

$$\frac{\Delta A_f}{A_f} = \frac{0.989 - 0.99}{0.99} \equiv -0.1\%$$

9.4

$$A_f = \frac{A_0}{1 + A_0 \beta} = \frac{1}{1/A_0 + \beta} = \frac{1}{\beta(1 + 1/A_0 \beta)}$$

so  $A_f + 1/\beta$  will be within  $x\%$  when  
 $1/(A_0 \beta) = 0.01 \times x$

(a) For 1%:  $A_0 \beta = 1/0.01 = 100$   
Many possible solutions.

$$\text{Let } A_0 = 10^5 \Rightarrow A_0 \beta = 100 \Rightarrow \beta = 10^{-3}$$

(b) For 5%:  $A_0 \beta = 1/0.05 = 20$

$$\text{Let } A_0 = 10^5 \Rightarrow A_0 \beta = 20 \Rightarrow \beta = 2 \times 10^{-4}$$

(c) For 10%:  $A_0 \beta = 1/0.1 = 10$

$$\text{Let } A_0 = 10^5 \Rightarrow A_0 \beta = 10 \Rightarrow \beta = 10^{-4}$$

(d) For 50%:  $A_0 \beta = 1/0.5 = 2$

Let  $A_o = 10^5$ ;  $A_o\beta = 2 \Rightarrow \beta = 2 \times 10^{-5}$

% error	$A_o$	$A_o\beta$	$1+A_o\beta$
1	$10^5$	100	101
5	$10^5$	20	21
10	$10^5$	10	11
50	$10^5$	2	3

9.5

$0 \leq p \leq 1$  linear

(a) For  $A_o = 1$ :

$$A_{f1} = \frac{A_o}{1 + A_o\beta} = \frac{1}{1+0} = 1 \text{ V/V}$$

$$A_{f2} = \frac{1}{1 + 1 \times 0.5} = 0.667 \text{ V/V}$$

$$A_{f3} = \frac{1}{1 + 1 \times 1} = 0.5 \text{ V/V}$$

$$(b) \text{ For } A_o = 10: A_{f1} = \frac{10}{1+0} = 10 \text{ V/V}$$

$$A_{f2} = \frac{10}{1 + \frac{10}{2}} = 1.6 \text{ V/V}$$

$$A_{f3} = \frac{10}{1 + 10 \times 1} = 0.909 \text{ V/V}$$

$$(c) \text{ For } A_o = 100: A_{f1} = \frac{100}{1+0} = 100 \text{ V/V}$$

$$A_{f2} = \frac{100}{1 + \frac{100}{2}} = 1.96 \text{ V/V}$$

$$A_{f3} = \frac{100}{1 + 100} = 0.99 \text{ V/V}$$

$$(d) \text{ For } A_o = 10^4: A_{f1} = \frac{10^4}{1+0} = 10^4 \text{ V/V}$$

$$A_{f2} = \frac{10^4}{1 + 10^4/2} = 1.99 \text{ V/V}$$

$$A_{f3} = \frac{10^4}{1 + 10^4} = 0.9999 \text{ V/V}$$

9.6

$$A_o : 2 \text{ mV} \rightarrow 10 \text{ V}$$

$$A_o = 10 \text{ V} / (2 \times 10^{-3}) \text{ V} = 5000 \equiv 74 \text{ dB}$$

$$A_F : 200 \text{ mV} \rightarrow 10 \text{ V}$$

$$A_F = (10^4 / (200)) = 500 \equiv 54 \text{ dB}$$

$$A_F = \frac{A_o}{1 + A_o\beta} = \frac{5000}{1 + 5000\beta} = 500$$

$$\Rightarrow 1 + 5000\beta = 10$$

$$\Rightarrow \beta = 9/5000 = 0.0018 \equiv -54 \text{ dB}$$

$$(1 + A_o\beta) = 10 \equiv 20 \text{ dB}$$

$$A_o\beta = 5000(9/5000) = 9 \equiv 19.08 \text{ dB.}$$

9.7

$$\frac{\partial A_f}{A_f} = \frac{1}{1 + A\beta} \cdot \frac{dA}{A}$$

$$\frac{dA_f/A_f}{dA/A} = \frac{1}{1 + A\beta} \equiv -20 \text{ dB}$$

$$\Rightarrow 1 + A\beta = +20 \text{ dB} \equiv 10$$

$$\therefore A\beta = 9$$

$$\text{Require } \frac{1}{1 + A\beta} = \frac{1}{2} \Rightarrow A\beta = 1$$

9.8

$$A_f = 25; \frac{\partial A_f}{A_f} = 1\%; \frac{dA}{A} = 10\%$$

$$\frac{\partial A_f}{A_f} = \frac{1}{1 + A\beta} \cdot \frac{dA}{A} \Rightarrow 1 = \frac{10}{1 + A\beta} \Rightarrow A\beta = 9$$

Since

$$A_f = \frac{A}{1 + \beta A} \Rightarrow 25 = \frac{A}{1 + 9} \rightarrow A = 250 \text{ V/V}$$

$$\text{thus } \beta = \frac{9}{250} = 0.036$$

9.9

$$A_f = 25; \frac{\partial A_f}{A_f} = 1\%; \frac{dA}{A} = 10\%$$

$$\frac{\partial A_f}{A_f} = \frac{1}{1 + A\beta} \cdot \frac{dA}{A} \Rightarrow 1 = \frac{10}{1 + A\beta} \Rightarrow A\beta = 9$$

Since:

$$A_f = \frac{A}{1 + A\beta} \Rightarrow 25 = \frac{A}{1 + 9} \rightarrow A = 250 \text{ V/V}$$

The lowest gain is  $A - 10\% A = 250 - 25$


$$= 225 \text{ V/V and } \beta = \frac{9}{250} = 0.036$$

### 9.10

For an output stage with gain varying between 2 and 12

$$A_o = 7 \pm 5V/V \text{ i.e. } 7V/V \pm 71.43\%$$

$$A_f = 100 \pm 5\%$$

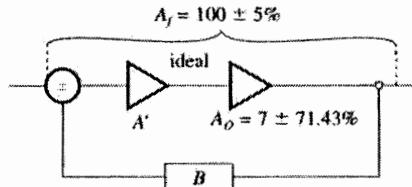

Referring to the schematic the total open-loop gain is:  $A = A' \times A_o$

Since the first stage is ideal the total open-loop gain variation is 71.43%

$$\text{Thus: } \frac{\partial A_o}{A_o} = \frac{1}{1 + \beta A} \cdot \frac{\partial A}{A} \rightarrow 5\% = \frac{71.43\%}{1 + \beta A}$$

$$\rightarrow \beta A = 13.286$$

Since

$$A_f = 100 = \frac{A}{1 + \beta A} = \frac{A}{14.286}$$

$$\Rightarrow A = 1428.6 V/V$$

$$\text{Thus, } \beta = \frac{13.286}{1428.6} = 0.0093$$

$$\text{if } \frac{\partial A_o}{A_o} = 0.5 = \frac{71.43}{1 + \beta A} \rightarrow \beta A = 141.86$$

$$\Rightarrow A_f = 100 = \frac{A}{141.86} \rightarrow A = 14286 V/V$$

$$\text{and } \beta = \frac{141.86}{14286} = 0.00993$$

Following the same procedure:

$$\text{if } A_f = 10 \text{ and } \partial A_f / A_f = 5\%$$

$$\beta A = 13.286$$

$$A = 142.86 \Rightarrow A' = \frac{142.86}{7} = 20.41 V/V$$

$$\text{if } A_f = 10 \text{ and } \partial A_f / A_f = 0.5\%$$

$$\beta A = 141.86$$

$$A = 1428.6 \Rightarrow A' = \frac{1428.6}{7} = 204.09 V/V$$

### 9.11

$$\begin{aligned} A(S) &= Am \frac{S}{S + W_L} \\ A_f(S) &= \frac{Am \frac{S}{S + W_L}}{1 + \frac{Am S}{S + W_L} \beta} = \frac{Am S}{S + W_L + Am \beta S} \\ &= \frac{Am}{1 + Am \beta} \cdot \frac{S}{S + \frac{W_L}{1 + Am \beta}} \end{aligned}$$

Thus

$$Am_f = \frac{Am}{1 + Am \beta}$$

$$W_{Lf} = \frac{W_L}{1 + Am \beta}$$

Both decreased by same amount

### 9.12

Worst case:  $A_{F1}$

$$= \frac{A_o}{1 + A_o \beta} = 9.8 \text{ (down 2\%)}$$

$$\text{full battery: } A_{F2} = \frac{2A_o}{1 + 2A_o \beta} = 10$$

$$\text{from } A_{F1}: 1 + A_o \beta = A_o / 9.8$$

$$\therefore \beta = \frac{1}{9.8} - \frac{1}{A_o}$$

$$\text{Then } A_{F2} = \frac{2A_o}{1 + 2A_o \left[ \frac{1}{9.8} - \frac{1}{A_o} \right]} = 10$$

$$\Rightarrow 1 + 2A_o \left[ \frac{1}{9.8} - \frac{1}{A_o} \right] = \frac{2A_o}{10}$$

$$\Rightarrow 2A_o \left[ \frac{1}{9.8} - \frac{1}{10} \right] = 2 - 1$$

$$\therefore 2A_o = 490$$

$$\text{[Check } \frac{2A_o}{1 + 2A_o \left[ \frac{1}{9.8} - \frac{2}{2A_o} \right] \beta_{\text{const}}} = 10$$

$$\frac{A_o}{1 + A_o \left[ \frac{1}{9.8} - \frac{1}{490} \right]} = 9.8]$$

If  $\beta$  varies by  $\pm 1\%$  the worst case for  $A_f$  is if  $\beta$  by 1%

$$A_{f1} = 9.8 = \frac{A_o}{1 + A_o \beta_{\text{new}}}$$

$$= \frac{A_o}{1 + A_o \beta 1.01} \quad \beta_{\text{new}} \triangleq 1.01 \beta$$

$$\beta = \frac{1}{9.8} - \frac{1}{A_o} = \frac{1}{9.8} - \frac{2}{490} = \frac{48}{490}$$

$$9.8(1 + A_o \beta 1.01) = A_o$$

$$9.8 \left( 1 + A_o \frac{48}{490} 1.01 \right) = A_o$$

$$\Rightarrow 2A_o = 645 \frac{V}{V}$$

### 9.13

$$A_f = \frac{A_0}{1 + A_0\beta} = 10 = \frac{100}{1 + 100\beta}$$

$$\therefore (1 + A_0\beta) = 100/10 = 10$$

$$f_L' = f_L / (1 + A_0\beta) = 100/10 = 10 \text{ Hz}$$

$$f_H' = f_H (1 + A_0\beta) = 100 \times 10 = 100 \text{ kHz}$$

If  $V_{NF} = \pm 10 \text{ mV}$ , then  $A_2\beta = 98.89$  and

$$A_2 = 10 \frac{\text{V}}{\text{V}}$$


$$\beta = 0.09899$$

If  $V_{NF} = \pm 1 \text{ mV}$ , then  $A_2\beta = 998.89$ , and

$$A_2 = 10 \frac{\text{K}}{\text{V}}, \beta = 0.099889$$
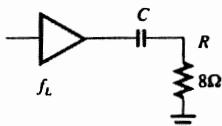
### 9.14

For an  $8\Omega$  loudspeaker and  $f_L = 100 \text{ Hz}$



$$f_L = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi \times 100 \times 8} = 199 \mu\text{F}$$

If feed-back is used and:  $A_f = 10 \text{ V/V}$ ,

$$A = 1000 \text{ V/V}$$

$$A_f = \frac{A}{1 + \beta A} \Rightarrow 1 + \beta A = \frac{1000}{10} = 100$$

$$f_{LF} = f_L / (1 + \beta A) = 100 / 100 = 1 \text{ Hz}$$

Since feed-back reduces the effective  $f_{LF}$ , then a smaller capacitor  $C$  can be chosen for a larger value of  $f_L$ .

If  $f_{LF}$  must now be 50 Hz:

$$50 = \frac{f_L}{100} \Rightarrow f_L = 5 \text{ kHz} = \frac{1}{2\pi \times 8 \times C}$$

$$\rightarrow C = 3.98 \mu\text{F}$$

### 9.15

$$V_o = \frac{V_s \cdot A_1 A_2}{1 + A_1 A_2 \beta} + \frac{V_N \cdot A_1}{1 + A_1 A_2 \beta}$$

$$= V_{SI} + V_{NF}$$

Closed loop again

$$\text{is: } \frac{V_o}{V_s} = \frac{A_1 \cdot A_2}{1 + A_1 A_2 \beta} = 10 \frac{\text{V}}{\text{V}} (1)$$

if the output ripple  $V_N$  is  $\pm 100 \text{ mV}$

$$\Rightarrow 100 \text{ mV} = \frac{1 \times 0.9}{1 + 0.9 A_2 \beta} \rightarrow A_2 \beta = 8.88$$

Substituting in (1):

$$\frac{0.9 A_2}{1 + 0.9 \times 8.88} = 10 \rightarrow A_2 = 100 \frac{\text{V}}{\text{V}}$$

$$\text{thus } \beta = \frac{8.88}{100} = 0.0888$$

Using the same procedure:

### 9.16

Nominal  $\frac{A}{1 + \beta A} = 100$ , when  $A$  reduces

$$\text{to } \frac{1}{10} \Rightarrow \frac{A / 10}{1 + \beta A / 10} = 99$$

Compare these two:

$$\beta A = 890 \beta A + 1 = 891$$

$$\Rightarrow A = 100(1 + \beta A) = 89.1 \times 10^3$$

$$\beta = \frac{890}{89.1 \times 10^3} = 0.01$$

when  $A$  increased 10 times

$$A_f = \frac{10A}{1 + 10\beta A} = \frac{89.1 \times 10^4}{1 + 8900} = 100.10$$

$$\text{when } A \rightarrow \infty \quad A_f = \frac{1}{\beta} = 100$$

### 9.17

$A_f$  has  $f_m$  high,  $A_f$  has  $A_M = 10 \text{ V/V}$

with  $f_L = 80 \text{ Hz}$ ,  $f_H = 8 \text{ kHz}$ .

$$A_F = \frac{A_1 A_2}{1 + A_1 A_2 \beta} = 100$$

Require  $f_{HF} = 40 \text{ kHz} = 8(1 + A_1 A_2 \beta)$

$$\therefore 1 + A_1 A_2 \beta = 40/8 = 5$$


$$\text{and } A_F = \frac{A_1 A_2}{5} = 100 \Rightarrow A_1 A_2 = 500$$

$$9.18 \Rightarrow A_1 = 500/A_2 = 500/10 = 50$$

$$1 + A_1 A_2 \beta = 5 \Rightarrow \beta = 4/A_1 A_2 = 4/500$$

$$\therefore \beta = 0.008$$

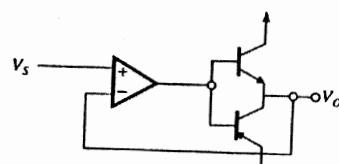
$$f_{LF} = f_L / (1 + A_1 A_2 \beta) = 80/5 = 16 \text{ Hz}$$



Dead band with be narrowed by the factor  $1 + A\beta = 1 + A$  since  $\beta = 1$

and since  $A >> 1$ ,  $1 + A \rightarrow A$
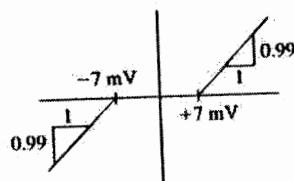
$$\therefore \text{new limits are } \pm \frac{0.7}{A} = \pm \frac{0.7}{100} = \pm 7 \text{ mV}$$



$$\text{New slope} = \text{gain} = A_f = \frac{A}{1+A}$$

$$\Rightarrow \frac{100}{1+100} = 0.99$$

9.19

For  $A = V_o/V_i = 10^2$  (select lowest  $A_0$ )  
to reduce % change in gain by factor of 10

$$1 + A\beta = 10 \Rightarrow \beta = 9/10^2$$


For  $A_2 = 10^2$ :  $A_{2F} = 10^3/10 = 10$

For  $A_1 = 10^3$ :  $A_{1F} = \frac{A}{1+\lambda\beta}$

$$\therefore A_{1F} = \frac{10^3}{1+10^3(9/10^2)} = \frac{10^3}{99} = 10.98$$

For  $A_3 = 0$ : stays saturated

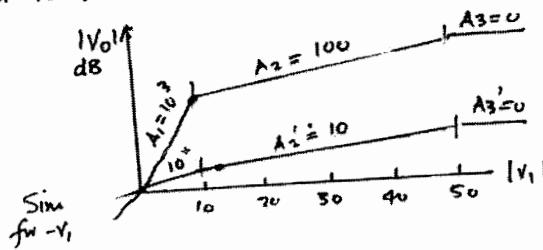[For 10mV in and  $A_1 = 10^3$ ,  $V_o = 10 V$ ?]  
[For 10mV in and  $A_2 = 10^2$ ,  $V_o = 1 V$ ]



Sim  
fw -V<sub>i</sub>

9.20

$$\beta = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} \text{ and open-loop}$$

gain 5 A

$$\Rightarrow A_f = \frac{A}{1+\beta A} = \frac{A}{1+\left(\frac{R_1 A}{R_1 + R_2}\right)}$$

$$\text{when: } A \gg 1 \rightarrow A_f \approx \frac{R_1 + R_2}{R_1}$$

$$A_f \approx 1 + \frac{R_2}{R_1}$$

For:  $A_f = 100 \text{ V/V}$ ,  $A = 10^4$ ,  $R_1 = 1 \text{ k}\Omega$

$$100 = \frac{10^4}{1 + 10^4 \times \frac{1 \text{ K}}{1 \text{ K} + R_2}}$$

$$\rightarrow 1 + \frac{10^7}{10^3 + R_2} = 10^2$$

$$\rightarrow R_2 = 100.01 \text{ k}\Omega$$

If we use the approximate result for  $A \gg 1$

$$100 = 1 + \frac{R_2}{1 \text{ K}} \rightarrow R_2 \approx 99 \text{ k}\Omega$$

If  $R_1$  is removed:


$$V_F = V_o \rightarrow \beta = 1 \rightarrow A_f = \frac{A}{1+A} \approx 1$$

9.21

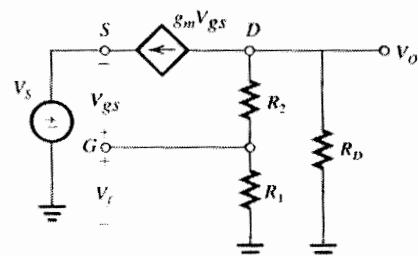(a) If  $R_2$  and  $R_1$  are removed and the transistor gate is grounded then we have a CG amplifier

Thus:  $A = g_m \cdot R_D$

Referring to Exercise 10.6, the equivalent small-signal circuit for Fig 10.7 c is:



$$\beta = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2}$$


The amount of feed-back  $1 + \beta A$  is:

$$1 + \frac{g_m R_D \cdot R_1}{R_1 + R_2}$$

(b) For a CG amplifier (with no feed-back)

$R_{in} = 1/g_m$  and  $R_D = R_D$

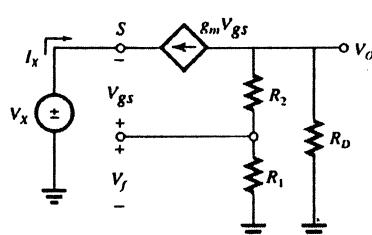(c) To obtain  $R_{inf}$  consider the following circuit



$$R_{inf} = \frac{V_x}{I_x}$$

$$I_x = -g_m V_{gs} \quad (\text{Eq 1})$$

$$V_o = I_x \cdot R_D$$

$$V_f = \frac{V_o R_1}{R_1 + R_2} = (I_x R_D) \frac{R_1}{R_1 + R_2} \quad (\text{Eq 2})$$

$$V_x = -V_{gs} + V_f \quad (\text{Eq 3})$$

Substituting Eq 1 and 2 into Eq 3:

$$V_x = \frac{I_x}{g_m} + \frac{I_x R_D R_1}{R_1 + R_2}$$


$$\Rightarrow \frac{V_x}{I_x} = \left( \frac{1}{g_m} + \frac{R_D R_1}{R_1 + R_2} \right)$$

$$\text{Rearranging: } R_{inf} = \left( \frac{1}{g_m} \right) \left( 1 + \frac{R_D R_1}{R_1 + R_2} \right)$$

Thus  $R_{inf} = R_{in} (1 + A\beta)$

The input impedance is increased by a factor of  $1 + A\beta$

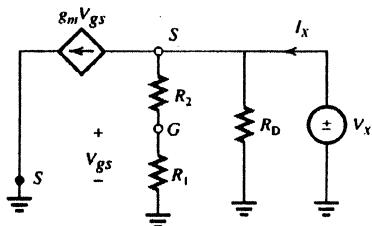To obtain  $R_{of}$  consider the following circuit:



$$R_{of} = \frac{V_x}{I_x}$$

$$I_x = g_m V_{gs} + \frac{V_x}{R_1 + R_2} + \frac{V_x}{R_D}$$

$$\text{but } V_{gs} = \frac{R_1 \cdot V_x}{R_1 + R_2}$$

$$\Rightarrow I_x = \frac{g_m R_1 V_x}{R_1 + R_2} + \frac{V_x}{R_1 + R_2} + \frac{V_x}{R_D}$$

$$= V_x \left\{ \frac{g_m R_1 + 1}{R_1 + R_2} + \frac{1}{R_D} \right\}$$

$$\Rightarrow R_{of} = \frac{V_x}{I_x} = \frac{1}{\frac{g_m R_1 + 1}{R_1 + R_2} + \frac{1}{R_D}}$$

to re-arrange let's multiply by  $\frac{R_D}{R_D}$

$$\Rightarrow R_{of} = \frac{R_D}{\frac{g_m R_1 R_D}{R_1 + R_2} + 1 + \frac{R_D}{R_1 + R_2}}$$



Since  $R_1 + R_2 >> R_D \rightarrow \frac{R_D}{R_1 + R_2} \approx 0$

$$R_{of} = \frac{R_D}{1 + \frac{g_m R_1 R_D}{R_1 + R_2}} = \frac{R_D}{1 + A\beta}$$

The output impedance is reduced by a factor of  $1 + A\beta$

## 9 . 22

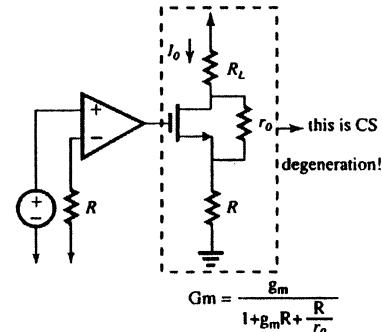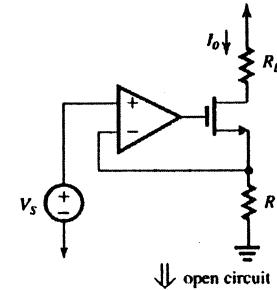(a) A positive change in  $V_S$  results in a positive change at the gate of Q, which in turn will cause  $I_O$  to increase, causing a positive change in  $V_f$



$$Gm = \frac{g_m}{1 + g_m R + \frac{R}{r_o}}$$

b)  $A = \mu \cdot G_m$

$$G_m = \frac{g_m}{1 + g_m R + \frac{R}{r_0}} \approx \frac{g_m}{1 + g_m R}$$

c)  $\beta = R$

$$d) A_f = \frac{A}{1 + \beta A} = \frac{\mu \cdot \frac{g_m}{1 + g_m R}}{1 + R\mu \frac{g_m}{(1 + g_m R)}}$$

e) when  $\beta A = \frac{R\mu g_m}{1 + g_m R} \gg 1$

$$A_f = \frac{1}{\beta} = \frac{1}{R}$$

9.23

$$\beta = \frac{V_f}{I_o}$$

$$V_f = \left( I_o \times \frac{R_M}{R_1 + R_2 + R_M} \right) \times R_1$$

$$\Rightarrow \beta = \frac{V_f}{I_o} = \frac{R_M R_1}{R_1 + R_2 + R_M}$$

To obtain  $A$ , remove  $R_1, R_2$  and  $R_M$  and ground the negative input of the OP-AMP

$$V_o = I_o R_L$$

$$V_o = \mu V_i \Rightarrow \mu V_i = I_o R_L$$

$$\rightarrow A = \frac{I_o}{V_i} = \frac{\mu}{R_L}$$


$$A_f = \frac{A}{1 + \beta A} = \frac{(\mu / R_L)}{1 + \left( \frac{R_M R_1}{R_1 + R_2} \right) (\mu / R_L)}$$

$$\text{if } \beta A \text{ is } \gg 1 \Rightarrow A_f \approx \frac{R_1 + R_2}{R_M \cdot R_1} \approx \frac{1}{\beta}$$

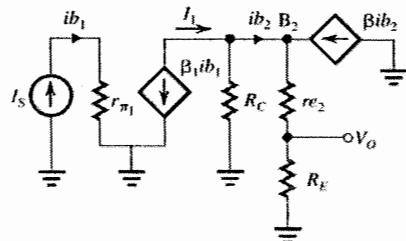9.24

The equivalent small-signal circuit


without the feed-back resistor  $R_F$  is:



$$I_I = -\beta_1 I_S$$

Reflecting  $r_{e2}$  and  $R_E$  towards the base  $B_2$

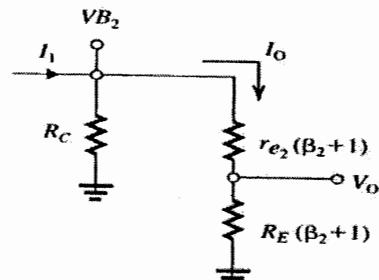But:  $\beta_2 R_E \gg R_C$  Therefore most of  $I_I$  will flow thru  $R_C$  and  $V_{B2}$  will be:



$$V_{B2} = I_I R_C = -\beta_1 I_S \cdot R_C$$

$$\text{Thus: } V_o = \frac{-\beta_1 I_S \cdot R_C \cdot R_E (\beta_2 + 1)}{(R_E + r_{e2})(\beta_2 + 1)}$$


we can also assume  $R_E \gg r_{e2}$  (e.g for

$$I_C = 1 \text{ mA}, \beta = 100 \rightarrow r_e = 25 \Omega$$

$$\text{Then: } V_o \approx -\beta_1 R_C I_S$$


$$\Rightarrow A = \frac{V_o}{I_S} = -\beta_1 \cdot R_C$$

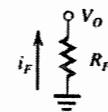To obtain  $\beta$ : if the signal voltage at the input is nearly zero:




$$\Rightarrow \beta = \frac{I_f}{V_o} = \frac{-1}{R_F}$$

To obtain  $A_f$ : At the input side:

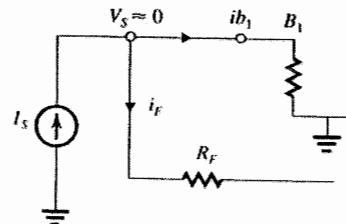

$$I_s = i_b_1 + i_F \quad i_b_1 = I_s - i_F$$

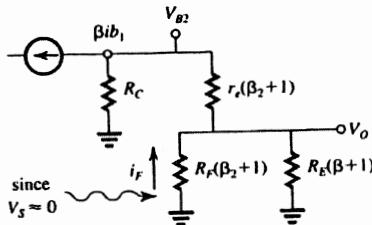At the output side, after reflecting the emitter resistors towards the base:



Recall that:  $R_C \ll \beta_1 R_E$   
 $R_E \ll R_F \rightarrow R_E \beta_2 \ll R_F \beta_2 \rightarrow R_C \ll R_F \beta_2$   
 Thus:  $R_C \parallel \{(\beta + 1)(r_e + R_F \parallel R_E)\} = R_C$   
 Therefore:

$$V_o \approx -\beta_1 i_b \times R_C = -\beta_1 (I_S - i_F) R_C$$

again, since we can neglect  $r_e$

$$V_o \approx V_{B2} = -\beta_1 (I_S - i_F) R_C$$

and  $V_o = -R_F i_F \rightarrow i_F = \frac{-V_o}{R_F}$

$$V_o = -\beta_1 I_S R_C - \beta_1 \frac{R_C}{R_F} V_o$$

$$\Rightarrow V_o \left(1 + \beta_1 \frac{R_C}{R_F}\right) = -\beta_1 R_C \cdot I_S$$

$$\Rightarrow A_f = \frac{V_o}{I_S} = \frac{-\beta_1 R_C}{1 + \beta_1 \frac{R_C}{R_F}}$$

which is the name result we would obtain from substituting  $A$  and  $\beta$  into:  $A_f = A/(1 + A\beta)$

If  $\beta_1 = 100$ ,  $R_C = R_E = 10 \text{ k}\Omega$

$R_F = 100 \text{ k}\Omega$

$$A = -100 \times 10 \text{ K} = -1 \times 10^6 \text{ V/A};$$

$$A_f = \frac{-10^6}{1 + 10^6 \times 10^{-5}} = -90.9 \text{ KV/A}$$

$$\beta = -1/100 \text{ K} = -1 \times 10^{-5}$$

### 9.25

To obtain  $A$  remove  $R_F$  and consider the small-signal response of the resulting CE:

$$V_o = -\beta I_i \cdot R_C \Rightarrow A = \frac{V_o}{I_i} = -\beta(R_C \parallel r_o)$$

if  $r_o \gg R_C \Rightarrow A \approx -\beta R_C$

If the voltage at the input is near to zero volts

$$\Rightarrow I_f = -\frac{V_o}{R_F} \rightarrow \beta_f = \frac{I_C}{V_o} = \frac{-1}{R_F}$$

$$A_f = \frac{A}{1 + \beta_f A} = \frac{-\beta R_C}{1 + \frac{\beta R_C}{R_F}}$$

For  $\beta = 100$ ,  $R_C = 10 \text{ K}$  and  $R_F = 100 \text{ K}$

$$A_f = \frac{-100 \times 10 \text{ K}}{1 + (100 \times 10 \text{ K})/100 \text{ K}} \\ = -90.9 \times 10^3 \text{ V/A}$$

### 9.26

$$A_F = \frac{A}{1 + A\beta} = \frac{10^3 \times 2}{1 + 2 \cdot 10^3 \times 10^{-5}} = 9.95 \text{ V}$$

$$R_{if} = R_i(1 + A\beta) = 1/201 = 201 \text{ K}\Omega$$

$$R_{of} = R_o/(1 + A\beta) = 1/201 = 4.975 \text{ K}\Omega$$

### 9.27

Here  $R_o$  is lowered by amount of feedback

$$\text{i.e., } (1 + A\beta) = 80$$

$$\Rightarrow AB = 79$$

$$R_o = R_{of}(1 + A\beta) = 100 \times 80 = 8 \text{ K}\Omega$$

### 9.28

The derivations

are also valid for the case when  $A$  is a function of frequency


To obtain  $Z_{if}$  and  $Z_{of}$  we must replace  $A$  by its  $A(S)$  form:

$$Z_{if} = R_i \cdot \left(1 + \frac{A_o}{\left(1 + \frac{S}{\omega_H}\right)} \cdot \beta\right)$$

$$Z_{of} = \frac{R_o}{1 + \frac{A_o}{\left(1 + \frac{S}{\omega_H}\right)} \beta}$$


To obtain the equivalent circuits:
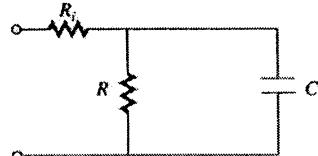
$$Z_{\text{if}} = R_i + \frac{R_i A_o \beta}{1 + \frac{S}{\omega_H}} \text{ which corresponds to:}$$



$$\text{where } R \parallel C = \frac{R}{1 + R C_s}; \text{ thus: } R = R_i A_o \beta$$
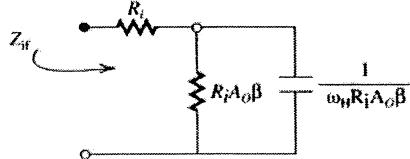
$$R C = \frac{1}{\omega_H} \rightarrow C = \frac{1}{\omega_H \cdot R_i A_o \beta}$$




$$Z_{\text{af}} = \frac{R_o}{1 + \frac{A_o \beta}{1 + \frac{S}{\omega_H}}} = \frac{1}{R_o + \frac{(A_o \beta / R_o)}{1 + \frac{S}{\omega_H}}}$$

$$= \frac{1}{\frac{1}{R_o} + \frac{1}{K} + \frac{S}{\omega_H K}}$$

$$\text{where } K = \frac{A_o \beta}{R_o}$$

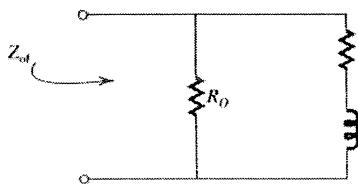This is equivalent to a circuit of the form:




$$R = \frac{1}{K} = \frac{R_o}{A_o \beta}$$

$$L = \frac{1}{\omega_H \cdot K} = \frac{R_o}{\omega_H A_o \beta}$$

### 9.29

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

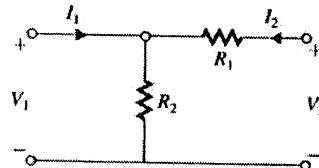

$$(a) h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} \Omega$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{R_2}{R_1 + R_2} \text{ V/V}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{-R_2}{R_1 + R_2} \text{ A/A}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{R_1 + R_2} \text{ A/V}$$

$$(b) \beta = \left. \frac{V_1}{V_2} \right|_{I_1=0} = h_{12} = \frac{R_2}{R_1 + R_2}$$


$$\Rightarrow \frac{R_1}{R_2} = \frac{1}{\beta} - 1 = 99$$

$$\Rightarrow R_2 = R_1 / 99 = 10.1 \Omega$$

Thus  $h_{11} = 10 \Omega$ ;  $h_{12} = 0.01 \text{ V/V}$

$$h_{21} = -0.01 \text{ V/V}; h_{22} = 0.99 \times 10^{-3} \text{ V}$$

(c)

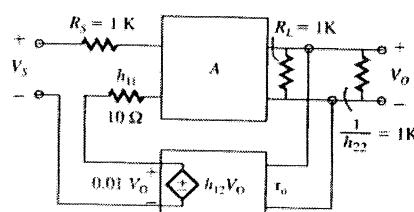

### 9.30

$$R_{\text{of}} = \frac{R_o}{1 + A\beta} = \frac{1000}{1 + A\beta} = 100 \Omega$$

$$\Rightarrow 1 + A\beta = 1000/100 = 10$$

$$\Rightarrow A_F = \frac{A}{1 + A\beta} = \frac{100}{10} = 10 \text{ v/v}$$

$$\text{If } \beta = 1: R_{\text{of}} \Rightarrow \frac{R_o}{1 + A} = \frac{1000}{1 + 10^4} = 9.9 \Omega$$

9.31

(a) If the loop gain is large  $\frac{V_o}{V_s} \approx \frac{1}{\beta}$

$$\beta = \frac{V_I}{V_O} = \frac{R_1}{R_1 + R_2} = \frac{1}{1+10}$$

$$= \frac{1}{11} \rightarrow \frac{V_O}{V_S} = \frac{1}{\beta} = 11 \text{ V/V}$$

(b) To solve for  $i_e$ , are  $i_a$ :

$$\text{At the base of } Q_1: iR_1 + iR_2 = i_{e2} - I_2$$

$$\left( \frac{i_{e1}R_S + 0.7}{R_1} \right) + \frac{i_{e1}}{\beta + 1} = i_{e2} - I_2$$

Substituting and re-organizing:

$$(0.1099) i_{e1} + 1.7 \cdot 10^{-3} = i_{e2}$$

$$i_a + i_{b2} = I_1$$

$$\Rightarrow \frac{\beta_1}{\beta_1 + 1} i_{e1} + \frac{1}{\beta_2 + 1} i_{e2} = I_1$$

$$\Rightarrow i_{e2} = (\beta_2 + 1) \left( I_1 - \frac{\beta_1}{\beta_1 + 1} i_{e1} \right)$$

$$= 101 \left( 0.1 \text{ m} - \frac{100}{101} i_{e1} \right)$$

$$0.1099 i_{e1} + 1.7 \times 10^{-3} = 10.1 \times 10^{-3} - 100 i_{e1}$$

$$\Rightarrow i_{e1} = 83.08 \mu\text{A}$$

$$\text{and: } i_{e2} = 1.708 \text{ mA}$$

At the base of  $Q_1$ :

$$V_{B1} = i_{e1} \cdot R_S + 0.7 = 0.708 \text{ V}$$


$$V_{R2} = V_{E2-B1} = R_2(i_{e2} - I_2)$$

$$= 10 \text{ k}(\text{1.708 m} - \text{1 m}) = 7.08 \text{ V}$$


$$V_{E2} = V_{B1} + V_{E2-B1} = 0.708 + 7.08 = 7.788 \text{ V}$$

c) A-circuit

(Figure a)

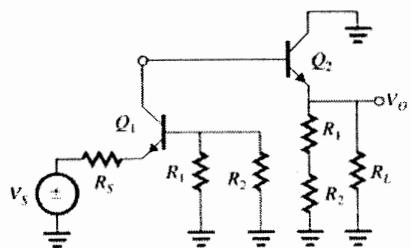

(Figure b)

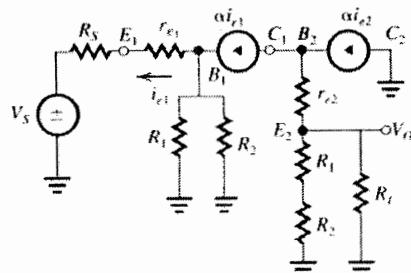

$$R_i = R_S + r_{e1} + \frac{R_1 \parallel R_2}{\beta + 1}$$

$$r_{e1} = \frac{V_T}{i_{e1}} = \frac{25 \text{ mV}}{83.08 \mu\text{A}} = 301 \Omega$$

$$R_i = 100 + 300 + \frac{1 \text{ k} \parallel 10 \text{ k}}{101}$$

$$R_i = 409 \Omega$$

$$R_o = R_L \parallel (R_1 + R_2)$$

$$= 1 \text{ k} \parallel (1 \text{ k} + 10 \text{ k}) = 916 \Omega$$

To obtain A: (see figure on previous page)

$$V_O = -\alpha i_{e1} \times (\beta + 1) \{ (R_1 + R_2) \parallel R_L \} \quad (1)$$

$$i_{e1} = -V_S / \{ R_S + r_{e1} + (R_1 \parallel R_2) / (\beta + 1) \} \quad (2)$$

Combining (1) & (2):

$$\Rightarrow V_O = \frac{\alpha V_S (\beta + 1) \{ (R_1 + R_2) \parallel R_L \}}{R_S + r_{e1} + (R_1 \parallel R_2) / (\beta + 1)}$$

$$A = \frac{V_O}{V_S} = \frac{\beta \{ (R_1 + R_2) \parallel R_L \}}{R_S + r_{e1} + (R_1 \parallel R_2) / (\beta + 1)}$$

$$= \frac{\beta R_O}{R_i} = 100 \times \frac{916}{409}$$

$$A = 224 \text{ V/V}$$

$$\text{d) As in part a)} \beta = \frac{R_1}{R_1 + R_2} = \frac{1}{11} = 0.0909$$

$$\text{e) } A_f = \frac{A}{1 + \beta A} = \frac{224}{1 + 224 \times 0.0909} = 10.48$$

$$R_{\text{ff}} = R_i(1 + A\beta) = 409 \times 21.36 = 8.7 \text{ k}\Omega$$

$$R_{\text{in}} = R_{\text{ff}} - R_S = 8.6 \text{ k}\Omega$$

$$R_{\text{out}} = 1/(1/43 - 1/1 \text{ k}) = 44.9 \Omega$$

$$\Delta A_f = \frac{10.48 - 11}{11} = -4.73\%$$

9.32

 $Q_3 + Q_4$  form current multiplier

$$\times 120/40 = \times 3$$

$$g_{m1} = 2\sqrt{\frac{1}{2}120(20/1)100} \approx 693 \mu A/V$$

$$g_{m5} = 2\sqrt{\frac{1}{2}60(20/1)1000} \approx 1550 \mu A/V$$

$$g_{m3} = 2\sqrt{\frac{1}{2}60(40/1)100} \approx 693 \mu A/V$$

$$g_{m4} = 2\sqrt{\frac{1}{2}60(120/1)300} \approx 2078 \mu A/V$$

$$g_{m2} = g_{m1} = 693 \mu A/V$$

$$r_{o1} = 24/100 \Rightarrow 240 K\Omega$$

$$r_{o2} = 24/100 \Rightarrow 240 K\Omega$$

$$r_{o3} = 24/100 \Rightarrow 240 K\Omega$$

$$r_{o4} = 24/300 \Rightarrow 80 K\Omega$$

$$r_{o5} = 24/100 \Rightarrow 24 K\Omega$$

(c) Open-loop gain  $A\beta \approx g_{m1}(r_{o1}||r_{o3}) \times 1$ 

$$\left[ \left( 3 \times g_{m1} \right) \left( \frac{r_{o4}}{3} \right) \right] \equiv g_{m1} r_{o1}$$

$$\beta = 1 : \therefore A \approx g_{m1}(r_{o2}||r_{o3})$$

$$\Rightarrow A \approx 693 \times 120 \times 10^{-3} = 84$$

$$(d) A_F = \frac{A}{1+A\beta} = \frac{84}{1+84} = 0.988 V/V$$

$$R_o = r_{o5} || r_{o5} = 12 K\Omega$$

$$R_{ref} = R_o / (1+A\beta) = 12/84 = 140 \Omega$$

(e) To obtain  $V_o/V_s = 5$  we could change direct connection from  $G_{S5}$  to  $G_{ZG}$  by voltage divider  $R_1/(R_1+R_2)$  to change  $\beta$  from 1 to  $1/5.3$ . Then


$$A_F = \frac{84}{1+84 \times 1/5.3} = \frac{84}{16.8} = 5$$

$$\text{Now } 1+A\beta = 16.8$$

$$R_{ref}'' = R_o / (1+A\beta'') = 12/16.8 = 714 \Omega$$

9.33

a) Transistors  $Q_1$  and  $Q_2$  are used in CS configuration. Therefore an increase in  $V_t$  causes the small-signal drain voltage of  $Q_1$  to increase, followed by a voltage increase at the drain of  $Q_2$ . Transistor  $Q_3$  is used in CD configuration. An increase in gate voltage at  $Q_3$  results in an increase at the output  $V_o$  (source of  $Q_3$ ) which through the voltage dividing feed-back causes  $V_t$  to increase. The feed-back is indeed negative.

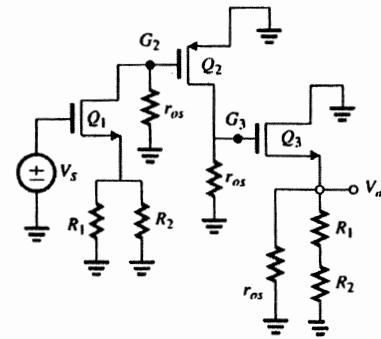b) If the loop gain  $1 + A\beta$  is large then  $A\beta \gg 1$ 

$$A_F = \frac{A}{1 + A\beta} \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_1} = 10$$

c) Find DC voltages :  $V_{ds} - V_t = V_{ov} \rightarrow V_{gs}$   
 $= V_{ov} + V_t$  for all transistors  $|V_{gs}| = 0.2 + 0.5 = 0.7 V$ .

Then:

$$V_{s1} = V_{DC} - V_{gs1} = 0.9 - 0.7 \rightarrow V_{s1}$$

$$= 0.2 V$$

$$V_{GS} = 0.2 V$$

$$V_{g1} = V_{GS} + V_{s1} = 0.7 + 0.2 = 0.9 V$$

$$V_{g2} = V_{ov} - V_{gs2} = V_{ov} - 0.7$$

For all current sources to operate in saturation

$$|V_{DS}| \geq |V_{ov}| \quad |V_{ov}| = 0.2 V$$

$$\text{For source } I_1 : |V_{DS}| = V_{DD} - V_{g2} = 0.7 V$$

$$I_1 : V_{bs} = V_{g1} = 0.9 V$$

$$I_2 : V_{as} = V_{g2} = 0.2 V$$

d) obtain the A-circuit

Load of feed-back network at the input:  $R_1 \parallel R_2$ Load of feed-back network at the output:  $R_1 + R_2$ 

The A-circuit is:

Where  $r_{os} = r_o$  is the output resistance of the current sources

### 9.34

Gain of each stage:

$$\begin{cases} \text{All } g_m's = 2I_D/V_{OV} = 2 \times 0.1 \text{ mA}/0.2 \\ \quad = 1 \text{ mA/V} \\ \text{all } r_o's = V_A/I_D = 10/0.1 \text{ mA} = 100 \text{ k}\Omega \end{cases}$$

$$\text{For } Q_1: A_{V1} = \frac{V_{G2}}{V_S} = g_{m\text{eff}}(r_{o\text{eff}} \parallel r_{OS})$$

$$\frac{V_{G2}}{V_S} = \frac{g_{m1}}{1 + g_{m1}R_S} \cdot (r_{O1}(1 + g_{m1}R_S) \parallel r_{OS})$$

$$R_S = R_1 \parallel R_2$$

$$R_S = 2 \text{ K} \parallel 18 \text{ K} = 1.8 \text{ K} \text{ and } 1 + g_m R_S = 1 + 1.8 = 2.8$$

$$\Rightarrow \frac{V_{G2}}{V_S} = \frac{1}{2.8}[(100 \text{ K} \times 2.8) \parallel 100 \text{ K}]$$

$$= 26.3 \text{ V/V}$$

For  $Q_2$ :

$$A_{V2} = \frac{V_{G3}}{V_{G2}} = g_{m2}(r_{O2} \parallel r_{OS})$$

$$r_{O2} = r_{os}$$

$$g_{m2} = g_m$$

$$\frac{V_{G3}}{V_{G2}} = g_m \frac{r_O}{2} = 1 \text{ mA} \times \frac{100 \text{ K}}{2} = 50 \text{ V/V}$$

For  $Q_3$ :

$$r_{OS} \parallel (R_1 + R_2) = 100 \text{ K} \parallel (18 \text{ K} + 2 \text{ K}) = 16.7 \text{ k}\Omega$$

For a common-drain amplifier:

$$A_V = \frac{r_O \parallel R_L}{(r_O \parallel R_L) + \frac{1}{g_m}}$$

$$\text{where } R_L = r_{OS} \parallel (R_1 + R_2)$$

$$\Rightarrow A_{V3} = \frac{V_O}{V_{G3}} = \frac{100 \text{ K} \parallel 16.7 \text{ K}}{(100 \text{ K} \parallel 16.7 \text{ K}) + 1/1 \text{ mA}} = 0.93$$

Find the overall voltage-gain:

$$A = A_{V1} \cdot A_{V2} \cdot A_{V3} = 26.3 \times 50 \times 0.93 = 1223 \text{ V/V}$$

$$(e) \text{ Find } \beta: \beta = \frac{R_1}{R_1 + R_2} = \frac{2}{2 + 18} = 0.1$$

$$(f) A_f = \frac{V_O}{V_S} = \frac{A}{1 + A\beta} = \frac{1223}{1 + 0.1 \times 1223} = 9.92 \text{ V/V}$$

$$\text{which is } \approx \frac{1}{\beta} = 10 \text{ as found in (b)}$$

(g) For the common-drain stage:

$$R_o = \frac{1}{g_m} \parallel (r_{OS} \parallel R_1 + R_2) = 1 \text{ K} \parallel 16.7 \text{ K} = 944 \Omega$$

$$R_{O\text{eff}} = \frac{R_O}{1 + A\beta} = \frac{944}{1 + 0.1 \times 1223} = 7.66 \Omega$$

Since  $R_L = \infty \Rightarrow R_{out} = R_{O\text{eff}}$

(a)  $i_{D1} = I_{ref}$

$$i_{D1} = i_{D2} = i_{D3} = i_{D4} = 50 \mu\text{A} \Rightarrow i_{D7} = 100 \mu\text{A}$$

$$i_{D8} = i_{D9} = 250 \mu\text{A}$$

$$\text{For } Q_6: 2.5 \text{ V} - I_{ref} \times 80 \text{ K} = -2.5 \text{ V} + V_{GS6} = -1.5 \text{ V}, V_{GS6} = 0.25 \text{ V}$$

$$V_{GS6} = V_a + V_{ov} = 0.75 + 0.25 = 1 \text{ V}$$

$$I_{ref} = \frac{4}{800 \text{ K}} = 0.05 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_6 V_{ov}^2$$

$$= \frac{1}{2} 100 \mu \left(\frac{W}{L}\right)_6 (0.25)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_6 = \frac{16}{1}$$

For  $Q_7$  and  $Q_8$ :

$$I_{D7} = 100 \mu\text{A} \rightarrow \left(\frac{W}{L}\right)_7 = \frac{32}{1}$$

$$I_{D8} = 250 \mu\text{A} \rightarrow \left(\frac{W}{L}\right)_8 = \frac{80}{1}$$

For  $Q_1$  and  $Q_2$ :

$$I_{D1,2} = 50 \mu\text{A} \rightarrow (W/L)_{1,2} = 16/1$$

For  $Q_3$  and  $Q_4$ : Since  $\mu_p C_{ox} = \frac{1}{2} \mu_n C_{ox}$  and

$$I_{D1} = I_{D2} = I_{D3} = I_{D4}$$

$$\left(\frac{W}{L}\right)_{3,4} = 2 \times \left(\frac{W}{L}\right)_{1,2} = \frac{32}{1}$$

For  $Q_5$ : Transistor  $Q_5$  must be sized such as

$$V_{DS5} = 0 \text{ V}$$

$$\text{Since: } V_{GS4} = V_{GS1} = V_{GS3}$$

$$\Rightarrow (2.5) \text{ V} - V_{GS3} - V_{GS5} = 0 \text{ V}$$

$$V_{GS3} = V_{IP} = +0.75 \text{ V} + 0.25 \text{ V} = 1 \text{ V}$$

$$\Rightarrow V_{GS5} = 2.5 - V_{GS3} = 1.5 \text{ V}$$

$$\Rightarrow V_{DS5} - V_{DS3} - V_{th} = 1.5 - 0.75 = 0.75 \text{ V}$$

$$\Rightarrow 250 \mu = \frac{1}{2} 100 \mu \left(\frac{W}{L}\right)_5 (0.75)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_5 \approx 9$$

(b) The common-range is the range of common-mode input voltage in which  $Q_1$ ,  $Q_2$ , and  $Q_3$  remain in saturation.

$Q_1$  and  $Q_2$  will enter the triode region when:

$$V_{G1,2} = V_{D1,2} + V_{th} = 1.5 + 0.75 = 2.25 \text{ V}$$

$Q_3$  will enter the triode region when:

$$V_{G1,2} = V_{G7,2} - V_{th} + V_{GS1,2} = 1 - 0.75 + 1 = 1.25 \text{ V}$$

Thus, the common-mode input range is:

$$1.25 \text{ to } 2.25 \text{ V}$$

$$(c) \text{ Find } g_m: g_m = \frac{2I_D}{V_{OV}} = \frac{100 \mu}{0.25} = 0.4 \text{ mA}$$

$$Q_5: V_{OV} = V_{GS5} - V_{th} = V_{GS} - V_{SS} - V_{th} = 2.5 \text{ V} - 1 \text{ V} - 0.75 \text{ V} - 0.75 \text{ V}$$


$$g_m = \frac{500 \mu}{0.75} = 0.67 \text{ mA/V}$$

$$(d) r_O = V_A/I_O$$

$$r_{O1} = r_{O2} = r_{O3} = r_{O4} = \frac{10}{50 \mu} = 200 \text{ k}\Omega$$

$$r_{O5} = r_{O8} = \frac{10}{250 \mu} = 40 \text{ k}\Omega$$

(e) A-circuit:

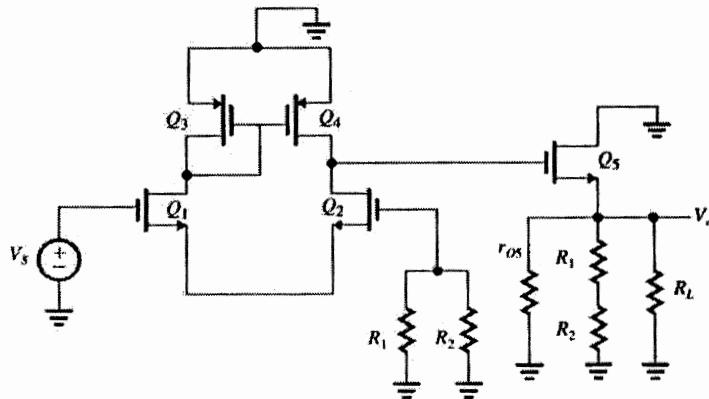

Gain: For the active-loaded differential path:

$$A_r = g_m(r_{os} \parallel r_{ot}) = 0.4 \text{ m} \times \frac{200 \text{ K}}{2} = 40 \frac{\text{V}}{\text{V}}$$

For the common drain

$$\text{stage: } A_1 = \frac{r_{os} \parallel R'_L}{(r_{os} \parallel R'_L) + \frac{1}{g_{ms}}}$$

where  $R'_L = r_{os} \parallel R_L (R_1 + R_2) = 22.2 \text{ k}\Omega$


$$\Rightarrow A_2 = \frac{40 \text{ K} \parallel 22.2 \text{ K}}{(40 \text{ K} \parallel 22.2 \text{ K}) + \frac{1}{0.67 \text{ m}}} = 0.91$$

Total gain:

$$A = A_1 \times A_2 = 40 \times 0.91 = 36.4 \frac{\text{V}}{\text{V}}$$

If
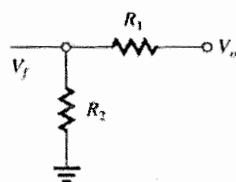
$$A_f = 10 \frac{\text{V}}{\text{V}} = \frac{A}{1 + A\beta} \Rightarrow \beta = \frac{1}{A_f} - \frac{1}{A} - \frac{1}{10} - \frac{1}{36.4} = 0.0725$$



$$\beta = \frac{R_2}{R_1 + R_2}$$

and  $R_1 + R_2 = 100 \text{ k}\Omega$

$$\Rightarrow R_2 = 0.0725 \times 100 \text{ K} = 7.25 \text{ k}\Omega$$

$$R_1 = 100 \text{ K} - 7.25 \text{ K} = 92.25 \text{ k}\Omega$$

(f) For the common drain stage

$$R_O = \frac{1}{g_{ms}} \parallel R'_L = 14.3 \text{ K} \parallel 1.5 \text{ K} = 1 \text{ k}\Omega$$

$$R_{of} = \frac{R_O}{1 + A\beta} = \frac{1 \text{ K}}{1 + 36.4 \times 0.0725} = 275 \text{ }\Omega$$

Excluding  $R_i$ :

$$R_{out} = 1 / \left( \frac{1}{275} - \frac{1}{100 \text{ K}} \right) = 276 \text{ }\Omega$$

### 9.35

(a)  $V_i$  is taken across  $R_i$ .

If  $V_i$  increases, so does the current at the output of  $A_1$ , and the voltage at the output of  $A_2$ . It follows that  $V_o$  increases and a portion of it is sampled by the Resistor divider  $R_i / (R_i + R_2)$ .

(b) Refer to circuit diagram.

(c) A-circuit

$$A = \frac{V_o}{V_s} = \left( \frac{82 \text{ K}}{82 \text{ K} + 9 \text{ K} + 10 \text{ K} \parallel 90} \right) \times \left( \frac{20 \times 5 \text{ K}}{3.2 \text{ K} + 5 \text{ K}} \right) \times (20 \times (20 \parallel 20)) \times \left( \frac{100 \text{ K} \parallel 1 \text{ K}}{100 \text{ K} \parallel 1 \text{ K} + 1 \text{ K}} \right)$$

$$A = (0.82) \times (12 \cdot 19) \times (200) \times (0.5)$$

$$A = 1000 \text{ V/V}$$

$$(d) \beta = \frac{10 \text{ K}}{10 \text{ K} + 90 \text{ K}} = 0.1$$

$$1 + A\beta = 1 + 0.1 \times 1000 = 101$$

$$(e) A_f = \frac{1000}{1 + 100} = 9.9 \text{ V/V}$$

$$(f) R_i = 82 \text{ K} + (10 \text{ K} \parallel 90 \text{ K}) + 9 \text{ K}$$

$$= 100 \text{ K}$$

$$R_{if} = R_i \cdot (1 + A\beta) = 100 \text{ K}(101)$$

$$= 10.1 \text{ M}\Omega$$

$$R_o = 10.1 \text{ M} - 9 \text{ K} \approx 10.1 \text{ M}\Omega$$

$$(g) R_o = (1 \text{ K} \parallel 100 \text{ K} \parallel 1 \text{ K}) = 500 \Omega$$

$$R_{ot} = \frac{R_o}{1 + A\beta} = \frac{500}{101} \approx 5 \Omega$$

$$\text{W/O } R_L : R_{out} = \frac{1}{\frac{1}{5} - \frac{1}{1 \text{ K}}} = 5.02 \Omega$$

$$(h) \text{ If } f_H = 100 \text{ Hz} \rightarrow f_H = 100 \times 101 = 10.1 \text{ kHz}$$

$$(i) \text{ if } A_1 = \frac{1}{2} A_1 \Rightarrow A = \frac{1000}{2} = 500$$

$$A_f = \frac{500}{1 + 50} = 9.8$$


$$\frac{\Delta A_f}{A_f} = \frac{9.8 - 9.9}{9.9} = -1.01\%$$

9.36

$$A = G_m = 100 \text{ mA/V} \quad \beta = 0.1 \text{ V/mA}$$

$$r_{in} = 10 \text{ k}\Omega, r_{out} = 100 \text{ k}\Omega$$

A-circuit

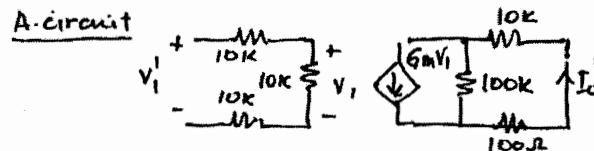

$$V_i' = V_i \cdot \frac{10}{10 + 10 + 10.1} = V_i / 3$$

$$I_o' = \frac{G_m V_i' 100}{100 + 10 + 0.1} = 30.28 V_i' \text{ mA}$$

$$A = \frac{I_o'}{V_i} = 30.28 \text{ mA/V}$$

$$A_f = \frac{A}{1 + A\beta} = \frac{30.28}{1 + 30.28(0.1)} = 7.52 \text{ mA/V}$$

$$R_L = R_S + R_{1d} + R_1 = 30 \text{ k}\Omega$$

$$R_{if} = R_L (1 + A\beta) = 120.8 \text{ k}\Omega$$

$$R_{in} = R_{if} - R_S = 110.8 \text{ k}\Omega$$

$$R_o = R_L + R_{op} + R_2 = 110.1 \text{ k}\Omega$$


$$R_{of} = R_o (1 + A\beta) = 143.4 \text{ k}\Omega$$

$$R_{out} = R_{of} - R_L = 43.4 \text{ k}\Omega$$

9.37

$$(a) A_f = \frac{A}{1 + A\beta} \text{ if } A \text{ is large then } A_f \approx \frac{1}{\beta} \\ = 0.1 \text{ A/V}$$

To obtain  $\beta$ :

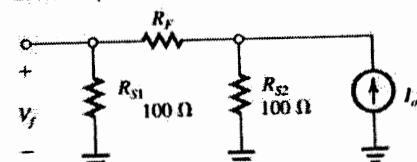


$$\beta = \frac{V_f}{I_o}$$

$$\beta = \frac{R_{S2} \cdot R_{S1}}{R_{S2} + R_F + R_{E1}} = \frac{100 \times 100}{100 + R_F + 100} \\ = \frac{10^4}{200 + R_F}$$

$$\text{If } \frac{1}{\beta} = 0.1 \rightarrow R_F = 800 \Omega$$

(b) A-circuit:

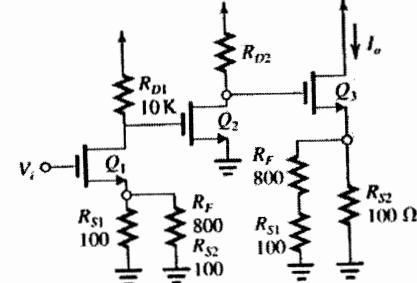

To obtain A:

For the first stage:

$$\frac{V_{D1}}{V_i} = \frac{-g_m \cdot R_{D1}}{1 + g_m (R_S \parallel R_F \parallel R_{S2})}$$

$$\text{Substituting: } g_m = 4 \text{ mA/V}$$

$$R_{D1} = 10 \text{ k} \Omega (R_{S1} \parallel R_F \parallel R_{S2}) = 90 \Omega$$

$$\frac{V_{D1}}{V_i} = -29.4 \text{ V/V}$$

For the second stage:

$$\frac{V_{D2}}{V_{D1}} = -g_m R_{D2} = -4 \times 10 = -40 \text{ V/V}$$

$$\text{For the third stage: } \frac{I_o}{V_{D2}} = \frac{I_{D3}}{V_{G3}} \\ = \frac{1}{1/g_m \parallel R_{S2} \parallel (R_{S1} \parallel R_F)}$$

$$\text{Substituting: } g_m = 4 \text{ mA/V } (R_{S2} \parallel R_{S1} \parallel R_F) = 90 \Omega$$

$$\frac{I_o}{V_{D2}} = 3 \text{ mA/V}$$

Combining the gain of the three stages:

$$A = \frac{I_o}{V_i} = -29.4 \times -40 \times 3 \times 10^{-3}$$

$$= 3.53 \text{ A/V}$$

$$(e) 1 + A\beta = 1 + 3.53 \times 10 = 36.3$$

$$A_f = \frac{V_o}{I_s} = \frac{A}{1 + A\beta} = \frac{3.53}{36.3} = 0.097 \text{ A/V}$$

The design value for  $A_f$  is 0.1 A/V

$$\frac{\Delta A_f}{A_f} = -\frac{0.003}{0.1} = -3\%$$

To change  $A_f$  such as it gets closer to 0.1 A/V  $R_f$  must be reduced, this will increase both the values of  $A$  and  $B$

$$(d) R_{o3} = r_{o3} + [R_{S2} \parallel (R_F + R_{S1})]$$


$$= 20 \text{ K} + 90 \approx 20 \text{ k}\Omega$$

$$R_{out} = R_{of} = (1 + A\beta)R_{o3} = 36.3 \times 20 \text{ K}$$

$$= 726 \text{ k}\Omega$$

(e) If the output is taken at  $V_{oc}$ :

The feed-back network changes to:

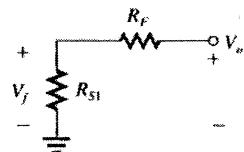


$$\beta = \frac{100}{800 + 100} = 0.111$$

Therefore the A-circuit changes at the source of  $Q_1$  to:

$$R_{S1} \parallel R_f = 100 \parallel 800$$

$$= 88.9 \Omega$$

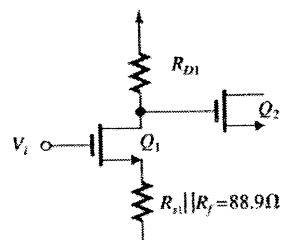

For the first stage:

$$\frac{V_{D1}}{V_i} = \frac{-g_m R_{D1}}{1 + g_m ((R_{S1} \parallel R_f))}$$

$$= -29.5 \text{ V/V}$$

$$\text{For the second stage: } \frac{V_{D2}}{V_{D1}}$$

$$= -40 \text{ V/V (unchanged)}$$

For the third stage:


$$\begin{aligned} \frac{V_{D2}}{V_{D1}} &= \frac{V_{S3}}{V_{G3}} \\ &= \frac{R_{S2} \parallel (R_F + R_{S1})}{1/g_m + R_{S2} \parallel (R_F + R_{S1})} \\ &= 0.265 \text{ V/V} \end{aligned}$$

Combining the gains of all three stages:

$$\begin{aligned} A &= \frac{V_o}{V_s} = -29.5 \times -40 \times 0.265 \\ &= 312.7 \text{ V/V} \\ (f) 1 + A\beta &= 1 + 312.7 \times 0.111 = 35.74 \\ R_{out2} &= (1 + A\beta)R_o \\ &= (1 + A\beta)(R_{S2} \parallel R_{S1} + R_F) \parallel r_o \parallel \frac{1}{g_m} \\ &= 35.74 \times (90 \parallel 20 \text{ K} \parallel 250) \\ &= 2.35 \text{ k}\Omega \end{aligned}$$

### 9.38

(a) The  $\beta$  circuit:

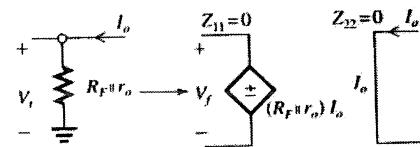


$$\beta = \frac{V_f}{I_o} = \frac{R_F r_o}{R_F + r_o}$$

$$A_f = \frac{A}{1 + A\beta} \text{ for } AB \gg 1, A_f \approx \frac{1}{\beta} \text{ if }$$

$$A_f = 10 \frac{\text{mA}}{\text{V}} \Rightarrow \beta = 100 \Omega$$

$$R_F = 100.5 \Omega$$

(b) The A-circuit:

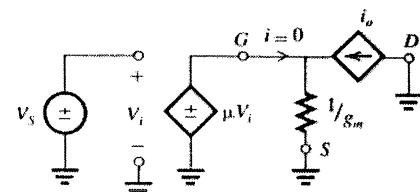

$$\mu = 1000 \text{ V/A}$$


$$g_m = 2 \text{ mA/V}$$

$$r_o = 20 \text{ K}$$

$$A = \frac{I_o}{V_s} = \mu g_m = 2 \text{ A/V}$$

$$\begin{aligned} (c) AB &= \mu g_m (R_F \parallel r_o) = 2 \times 100 = 200 \\ 1 + A\beta &= 201 \end{aligned}$$

This figure is for 9.39

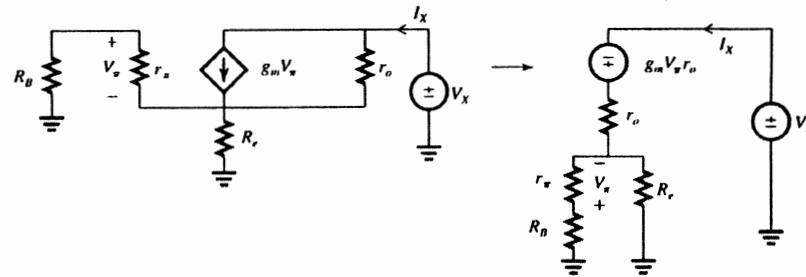

$$(d) A_f = \frac{A}{1 + A\beta} = \frac{2}{201} = 9.95 \text{ mA/V}$$

$$(e) R_O = r_o \Rightarrow R_{of} = r_o(1 + A\beta) \\ = 20 \text{ k} \times 201 = 4.02 \text{ M}\Omega$$

9.39

$$V_\pi = -\frac{r_\pi I_X \cdot R_e}{R_e + R_B + r_\pi}$$

$$V_X + g_m V_\pi r_o = I_X \{ r_o + (R_e \parallel r_\pi + R_B) \}$$

$$V_X = \frac{r_\pi \cdot R_e}{R_e + R_B + r_\pi} g_m r_o I_X$$

$$\frac{V_X}{I_X} = r_o + (R_e \parallel r_\pi + R_B)$$

$$= I_X \{ r_o + R_e \parallel (r_\pi + R_B) \}$$

$$\frac{V_X}{I_X} = r_o + \left( R_e \parallel (r_\pi + R_B) + g_m r_o \frac{r_\pi R_e}{R_e + R_B + r_\pi} \right)$$

$$\left\{ 1 + g_m r_o \cdot \frac{r_\pi \cdot R_e}{R_e + R_B + r_\pi} \times \frac{R_e + R_B + r_\pi}{R_e(r_\pi + R_B)} \right\}$$


$$R_O = r_o + R_e \parallel (r_\pi + R_B) \left\{ 1 + g_m r_o \frac{r_\pi}{r_\pi + R_B} \right\}$$

$$\text{If } R_B = 0 \quad R_O = r_o + (R_e \parallel r_\pi) \{ 1 + g_m r_o \}$$

$R_O$  is maximum when  $R_e \gg r_\pi$  then:

$$R_O = r_o + r_\pi \{ 1 + g_m r_o \}$$

If  $R_B = 0$  and  $R_e = \infty$ :

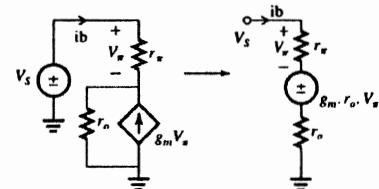

$$V_\pi = ib \cdot r_\pi$$

$$V_S - g_m r_o V_\pi = ib(r_\pi + r_o) \Rightarrow V_S = g_m r_o r_\pi ib + ib(r_\pi + r_o)$$


$$\Rightarrow ib = \frac{V_S}{g_m r_o r_\pi + r_\pi + r_o}$$

and:

$$g_m V_\pi = g_m r_\pi ib = \frac{g_m r_\pi V_S}{g_m r_o r_\pi + r_\pi + r_o}$$

$$\text{and } ir_o = ib + g_m V_\pi \\ = (1 + g_m r_\pi) \cdot \frac{V_S}{g_m r_o r_\pi + r_\pi + r_o}$$


9.40

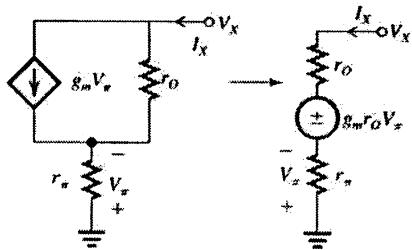

$$\begin{aligned}
 V_x &= -I_x r_\pi \\
 V_x - g_m r_o I_x &= I_x (r_o + r_\pi) \\
 \frac{V_x}{I_x} &= R_o = r_o + r_\pi + g_m r_o r_\pi \\
 &= r_\pi + r_o(1 + g_m r_\pi) \\
 &= r_\pi + r_o(1 + h_{fe}) \\
 &\approx h_{fe} r_o
 \end{aligned}$$

$$\begin{aligned}
 \beta &= \frac{V_f}{I_o} = \frac{R_1 \cdot R_3}{R_1 + R_2 + R_3} \\
 \text{if } A\beta \gg 1 \Rightarrow A_f &\approx \frac{1}{\beta} = \frac{R_1 + R_2 + R_3}{R_1 R_3} \\
 \text{If } A_F &= 100 \text{ mA/V} \quad 0.1 = \frac{200 + R_2}{100 \times 100} \\
 \rightarrow R_2 &= 800 \Omega \quad \beta = 10
 \end{aligned}$$

A-circuit:

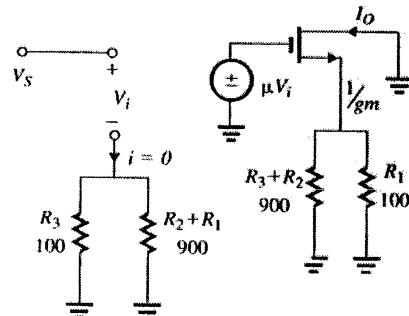

$$\begin{aligned}
 I_o &= \frac{\mu V_s}{1/g_m + R_1 \parallel (R_1 + R_2)} \\
 A &= \frac{I_o}{V_s} = \frac{\mu}{1/g_m + R_1 \parallel (R_1 + R_2)}
 \end{aligned}$$

$$\text{For } g_m = 1 \text{ mA/V} \quad A = \frac{\mu}{1 \text{ K} + 90} = \frac{\mu}{1090}$$

Amount of feed-back:  $1 + A\beta = 1000$   
i.e. 60 dB


$$\text{and } \beta = 10 \Rightarrow A = \frac{999}{10} = 99.9$$

$$\mu = 1090 \times 99.9 \approx 109 \times 10^3 \text{ V/V}$$

$R_o$  is degenerated by  $R_1/(R_2 + R_3)$


$$\begin{aligned}
 R_o &\equiv r_o + g_m r_o [R_1/(R_2 + R_3)] + [R_1/(R_2 + R_3)] \\
 &\approx 50 \text{ k}\Omega + 90 \Omega + 4.5 \text{ k}\Omega = 54.59 \text{ k}\Omega
 \end{aligned}$$
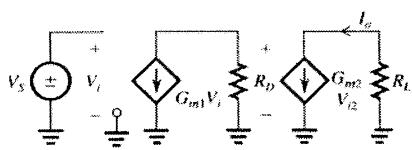
$$R_{out} = R_o(1 + A\beta) = 54.59 \text{ M}\Omega$$



9.42

Feed-back circuit:

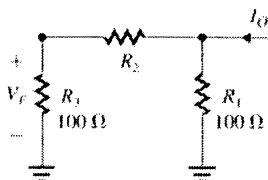

9.43

$$\begin{aligned}
 I_{D1} &= I_{D2} = I_{D3} = I_{D4} = 0.1 \text{ mA} \\
 I_{D5} &= 0.8 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 g_{m1} &= g_{m2} = g_{m3} = g_{m4} = \frac{2 \times 0.1 \text{ m}}{0.2} \\
 &\approx 1 \text{ mA/V}
 \end{aligned}$$

$$g_{m5} = \frac{2 \times 0.8 \text{ m}}{0.2} = 8 \text{ mA/V}$$


$$r_{o2} = \frac{|V_A|}{I_{D2}} = \frac{20}{0.1 \text{ m}} = 200 \text{ k}\Omega$$

$$r_{o5} = \frac{20}{0.8 \text{ m}} = 25 \text{ k}\Omega$$

$$|V_{G3}| = 0.2 + 0.4 = 0.6 \text{ V}$$

9.44

(a)

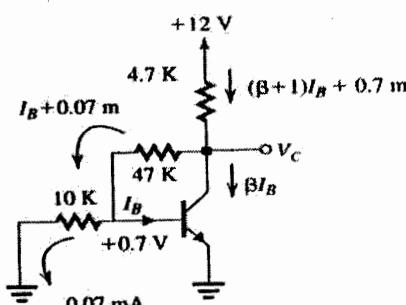

$$V_C = 0.7 + (I_B + 0.07)47 = 3.99 + 47 I_B$$

$$\text{and } \frac{12 - V_C}{4.7} = (\beta + 1)I_B + 0.07$$

Solving both equations results in:  $I_B \approx 0.015 \text{ mA}$

$I_C \approx 1.5 \text{ mA}$  and  $V_C = 4.7 \text{ V}$

$$V_{pi} = I_i(R_s \parallel R_f \parallel r_\pi)$$

$$V_o = -g_m V_{pi} (R_f \parallel R_c)$$

$$\Rightarrow A = \frac{V_o}{I_i} = -g_m (R_f \parallel R_c) (R_s \parallel R_f \parallel r_\pi)$$

$$g_m = \frac{I_C}{V_T} = \frac{1.5 \text{ mA}}{25 \text{ m}} = 60 \text{ mA/V} \text{ and}$$


$$r_\pi = \frac{\beta}{g_m} = \frac{100}{60 \text{ mA}} = 1.67 \text{ k}\Omega$$

Substituting:  $A = -358.7 \text{ k}\Omega$

$$R_i = R_s \parallel R_f \parallel r_\pi = 1.4 \text{ k}\Omega$$

$$R_o = R_c \parallel R_f = 4.27 \text{ k}\Omega$$

(d) To determine  $\beta$ :

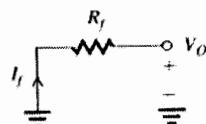


$$\beta = \frac{I_f}{V_o} = \frac{-1}{R_f} = \frac{-1}{47 \text{ k}\Omega}$$

$$A\beta = \frac{358.7}{47} = 7.63 \quad 1 + A\beta = 8.63$$



$$(e) A_f = \frac{V_o}{I_s} = \frac{A}{1 + A\beta} = \frac{-358.7}{8.63} = -41.6 \text{ k}\Omega$$

$$R_{if} = \frac{R_i}{1 + A\beta} = \frac{1.4 \text{ K}}{8.63} = 162.2 \Omega$$

(b)

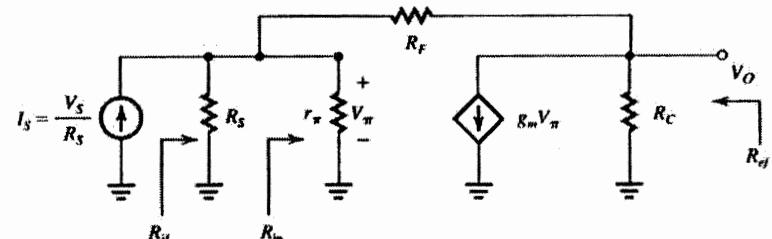

(c) A-circuit:

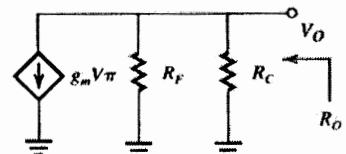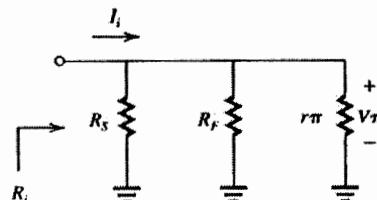

To find A:

$$R_{oi} = \frac{R_o}{1 + A\beta} = \frac{4.27 \text{ K}}{8.63} = 495 \Omega$$

$$R_{in} = \frac{1}{\frac{1}{R_{if}} - \frac{1}{R_s}} = \frac{1}{\frac{1}{162.2} - \frac{1}{10 \text{ K}}} = 164.87 \Omega$$

$$R_{out} = \frac{1}{\frac{1}{R_{oi}} - \frac{1}{R_L}} = \frac{1}{\frac{1}{495} - \frac{1}{\infty}} = 495 \Omega$$

$$V_s = I_s \cdot R_s$$

$$\frac{V_o}{V_s} = \frac{V_o}{I_s \cdot R_s} = \frac{-41.6 \text{ K}}{10 \text{ K}} = -4.16 \text{ V/V}$$

if  $A\beta \gg 1$

$$\Rightarrow A_f \approx -47 \text{ k}\Omega$$

$$\rightarrow \frac{V_o}{V_s} = \frac{-47}{10} = -4.7 \text{ V/V}$$

9.45

(a) if  $A\beta \gg 1 \Rightarrow A_f \approx \frac{1}{\beta}$  with  $\beta = \frac{-1}{R_f}$

$$A_f = \frac{V_o}{I_s} = -R_f$$

$$\text{Since } V_s = I_s \cdot R_s \Rightarrow \frac{V_o}{V_s} = \frac{A_f}{R_s} = \frac{-R_f}{R_s}$$

$$\text{For } \frac{V_o}{V_s} \approx -10 \frac{\text{V}}{\text{V}} = \frac{-R_f}{1 \text{ k}\Omega} \Rightarrow R_f = 10 \text{ k}\Omega$$

(b)  $\mu = 10^3 \text{ V/V}$ ,  $R_{id} = 100 \text{ k}\Omega$

$$r_o = 1 \text{ k}\Omega$$

$$R_t = \infty, R_f = 10 \text{ K}, R_s = 1 \text{ K}$$

$$R_i = R_{id} \parallel R_F \parallel R_S = 100 \parallel 10 \parallel 1 = 901 \Omega$$

$$A = \frac{V_o}{I_i} = -\mu R_i \frac{(R_F \parallel R_L)}{r_o + (R_F \parallel R_L)}$$

$$= \frac{-10^3 \times 901(10 \text{ K})}{1 \text{ K} + 10 \text{ K}} = -819 \text{ k}\Omega$$

$$A\beta = \frac{819}{10} = 81.9$$

$$1 + A\beta = 82.9$$

$$A_f = \frac{A}{1 + A\beta} = \frac{-819 \times 10^3}{82.9} = -9.88 \text{ k}\Omega$$

$$\frac{V_o}{V_s} = \frac{-9.88}{1} = -9.88 \text{ V/V}$$

To find  $R_{in}$ : Since  $R_{id}$  is large

$$(\text{Eq 10.58}) R_{in} \approx \frac{R_F}{\mu'}$$

$$\mu' = \frac{\mu(R_F \parallel R_L)}{r_o + (R_F \parallel R_L)} = 909$$

$$R_{in} = \frac{10 \text{ K}}{909} = 11 \Omega$$

$$\text{Since: } R_i \gg \frac{r_o}{1 + \mu \frac{R_i}{R_F}}$$

$$R_{out} \approx \frac{R_F \cdot r_o}{R_i + \mu} = \frac{10}{0.901} \times \frac{1}{1} = 11.1 \Omega$$

$$r_o = 1000 \Omega \quad \mu = 1000$$

$$(e) f_H = 1 \text{ kHz} \Rightarrow f_{HF} = 1 \text{ K}(1 + A\beta)$$

$$= 1 \text{ K} \times 82.9 = 82.9 \text{ kHz}$$

9.46

$$(a) V_{ov} = V_{gs} - V_i \Rightarrow V_{gs1,2} V_{ov} + V_i \\ = 0.2 + 0.5 = 0.7 \text{ V}$$

$$V_{g1} = V_{gs1} = 0.7 \text{ V}$$

$$V_o = V_{gs1} = 0.7 \text{ V}$$

$$V_{g2} = V_o + V_{gs2} = 0.7 + 0.7 = 1.4 \text{ V}$$

$$(b) I_{D1} = I_{D2} = 0.5 \text{ mA}$$

$$g_m = \frac{2I_D}{V_{ov}} \rightarrow g_{m1,2} = \frac{2 \times 0.5 \text{ mA}}{0.2} = 5 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} \rightarrow r_{o1,2} = \frac{10}{0.5 \text{ mA}} = 20 \text{ k}\Omega$$

(c) A-circuit:


$$V_1 = I_S R_F \quad V_2 = -g_{m1} r_{o1} (I_S R_F)$$

$$V_o = \frac{V_2 \cdot (R_F \parallel r_{o2})}{1/g_{m2} + (R_F \parallel r_{o2})}$$

$$= \frac{-g_{m1} \cdot r_{o1} (I_S R_F) (R_F \parallel r_{o2})}{1/g_{m2} + (R_F \parallel r_{o2})}$$

$$A = \frac{V_o}{I_S} = \frac{-g_{m1} \cdot r_{o1} \cdot R_F (R_F \parallel r_{o2})}{1/g_{m2} + (R_F \parallel r_{o2})}$$

(d)

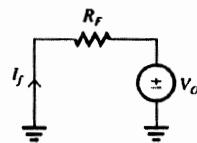

$$\beta = \frac{I_f}{V_o} = \frac{-1}{R_f}$$

$$A\beta = \frac{1 \cdot r_{o1} \cdot (R_F \parallel r_{o2})}{1/g_{m2} + (R_F \parallel r_{o2})}$$

$$1 + A\beta = \frac{1/g_{m2} + (1 + g_{m1} r_{o1}) (R_F \parallel r_{o2})}{1/g_{m2} + (R_F \parallel r_{o2})}$$

$$(e) A_f = \frac{A}{1 + A\beta}$$



$$= \frac{-g_{m1} \cdot r_{o1} \cdot R_F (R_F \parallel r_{o2})}{1/g_{m2} + (1 + g_{m1} \cdot r_{o1}) (R_F \parallel r_{o2})}$$

(f)  $R_i = R_f$

$$R_o = R_F \parallel r_{o2} \parallel 1/g_{m2}$$

$$R_{if} = \frac{R_i}{1 + A\beta} \Rightarrow \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{A\beta}{R_i} = \frac{1}{R_i} + \frac{A\beta}{R_f}$$

(c)

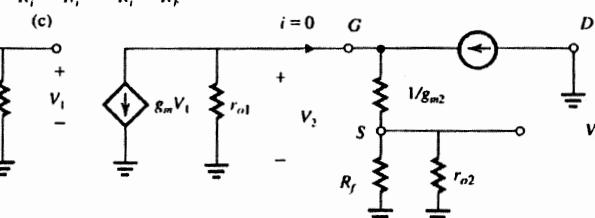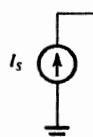


9.47

$$A_f = \frac{V_o}{I_s}$$

Across  $R_f$ :  $I_f = \frac{V_{gs} - V_o}{R_f} \cdot g_m V_{gs} - \frac{V_o}{R_f}$  (1)

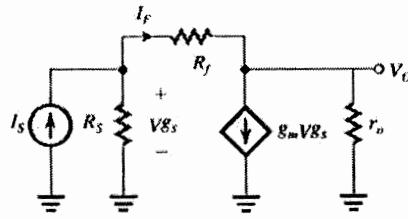At the output:  $I_f = g_m V_{gs} + \frac{V_o}{r_o}$  (2)



Combining (1) and (2):

$$\frac{V_{gs}}{R_f} - \frac{V_o}{R_f} = g_m V_{gs} + \frac{V_o}{r_o}$$

$$\Rightarrow V_{gs} \left( \frac{1}{R_f} - g_m \right) = V_o \left( \frac{1}{r_o} + \frac{1}{R_f} \right)$$

$$= \frac{V_o}{(r_o \parallel R_f)} \quad (3)$$

At the input:  $I_f = I_s - \frac{V_{gs}}{R_s} \Rightarrow$  Combining with (1)

$$\frac{V_{gs}}{R_f} - \frac{V_o}{R_f} = I_s - \frac{V_{gs}}{R_s} \Rightarrow V_{gs} \left( \frac{1}{R_s} + \frac{1}{R_f} \right)$$

$$= I_s + \frac{V_{gs}}{R_s} \Rightarrow \frac{V_{gs}}{(R_f \parallel R_s)} = I_s + \frac{V_o}{R_f}$$

$$\Rightarrow V_{gs} = I_s (R_f \parallel R_s) + V_o \frac{(R_f \parallel R_s)}{R_f} \quad (4)$$

To simplify let's call:  $K_1 = \frac{1}{R_f} - g_m$

$K_2 = R_f \parallel R_s$  and  $K_3 = r_o \parallel R_f$

The Eq (3) and (4) become:

$$V_{gs} K_1 = \frac{V_o}{K_3} \quad V_{gs} = I_s K_2 + V_o \frac{K_2}{R_f}$$

Combining:  $I_s K_2 \cdot K_1 + V_o \frac{K_2 \cdot K_1}{R_f} = \frac{V_o}{K_3}$

$$I_s K_1 \cdot K_2 = V_o \left( \frac{1}{K_3} - \frac{K_1 \cdot K_2}{R_f} \right)$$

$$\rightarrow \frac{V_o}{I_s} = \frac{K_1 \cdot K_2}{\frac{1}{K_3} - \frac{K_1 \cdot K_2}{R_f}}$$

$$\frac{V_o}{I_s} = \frac{K_1 \cdot K_2 \cdot K_3}{1 - \frac{K_1 \cdot K_2 \cdot K_3}{R_f}} \text{ where we recognize an}$$

$$\text{Eq of the form: } \frac{A}{1 + A\beta} \text{ with } \beta = \frac{-1}{R_f}$$

Substituting for  $K_1$ ,  $K_2$ ,  $K_3$  and re-arranging the signs:

$$\frac{V_o}{I_s} = \frac{-\left(g_m - \frac{1}{R_f}\right)(R_f \parallel R_s)(r_o \parallel R_f)}{1 + \left(g_m - \frac{1}{R_f}\right)(R_f \parallel R_s)\frac{(r_o \parallel R_f)}{R_f}}$$

For the feed-back analysis method to be accurate

$$g_m \gg \frac{1}{R_f}$$

9.48

A-circuit:

$$V_i = g_{m1} V_{gs} \cdot R_{D1} \quad V_{gs} = -I_s (R_f \parallel 1/g_{m1})$$

$$\Rightarrow V_i = g_{m1} \cdot R_{D1} (R_f \parallel 1/g_{m1})$$

$$V_o = -g_{m2} V_i (R_{D2} \parallel R_f)$$

$$\Rightarrow \frac{V_o}{I_s} = -g_{m2} (R_{D2} \parallel R_f) \times g_{m1} R_{D1} (R_f \parallel 1/g_{m1})$$


$$= g_{m1} \cdot g_{m2} \cdot R_{D1} \cdot (R_{D2} \parallel R_f) (R_f \parallel 1/g_{m1})$$

$$\beta = \frac{-1}{R_f} \Rightarrow A_f = \frac{A}{1 + A\beta}$$

$$= \frac{-g_{m1} \cdot g_{m2} \cdot R_{D1} (R_{D2} \parallel R_f) (R_f \parallel 1/g_{m1})}{1 + \frac{g_{m1} g_{m2} R_{D1}}{R_f} (R_{D2} \parallel R_f) (R_f \parallel 1/g_{m1})}$$

$$R_i = \left( R_f \parallel \frac{1}{g_{m1}} \right) \text{ and } R_{il} = \frac{R_i}{1 + A\beta}$$
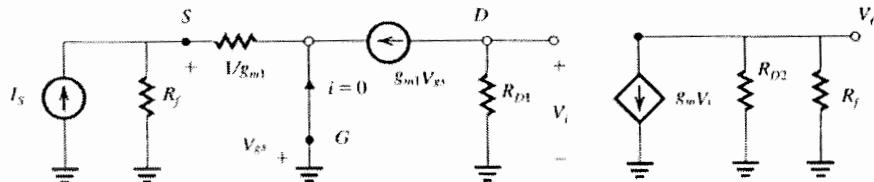
$$R_o = (R_{D2} \parallel R_f) \text{ and } R_{ol} = R_o / (1 + A\beta)$$



This figure is for 9.48

### 9.49

(a) Due to the feed-back we can assume that  $i_f$  is very small.

$$\Rightarrow V_O \approx V_{B1} = 0.7 \text{ V}$$

$$V_{B2} = V_O + 0.7 = 1.4 \text{ V}$$

$$I_{RE} = \frac{0.7 + 5}{10 \text{ K}} = 0.57 \text{ mA} \approx I_{E2}$$

$$I_{RC} = \frac{5 - 1.4}{10 \text{ K}} = 0.36 \text{ mA}$$

$$I_{C1} = I_{RC} - \frac{I_{C1}}{\beta} = 0.36 \text{ mA} - \frac{0.56 \text{ mA}}{100} \\ = 0.35 \text{ mA}$$

(b) A-circuit: neglecting  $r_{e1}$  and  $r_{e2}$

$$g_{m1} = \frac{0.35 \text{ mA}}{25 \text{ m}} = 14 \frac{\text{mA}}{\text{V}}$$

$$r_{\pi1} = \frac{100}{14 \text{ mA}} = 7.14 \text{ k}\Omega$$

$$r_{\pi2} = \frac{25 \text{ m}}{0.58 \text{ mA} \times 0.99} = 43.5 \text{ }\Omega$$

$$V_{\pi1} = I_S (r_{\pi1} \parallel R_f) = I_S (7.14 \text{ K} \parallel 10 \text{ K}) \\ = I_S \times 4.16 \text{ K}$$

$$V_O = \frac{-g_{m1} \cdot V_{\pi1} \cdot R_C \cdot R_F \parallel R_E (\beta + 1)}{R_C + (\beta + 1)(r_{\pi2} + R_F \parallel R_E)} \\ = -\frac{14 \text{ mA} \times 10 \text{ K} \times 5 \text{ K} \times (101)}{10 \text{ K} + 101(43.5 + 5 \text{ K})} V_{\pi1}$$

$$= -136 \text{ V}_{\pi1}$$

$$V_O = (-136 \times 4.16 \text{ K}) I_S$$

$$\Rightarrow A = \frac{V_O}{I_S} \approx -566 \text{ k}\Omega$$

$$R_I = R_f \parallel r_{\pi} = 4.16 \text{ k}\Omega$$

$$\left( \frac{R_C + r_{\pi2}}{\beta + 1} \right) \parallel R_E \parallel R_f$$

$$= \left[ \frac{10 \text{ K} + 43.5}{101} \right] \parallel 5 \text{ K} = 97.5 \text{ }\Omega$$

$$(C) \quad \beta = -\frac{1}{R_f} = \frac{-1}{10 \text{ K}} = -100 \frac{\mu\text{A}}{\text{V}}$$

$$A\beta = 100 \mu \times 566 \text{ k}\Omega = 56.6$$

$$1 + A\beta = 57.6$$


$$(d) \quad A_f = \frac{A}{1 + A\beta} = 9.8 \text{ k}\Omega$$

$$R_{if} = \frac{R_I}{1 + A\beta} = \frac{4.16 \text{ K}}{58.4} = 73.14 \text{ }\Omega$$

$$R_{of} = \frac{R_O}{1 + A\beta} = \frac{140.5}{58.4} = 2.4 \text{ }\Omega$$

### 9.50

A-circuit

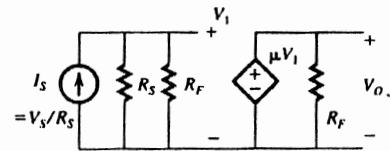

$$\beta = -1/R_f$$



$$V_O = -\mu V_1$$

$$V_1 = I_S (R_S \parallel R_F)$$

$$\therefore V_O = -\mu I_S (R_S \parallel R_F)$$


$$A = \frac{V_O}{I_S} = -\mu \frac{R_S R_F}{(R_S \parallel R_F)}$$
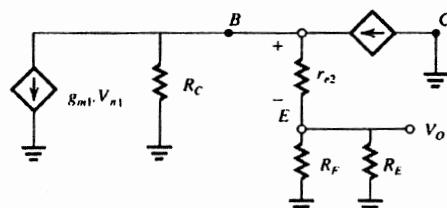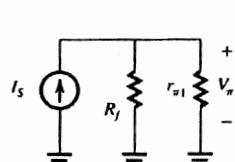
$$A_F = \frac{A}{1 + A\beta} = \frac{-\mu(R_S \parallel R_F)}{1 + \mu(R_S \parallel R_F)R_F} \\ = \frac{-\mu(R_S \parallel R_F)}{1 + \mu \left( \frac{R_S \parallel R_F}{R_F} \right)}$$



This figure is for 9.49

This figure is for 9.50 (b)

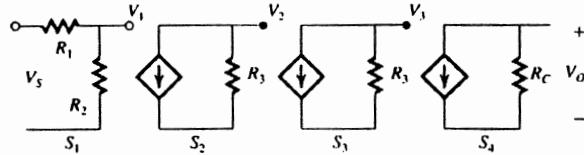

$$\frac{-\mu R_s R_f}{R_s + R_f + \mu R_s} = \frac{-R_f}{1 + \frac{R_f + R_s}{\mu R_s}} \approx -R_f \text{ if } \mu \text{ is large}$$

large

$$\frac{V_o}{V_s} = \frac{V_o I_s}{I_s V_s} = -R_f \frac{1}{R_s} = \frac{-R_f}{R_s}$$

(b) For circuit of Fig p8.46 (b)

$$I_B = \frac{V_{CC} \frac{10}{10+15} - V_{BE}}{[(15 \parallel 10) + (4.7 \times 10)] \times 10^3} = \frac{15(10/25) - 0.7}{(6 + 474.4) \times 10^3} = \frac{5.3 \text{ V}}{480.7 \text{ K}} \approx 0.011 \text{ mA}$$

$$I_C = 100 I_B = 1.1 \text{ mA}$$

$$r_e = V_T / I = 22.6 \Omega$$

$$r_\pi = (\beta + 1)r_e = 2.286 \text{ K}$$

$$g_m = \beta / r_\pi = 100 / 2.286 \text{ K} \rightarrow 43.7 \text{ mA/V}$$

$$R_{in} = (15 \parallel 10 \parallel 2.286) \text{ K} = 1.5 \text{ K}$$

$$R_C \parallel R_B \parallel r_\pi = (7.5 \parallel 6 \parallel 2.286) = 1.35 \text{ K}$$

For S<sub>1</sub>:  $R_1 = R_S, R_2 = R_{in} \parallel R_f$

$$\therefore V_1 = 1.5 / 11.5 V_s = 0.13 V_s$$

For S<sub>2</sub>:  $R_3 = R_C \parallel R_B \parallel r_\pi$

$$\therefore \frac{V_2}{V_1} = -g_m R_3 = -43.7 \times 1.35 = -59 \text{ V/V}$$

For S<sub>3</sub>: Same as S<sub>2</sub>  $\therefore \frac{V_3}{V_2} = -59 \text{ V/V}$

For S<sub>4</sub>:

$$\frac{V_o}{V_3} = -g_m R_C = -43.7 \times 7.5 = -327.75 \text{ V/V}$$

$$\frac{V_o}{V_s} = -0.13 \times 59 \times 59 \times 327.75$$

$$\rightarrow \frac{V_o}{V_s} = -1.488 \times 10^5$$

Because we have ignored  $r_o$  etc let us estimate

$$V_o / V_s = -1 \times 10^5 \text{ which is quite large.}$$

Then  $A_f = \frac{A}{1 + A\beta} \approx 100 \text{ needed}$

$$= \frac{10^5}{1 + 10^5 \beta} = \frac{1}{\beta} = 100$$

Select  $R_f$  so that

$$R_f / R_S = 100 \rightarrow R_f = 100 \times 10 \text{ K} = 1 \text{ M}\Omega$$

We can ignore leading effect of  $R_f$  in A-circuit.  $R_L$  will cause loading of  $R_C$

$$V_L = \left( \frac{R_L}{(R_C + R_L)} \right) V_o$$

$$V_L = (1/8.5) = 0.11 V_o$$

Now  $A_o \approx 1.65 \times 10^4$

$$A_f = \frac{10^4}{1 + 10^4 / 100} = 99.4$$

## 9.51

(a) To lower  $R_{in}$  and raise  $R_{out}$  SHUNT - SERIES

(b) To raise  $R_{in}$  and  $R_{out}$  SERIES - SERIES

(c) To lower  $R_{in}$  and  $R_{out}$  SHUNT - SHUNT

## 9.52

$A_f = -100 \text{ A/A}$  and  $1 + A\beta$  is 40 dB

$$\Rightarrow 1 + A\beta = 100$$

$$A\beta = 99$$

and since  $A_f = A/(1 + A\beta) \Rightarrow$

$$A = -100 \times 100 = -10.000 \text{ A/A}$$

$$\text{and } \beta = -0.0099$$

$$R_i = R_S \parallel R_{in} \parallel (R_1 + R_2) \text{ and}$$

$$R_S = R_{in} = \infty \Rightarrow R_i = R_1 + R_2$$

$$R_{in} \cong \frac{R_2}{\mu} \Rightarrow 1 \text{ K} = \frac{R_2}{\mu}$$

If we assume that  $\frac{1}{g_m} \ll (R_1 \parallel R_2 \parallel r_{o2})$  then

we can use eq (10.73)

$$A\beta = \frac{\mu R_1}{R_2} \rightarrow A\beta = \frac{(R_1 + R_2)}{(R_2 / \mu)}$$

$$\rightarrow 99 = \frac{R_1 + R_2}{1 \text{ K}} \quad (1)$$

$$\beta = \frac{-R_1}{R_1 + R_2}$$

$\Rightarrow$  For  $\beta = -0.0099$

$$R_2 = (100.01)R_1 \quad (2)$$

Combining (1) and (2):  $R_1 + R_2 = 99 \text{ K}$

$$R_2 = (100.01)R_1$$

$$\Rightarrow R_1 = 980.1 \Omega$$

$$R_2 = 98.02 \text{ k}\Omega$$

$$99 = \frac{\mu \cdot 99 \text{ K}}{98.02 \text{ K}} \rightarrow \mu = 98.02 \text{ V/V}$$

Given  $g_m = 5 \text{ mA/V}$  and  $r_o = 20 \text{ K}$  we

observe that the assumption  $\frac{1}{g_m} \ll$

$(R_1 \parallel R_2 \parallel r_{o2})$  is not valid

$$\left( \frac{1}{5 \text{ m}} = 200 \Omega \right)$$

$$\approx ((980.1 \parallel 98.02 \text{ K} \parallel 20 \text{ K}) = 925.5)$$

, cannot be used.

Instead we use:

$$-10.000 = \frac{-\mu \cdot 99 \text{ K}}{200 + 925.5} \left( \frac{20 \text{ K}}{20 \text{ K} + 970.4} \right)$$

$$\Rightarrow \mu = 119.2$$

To calculate  $R_{out}$  we cannot use .


$$R_o = r_{o2} + g_m r_{o2} (R_1 \parallel R_2) + (R_1 \parallel R_2) = 119 \text{ k}\Omega$$

$$R_{out} = R_o(1 + A\beta) = 11.950$$

Since:  $R_{out} = R_{out} - R_L$  and  $R_L = 0$

$$\Rightarrow R_{out} = R_{out} = 9.7 \text{ M}\Omega$$

This figure is for 9.53 (c)

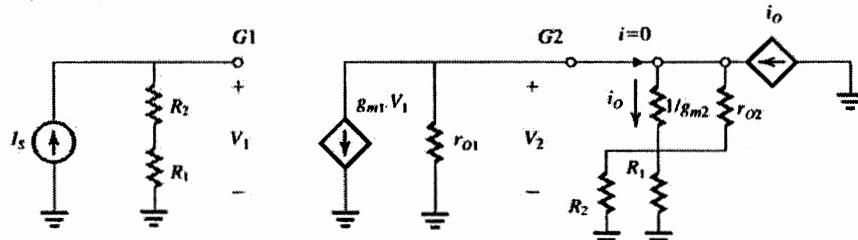

9.53

$$(a) V_{GS} = V_{OV} + V_1$$

$$= 0.2 + 0.5 = 0.7 \text{ V}$$

$$\Rightarrow V_{GSI} = V_{GI} = 0.7 \text{ V}$$

Since  $I_{G1} = 0 \rightarrow V_{S2} = 0.7$

$$I_{D2} = \frac{V_{S2}}{R_2} = \frac{0.7}{3.5 \text{ K}} = 0.2 \text{ mA}$$

$$(b) g_m = \frac{2I_D}{V_{OV}} = \frac{0.4 \text{ m}}{0.2} = 2 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{10}{0.2 \text{ m}} = 50 \text{ k}\Omega$$

(c) The A-circuit:




$$V_1 = I_S (R_1 + R_2)$$

$$V_2 = -g_m r_{o1} V_1 = -g_m r_{o1} (R_1 + R_2) I_S$$

$$\begin{aligned} i_o &= \frac{V_2}{1/g_m + R_2 \parallel R_1 \parallel r_{o2}} \\ &= \frac{-g_m r_{o1} (R_1 + R_2) I_S}{1/g_m + R_2 \parallel R_1 \parallel r_{o2}} \\ \Rightarrow A &= \frac{i_o}{I_S} = \frac{-g_m \cdot r_{o1} \cdot (R_1 + R_2)}{1/g_m + (R_2 \parallel R_1 \parallel r_{o2})} \\ &= \frac{-2 \times 50(3.5 + 14) \text{ K}}{500 + (3.5 \parallel 14 \parallel 50) \text{ K}} = -555.3 \text{ A} \end{aligned}$$

$$R_i = R_2 + R_1 = 3.5 + 14 = 17.5 \text{ k}\Omega$$

To get  $R_O$ :

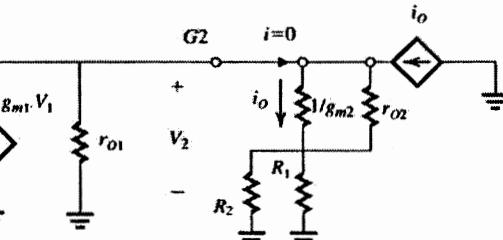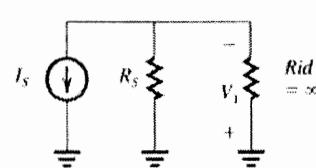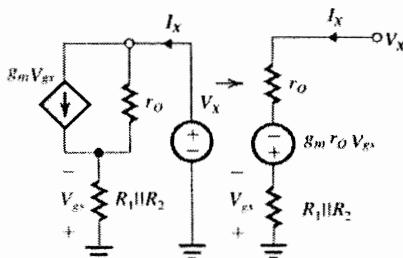

$$V_{GS} = -I_x (R_1 \parallel R_2)$$

$$V_X + g_m r_o V_{GS} = I_x (r_o + R_1 \parallel R_2)$$

$$R_o = \frac{V_X}{I_x} = r_o + R_1 \parallel R_2 + g_m r_o (R_1 \parallel R_2)$$

$$R_o = 50 \text{ K} + (3.5 \parallel 14) \text{ K} + 2 \times 50(3.5 \parallel 14) \text{ K}$$

$$R_o = 332.8 \text{ k}\Omega$$

$$(d) \beta = \frac{-R_1}{R_1 + R_2} = \frac{-3.5}{17.5} = -0.2$$

$$(e) A\beta = 555.3 \times 0.2 = 111.06$$

$$A_f = \frac{A}{1 + A\beta} = \frac{-555.3}{112.06} = -5 \text{ A/A}$$

$$(f) R_{in} = R_{if} \parallel R_s \text{ since } R_s = \infty \Rightarrow R_{in} = R_{if}$$

$$R_{in} = \frac{R_i}{1 + A\beta} = \frac{17.5 \text{ K}}{112.06} = 156.2 \text{ }\Omega$$

$$R_{out} = R_{of} - R_L \text{ but } R_L = 0 \Rightarrow R_{out} = R_{of}$$

$$R_{out} = R_o (1 + A\beta) = 332.8 \text{ K} \times 112.06 = 37.3 \text{ M}\Omega.$$


9.54

(a) if  $\mu$  is large, the loop gain is large and the current at the negative input is

$$\sim 0 \Rightarrow V_{in} \sim -R_s \cdot I_S$$


$$\text{Since } I_S \equiv I_O \Rightarrow \frac{I_O}{I_S} \approx 1 \text{ A/A}$$

(b) A-circuit:

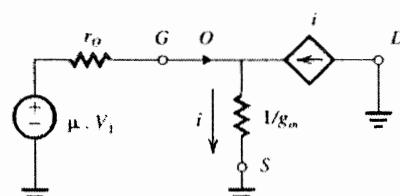

$$\begin{aligned}
 V_i &= I_s \cdot R_s \\
 \Rightarrow I_o &= i = \mu \cdot R_s g_m \cdot I_s \\
 i &= \frac{(\mu \cdot V_i)}{1/g_m} \\
 \Rightarrow A &= \frac{I_o}{I_s} = \mu \cdot R_s \cdot g_m \\
 R_i &= R_s \quad R_o = r_{o2} \\
 (\text{c}) \beta &= 1 \\
 (\text{d}) A\beta &= \mu \cdot R_s \cdot g_m \\
 A_f &= \frac{A}{1 + A\beta} = \frac{\mu \cdot R_s \cdot g_m}{1 + \mu \cdot R_s \cdot g_m} \\
 \text{If } r \gg 1 &\Rightarrow A_f \approx 1 \\
 (\text{e}) R_{if} &= \frac{R_i}{1 + A\beta} = \frac{R_s}{1 + \mu R_s \cdot g_m} \Rightarrow \frac{1}{R_{if}} \\
 &= \frac{1}{R_s} + \mu \cdot g_m \\
 R_{if} &= R_s \parallel 1/\mu \cdot g_m \\
 \text{since } R_{if} &= R_s \parallel R_{in} \\
 \Rightarrow R_{in} &= \frac{1}{\mu \cdot g_m} \text{ if } r \gg 1 \rightarrow R_{in} = 0 \\
 R_{of} &= R_o(1 + A\beta) = r_{o2}(1 + \mu R_s g_m) \\
 R_{of} &= R_{out} + R_L \text{ and} \\
 R_L &= 0 \Rightarrow R_{out} = \frac{1}{g_m} + \mu R_s \\
 \text{if } \mu >> 1 &\Rightarrow R_{out} = \infty
 \end{aligned}$$


For Q1:

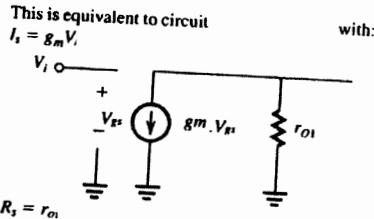


$$\begin{aligned}
 R_s &= r_{o1} \\
 I_o &= V_o g_m \frac{\mu g_m r_{o1}}{1 + \mu g_m r_{o1}} \\
 V_{R2} &= V_{R1} \text{ if } \mu g_m r_{o1} > 1 \\
 R_{out} &= r_{o2}(1 + \beta A) \\
 &= r_{o2}(1 + \mu r_{o1} g_m) \\
 &\approx \mu(r_{o2} g_m r_0)
 \end{aligned}$$

9.55

(a) When  $V_x$  is positive:

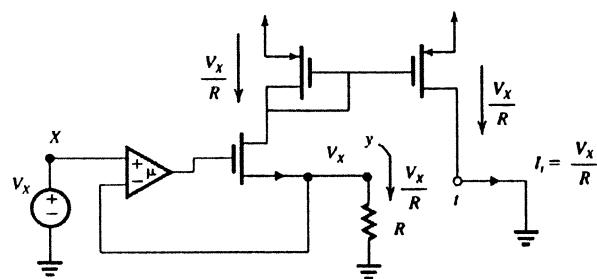


When  $V_x$  is negative:

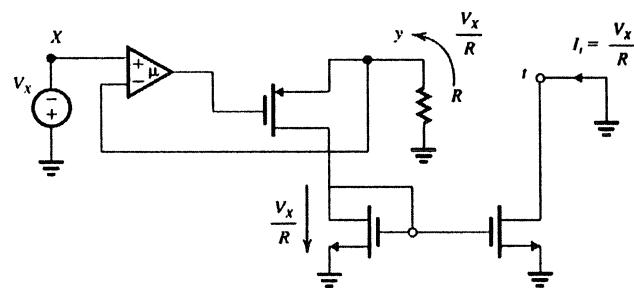


(b) When  $I_y$  is positive:

$$R_{in} = \frac{1}{\mu(g_{mp} + g_{mn})} \sim 0 \text{ (if } \mu \gg 1)$$

When  $I_y$  is negative:

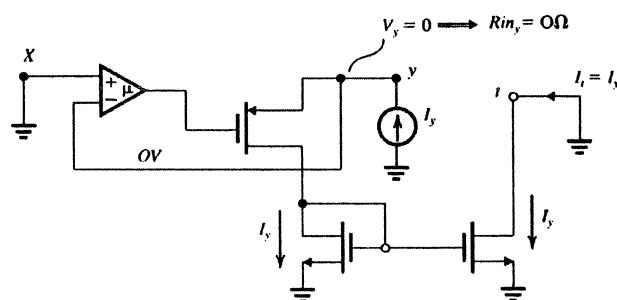

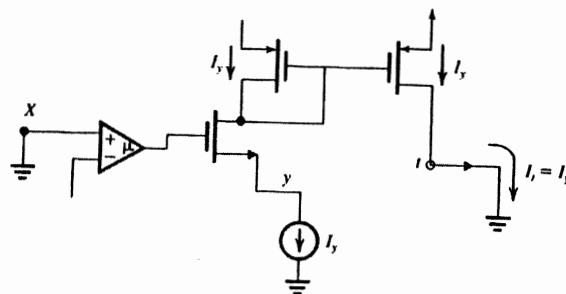

(c) When  $R_{\text{out}}$  is  $r_{O2} \parallel r_{O4}$

9.56

Neglect  $I_{B2}; I_{B1} \approx \frac{200}{100} = 2 \mu\text{A}$   
 $V_{BE} = 0.7\text{V} \quad \therefore V_{B1} = +0.7\text{V}$   
 But no d.c. component in  $V_S$   
 $\therefore I_{RS} (\text{into } V_S) = 0.7/10\text{k} = 0.07 \mu\text{A}$   
 Thus  $I_F = I_{RS} + I_{B1} = 0.07 + 0.002 = 0.072 \mu\text{A}$

$$V_{E2} = 0.7 + 10 \times 0.072 = 0.7 + 0.72 = 1.42\text{V}$$

$$I_{C2} = 1.42/140 + 0.072 = 10.2 \mu\text{A}$$

$$I_{B2} = I_{E2}/(\beta+1) = 0.1 \mu\text{A} \approx \frac{1}{2} 200 \mu\text{A}$$

Heretofore:

$$I_{B1} = \frac{200 \mu\text{A} - 100 \mu\text{A}}{100} = 0.001 \mu\text{A}$$

$$V_{E1} = 0.7 + 10 \times 0.073 = 1.41\text{V}$$

$$I_{E2} = 1.41/140 + 0.071 = 10.1 \mu\text{A}$$

$$I_{B2} = 10.1/101 = 100 \mu\text{A} \quad \therefore I_{C2} = 10 \mu\text{A}$$


$$V_{B2} = V_{E2} + V_{BE} = 1.41 + 0.7 = 2.11\text{V}$$

$$V_o = 10 - 10 \times 500 \Omega = +5\text{V}$$

$$r_{O1} = V_T = \frac{25\text{mV}}{I_E} = 250 \Omega, r_{O2} = 25 \Omega$$

$$\beta = \frac{R_E}{R_F + R_E} = \frac{140}{10\text{k} + 140} \approx 0.0138$$

A-circuit

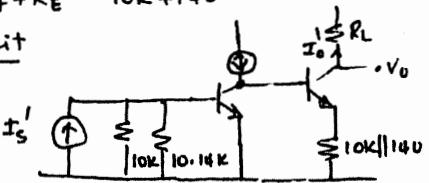

$$V_{B1} = 10.14 \text{k} \parallel 10\text{k} \parallel \beta(250) I_s' \\ = 4.2 \times 10^3 \text{ I}'_s$$

$$\Rightarrow \frac{I_o'}{I_s'} = \frac{4.2 \times 10^3 (\beta+1)(r_{e2} + 10\text{k} \parallel 140)}{250} \\ \times \frac{1}{(r_{e2} + 10\text{k} \parallel 140)}$$

$$= 1.69 \times 10^3 \text{ A/A}$$

$$A_F \equiv \frac{I_o}{I_s} = \frac{A}{1+\beta A} = \frac{1.69 \times 10^3}{1 + 1.69 \times 10^3 \times (0.0138)} \\ = 69.6$$

$$\Rightarrow \frac{V_o}{V_S} = \frac{I_o R_L}{I_s R_S} = \frac{500}{10^4} \cdot 69.6 = 3.5 \text{ V/V}$$


$$R_i = 10\text{k} \parallel 10.14\text{k} \parallel 25\text{k} = 4.2 \text{ k}\Omega$$

$$R_{if} = R_i / (1 + \beta A) = \frac{4.2}{1 + 23.3} = 172.8 \Omega$$


$$\Rightarrow R_{in} = R_{if} \parallel R_s \Rightarrow R_{in} = 175.8 \Omega$$

9.57

A-Circuit

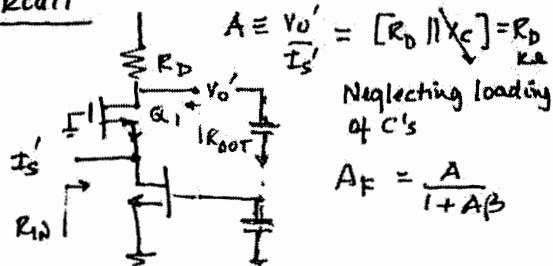

B-Circuit

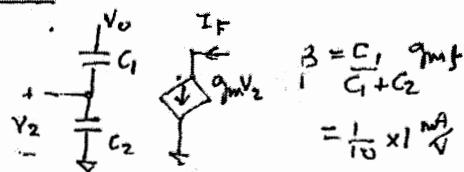

Here,  $g_{m1} = 5 \text{ mA/V}$ ,  $g_{mf} = 1 \text{ mA/V}$   
 $R_D = 10 \text{ k}\Omega$

Thus  $A = 10 \text{ k}\Omega$

$$A_F = \frac{10 \text{ k}\Omega}{(1 + 10 \text{ k}\Omega / 10 \text{ k}\Omega)} = 5 \text{ k}\Omega$$

$$R_{IN} = (R_D \parallel r_o) \rightarrow R_D$$

$$R_{IF} = R_D / (1 + A_B) \text{ shunt} = \frac{R_D}{2} = 5 \text{ k}\Omega$$

$$R_{OUT} = R_D / (1 + A_B) = \frac{R_D}{2} = 5 \text{ k}\Omega$$

9.58

$$(a) V_{B1} \approx 12 - \frac{15}{100 + 15} = 1.57 \text{ V}$$

$$V_{E1} \approx 1.57 - 0.7 = 0.87 \text{ V}$$

$$I_{E1} = 0.87 / 0.7 = 1 \text{ mA} \rightarrow g_{m1}$$

$$= \frac{\alpha I_{E1}}{V_T} = \frac{0.99 \times 1}{25} \approx 40 \text{ mA/V}$$

$$V_{C1} \approx 12 - 10 \times 1 = 2 \text{ V}$$

$$V_{E2} \approx 2 - 0.7 = 1.3 \text{ V}$$

$$I_{E2} \approx 1.3 / 3.4 \approx 0.4 \text{ mA} \rightarrow g_{m2}$$

$$= \frac{0.99 \times 0.4}{25} \approx 16 \text{ mA/V}$$


$$V_{C2} \approx 12 - 0.4 \times 8 = 8.8 \text{ V}$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{40 \text{ mA}} = 2.5 \text{ k}\Omega$$

$$r_{\pi 2} = \frac{100}{16 \text{ mA}} = 6.25 \text{ k}\Omega$$

$$r_{e2} = \frac{V_T}{I_{E2}} = \frac{25}{0.4} = 62.5 \text{ }\Omega$$

(b)

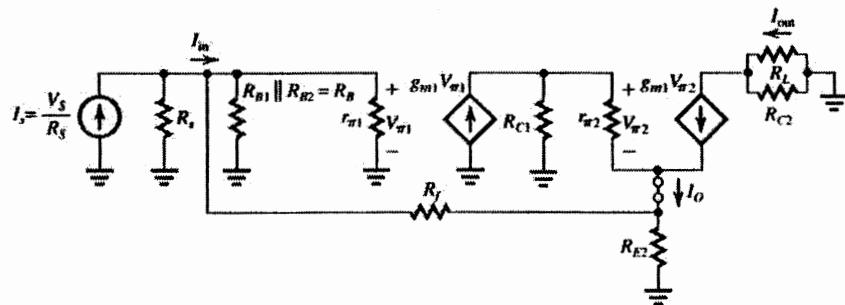

To obtain A:

$$R_B = R_{B1} \parallel R_{B2}$$

$$V_{\pi1} = I_s [R_S \parallel (R_{E2} + R_f) \parallel R_B \parallel r_{\pi1}] \\ = 1.535 \text{ k} \times I_s$$

$$V_{\pi2} = -g_{m1} V_{\pi1}$$


$$\{R_{C1} \parallel [r_{\pi2} + (\beta + 1)(R_{E2} \parallel R_f)]\} \\ = I_O \approx \frac{V_{\pi2}}{r_{\pi2} + (R_{E2} \parallel R_f)}$$

Combining these equations we obtain:

$$A = \frac{I_O}{I_s} = -201.45 \text{ A/A}$$

$$R_i = R_S \parallel (R_{E2} + R_f) \parallel R_B \parallel r_{\pi1} = 1.535 \text{ k}\Omega$$

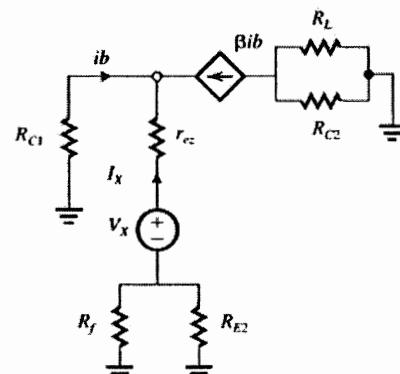$R_O$  is obtained by looking into nodes Y and Y', with  $I_i$  set to zero




$$R_O = \frac{V_x}{I_o}$$

$$I_x = -(\beta + 1)ib$$


$$-R_{C1} \times ib = (\beta + 1)ib[r_{\pi2} + R_f \parallel R_{E2}] + V_x$$

Replacing  $-ib$  by  $I_o/(\beta + 1)$

See Figure below.

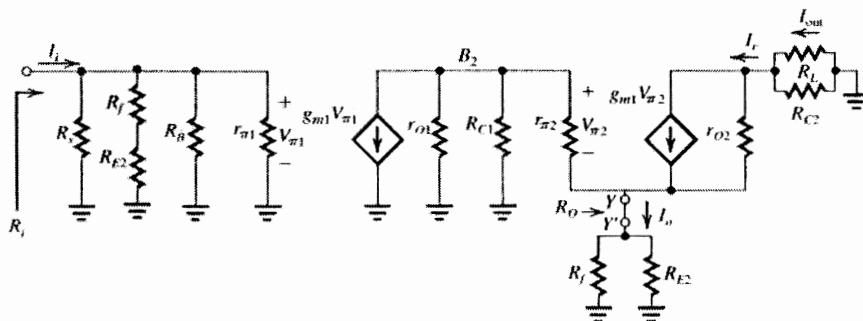




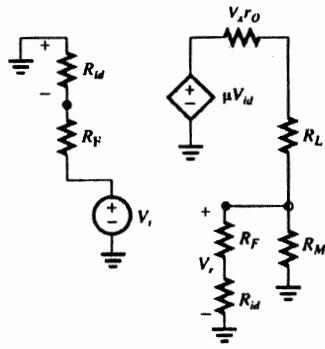

$$\begin{aligned}
 r_{DS} &= \frac{V_A}{I_{DS}} = 30 \text{ k}\Omega \\
 r_{O4} &= \frac{V_A}{I_{DS}} = \frac{24}{0.3 \times 10^{-3}} = 80 \text{ k}\Omega \\
 g_{m2} &= \sqrt{2k'n\left(\frac{W}{L}\right)} I_{DS2} \\
 &= \sqrt{2.120 \times 10^{-6} \cdot 20 \cdot 100 \times 10^{-6}} \\
 &= 0.693 \times 10^{-3} = 0.693 \text{ mS} \\
 g_{m3} &= \sqrt{2k'n\left(\frac{W}{L}\right)} I_{DS3} \\
 &= 2 \text{ mS}
 \end{aligned}$$

9.62

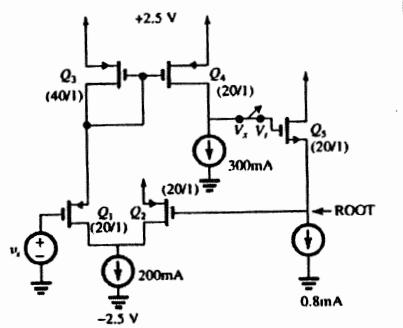

Breaking at the gate of QS:

$$\begin{aligned}
 \frac{V_r}{V_i} &= \left( \frac{g_{m2}r_{DS}}{1 + g_{m2}r_{DS}} \right) \left( \frac{1}{2} g_{m3}r_{O4} \right) \\
 &= \frac{2 \times 10^{-3} \cdot 30 \times 10^3}{1 + 2 \times 10^{-3} \cdot 30 \times 10^3} \\
 &\quad \left( \frac{1}{2} \cdot 0.693 \times 10^{-3} \cdot 80 \times 10^3 \right) \\
 &= 27.26
 \end{aligned}$$

$$1 + A\beta = 28.26$$

$$R_{out} = \frac{1}{g_{m3}(1 + A\beta)} = 17.7 \Omega$$


$$k'n = 2k'r_p = 120 \mu\text{A/V}^2$$

$$V_t = 0.7V$$


$$V_A = 24V/\mu\text{m}$$

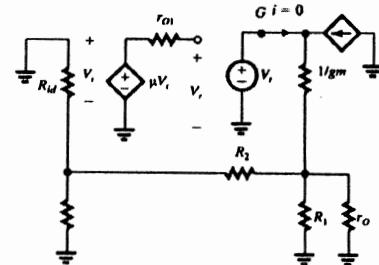9.63

$$\begin{aligned}
 \frac{-V_r}{V_i} &= \frac{(R_2 + R_S \parallel R_{id}) \parallel (R_1 \parallel r_O)}{\frac{1}{g_m} + (R_2 + R_S \parallel R_{id}) \parallel (R_1 \parallel r_O)} \\
 &\quad \cdot \frac{R_S \parallel R_{id}}{R_S \parallel R_{id} + R_2} \cdot \mu \\
 \text{Since } R_{id} &= R_S = \infty \Rightarrow \text{The expression reduces to} \\
 A\beta &= \frac{-V_r}{V_i} = \mu \frac{R_1 \parallel r_O}{\frac{1}{g_m} + (R_1 \parallel r_O)} = 997
 \end{aligned}$$



9.64

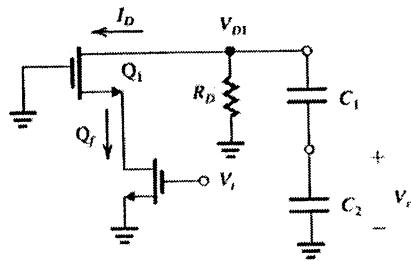

Assume that  $C_1$  and  $C_2$  are small and do not load the output.

Neglect  $r_{\text{af}}$  and  $r_{\text{or}}$ .

Since  $I_D = I_{D1} = I_{D2}$

$$V_{D1} = -gm_f V_t \cdot R_D$$


$$V_r = V_{D1} \cdot \frac{1/SC_2}{\frac{1}{SC_2} + \frac{1}{SC_1}}$$

$$\Rightarrow \frac{-V_r}{V_t} = \frac{C_1}{C_2 + C_1} \cdot gm_f \cdot R_D$$

$$A\beta = \frac{0.9}{0.1 + 0.9} \cdot 1 \times 10 = 9$$

9.66

$\omega$	$\text{Ang}(A)$	$ A B_1$	$ A B_2$
0	0	$10^3$	$10^2$
$10^2$	45	$7.07 \times 10^4$	70.7
$10^3$	95.7	$9.85 \times 10^3$	9.85
$10^4$	180	500	0.5
$\infty$	0	0	0

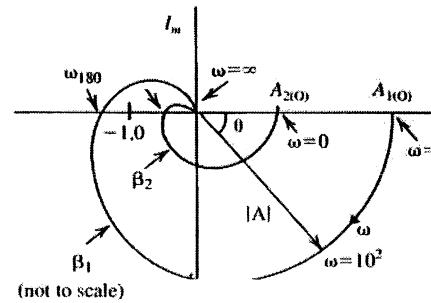

9.65

$$A(S) = \frac{10^5}{1 + 5/100}$$

$$\text{Ang}(A) = -\tan^{-1} \frac{\omega}{100} - 2\tan^{-1} \frac{\omega}{10^4}$$

at  $\omega_{180}$ :  $\text{Ang}(A) = -180^\circ$  for  $\omega_{180} \gg 100$

$$\Rightarrow 180^\circ = 90^\circ + 2\tan^{-1} \left[ \frac{\omega_{180}}{10^4} \right]$$

$$\text{hence } \tan^{-1} \frac{\omega_{180}}{10^4} = \frac{90^\circ}{2}$$

$$\text{i.e. } \frac{\omega_{180}}{10^4} = \tan(45^\circ) = 1$$

$$\therefore \omega_{180} = 10^4 \text{ rad/s}$$

$$|A\beta| = \frac{10^5 \beta}{\sqrt{1 + (10^4/10^2)^2}} \cdot \frac{1}{(\sqrt{1+1})^2} = 1$$

$$\Rightarrow \beta = 0.002$$

$$A_f(0) = \frac{10^5}{1 + 10^5(0.002)} \approx 500 \text{ V/V}$$

9.67

$$A(S) = \frac{10^3}{1 + 5/10^4}$$

$$\beta(S) = \frac{K}{(1 + 5/10^4)^2}$$

$$\text{Ang}(AB) = -\tan^{-1} \frac{\omega}{10^4} - 2\tan^{-1} \frac{\omega}{10^4}$$

$$= -3\tan^{-1} \frac{\omega}{10^4}$$

$$\text{For } 180^\circ: \omega_{180} = \sqrt{3} \times 10^4 \text{ rad/s}$$

$$\text{For } 1 |A\beta(\omega_{180})| < 1$$

$$\frac{10^3}{\sqrt{1 + (\sqrt{3})^2}} \cdot \frac{K}{1 + (\sqrt{3})^2} \leq 1$$

$$\Rightarrow K \leq 0.008$$

9.68

$$A(S) = \frac{1000}{(1 + S/10^4)(1 + S/10^5)^2}$$

and  $\beta$  is independent of frequency

$$\text{Ang}(A) = -\tan^{-1} \frac{\omega}{10^4} - 2\tan^{-1} \frac{\omega}{10^5}$$

$$\text{try } \omega \approx 10^4: 0.5 \cdot 45^\circ + 2 \times 5.7 = 56.4^\circ$$

$$\text{try } \omega = 10^5: 0.5 \cdot 84.2^\circ + 2 \times 45 = 174.2^\circ$$

Iteration yields  $\omega = 1.1 \times 10^5 \text{ rad/s}$

For oscillations:  $|AB(\omega_{180})| \geq 1$

$$\frac{\beta \cdot 10^3}{(\sqrt{1+11^2})(\sqrt{1+1.1^2})} \geq 1$$

$$\Rightarrow \beta \geq 0.0244$$

9.69

$$A(jf) = \frac{(10 \times 10^6)/10^4}{1 + jf/10^4}$$

$$\therefore A(jf) = \frac{10^3}{1 + jf/10^4}$$

$\beta = 0.1$  independent of frequency

$$A_f(jf) = \frac{10^3}{1+10^3(0.1)} \cdot \frac{1}{1 + \frac{jf}{10^4(1+10^3(0.1))}}$$

$$= \frac{9.9}{1 + jf/(101 \times 10^4)}$$

$$A_f(0) = 9.9 \text{ v/v}$$

$$f_{pf} = 10^4 (101) = 1.01 \text{ MHz}$$

$$\text{for } \frac{f}{f_{pf}} \gg 1 : A_f \approx 9.9 \frac{10^4(101)}{f}$$

$$\text{for } A_f = 1 : f = f_t = 10 \text{ MHz}$$

Pole is shifted by  $(1 + A(0)\beta) = 101$

9.70

$$A(j_f) = \frac{10^3}{(1 + j_f/10^4)(1 + j_f/10^5)}$$

(a) closed-loop poles given by

$$1 + A(j_f)B = 0$$

using  $P = j_f$

$$P^2 + P(10^4 + 10^5) + (1 + 10^3\beta)10^4 \cdot 10^5 = 0$$

$$\text{i.e. } P^2 + (1.1 \times 10^9)P + 10^9(1 + 10^3\beta) = 0$$

compare terms with

$$(P + f_{pf})^2 = P^2 + 2f_{pf} \cdot P + f_{pf}^2$$

$$2f_{pf} = (1.1 \times 10^9)$$

$$(1 + 10^3\beta) \times 10^9 = f_{pf}^2$$

$$\Rightarrow f_{pf} = 5.5 \times 10^5$$

$$\text{and } (1 + 10^3\beta) = 3025 \Rightarrow$$

$$\beta = 2.025 \times 10^{-3}$$

(b) At 55 kHz

$$A(f) = \frac{10^3}{\left(1 + j\frac{55 \times 10^3}{10^4}\right)\left(1 + j\frac{55 \times 10^3}{10^5}\right)}$$

$$= \frac{10^3}{(1 + j5.5)(1 + j0.55)}$$

$$= \frac{10^3}{1 + j6.05 - 3.025} = \frac{10^3}{-2.025 + j6.05}$$

$$= -24.75(2.025 + j6.05) = -49.75 - j149.74$$

$$|A(55 \text{ kHz})| = 157.7$$

$$A_f(55 \text{ kHz}) = \frac{-49.75 - j149.74}{1 - (49.75 + j149.74)2.025 \times 10^{-3}}$$

$$= -\frac{49.75 + j149.74}{0.9}(0.9 + j0.3) = 0.16 - j166.3$$

$$|A_f(55 \text{ kHz})| = 166.3$$

(c) from  $S^2 + (\omega_0/Q)S + \omega_0^2$  cf above

$$Q = \frac{f_{pf}}{2f_{pf}} = \frac{1}{2}$$

$$(d) P^2 + 1.1 \times 10^5 P + (1 + 10^3\beta) = 0$$

$$\Rightarrow P^2 + 1.1 \times 10^5 P + 21.25 \times 10^9 = 0$$

$$P = \frac{-1.1 \times 10^5 \pm \sqrt{(1.1 \times 10^5)^2 - 4(21.25 \times 10^9)}}{2}$$

$$= \frac{-1.1 \times 10^5 \pm j2.7 \times 10^5}{2}$$

$$= -5.5 \times 10^4 \pm j1.35 \times 10^5 \text{ Hz}$$

$$Q = \frac{|P|}{2(5.5 \times 10^4)}$$

$$= \frac{\sqrt{(5.5 \times 10^4)^2 + (1.35 \times 10^5)^2}}{1.1 \times 10^5}$$

$$= 1.33$$

9.71

$$A(jf) = \frac{10^3}{(1 + jf/10)(1 + jf/f_p)}$$

$$A_f(0) = \frac{10^3}{1 + 10^3 \beta} = 100$$

$$\Rightarrow \beta = 9 \times 10^{-3} \text{ v/v}$$

Maximally flat when  $Q = 0.707 = 1/\sqrt{2}$

from

$$f^2 + f(f_1 + f_2) + (1 + A_0\beta)(f_1 \times f_2) = 0$$

$$Q = \sqrt{\frac{(1 + A_0\beta)f_1 f_2}{f_1 + f_2}}$$


$$\Rightarrow \frac{\sqrt{(1 + 10^3\beta)10^3 f_{pf}}}{10^3 + f_{pf}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow f_{pf}^2 + (2 \times 10^3)f_{pf} + 10^6 = 2(1 + 10^3\beta)^2 10^6$$

$$\Rightarrow f_{pf} = \frac{18 \times 10^3 \pm \sqrt{(18 \times 10^3)^2 - 4(10^6)}}{2}$$

$$= 17.94 \text{ kHz.}$$

9.72

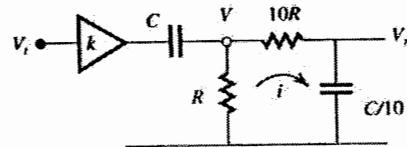

$$\begin{aligned} i &= \frac{SCV_r}{10} \Rightarrow V = V_r + SCR V_r \\ &= V_r(1 + SCR) \\ \text{By KCL: } \Sigma_i &= 0 \Rightarrow a + V \\ \Rightarrow \frac{(KV_r - V)}{1/SC} &= \frac{V}{R} + i = \frac{V}{R} + \frac{SCV_r}{10} \\ KSCV_r - SCV_r(1 + SCR) &= V_r \left( \frac{1 + SCR}{R} + \frac{SC}{10} \right) \end{aligned}$$

Collecting terms:

$$KSCV_r R = V_r [(SCR)^2 + 2.1 SCR + 1]$$

Thus  $L(S) \Delta = V_r / V$ ,

$$\begin{aligned} &= \frac{-K/CR S}{S^2 + \frac{2.1 S}{CR} + \frac{1}{CR^2}} \\ &= \frac{-K/CR S}{S^2 + \left(\frac{\omega_0}{Q}\right)S + \omega_0^2} \end{aligned}$$

from which  $\omega_0 = 1/CR$

$$Q = \frac{1}{2.1 - K}$$

Poles coincide when  $Q = 1/2$

$$\Rightarrow K = 2.1 - 2 = 0.1$$

maximally flat when  $Q = 1/\sqrt{2}$

$$\Rightarrow K = 2.1 - 1.414 = 0.686$$

Oscillates when  $Q \rightarrow \infty$

$$\Rightarrow K = 2.1$$

9.73

$$\begin{aligned} A(f) &= \frac{-K}{1 + j_f/10^5} \\ \text{for } \beta = 1 : A\beta &= \frac{K^3}{\left(1 + \frac{j_f}{10^5}\right)^3} \\ \text{For oscillations to occur: } |A\beta| &\geq 1 \text{ at } \\ \phi(A\beta) &= 180^\circ \\ 3\tan^{-1} & \end{aligned}$$

$$\left(\frac{f_{180^\circ}}{10^5}\right) = 180^\circ \Rightarrow f_{180^\circ} = \sqrt{3} \times 10^5 \text{ Hz}$$

$$f_{180^\circ} = 173.2 \text{ kHz}$$

Amplifier is unstable if  $|A\beta| \geq 1$  at  $f_{180^\circ}$

$$\left[ \frac{K}{\sqrt{1 + (\sqrt{3})^2}} \right]^3 \geq 1 \rightarrow K \geq 2$$

9.74

$$A(f) = \frac{10^5}{1 + j_f/10}$$

$$\text{for } \beta = 1: A(f)\beta = \frac{10^5}{1 + j_f/10}$$

$$\text{for } f \gg 10: |A\beta| \approx 10^5 \cdot \frac{10}{f_1}$$

$$\Rightarrow f_1 = 1 \text{ MHz}$$

$$\text{at } f_1: \text{phase margin} = 180^\circ - \tan^{-1} \frac{10^5}{10}$$

$$= 90^\circ$$

9.75

$$A(f) = \frac{10^5}{1 + j_f/10 (1 + j_f/10^4)}$$

$$A\beta(0) = 10^5 \beta$$

$$A_F(0) = 100 = \frac{10^5}{1 + 10^5 \beta} \Rightarrow \beta \approx 0.01$$

$$\begin{aligned} |A\beta| &= 1 \Rightarrow |1 + j_f/10| \cdot |1 + j_f/10^4| \\ &= 10^5 \beta = 10^3 \end{aligned}$$

$$(1 + f^2/10^2)(1 + f^2/10^8) = 10^6$$

$$f^4 + f^2(10^8 + 10^2) - (10^8)(10^2)10^6 = 0$$

$$f \approx \frac{-10^8 + \sqrt{10^{16} + 4 \times 10^6}}{2}$$

$$\Rightarrow 61.8 \times 10^6 \Rightarrow f = 7.86 \text{ kHz}$$

Phase margin

$$= 180 - \left( \tan^{-1} \frac{7.86 \times 10^3}{10} + \tan^{-1} \frac{7.86}{10} \right)$$

$$\approx 180^\circ - 90^\circ - 38.16^\circ = 51.8^\circ$$

$$\text{For } PM \geq 45^\circ: \tan^{-1} \frac{f_1}{10^4} \leq 45^\circ$$

$$\Rightarrow f_1 \leq 10^4$$

thus

$$|A\beta| = 1 = \frac{10^5 \beta}{\sqrt{1 + (10^4)^2} - \sqrt{2}}$$

$$\Rightarrow \beta = \frac{\sqrt{2}}{100} = 0.0141$$

9.76

$$|1 + e^{-j\theta}| = |1 + \cos\theta - j\sin\theta|$$

$$= [(1 + \cos\theta)^2 + (\sin\theta)^2]$$

$$= [1 + 2\cos\theta + \cos^2\theta + 1 - \cos^2\theta]^{1/2}$$

$$= \sqrt{2}(1 + \cos\theta)^{1/2}$$

$$\text{for } 5\%: 1 + \cos\theta = \frac{1}{1.05^2(2)} = 0.4535$$

$$\theta = 123.13^\circ \text{ and } PM = 180 - \theta = 56.87^\circ$$

$$\text{for } 10\%: 1 + \cos \theta = \frac{1}{1.1^2(2)} = -0.586$$

$\theta = 125.93^\circ$  and  $PM = 54.07^\circ$

for 0.1 dB  $= 10^{0.1/20} = 1.0116$

$$\cos \theta = \frac{1}{2(1.0116)^2} - 1 = -0.5114$$

$\theta = 120.76^\circ$  and  $PM = 59.24^\circ$

for 1 dB  $= 10^{1/20} = 1.122$

$$\cos \theta = \frac{1}{2(1.122)^2} - 1 = -0.6028$$

$\theta = 127.07^\circ$  and  $PM = 52.93^\circ$

### 9.77

$$A(j_f) = \frac{10^5}{\left(1 + \frac{j_f}{10^3}\right)\left(1 + \frac{j_f}{3.16 \times 10^3}\right)\left(1 + \frac{j_f}{10^6}\right)}$$

Assume  $\beta$  independent of frequency

For  $45^\circ$  PM:  $\theta = 180 - 45$

$$\tan^{-1} \frac{f_1}{10^3} + \tan^{-1} \frac{f_1}{3.16 \times 10^3} + \tan^{-1} \frac{f_1}{10^6} = 135^\circ$$


solve  $\Rightarrow f_1 = 3.16 \times 10^3$  Hz

$$|AB(f_1)| = 1 = \frac{10^5 \beta}{\sqrt{1 + (3.16)^2} \cdot \sqrt{2} \cdot \sqrt{1 + (0.316)^2}}$$

$$\Rightarrow \beta = 49 \times 10^{-6}$$

$$Af(0) = \frac{10^5}{1 + 10^5(4.9 \times 10^{-6})} = 16.9 \times 10^3$$


### 9.78

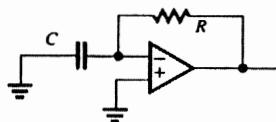

$$\beta = \frac{1/SC}{R + 1/SC} = \frac{1}{1 + SCR}$$

$$\beta(f) = \frac{1}{1 + j2\pi f CR}$$
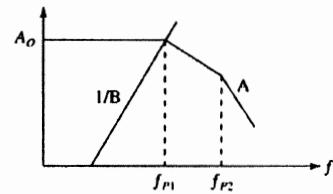
$$A(j_f) = \frac{10^5}{\left(1 + \frac{j_f}{10^6}\right)\left(1 + \frac{j_f}{10^7}\right)}$$



From sketch, we need

$$A_o \frac{1}{2\pi f_{p1} CR} = 1 = AB$$

$$\Rightarrow RC = \frac{A_o}{2\pi f_{p1}} = \frac{10^5}{2\pi \times 10^6} = 159.2 \mu s$$

At 1 MHz  $\text{Ang}(\beta) = -90^\circ$

$$\text{Ang}(A) = -\tan^{-1} 1 - \tan^{-1} 0.1$$

$$= -45 - 5.7 = -50.7^\circ$$

$$\therefore PM = 180 - (90 + 50.7) = 39.3^\circ$$

Gain margin exists at  $\omega_{180}$

$$\text{then } \tan^{-1} \frac{f_1}{10^6} + \tan^{-1} \frac{f_1}{10^7} = 90^\circ$$

$\therefore f_{180} = \sqrt{10^6 \cdot 10^7} = \text{geometric mean}$

$$= 3.16 \text{ MHz}$$

$$A\beta(f_{180}) = 20 \log |A| - 20 \log |1/\beta|$$

$|A|$  has fallen 10 dB,  $|\beta|$  has risen 10 dB

thus  $GM = 1(10) - (-10) = 20 \text{ dB}$

### 9.79

For  $90^\circ$  PM:

$$\tan^{-1} \frac{f_1}{10^3} + \tan^{-1} \frac{f_1}{10^6} + \tan^{-1} \frac{f_1}{10^7} = 90^\circ$$

From graph  $f_1 = 3 \times 10^4$  Hz

thus  $71.6 + 16.7 + 1.72 = 89.9^\circ$  (close)

$$|A(f_1)| = \frac{10^5}{\sqrt{1 + 3^2} \cdot \sqrt{1 + 0.3^2} \cdot \sqrt{1 + 0.03^2}}$$

$$|A\beta| = 1 \Rightarrow B = 33.0 \times 10^{-6}$$

$$\therefore Af(0) = \frac{10^5}{1 + 10^5 \beta} = 2.32 \times 10^4$$

For PM =  $45^\circ$   $f_1 \approx 10^6$  Hz from graph

thus  $84.3 + 45 + 5.7 = 135^\circ$  (ok)

$$|A(f_2)| = \frac{10^5}{\sqrt{1 + 10^2} \cdot \sqrt{2} \cdot \sqrt{1 + 0.1^2}} = 7 \times 10^3$$

$$|A\beta| = 1 \Rightarrow \beta = 1.43 \times 10^{-4}$$

$$\therefore Af(0) = \frac{10^5}{1 + 10^5 \beta} = 6.54 \times 10^3$$

9.80

$$f_1 = 2 \text{ MHz}$$

$$A_o = 80 \text{ dB} = 10^4$$

$$\Rightarrow f_p = f_1 / A = (2 \times 10^6) / 10^4 = 200 \text{ Hz}$$

9.81

$$f_{p1} = 2 \text{ MHz}, \quad f_{p2} = 10 \text{ MHz}$$

$$A_o = 80 \text{ dB} = 10^4$$

$$f_b = \frac{f_p}{A_o} = \frac{10 \times 10^6}{10^4} = 10^3 \text{ Hz}$$

$$f_b' = 1/(C_x + C_e) 2\pi R_x \rightarrow C \times \frac{2 \times 10^6}{10^3} = 2000 \text{ pF}$$

9.82

$$R_1 = R_2 = R$$

$$C_2 = \frac{C_1}{10} = C$$

$$C_f \gg C; \quad g_m = \frac{100}{R}$$

$$\omega_1 = \frac{1}{C_1 R_1} = \frac{1}{10 \cdot C \cdot R}$$

$$\omega_2 = \frac{1}{C_2 R_2} = \frac{1}{C \cdot R}$$


$$\omega_{p1} = \frac{1}{g_m R_2 \cdot C_f R_1} = \frac{1}{100 \cdot C_f \cdot R}$$

$$\begin{aligned} \omega_{p2} &= \frac{g_m C_f}{C_1 C_2 + C_f (C_1 + C_2)} \\ &= \frac{g_m C_f}{C_1 (C_2 + C_f) + C_f C_2} \end{aligned}$$

for  $C_f \gg C \Rightarrow \omega_{p2} \approx \frac{g_m}{C_1 + C_2}$

$$= \frac{100}{11 \times CR} = \frac{9.1}{CR}$$

9.83

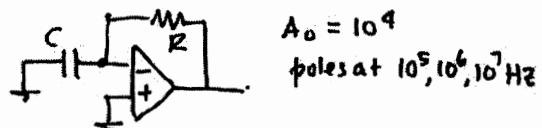

$$A_o = 10^4$$

poles at  $10^5, 10^6, 10^7 \text{ Hz}$

For  $\beta = 1$ ,  $f_p$  must be kept  $\times 10^4$  lower than lowest amplifier pole at  $10^5 \text{ Hz}$

$$\Rightarrow f_p = \frac{10^5}{10^4} = 10 \text{ Hz}$$

$$f_p = \frac{1}{2\pi C R} \quad \text{and} \quad R = 1 \text{ M}\Omega$$

$$\Rightarrow C = \frac{1}{2\pi \frac{10^6}{(10)}} = 15.9 \text{ nF}$$

9.84

$$A_o = 80 \text{ dB} = 10^4$$

$$f_{p1} = 10^5 = \frac{1}{2\pi C_1 R_1} \Rightarrow R_1 = \frac{1}{2\pi f_{p1} C_1}$$

$$\Rightarrow R_1 = \frac{1}{2\pi \cdot 10^5 \cdot (150 \times 10^{-12})} = 10.62 \text{ k}\Omega$$

$$f_{p2} = 10^6 = \frac{1}{2\pi C_2 R_2}$$

$$\Rightarrow R_2 = \frac{1}{2\pi \cdot 10^6 \cdot (5 \times 10^{-12})} = 31.85 \text{ k}\Omega$$

Assuming  $f_{p2} \gg f_{p3}$

$$f_{p1} = \frac{f_{p3}}{10^4} = \frac{2 \times 10^6}{10^4} = 200 \text{ Hz}$$

and  $f_{p1} = \frac{1}{2\pi g_m R_1 R_2 C_f}$

$$\Rightarrow C_f = \frac{1}{2\pi g_m R_1 R_2 f_{p1}}$$


$$\therefore C_f = \frac{1}{2\pi (40 \times 10^{-3})(10.62 \times 10^3)(31.85 \times 10^3) 200}$$

$$= 58.8 \text{ pF}$$

$$f_{p2} = \frac{1}{2\pi C_1 C_2 + C_f (C_1 + C_2)} \frac{g_m C_f}{2\pi C_1 C_2 + C_f (C_1 + C_2)}$$

$$= \frac{1}{2\pi (150 \times 5) 10^{-24} + 58.8 (155) 10^{-24}} = 37.95 \text{ MHz}$$


9.85

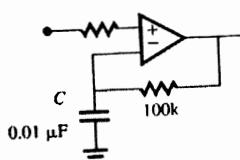

$$\beta(S) = \frac{1}{1 + SCR}$$

$$= \frac{1}{1 + 10^{-3}S}$$
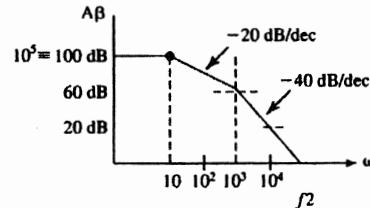
$$(a) A\beta(S) = \frac{10^5}{1 + S/10} \cdot \frac{1}{1 + S/10^3}$$



(b) From plot  $|A\beta| = 20 \text{ dB}$  at  $10^4 = \omega$

$$\text{Hence } |A\beta| = 1 \text{ at } 31.6 \text{ Krad/s } \left( \frac{1}{2} \text{ dec} \right)$$

At  $\omega = 10^4$  the phase is  $-180^\circ$  decreasing at a rate of  $45^\circ/\text{dec}$ , at  $31.6 \text{ K} \frac{\text{rad}}{\text{s}} \frac{1}{2}$  (dec above

$\omega = 10^4$ ) the phase margin is  $-22.5^\circ$ .

The circuit will oscillate.

$$(c) A_f(S) = \frac{\frac{10^3}{1 + S/10}}{1 + \frac{10^3}{1 + S/10} \cdot \frac{1}{1 + S/10^3}}$$

$$= \frac{10^3(1 + S/10^3)}{(1 + S/10)(1 + S/10^3) + 10^3}$$

$$\therefore A_f(S) = \frac{1 + S/10^3}{1 + S/10^6 + S^2/10^9} = \frac{10^6S + 10^9}{S^2 + 10^3S + 10^9}$$

Zero at  $S = -10^{-3} \text{ rad/s}$


$$\text{poles at } \frac{-10^3 \pm \sqrt{10^6 - 4 \times 10^9}}{2}$$

$$= -10^3 \pm j 63.2 \times 10^3$$

$$= -500 \pm j 31.6 \times 10^3 \text{ rad/s}$$

$$\omega_0 = 31.6 \text{ Krad/s}$$

$$Q = 31.6$$

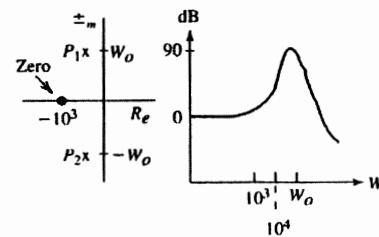

10.1

$$\begin{aligned} V_{ICM(max)} &\leq V_{DD} - |V_{tp}| - |V_{ov1}| - |V_{ov5}| \\ &\leq +2.5 - 0.7 - 0.3 - 0.3 \\ &\leq +1.2V \end{aligned}$$

$$\begin{aligned} V_{ICM(min)} &\geq -V_{SS} + V_{OV3} + V_{tn} - |V_{tp}| \\ &\geq -2.5 + 0.3 (+0.7 - 0.7) \\ &\geq -2.2V \end{aligned}$$

$$\begin{aligned} -V_{SS} + V_{OV6} &\leq V_0 \leq V_{DD} - |V_{OV7}| \\ -2.5 + 0.3 &\leq V_0 \leq +2.5 - 0.3 \\ -2.2V &\leq V_0 \leq +2.2V \end{aligned}$$

10.2

$$V_A' = 25V/\mu m, |V_P'| = 20V/\mu m, L = 0.8\mu m$$

$$\text{Hence } V_A = 20V \text{ and } |V_P| = 16V$$

$$\text{For all devices } V_{ov} = 0.25V$$

$$A = A_1 A_2 = Gm_1 (r_{o2} \| r_{o4}) Gm_2 (r_{o6} \| r_{o7})$$

$$[r_{op} \| r_{on}] = \left[ \frac{V_A}{I} \times \frac{V_P}{I} \right] \times \frac{I}{V_A + V_P} = \left[ \frac{V_A \| V_P}{I} \right]$$

$$\text{For } A_2: R_o = \frac{8.89}{I} \rightarrow \frac{8.89V}{0.4mA} = 22.2k\Omega$$

To avoid systematic output dc. offset

$$\frac{(W/L)_6}{(W/L)_4} = \frac{2(W/L)_7}{(W/L)_5}$$

Since Q5, Q6, Q7 carry I and Q4 only I/2 satisfy requirement by making Q4 have  $(W/L)/2$

$$\text{Since } g_m = \sqrt{2(\mu C_{ox})(W/L)I} = 2k(V_{ov})$$

$$g_{m1} = 2I_1/V_{ov} = 0.4mA/0.25V = 1.6mA/V$$

$$g_{m6} = 2I_6/V_{ov} = 3.2mA/V$$

$$\therefore A = (1.6)(44.4)(3.2)(22.2) = 5047 \text{ v/v}$$

For unity gain amplifier

$$A_f = \frac{A}{1+\lambda\beta} = \frac{5047}{1+5047\beta} = 1$$

$$\text{Thus } (1+\lambda\beta) = 5047$$

$$\text{Then } R_{of} = R_o / (1+\lambda\beta)$$

$$= 22.2k/5047 \approx 4.4\Omega$$

10.3

$$A = A_1 A_2 = Gm_1 (r_{o2} \| r_{o4}) Gm_2 (r_{o6} \| r_{o7})$$

$$\begin{aligned} &= \frac{2I_1}{V_{ov}} \cdot \frac{1}{2} \frac{V_A}{I_1} \cdot \frac{2I_2}{V_{ov}} \cdot \frac{1}{2} \frac{V_A}{I_2} \\ &= \left[ \frac{V_A}{V_{ov}} \right]^2 = 2500 \end{aligned}$$

$$\text{where } V_A = 10V/\mu m \times 1\mu m = 10V$$

$$\text{Hence } V_{ov} = V_A/50 = 10/50 = 0.2V$$

10.4

$$CMRR = g_{m1}(r_{o2} \| r_{o4}) \times 2g_{m3}R_{ss} \text{ with}$$

$$R_{ss} = r_{os}$$

$$80dB = \frac{2I_1}{V_{ov}} \left( \frac{1}{2} \times \frac{V_A}{I_1} \right) \times 2 \times \frac{2I_3}{V_{ov}} \left( \frac{V_A}{I_3} \right)$$

$$= \left( \frac{V_A}{V_{ov}} \right)^2 \times 2 \text{ (Note } I_3 = 2I_1 \text{)}$$

$$10000 = 2 \left( \frac{V_A}{V_{ov}} \right)^2.$$

$$V_A = V_{ov} \sqrt{\frac{10000}{2}}$$

$$V_A = .15 \times \frac{100}{\sqrt{2}}$$

$$V_A = V_A \times L \Rightarrow 20 \frac{V}{\mu m} \times L$$

$$L = \frac{0.15 \times 100}{20 \times \sqrt{2}} \Rightarrow L = \frac{15}{20\sqrt{2}} = 0.53 \mu m$$

### 10.5

$$G_{m1} = 0.3 \text{ mA/V}, G_{m2} = 0.6 \text{ mA/V}, C_2 = 1 \text{ pF}$$

$$r_{o2} = r_{o4} = 222 \text{ k}\Omega, r_{o6} = r_{o7} = 111 \text{ k}\Omega$$

$$(a) f_{p2} = \frac{G_{m2}}{2\pi C_2} = \frac{0.6 \times 10^{-3}}{2\pi 10^{-12}} = 95.5 \text{ MHz}$$

$$(b) R = \frac{1}{G_{m2}} = \frac{1}{0.6} = 1.66 \text{ k}\Omega$$

$$(c) \text{For } PM = 80^\circ: \tan^{-1} \frac{f_t}{f_{p2}} = 10^\circ$$

$$f_t = f_{p2} \tan 10^\circ$$

$$= 95.5 \times 0.176 = 16.84 \text{ MHz}$$

$$C_C = \frac{G_{m1}}{2\pi f_t} = \frac{0.3 \times 10^{-3}}{2\pi 16.84 \times 10^6} = 2.83 \text{ pF}$$

$$A = A_1 A_2 = G_{m1}(r_{o2} \parallel r_{o4}) G_{m2}(r_{o6} \parallel r_{o7})$$

$$= 0.3 \times 111 \times 0.6 \times 55.5$$

$$= 1109 = 60.8 \text{ dB}$$

$$\text{Dominant pole } f_{p1} = f_t / |A|$$

Thus fp1 is approx 3 decades below ft i.e. at 16.84 KHz providing uniform 20 dB/dec slope drawn to fit.

$$(d) f_t = \frac{G_{m1}}{2\pi C_C} \therefore \text{to double } f_t, \text{ halve } C_C$$

$$C_{C(\text{new})} = 1.4 \text{ pF}$$

$$\tan^{-1} \frac{f_t}{f_p} = \tan^{-1} \frac{33.7}{95.5} = 19.4^\circ$$

The zero must be moved to reduce the

$$19.1 - 10 = 9.4^\circ$$

$$\tan^{-1} \frac{f_t}{f_z} = 9.4^\circ \rightarrow \frac{f_t}{f_z} = 0.16$$

$$\Rightarrow f_z = 0.16 f_t = 0.16 \times 33.7 = 5.6 \text{ MHz}$$

$$f_t = \frac{1}{2\pi C_C \left[ R - \frac{1}{G_m} \right]} \rightarrow \left[ R - \frac{1}{G_m} \right] = \frac{1}{2\pi f_t C_C}$$

$$\text{Hence } [R - 1/G_m] = \frac{10^{12} \cdot 10^{-6}}{2\pi 5.6 \times 1.4}$$

$$R = 1.67 + 20.3 = 21.97 \text{ k}\Omega$$

### 10.6

Two-stage amp with  $C_2 = 1 \text{ pF}$

$$f_t = 100 \text{ MHz}, PM = 75^\circ$$

$$\text{For } PM = 75^\circ: \tan^{-1} \frac{f_t}{f_{p2}} = 15^\circ$$

$$\therefore f_{p2} = f_t + \tan 15^\circ = 3.73 f_t = 373 \text{ MHz}$$

$$f_{p2} = \frac{G_{m2}}{2\pi C_2} = \frac{1}{2\pi R_2 10^{-12}} = 373 \text{ MHz}$$

$$\Rightarrow R_2 = \frac{10^{12}}{2\pi (373 \times 10^6)} = 426 \text{ }\Omega$$

$$\Rightarrow G_{m2} = \frac{1}{R_2} = 2.35 \times 10^{-3} \text{ mA/V}$$

$$\text{To move zero to infinity, } R = \frac{1}{G_{m2}} = 426 \text{ }\Omega$$

$$SR = \frac{I}{C_C} = \frac{200 \mu\text{A}}{C_C}$$

$$SR = 2\pi f_t V_{ov1} = 2\pi 10^8 \times 0.2 = 1.26 \times 10^8$$

$$\Rightarrow C_C = \frac{200 \times 10^{-6}}{1.26 \times 10^8} \Rightarrow 1.6 \text{ pF}$$

### 10.7

$$G_{m1} = 1 \text{ mA/V}, G_{m2} = 2 \text{ mA/V},$$

$$R = 500 \text{ }\Omega$$

$$f_t = \frac{G_{m1}}{2\pi C_C} \Rightarrow C_C = \frac{G_{m2}}{2\pi f_t}$$

$$= \frac{1 \times 10^{-3}}{2\pi 100 \times 10^6} = 1.59 \text{ pF}$$

$$\text{For } \frac{1}{G_{m2}} - R = \frac{10^3}{2} - 500 = 0$$

Zero has been moved to  $\infty$

$$\text{For } PM = 60^\circ: f_t = f_{p2} \tan(90 - 60)^\circ$$

$$\Rightarrow f_{p2} = f_t / \tan 30^\circ = 173 \text{ MHz}$$

$$C_2 = \frac{G_{m2}}{2\pi f_{p2}} = \frac{2 \times 10^{-3}}{2\pi (173 \times 10^6)} = 1.84 \text{ pF}$$

### 10.8

$$SR = 60 \text{ V}/\mu\text{s}$$

$$f_t = 50 \text{ MHz}$$

$$(a) SR = 2\pi f_t V_{ov1}$$

$$\Rightarrow V_{ov1} = SR / 2\pi f_t$$

$$= \frac{60 \times 10^6}{2\pi (50 \times 10^6)} \approx 0.2 \text{ V}$$


$$(b) SR = \frac{I}{C_C} \Rightarrow C_C = \frac{100 \mu\text{A}}{60 \times 10^6} = 1.67 \text{ pF}$$

$$(c) I = \frac{1}{2} \mu C_C (W/L) [V_{ov}]^2$$

$$\Rightarrow \left(\frac{W}{L}\right) = \frac{2I}{50(0.2)^2} = \frac{100}{1}$$
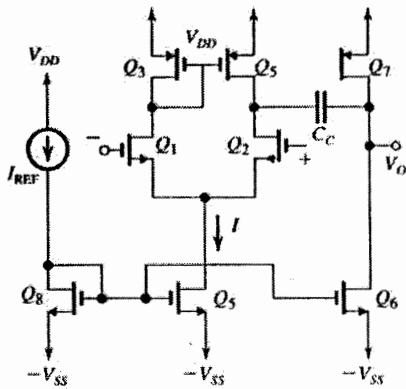
### 10.9

Invert circuit leaving  $V_{DD} \times V_{SS}$  and never all arrows on FETs.



$$V_{ICM(\text{Max})} = V_{DD} - |V_{ov1}| + V_{f_n}$$

$$= +1.65 - 0.2 + 0.5$$

$$= +1.75V$$

$$V_{ICM(\text{Min})} = -V_{SS} + V_{ov_{II}} + V_{ov_1} + V_T$$

$$= -1.65 + 0.2 + 0.2 + 0.5$$

$$= -0.75V$$

$$-V_{SS} + 2V_{ov} + V_T \leq V_0 \leq +V_{DD} - 2V_{ov}$$

$$-1.65 + 0.4 + 0.5 \leq V_0 \leq +1.65 - 0.4$$

$$-0.75V \leq V_0 \leq +1.25V$$

### 10.10

a)

$$PSRR = g_m I (r_{o2} \parallel r_{o4}) g_m r_{o6}$$

$$= \frac{2 \times I/2}{V_{ov}} \left( \frac{V_A}{2(I/2)} \right) \frac{2I}{V_{ov}} \frac{V_A}{I} = 2 \left( \frac{V_A}{V_{ov}} \right)^2$$

$$b) |V_{ov}| = 0.2V, PSRR = 80\text{dB},$$

$$|V_A| = 20V/\mu\text{m}$$

$$PSRR = 2 \left| \frac{V_A}{V_{ov}} \right|^2 = 80 \text{ dB} = 10000$$

$$= 2 \left| \frac{20 \times L}{0.2} \right|^2 \Rightarrow \frac{100}{\sqrt{2}} = 100L \Rightarrow L = 0.7\mu\text{m}$$

### 10.11

$$V_{BIAS1}: V_S \text{ can rise to } V_{DD} + V_T - V_{ov}$$

$$V_{D3} \text{ can rise to } V_{S3} - V_{ov}$$

$$\therefore V_{BIAS1} = V_{DD} - V_{ov_{10}} - V_{ov_4} + V_T$$

$$= 1.65 - 0.2 - 0.2 + 0.5$$

$$= 1.75V$$

$$V_{BIAS2} = V_{DD} - V_{ov_{10}}$$

$$= +1.65 - 0.2 = +1.45V$$

$$V_{BIAS3} = -V_{SS} + V_{ov_{II}}$$

$$= -1.65 + 0.2 = -1.45V$$

### 10.12

$$I = 125\mu\text{A}, I_B = 150\mu\text{A}, V_T = 0.2V$$

$$\text{For } Q_9, Q_{10}: I_B = 150\mu\text{A}$$

$$I = \frac{1}{2} (\mu C_{ox})(W/L)(V_{ov})^2$$

$$150 = \frac{1}{2} 90 (W/L)(0.2)^2$$

$$\Rightarrow (W/L)_{9,10} = (83.33/1)$$

$$\text{For } Q_1, Q_2: I = 125\mu\text{A}/2$$

$$\frac{1}{2} 125 = \frac{1}{2} 250 (W/L)(0.2)^2$$

$$\Rightarrow (W/L)_{1,2} = (12.5/1)$$

$$\text{For } Q_{11}: I = 125\mu\text{A}$$

$$125 = \frac{1}{2} 250 (W/L)(0.2)^2$$

$$\Rightarrow (W/L)_{11} = (25/1)$$

$$\text{For } Q_3, Q_4: I = 125\mu\text{A}/2$$

$$\frac{1}{2} 125 = \frac{1}{2} 60 (W/L)(0.2)^2$$

$$\Rightarrow (W/L)_{3,4} = (52/1)$$

$$\text{For } Q_5, Q_6, Q_7, Q_8: I = 125\mu\text{A}/2$$

$$\frac{1}{2} 125 = \frac{1}{2} 250 (W/L)(0.2)^2$$

$$\Rightarrow (W/L)_{5,6,7,8} = (12.5/1)$$

10.13

$$G_m = \frac{T}{V_{ov}}$$

$$r_o = \frac{V_A}{T}$$

$$R_o = R_{o4} \parallel R_{o6}$$

$$R_{o4} = g_{m4} r_{o4} (r_{o2} \parallel r_{o1} \parallel r_{o3})$$

$$R_{o6} = g_{m6} (r_{o6} \parallel r_{o8})$$

$$A = G_m \cdot R_o$$

$$Q_{10}: I = I_B \Rightarrow g_{m10} = 0.75 \text{ mA/V}$$

$$r_{o10} = 66.6 \text{ k}\Omega$$

$$Q_x: I = 125 \text{ mA} \Rightarrow g_x = 0.31 \text{ mA/V}$$

$$r_{ox} = 160 \text{ k}\Omega$$

$$\therefore R_{o4} = 0.31 \times 160 \times 47 \text{ k} = 235 \text{ k}\Omega$$

$$R_{o6} = 0.31 \times 160 \times 160 \text{ k} = 8000 \text{ k}\Omega$$

$$R_o = 2.35 \parallel 8000 = 1.8 \text{ M}\Omega$$

$$A = g_m, R_o = 0.31 \times 1800 = 558$$

$$\frac{r_o}{V_i} = 1 + \frac{(1/\beta)}{(1/g_m)} = 1 + \frac{g_m}{\beta} = 10$$

$$\therefore \beta = 1/10 = 0.1$$

$$A_F = \frac{A}{1 + A\beta} = \frac{558}{1 + 558 \times 0.1} = 9.8$$

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{1.8}{56.8} = 31.69 \text{ k}\Omega$$

10.14

$$SR = \frac{I}{C_L} \Rightarrow I = SR \times C_L$$

$$= 10 \times 10^6 \times 10 \times 10^{-12}$$

$$= 100 \mu\text{A}$$

$$(1) I_B = 1.21 = 120 \mu\text{A}$$

$$(2) f_p = \frac{1}{2\pi C_L R_o} \cdot f_t = \frac{G_m}{2\pi C_L}$$

$$G_m = \frac{2I/2}{V_{ov}} = \frac{100 \mu\text{A}}{0.2 \text{ V}} = 0.5 \text{ mA/V}$$

$$f_t = \frac{0.5 \times 10^{-3}}{2\pi 10 \times 10^{-12}} = 7.96 \text{ MHz}$$

$$(4) R_{of} = \frac{1}{G_m} = \frac{1000}{0.5} = 2 \text{ k}\Omega$$

$$A_V = f_t / f_p = G_m R_o$$

$$\text{But } R_{of} = \frac{R_o}{1 + G_m R_o} \Rightarrow R_o = 2 \text{ m}\Omega$$

$$\therefore A_V = 0.5 \times 10^{-3} \times 2 \times 10^6 = 1000$$

$$f_p = f_t / 1000 = 7.96 \text{ kHz}$$

$$(5) \theta = -\tan^{-1} \frac{f_t}{f_p} - 2 \left( \tan^{-1} \frac{f_t}{f_p} \right)$$

$$Pm @ f_p^2 = 90^\circ - \tan^{-1} \frac{f_t}{f_p^2}$$

$$= 90^\circ - \tan^{-1} \left[ \frac{7.96 \text{ MHz}}{25 \text{ MHz}} \right]$$

$$= 90^\circ - 17.7^\circ = 72.3^\circ$$

$$(4) \text{ For } pm = 75^\circ: \tan^{-1} \frac{f_t}{f_p^2} = 15^\circ$$

$$\text{Thus } f_t^* = f_p^2 \tan 15^\circ$$

$$= 25 \text{ MHz} \times 0.27 = 6.7 \text{ MHz}$$

$$(5) \frac{f_t^*}{f_t} = \frac{C_L}{C_L^*} \Rightarrow \frac{6.7}{7.96} = \frac{10 \text{ pF}}{C_L^*}$$

$$\Rightarrow C_L^* = C_L \frac{7.96}{6.7} = C_L \times 1.19$$

$\therefore$  Increase  $C_L$  by 19%

$$(6) SR^* = \frac{I}{C_L^*} \Rightarrow \frac{SR}{1.19} = 8.4 \text{ V}/\mu\text{s}$$

10.15

$$A = 80 \text{ dB}, f_t = 10 \text{ MHz}, C_L = 10 \text{ pF}$$

$$I_B = I \text{ All same } |V_{ov}|, L = 0 \mu\text{m}$$

$$|V_A| = 20 \text{ V}$$

$$g_m = \frac{2I}{V_{ov}} \text{ and } f_t = \frac{g_m}{2\pi C_L}$$

$$A = g_m [g_m r_{o4} (r_{o2} \parallel r_{o1})] \parallel (g_m r_{o6} r_{o8})$$

$$\text{Consider } Q_1: I_1 = \frac{1}{2} k_n [W/L]_1 [V_{ov}]^2$$

$$= \frac{1}{2} 200 [W/L]_1 [V_{ov}]^2$$

$Q_1, Q_2, Q_3, Q_6, Q_7, Q_8$  are same

$$g_{m1} = \frac{2I_1}{V_{ov}} \text{ and } r_{o1} = \frac{V_A}{I_1}$$

$$\text{Consider } Q_3, Q_4: I_3 = \frac{1}{2} k_p [W/L]_3 [V_{ov}]^2$$

$$I_1 = \frac{1}{2} \frac{200}{2.5} [W/L]_3 [V_{ov}]^2$$

$$\Rightarrow [W/L]_3 = 2.5 [W/L]_1$$

$$g_{m3,4} = g_{m1} \text{ and } r_{o3,4} = r_{o1}$$

$$\text{Consider } Q_9, Q_{10}: I_{10} = \frac{1}{2} k_p (W/L)_{10} [V_{ov}]^2$$

$$2I_1 = \frac{1}{2} \frac{200}{2.5} (W/L)_{10} [V_{ov}]^2$$

$$\Rightarrow (W/L)_{10} = 5(W/L)_1$$

$$g_{m10} = 2g_{m1} \text{ and } r_{o9,10} = r_{o1/2}$$

$$\text{Consider } Q_{11}: I_{11} = \frac{1}{2} k_n (W/L)_{11} [V_{ov}]^2$$

$$2I_1 = \frac{1}{2} 200 (W/L)_{11} [V_{ov}]^2$$

$$\Rightarrow (W/L)_{11} = 2(W/L)_1$$

$$g_{m11} = 2g_{m1} \text{ and } r_{o11} = r_{o1/2}$$

Thus

$$A = g_{m1} \left[ g_{m1} r_{o1} \left( r_{o1} \parallel \frac{r_{o1}}{2} \right) \right] \parallel [g_{m1} r_{o1} r_{o1}]$$

$$= g_{m1} \left[ g_{m1} r_{o1} \left( r_{o1} \parallel \frac{r_{o1}}{2} \parallel r_{o1} \right) \right]$$

$$10^4 = \frac{1}{4} g_{m1} g_{m1} r_{o1} r_{o1}$$

$$\Rightarrow g_{m1} r_{o1} = 200$$

$$\text{Non } g_{m1} r_{o1} = \frac{2I}{V_{ov}} - \frac{V_A}{I}$$

$$\Rightarrow V_{ov} = 2V_A / 200 = 2(20) / 200 = 0.2V$$

$$\text{Hence } g_{m1} = \frac{1}{2\pi f_c C_L} = 0.628 \text{ mA/V}$$

$$\rightarrow r_{o1} = 200 / g_{m1} = 318 \text{ k}\Omega$$

$$g_m = \frac{2I}{V_{ov}} \Rightarrow I = \frac{g_m V_{ov}}{2}$$

$$\rightarrow I_1 = \frac{g_{m1} V_{ov}}{2} = \frac{0.678 \text{ mA/V} \times 6.7V}{2} = 62.8 \mu\text{A}$$

$$\text{SR} = 2\pi f_c V_{ov} = 2\pi 10 \times 10^6 \times 0.2 = 12.5 \text{ V/}\mu\text{s}$$

$Q_1, Q_2, Q_3, Q_4, Q_5, Q_6, Q_7, Q_8$ :

$$I = \frac{1}{2} k_n (W/L) [V_{ov}]^2$$

$$62.8 = \frac{1}{2} 200 (W/L) [V_{ov}]^2$$

$$\Rightarrow (W/L)_1 = 15.7$$

$$\text{For } Q_3, Q_4: I = \frac{1}{2} \frac{200}{2.5} (W/L) [V_{ov}]^2$$

$$62.8 = \frac{1}{2} \frac{200}{2.5} (W/L) [0.2]^2$$

$$\Rightarrow (W/L)_3 = 2.5 (W/L)_1 = 39.25$$

For  $Q_9, Q_{10}$ :

$$(W/L)_9 = 5(W/L)_1 = 78.5$$

$$\text{For } Q_{11}: (W/L)_{11} = 2(W/L)_1 = 31.4$$

For  $L = 1 \mu\text{m}$ :  $W_x = [W/L]_x \mu\text{m}$

$\therefore$  width for  $Q_1, Q_2, Q_3, Q_6, Q_7, Q_8 = 15.7 \mu\text{m}$

for  $Q_3, Q_4 = 39.25 \mu\text{m}$


for  $Q_9, Q_{10} = 78.5 \mu\text{m}$

for  $Q_{11} = 31.4 \mu\text{m}$

### 10.16

Simply invert circuit relative to  $V_{DD}, V_{SS}$  and reverse all arrows on FETs

### 10.17

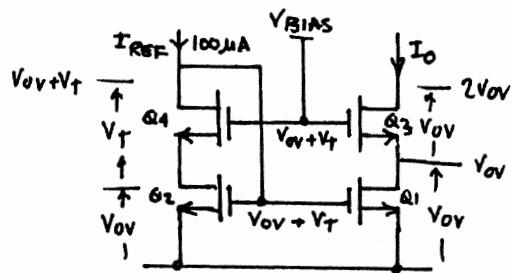

All same  $K(W/L)$   $\therefore I_o \approx I_{REF}$

All same  $r_o = V_A/I = 10V/100\mu A = 100k\Omega$   
 $I = \frac{1}{2} K [W/L] [V_{ov}]^2$

$V_{D3} = V_o$ :  $V_o(\min) = 2V_{ov}$

$R_o$  (looking into  $V_{D3}$  and assuming  $I_o$  current source is ideal,  $r'_o = \infty$ )


$$= r_o \left( 1 + g_m r_o \right) \approx g_m r_o^2$$

$$g_m = \frac{2I}{V_{ov}} = \frac{2 \times 100}{0.2} = 1mA/V$$

$$\text{Then } R_o \approx g_m r_o^2 = 1 \times 10^5 \times 10^5 \approx 10^4 M\Omega$$

10.18

Model:

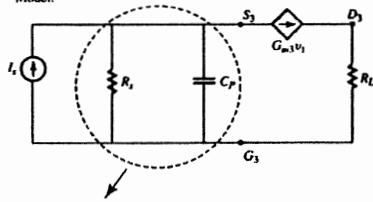

$$\boxed{-Z} \Rightarrow R_s \parallel \frac{1}{C_p S} = \left[ \frac{\frac{1}{R_s C_p S}}{R_s + \frac{1}{C_p S}} \right] \frac{C_p S}{C_p S} = \frac{R_s}{R_s C_p S + 1}$$

Summing currents at node  $S_3$ :

$$-I_S + g_{m3}V_1 + V_1 \frac{(1 + R_s C_p S)}{R_s} = 0$$

$$\frac{V_1}{I_S} = \frac{1}{g_{m3} + \frac{(1 + R_s C_p S)}{R_s}} = \frac{1}{\left(g_{m3} + \frac{1}{R_s}\right) + C_p S}$$

$$W_{3 \text{ dB}} = \frac{\left(g_{m3} + \frac{1}{R_s}\right)}{C_p} \text{ so}$$

$$f_{3 \text{ dB}} = \frac{\left(g_{m3} + \frac{1}{R_s}\right)}{2\pi C_p} \approx \frac{g_{m3}}{2\pi C_p}$$

$$\rho \mu = 180 - \phi_{\text{total}} = 90^\circ - \tan^{-1}\left(\frac{f_t}{f_p}\right)$$

$$\text{For } P_m = 75^\circ: \frac{f_t}{f_p} = \tan 15^\circ = 0.27$$

$$\frac{f_t}{f_p} = \frac{C_p}{C_L} = 0.27$$

$$\therefore C_p = 0.27 C_L$$

10.19

$$I_3 = I_1 \sqrt{\frac{I_{31} I_{32}}{I_{31} I_{32}}} \\ = 154 \sqrt{\frac{10^{-14} \cdot 10^{-14}}{3 \times 10^{-14} \cdot 6 \times 10^{-14}}} \\ = 36.3 \mu\text{A}$$

10.20

$$I_{E_{TOT}} = 0.73 \text{ mA}$$

$$I_{EA} = 0.25(0.73) = 0.1825 \text{ mA}$$

$$I_{EB} = 0.75(0.73) = 0.5475 \text{ mA}$$

$$V_{EB_A} = V_T \ln \frac{0.1835 \times 10^{-3}}{0.25 \times 10^{-14}} = 0.625 \text{ V}$$

$$g_{mA} = \frac{I_C}{V_T} = \frac{I_E}{V_T} = 7.3 \text{ mA/V}$$

$$r_{eA} = \frac{\alpha}{g_{mA}} = 134.3 \Omega$$

$$r_{eA} = (\beta + 1)r_{eA} = 6.85 \text{ k}\Omega$$

$$r_{nA} = \frac{V_A}{I_{CA}} = 274 \text{ k}\Omega$$

$$V_{EB_B} = V_{EB_A} = 0.625 \text{ V}$$

$$g_{mB} = \frac{0.5475}{25} = 21.9 \text{ mA/V}$$

$$r_{eB} = \frac{\alpha}{g_{mB}} = 44.7 \Omega$$

$$r_{eB} = (\beta + 1)r_{eB} = 2.28 \text{ k}\Omega$$

$$r_{nB} = 91.3 \text{ k}\Omega$$

10.21

$$\text{Let } V_{BE} = 0$$

$$\text{For breakdown } V_{ID} = V_{Bi} - V_{B2}$$

$$> V_{BE1} + V_{BE2} + 7 + 50$$

$$\text{or } V_{ID} \geq 58.4 \text{ V}$$

10.22

$$V_{SG1} + V_{GS2} = V_{SG4} + V_{GS3}$$

Since  $V_g$ 's are equal

$$\sqrt{\frac{I_1}{K_1}} + \sqrt{\frac{I_2}{K_2}} = \sqrt{\frac{I_3}{K_3}} + \sqrt{\frac{I_4}{K_4}}$$

$$\sqrt{I_1} \left[ \frac{1}{\sqrt{K_1}} + \frac{1}{\sqrt{K_2}} \right] = \sqrt{I_3} \left[ \frac{1}{\sqrt{K_3}} + \frac{1}{\sqrt{K_4}} \right]$$

$$\text{or } \sqrt{\frac{I_1}{I_3}} = \frac{\sqrt{\frac{1}{K_1}} + \sqrt{\frac{1}{K_2}}}{\sqrt{\frac{1}{K_3}} + \sqrt{\frac{1}{K_4}}}$$

$$K_1 = K_2, \quad K_3 = K_4 = 16 K_1$$

$$\sqrt{I_1} = \sqrt{I_3} \sqrt{\frac{K_2}{K_4}}$$

$$\text{or } I_1 = I_3 \frac{K_2}{K_4} \\ = \frac{I_3}{16} = \underline{\underline{100 \mu\text{A}}}$$

### 10.23

$$\text{Assume } V_{BE} = 0.7 \text{ V}$$

$$I_{ref} = \frac{5 - 14 - (-5)}{R_s}$$

$$= 220.5 \mu\text{A}$$

At this current level


$$V_{BE} = V_T \ln \frac{220.6 \times 10^{-3}}{10^{14}} = 595 \text{ mV}$$

$$\Rightarrow I_{ref} = \frac{10 - 2(0.595)}{39 \text{ k}} = 226 \mu\text{A}$$

$$\text{For } I_{ref} = 0.75 \text{ mA } V_{BE} = 0.625 \text{ V}$$

$$R_s = \frac{10 - 2(0.625)}{0.73 \times 10^{-3}} = 12 \text{ k}\Omega$$

### 10.24

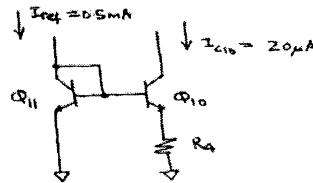

$$I_{c10} R_4 = V_{BE11} - V_{BE10}$$

$$= V_T \ln \frac{I_{ref}}{I_{c10}}$$

$$\therefore R_4 = \frac{25 \times 10^3}{20 \times 10^{-6}} \ln \frac{0.5 \times 10^{-3}}{20 \times 10^{-6}} = 4.02 \text{ k}\Omega$$

$$V_{BE11} = V_T \ln \frac{0.5 \times 10^{-3}}{10^{-14}} = 616 \text{ mV}$$

$$V_{BE10} = V_T \ln \frac{20 \times 10^{-6}}{10^{-14}} = 535 \text{ mV}$$

### 10.25

Assume  $\beta_p \gg 1$

$$I_{C10} = \frac{2I}{1 + 2/\beta_p} + \frac{2I}{\beta_p}$$

$$\approx 2I \left( 1 - \frac{2}{\beta_p} + \frac{1}{\beta_p} \right)$$

$$= 2I(1 - 1/\beta_p)$$

$$\Rightarrow I \approx \frac{I_{C10}}{2} \left( 1 + \frac{1}{\beta_p} \right)$$

$$\text{Thus } \frac{1}{\beta_p} = 0.1 \Rightarrow \beta_p = 10$$

Without the above assumption and using the exact relationship  $\beta_p = 7.79$ ,

### 10.26

In this case

$$\frac{4I}{1 + 2/\beta_p} + \frac{2I}{\beta_p} = I_{C10}$$

For  $\beta_p \gg 1$

$$I_{C10} \approx 4I \text{ or } I = 4.75 \mu\text{A}$$

To correct we need  $I_{C10} = 38 \mu\text{A}$

$$\Rightarrow R_4 = \frac{V_T}{I_{C10}} \ln \frac{0.73 \text{ mA}}{I_{C10}} = 1.94 \text{ k}\Omega$$

### 10.27

At  $I = 9.5 \mu\text{A}$

$$V_{BES} = V_{BE6} = 517 \text{ mV}$$

$$\text{and } V_{BG} = V_{BE6} + IR_2$$


$$= 526.5 \text{ mV}$$

$$\text{If } R_2 \text{ is shorted } V_{BES} = V_{BG} = 526.5 \text{ mV}$$

$$\text{and } I_{C6} = I_s e^{\frac{V_{BE6}}{VT}}$$

$$= 14 \mu\text{A}$$

### 10.28

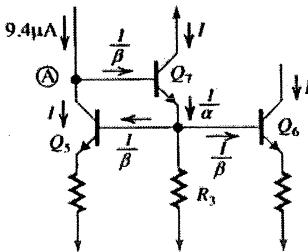

$$\Sigma I @ A/I = I + I/\beta = 9.4 \mu\text{A}$$

$$\Rightarrow I = \frac{9.4}{1 + r\beta} = 9.353 \mu\text{A}$$

$$I_{R3} = \frac{I}{\alpha} = \frac{2I}{\beta} = 9.307 \mu\text{A}$$

$$V_{BS} = I_{R3} R_3 = V_{BES} + \frac{IR}{\alpha}$$

$$V_{BES} = V_T \ln \frac{9.353 \mu}{10^{-14}} = 516.4 \text{ mV}$$

$$\text{Thus } V_{BS} = 525.8 \text{ mV}$$

$$\text{and } R_3 = \frac{V_{BS}}{I_{R3}} = 56.5 \text{ k}\Omega$$

### 10.29

Assume equal collector current

$$I_{C1} = I_{C2} = 9.5 \mu\text{A}$$

$$I_m = I_{B1} - I_{B2} = \frac{I_{C1}}{\beta_1} - \frac{I_{C2}}{\beta_2}$$

$$= 15.7 \text{ mA}$$

$$I_B = \frac{1}{2}(I_{B1} - I_{B2})$$

$$= 55.4 \text{ mA}$$

10.30

$$I_B = 40 \mu A, I_{BE} = 4 \mu A$$

Thus, base currents are

$$I_{B1} = (I_B \pm \frac{I_{BE}}{2})$$

$$= \frac{9.5}{2} \mu A$$

$$\hat{B}_N = \frac{9.5 \mu A}{20 \mu A} = \underline{\underline{250}}$$

$$\check{B}_N = \frac{9.5 \mu A}{42 \mu A} = \underline{\underline{226}}$$

$$\Rightarrow \Delta \beta_N = 24$$

$$\overline{\beta}_N = \frac{\hat{B}_N + \check{B}_N}{2} = 238$$

10.31

$$I_{C1} + I_{C2} = 19 \mu A$$

Mirror forces  $I_{C2} = 0.9 I_{C1}$

$$\text{Thus } I_{C1} = \frac{19}{1.9} \mu A = 10 \mu A$$

$$\text{and } I_{C2} = 9 \mu A$$

$$\begin{aligned} V_{DS} &= \Delta V_{AE} \\ &= V_{BE1} - V_{BE2} \\ &= V_T \ln \frac{10}{9} = \underline{\underline{2.63 \text{ mV}}} \end{aligned}$$

10.32

$$\text{At } I_{C17} = 550 \mu A, V_{BE17} = 618 \text{ mV}$$

$$I_{B17} = \frac{550}{200} = 2.75 \mu A$$

$$\Rightarrow I_{C16} = 9.5 \mu A = I_{B17} + \frac{I_{B17} R_8 + V_{BE17}}{R_9}$$

$$\text{or } R_9 = 99.7 \text{ k}\Omega$$

10.33

Neglecting base currents

$$I_{C18} = I_{C19} = \frac{180}{2} = 90 \mu A$$

$$V_{BE18} = V_T \ln \frac{90 \times 10^{-6}}{10^{-14}} = 573 \text{ mV}$$

$$\text{Thus } R_{10} = \frac{V_{BE18}}{I_{C18}} = 6.37 \text{ k}\Omega$$

$$I_{C14} = 3 \times 10^{-14} e^{573/25} = 270 \mu A = I_{C20}$$

10.34

$$I_{Vcc} = I_{C12} + I_{C13A} + I_{C13B} + I_{C14} + I_{C9} + I_{C8}$$

$$+ I_{C7} + I_{C16}$$

$$= (730 + 180 + 550 + 154 + 19 + 19 + 10.5$$

$$+ 162) \mu A$$

$$= 1.68 \text{ mA}$$

$$P_{Diss} = P_Q = I_{Vcc}(V_{CC} + V_{EE})$$

$$= 1.68(15 + 15) \text{ mW}$$

$$= 50.4 \text{ mW}$$

10.35

Series connection of devices assures the same bias currents.

$$R_{id} = (\beta + 1)(6r_e)$$

$$r_e = \frac{V_T}{9.5 \mu A} = 2.63 \text{ k}\Omega$$

$$R_{id} = 3.17 \text{ M}\Omega$$

$$r_e = \frac{v_{id}}{6r_e}, i_o = 2i_e$$

$$\Rightarrow G_{m1} = \frac{i_o}{v_{id}} = \frac{2}{6r_e} = \frac{1}{3r_e}$$

$$= 127 \mu A/V$$

$$R_{o4} = r_o(1 + gm(R_E \| r_e))$$

$$g_m = 1/r_e$$

$$R_E = 2r_e = 5.36 \text{ k}\Omega$$

$$r_s = (\beta_p + 1)r_e = 134 \text{ k}\Omega$$

$$\text{Thus } R_{o4} = 15.4 \text{ M}\Omega$$

$$R_{o6} = 18.2 \text{ M}\Omega \text{ (from text)}$$

$$R_{o1} = R_{o4} \| R_{o6} = 8.34 \text{ M}\Omega$$

$$G_{m1} R_{o1} = 127 \times 8.34 = 1059 \text{ V/V}$$

See gain decreases due to negative feedback

10.36

$$R_o = r_{o6}(1 + g_{m6}(R_2 \| r_{v6}))$$

need to double the second factor

Since  $r_{v6} \gg R_2$

$$R_{o6} \approx r_{o6}(1 + g_{m6} R_2)$$

Thus

$$1 + g_{m6} R'_2 = 2(1 + g_{m6} R_2)$$

$$g_{m6} = \frac{1}{2.63 \text{ k}\Omega}, R_2 = 1 \text{ k}\Omega$$

$$R'_2 = 4.63 \text{ k}\Omega$$

### 10.37

$$\begin{aligned}
 I_{c5} &= I_{c6} = I_{c7} \\
 \Rightarrow r_{e5} &= r_{e6} = r_{e7} = 2.63 \text{ k}\Omega \\
 (\text{a}) V_{b6} &= (r_{e6} + R_2) i_e = 4.63 \text{ k}\Omega \times i_e \\
 (\text{b}) R_B &= (50\text{k} \parallel r_{e5} \parallel r_{e6}) \\
 &= 45.1 \text{ k}\Omega \\
 \Rightarrow i_{c2} &= \frac{V_{b6}}{R_B} = 0.103 i_e \\
 (\text{c}) i_{b7} &= \frac{i_{c2}}{\beta + 1} = \frac{0.103}{201} i_e = 510 \mu\text{A} \times i_e \\
 (\text{d}) V_{b7} &= V_{b6} + r_{e7} i_{e7} \\
 &= (4.63 \text{ k}\Omega + 2.63 \text{ k}\Omega \times 0.103) i_e \\
 &= 4.9 \text{ k}\Omega \times i_e \\
 (\text{e}) R_{ia} &= \frac{V_{b7}}{i_e} = 4.9 \text{ k}\Omega
 \end{aligned}$$

### 10.38

$$\begin{aligned}
 \frac{\Delta I}{I} &= \frac{\Delta R}{R + \Delta R + r_e} \\
 \Delta I &\approx \text{cami } V_{DS} = \frac{V_{DS}}{2r_e} \\
 \text{Thus } \frac{V_{DS}}{2r_e} &= \frac{\Delta R}{R + \Delta R + r_e}; \quad r_e I = V_T \\
 \frac{V_{DS}}{2r_e I} &= \frac{\Delta R}{R} \left[ \frac{1}{1 + \frac{r_e}{R} + \frac{\Delta R}{R}} \right] (*) \\
 \frac{V_{DS}}{2V_T} \left( 1 + \frac{r_e}{R} \right) &= \frac{\Delta R}{R} \left( 1 - \frac{V_{DS}}{2V_T} \right) \\
 \frac{\Delta R}{R} &= \frac{V_{DS}}{2V_T} \frac{1 + (r_e/R)}{1 - \frac{V_{DS}}{2V_T}}
 \end{aligned}$$

(b)  $V_{DS} = 5 \text{ mV}$ ,  $r_e = 2.63 \text{ k}\Omega$ ,  $R = 1 \text{ k}\Omega$

$$\frac{\Delta R}{R} = \frac{5}{2(25)} \frac{1 + 2.63}{1 - \frac{5}{2(25)}} = 0.40$$

(c)  $R_2$  completely shorted

$$\Rightarrow \frac{\Delta R}{R} = -1$$

$$\text{From } (*) \frac{V_{DS}}{2V_T} = -1 \frac{1}{r_e/R}$$

$$\Rightarrow V_{DS} = -19 \text{ mV} \text{ (or } 19 \text{ mV})$$

### 10.39

Current in the collector of  $Q_3$  remains unchanged at  $9.5 \mu\text{A}$

$$\text{Thus } I_{E3} = I_{E4} = \frac{51}{50} 9.5 \mu\text{A} = 9.69 \mu\text{A}$$

$$I_{C4} = \frac{20}{21} \cdot I_{E4} = 9.23 \mu\text{A}$$

$$\Delta I = 9.5 - 9.23 = 0.27 \mu\text{A}$$

$$V_{OS} = \frac{\Delta I}{G_m} = 2r_e \Delta I$$


with

$$r_e = 2.63 \text{ k}\Omega;$$

$$V_{OS} = 2 \times 2.63 \times 10^3 \times 0.27 \times 10^{-6} = 1.4 \text{ mV}$$

10.40

### Ignoring body effect

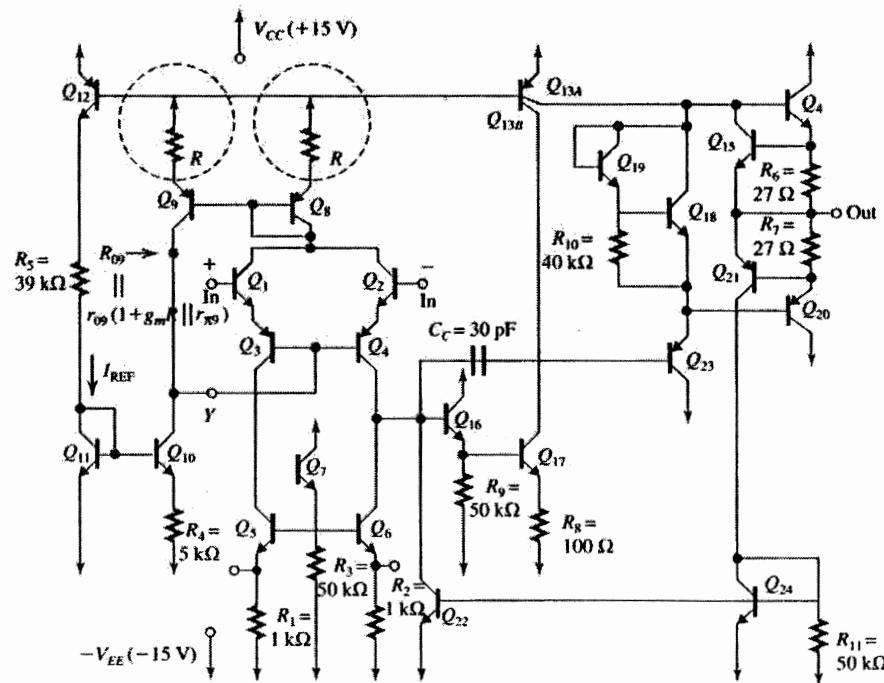

$R = 5 \text{ k}\Omega$  to make  $R_{o9} = R_{o10}$  since  $I$  is the same for  $Q_9$  &  $Q_{10}$

$$R_O(\text{left of Y}) = R_{o9} \parallel R_{o10} = \frac{1}{2} r_o [1 + g_m(5 K \parallel r_x)]$$

### 10.41

Following the instruction of the problem, the resistance seen between the common base connection of  $Q_3$  and  $Q_4$  and ground is :

$$R_f = (1 + A\beta)R_O = (1 + \beta_p)R_O$$

Since the loop is broken, we have :

$$\frac{i}{\beta_p} + \frac{i}{\beta_p} \approx \frac{v_{icm}}{R_f} \Rightarrow$$

$$\frac{2i}{\beta_p} \approx \frac{v_{icm}}{(1 + \beta_p)R_O} \Rightarrow i = \frac{\beta_p}{1 + \beta_p 2R_O} \frac{v_{icm}}{2R_O} = \frac{v_{icm}}{2R_O}$$

$$i_o = E_m i \Rightarrow G_{mem} = \frac{i_o}{v_{icm}} = \frac{E_m i}{v_{icm}} = \frac{E_m}{2R_O}$$

$$CMRR = \frac{G_{m1}}{G_{mem}} = \frac{g_{m1}}{\frac{E_m}{2R_O}} = \frac{2g_{m1}R_O}{E_m} = \frac{2g_{m1}(R_{o9} \parallel R_{o10})}{E_m}$$

### 10.42

$$R_{i2} = (\beta + 1)[r_{e16} + (R_{i17} \parallel R_g)]$$

$$r_{e16} = 1.54 \text{ k}\Omega$$

$$r_{e17} = 45.5 \text{ }\Omega$$

$$R_{i17} = 201(45.5 + 50) = 19.2 \text{ k}\Omega$$

$$\Rightarrow R_{i2} = 201[(1.54 + 19.2 \parallel 50)] \text{ k}\Omega = 3.1 \text{ M}\Omega$$

$$v_{b17} = \frac{(R_{i17} \parallel R_g)}{r_{e16} + (R_{i17} \parallel R_g)} v_{i2}$$

$$= 0.9 v_{i2}$$

$$i_{c17} = \frac{\alpha}{r_{e17} + R_s} 0.9 v_{i2}$$

$$\Rightarrow G_{m2} = \frac{\alpha(0.9)}{45.5 + 50} = 9.38 \text{ mA/V}$$

### 10.43

$$R_{o17} = 787 \text{ k}\Omega$$

$$i_{c13B} = 550 \mu\text{A}$$

$$g_{mB8} = 22 \text{ mA/V};$$

$$r_{aB8} = (\beta + 1)/g_m = 2.32 \text{ k}\Omega$$

$$r_o = \frac{50}{550 \mu\text{A}} = 90.9 \text{ k}\Omega$$

$$R_{o13B} = r_o(1 + g_m(R_E \parallel r_o))$$

$$= 90.9[1 + 22(R_E \parallel 2.32)]$$

$$= 787$$

$$\Rightarrow R_E \parallel 2.32 = 0.348$$

$$\text{and } \frac{1}{R_E} = 2.44 \text{ or } R_E = 0.410 \text{ k}\Omega$$

$$R_E = 410 \text{ }\Omega$$

$$\text{Current } \frac{R_{E12}}{R_E} = \frac{550 \mu\text{A}}{730 \mu\text{A}} \Rightarrow R_{E12} = 309 \text{ }\Omega$$

$$\frac{R_{E13A}}{R_E} = \frac{550}{180} = 1.25 \text{ k}\Omega$$

### 10.44

$$V_o = V_{CC} - V_{CEset18A} - V_{BE14}$$

$$= 4.2 \text{ V}$$

$$V_o \approx -V_{EE} + V_{CEset17} + V_{BE23} + V_{BE20}$$

$$= -5 + 0.2 + 0.6 + 0.6$$

$$= -3.6 \text{ V}$$

### 10.45

With  $Q_{23}$  removed, current in  $Q_{17}$  increases to  $730 \mu\text{A}$ . This changes  $G_{m2}$

$$r_{e17} = \frac{V_T}{730 \mu\text{A}} = 34.2 \text{ }\Omega$$

$$\Rightarrow G_{m2} = 0.923 \frac{\alpha}{100 + 34.2} = 6.8 \text{ mA/V}$$

Because  $r_{e17} \gg r_{o13B} R_{o2}$  remains Virtually unchanged at  $81 \text{ k}\Omega$

$$R_{i3} = (\beta + 1)(R_L \parallel r_{o13A}) = 74 \text{ k}\Omega$$

$$\Rightarrow A_v = -6.8(81) \frac{74}{74 + 81} = -263 \text{ V/V}$$

### 10.46

Ignore base current of Qs

$$180 \mu\text{A} = I_{C15} + \frac{I}{\beta_{T1}}$$

$$\text{where } I = I_{R6}$$

$$I_{C15} = I_S e^{\frac{V_{BE}}{kT}}$$

$$\text{where } V_{BE} = IR_6$$

$$\text{Thus } I = \frac{V_T}{27} \ln \left[ \frac{180 \mu\text{A} - \frac{I}{201}}{I_S} \right]$$

$$\approx 191,422 \text{ V/V}$$

$$= 105.6 \text{ dB}$$

Output current is limited to  $\pm 20$  mA  
(see problem 37 and 38)

$$\Rightarrow |V_o| < 20 \text{ mA} (200)$$

$$|V_o| < 4 \text{ V}$$

To obtain a seed solution, let  $I = 0$  right hand side

$$\Rightarrow I = \frac{V_T}{27} \ln \frac{180 \mu\text{A}}{10^{-14}} = 21.9 \text{ mA}$$

Iterating  $I = 21.0 \text{ mA}$

### 10.47

Maximum output current of the 1<sup>st</sup> stage = 19  $\mu\text{A}$

$$\Rightarrow I_{C22} = 19 \mu\text{A} \Rightarrow V_{BE22} = V_{BE24} = 534 \text{ mV}$$

$$\Rightarrow I_{R11} = \frac{534}{50} = 10.7 \mu\text{A}$$

$$\therefore I_{c21} = (19 + 10.7) \mu\text{A} = 29.7 \mu\text{A}$$

$$\text{and } V_{BE21} = 545.3 \text{ mV}$$

$$V_{BE21} = IR_7 \Rightarrow I = 20.2 \text{ mA}$$

A simple doubling of  $R_7$

### 10.48

$$\frac{V_o}{V_i} = \frac{243.147}{0.97} = 250.667 \text{ V/V} \approx \underline{108 \text{ dB}}$$

$$\frac{R_L}{R_o + R_L} = 0.9 \Rightarrow R_o = R_L \left( \frac{1}{0.97} - 1 \right)$$

$$\text{or } R_o = \underline{61.9 \Omega}$$

$$\frac{V_o}{V_i} \Big|_{R_L=200} = 250.667 \cdot \frac{200}{200 + 61.9}$$

### 10.49

86° PM says that 2<sup>nd</sup> pole introduces 10° of phase shift at 1MHz

$$\text{i.e. } \tan^{-1} \frac{f_t}{f_{p2}} = 10^\circ$$

$$\text{or } f_{p2} = \underline{5.47 \text{ MHz}}$$

### 10.50


Each pole adds 5° of phase shift

$$\tan^{-1} \frac{10^k}{f_{2,k}} = 5^\circ$$

$$\Rightarrow f_{2,k} = \underline{11.4 \text{ MHz}}$$

### 10.51

Consider Bode plot

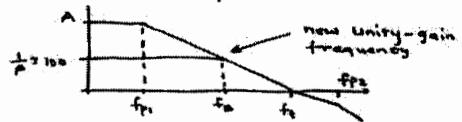

85° of closed-loop phase margin

$$\Rightarrow \tan^{-1} \frac{f_t}{f_{p2}} = 5^\circ$$

$$\text{or } f_t = \underline{437 \text{ kHz}}$$

Recalling the 'broadbanding' effect of negative feedback, we get

$$f_t = f_{p1} (1 + \alpha \beta) = f_{p1} \alpha \beta$$

$$\text{Loop gain } \alpha \beta = 2.43 \times 10^5 \cdot \frac{1}{100} = 2.43 \times 10^3$$

$$\Rightarrow f_{p1} = \underline{150 \text{ Hz}}$$

$$f_t = \frac{C_m}{2 \pi C_L} = 437 \text{ kHz}$$

$$\Rightarrow C_L = \frac{1}{5.26 \times 10^5 (2\pi) 437 \times 10^3} = \underline{0.69 \text{ pF}}$$

### 10.52


$$\text{dominant pole } f_p = \frac{1}{2\pi R (A_C)} ; A = 1000$$

with single pole response

$$A_{ofp} = f_t \Rightarrow f_p = \frac{5 \times 10^6}{10^6} = 5 \text{ Hz}$$


$$\Rightarrow R = \frac{1}{2\pi (5) 1000 (50 \text{ pF})} = \underline{637 \text{ k}\Omega}$$

10.53

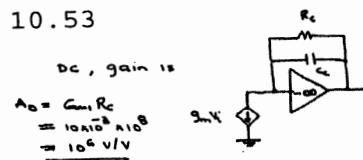

$$f_P = \frac{1}{2\pi R_C C_e} = \frac{1}{2\pi \times 10^8 \times 50 \times 10^{-12}} = 31.8 \text{ Hz}$$

$$f_T = A_0 f_P = 31.8 \text{ MHz}$$

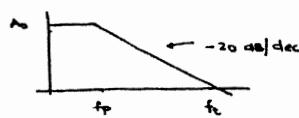

$$SR = \frac{2I}{C_C}$$

$$G_{m1} = \frac{I}{2V_T} \Rightarrow 2I = 4G_{m1}V_T$$

$$SR = \frac{4G_{m1}V_T}{C_C} = \frac{4(10 \times 10^{-8})(25 \times 10^{-3})}{50 \times 10^{-12}} = 20 \text{ V/NS}$$

10.54

$$I_{E1} = I_{E2} = 50 \mu\text{A} = I_{E3} = I_{E4}$$

$$I_{E5} = I_{mA}; V_{BE5} = V_{BE6}$$

$$\therefore I_{E6} = I_{mA} = I_{E7}$$

$$r_{e1} = r_{e2} = 500 \Omega$$

$$r_{e3} = r_{e6} = r_{e7} = 25 \Omega$$

$$G_{m1} = 2 \left( \frac{1}{2r_{e1}} \right) = 2 \text{ mA/V}$$

$$R_{o1} = (\beta + 1) (r_{e1} \parallel r_{e6})$$

$$= 1.25 \text{ k}\Omega$$

$$\text{and } A_1 = G_{m1}R_{o1} = 2.5 \text{ V/V}$$

10.55

$$I = 10 \mu\text{A}, \frac{I_{S2}}{I_{S1}} = 2,$$

$$R_2 = 1.73 \text{ k}\Omega, R_3 = R_4 = 20 \text{ k}\Omega,$$

$$I_S = 10 \mu\text{A}, I_6 = 40 \mu\text{A}$$

$$\text{From } V_{BE5} = V_{BE1} \Rightarrow V_T \ln \frac{I_S}{I_{S1}} = V_T \ln \frac{I_1}{I_{S1}}$$

$$\text{or } \frac{I_S}{I_{S1}} = \frac{I_1}{I_{S1}}$$

Since  $I_S = 10 \mu\text{A} = I_1$ , then  $\frac{I_{S2}}{I_{S1}} = 1$  or equivalently  $Q_1$  and  $Q_5$  have the same emitter area.

For  $Q_6: I_6 = 40 \mu\text{A}$  or  $I_6 = 4I_1$ . Similar to  $Q_5$ :

$$V_{BE6} = V_{BE1}, \text{ therefore: } \frac{I_{S6}}{I_{S1}} = 4. \text{ If a resistor } R_6 \text{ is connected to the emitter of } Q_6 \text{ and the current } I_6 \text{ is reduced to } 10 \mu\text{A}, \text{ then we can write:}$$

$$V_T \ln \frac{I_1}{I_{S1}} - V_T \ln \frac{I_6}{I_{S6}} = R_6 I_6$$

$$\Rightarrow V_T \ln \frac{I_1 I_{S6}}{I_{S1} I_6} = R_6 I_6$$

$$\therefore 25 \times 10^{-5} \times \ln 4 = R_6 \times 10 \times 10^{-6}$$

$$\Rightarrow R_6 = 3.5 \text{ k}\Omega$$

The output resistance of  $Q_5$  is simply  $r_{o5}$ :

$$R_{o5} = r_o = \frac{V_A}{I_C} = \frac{30}{10 \mu\text{A}} = 3 \text{ M}\Omega$$

For Q6, the output resistance is increased by a factor of  $(1 + g_m R'_{E})$  where


$$R'_{E} = R_6 \parallel r_{o6} \text{ (See Eq. on page of the Text.)}$$

$$R_{o6} = (1 + g_m R'_{E})r_{o6}$$

$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{10}{25} = 0.4 \text{ mA/V}$$

$$r_{o6} = \frac{\beta_n}{g_m} = \frac{40}{0.4} = 100 \text{ k}\Omega, r_{o6} = 3 \text{ M}\Omega$$
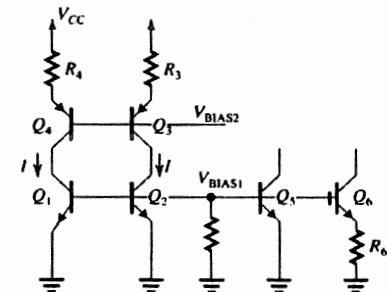
$$R_{o6} = (1 + 0.4 \times (3.5 \text{ k}\Omega \parallel 100 \text{ k}\Omega)) \times 3 \text{ M}\Omega = 7 \text{ M}\Omega$$



### 10.56

a)  $V_{CC} = 3 \text{ V}$   $V_{BIAS} = 2.3 \text{ V}$

The minimum allowed value of  $V_{ICM}$  in the circuit of Fig. 12.40(a) is limited by the need to keep  $Q_1$  in the active mode. Since the collector of  $Q_1$  is at a voltage  $V_{BG3} \approx 0.7 \text{ V}$ , we see that the voltage applied to the base of  $Q_1$  cannot go lower than  $0.1 \text{ V}$ . Thus  $V_{ICM\min} = 0.1 \text{ V}$


For  $V_{ICM\max}$ , see Eq. on page of the Text:

$$V_{ICM\max} = V_{CC} - 0.8 \text{ V} = 3 \text{ V} - 0.8 \text{ V} = 2.2 \text{ V}$$

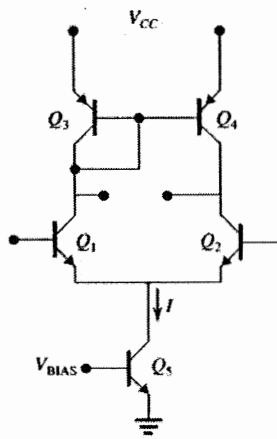b) Similarly,  $V_{ICM\max}$  is limited by the need to keep  $Q_1$  in the active mode.  $V_{ICM\max} = V_{CC} - 0.1 \text{ V} = 2.9 \text{ V}$

The lower end of the input common-mode range is achieved when the voltage across  $Q_5$ ,  $V_{CES}$ , does not fall below  $0.1 \text{ V}$ . Hence:

$$V_{ICM\min} = 0.1 + 0.7 = 0.8 \text{ V}$$



### 10.57

$$V_{CC} = 3 \text{ V}, V_{BIAS} = 2.3 \text{ V},$$

$$I = 20 \mu\text{A}, R_C = 20 \text{ k}\Omega$$

From Equations we have :

$$\begin{aligned} V_{ICM\min} &= V_{RC} - 0.6 \text{ V} = \frac{I}{2} \times R_C - 0.6 \text{ V} \\ &= \frac{20}{2} \times 10^{-6} \times 20 \times 10^3 - 0.6 = -0.4 \text{ V} \end{aligned}$$

$$V_{ICM\max} = V_{CC} - 0.8 \text{ V} = 2.2 \text{ V}$$

$$-0.4 \text{ V} \leq V_{ICM} \leq 2.2 \text{ V}$$

$$\begin{aligned} \frac{v_o}{v_{id}} &= -g_{m1,2}R_C = -\frac{I/2}{V_T}R_C \\ &= -\frac{V_{RC}}{V_T} = -\frac{20/2 \times 10^{-6} \times 20 \times 10^3}{25 \times 10^{-3}} = 8 \text{ V/V} \end{aligned}$$

### 10.58

$$\frac{v_o}{v_{id}} = -g_{m3,4}R_C.$$

With  $A_V = 10 \text{ V/V}$  and  $I_6 = 10 \mu\text{A}$ , we have :

$$g_{m3} = \frac{I_{C3}}{V_T} = \frac{10/2 \times 10^{-6}}{25 \times 10^{-3}}$$

$$\Rightarrow g_{m3,4} = 0.2 \text{ mA/V}$$

Then  $10 \text{ V/V} = -0.2R_C \Rightarrow R_C = 50 \text{ k}\Omega$

$$R_{id} = 2r_{m3,4} = 2 \frac{\beta_n}{g_{m3}} = 2 \times \frac{40}{0.2} = 400 \text{ k}\Omega$$

To find the common-input range, we calculate

$$V_{RC}: V_{RC} = 50 \text{ k}\Omega \times \frac{10}{2} \mu\text{A} = 0.25 \text{ V} \text{ From}$$

discussion on page of the Text :

$$V_{ICM\min} = 0.1 + 0.7 = 0.8 \text{ V},$$

$$V_{ICM\max} = V_{CC} - V_{RC} - 0.1 + 0.7$$

$$= 3 - 0.25 - 0.1 + 0.7$$

$$= 3.35 \text{ V}$$

$$0.8 \text{ V} \leq V_{ICM} \leq 3.35 \text{ V}$$

As we can see, in the circuit in Fig. 12.41, the input common-mode range is extended above  $V_{CC}$ .

### 10.59

$$R_{id} = 2r_{e1} = 2p_F/g_{m1} = 2 \times 10 \times \frac{25 \times 10^{-3}}{\frac{6}{2} \times 10^{-6}}$$

$$= 167 \text{ k}\Omega$$

To find the short-circuit trans conductance, we short the output to ground as shown in Fig. 12.43(b) on the same page of the Text:

$$G_{m1} = \frac{i_{C1}}{V_{id}/2} \text{ (see Example 12.5)}$$

$$r_{o1} = \frac{|V_{AP}|}{I_{C1}} = \frac{20}{3} = 6.7 \text{ M}\Omega$$

$$r_{o2} = \frac{|V_{AD}|}{I_{C2}} = \frac{30}{3} = 10 \text{ M}\Omega$$

$$r_{e2} = \frac{1}{g_{m2}} = \frac{V_T}{I_{C2}} = \frac{25}{3} = 8.3 \text{ k}\Omega$$

$R_7 = 22 \text{ k}\Omega$  and if we neglect  $r_{o1}$  and  $r_{o2}$  as they are large, we can write :

$$i_{e2} = g_{m2} \left( \frac{v_{id}}{2} \right) \frac{R_7}{r_{e2} + R_7} = \frac{3 \times 10^{-6}}{25 \times 10^{-3}}$$

$$\left( \frac{v_{id}}{2} \right) \frac{22 \text{ k}\Omega}{8.3 \text{ k}\Omega + 22 \text{ k}\Omega} = 87.1 \times 10^{-6} \frac{v_{id}}{2}$$

$$G_{m1} = \frac{i_{e1}}{v_{id}/2} = 0.087 \text{ mA/V}$$

$$\text{Now to calculate } R_o : R_o = \left( R_{o9} \parallel R_{o7} \parallel \frac{R_L}{2} \right)$$

$$R_{o9} = r_{o9} + (R_9 \parallel r_{m9})(1 + g_{m9}r_{o9}),$$

$$r_{o9} = \frac{V_{AE}}{I_{en}} = \frac{20}{6} = 6.7 \text{ M}\Omega,$$

$$r_{m9} = \frac{\beta_P}{g_{m9}} = \frac{10}{6/25} = 41.7 \text{ k}\Omega$$

$$R_{o9} = 6.7 \text{ k}\Omega + (33 \text{ k}\Omega \parallel 41.7 \text{ k}\Omega)$$

$$\left( 1 + \frac{6 \times 10^{-6}}{25 \times 10^{-3}} \times 6.7 \times 10^6 \right)$$

$$\Rightarrow R_{o9} = 36.3 \text{ M}\Omega$$

$$R_{o7} = r_{o7} + (R_7 \parallel r_{m7})(1 + g_{m7}r_{o7}),$$

$$r_{o7} = \frac{V_{AN}}{I_{C7}} = \frac{30}{3} = 10 \text{ M}\Omega,$$

$$r_{m7} = \frac{30}{6/25} = 5 \text{ k}\Omega$$

$$g_{m7} = \frac{6}{25} = 0.24 \text{ mA/V}$$

$$R_{o7} = 10 \text{ k}\Omega + (22 \text{ k}\Omega \parallel 5 \text{ k}\Omega)$$

$$(1 + 0.24 \times 10^{-3} \times 10 \times 10^6)$$

$$\Rightarrow R_{o7} = 19.8 \text{ M}\Omega$$

$$\therefore R = 36.3 \parallel 19.8 \parallel 1.3/2 = 0.62 \text{ M}\Omega$$

$$A_d = G_{m1}R = 0.087 \times 10^{-3} \times 0.62 \times 10^6$$

$$= 54 \text{ V/V}$$

$$A_d = 54 \frac{\text{V}}{\text{V}}$$

### 10.60

$$A_{\text{open}} = G_{m1} \cdot R_{\text{out}}$$

$$G_{m1} = \frac{i_o}{V_{id}/2} \text{ where}$$

$$i_o \approx i_{\pi 7} = g_{m1} = \left( \frac{V_{dd}}{2} \right) \left[ \frac{R_7}{R_7 + r_{\pi 7}} \right]$$

$$R_7 = \frac{0.2 \text{ V}}{(2I + I)} = \frac{0.2 \text{ V}}{3I} \text{ and}$$

$$r_{\pi 7} \approx \frac{1}{g_{m1}} = \frac{V_T}{I_{C7}} = \frac{25 \text{ m}}{2I}$$

$$\therefore G_{m1} = \left[ \frac{I_{C1}}{V_T} \right] \left[ \frac{\left( \frac{0.2}{3I} \right)}{\left( \frac{25 \text{ m}}{2I} \right) + \left( \frac{0.2}{3I} \right)} \right]$$

$$= \frac{I}{25 \text{ m}} \left[ \frac{\frac{0.2}{3I}}{\frac{75 \text{ m}}{2I} + \frac{0.4}{6I}} \right] = \frac{I}{25 \text{ m}} \left[ \frac{0.2 \times 6I}{0.475 \times 3I} \right]$$

$$G_{m1} = 33.7I$$

$$R_{\text{out}} = R_{O7} \parallel R_{O9}$$

$$R_{O7} = r_{O7} + (R_7 \parallel r_{\pi 7})(1 + g_{m7}r_{O7})$$

using  $\beta_n = 40$ ,  $V_{An} = 30$ :

$$r_{O7} = \frac{V_{An}}{I_{C7}} = \frac{30}{2I}$$

$$r_{\pi 7} = \frac{\beta_n}{g_{m7}}$$

$$g_{m7} = \frac{I_{C7}}{V_T} = \frac{2I}{25 \text{ m}}$$

$$r_{\pi 7} = \frac{40}{2I} \times 25 \text{ m} = \frac{1}{2I}$$

$$R_{O7} = \frac{30}{2I} + \left[ \frac{\frac{0.2}{3I} \times \frac{1}{2I}}{\left( \frac{0.2}{3I} + \frac{1}{2I} \right)} \right] \times \left[ 1 + \frac{2I}{25 \text{ m}} \times \frac{30}{2I} \right]$$

$$R_{O7} = \frac{30}{2I} + \frac{\left[ \frac{0.2}{6I} \right]}{\left[ \frac{0.4 + 3}{6I} \right]} \times [1 + 1, 200]$$

$$= \frac{30}{2I} + \frac{0.2}{3.4I} \times 1, 201$$

$$R_{O7} = \frac{102 + 240.2}{6.8I} = \frac{50.3}{I}$$

$$R_{O9} = r_{O9} + (R_9 \parallel r_{\pi 9})(1 + g_{m9}r_{O9}) \text{ where}$$

$$R_9 = \frac{0.3}{2I}$$

using  $\beta_p = 10$  and  $|V_{A_p}| = 20 \text{ V}$

$$r_{O9} = \frac{|V_{A_p}|}{I_{C9}} = \frac{20}{2I}$$

$$g_{m9} = \frac{I_{C9}}{V_T} = \frac{2I}{25 \text{ m}}$$

$$r_{\pi 9} = \frac{B_p}{g_{m9}} = \frac{10 \times 25 \text{ m}}{2I}$$

$$R_{O9} = \frac{20}{2I} + \frac{\left[ \frac{0.3 \times 0.25}{2I} \right]}{\left( \frac{0.3 + 0.25}{2I} \right)} \times \left[ 1 + \frac{2I}{25 \text{ m}} \times \frac{20}{2I} \right]$$

$$= \frac{20}{2I} + \frac{0.075}{(0.55)2I} \times [80I]$$

$$R_{O9} = \frac{(20 + 109.2)}{2I} = \frac{129.2}{2I} =$$

$$R_{\text{out}} = R_{O7} \parallel R_{O9} = \frac{\frac{I}{I} \times \frac{64.6}{I}}{\left( \frac{50.3 + 64.6}{I} \right)} = \frac{3,249.4}{114.9I}$$

$$= \frac{28.3}{I}$$

$$A_{\text{open}} = 33.7I \times \frac{28.3}{I} = 0.84 \text{ V/V}$$

$$R_{\text{out}} = R_{O7} \parallel R_{O9} \parallel \left( \frac{R_L}{2} \right) = \frac{\frac{28.3 \cdot R_L}{I}}{\frac{28.3(2) + IR_L}{2I}}$$

$$= \frac{28.3(R_L)}{56.6 + IR_L}$$

$$A_d = 33.7I \times \frac{28.3(R_L)}{56.6 + IR_L} = \frac{953.7IR_L}{56.6 + IR_L}$$

$$\text{For } A_d = 160 \text{ V/V} = \frac{953.7 \times 2 \times 10^6 \times I}{56.6 + I \times 2 \times 10^6}$$

$$160(56.6) + [I \times 2 \times 10^6 \times 160 - I \times 953.7 \times 2 \times 10^6] = 0$$

$$I(320 \times 10^6 - 1, 907 \times 10^6) = -9056$$

$$I = \frac{-9056}{-1, 587 \text{ M}} = 5.7 \mu\text{A}$$

$$\text{For } A_d = 320 \text{ V/V} = \frac{1, 907 \text{ M} \times I}{56.6 + I(2 \text{ M})}$$

$$320(56.6) = [1, 907 \text{ M} - 320(2 \text{ M})]I$$

$$I = \frac{18, 112}{1, 267 \text{ M}} = 14.3 \mu\text{A}$$

### 10 . 61

(a) To find the loop gain of the common-mode feedback loop for the circuit in Fig. 12.44 of the Text, we set the input voltage to zero (that is,  $I_1$ , and  $I_2$  are zero), break the loop at the input of the common-mode feedback circuit block, apply a test voltage  $v_i$  to the input of common-mode feedback circuit and find the output voltage  $v_o$  at the output of the amplifier (where the loop was broken), and then  $A\beta = -\frac{v_o}{v_i}$ . Looking at half circuit and assuming that  $r_{o7}$  is relatively large, we

$$\text{have : } i_{o7} \approx \frac{v_i}{(\beta + 1)(r_{e7} + R_7)} \text{. Note that}$$

$(\beta + 1)(r_{e7} + R_7)$  is the small-signal input resistance seen at the base of  $Q_7$ .

$$\text{Thus, } i_o = i_{e7} = \beta i_{o7} \approx \frac{\beta v_i}{(\beta + 1)(r_{e7} + R_7)}$$

$$= \frac{v_i}{\frac{\beta + 1}{\beta}(r_{e7} + R_7)} \approx \frac{v_i}{r_{e7} + R_7}$$

$$v_o = -i_o \times (R_{o7} \parallel R_{o9}) \approx -\frac{v_i(R_{o7} \parallel R_{o9})}{r_{e7} + R_7}$$

$$\Rightarrow A\beta = -\frac{v_o}{v_i} \approx \frac{R_{o7} \parallel R_{o9}}{r_{e7} + R_7}$$

(b) From Example 12.6 of the Text, we have :  $R_{o7} = 23 \text{ M}\Omega$  and

$$R_{o9} = 12.9 \text{ M}\Omega \Rightarrow R_{o7} \parallel R_{o9} = 8.3 \text{ M}\Omega$$

$$r_{e7} = \frac{25 \text{ mV}}{10 \mu\text{A}} = 2.5 \text{ k}\Omega \text{ and } R_7 = 20 \text{ k}\Omega$$

$$\text{Thus, } A\beta = \frac{R_{o7} \parallel R_{o9}}{r_{e7} + R_7} = \frac{8.3 \text{ M}\Omega}{2.5 \text{ k}\Omega + 20 \text{ k}\Omega}$$

$$= 368.9 \Rightarrow A\beta \approx 368.9$$

(c) With the CMF present, we have

$$\Delta V_{CM} = \frac{\Delta V_{CM} \text{ when CMF is absent}}{1 + A\beta}$$

$$\Rightarrow \Delta V_{CM} = \frac{2.5 \text{ V}}{1 + 368.9} = 6.76 \text{ mV}$$

Note that the corresponding value for  $\Delta V_{CM}$  found by a different approach in Example 12.6 is 6.75mV which is only 0.1% off from the calculated value in this problem.

### 10 . 62

$$I_Q = 0.4 \text{ mA} \quad I_{LMax} = 10 \text{ mA}$$

a) The output voltage  $v_o$  can swing as low as 0.1V when  $Q_P$  is in active, and  $Q_N$  supplies the load current :  $v_{min} = 0.1 \text{ V}$

$v_o$  can go up as high as  $V_{CC} - 0.1 \text{ V}$  when  $Q_N$  is inactive and  $Q_P$  supplies the load current :

$$0.1 \text{ V} \leq v_o \leq V_{CC} - 0.1 \text{ V}$$

$$\text{b) } i_L = 0 \quad R_o = R_{oN} \parallel R_{op}$$

$$i_L = 0 \Rightarrow i_p = i_N = I_Q = 0.4 \text{ mA}$$

$$r_{oN} = \frac{V_{AN}}{I_N} = \frac{30}{0.4} = 75 \text{ k}\Omega$$

$$r_{op} = \frac{V_{AP}}{I_P} = \frac{20}{0.4} = 50 \text{ k}\Omega$$

$$R_O = 30 \text{ k}\Omega$$

$$\text{c) } R_{op} = \frac{R_o}{1 + A\beta} = \frac{30 \text{ k}\Omega}{1 + 10^3 \times 1} = 0.3 \Omega$$

d)  $i_L = 10 \text{ mA}$  Since  $i_L$  is at its max, then  $Q_N$  is

inactive mode. Hence:  $i_N = \frac{I_Q}{2} = 0.2 \text{ mA}$  and

since we have:  $i_p = i_N + i_L \Rightarrow i_p = 10.2 \text{ mA}$

e)  $i_L = -10 \text{ mA}$  then  $Q_P$  is inactive and

$$i_p = 0.2 \text{ mA}$$

$$\text{For } Q_N, i_p - i_L i_N = 0.2 - (-10) = 102 \text{ mA}$$

### 10 . 63

$$v_{B7} = v_{BEN} = V_T \ln \frac{i_N}{I_{SN}}$$

$$v_{B6} = R_S i_4 + v_{BES} = R_S i_4 + V_T \ln \frac{i_4}{I_{SS}} \text{ Note that}$$

$$i_4 = i_5$$

If we substitute for  $i_4 = \frac{v_{BEP} - v_{BE4}}{R_4}$ , then :

$$v_{B6} = \frac{R_S}{R_4} (v_{BEP} - v_{BE4}) + V_T \ln \frac{i_4}{I_{SS}} \text{ Note that}$$

$$R_S = R_4$$

$$v_{B6} = V_T \ln \frac{i_p}{I_{SP}} - V_T \ln \frac{i_4}{I_{SS}} + V_T \ln \frac{i_4}{I_{SS}}$$

$$V_T \ln \frac{i_p}{I_{SP}} \times \frac{i_{s4}}{i_4} \times \frac{i_4}{I_{SS}}$$

Now substitute for  $I_{SS} = I_{S4} \frac{I_{SN}}{I_{SP}}$ , then we have:

$$v_{B6} = V_T \ln \frac{i_p}{I_{SP}} \frac{I_{S4}}{I_{S4}} \frac{I_{SP}}{I_{SN}} = V_T \ln \frac{i_p}{I_{SN}}$$

Now if we consider  $V_E$  and write :

$$v_E = v_{B6} + v_{BE6} = v_{B7} + v_{BE7}$$

$$\Rightarrow V_T \ln \frac{i_p}{I_{SN}} + v_T \ln \frac{i_6}{I_{S6}} = V_T \ln \frac{i_N}{I_{SN}} + V_T \ln \frac{i_7}{I_{S7}}$$

$$\Rightarrow \frac{i_p}{I_{SN}} \times \frac{i_6}{I_{S6}} = \frac{i_N}{I_{SN}} \times \frac{i_7}{I_{S7}}$$

$$\Rightarrow i_7 = \frac{I_{S7}}{I_{S6}} \cdot i_6 \text{ Note that } I_{S7} = I_{S6}, \text{ hence}$$

$$i_7 = \frac{i_p}{i_N} i_6$$

We can write :  $i_6 + i_7 = I$ . hence :

$$i_6 + \frac{i_p}{i_N} i_6 = I \Rightarrow i_6 = \frac{I i_N}{i_p + i_N}$$

$$i_7 = \frac{i_p}{i_N} \times I \frac{i_N}{i_N + i_p} \Rightarrow i_7 = I \frac{i_p}{i_p + i_N}$$

#### 10.64

$$\text{For } Q_7 \text{ we can write : } v_{B7} = v_{BEN} = V_T \ln \frac{i_N}{I_{SN}}$$

At node E, we have :

$$\begin{aligned} v_E &= v_{EB7} + v_{B7} = V_T \ln \frac{i_7}{I_{S7}} + V_T \ln \frac{i_N}{I_{SN}} \\ &= V_T \ln \frac{i_7}{I_{S7} I_{SN}} \end{aligned}$$

$$i_{CT} = I \frac{i_p}{i_p + i_N}$$

$$\therefore v_E = V_T \ln \left[ \frac{i_p i_N}{i_N + i_p I_{SN} I_{S7}} \right]$$

#### 10.65

$$I_Q = 0.36 \text{ mA}, I = 10 \mu\text{A}, I_{SN} = 8I_{S10},$$

$$I_{S7} = 4I_{S11}$$

From Eq. 12.138, we have :

$$I_Q = 2 \left( \frac{I_{REF}^2}{I} \right) \frac{I_{SN} I_{S7}}{I_{S10} I_{S11}} \Rightarrow 0.36 \times 10^{-3}$$

$$= 2 \left( \frac{I_{REF}^2}{10 \times 10^{-6}} \times 8 \times 4 \right)$$

$$I_{REF}^2 = \frac{0.36 \times 10^{-8}}{64} \Rightarrow I_{REF} = 7.5 \mu\text{A}$$

The minimum current in the inactive output transistors,  $Q_N$  and  $Q_P$  is  $\frac{1}{2} I_Q$  or 0.18 mA.

### 11.1

$$T(s) = \frac{1}{(s+1)(s^2+s+1)} = \frac{1}{s^3+2s^2+2s+1}$$

$$T(j\omega) = [j(2\omega - \omega^3) + (1 - 2\omega^2)]$$

$$|T(j\omega)| = [(2\omega - \omega^3)^2 + (1 - 2\omega^2)^2]^{-1}$$

$$= [4\omega^2 - 4\omega^4 + \omega^6 + 1 - 4\omega^2 + 4\omega^4]^{-\frac{1}{2}}$$

$$= [1 + \omega^6]^{-\frac{1}{2}}$$

$$= \frac{1}{\sqrt{1 + \omega^6}}$$

For phase Angle:

$$\phi(\omega) = \tan^{-1} \left[ \frac{\text{Im}[T(j\omega)]}{\text{Re}[T(j\omega)]} \right]$$

$$= -\tan^{-1} \left[ \frac{2\omega - \omega^3}{1 - 2\omega^2} \right]$$

For  $\omega = 0.1$ :

$$|T(j\omega)| = (1 + 0.1^6)^{-1/2} \approx 1$$

$$\phi(\omega) = -11.5^\circ = -0.20 \text{ rad}$$

For  $\omega = 1 \text{ rad/s}$ :

$$|T(j\omega)| = (1 + 1^6)^{-1/2} = 1/\sqrt{2} = 0.707$$

$$\phi = -\tan^{-1} \left( \frac{1}{-1} \right) = -135^\circ = 2.356 \text{ rad}$$

Note:  $G = -3 \text{ dB}$

Also:  $\tan^{-1}(-1) = -45^\circ \text{ or } -135^\circ$

$$\tan^{-1} \left( \frac{-1}{1} \right) = -45^\circ$$

$$\tan^{-1} \left( \frac{1}{-1} \right) = -135^\circ$$

For  $\omega = 10 \text{ rad/s}$ :

$$|T(j\omega)| = (1 + 10^6)^{-1/2} = 0.001$$

$$\phi = -\tan^{-1} \left[ \frac{2(10) - 10^3}{1 - 2(10^7)} \right]$$

$$= -\tan^{-1} \left[ \frac{-980}{-199} \right]$$

$$= - \left[ 180^\circ + \tan^{-1} \left( \frac{980}{199} \right) \right]$$

$$= -258.5^\circ$$

$$= 4.512 \text{ rad}$$


Now consider an input of  $A \sin \omega t$  to  $T(s)$ . The output is then given by:

$$A|T(j\omega)| \sin(\omega t + \phi(\omega))$$


Using this result, the output to each of the following inputs will be:

INPUT	OUTPUT
$2\sin(0.1t)$	$2\sin(0.1t - 0.2) \text{ ie } 2 \times 1 = 2$
$2\sin(1t)$	$\sqrt{2}\sin(t - 2.356) \text{ i.e. } 2 \times 1/\sqrt{2} = \sqrt{2}$
$2\sin(10t)$	$2 \times 10^{-3} \sin(10t - 4.512)$

### 11.2

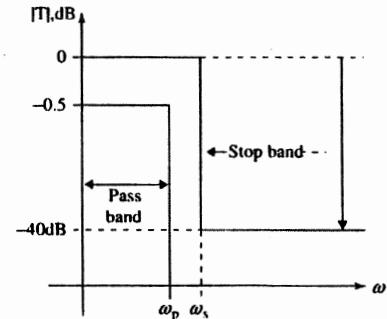

11.3

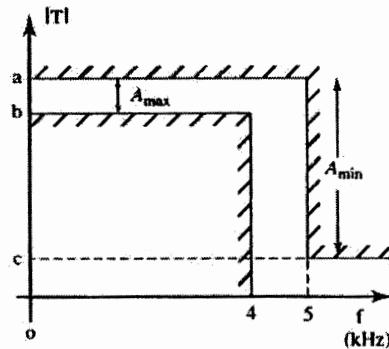

Note  $|T|$  is shown in a linear scale but  $A_{\max}$  and  $A_{\min}$  are in dB

From the problem


$$\frac{a}{b} = 1.1, C = 0.1\% a \text{ or } \frac{C}{a} = 0.001$$

$$\begin{aligned} A_{\max} &= 20 \log_{10} a - 20 \log_{10} b \\ &= 20 \log_{10} a / b \\ &= 20 \log_{10}(1.1) \\ &= 0.83 \text{ dB} \end{aligned}$$

$$\begin{aligned} A_{\min} &= 20 \log_{10} a - 20 \log_{10} c \\ &= 20 \log_{10} \left( \frac{a}{c} \right) \\ &= 20 \log_{10}(0.001) \\ &= -60 \text{ dB} \end{aligned}$$

$$\text{Selectivity} = \frac{\omega_s}{\omega_p} = \frac{2\pi S}{2\pi P} = 1.25$$

11.4

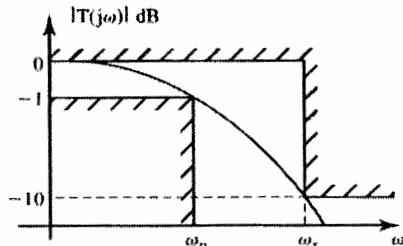

$$T(s) = \frac{k}{1 + s\tau} \text{ If } \tau = 1 \text{ s and DC gain} = 1$$

$$= \frac{1}{1 + 1s}$$

then  $k = 1$

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \omega^2}}$$

At the passband edge:

$$|T(j\omega_p)| = \frac{1}{\sqrt{1 + \omega_p^2}} = 10^{-1/20}$$

$$\therefore \omega_p = 0.5088 \text{ rad/s}$$

At the stopband edge:

$$|T(j\omega_s)| = \frac{1}{\sqrt{1 + \omega_s^2}} = 10^{-10/20}$$

$$\therefore \omega_s = 3 \text{ rad/s}$$

$$\text{Selectivity} = \frac{\omega_s}{\omega_p} = \frac{3}{0.5088} = 5.9$$


11.5

Passband is defined by:  $f \geq 2 \text{ kHz}$

$$\Rightarrow \omega_p = 2\pi(2000) \text{ rad/s}$$

Stopband is defined by:  $f \leq 1 \text{ kHz}$
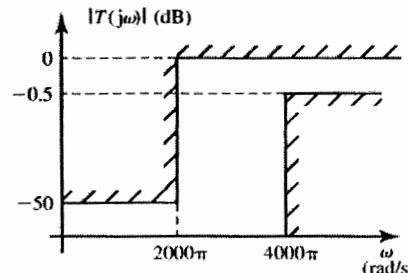
$$\Rightarrow \omega_s = 2\pi(1000) \text{ rad/s}$$




Note we assumed a maximum transmission of 0 dB.

11.6

Passband:  $f \in \{[0, 10 \text{ kHz}] \cup [20 \text{ kHz}, \infty]\}$

Stopband:  $f \in [12 \text{ kHz}, 16 \text{ kHz}]$
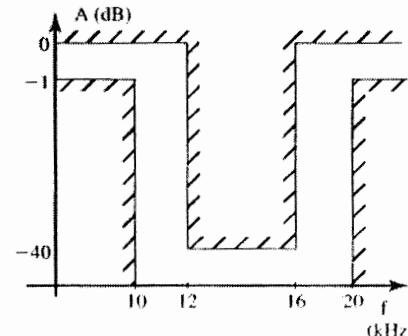
$$A_{\max} = 1 \text{ dB}, A_{\min} = -40 \text{ dB}$$



## 11.7

Poles at  $-1$  and  $-0.5 \pm j0.8$  gives a denominator:

$$\begin{aligned} D(s) &= (s+1)(s+0.5-j0.8)(s+0.5+j0.8) \\ &= (s+1)(s^2 + 2(0.5)s + 0.5^2 + 0.8^2) \\ &= (s+1)(s^2 + s + 0.89) \end{aligned}$$

Zeros at  $\infty$  and  $\pm jz$  give a numerator:

$$N(s) = k(s+jz)(s-jz) = k(s^2 + 4)$$

Note there is one zero at  $\infty$  because Degree

$$(D(s)) - \text{Degree}(N(s)) = 1$$

$$T(s) = \frac{k(s^2 + 4)}{(s+1)(s^2 + s + 0.89)}$$

$$|T(j\omega)| = \frac{k(4)}{0.89} = 1 \quad \therefore \text{DC gain} = 1$$

$$\Rightarrow k = 0.225$$


$$\therefore T(s) = \frac{0.2225(s^2 + 4)}{(s+1)(s^2 + s + 0.89)}$$

$$G_{m1} = 1 \text{ mA/V}, G_{m2} = 2 \text{ mA/V},$$

$$R = 500 \Omega$$

$$f_t = \frac{G_{m1}}{2\pi C_C} \Rightarrow C_C = \frac{G_{m1}}{2\pi f_t}$$

11.8

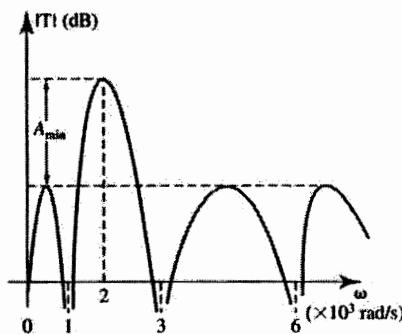

Numerator is given by

$$\begin{aligned} a_1 &= (s - \omega_p)(s^2 + (10^3)^2)(s^2 + (3 \times 10^3)^2) \\ &= (s^2 + (6 \times 10^3)^2) \\ &= a_7 s(s^2 + 10^6)(s^2 + 9 \times 10^6)(s^2 + 36 \times 10^6) \end{aligned}$$

Degree of Numerator  $\Delta m = 7$

Degree of Denominator  $\Delta N$

Given that there is one zero at  $\infty$ :

$$N - M = 1 \Rightarrow N = 8$$

$$\therefore T(s) = \frac{a_7 s(s^2 + 10^6)(s^2 + 9 \times 10^6)(s^2 + 36 \times 10^6)}{s^8 + b_2 s^7 + b_6 s^6 + \dots + b_0}$$

From circuit: current drawn from  $V_{DD}$  rail = 2 mA

= current return to  $V_{SS}$  rail


$$\therefore \text{Power} = (V_{DD} + V_{SS}) \times 2 I_B \Rightarrow$$

$$1 \text{ mW} = (1.65 + 1.65) \times 2 I_B$$

$$\therefore I_B = \frac{1 \text{ mW}}{4 \times 1.65 \text{ V}} = 151.5 \mu\text{A}$$

$$\Rightarrow I = I_B / 1.2 = 126.3 \mu\text{A}$$

11.9

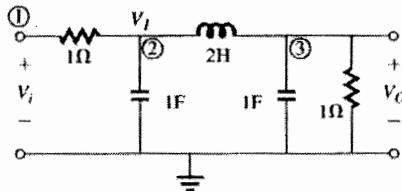

The easiest way to solve the circuit is to use nodal analysis at nodes (1), (2), (3)

At node (3)  $\sum I = 0$

$$\frac{V_o}{1} + \frac{V_o}{1/s} + \frac{V_o - V_i}{2s} = 0$$

$$\therefore V_i = V_o(2s^2 + 2s + 1) \quad \text{Eq. (a)}$$

At node (2)  $\sum I = 0$

$$\frac{V_i - V_i}{1} + \frac{V_i}{1/s} + \frac{V_i - V_o}{2s} = 0$$

$$\therefore V_i(2s^2 + 2s + 1) = V_o + 2sV_i \quad \text{Eq. (b)}$$

(a)  $\rightarrow$  (b)

$$V_o(2s^2 + 2s + 1)^2 = V_o + 2sV_i$$

$$V_o(4s^4 + s^3(4+4) + s^2(2+4+2) + s(2+2)+1) = V_o + 2sV_i$$

$$= V_o + 2sV_i$$

$$\frac{V_o(s)}{V_i(s)} \triangleq T(s) = \frac{2s}{4s^4 + 8s^3 + 8s^2 + 4s}$$

$$T(s) = \frac{0.5}{s^3 + 2s^2 + 2s + 1}$$

Poles are given by:

$$s^3 + 2s^2 + 2s + 1 = 0$$

$$(s+1)(s^2 + s + 1) = 0$$

$\therefore$  Poles are  $s = -1$  and  $s = -\frac{1}{2} \pm j\sqrt{3}/2$

11.10

$$A_{\min} = 1 \text{ dB}, A_{\max} = 20 \text{ dB}, \omega/\omega_p = 1.3$$

$$\text{Using: } A(\omega_s) = 10 \log \left[ 1 + t^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$$

$$= A_{\min}$$

$$t = [10^{1/10} - 1]^{1/2} = 0.5088$$

$$A_{\min} = 10 \log \left[ 1 + t^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$$

$$10^{A_{\min}/10} - 1 = t^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N}$$

$$\log(10^{A_{\min}/10} - 1) = \log \left( t^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right)$$

$$N = \frac{\log \{ (10^{A_{\min}/10} - 1) / t^2 \}}{2 \log (\omega_s / \omega_p)}$$

$$= 11.3 \Rightarrow \text{choose } N = 12$$

The actual value of stopband attenuation can be calculated using the integer value of  $N$ :

$$A(\omega_s) = 10 \log \left[ 1 + t^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]; N = 12$$

$$= 27.35 \text{ dB actual attenuation}$$

If the stopband specs are to be met exactly we need to find  $A_{\max}$ .

$$t^2 = \frac{10^{A_{\max}/10} - 1}{(\omega_s / \omega_p)^{2N}}$$

$$A_{\max} = 20$$


$$N = 12$$

$$= 0.1824$$

$$\therefore A_{\max} = 10 \log(1 + t^2)$$

$$= 0.73 \text{ dB}$$

11.11

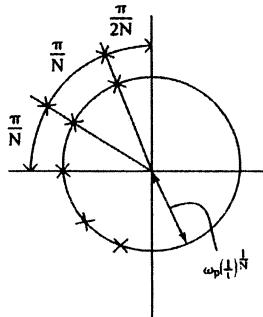

$$\omega_p = 10^3 \text{ rad/s} \quad N = 5$$

$$A_{\max} = 1 \text{ dB} \Rightarrow t = 0.5088$$

find solution graphically

$$\begin{aligned} P_1 &= \omega_o \left( \frac{1}{t} \right)^{1/5} \times \left( \frac{\pi}{2} + \frac{\pi}{2N} \right) \\ &= 873.59 \times \left( \frac{6\pi}{10} \right) \\ &= 873.59 \left[ \cos\left(\frac{6\pi}{10}\right) \pm j \sin\left(\frac{6\pi}{10}\right) \right] \\ &= -269.96 \pm j830.84 \\ P_2 &= 873.59 \times \left[ \frac{\pi}{2} + \frac{\pi}{2N} + \frac{\pi}{N} \right] \\ &= -706.75 \pm j513.49 \\ P_3 &= 873.59 \times \pi = -873.59 \end{aligned}$$

11.12

$$f_p = 10 \text{ kHz} \quad \omega_p = 1.5 \quad A_{\min} = 15 \text{ dB}$$

$$f_s = 15 \text{ kHz} \quad \omega_p = 1.5 \quad A_{\max} = 2 \text{ dB}$$

$$t^2 = 10^{A_{\max}/10} - 1 \Rightarrow t = 0.76478$$

Manipulation Eq (16.15) we get:


$$N \doteq \frac{\log\left(\left(10^{A_{\min}/10} - 1\right)/t^2\right)}{2\log(\omega_s/\omega_p)} = 4.88$$

∴ use  $N = 5$

finding natural modes graphically:-

$$\text{radius} = \omega_p \left( \frac{1}{t} \right)^{1/5} \Delta\omega_o$$

$$\omega_o = 6.629 \times 10^4$$

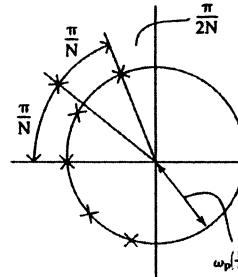

$$P_1 = \omega_o \times \left( \frac{\pi}{2} + \frac{\pi}{2N} \right) = \omega_o \times \left( \frac{6\pi}{10} \right)$$

$$= \omega_o \left( \cos\left(\frac{6\pi}{10}\right) \pm j \sin\left(\frac{6\pi}{10}\right) \right)$$

$$= \omega_o (-0.309 \pm j0.951)$$

$$P_2 = \omega_o \left( \cos\left(\frac{8\pi}{10}\right) \pm j \sin\left(\frac{8\pi}{10}\right) \right)$$

$$= \omega_o (-0.809 \pm j0.588)$$

$$P_3 = \omega_o (\cos\pi \pm j \sin\pi) = -\omega_o$$

Given a natural mode  $= \alpha \pm j\beta$ , the following term results

$$(s + \alpha + j\beta)(s + \alpha - j\beta)$$

$$= s^2 + 2\alpha s + \alpha^2 + \beta^2$$

$$= s^2 + 2Re[P]s + |P|^2$$

Also, note that for a Butterworth, all natural modes have a magnitude of  $\omega_o$ .

$$P_1 \text{ yields: } s^2 + 0.618\omega_o s + \omega_o^2$$

$$P_2 \text{ yields: } s^2 + 1.618\omega_o s + \omega_o^2$$

$$P_3 \text{ yields: } s + \omega_o$$

$$\therefore T(s) = \frac{k}{(s + \omega_o)(s^2 + 0.618\omega_o s + \omega_o^2)}$$

$$\times \frac{1}{s^2 + 1.618\omega_o s + \omega_o^2}$$

for unity dc gain

$$|T(j\omega)| = \frac{k}{\omega_o^5} = 1 \Rightarrow k = \omega_o^5$$

$$\therefore T(s) = \frac{\omega_o^5}{(s + \omega_o)(s^2 + 0.618\omega_o s + \omega_o^2)}$$

$$= \frac{1}{(s^2 + 1.618\omega_o s + \omega_o^2)}$$


for attenuation at 20 kHz

$$\frac{\omega_1}{\omega_p} = \frac{20}{10} = 2$$

$$A(\omega_s) = 10 \log \left[ 1 + i^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$$

$$= 27.8 \text{ dB}$$

### 11.1.3

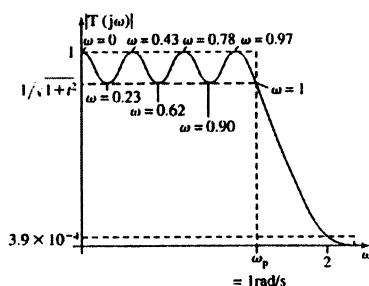

Given  $A_{\max} = 1 \text{ dB} \Rightarrow t = 0.5088$

$$|T(j\omega)| = \left[ 1 + t^2 \cos^2 \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \right]^{-1/2}$$

for  $\omega \leq \omega_p$

If  $|T(j\omega)| = 1$

$$1 = 1 + t^2 \cos^2 \left( N \cos^{-1} \left( \omega / \omega_p \right) \right)$$

$$\omega_p = 1$$

$$N \cos^{-1}(\omega / 1) = \cos^{-1}(0)$$

$$\cos^{-1}(\omega) = \frac{2i+1}{2N}\pi$$

$$\therefore \omega_i = \cos \left[ \frac{2i+1}{2N}\pi \right]$$

$\omega$  s repeat after this value  $i = 0, 1, \dots, \frac{N-1}{2}$

$$\omega_0 = 0.9749$$

$$\omega_1 = 0.7818$$

$$\omega_2 = 0.4339$$

$$\omega_3 = 0$$

$\omega$  values at which  $|T| = 1$

note  $\omega_4 = -0.4339$

$$= -\omega_2$$

If  $|T| = 1 / \sqrt{1 + t^2}$ , then

$$1 / \sqrt{1 + t^2} = \left[ 1 + t^2 \cos^2 \left( N \cos^{-1} \left( \omega / \omega_p \right) \right) \right]^{-1/2}$$

$$1 = \cos \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right)$$

$$N \cos^{-1}(\omega) = \cos^{-1}(0)$$

$$= i\pi \quad i = 0, 1, 2, \dots$$

$$\omega_i = \cos \left[ \frac{i\pi}{N} \right] \quad i = 0, 1, 2, \dots \frac{N}{2}$$

$$\omega_0 = 1.0$$

$$\omega_1 = 0.9010$$

$$\omega_2 = 0.6235$$

$$\omega_3 = 0.2252$$

$\omega$  values at which

$$|T| = (1 + t^2)^{-1/2}$$

$$\text{Note } \omega_4 = 0.2252$$

$$= -\omega_3$$

To find  $|T(jz)|$

since  $\omega > \omega_p$

$$|T(j\omega)| = \left[ 1 + t^2 \cosh^2 \left( N \cosh^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \right]^{-1/2}$$

$$= [1 + 0.5088^2 \cosh^2(7 \cosh^{-1} 2)]^{-1/2}$$

$$= 3.898 \times 10^{-4} \text{ V/V}$$

$$|T|_{ob} = -68.2 \text{ dB}$$

For roll-off consider

$$T(s) = \frac{k}{s^2 + b_6 s^6 + \dots b_0}$$

$$\text{for } \omega \gg \omega_p \quad |T(j\omega)| \approx \frac{k}{\omega^2}$$

$$\therefore \text{Roll-off is } \frac{1}{2^7} \text{ or } 20 \log \left( \frac{1}{2^7} \right)$$

per octave = -42 dB/octave.

### 11.1.4

$$\omega_s / \omega_p = 2$$


$$A_{\max} = 1 \text{ dB} \Rightarrow t = \sqrt{10^{\frac{A_{\max}}{10}} - 1} = 0.5088$$

$$|T_B| = [1 + t^2 (\omega_s / \omega_p)^{2N}]^{-1/2}$$

$$|T_C| = \left[ 1 + t^2 \cosh^2 \left( N \cosh^{-1} \left[ \frac{\omega_s}{\omega_p} \right] \right) \right]^{-1/2}$$

$$|T_B| = 6.13 \times 10^{-2} \Rightarrow -24.3 \text{ dB}$$

$$|T_C| = 5.43 \times 10^{-3} \Rightarrow -45.3 \text{ dB}$$

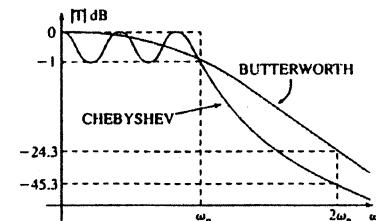

### 11.15

(a)  $f_p = 3.4$  kHz

$$A_{\max} = 1 \text{ dB} \Rightarrow t = 0.5088$$

$$f_s = 4 \text{ kHz } A_{\min} = 35 \text{ dB}$$

$$\omega_s / \omega_p = 1.176$$

Using Eq (16.22):

$$A(\omega s) = 10 \log \left[ 1 + t^2 \operatorname{Cosh}^2 \left( N \operatorname{Cosh}^{-1} \left( \frac{\omega_s}{\omega_p} \right) \right) \right]$$

& trying different values for  $N$

$$N \quad A(\omega_s)$$

$$8 \quad 28.8 \text{ dB}$$

$$9 \quad 33.9 \text{ dB}$$

$$10 \quad 38.98 \text{ dB}$$

$\therefore$  Use  $N = 10$

$$\text{Excess attenuation} = 39 - 35 = 4 \text{ dB}$$

(b) Poles are given by:

$$P_k = -\omega_p \operatorname{Sin} \left( \frac{2k-1}{N} \cdot \frac{\pi}{2} \right) \operatorname{Sinh} \left( \frac{1}{N} \operatorname{Sinh}^{-1} \left( \frac{1}{t} \right) \right)$$

$$+ j \omega_p \operatorname{Cos} \left( \frac{2k-1}{N} \cdot \frac{\pi}{2} \right) \operatorname{Cosh} \left( \frac{1}{N} \operatorname{Sinh}^{-1} \left( \frac{1}{t} \right) \right)$$

for  $k = 1, 2, \dots, N$ .

Since  $t = 0.5088$  and  $N = 10$

$$\operatorname{Sinh}(1/N \operatorname{Sinh}^{-1}(1/t)) = 0.1433$$

$$\operatorname{Cosh}(1/N \operatorname{Sinh}^{-1}(1/t)) = 1.010$$

$$\therefore P_1 = \omega_p \left[ -0.1433 \operatorname{Sin} \left( \frac{\pi}{20} \right) + j 1.010 \operatorname{Cos} \left( \frac{\pi}{20} \right) \right]$$

$$= \omega_p (-0.0224 + j0.9978)$$

$$P_2 = \omega_p (-0.0650 + j0.900)$$

$$P_3 = \omega_p (-0.1013 + j0.7143)$$

$$P_4 = \omega_p (-0.1277 + j0.4586)$$

$$P_5 = \omega_p (-0.1415 + j0.1580)$$

Now it should be realized that the remaining poles are complex conjugates of the above.

pole-pair  $P_1$  &  $P_1^*$  give a factor:

$$S^2 + 2(0.0224)\omega_p S + \omega_p^2 (0.0224^2 + 0.9978^2)$$

$$= S^2 + 0.0448\omega_p S + 1.023\omega_p^2$$

i.e. this factor is from  $(S - P_1)(S - P_1^*)$

$$P_2 \text{ yields: } S^2 + 0.130\omega_p S + 0.902\omega_p^2$$

$$P_3 \text{ yields: } S^2 + 0.203\omega_p S + 0.721\omega_p^2$$

$$P_4 \text{ yields: } S^2 + 0.255\omega_p S + 0.476\omega_p^2$$

$$P_5 \text{ yields: } S^2 + 0.283\omega_p S + 0.212\omega_p^2$$

Now  $T(S)$  is given by

$$T(S) = \frac{k\omega_p^{10}}{E^2 (S - P_1)(S - P_1^*)(S - P_2)(S - P_3)(S - P_4)(S - P_5)}$$


where the second order terms of the denominator are given above.

$k$  is the dc gain

$\therefore$  we want the dc gain to be

$$k = \frac{1}{1+t^2} = 0.8913$$


$$\omega_p = 2\pi \times 3400$$

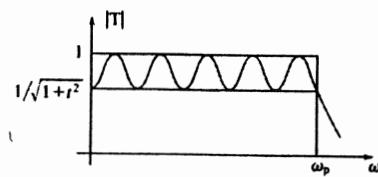

### 11.16

$$f_o = 100 \text{ kHz } R_i(\infty) = 100 \text{ k}\Omega$$

$$|T(\infty)| = 1$$

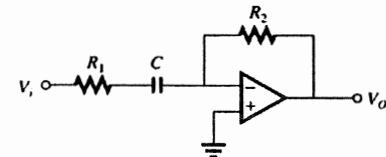

$$R_i(\infty) = R_1 = 100 \text{ k}\Omega$$

$$|T(\infty)| = R_2/R_1 = 1$$


$$R_2 = R_1 = 100 \text{ k}\Omega$$

$$CR_1 = 1/W_o$$

$$C = \frac{1}{W_o R_1} = \frac{1}{2\pi 100 \times 10^3 \times 100 \times 10^3} \\ = 15.9 \text{ nF}$$

### 11.17

Use general first-order circuit:

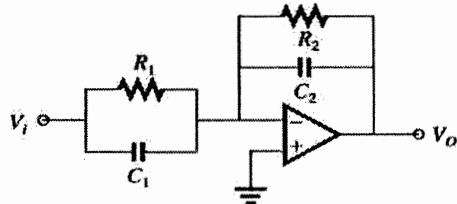

-Zero at 1 kHz; Pole at 100 kHz

$$-|T(\omega)| = 1; R_i(\omega) = 1 \text{ k}\Omega$$

$$\text{Thus: } R_i(\text{DC}) = R_1 = 1 \text{ k}\Omega$$

$$T(\text{DC}) = -R_2/R_1 = -1$$

$$R_2 = R_1 = 1 \text{ k}\Omega$$

For a pole at 100 kHz

$$C_2 R_2 = \frac{1}{W_o} \Rightarrow C_2 = \frac{1}{2\pi f_o R_2} \\ = 1.59 \text{ nF}$$

$$\text{For the circuit } T(S) = \frac{a_1 S + a_0}{S + W_o}$$


$$\text{Thus the Zero at } -a_0/a_1 = -2\pi 10^3$$

$$C_1 R_1 = a_1/a_0$$

$$C_1 = \frac{1}{2\pi 10^3 R_1} \\ = 159 \text{ nF}$$

$$\text{High freq gain} = \frac{-C_1}{C_2} = -100$$

$$= 40 \text{ dB}$$

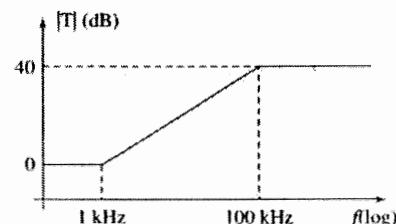

$$\text{gain} = 10^{12/20} = 3.98 \approx 4$$

want  $R_i = R_1$  large

$$\therefore R_1 = 100 \text{ k}\Omega$$

$$\text{Total gain} = A_{LP} A_{HP} = 4$$

$$A_{LP} = -R_2/R_1 \Rightarrow R_2 = -A_{LP} R_1 \text{ and}$$

$$R_2 \leq 100 \text{ k}\Omega$$

$$\therefore \text{make } A_{LP} = -1 A_{HP} = -4$$

$$R_2 = 100 \text{ k}\Omega$$

$$R_2 C_1 = \frac{1}{W_{o,LP}}$$


$$C_1 = \frac{1}{2\pi f_{o,LP} R_2} = \frac{1}{2\pi(10 \times 10^3)100 \times 10^3} \\ = 0.159 \text{ nF}$$

$$A_{HP} = \frac{-R_4/R_3 = -4}{R_4 = 4R_3} \left. \right\} \text{make } R_4 = 100 \text{ k}\Omega \\ R_3 = 25 \text{ k}\Omega$$

$$\text{Now } R_3 C_2 = 1/W_{o,HP}$$

$$C_2 = \frac{1}{2\pi f_{o,HP} R_3} \\ = \frac{1}{2\pi(100 \times 10^3)25 \times 10^3} \\ = 63.7 \text{ nF}$$

### 11.19

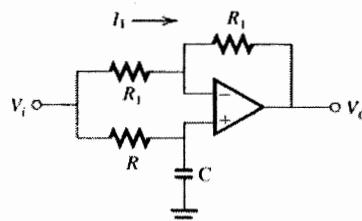

At +ve terminal

$$V_1 = \frac{1/SC}{1/SC + R_1} V_i$$

$$= \frac{1}{1 + S\tau} V_i \quad \tau = R_C$$

$V_- = V_+$  due to virtual short between terminals


$$\therefore I_1 = \left( V_i - \frac{1}{1 + S\tau} V_i \right) \frac{1}{R_1}$$

$$V_o = V_2 - I_1 R_1$$

$$= \frac{V_i}{1 + S\tau} - \left( V_i - \frac{V_i}{1 + S\tau} \right) \frac{R_1}{R_1}$$

$$\frac{V_o}{V_i} = \frac{1 - (1 + S\tau) + 1}{1 + S\tau} = \frac{1 - S\tau}{1 + S\tau}$$

### 11.18

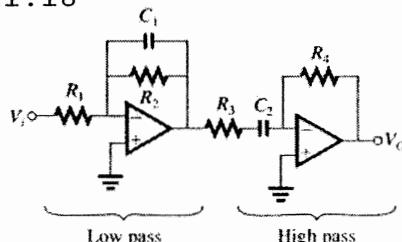


$$\begin{aligned}
 &= \frac{\omega_o - S}{\omega_o + S} \quad \omega_o = \frac{1}{\tau} \\
 &= -\frac{S - \omega_o}{S + \omega_o} = T(S) \\
 T(jW) &= \frac{j\omega - \omega_o}{j\omega + \omega_o} \\
 \phi(W) &= 180^\circ + \tan^{-1}\left(\frac{\omega}{-\omega_o}\right) - \tan^{-1}\left(\frac{\omega}{\omega_o}\right) \\
 &= 360^\circ - 2\tan^{-1}\left(\frac{\omega}{\omega_o}\right) \because \tan^{-1}\left(\frac{\omega}{\omega_o}\right) \\
 &= -2\tan^{-1}\left(\frac{\omega}{\omega_o}\right) = 180^\circ - \tan^{-1}\left(\frac{\omega}{\omega_o}\right)
 \end{aligned}$$

Now this equation can be rearranged:

$$\begin{aligned}
 \frac{W}{W_o} &= \tan(-\phi/2) \Leftrightarrow \omega_o = \frac{1}{2} = \frac{1}{R_C} \\
 R_C W &= \tan(-\phi/2) \\
 \therefore R &= \frac{\tan(-\phi/2)}{CW} = 10^4 \tan(-\phi/2) \\
 \phi &= -30^\circ, -60^\circ, -90^\circ, -120^\circ, -150^\circ \\
 R &= 2.68 \text{ k}\Omega, 5.77 \text{ k}\Omega, 10 \text{ k}\Omega, 17.32 \text{ k}\Omega, \\
 &\quad 37.32 \text{ k}\Omega
 \end{aligned}$$

### 11.20

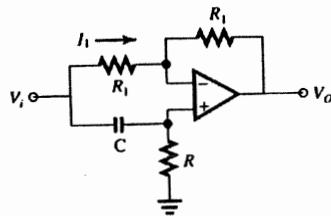

$$V+ = \frac{R}{R + 1/SC} V_i = \frac{S}{S + \omega_o} V_i$$

$$\text{Where } \omega_o = \frac{1}{R_C}$$

$$I_1 = \frac{V_i - (S/S + \omega_o)V_i}{R_1}$$

$$\begin{aligned}
 V_o &= \frac{S}{S + \omega_o} V_i - I_1 R_1 \\
 &= \frac{S}{S + \omega_o} V_i - V_i \left(1 - \frac{S}{S + \omega_o}\right)
 \end{aligned}$$

$$\frac{V_o}{V_i} = \frac{2S - S - \omega_o}{S + \omega_o} = \frac{S - \omega_o}{S + \omega_o}$$

Now:

$$\phi(W) = \tan^{-1}\left(\frac{\omega}{-\omega_o}\right) - \tan^{-1}\left(\frac{\omega}{\omega_o}\right)$$

$$\begin{aligned}
 \text{Note } \tan^{-1}\left(\frac{\omega}{-\omega_o}\right) &= 180^\circ - \tan^{-1}\left(\frac{\omega}{\omega_o}\right) \\
 &= 180 - \tan^{-1}\left(\frac{\omega}{\omega_o}\right) - \tan^{-1}\left(\frac{\omega}{\omega_o}\right) \\
 &= 180 - 2\tan^{-1}\left(\frac{\omega}{\omega_o}\right)
 \end{aligned}$$

Clearly  $\phi(O) = 180^\circ$  &  $\phi(\omega \rightarrow \infty) = 0^\circ$

### 11.21 Low pass $\omega_o = 10^3 \text{ rad/s}$

$$\begin{aligned}
 Q &= 1 \\
 \text{DC gain} &= 1
 \end{aligned}$$

$$T(S) = \frac{a_o}{S^2 + S\frac{\omega_o}{Q} + \omega_o^2}$$

$$T(O) = a_o \omega_o^2 = 1$$

$$a_o = W_o^2 = 10^6$$

$$\therefore T(S) = \frac{10^6}{S^2 + 10^3 S + 10^6}$$

$$\omega_{\max} = \omega_o \sqrt{1 - 1/2Q^2}$$

$$= \frac{\omega_o}{\sqrt{2}}$$

$$= 0.707 \text{ rad/s}$$

$$|T_{\max}| = \frac{|a_o|Q}{\omega_o^2 \sqrt{1 - \frac{1}{4Q^2}}} \Leftrightarrow a_o = \omega_o^2$$

$$= \frac{|\omega_o^2|}{\omega_o^2 \sqrt{3/4}}$$

$$= 2/\sqrt{3}$$

$$= 1.15 \text{ V/V}$$

$$= 1.21 \text{ dB}$$


### 11.22

$$W_p = 1 \text{ rad/s}$$

$$A_{\max} = 3 \text{ dB}$$

$$10^{-3/20} = 0.708 \approx \frac{1}{\sqrt{2}}$$

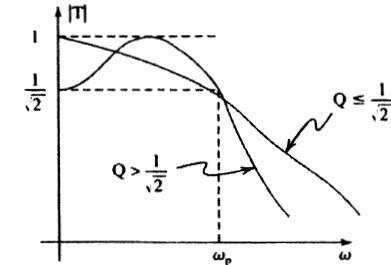There are many Q-values which may be used



$Q \leq 1/\sqrt{2}$  - no peaking

$Q > 1/\sqrt{2}$  - peaking

Solution 1  $Q \leq 1/\sqrt{2}$

For  $Q = 1/\sqrt{2}$  the response is maximally flat.

Because this is desirable, use:  $Q = \frac{1}{\sqrt{2}}$

$$T(S) = \frac{a_o}{S^2 + SW_o\sqrt{2} + W_o^2}$$

$$|T(O)| = \frac{a_o}{W_o^2} = 1$$

$$a_o = W_o^2$$

$$|T(j1)|^2 = \frac{W_o^2}{(W_o^2 - 1) + 2W_o^2} = \left(\frac{1}{\sqrt{2}}\right)^2$$

$$W_o = 1 \text{ rad/s}$$

$$\therefore T_1(S) = \frac{1}{S^2 + \sqrt{2}S + 1}$$

Solution 2  $Q > 1/\sqrt{2}$

From the figure:

$$|T(O)| = 1/\sqrt{2} = \frac{a_o}{W_o^2}$$

$$\therefore a_o = w_o^2/\sqrt{2}$$

$$\text{Now } |T|_{\max} = \frac{|a_o|}{W_o^2 \sqrt{1 - 1/4Q^2}} = 1$$

$$\frac{Q}{\sqrt{2}\sqrt{1 - 1/4Q^2}} = 1$$

$$Q = \sqrt{2}\sqrt{1 - 1/4Q^2}$$

$$\therefore Q^2 = 2\left(1 - \frac{1}{4Q^2}\right)$$

$$= 2 - \frac{1}{2Q^2}$$

$$Q^4 - 2Q^2 + \frac{1}{2} = 0$$

Solving for  $Q^2$  gives:

$$Q^2 = 1 \pm \sqrt{2}$$

ASIDE:

$$\therefore Q > 1/\sqrt{2}$$

$$Q^2 > 1/2$$

$$4Q^2 > 2$$

$$\frac{1}{4Q^2} < \frac{1}{2}$$

$$\therefore 1 - \frac{1}{4Q^2} > 1/2$$

$$\therefore \left|1 - \frac{1}{4Q^2}\right| = 1 - \frac{1}{4Q^2}$$

$$\Rightarrow Q = 0.5412 \text{ or } 1.3066$$

$$\therefore Q > \frac{1}{\sqrt{2}} \text{ use } Q = 1.3066$$

Now at the passband edge

$$|T(j1)| = 1/\sqrt{2}$$

$$|T(j1)|^2 = \frac{(W_o^2/\sqrt{2})^2}{(W_o^2 - 1)^2 + \frac{W_o^2}{Q^2}} = \frac{1}{2}$$

$$\frac{W_o^4}{2} = \frac{1}{2} \left[ W_o^4 - 2W_o^2 + 1 + \frac{W_o^2}{Q^2} \right]$$

$$W_o^2(2 - 1/Q^2) = 1$$

$$W_o = 0.841$$

$$\therefore T_2(S) = \frac{W_o^2/\sqrt{2}}{S^2 + W_o/QS + W_o^2} = \frac{0.5}{S^2 + 0.644S + 0.707}$$

$$\text{If } W_o = 2$$

$$|T_1(j2)| = 0.242 \quad |T_2(j2)| = 0.1414$$

$$\therefore A_{\min,1} = -12.3 \text{ dB} \quad A_{\min,2} = -17 \text{ dB}$$


### 11.23

$V_2$  lags  $V_1$  by  $120^\circ$

$V_3$  lags  $V_2$  by  $120^\circ$

$$w = 2\pi 60 \quad C = 1 \mu F$$
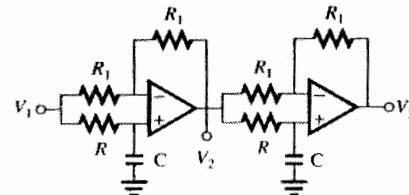
$$T(s) = \frac{s - w_o}{s + w_o} \quad w_o = \frac{1}{RC}$$



$$\phi(\omega) = 180^\circ + \tan^{-1}\left(\frac{\omega}{-\omega_o}\right) - \tan^{-1}\left(\frac{\omega}{\omega_o}\right)$$

$$\text{sub: } \tan\left(\frac{\omega}{-\omega_o}\right) = 180 - \tan^{-1}\left(\frac{\omega}{\omega_o}\right)$$

$$\Rightarrow \phi(\omega) = -2\tan(\omega/\omega_o)$$

Now  $\phi = -120^\circ$  at  $\omega = 2\pi 60$


$$-120^\circ = -2\tan(WRC)$$

$$-60^\circ = -\tan^{-1}(2\pi 60 \times R \times 10^{-6})$$

$$R = 4.59 \text{ k}\Omega$$

$R_1$  can be arbitrarily chosen use  $R_1 = 10 \text{ k}\Omega$

11.24

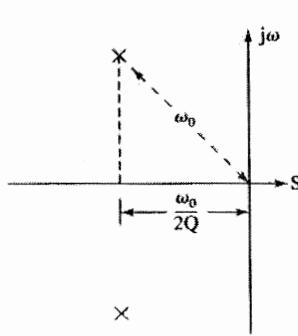

Natural Modes:

$$-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$$

$$\omega_o = \sqrt{\left(\frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} = 51.0$$

$$\frac{\omega_o}{2Q} = \frac{1}{2} \Rightarrow \frac{\omega_o}{Q} = 1$$

$$T(s) = \frac{a_2 s^2}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2} = \frac{a_2 s^2}{s^2 + s + 1}$$

$$|T(j\infty)| = a_2 = 1$$

$$\therefore T(s) = \frac{s^2}{s^2 + s + 1}$$

11.25

For a 2nd-order bandpass

$$T(S) = \frac{a_1 S}{S^2 + S \frac{\omega_o}{Q} + \omega_o^2}$$

$$T(j\omega) = \frac{j\omega a_1}{(\omega_o^2 - \omega^2) + \frac{j\omega \omega_o}{Q}}$$

$$|T(j\omega)| = \frac{aW}{\left[(\omega_o^2 - \omega^2)^2 + \frac{\omega^2 \omega_o^2}{Q^2}\right]^{1/2}}$$

Part (a):

$$|T(j\omega_1)| = |T(j\omega_2)|$$

$$= \frac{aW_1}{\sqrt{(\omega_o^2 - \omega_1^2)^2 + \left(\frac{\omega_1 \omega_o}{Q}\right)^2}}$$

$$= \frac{aW_2}{\sqrt{(\omega_o^2 - \omega_2^2)^2 + \left(\frac{\omega_2 \omega_o}{Q}\right)^2}}$$

$$= \omega_1^2 \left[ (\omega_o^2 - \omega_1^2)^2 + \left(\frac{\omega_1 \omega_o}{Q}\right)^2 \right]$$

$$= \omega_2^2 \left[ (\omega_o^2 - \omega_2^2)^2 + \left(\frac{\omega_2 \omega_o}{Q}\right)^2 \right]$$

$$\omega_1^2 (\omega_o^4 - 2\omega_o^2 \omega_1^2 + \omega_1^4) = \omega_2^2 (\omega_o^4 - 2\omega_o^2 \omega_2^2 + \omega_2^4)$$

$$\omega_1^2 \omega_o^4 + \omega_1^2 \omega_2^4 = \omega_2^2 \omega_o^4 + \omega_2^2 \omega_1^4$$

$$\omega_o^4 (\omega_1^2 - \omega_2^2) = \omega_2^2 \omega_1^4 - \omega_1^2 \omega_2^4$$

$$\omega_o^4 (\omega_1^2 - \omega_2^2) = \omega_2^2 \omega_1^2 (\omega_1^2 - \omega_2^2)$$

$$\omega_o^4 = \omega_1^2 \omega_2^2$$

$$\omega_o^2 = \omega_1 \omega_2 \quad \text{Q.E.D.}$$

(b) For Fig. 16.4:

$$\omega_{p1} = 8100 \text{ rad/s}$$

$$\omega_{p2} = 10000 \text{ rad/s}$$

$$A_{\max} = 1 \text{ dB}$$

$$\omega_o^2 = (8100)(10000)$$

$$\omega_o = 9000 \text{ rad/s}$$

$$|T(j\omega_{p1})| = |T(j\omega_{p2})| = 10^{-1/20} = 0.8913$$

$$|T(j\omega_o)| = \frac{\omega_o a_1}{\sqrt{(\omega_o^2 - \omega_o^2)^2 + \left(\frac{\omega_o^2}{Q}\right)^2}} = 1$$

$$\Rightarrow \frac{\omega_o a_1}{\omega_o^2/Q} = 1$$

$$\therefore \frac{Q a_1}{\omega_o} = 1 \Rightarrow a_1 = \frac{\omega_o}{Q}$$

$$|T(j\omega_{p1})|^2 = |T(j0.9\omega_o)|^2 = 0.8913^2$$

$$\frac{(\omega_o/Q)^2(0.9\omega_o)^2}{(\omega_0^2 - (0.9\omega_o)^2)^2 + \left(\frac{0.9\omega_o}{Q}\right)^2} = 0.8913^2$$

$$\left(\frac{\omega_o}{Q}(0.9\omega_o)\right)^2 = 0.8913^2 \left[ (\omega_0^2 - (0.9\omega_o)^2)^2 + \left(\frac{0.9\omega_o}{Q}\right)^2 \right]$$

$$\frac{0.81\omega_0^4}{Q^2} = 0.8913^2 \left[ W_0^4(1 - 0.81)^2 + \frac{0.81\omega_0^4}{Q^2} \right]$$

$$\frac{0.81\omega_0^4}{Q^2}(1 - 0.8913^2) = 0.8913^2 \omega_0^4 \times (1 - 0.81)^2$$

SUB  $\omega_o = 9000$  gives  
 $Q = 2.41$

$$\text{Now } Q_1 = \frac{\omega_o}{Q} = 0.415\omega_o$$

$$\therefore T(S) = \frac{0.415\omega_o S}{S^2 + 0.415\omega_o S + \omega_0^2}$$

IF  $WS_1 = 3000 \text{ rad/s}$

$$|T(j3000)| = \frac{0.415\omega_o(3000)}{\sqrt{(W_0^2 - 3000^2)^2 + (\omega_o 3000 \times .415)^2}} = 0.1537$$

$$\therefore A_{\min} = -20\log(0.1537) = 16.3 \text{ dB}$$

Now  $\omega_{s1}$  and  $\omega_{s2}$  are geometrically symmetrical

about  $\omega_o$ :

$$\omega_{s1}\omega_{s2} = \omega_0^2$$

$$\omega_{s2} = \frac{9000^2}{3000}$$

$$= 27000 \text{ rad/s}$$

## 11.26

$$Q = \frac{\omega_o}{BW\sqrt{10^{A/10} - 1}}$$

$$\omega_o = 2\pi(60) \quad BW = 2\pi 6 \quad A = 20 \text{ dB} \\ = 1.005$$

$$T(S) = a_2 \frac{S^2 + \omega_0^2}{S^2 + S \frac{\omega_o}{Q} + \omega_0^2}$$

$$|T(0)| = \frac{a_2 \omega_0^2}{\omega_0^2} = 1 \leftarrow \text{DC Gain}$$

$$Q_2 = 1$$

$$T(S) = \frac{S^2 + (2\pi 60)^2}{S^2 + S \frac{2\pi 60}{1.005} + (2\pi 60)^2}$$

$$T(S) = \frac{S + 1.421 \times 10^5}{S^2 + 375.1s + 1.421 \times 10^5}$$

## 11.27


FOR ALL PASS:

$$T(S) = Q_2 \frac{S^2 - SW_o/Q + \omega_0^2}{S^2 + SW_o/Q + \omega_0^2}$$

If Zero frequency < pole frequency


$$T(S) = Q_2 \frac{S^2 - SW_n/Q + \omega_n^2}{S^2 + SW_o/Q + \omega_0^2} \quad \omega_n < \omega_o$$

$$\text{At DC: } |T| = a \frac{\omega_n^2}{\omega_0^2} \text{ where } \frac{\omega_n^2}{\omega_0^2} < 1$$

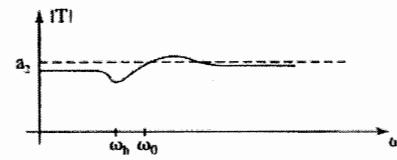

If Zero frequency > pole frequency  
 then  $\omega_n > \omega_o$

$$\text{At DC: } |T| = Q_2 \frac{\omega_n^2}{\omega_0^2} \text{ where } \frac{\omega_n^2}{\omega_0^2} > 1$$

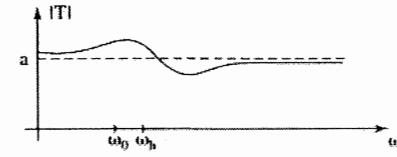

## 11.28

$$T(S) = \frac{S^2 - SW_o/Q^1 + \omega_0^2}{S^2 + SW_o/Q_o + \omega_0^2} a$$


Zero  $Q < \text{pole } Q \Rightarrow Q^1 < Q_o$

At  $W = W_o$ :

$$|T| = \frac{a_2 \omega_0^2 / Q'}{\omega_0^2 / Q_o} = \frac{a_2 Q_o}{Q'} > a_2$$

If  $Q^1 > Q_o$

$$|T(j\omega_o)| = \frac{Q_2 Q_o}{Q_1} < Q_2$$

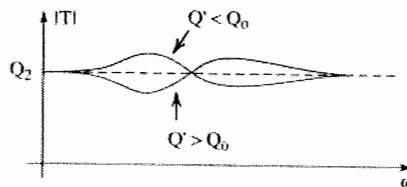

11.29

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{If } L' = 1.01L$$

$$\omega'_0 = (1.01LC)^{-1/2}$$

$$= 0.9950 \frac{1}{\sqrt{LC}}$$

$$= 0.9950 \omega_0$$

$$\therefore \Delta \omega_0 = -0.5\%$$


$$\text{If } C' = 1.01C$$

$$\omega'_0 = 0.9950 \omega_0$$

$$\Delta \omega_0 = -0.5\%$$

Changing R has no effect on  $\omega_0$

11.30

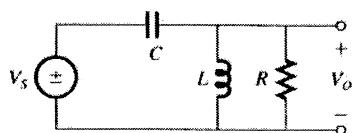

Use voltage divider rule:

$$V_o = \frac{Z_{R \parallel L}}{Z_{R \parallel L} + Z_C} V_s$$

$$\frac{V_o}{V_s} = \frac{\left(\frac{1}{R} + \frac{1}{sL}\right)^{-1}}{\left(\frac{1}{R} + \frac{1}{sL}\right)^{-1} + \frac{1}{sC}}$$

$$= \frac{sC}{\left(\frac{1}{sL} + \frac{1}{R}\right) + sC}$$

$$\therefore T(s) = \frac{V_o(s)}{V_s(s)} = \frac{s^2}{s^2 + s/R + 1/LC}$$

11.31

$$\text{Low Pass: } \omega_0 = 10^5, C = 0.1 \mu F$$

$$Q = \frac{1}{\sqrt{2}}$$

$$Q = \omega_0 CR$$

$$R = \frac{Q}{\omega_0 C}$$

$$= \frac{1}{\sqrt{2} \times 10^5 \times 0.1 \times 10^{-6}}$$


$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$L = \frac{1}{\omega_0^2 C}$$

$$= \underline{\underline{1mH}}$$

$$= \underline{\underline{70.7 \Omega}}$$

11.32

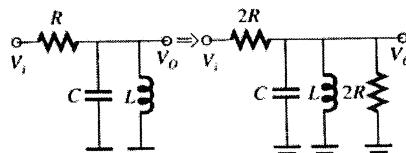

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega \omega_0 CR$$

$$A_{mid} = 1$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 C(2R \parallel 2R)$$

$$= \omega_0 CR$$

$$A_{mid} = \frac{2R}{2R + 2R} = \frac{1}{2}$$

11.33

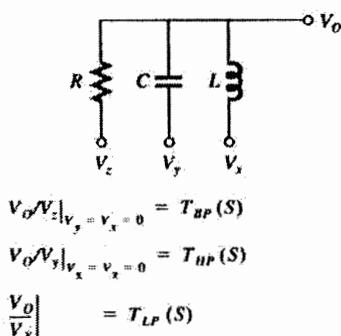

$$V_o/V_z|_{V_y=V_x=0} = T_{BP}(S)$$

$$V_o/V_y|_{V_x=V_z=0} = T_{HP}(S)$$

$$\frac{V_o}{V_x}|_{V_y=V_z} = T_{LP}(S)$$

Using superposition


$$\begin{aligned} V_o &= \frac{V_o}{V_x} V_x + \frac{V_o}{V_y} V_y + \frac{V_o}{V_z} V_z \\ &= T_{LP} V_x + T_{HP} V_y + T_{BP} V_z \end{aligned}$$

$$\frac{\frac{1}{LC} V_x + S^2 V_y + \frac{S}{RC} V_z}{S^2 + S/RC + \frac{1}{LC}}$$

$$\therefore V_o = V_x \frac{y_{LC}}{S^2 + S/R_C + 1/L_C}$$

$$V_x \frac{S^2}{S^2 + S/R_C + 1/L_C} + V_z \frac{S/R_C}{S^2 + S/R_C + 1/L_C}$$

11.34

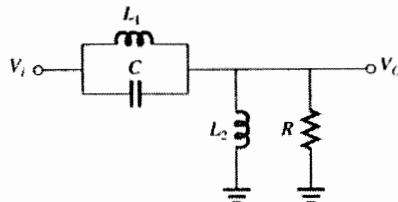

From Eq 16.46

$$T(S) = \frac{S^2 + 1/L_1 C}{S^2 + S(1/CR) + \frac{1}{(4 \parallel L_2) C}}$$

$$\text{Required notch } \omega_n^2 = \frac{1}{L_1 C} = (0.9\omega_o)^2$$

but:

$$\omega_o^2 = \frac{1}{(L_1 \parallel L_2) C} \text{ where}$$

$$L_1 \parallel L_2 = \frac{1}{4^{-1} + L_2^{-1}} = \frac{L_1 L_2}{L_1 + L_2}$$

$$= \frac{L_1 + L_2}{L_1 L_2 C}$$

$$= \frac{L_1 + L_2}{L_2} (0.9 \omega_o)^2$$

$$1 = \left(\frac{L_1}{L_2} + 1\right) 0.9^2$$

$$\therefore L_1/L_2 = \frac{1}{0.9^2} - 1 = 0.2346$$

For  $\omega \ll \omega_o$ :

$$|T| \approx \frac{1/L_1 C}{1/(L_1 \parallel L_2) C} = \frac{L_2}{L_1 + L_2}$$

i.e. inductors dominate!

For  $\omega \gg \omega_o$ ,  $L_1$  &  $L_2$  are "open"  $C$  is shorted

$$|T| \approx 1$$

11.35

$$L = C_1 R_1 R_3 / R_2$$

$$\text{Choose } R_1 = R_2 = R_3 = R_5 = 10 \text{ k}\Omega$$

$$\therefore L = C_4 \times 10^8$$

For:

$$L = 10 \text{ H} = C_4 \times 10^8 \Rightarrow C_4 = 100 \text{ nF}$$

$$L = 1 \text{ H} \Rightarrow C_4 = 10 \text{ nF}$$

$$L = 0.1 \text{ H} \Rightarrow C_4 = 1 \text{ nF}$$

11.36

$$A_{\max} = 10 \log(1 + r^2) = 3 \text{ dB}$$

$$\therefore r = 0.998 \approx 1$$

$$\omega_o = \omega_p = 10^4$$


For circuit Q use fig 16.13 (a)

DC Gain


$$= 1 = R_2 / R_1 \Rightarrow R_1 = R_2 = 10 \text{ k}\Omega$$

$$CR_2 = 1/\omega_o \Rightarrow C = 1/R_2 \omega_o = \frac{1}{10^4 \cdot 10^4}$$

= 10 nF

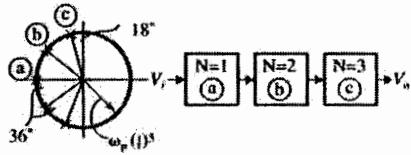

For circuit (b)

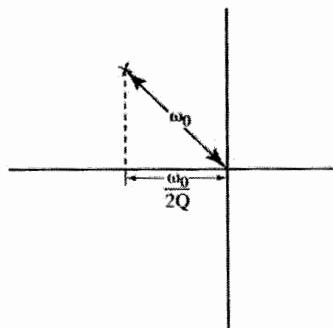

$$\omega_o = 10^4 \text{ rad/s}$$

$$\frac{\omega_o}{2Q} = \omega_o \cos 36^\circ$$

$$Q = \frac{1}{2 \cos 36^\circ} = 0.618$$

$$T(S) = \frac{k R_2}{\frac{C_4 C_6 R_1 R_3 R_5}{S^2 + S/C_6 R_6 + \frac{R_2}{C_4 C_6 R_1 R_3 R_5}}}$$

$$\omega_o^2 = \frac{R_2}{C_4 C_6 R_1 R_3 R_5}$$

$$\text{Let } R_1 = R_3 = R_5 = R_2 = R$$

$$C_4 = C_6 = C$$

$$\omega_o^2 = \frac{1}{R^2 C^2}$$

$$\text{USE } C_4 = C_6 = 100 \text{ nF}$$

$$\therefore R = \frac{1}{\omega_o C} \Rightarrow R_1 = R_2 = R_3 = R_5 = 1 \text{ k}\Omega$$

Now using:

$$\frac{\omega_o}{Q} = \frac{1}{C_6 R_6} \quad \& \quad Q = 0.618$$

$$R_6 = \frac{Q}{C_6 \omega_o} = 618 \Omega$$

For circuit (c) use

$$\omega_o = 10^4 \text{ which is the same as for circuit (b).}$$

$$\therefore C_4 = C_6 = 100 \text{ nF}$$

$$R_1 = R_2 = R_3 = R_5 = 1 \text{ k}\Omega$$

$$\text{Now: } Q = \frac{1}{2 \cos 72^\circ} = 1.618$$

$$R_6 = Q / \omega_o C_6 = 1.618 \text{ k}\Omega$$

11.37

$$f_o = 4 \text{ kHz} \quad f_N = 5 \text{ kHz} \quad Q = 10$$

now  $C_4 = 10 \text{ nF}$  and  $k = 1 \equiv \text{dc gain}$

$$W_D = [C_4(C_{61} + C_{62})R_1 R_3 R_5 / R_2]^{-1/2}$$

$$C_{61} + C_{62} = C_6$$

$$\text{Choose } C_6 = C_4 = 10 \text{ nF}$$

$$R_1 = R_3 = R_5 = R_2 = R$$

$$\therefore \omega_o = (C_4 C_6 R^2)^{-1/2}$$

$$R = \frac{1}{\omega_o C_4}$$

$$\Rightarrow R_1 = R_3 = R_5 = R_2 = 3.979 \text{ k}\Omega$$

$$\omega_o = (C_4 C_6 R^2)^{-1/2}$$

$$C_{61} = \frac{1}{\omega_o^2 R^2 C_4} \Rightarrow C_{61} = 6.4 \text{ nF}$$

$$C_{62} = 3.6 \text{ nF}$$

$$Q = R_6 \sqrt{\frac{C_{61} + C_{62}}{C_4} \cdot \frac{R_2}{R_1 R_3 R_5}}$$

$$= R_6 \sqrt{\frac{1}{R_1^2}} = R_6 / R_1 \Rightarrow R_6 = 39.79 \text{ k}\Omega$$

11.38  $\theta = 180^\circ$  at  $f_o$ !

$$\therefore \text{Use } f_o = 1 \text{ kHz} \quad Q = 1$$

$$W_D^2 = \frac{R_2}{C_4 C_6 R_1 R_3 R_5}$$

$$\text{Let } C = C_4 = C_6 = 1 \text{ nF}$$

$$R_1 = R_3 R_5 = R_2 = R \\ = 1/C^2 R^2$$

$$R = \frac{1}{W_D C} = 159.16 \text{ k}\Omega = R_1 = R_3 = R_5 = R_2$$

$$\frac{W_D}{Q} = \frac{1}{R_6 C_6} \Rightarrow R_6 = \frac{Q}{C_6 W_D} \\ = \frac{1}{10^{-9} 2 \pi 10^3}$$

$$\therefore R_6 = 159.16 \text{ k}\Omega$$



$$\text{Now } \frac{1}{R_3} = \frac{1}{R_3 \frac{\omega_o^2}{\omega_n^2}} + \frac{1}{R_{32}}$$

$$\frac{1}{R_{32}} = \frac{1}{R_3} \left[ 1 - \frac{\omega_n^2}{\omega_o^2} \right]$$

$$R_{32} = \frac{R_3}{1 - \omega_n^2 / \omega_o^2}$$

### 11.42

$T(s)$

$$= \frac{0.4508 (S^2 + 1.6996)}{(S + 0.7294) (S^2 + 0.2786s + 1.0504)}$$

Part (a) Replace s with  $s/\omega_p$

$T(s)$

$$= \frac{0.4508 (S^2 / \omega_p^2 + 1.6996)}{\left( \frac{S}{\omega_p} + 0.7294 \right) \left( \frac{S^2}{\omega_p^2} + \frac{0.27865}{\omega_p} + 1.0504 \right)}$$

$T(s)$

$$= \frac{0.4508 \omega_p (S^2 + 1.6996 \omega_p^2)}{(S + 0.7294 \omega_p) (S^2 + 0.2786 \omega_p S + 1.0504 \omega_p^2)}$$

Sub  $\omega_p = 10^4 \text{ rad/s}$

$T(s)$

$$= \frac{4508 (S^2 + 1.6996 \times 10^8)}{(S + 7294) (S^2 + 2786s + 1.0504 \times 10^8)}$$

Part (b)

First decompose  $T(s)$  into 1st and 2nd-order sections with unity DC gain!

$$T_1(s) = \frac{k_1}{S + 7294} \quad T_1(o) = \frac{k_1}{7294} = 1 \\ \Rightarrow k_1 = 7294$$

Now  $k_1, k_2 = 4508 \Rightarrow k_2 = 0.6180$

$$\therefore T_2(s) = \frac{0.6180 (S^2 + 1.6996 \times 10^8)}{S^2 + 2786s + 1.0504 \times 10^8}$$

As a check:

$$T_2(o) = \frac{0.6180 (1.6996 \times 10^8)}{1.0504 \times 10^8} = 1.000$$

AS EXPECTED!

$$\therefore T(s) = T_1(s) \cdot T_2(s)$$

$\omega_n = 7294 \text{ rad/s} \quad \text{DC Gain} = 1$

Let  $C = 10 \text{ nF}$

$$R_1 = R_2 = \frac{1}{\omega_n C} \Rightarrow R_1 = R_2 = 13.71 \text{ k}\Omega$$

$$11.43 \quad R_L = R_H = R_B / Q \Rightarrow R_B = QR_H$$

$$R_L = R_H$$

$$\frac{V_o}{V_i} = -K \frac{\frac{R_f}{R_H} S^2 - S \left( \frac{R_f}{R_H} \right) \omega_o + \left( \frac{R_f}{R_L} \right) \omega_o^2}{S^2 + S \frac{\omega_o}{Q} + \omega_o^2}$$

$$= -K \frac{\frac{R_f}{R_H} S^2 - \frac{\omega_o}{Q} S + \omega_o^2}{S^2 + S \frac{\omega_o}{Q} + \omega_o^2}$$

$$\text{Flat Gain} = -K R_f / R_H$$

Part (b)

$$- \omega_o = 10^4 \text{ rad/s} \quad Q = 2 \quad \text{Flat Gain} = 10$$

$$\text{Choose } C = 10 \text{ nF} \Rightarrow R = \frac{1}{\omega_o C} = 10 \text{ k}\Omega$$

$$\text{Choose } R_f = R_1 = 10 \text{ k}\Omega$$

$$\frac{R_1}{R_2} = 2Q - 1 = 3 \Rightarrow R_2 = 10 \text{ k}\Omega$$

$$R_3 = 30 \text{ k}\Omega$$

$$\text{Now } K = 2 - 1/Q = 1.5$$

$$\therefore \text{Flat Gain} = 10 = (1.5) \frac{R_f}{R_H}$$

$$\therefore \frac{R_H}{R_f} = 0.15$$

$$\text{Choose } R_f = 100 \text{ k}\Omega$$

$$R_H = R_L = 15 \text{ k}\Omega$$

$$R_B = QR_H = 30 \text{ k}\Omega$$

11.44 Note  $\omega_n$  does not depend on R or C From

$$\frac{R_H}{R_L} = \left( \frac{\omega_n}{\omega_o} \right)^2$$

$$\therefore \omega_n = \omega_o \sqrt{\frac{R_H}{R_L}} \quad \text{Nominally } R_H = R_L \pm 1\%$$

Thus:

$$\omega_n = \omega_o \sqrt{\frac{1.01}{0.99}} \quad \omega_n = \omega_o \sqrt{\frac{0.99}{1.01}} \\ = 1.01 \omega_o \quad = 0.99 \omega_o$$

$\therefore \omega_n$  can deviate from  $\omega_o$  by  $\pm 1\%$

### 11.45

Use Tow Thomas to realize a LPN

$$\omega_o = 10^4 \quad \omega_n = 1.2\omega_o \quad Q = 10$$

DC Gain = 1

$$C = 10 \text{ nF} \quad r = 20 \text{ k}\Omega$$

$$R = \frac{1}{\omega_o C} = 10 \text{ k}\Omega$$

From 16.16 (e):

$$\text{DC Gain} = a_2 \frac{\omega_n^2}{\omega_o^2} = 1$$

$$a_2 \frac{1.2^2 \omega_o^2}{\omega_o^2} = 1$$

$$a_2 \frac{1}{1.2^2} = \text{HF Gain}$$

$$C_1 = Ca_2 = \frac{10 \times 10^{-9}}{1.2^2} = 6.94 \text{ nF}$$

$$R_2 = \frac{R(\omega_o / \omega_n)^2}{\text{HF Gain}} = R \left( \frac{1}{1.2} \right)^2 \times (1.2)^2 = R = 10 \text{ k}\Omega$$

$$R_1 = R_3 = \infty$$

### 11.46

For all pass:

$T(S)$

$$-g^2 \left( \frac{C_1}{C} \right) + S \frac{1}{C} \left( \frac{1}{R_1} - \frac{r}{RR_3} \right) + \frac{1}{C^2 RR_2}$$

$$\omega_z^2 = \frac{1}{C^2 RR_2} \cdot \frac{C}{C_1} \Rightarrow \omega_z = \frac{1}{C \sqrt{RR_2}} \cdot \sqrt{\frac{C}{C_1}}$$

$$Q_Z = \frac{\omega_z}{\frac{1}{C} \left( \frac{1}{R_1} - \frac{r}{RR_3} \right) \frac{C}{C_1}}$$

$$Q_Z = \frac{\sqrt{\frac{1}{C^2 RR_2} \frac{C}{C_1}}}{\frac{1}{C} \left( \frac{1}{R_1} - \frac{r}{RR_3} \right) \left( \frac{C}{C_1} \right)}$$

$$\frac{1}{\sqrt{RR_2} \left( \frac{1}{R_1} - \frac{r}{RR_3} \right) \sqrt{\frac{C}{C_1}}}$$

For All Pass  $R_1 \Rightarrow \infty$

To adjust  $Q_Z$ , trim  $r$  or  $R_2$  (independent of  $W_z$ !)

Now  $\omega_o = \frac{1}{CR}$  so do not trim R or C!

Note if we trim  $R_2$  or  $C_1$  to adjust  $W_z$  This will also affect  $Q_z$ . So the options are:

For  $W_z$ : (a) trim  $R_2$  and ( $r$  or  $R_3$ ) to maintain the value of  $Q_z$ .

OR

(b) trim  $C_1$ , and  $r$  or  $R_3$

Prefer not to trim a capacitor so use (a) !

### 11.47

$T(s)$

$$= \frac{0.4508 (S^2 + 1.6996)}{(S + 0.7294)(S^2 + 0.27865 + 1.0504)}$$

Part (a) Replace s with  $s/\omega_p$

$$\omega_p = 10^4 \text{ rad/s.}$$

$T(s)$

$$= \frac{0.4508 (S^2 / \omega_p^2 + 1.6996)}{\left( \frac{S}{\omega_p} + 0.7294 \right) \left( \frac{S^2}{\omega_p^2} + \frac{0.27865}{\omega_p} + 1.0504 \right)}$$

$T(s)$

$$= \frac{0.4508 \omega_p (S^2 + 1.6996 \omega_p^2)}{(S + 0.7294 \omega_p)(S^2 + 0.27865 \omega_p S + 1.0504 \omega_p^2)}$$

$$= \frac{4508 (S^2 + 1.6996 \times 10^8)}{(S + 7294)(S^2 + 27865 + 1.0504 \times 10^8)}$$

For FIRST ORDER SECTION

$$\omega_o = 7294 \quad \text{DC Gain} = 1$$

Choose  $C = 10 \text{ nF}$

$$R_1 = R_2 = \frac{1}{\omega_o C} \Rightarrow R_1 = R_2 = 13.71 \text{ k}\Omega$$

For SECOND ORDER SECTION

$$\omega_n^2 = 1.6996 \times 10^8 \Rightarrow \omega_n = 13.037 \times 10^3$$

$$\omega_o^2 = 1.0504 \times 10^8 \Rightarrow \omega_o = 10.249 \times 10^3$$

$$\frac{\omega_o}{Q} = 2786 \Rightarrow Q = 3.6787$$

DC gain = 1

For Tow Thomas LPN

Choose  $C = 10 \text{ nF}$

$$R = \frac{1}{\omega_o C} = \frac{1}{10.249 \times 10^3 \times 10 \times 10^{-9}} = 9.757 \text{ k}\Omega$$

Choose  $r = 20 \text{ k}\Omega$

(e):

$$T(s) = a_Z \frac{\omega_n^2}{\omega_o^2} = 1 \Rightarrow a_Z \frac{\omega_o^2}{\omega_n^2} = 0.618$$

$\therefore$  HF gain =  $a_Z = 0.618$

$$C_1 = C \times \text{HF gain} \Rightarrow C_1 = 0.618 \text{ nF}$$

$$R_2 = R (\omega_o / \omega_n)^2$$

$$R_2 = 0.618 R \Rightarrow R_2 = 6.03 \text{ k}\Omega$$

$$R_1 = R_3 = \infty \quad QR = 35.89 \text{ k}\Omega$$

11.48

$$t(S) = \frac{s^2 + s\left(\frac{1}{C_1} + \frac{1}{C_2}\right)\frac{1}{R_3} + \frac{1}{C_1 C_2 R_3 R_4}}{s^2 + s\left(\frac{1}{C_1 R_3} + \frac{1}{C_2 R_4} + \frac{1}{C_2 R_3}\right) + \frac{1}{C_1 C_2 R_3 R_4}}$$

But  $C_1 = C_2 = C$  &  $R_3 = R_4 = R$ ,  $RC = \tau$

$$\therefore t(S) = \frac{s^2 + s^2/RC + 1/R^2 C^2}{s^2 + s/RC + \frac{1}{R^2 C^2}}$$

$$= \frac{s^2 + s^2/\tau + 1/\tau^2}{s^2 + s^2/\tau + 1/\tau^2}$$

Zeros defined by  $w_i = 1/\tau$

$$Q_i = \frac{1}{2}$$

$\Rightarrow$  Double Root at  $S = -1/\tau$

Poles of  $t(S)$  are given by the quadratic formula:

$$S = \frac{-3 \pm \sqrt{5}}{2\tau} = \frac{-3 \pm \sqrt{5}}{2\tau}$$


i.e. two roots on the negative real axis

If the network is placed in the negative feedback path of an ideal amplifier ( $A = \infty$ ) then the poles are given by the zeros of  $t(S)$ :

Closed loop poles:

$$S = -1/\tau \text{ (multiplicity = 2)}$$

11.49

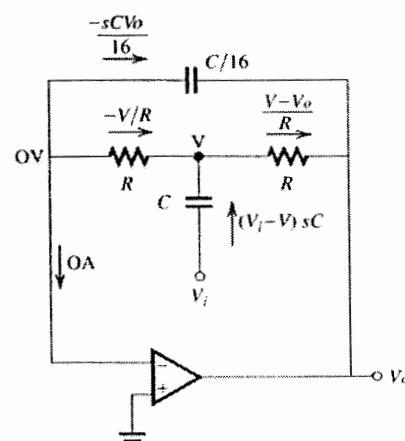

$$\text{Note first } \frac{-sCV_o}{16} = \frac{-V}{R}$$

$$V = -\frac{sCRV_o}{16}$$

$\Sigma I$  at  $V$

$$-\frac{V}{R} + sC(V_i - V) - \frac{V - V_o}{R} = 0$$

$$\frac{sCV_o R}{16} + sCV_i + \frac{s^2 C^2 R V_o}{16} + \frac{sCV_o}{16}$$

$$+ \frac{V_o}{R} = 0$$

mult by:  $16R$  and let  $RC = \tau$

$$s\tau V_o + 16\tau V_i s + s^2 \tau^2 V_o + s\tau V_o + 16V_o = 0$$

$$V_o [s^2 \tau^2 + s \times 2\tau + 16] = -16 s^2 V_i$$

$$\therefore \frac{V_o}{V_i} = -\frac{16s\tau}{s^2 \tau^2 + 2\tau s + 16}$$

$$\therefore T(s) = \frac{s/16/RC}{s^2 + s^2/RC + 16/R^2 C^2}$$

$$\text{Let } \omega_o^2 = \frac{16}{(RC)^2} \Rightarrow \omega_o = \frac{4}{RC}$$

$$\frac{\omega_o}{Q} = \frac{2}{RC} \Rightarrow Q = \frac{RC\omega_o}{2} = 2$$

$$\frac{\omega_o}{Q} = \frac{2}{RC} \Rightarrow Q = \frac{RC\omega_o}{2} = 2$$

$$\therefore \frac{V_o}{V_i} = \frac{-4\omega_o s}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2}$$


$$|T|_{s=0} = 0 \quad \text{Bandpass}$$

$$|T|_{s=\infty} = 0$$

$$|T(j\omega_o)| = 4/1/2 = 8 \frac{V}{V} \text{ CENTER FREQ}$$

GAIN

11.50

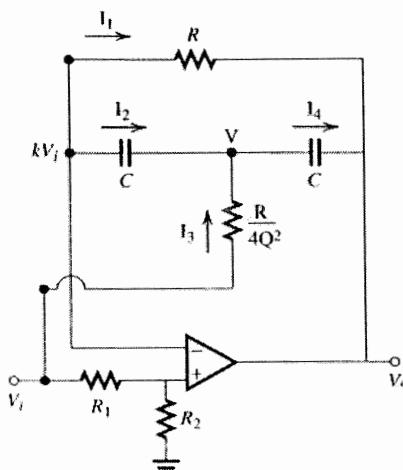

$$RC = 2Q/\omega_o$$

$$k = \frac{R_2}{R_1 + R_2}$$

$V_+$  =  $V_{out}$  =  $kV_i$  due to virtual short

$$I_1 = -I_2$$

$$\frac{kV_i - V_o}{R} = \frac{V - kV_i}{1}$$

$$V = \frac{1}{SCR}(kV_i - V_o + SCRkV_i)$$

$\Sigma I$  at  $V = 0$

$$I_2 + I_3 - I_4 = 0$$

$$SC(kV_i - V) + \frac{4Q^2}{R}(V_i - V) \\ - SC(V - V_o) = 0 \\ SC\left(kV_i - \frac{kV_i}{SCR} + \frac{V_o}{SCR} - kV_i\right) \\ + \frac{4Q^2}{R}\left(V_i - \frac{kV_i}{SCR} + \frac{V_o}{SCR} - kV_i\right) \\ - SC\left(\frac{kV_i}{SCR} - \frac{V_o}{SCR} + kV_i - V_o\right) = 0 \\ \Rightarrow - \frac{kV_i}{R} + \frac{V_o}{R} \\ + \frac{4Q^2}{R}\left(V_i - \frac{kV_i}{SCR} + \frac{V_o}{SCR} - kV_i\right) \\ - \frac{SC\left(\frac{kV_i}{SC} - \frac{V_o}{SC} + kRV_i - V_oR\right)}{R} = 0 \\ \Rightarrow \text{SUB CR} = \frac{2Q}{\omega_o} \quad \& \quad R = \frac{2Q}{C\omega_o} \\ - kV_i + V_o \\ + \frac{2Q^2kV_i\omega_o}{S2Q} + \frac{V_o\omega_o 4^2 Q^2}{S2Q} - 4Q^2kV_i \\ - kV_i + V_o - SK2Q/\omega_o V_i + SV_o \frac{2Q}{\omega_o} = 0$$

$$V_o \left[ 1 + \frac{2Q\omega_o}{S} + 1 + \frac{2QS}{\omega_o} \right] \\ = V_i \left[ k - 4Q^2 + \frac{2kQ\omega_o}{S} + 4Q^2k + k + \frac{2kQS}{\omega_o} \right]$$

$$\Rightarrow V_o \left[ S^2 \frac{2Q}{\omega_o} + 2S + 2Q\omega_o \right] = V_i \left[ S^2 \frac{2kQ}{\omega_o} + \right.$$

$$S(4Q^2k - 4Q^2 + 2k) + 2kQ\omega_o \\ \Rightarrow \frac{V_o}{V_i} = \frac{S^2 \frac{2kQ}{\omega_o} + S(4Q^2k - 4Q^2 + 2k) + 2kQ\omega_o}{S^2 \frac{2Q}{\omega_o} + 2S + 2Q\omega_o}$$

$$= k \frac{S^2 + S \frac{\omega_o}{Q} \left( 2Q^2 - \frac{2Q^2}{k} + 1 \right) + \omega_o^2}{S^2 + S \frac{\omega_o}{Q} + \omega_o^2}$$

$$\text{Recall } k = \frac{R_2}{R_1 + R_2} \text{ and } \frac{1}{k} = 1 + \frac{R_1}{R_2}$$

$$\Rightarrow \frac{V_o}{V_i} = \left( \frac{R_L}{R_1 + R_2} \right) \frac{S^2 + S \frac{\omega_o}{Q} \left( 1 - \frac{R_L}{R_2} \cdot 2Q^2 \right) + \omega_o^2}{S^2 + S \frac{\omega_o}{Q} + \omega_o^2}$$

$$\therefore T(S) = \frac{R_2}{R_1 + R_2}$$

$$\frac{S^2 + S \frac{\omega_o}{Q} \left( 1 - \frac{2Q^2 R_1}{R_2} \right) + \omega_o^2}{S^2 + S \frac{\omega_o}{Q} + \omega_o^2}$$

For All Pass

$$\text{we want } T(S) \propto \frac{S^2 + \frac{\omega_o}{Q}(-1)S + \omega_o^2}{S^2 + S \frac{\omega_o}{Q} + \omega_o^2} \\ \Rightarrow 1 - \frac{2Q^2 R_1}{R_2} = -1$$

$$2Q^2 \frac{R_1}{R_2} = 2$$

$$\frac{R_1}{R_2} = \frac{1}{Q^2}$$

$$\therefore \frac{R_2}{R_1} = Q^2 \quad \& \quad \frac{R_2}{R_1 + R_2} = \frac{R_2/R_1}{1 + R_2/R_1} \\ = \frac{Q^2}{1 + Q^2}$$


For Notch:

$$1 - 2Q^2 \frac{R_1}{R_2} = 0$$

$$\frac{R_1}{R_2} = \frac{1}{2Q^2}$$

$$\frac{R_2}{R_1} = 2Q^2 \quad \& \quad \frac{R_2}{R_1 + R_2} = \frac{2Q^2}{1 + 2Q^2}$$

### 11.51

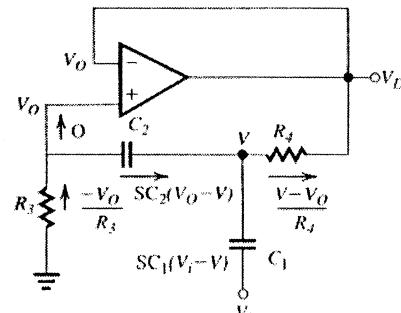

$\therefore$  No current can't flow into the terminal

$$-\frac{V_o}{R_3} = SC_2(V_o - V)$$

$$V = V_o \left( 1 + \frac{1}{SC_2 R_3} \right)$$

$\Sigma I @ V = 0$

$$-\frac{V_o}{R_3} + \frac{V_i - V}{R_4} SC_1 = \frac{V - V_o}{R_4}$$

$$V_o \left[ -\frac{1}{R_3} + \frac{1}{R_4} \right] + V \left[ -SC_1 - \frac{1}{R_4} \right] = -SC_1 V_i$$

$$V_o [R_i - R_1] + V [SC_1 R_3 R_4 + R_1] = V S C_1 R_3 R_4$$

$$V_o (R_4 - R_3) + V_o \left( 1 + \frac{1}{S C_2 R_3} \right) (S C_1 R_3 R_4 + R_1) \\ = S C_1 R_3 R_4 V_i$$

$$V_o (R_4 - R_3 + S C_1 R_3 R_4 + R_1 + \frac{C_1 R_4 + \frac{1}{S C_2}}{C_2})$$

$$= S C_1 R_3 R_4 V_i$$

$$V_o (S^2 C_1 C_2 R_3 R_4 + S C_1 R_4 + S C_2 R_4 + 1)$$

$$= S^2 C_1 R_3 R_4 C_2 V_i$$

$$\therefore \frac{V_o}{V_i} = \frac{S^2 C_1 C_2 R_3 R_4}{S^2 C_1 C_2 R_3 R_4 + S C_1 R_4 + S C_2 R_4 + 1}$$

$$= \frac{S^2}{S^2 + S \left( \frac{1}{C_2 R_3} + \frac{1}{C_1 R_4} \right) + \frac{1}{C_1 C_2 R_3 R_4}}$$

$$\text{Note } \begin{cases} |T(O)| = 0 \\ |T(\infty)| = 1 \end{cases} \therefore \text{High Pass}$$

$$\text{High Freq Gain} = 1 \frac{V}{V} \\ 3 \text{ dB freq} = 10^3 \text{ rad/s}, \quad Q = \frac{1}{\sqrt{2}} \text{ for max flat.}$$

$$\therefore w_o = 10^3 \frac{\text{rad}}{\text{s}}, \quad C_1 = C_2 = 10 \text{ nF}$$

$$\text{clearly } w_o^2 = \frac{1}{C_1 C_2 R_3 R_4} \text{ and}$$

$$\frac{w_o}{Q} = \frac{1}{C_2 R_3} + \frac{1}{C_1 R_4} = \frac{C_1 + C_2}{C_1 C_2 R_3}$$


$$= \frac{2C}{C^2 R_3} = \frac{2}{CR_3} = \sqrt{2} \times 10^3$$

$$R_3 = \frac{2}{10 \times 10^{-9} \times 10^3 \times \sqrt{2}}$$

$$R_3 = 141.4 \text{ k}\Omega$$

$$R_4 = \frac{1}{w_o^2 C_1 C_2 R_3} \Rightarrow R_4 = 70.7 \text{ k}\Omega$$

### 11.52

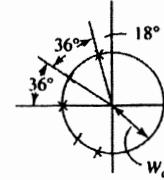

$$A_{max} = 3 \text{ dB}$$

$$\epsilon = (10^{3/10} - 1)^{-1/2} \approx 1$$

$$\omega_o = \omega_p \left( \frac{1}{\epsilon} \right)^{1/N} = \omega_p = 2\pi 5000 = 10^4 \pi$$

$$Q_1 = \frac{1}{2 \cos 36^\circ} = 0.618$$

$$Q_2 = \frac{1}{2 \cos 72^\circ} = 1.618$$

For first order section:

$$\omega_o = 10^4 \pi \quad \text{dc gain} = 1$$

From 16.13 (a)

$$R_1 = R_2 = 10 \text{ k}\Omega$$

$$C = \frac{1}{\omega_o R_2} = \frac{1}{10^4 \pi \cdot 10^4} = 3.18 \text{ nF}$$

Second order section  $Q = 0.618$ :

From 16.34 (c)  $m = 4Q^2 = 1.528$

$$RC = \frac{2Q}{\omega_o} \text{ let } R_1 = R_2 = 10 \text{ k}\Omega$$

$$C = \frac{2Q}{\omega_o R} \Rightarrow C_4 = C = 3.93 \text{ nF}$$

$$C_3 = \frac{C}{m} = 2.57 \text{ nF}$$

Second Order Section  $Q = 1.618$ :

$$C = \frac{2Q}{\omega_o R} \quad m = 4Q^2 = 10.472$$

$$= 10.3 \text{ nF} \Rightarrow R_1 = R_2 = 10 \text{ k}\Omega$$

$$C_4 = C = 10.3 \text{ nF}$$

$$C_3 = \frac{C}{m} = 0.984 \text{ nF}$$

### 11.53

For a bandpass filter


$$t(s) = \frac{\omega_o / Qs}{s^2 + s\omega_o/Q + \omega_o^2}$$

center freq. gain = 1


complementary transfer function :

$$t' = 1 - t$$
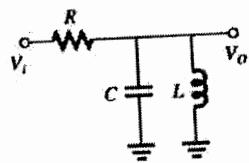
$$= \frac{s^2 + \omega_o^2}{s^2 + s\omega_o/Q + \omega_o^2} = \text{NOTCH!}$$



⇒ INTERCHANGE  $V_i$  & gnd to get:

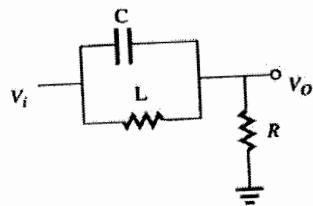

11.54

$$T(s) = \frac{s/RC}{s^2 + s/RC + 1/LC}$$

$$\omega_o = \frac{1}{\sqrt{LC}} \quad Q = R \sqrt{\frac{C}{L}}$$

For  $\omega_o$

$$\frac{\partial \omega_o}{\partial L} = \frac{\partial (LC)^{-1/2}}{\partial L} = -\frac{1}{2} L^{-3/2} C^{-1/2} = \frac{\omega_o}{2L}$$

$$\frac{\partial \omega_o}{\partial C} = -\frac{\omega_o}{2C}$$

$$\frac{\partial \omega_o}{\partial R} = 0$$

$$\therefore S_L^{wo} = \frac{\partial \omega_o}{\partial L} \frac{L}{\omega_o} = -1/2$$

$$S_C^{wo} = \frac{\partial \omega_o}{\partial C} \times \frac{C}{\omega_o} = -1/2$$

$$S_R^{wo} = \frac{\partial \omega_o}{\partial R} \frac{R}{\omega_o} = 0$$

For  $Q$

$$\frac{\partial Q}{\partial L} = \frac{R\sqrt{C}}{L\sqrt{L}} \left( -\frac{1}{2} \right) = -\frac{Q}{2L}$$

$$\frac{\partial Q}{\partial C} = \frac{1}{2} \frac{R}{\sqrt{LC}} = \frac{1}{2} \frac{R\sqrt{C}}{C\sqrt{L}} = \frac{Q}{2C}$$

$$\frac{\partial Q}{\partial R} = \sqrt{C/L} = \frac{R}{R} \sqrt{C/L} = Q/R$$

$$S_L^Q = -\frac{Q}{2C} \times \frac{L}{Q} = -\frac{1}{2}$$

$$S_C^Q = \frac{Q}{2C} \times \frac{C}{Q} = \frac{1}{2}$$

$$S_R^Q = -\frac{Q}{R} \times \frac{R}{Q} = -1$$

11.55

$$s^2 + s \frac{\omega_o}{Q} \left[ 1 + \frac{2Q^2}{A+1} \right] + \omega_o^2 = 0$$

Now the actual  $\omega_o$  and  $Q$  are given by:

$$\omega_{o,a} = \omega_o \text{ and } Q_a = \frac{Q}{1 + \frac{2Q^2}{(A+1)}}$$

$$S_A^{wo,a} = 0$$

$$S_A^{Q,a} = \frac{A}{A+1} \frac{2Q^2(A+1)}{1+2Q^2/(A+1)}$$

$$\therefore S_A^{Q,a} \equiv \frac{2Q^2}{A}$$

11.56

$$R_1 = R_2,$$

$$\omega_o = \frac{1}{\sqrt{C_3 C_4 R_1 R_2}}$$

$$Q = \frac{1}{\sqrt{C_3 C_4 R_1 R_2 \left( \frac{1}{C_4} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \right)}}$$

$$\frac{\partial \omega_o}{\partial C_3} = \frac{-1}{2C_3 \sqrt{C_3 C_4 R_1 R_2}}$$

$$\frac{\partial \omega_o}{\partial C_3} = \frac{-1}{2C_3 \sqrt{C_3 C_4 R_1 R_2}} = \frac{-\omega_o}{2C_3}$$

$$S_{C_3}^{wo} = \frac{\partial \omega_o}{\partial C_3} \frac{C_3}{\omega_o} = -\frac{1}{2}$$

$$\text{clearly } S_{C_3}^{wo} = S_{C_4}^{wo} = S_{R_1}^{wo} = S_{R_2}^{wo} = -\frac{1}{2}$$

$$\frac{\partial Q}{\partial C_3} = \frac{-1}{2C_3 \sqrt{C_3 C_4 R_1 R_2} \left( \frac{1}{C_4} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \right)} = \frac{-Q}{2C_3}$$

$$\therefore S_{C_3}^Q = -\frac{1}{2}$$

$$\frac{\partial Q}{\partial C_4} = \frac{Q}{2C_4} \Rightarrow S_{C_4}^Q = +\frac{1}{2}$$

$$\frac{\partial Q}{\partial R_1} = \frac{1/\sqrt{R_1} - \sqrt{R_1}/R_2}{R_1 \left( \frac{1}{\sqrt{R_1}} + \frac{1}{\sqrt{R_2}} \right)} \cdot \frac{Q}{2}$$

$$= \frac{\sqrt{R_2}/R_1 - \sqrt{R_1}/R_2}{R_1 \left( \frac{1}{\sqrt{R_1}} + \frac{1}{\sqrt{R_2}} \right)} \cdot \frac{Q}{2}$$

$$S_{R_1}^Q = \frac{\sqrt{R_2/R_1} - \sqrt{R_1/R_2}}{\sqrt{R_2/R_1} + \sqrt{R_1/R_2}}$$

If  $R_1 = R_2 \Rightarrow S_{R_1}^Q = 0$

$$S_{R_2}^Q = 0$$

### 11.57

$$\omega_o = \frac{1}{\sqrt{C_4 C_6 R_1 R_3 R_5 R_2}}$$

$$Q = R_6 \sqrt{\frac{C_6}{C_4 R_1 R_3 R_5}} \frac{R_2}{R_1}$$

$$\frac{\partial \omega_o}{\partial C_4} = \frac{-\omega_o}{2C_4}$$

$$\therefore S_{C_4}^{\omega_o} = \frac{-\omega_o}{2C_4} \times \frac{C_4}{\omega_o} = -\frac{1}{2}$$

$$\text{Similarly } S_{C_6}^{\omega_o} = S_{R_1}^{\omega_o} = S_{R_3}^{\omega_o} = S_{R_5}^{\omega_o} = \frac{1}{2}$$

$$\frac{\partial \omega}{\partial R_2} = \frac{\omega_o}{2R_2} \Rightarrow S_{R_2}^{\omega_o} = \frac{1}{2}$$

Now for  $Q$ :

$$\frac{\partial Q}{\partial R_6} = \frac{Q}{R_6} \Rightarrow S_{R_6}^Q = \frac{\partial Q}{\partial R_6} \frac{R_6}{Q} = +1$$

$$\frac{\partial Q}{\partial C_6} = \frac{Q}{2C_6} \Rightarrow S_{C_6}^Q = S_{R_2}^Q = +\frac{1}{2}$$

$$\frac{\partial Q}{\partial C_4} = -\frac{Q}{2C_4} \Rightarrow S_{C_4}^Q = S_{R_1, R_3, R_5}^Q = -\frac{1}{2}$$

### 11.58

charge transferred  $\Rightarrow Q = CV$

$$= 10^{-12}(1)$$

$$= 1 \text{ pC}$$

For  $f_O = 100 \text{ kHz}$ , average current is given by:

$$I_{\text{AVE}} = \frac{Q}{T} = 1 \text{ pC} \times \frac{1}{100 \times 10^3}$$

$$= 0.1 \mu\text{A}$$

For each clock cycle, the output will change by the same amount as the change in voltage across  $C_2$ :

$$\therefore \Delta V = Q/C_2 = \frac{1 \text{ pC}}{10 \text{ pF}} = 0.1 \text{ V}$$

For  $\Delta V = 0.1 \text{ V}$  for each clock cycle, the amplifier will saturate in

$$v_{\text{cycles}} = \frac{10 \text{ V}}{0.1 \text{ V}} = 100 \text{ cycles}$$

$$\text{slope} = \frac{\Delta V}{\Delta t} = \frac{10 \text{ V}}{(100 \text{ cycles})(1/100 \times 10^3)} \\ = 10^4 \frac{\text{V}}{\text{s}}$$

### 11.59

$$f_C = 400 \text{ kHz} \quad f_O = 10 \text{ kHz} \quad Q = 20$$

$$C_1 = C_2 = 20 \text{ pF} = C$$

$$C_3 = C_4 = \omega_o T_C C \\ = 2\pi(10^4) \frac{1}{400 \times 10^3} 20 \times 10^{-12}$$

$$= 3.14 \text{ pF}$$

$$C_5 = \frac{\omega_o T_C C}{Q}$$

$$= \frac{C_3}{Q} = 0.157 \text{ pF}$$

$$C_6 = \frac{\omega_o T_C C}{Q} \times \text{centre frequency gain}$$

$$= 0.157 \text{ pF}$$

Note that the clock frequency has doubled. Hence the period,  $T_C$ , is halved. Therefore, for the same integratity capacitors, the resistors (switched capacitors) will change by the factor of 2. so compensates for this by changing the switched caps by a factor of 1/2.

### 11.60

$$\text{for } Q = 40$$

$$f_C = 200 \text{ kHz} \quad f_O = 10 \text{ kHz}$$

$$C_1 = C_2 = 20 \text{ pF} = C$$

$$C_3 = C_4 = \omega_o T_C C$$

$$= 2\pi(10^4) \left( \frac{1}{200 \times 10^3} \right) 20 \times 10^{-12}$$

$$= 6.28 \text{ pF}$$

$$C_5 = \frac{\omega_o T_C C}{Q} = \frac{C_3}{Q} = 0.157 \text{ pF}$$

$$C_6 = \frac{\omega_o T_C C}{Q} = C_5 = 0.157 \text{ pF}$$

### 11.61

$$\omega_o = 10^4, Q = 1/\sqrt{2}, f_C = 100 \text{ kHz}$$

$$\text{DC gain} \Rightarrow \frac{R_4}{R_6} \Rightarrow \frac{C_6}{C_4} = 1$$

$$C_1 = C_2 = 10 \text{ pF}$$



$$C_3 = C_4 = C_6 = \omega_o T_C C$$

$$= 10^4 \left( \frac{1}{100 \times 10^3} \right) 10 \times 10^{-12}$$

$$= 1 \text{ pF}$$

$$C_5 = C_4/Q = 1.41 \text{ pF}$$

11.62

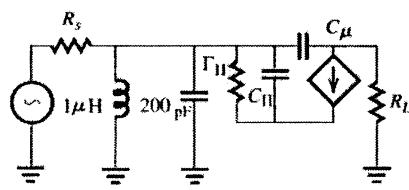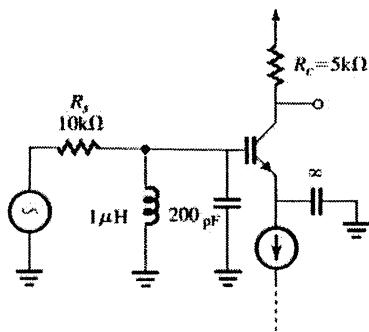

$$r_e = 25 \Omega, C_\mu = 1 \text{ pF}, C_\pi = 10 \text{ pF},$$

$$\beta = 200$$

$$r_\pi = (\beta + 1)\sqrt{2} = 5.025 \text{ k}\Omega$$

From base to collector

$$\frac{V_C}{V_b} = -\frac{\beta}{\beta + 1} \cdot \frac{R_2}{r_e} = -199 = k$$

Total capacitance at base

$$C_T = C_\pi + 200 \text{ p} + C_\mu(1 - k) \text{ Miller Effect}$$

$$= 10 + 200 \text{ p} + 1(1 + 199)$$

$$= 410 \text{ pF}$$

$$\therefore \omega_o = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{10^{-6} \times 410 \times 10^{-12}}} =$$

$$= 49.4 \times 10^6 \text{ rad/s}$$

$$\text{centre frequency gain} = \frac{r_\pi}{R_s + r_\pi} \cdot k$$

$$= \frac{5.025}{10 + 5.025} \times -199$$

$$= -66.6 \text{ V/V}$$

$$BW = \frac{1}{RC}$$

$$= \frac{1}{(R_s \parallel r_\pi) 410 \text{ pF}}$$

$$= 729 \times 10^3 \text{ rad/s}$$

$$Q = \frac{\omega_o}{BW}$$

$$= 49.4 / 7293$$

$$= 67.7$$

11.63

$$Q_o = \frac{R_p}{\omega_o L} \Rightarrow R_p = Q_o \omega_o L$$

$$= 200(2\pi 10^6)(10 \times 10^{-6})$$

$$= 12.57 \text{ k}\Omega$$

$$\omega_o = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{\omega_o^2 L}$$

$$= \frac{1}{(2\pi 10^6)^2 10 \times 10^{-6}}$$

$$= 2.533 \text{ nF}$$


$$B = \frac{1}{RC}$$

$$R_r = \frac{1}{(2\pi \times 10 \times 10^3)(2.533 \times 10^{-9})} = 6.283 \text{ k}\Omega$$

$$\therefore \frac{1}{R_1 + R_p + R_r}$$

$$\Rightarrow R_1 = 12.57 \text{ k}\Omega \text{ ie. } R_1 \parallel R_p = R_r$$

11.64

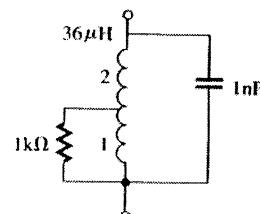

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$= (2\pi(36 \times 10^{-6})10^{-9})^{-1}$$

$$= 838.8 \text{ kHz}$$

$$R_p = n^2 R$$


$$= 9 (1 \text{ k}\Omega)$$

$$= 9 \text{ k}\Omega$$

$$Q = R_p \omega_o L$$

$$= \frac{9 \times 10^3}{2\pi 838.8 \times 10^3 \times 36 \times 10^{-6}} \\ = 47.4$$

11.65

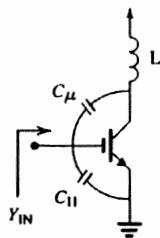

$$\text{for } \omega C_\mu \ll \frac{1}{WL}$$

$$\therefore \omega^2 \ll \frac{1}{LC_\mu}$$

i.e. well below resonance

$$\therefore \text{gain} = -g_m(j\omega L)$$

$$\therefore y_{in} = \frac{1}{r_\pi} + j\omega C_\pi + j\omega C_\mu(1 + g_m j\omega L) \\ = \left(\frac{1}{r_\pi} - \omega^2 g_m C_\mu\right) + j\omega(C_\pi + C_\mu)$$

AS REQUIRED!

11.66

$$T(S) = \frac{a_1 s}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2}$$

$$T(j\omega) = \frac{j a_1 \omega}{\omega_o^2 - \omega^2 + \frac{j \omega \omega_o}{Q}}$$

$$T(j\omega_o) = \frac{j a_1 \omega_o}{j \omega_o^2 Q} = \frac{a_1 Q}{\omega_o}$$

$$|T(j\omega)| = a_1 \omega \left[ (\omega_o^2 - \omega^2)^2 + \left(\frac{\omega \omega_o}{Q}\right)^2\right]^{-\frac{1}{2}} \\ = \frac{a_1 \omega Q / \omega \omega_o}{\sqrt{1 + Q^2 \left(\frac{\omega_o^2 - \omega^2}{\omega_o \omega}\right)^2}}$$

$$\text{Now } \omega = \omega_o + \delta\omega, \frac{\delta\omega}{\omega_o} \ll 1$$

$$\text{and } \omega^2 \geq \omega_o^2 \left(1 + \frac{2\delta\omega}{\omega_o}\right)$$

$$\text{so } \omega_o^2 - \omega^2 = -2\delta\omega \omega_o$$

$$\therefore |T(j\omega)| = \frac{a_1 Q / \omega_o}{\sqrt{1 + Q^2 \left(\frac{2\delta\omega}{\omega_o}\right)^2}}$$

$$\text{for } Q \gg 1: Q^2 \left(\frac{2\delta\omega}{\omega}\right)^2 \cong Q^2 \left(\frac{2\delta\omega}{\omega_o}\right)^2$$

$$\therefore \omega \approx \omega_o !$$

$$\Rightarrow |T(j\omega)| \cong \frac{|T(j\omega_o)|}{\sqrt{1 + Q^2 \left(\frac{2\delta\omega}{\omega_o}\right)^2}}$$

$$= \frac{|T(j\omega_o)|}{\sqrt{1 + 4Q^2 \left(\frac{\delta\omega}{\omega_o}\right)^2}}$$

For N bandpass sections, synchronously tuned in cascade, half power is given by:

$$\left( \frac{1}{\sqrt{1 + 4Q^2 \left(\frac{\delta\omega}{\omega_o}\right)^2}} \right)^N = \frac{1}{\sqrt{2}}$$

$$\left( 1 + 4Q^2 \left(\frac{\delta\omega}{\omega_o}\right)^2 \right)^N = 2$$

$$4Q^2 \left(\frac{\delta\omega}{\omega_o}\right)^2 = 2^{1/N} - 1$$

$$\delta\omega = \frac{\omega_o}{2Q} \sqrt{2^{1/N} - 1}$$

$\therefore$  Bandwidth:

$$B = 28\omega = \frac{\omega_o}{Q} \sqrt{2^{1/N} - 1}$$

11.67

For first order lowpass:

$$T(S) = \frac{\omega_o}{S + \omega_o} \quad |T(j\omega)| = \frac{\omega_o}{\sqrt{\omega^2 + \omega_o^2}}$$

for a bandpass response around  $\omega_o$  with

$$\omega_o = \frac{\omega_o}{2Q} :$$

$$|T(j\omega)| \cong \frac{\omega_o / 2Q}{(\delta\omega)^2 + \left(\frac{\omega_o}{2Q}\right)^2}$$

$$= \frac{\omega_o / 2Q}{\frac{\omega_o}{2Q} \sqrt{\left(\frac{2Q}{\omega_o}\right)^2 (\delta\omega)^2 + 1}}$$

$$= \frac{1}{\sqrt{1 + 4Q^2 (\delta\omega / \omega_o)^2}}$$

Now at  $\omega = \omega_0$  or  $\delta\omega = 0$

$|r(j\omega_0)| = 1$ , then

$$T(j\omega) = \frac{|T(j\omega_0)|}{\sqrt{1 + 4Q^2\left(\frac{\delta\omega}{\omega_0}\right)^2}}$$

Part (b)

For N synchronously tuned sections in cascade;  
3 dB bandwidth is given by:

$$(|T|/|T_B|)^N = \frac{1}{\sqrt{2}}$$

$$(|T|/|T_B|)^2 = \frac{1}{2^{1/N}} \text{ OR}$$

$$1 + 4Q^2\left(\frac{\delta\omega}{\omega_0}\right)^2 = 2^{1/N} \text{ OR}$$

$$2\delta\omega = \frac{\omega_0}{Q} \sqrt{2^{1/N} - 1} \quad (16.110)$$

Thus:  $|T(j\omega)|_{\text{overall}} = |T(j\omega)|^N$

$$= \frac{|T(j\omega)|_{\text{overall}}}{\left[1 + 4Q^2\left(\frac{\delta\omega}{\omega_0}\right)^2\right]^{N/2}}$$

NOTE

$$\begin{aligned} Q &= \frac{\omega_0}{Q} \sqrt{2^{1/N} - 1} \\ &= \frac{|T(j\omega_0)|_{\text{overall}}}{\left[1 + 4 \frac{\omega_0^2}{B^2} (2^{1/N} - 1) \left(\frac{\delta\omega}{\omega_0}\right)^2\right]^{\frac{N}{2}}} \\ &= \frac{|T(j\omega_0)|_{\text{overall}}}{\left[1 + 4 (2^{1/N} - 1) \left(\frac{\delta\omega}{B}\right)^2\right]^{\frac{N}{2}}} \end{aligned}$$

Part (c)(i)

for bandwidth =  $2B$ , i.e.  $\delta\omega = \pm B$

$$\begin{aligned} Att &= -20\log(1 + (2^{1/N} - 1)(1))^{-N/2} \\ &= -10N \log(1 + 2^{2+1/N} - 4) \\ &= 10N \log(2^{2+1/N} - 3) \end{aligned}$$

N	1	2	3	4	5
Att(dB)	6.70	8.49	9.28	9.79	10.13

Part (ii)

3 dB bandwidth  $\delta\omega = \pm B/2$

$$30 \text{ dB bandwidth } \frac{\delta\omega}{B} = x$$

$$-30 = -20 \frac{N}{2} \log(1 + 4(2^{1/N} - 1)x^2)$$

$$3 = N \log(1 + 4(2^{1/N} - 1)x^2)$$

$$x = \left[ \frac{10^{3/N} - 1}{4(2^{1/N} - 1)} \right]^{1/2}$$

Ratio of 30 dB to 3 dB

$$BW = \frac{2Bx}{B} = 2x$$

N	1	2	3	4	5
Ratio	31.6	8.6	5.7		4.5

## 11.6.8

(a) For the narrowband approximation variation of  $\Omega$  around O is equivalent to  $\omega$  around  $\omega_0$ . Thus, a low-pass maximally flat filter of bandwidth  $B/2$  and order N for which

$|T| = [(1 + (\Omega/B/2)^{2N})]^{-1/2}$  is transformed to a band-pass maximally flat filter of bandwidth  $B/2$  and order  $2N$ , and centre frequency  $\omega_0$  for which:

$$|T| = \left(1 + \left(\frac{\delta\omega}{B/2}\right)^{2N}\right)^{-1/2}$$

(b) For bandwidth  $2B$ ,  $\delta\omega = B$  &

$$\begin{aligned} |T| &= \left(1 + \left(\frac{B}{B/2}\right)^{2N}\right)^{-1/2} \\ &= (1 + 2^{2N})^{-1/2} \text{ thus:} \end{aligned}$$

N	1	2	3	4	5
T	0.447	0.242	0.124	0.062	0.031
T  <sub>dB</sub>	-6.99	-16.3	-18.1	-24.1	-30.1

For 30 dB bandwidth,

$$\begin{aligned} -30 &= 20 \log x \Rightarrow x = 10^{-3/2} \\ &= \frac{1}{31.6} \end{aligned}$$

$$\left(\frac{\delta\omega}{B/2}\right)^{2N} = (31.6)^2$$

$$\left(\frac{\delta\omega}{B/2}\right)^{2N} = 999 - 1 = 998$$

Now the ratio of 30 dB to 3 dB bandwidth is

$$\text{ratio} = \frac{2\delta\omega}{B} = \frac{\delta\omega}{B/2} = 998^{1/2N}$$

N	1	2	3	4	5
ratio	31.6	5.62	3.16	2.37	1.99

11.69

$$A_{\max} = 3 \text{ dB} \Rightarrow \epsilon = \sqrt{10^{A_{\max}/10} - 1} \approx 1$$

Poles of lowpass prototype are given by

Poles:  $-\omega_p, \omega_p(-1/2 \pm j\sqrt{3}/2)$

Make  $\omega_p = B/2$

$$\Rightarrow \text{poles: } \left\{ \frac{-B}{2}, \frac{+B}{2} \left( -\frac{1}{2} \pm j\frac{\sqrt{3}}{2} \right) \right\}$$

Using the low-pass to bandpass transformation:

Poles of the bandpass filter:

$$\frac{-B}{2} \pm j\omega_o$$

$$\frac{-B}{4} \pm j\left(\frac{\sqrt{3}}{4}B + \omega_o\right) \text{ and}$$

$$\frac{-B}{4} \pm j\left(\frac{\sqrt{3}}{4}B - \omega_o\right)$$


For the three circuits:

$$(1) \omega_{o1} = \omega_o, B_1 = B, Q_1 = \omega_o/B$$


$$(2) \omega_{o2} \equiv \frac{\sqrt{3}}{4}B + \omega_o, B_2 = \frac{B}{2}, Q_2 \equiv \frac{2\omega_o}{B}$$

$$(3) \omega_{o3} \equiv \frac{\sqrt{3}}{4}B - \omega_o, B_3 = \frac{B}{2}, Q_3 \equiv \frac{2\omega_o}{B}$$

x

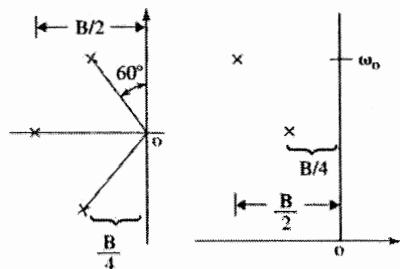

### 12.1

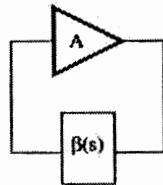

$$A = A_0 > 0$$

$$\beta(s) = \frac{K \frac{\omega_o}{Q} s}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2}$$

$$(a) \text{ for oscillations } 1 - A\beta(s) = 0$$

$$A_0 K \frac{\omega_o}{Q} s = s^2 + s \frac{\omega_o}{Q} + \omega_o^2$$

$$\omega_o^2 - \omega^2 = j\omega \left( \frac{\omega_o}{Q} \right) (A_0 K - 1)$$

at the freq. of oscillation, both Real & imaginary parts are 0.

$$\therefore \omega = \omega_o \text{ & } A_0 K = 1$$

(b)

$$L(j\omega) \stackrel{\Delta}{=} A\beta(j\omega) = \frac{AK \frac{\omega_o}{Q} j\omega}{(\omega_o^2 - \omega^2) + j\omega \left( \frac{\omega_o}{Q} \right)}$$

$$\therefore \phi(\omega) = 90^\circ - \tan^{-1} \left( \frac{\omega \omega_o / Q}{\omega_o^2 - \omega^2} \right)$$

$$\text{Now } \frac{\partial}{\partial x} \tan^{-1} v = \frac{1}{1+v^2} \cdot \frac{\partial v}{\partial x}$$

$$\therefore \frac{\partial \phi}{\partial \omega} = \frac{1}{1 + \left( \frac{\omega \omega_o / Q}{\omega_o^2 - \omega^2} \right)^2} \cdot \frac{\partial}{\partial \omega} \left( \frac{\omega \omega_o / Q}{\omega_o^2 - \omega^2} \right)$$

$$= \frac{-(\omega_o^2 - \omega^2)^2}{(\omega_o^2 - \omega^2) + \left( \frac{\omega \omega_o / Q}{\omega_o^2 - \omega^2} \right)^2} \cdot \left[ \frac{\frac{\omega_o(\omega_o^2 - \omega^2)}{Q} - 2\omega \frac{\omega \omega_o}{Q}}{(\omega_o^2 - \omega^2)^2} \right]$$

$$\left. \frac{d\phi}{d\omega} \right|_{\omega = \omega_o} = \frac{-1}{\omega_o^4 / Q^2} \cdot \frac{2\omega_o^3}{Q}$$

$$= -\frac{2Q}{\omega_o}$$

$$(c) \Delta \omega_o = \frac{\Delta \phi}{\partial \phi / \partial \omega} = \frac{\Delta \phi}{-2Q / \omega_o}$$

$$= \frac{-\Delta \phi \omega_o}{2Q}$$

$\therefore$  Per unit change in  $\omega_o$  is given by

$$\frac{\Delta \omega_o}{\omega_o} = \frac{-\Delta \phi}{2Q}$$

### 12.2

For the circuit of problem 12.1, the poles, which are the zeros of the characteristic equation, are given by:

$$1 - L(S) = 0$$

$$L(S) = 1$$

$$\frac{AK \left( \frac{\omega_o}{Q} \right) s}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2} = 1$$

$$s^2 + s \frac{\omega_o}{Q} + \omega_o^2 - AK \left( \frac{\omega_o}{Q} \right) s = 0$$

$\therefore$  Poles are at :

$$s = \frac{-\frac{\omega_o}{Q}(1 - AK) \pm \sqrt{\left( \frac{\omega_o}{Q} \right)^2 (1 - AK)^2 4\omega_o^2}}{2}$$

$$= -\omega_o \left[ \frac{1 - AK}{2Q} \pm \sqrt{\left( \frac{1 - AK}{2Q} \right)^2 - 1} \right]$$

$$= -\omega_o \left( \frac{1 - AK}{2Q} \right) \left[ 1 \pm j \sqrt{\left( \frac{2Q}{1 - AK} \right)^2 - 1} \right]$$

Radial distance of  $\omega_o \Rightarrow$

$$|S|^2 = \omega_o^2 \left( \frac{1 - AK}{2Q} \right)^2 \left[ 1 + \left( \frac{2Q}{1 - AK} \right)^2 - 1 \right]$$

$$= \omega_o^2$$

$\therefore |S| = \omega_o$  independent of A or K !

(a) For poles on jw-axis  $\Rightarrow$  real part = 0


$$\therefore -(1 - AK) = 0 \Rightarrow AK = 1$$

(b) For poles in RHS  $\Rightarrow$  Real Part  $> 0$

$$-(1 - AK) > 0$$

$$AK > 1$$

12.3

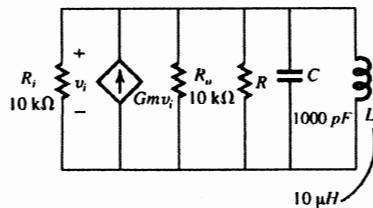

$$\text{For resonator: } \omega_o = \frac{1}{\sqrt{LC}} = 10^7 \frac{\text{rad}}{\text{s}}$$

$$\frac{\omega_o}{Q} = \frac{1}{RC}$$

$$R = \frac{Q}{\omega_o C} = \frac{100}{10^7 \times 1000 \times 10^{-12}} = 10 \text{ k}\Omega$$

Oscillation will occur at  $\omega_o = 10^7 \frac{\text{rad}}{3}$

when  $G_m = (R_i \parallel R_o \parallel R) = 1$  i.e. gain = 1

$$\therefore G_m = \frac{1}{10 \text{ K} \parallel 10 \text{ K} \parallel 10 \text{ K}} = \frac{3}{10^4} = 300 \frac{\mu\text{A}}{\text{V}}$$

12.4

At  $\omega_o A\beta = 1$

If  $\beta(\omega_o)$  is -20 dB with a phase shift of 180° then clearly A should have a gain of 20 dB (i.e.  $A(\omega_o) = 10$ ) with a phase shift of ±180°  
i.e.  $A = -10$

12.5

$$L_- = -V \frac{R_3}{R_2} - V_D \left(1 + \frac{R_3}{R_2}\right)$$

$$6 = 10 \frac{R_3}{R_2} + 0.7 \left(1 + \frac{R_3}{R_2}\right)$$

$$= 10.7 \frac{R_3}{R_2} + 0.7$$

$$\frac{R_3}{R_2} = 0.495 \text{ By symmetry } \frac{R_4}{R_3} = 0.495$$

Use  $R_2 = R_3 = 10 \text{ k}\Omega$


$\therefore R_3 = R_4 \approx 5 \text{ k}\Omega$

Slope of limiting characteristic

$$\frac{R_4}{R_3} = 0.1$$

$$\therefore R_1 = \frac{1}{0.1} R_4 = 50 \text{ k}\Omega$$

12.6

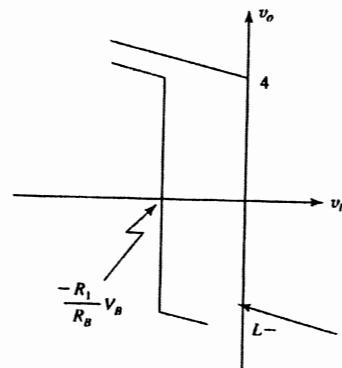

For  $V_B$  connected via  $R_B$  to the virtual ground, a current  $= \frac{V_B}{R_B}$  flows into the node. To compensate,  $v_I$  must be moved by  $\Delta v_I$ , in a direction opposite to  $V_B$ , to produce a current  $=$

$$\frac{\Delta v_I}{R_1} = \frac{-v_B}{R_B}$$

$$\therefore \Delta v_I = -\frac{R_1}{R_B} V_B$$

$v_D = 0 \sim$  assumed

$$L_- = -5 = -15 R_3 / R_2$$

$$\frac{R_3}{R_2} = \frac{1}{3} = R_4 / R_5$$

Given  $R_{in} = 100 \text{ k}\Omega \Rightarrow R_1 = 100 \text{ k}\Omega$

Slope =  $R_4 / R_1 \leq 0.05$

$$R_4 \leq R_1 \times 0.05$$

$R_4 \leq 5 \text{ k}\Omega \Rightarrow \text{Let } R_4 = 4.3 \text{ k}\Omega$

$$\therefore R_3 = R_4 \Rightarrow R_3 = 4.3 \text{ k}\Omega$$

$$R_2 = R_3 = 3R_4 = 12.9 \text{ k}\Omega$$

For standard resistance values:

$$R_2 = R_3 = 13 \text{ k}\Omega$$

$$\therefore L = -15 \frac{R_3}{R_2} = -15 \times \frac{4.3}{12.9}$$


$$= -4.96 \text{ V} \cong -5 \text{ V}$$

Offset is +5 V  $\Rightarrow$  use  $V_B = -15 \text{ V}$

$$\text{and } S = R_1 / R_B = 15$$

$$\therefore R_B = 3R_1 = 300 \text{ k}\Omega$$

### 12.7

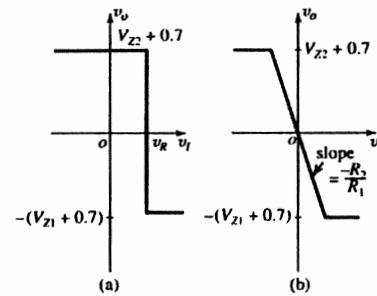

### 12.8

$$\begin{aligned} \frac{V_o}{V_u} &= \frac{1/\text{sc} \parallel R}{1/\text{sc} \parallel R + 1/\text{sc} + R} \\ &= \frac{(R/\text{sc}) / \left( \frac{1}{\text{sc}} + R \right)}{\left( \frac{R}{\text{sc}} \right) + \frac{1}{\text{sc}} + R} \\ &= \frac{\frac{R}{\text{sc}}}{\frac{R}{\text{sc}} + \left( \frac{1}{\text{sc}} + R \right)^2} \times \frac{\text{sc}^2 C^2}{\text{sc}^2 C^2} \\ &= \frac{SCR}{SCR + (1 + SCR)^2} \\ &= \frac{SCR}{SCR + (1 + 2SCR) + S^2 C^2 R^2} \\ &= \frac{\frac{1}{RC} S}{S^2 + S \frac{3}{RC} + \frac{1}{R^2 C^2}} \end{aligned}$$

Note  $\frac{V_o}{V_u}$  has zeros at 0 and  $\infty$

i.e. A Band pass!

$$\omega_o^2 = \frac{1}{R^2 C^2} \Rightarrow \omega_o = \frac{1}{RC}$$

$$\frac{\omega_o}{Q} = \frac{3}{RC} \Rightarrow Q = \frac{1}{3}$$

For centre frequency gain:

$$S = j\omega_o = j/RC$$

$$\begin{aligned} \left. \frac{V_o}{V_u} \right|_{S=j/RC} &= \frac{\frac{1}{RC} j/RC}{-\frac{1}{R^2 C^2} + \frac{3}{RC} \left( \frac{j}{RC} \right) + \frac{1}{R^2 C^2}} \\ &= \frac{1}{3} = \text{centre freq. gain} \end{aligned}$$

### 12.9

$$L(j\omega) = \frac{1 + R_2/R_1}{3 + j(WCR - \frac{1}{WCR})} \quad \text{Eq(17.11)}$$

$$\phi(\omega) = -\tan^{-1} \left( \frac{WCR - \frac{1}{WCR}}{3} \right)$$

$$\text{using } \frac{\partial \tan^{-1} v}{\partial x} = \frac{1}{1 + v^2} \frac{\partial v}{\partial x}$$

$$\frac{\partial \phi}{\partial \omega} = \frac{-1}{1 + \left( \frac{WCR - \frac{1}{WCR}}{3} \right)^2} \cdot \frac{1}{3} \left( CR + \frac{1}{W^2 CR} \right)$$

$$\left. \frac{\partial \phi}{\partial \omega} \right|_{\omega=\frac{1}{RC}} = \frac{-1}{3} (CR + CR) = \frac{-2}{3} CR$$

for  $\Delta\phi = -0.1 \text{ rad}$

$$\begin{aligned} \Delta\omega_o &= \frac{\Delta\phi}{\partial \phi / \partial \omega} = \frac{-0.1}{-2/3 \frac{1}{\omega_o}} \\ &= 0.15 \omega_o \end{aligned}$$

∴ New frequency of oscillation

$$= 1.15 \omega_o = \frac{1.15}{RC}$$

### 12.10

$$L(s) = \frac{1 + R_2/R_1}{3 + SCR + 1/SCR}$$

Poles of closed loop given by:  $L(S) = 1$

$$1 + R_2/R_1 = 3 + SCR + \frac{1}{SCR}$$

$$O = S^2 + \frac{S}{RC} \left( 2 - \frac{R_2}{R_1} \right) + \frac{1}{R^2 C^2}$$

$$Q = \frac{1}{(2 - R_2/R_1)}$$

for  $Q = \infty$  - poles on jω axis

$$-R_2/R_1 = 2$$

for poles in R.H.P.  $R_2/R_1 > 2$

### 12.11

assuming resistance of limiting network is very low

At positive peak

$$v_o = \left( \frac{1 + 20.3}{10} K \right) v_o = 3.03 v_o \quad (1)$$

$$v_o - \left[ \frac{R_5}{R_5 + R_6} \cdot (v_o - (-15)) \right] - 0.7 = v_f \quad (2)$$

Now for  $10V_{p-p}$  out

$$v_o = 5 V$$

$$\dot{v}_o = \frac{5}{3.03} = 1.65 V$$

using (2)  $R_5 = 1 k\Omega$

$$5 - \left( \frac{1}{1 + R_6} \cdot (V_o + 15) \right) - 0.7 = 1.65$$

$$\frac{20}{1 + R_6} = 2.65$$

$$R_6 = \frac{20}{2.65} - 1$$

$$R_6 = 6.5 k\Omega = R_3$$

If  $R_3 = R_6 = \infty$  from (2)


$$v_o - \left( \frac{1}{1 + \infty} (V_o + 15) \right) - 0.7 = \frac{v_o}{3.03}$$

$$v_o - 0.7 = \frac{v_o}{3.3}$$

$$v_o = 1.04 V$$

∴ output is  $2 v_o = 2.08 V_{p-p}$ .

### 12.12

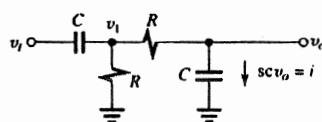

$$\frac{v_i - v_o}{R} = SCR v_o \Rightarrow v_i - v_o(1 + SCR)$$

$\Sigma I$  at  $v_i$

$$\frac{v_i}{R} + SC(v_i - v_i) + SCR v_o = 0$$

$$v_o(1 + SCR) + SCR(v_o + v_o SCR) - SCR v_i +$$

$$SCR v_o = 0$$

$$v_o(1 + SCR + SCR + S^2 C^2 R^2 + SCR) = SCR v_i$$

$$\beta(s) \triangleq \frac{v_o}{v_i} = \frac{SCR}{S^2 C^2 R^2 + 3SCR + 1}$$

$$= \frac{1}{3 + SCR + 1/(SCR)}$$

$$A = 1 + R_2/R_1$$

$$\beta(j\omega) = \frac{1}{3 + j(\omega CR - \frac{1}{\omega CR})}$$

Zero phase when  $\omega CR = \frac{1}{\omega CR}$

$$\omega = \frac{1}{CR}$$


$$|\beta(W = 1/RC)| = \frac{1}{3}$$

for oscillations  $1 + R_2/R_1 \geq 3 \Rightarrow \frac{R_2}{R_1} \geq 2$

$$L(s) = A\beta = \frac{1 + R_2/R_1}{3 + SCR + SCR}$$

$$L(j\omega) = \frac{1 + R_2/R_1}{3 + j(WCR - \frac{1}{WCR})}$$

### 12.13

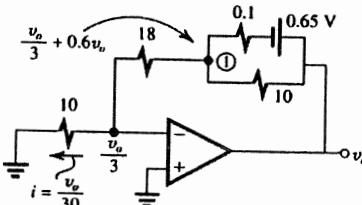

$\Sigma I$  at node 1

$$\frac{v_o}{30} + 0.6v_o = \frac{v_o}{10}$$

$$+ v_o - 0.65 - \frac{v_o}{3} - 0.65 = \frac{0.1}{0.1}$$

$$0.00666v_o + 0.666v_o - 0.65$$

$$v_o = 10.156 V$$

∴ Max. output =  $20.3 V_{p-p}$

### 12.14

$$\omega_o = \frac{1}{RC} = 2\pi 10^4 \quad R = 10 k\Omega$$

$$C = \frac{1}{10^4 \times 2\pi \times 10^4} \Rightarrow C \approx 1.6 nF$$

$$\beta(j\omega) = \left[ 3 + j\left(\omega CR - \frac{1}{\omega CR}\right) \right]^{-1}$$

$$\therefore \phi(\omega) = -\tan^{-1} \left( \frac{WCR - \frac{1}{WCR}}{3} \right)$$

using  $\frac{\partial \tan^{-1} v}{\partial x} = \frac{1 - \frac{\partial v}{\partial x}}{1 + v^2}$  we get

$$\frac{\partial \phi(\omega)}{\partial \omega} = \frac{-1}{1 + \left( \frac{WCR - \frac{1}{WCR}}{3} \right)^2} \left[ \frac{RC + 1/W^2 RC}{3} \right]$$


$$\text{At } \omega = \omega_o = \frac{1}{RC} \quad \frac{\partial \phi(\omega)}{\partial \omega} = \frac{-2}{3} RC$$

Now  $5.7^\circ \approx 0.1 \text{ rad}$  (lag  $\approx -0.1 \text{ rad}$ )

$$\therefore \Delta \omega_o = \frac{-0.1}{-2/3 RC} = 0.15 \omega_o = 1.5 \text{ kHz}$$

$\therefore$  New frequency of oscillation  $= 8.5 \text{ kHz}$

To restore Operation:

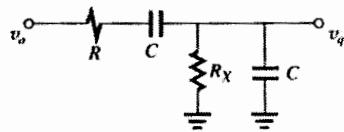

$$\begin{aligned} \beta(s) &= \frac{Rx \parallel \frac{1}{SC}}{Rx \parallel \frac{1}{SC} + R + \frac{1}{SC}} \\ &= \frac{\frac{Rx/SC}{Rx+1/SC}}{\frac{Rx+1/SC}{Rx+1/SC} + R + \frac{1}{SC}} \\ &= \frac{Rx/SC}{Rx/SC + RRx + \frac{R}{SC} + \frac{Rx}{SC} + \frac{1}{S^2 C^2}} \end{aligned}$$

$$\therefore \beta(s) = \frac{1}{2 + \frac{R}{Rx} + SCR + \frac{1}{SCRx}}$$

$$\phi = -\tan^{-1} \left( \frac{WCR - \frac{1}{WRC}}{2 + R/Rx} \right)$$

Now it is required that  $\phi = 5.7^\circ$  at  $\omega > \omega_o$ !

where  $\omega_o = 1/RC$

$$\therefore \omega_o RC = \frac{-1}{\omega_o Rx C} = \left( 2 + \frac{R}{Rx} \right) \tan^{-1}(-5.7)$$

$$1 - \frac{1}{\omega_o Rx C} = (2 + R/Rx)(-0.1)$$

$$1 + 0.2 = \frac{1}{\omega_o Rx C} - 0.1 \frac{R}{Rx}$$

$$Rx = \frac{1/\omega_o C - 0.1 R}{1.2}$$

given:

$$\omega_o = 2\pi 10^4$$

$$C = 1.6 \times 10^{-9}$$

$$R = 10^4$$

$$Rx = 7.5 \text{ k}\Omega$$

Now:


$$\begin{aligned} \beta(j\omega_o) &= \frac{1}{2 + 10/7.5 + j(1 - 1/\omega_o CRx)} \\ &= (3.333 - j0.326)^{-1} \end{aligned}$$

$$|\beta(j\omega_o)| = \frac{1}{3.35}$$

$\therefore 1 + R_2/R_1 = 3.35$  for oscillations

$$\frac{R_2}{R_1} = 2.35 \text{ (not 2 as before)}$$

## 12.15

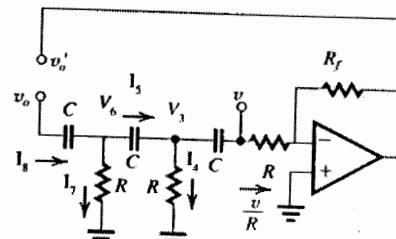

$$V_3 = v + \frac{1}{SCR} \frac{v}{R} = v \left( 1 + \frac{1}{SCR} \right)$$

$$I_4 = \frac{v \left( 1 + \frac{1}{SCR} \right)}{R} = \frac{v}{R} + \frac{v}{SCR^2}$$

$$I_5 = I_4 + \frac{v}{R} = \frac{2v}{R} + \frac{v}{SCR^2}$$

$$V_6 = V_3 + \frac{I_5}{sC}$$

$$= v + \frac{v}{SCR} + \frac{1}{sC} \left( 2 \frac{v}{R} + \frac{v}{SCR^2} \right)$$

$$V_6 = v + \frac{3v}{SCR} + \frac{v}{s^2 C^2 R^2}$$

$$I_7 = \frac{v}{R} + \frac{3v}{SCR^2} + \frac{v}{s^2 C^2 R^2}$$

12.16

$$I_8 = I_5 + I_1$$

$$I_8 = \frac{3v}{R} + \frac{4v}{sCR^2} + \frac{v}{s^2C^2R^3}$$

$$V_o = V_6 + \frac{I_8}{sC}$$

$$\begin{aligned} v_o &= v + \frac{3v}{sCR} + \frac{v}{s^2C^2R^2} + \frac{3v}{sCR} + \frac{4v}{s^2C^2R^2} + \frac{v}{s^3C^3R^3} \\ &= v + \frac{6v}{sCR} + \frac{5v}{s^2C^2R^2} + \frac{v}{s^3C^3R^3} \end{aligned}$$

Now loop gain =

$$L(s) = \frac{-v_o}{v_o}$$

$$v_o^l = \frac{R_f}{R} \cdot v$$

$$\begin{aligned} L(s) &= \frac{\frac{R_f}{R} \cdot v}{v \left( 1 + \frac{6}{sCR} + \frac{5}{s^2C^2R^2} + \frac{1}{s^3C^3R^3} \right)} \\ &= \frac{\frac{s^3R_f}{R}}{s^3 + \frac{6s^2}{RC} + \frac{5s}{C^2R^2} + \frac{1}{C^3R^3}} \\ L(j\omega) &= \frac{-j\omega^3 R_f / R}{\frac{1}{C^3R^3} - \frac{6\omega^2}{RC} + j\left(\frac{5\omega}{C^2R^2} - \omega^3\right)} \end{aligned}$$

$L(j\omega)$  is real if

$$\frac{6\omega^2}{RC} = \frac{1}{R^3C^3}$$


$$\omega_o = \frac{1}{\sqrt{6}RC}$$

$$\begin{aligned} L(j\omega_o) &= \frac{\omega_o^2 R_f / R}{-\omega_o^2 + 5/R^2C^2} \\ &= \frac{R_f / R \omega_o^2}{-\omega_o^2 + 30\omega_o^2} \\ &= \frac{R_f / R}{29} \end{aligned}$$

Now loop Gain = 1 if  $R_f = 29$  R

$\therefore$  Minimum value for  $R_f = 29$  R

$$f_o = \frac{0.065}{RC}$$

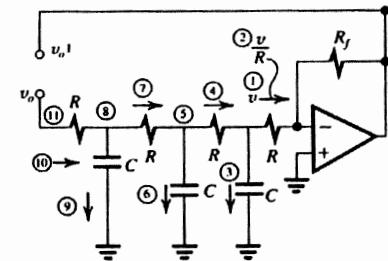

$$(3) i = sCv$$

$$(4) sCv = v/R$$

$$(5) v + \left( SCv + \frac{v}{R} \right) R = 2v + SCRv$$

$$(6) 2SCRv + S^2C^2Rv$$

$$(7) = (6) + (4) = 3SCRv + S^2C^2Rv + \frac{v}{R}$$

$$(8) 2v + SCRv + v + 3SCRv + S^2C^2R^2v = 3v + 4SCRv + S^2C^2R^2v$$

$$(9) 3SCRv + 4S^2C^2Rv + S^3C^3R^2v$$

$$(10) = (7) + (9)$$

$$= 6SCRv + 5S^2C^2Rv + \frac{v}{R} + S^3C^3R^2v$$

$$(11) = (8) + (10) \times R$$

$$v_o = 4v + 10SCRv + 6S^2C^2R^2v + S^3C^3R^3v$$

$$\begin{aligned} L(s) &= \frac{v_o^l}{v_o} = \frac{vR_f / R}{v(S^3C^3R^3 + 6S^2C^2R^2 + 10SCR + 4)} \\ &= \frac{R_f / R}{S^3C^3R^3 + 6S^2C^2R^2 + 10SCR + 4} \end{aligned}$$

$$L(j\omega) = \frac{R_f / R}{(4 - 6\omega^2C^2R^2) + j(10\omega CR + (\omega^3C^3R^3))}$$

$L(j\omega)$  is purely real if

$$10\omega CR = \omega^3C^3R^3$$

$$\omega_o = \frac{1}{\sqrt{10}RC}$$

Given  $R = 10$  kΩ,  $f_o = 10$  kHz.

$$\begin{aligned} C &= \frac{1}{\sqrt{10} \times 10^4 \times 2\pi 10^4} \\ &= 0.503 \text{ nF} \end{aligned}$$

Now,

$$|L(j\omega_o)| = \frac{R_f / R}{4 - 6\omega_o^2R^2C^2} \quad \text{sub for } \omega_o$$

$$= \frac{R_f/R}{4 - 6 \frac{1}{10 R^2 C^2} R^2 C^2}$$


$$= \frac{R_f/R}{4 - 6/10} \geq 1$$

$\therefore R_f/R \geq 3.4$

$R_f \geq 34 \text{ k}\Omega$

### 12.17

for 2<sup>nd</sup> indicator

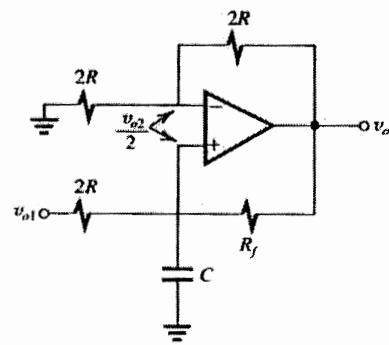

From the voltage divider around the upper branch:

$$v_+ = v_- = \frac{1}{2} v_{o2}$$

$\Sigma I = 0$  at the input

$$\frac{1}{2} \frac{v_{o2} - v_{o1}}{2R} + SC \frac{v_{o2}}{2} + \frac{\frac{v_{o2}}{2} - v_{o2}}{R_f} = 0$$

$$\frac{v_{o2} - 2v_{o1}}{2R} + SC v_{o2} - \frac{v_{o2}}{R_f} = 0 \quad R_f = \frac{2R}{H\Delta}$$

$$v_{o2} \left( \frac{1}{2} + SC - \frac{H\Delta}{2R} \right) = \frac{v_{o1}}{R}$$

$$v_{o2} \left( SCR - \frac{\Delta}{2} \right) = v_{o1}$$

$$\therefore \frac{v_{o2}}{v_{o1}} = \frac{1}{SCR - \Delta/2}$$

$$\text{Now: } \frac{v_{o1}}{v_s} = \frac{-1}{SCR}$$

$$\therefore L(S) = \frac{-1/SCR}{SCR - \Delta/2}$$

Characteristic equation  $L(s) = 1$

$$\therefore S^2 C^2 R^2 - \frac{SCR\Delta}{2} + 1 = 0$$

$\therefore$  Poles are

$$S_p = \frac{\frac{RC\Delta}{2} \pm \sqrt{\frac{R^2 C^2 \Delta^2}{4} - 4 C^2 R^2}}{2 R^2 C^2}$$

$$= \frac{\Delta/2 \pm 2j\sqrt{1 - (\Delta/4)^2}}{2RC}$$

$$\text{for } \Delta \ll 1 \quad \left(1 - \left(\frac{\Delta}{4}\right)^2\right)^{1/2} \approx \left(1 - \frac{1}{2}\left(\frac{\Delta}{4}\right)^2\right)$$

$$\therefore S_p = \left[ \Delta/2 \pm j2\left(1 - \frac{1}{2}\left(\frac{\Delta}{4}\right)^2\right) \right] \frac{1}{2RC}$$

$$= \frac{\Delta \pm j\left(2 - \left(\frac{\Delta}{4}\right)^2\right)}{2RC}$$

Now:

$$R_s [S_p] > 0 \Rightarrow \text{Poles in R.H.P.!}$$

for  $\Delta \ll 1$

$$S_p \approx \frac{\Delta/2 \pm j2}{2RC} = \frac{1}{RC} \left( \frac{\Delta}{4} \pm j \right) \text{ Q.E.D.}$$

### 12.18

The transmission of the filter normalized to the centre frequency,  $\omega_0$  is:

$$|T(j\omega)| = \frac{\omega \omega_0 / Q}{(\omega_0^2 - \omega^2)^2 + \frac{\omega^2 \omega_0^2}{Q^2}}$$

$$= \frac{(1/Q)(\frac{\omega_0}{\omega})}{\left(\left(\frac{\omega_0}{\omega}\right)^2 - 1\right)^2 + \frac{1}{Q^2}\left(\frac{\omega_0}{\omega}\right)^2}$$

Relative to the amplitude of the fundamental

(a) The second harmonic = 0

(b) The third harmonic

$$= \frac{\frac{1}{3} \times \frac{1}{20} \times \frac{1}{3}}{\frac{1}{3} \left(\frac{1}{9} - 1\right)^2 + \left(\frac{1}{20}\right)^2 \left(\frac{1}{9}\right)} = 6.25 \times 10^{-3}$$

(c) The fifth harmonic

$$= \frac{\frac{1}{5} \times \frac{1}{20} \times \frac{1}{5}}{\frac{1}{5} \left(\frac{1}{25} - 1\right)^2 + \left(\frac{1}{20}\right)^2 \left(\frac{1}{25}\right)} = 2.08 \times 10^{-3}$$

(d) The 4<sup>th</sup> harmonic = 6<sup>th</sup> = 10<sup>th</sup> = 0

7<sup>th</sup> harmonic =  $1.04 \times 10^{-3}$

9<sup>th</sup> harmonic =  $0.625 \times 10^{-3}$


$\therefore \frac{\text{RMS of 2<sup>nd</sup> to 10<sup>th</sup> harmonic}}{\text{RMS of fundamental}}$  is

$$[6.25^2 + 2.08^2 + 1.04^2 + 0.625^2]^{1/2} \times 10^{-3}$$

$$= 6.7 \times 10^{-3} \text{ OR } 0.7\%$$

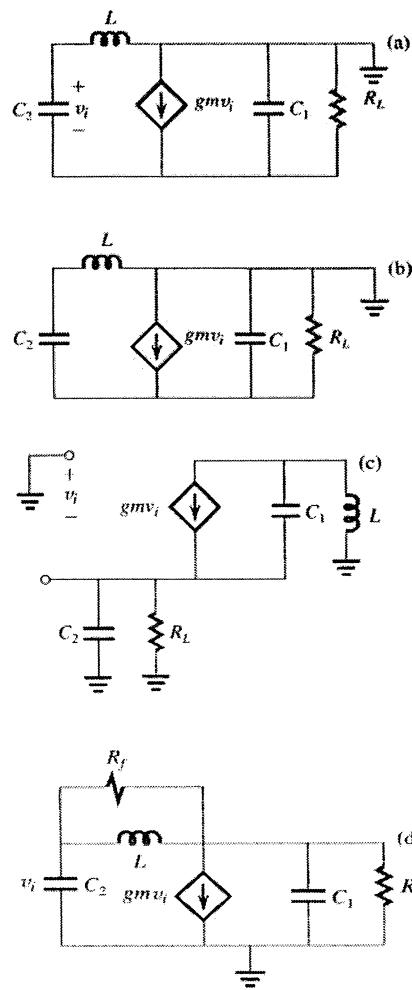
### 12.19

Consider the small signal models for each circuit. Assume  $r_o$  very large:



Given  $R_f \gg \omega_0 L$ , circuits (a), (b) and (d) are the same except for the reference (ground) node.

For circuit (a), (b) & (d)

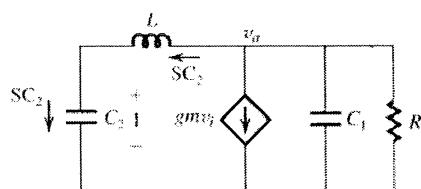

-Break the loop at  $v_i$  and assume unit return.

$$v_o = 1 + SC_2 sL$$

$$= 1 + S^2 C_2 sL$$

$$\Sigma I = 0 \text{ at } v_o$$

$$g_m + SC_2 + SC_1(1 + S^2 C_2 sL) + \frac{(1 + S^2 C_2 sL)}{R} = 0$$

$$\therefore g_m + 1/R + S(C_1 + C_2) + \frac{S^2 C_2 L}{R} + S^3 C_2 sL = 0$$

This is the characteristic equation.

For  $s = j\omega$ :

$$g_m + \frac{1}{R} - \frac{\omega^2 C_2 L}{R} + j((C_1 + C_2)\omega - \omega^3(C_1 C_2 L)) = 0$$

IMAGINARY PART = 0:

$$C_1 + C_2 = \omega^2 C_1 + C_2 L$$

$$\omega = \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}} \equiv \text{Frequency of Oscillation}$$


REAL PART = 0

$$g_m + \frac{1}{R} = \frac{\omega^2 C_2 L}{R}$$

$$g_m R = \left(\frac{C_1 + C_2}{C_1 C_2 L}\right) C_2 L - 1$$

$$g_m R = \frac{C_2}{C_1} \equiv \text{LIMIT ON GAIN}$$

For Circuit (c)

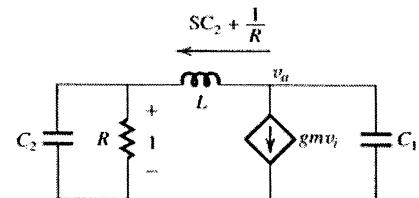

$$v_o = \left(SC_2 + \frac{1}{R}\right) SL + 1$$

$$\Sigma I = 0 \text{ at } v_o, v_i = 1$$

$$g_m + SC_2 + \frac{1}{R} + SC_1 \left[ SL \left( SC_2 + \frac{1}{R} \right) + 1 \right] = 0$$

$$g_m + \frac{1}{R} + SC_2 + S^3 C_1 C_2 L + \frac{S^2 C_1 L}{R} + SC_1 = 0$$

THE CHARACTERISTIC EQUATION

$$g_m + \frac{1}{R} + S(C_1 + C_2) + \frac{S^2 C_2 L}{R} + S^3 C_1 C_2 L = 0$$

Note this is the same as above, with  $C_1 \leftrightarrow C_2$

$$\therefore \omega_0 = \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}} \text{ and } g_m R = \frac{C_1}{C_2}$$

12.20

$$(a) \text{frequency of oscillation } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{gain} \gg 1 \text{ gain} = \frac{RC}{2r_e} = \frac{RC}{2v_T/I/2}$$

$$= \frac{IRC}{4v_T}$$

for  $v_T = 0.025 \text{ V}$  then

$$IRC \geq 4v_T$$

$RC \geq 0.1/I$  for oscillations to start.

$$(b) \text{For } RC = \frac{1}{I} (\text{k}\Omega) \text{ we have}$$

$$\text{gain} = \frac{1/I}{2\left(\frac{2v_T}{I}\right)} = \frac{1}{4 \times 0.025} = 10$$


Oscillations will start ( $10 > 1$ ) and grow until Q1, Q2 go into cutoff. Output will go from  $V_{CC}$  to

$$V_{CC} - IRC = V_{CC} - 1.$$

Therefore, output will be  $1V_{P-P}$ . Fundamental

has a P-P amplitude of  $\frac{4}{\pi} = 1.27 V_{P-P}$

12.21

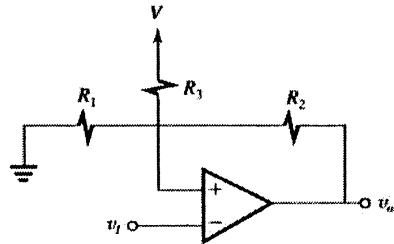

(a)  $\Sigma I$  at + v<sub>L</sub> node:

$$\frac{V_{TH}}{R_1} = \frac{V - V_{TH}}{R_3} + \frac{L_T - V_{TH}}{R_2}$$

$$V_{TH}\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) = \frac{V}{R_3} + \frac{L_T}{R_2}$$

$$\begin{aligned} V_{TH} &= (V/R_3 + L_T/R_2)\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)^{-1} \\ &= \left(\frac{V}{R_3} + \frac{L_T}{R_2}\right)R_1 \parallel R_2 \parallel R_3 \end{aligned}$$

Similarly

$$V_{NL} = \left(\frac{V}{R_3} + \frac{L_T}{R_2}\right)(R_1 \parallel R_2 \parallel R_3)$$

(b) Now

$$V_{TH} = 5.1 = \left(\frac{15}{R_3} + \frac{13}{R_2}\right)\left(\frac{1}{10} + \frac{1}{R_2} + \frac{1}{R_3}\right)^{-1}$$

$$\frac{5.1}{10} + \frac{5.1}{R_2} + \frac{5.1}{R_3} = \frac{15}{R_3} + \frac{13}{R_2}$$

$$0.51 = \frac{7.9}{R_2} + \frac{9.9}{R_3} \quad (1)$$

AND

$$V_{NL} > 4.9 = \left(\frac{15}{R_3} - \frac{13}{R_2}\right)\left(\frac{1}{10} + \frac{1}{R_2} + \frac{1}{R_3}\right)^{-1}$$

$$0.49 = \frac{-17.9}{R_2} + \frac{10.1}{R_3} \quad (2)$$

$$(1) \times \frac{10.1}{9.9} \Rightarrow 0.52 = \frac{8.06}{R_2} + \frac{10.1}{R_3}$$

$$(2) \Rightarrow 0.49 = \frac{-17.9}{R_2} + \frac{10.1}{R_3}$$

SUBTRACT TO GET  $\Rightarrow$


$$0.52 - 0.49 = \frac{8.06 + 17.9}{R_2}$$

$$R_2 = \frac{25.96}{0.0303} = 856.8 \text{ k}\Omega$$

$$\frac{10.1}{R_3} = 0.49 + \frac{17.9}{856.8}$$

$$R_3 = 19.8 \text{ k}\Omega$$

12.22

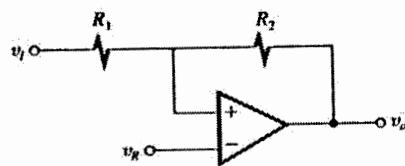

(a) for  $v_I = v_{TL}$  and  $v_O = L_+$  initially

$$\frac{L_+ - v_R}{R_2} = \frac{v_R - v_{TL}}{R_1}$$

$$v_{TL} = v_R - \frac{R_1}{R_2} v_R - \frac{R_1}{R_2} L_+$$

$$\therefore v_{TL} = v_R \left(1 - \frac{R_1}{R_2}\right) - \frac{R_1}{R_2} L_+$$

Similarly

$$\frac{L_- - v_R}{R_2} = \frac{v_R - v_{TH}}{R_1}$$

$$v_{TH} = v_R \left(1 + R_2/R_1\right) - \frac{R_1}{R_2} L_-$$

(b) Given

$$L_+ = -L_- = V$$

$$R_1 = 10 \text{ k}\Omega$$

$$V_{TL} = 0$$

$$V_{TH} = V/10$$

Substituting these values we get:

$$O = V_R \left(1 + 10/R_2\right) - 10/R_2 V \quad (1)$$

$$\frac{V}{10} = V_R \left(1 + 10/R_2\right) + 10/R_2 V \quad (2)$$

$$(1) - (2) - \frac{V}{10} = -\frac{20}{R_2} v$$

$$R_2 = 200 \text{ k}\Omega$$

$$O = V_R \left(1 + 10/200\right) - \frac{10}{200} V$$


$$V_R = \frac{10/200 \text{ V}}{1 + 10/200} = 47.62 \text{ mV}$$

12.23



Output levels =  $\pm 0.7 \text{ V}$

$$\text{Threshold levels} = \pm \frac{10}{10 + 60} \times 0.7 = 0.1 \text{ V}$$
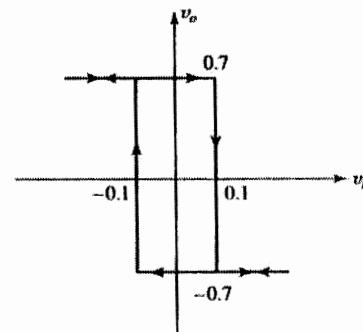
$$i_{D,\max} = \frac{12 - 0.7}{10} - \frac{0.7}{10 + 60} = 1.12 \text{ mA}$$



12.24

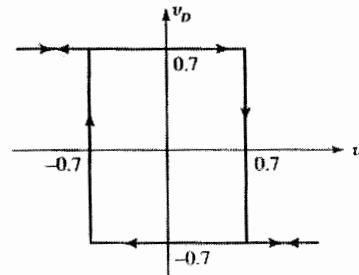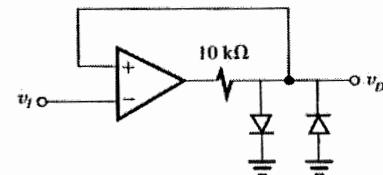


12.25

(a) A 0.5 V peak sine wave, is not large enough to change the state of the circuit. Hence, the output will be either +12 V or -12 V at DC.

(b) The 1.1 V peak will change the state when

$$1.1 \sin \theta = 1$$

$$\theta = 65.40^\circ$$

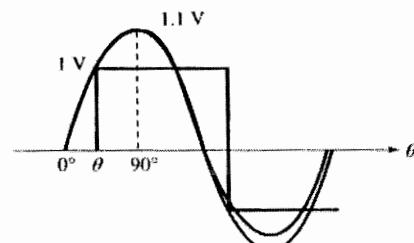

$\therefore$  The output is a symmetric square wave at frequency  $f$ , and lags the sine wave by an angle of  $65.4^\circ$ . The square wave has a swing of  $\pm 12 \text{ V}$ . Since  $V_{TH} - V_{TL} = 1 \text{ V}$ , if the average shifts by an amount so either the +ve or -ve swing is  $< 1 \text{ V}$ , then no change of state will occur. Clearly, if the shift is  $0.1 \text{ V}$ , the output will be a DC voltage.

### 12.26

$$\text{For } L_+ = -L_- = 7.5 \text{ V}$$

$$V_Z = 6.8 \text{ V with } V_D = 0.7 \text{ V.}$$

$$\text{For } V_{TH} = -V_{TL} = 7.5 \text{ V} \Rightarrow R_1 = R_2$$

$$\text{For } v_i = 0 \quad I_{R_2} = 0.1 \text{ mA} = \frac{7.5}{R_1 + R_2}$$

$$\Rightarrow R_1 = R_2 = 37.5 \text{ k}\Omega$$

$$I_D = 1 \text{ mA} = \frac{12 - 7.5}{R} = \frac{7.5}{2R_1}$$

$$1 = \frac{4.5}{R} + 0.1$$

$$R = 4.1 \text{ k}\Omega$$

### 12.27

$$T = 2\pi \ln \frac{1+\beta}{1-\beta} \quad \beta = \frac{R_1}{R_1 + R_2} = \frac{10}{26}$$

$$T = 2(10 \times 10^{-9})(62 \times 10^3) \ln \left( \frac{1 + 10/26}{1 - 10/26} \right)$$

$$T = 1.006 \text{ ms} \Rightarrow f = 994.5 \text{ Hz}$$

### 12.28 for $\pm 5V_{\text{outputs}}$

$$V_z = 5 - 2V_{\text{DIODE}} = 5 - 1.4 = 3.6 \text{ V}$$

For  $\pm 5V_{\text{out}}$ :

$$R_1 = R_2 \quad L_+ = -L_- = 5 \text{ V}$$

$$V_{TH} = -V_{TL} = 5 \text{ V}$$

Max current in feedback network =  $0.2 \text{ mA}$

$$\therefore 0.2 = \frac{5}{R_1 + R_2} \Rightarrow R_1 = R_2 = 25 \text{ k}\Omega$$

Max diode current =  $1 \text{ mA}$

$$\therefore \frac{13 - 5}{R_x} = (0.2 + 1) \text{ mA}$$

$$R_x = \frac{8}{1.2} = 6.67 \text{ k}\Omega$$

Now from Fig 17.25(c)

$$\text{slope} = \frac{-L_-}{RC} = \frac{V_{TH} - V_{TL}}{T/2}$$

for  $f = 1 \text{ kHz}$

$T = 10^{-3} \text{ sec.}$


$C = 0.01 \mu\text{F}$

$$\frac{5}{RC} = \frac{10}{10^{-3}/2} \Rightarrow R = 25 \text{ k}\Omega$$

### 12.29

$$\text{For } 15 \text{ V}_{pp} \text{ output } V_z = 15/2 - 0.7 \\ = 6.8 \text{ V}$$

For the integrator:

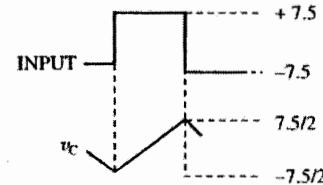

i.e.  $V_C$  should ramp between  $V_{TH}$  &  $V_{TL}$ !

$$v_C(t_1) = \frac{1}{RC} \int_{t_0}^{t_1} v dt + v_c(t_0)$$

$v$  is a square wave

$$\frac{7.5}{2} = \frac{1}{RC} (t_1 - t_0)(7.5 - (-7.5)) - \frac{7.5}{2}$$

$$(t_1 - t_0) = \frac{T}{2}$$

$$7.5 = \frac{1}{RC} \frac{T}{2} (15)$$

$$1 = \frac{T}{RC} \Rightarrow R = \frac{T}{RC} = \frac{1}{fC}$$

$$= \frac{1}{10^4 (0.5 \times 10^{-9})}$$

$$\therefore R = R_{1-6} = 200 \text{ k}\Omega$$

Minimum level current =  $1 \text{ mA}$

$$\frac{13 - 7.5}{R_x} = 1 + \frac{7.5}{R_1 + R_2} + \frac{7.5 - V_C}{R_5}$$

Maximum current into the integrator when

$$V_C = \frac{-7.5}{2}$$

$$\therefore \frac{5.5}{7.5} = 1 + \frac{7.5}{400} + \frac{11.25}{200}$$

$$\therefore R_1 = 5.12 \text{ k}\Omega \Rightarrow$$

$$R_1 = 5.1 \text{ k}\Omega$$

Integrator output is triangular, with period  
 $= 100 \mu\text{s}$  and  $\pm 7.5 \text{ V}$  peaks (i.e.  
 $2 \times$  voltage at capacitor)

### 12.30


See sketches that follow:




$$V_A(t = T) = V_{ref} = -(L_+ - L_-) e^{-T/RC}$$

$$\frac{V_{ref}}{L_+ - L_-} = e^{-T/RC}$$

$$T = -RC \ln\left(\frac{V_{ref}}{L_+ - L_-}\right) = RC \ln\left(\frac{L_+ - L_-}{V_{ref}}\right)$$


Q.E.D.

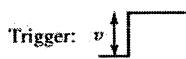Trigger: 

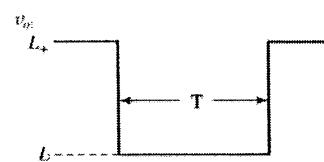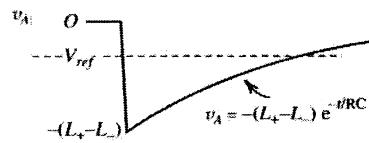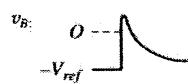
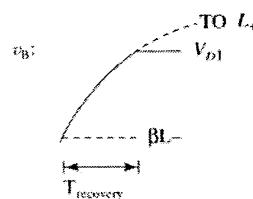
### 12.31

For recovery,  $v_B$  goes from  $\beta L_-$  to  $L_+$ , until  $D_1$  conducts at  $V_{D1} = 0.7 \text{ V}$



For recovery

$$v_B = -0.1(12) + (12 + 1.2)(1 - e^{-t/\tau})$$

$$= 12 - 13.2e^{-t/\tau}$$

At  $T$  recovery:

$$V_{D1} = 12 - 13.2e^{-T/\tau}$$

$$\tau = R_3 C_1$$

$$Tr = -R_3 C_1 \ln\left(\frac{V_{D1} - 12}{13.2}\right)$$

$$= -(6171)(0.1 \times 10^{-6}) \ln\left(\frac{11.3}{13.2}\right)$$

$$= 96 \mu\text{s}$$

### 12.32

Choose  $C_1 = 1 \text{nF}$        $C_2 = 0.1 \text{nF}$

$$R_1 = R_2 = 100 \text{ k}\Omega \Rightarrow \beta = \frac{1}{2}$$

$$T \cong C_1 R_3 \ln\left(\frac{0.7 + 13}{-13(0.5 - 1)}\right)$$

$$10^{-4} = 10^{-9} R_3 \ln\left(\frac{13.7}{13(0.5)}\right)$$

$$R_3 = 134.1 \text{ k}\Omega$$

Need  $R_4 \gg R_1 \Rightarrow$  choose  $R_4 = 470 \text{ k}\Omega$

$$\text{Min trigger voltage} = (\beta L_+ - V_{D2} + V_{D1})$$

$$= 6.5 \text{ V}$$

For recovery

$$v_B = 13 - (13 - \beta L_-) e^{-t/\tau}$$

$$= 13 - 19.5e^{-t/\tau} = 0.7$$

$$\therefore t_{\text{recovery}} = -\tau \ln\left(\frac{12.3}{19.5}\right)$$

$$= -(134.1 \times 10^3)(10^{-9})(-0.4608)$$


$$= 61.8 \mu\text{s}$$

### 12.33

For  $v_t > 2/3 V_{CC}$  comp -1 = "1" and comp -2 = "0" and flip flop is reset. I.E.  $v_o = 0 \text{ V}$ .

Now  $v_o$  will not change until  $v_t = 1/3 V_{CC}$ , when comp -2 = "1" and comp -1 = "0" and FF is set. I.E.  $V_O = V_{CC}$

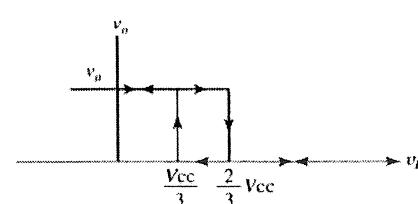For  $\frac{1}{3} V_{CC} < v_t < \frac{2}{3} V_{CC}$ , comp -1 = comp -2 = "0" and no change of state will occur.



i.e. an inverting bistable circuit.

### 12.34

(a)  $C = \ln F$

$$v_C = V_{CC}(1 - e^{-t/\tau})$$

where  $\tau = RC$

Pulse width of 10  $\mu s$  when  $v_C = V_{TH}$

$$= \frac{2}{3}V_{CC}$$

$$\therefore \frac{2}{3} = 1 - e^{-t/RC}$$

$$t = T = 10 \mu s$$

$$\begin{aligned} -\frac{T}{RC} &= \ln\left(\frac{1}{3}\right) \Rightarrow R = \frac{-T}{C\ln(1/3)} \\ &= 9.1 \text{ k}\Omega \end{aligned}$$

(b) for  $T = 20 \mu s$ ,  $R = 9.1 \text{ k}\Omega$ ,  $C = \ln F$

$$\therefore V_{TH} = 15(1 - e^{-t/RC})$$

$$= 15 \left( 1 - e^{\frac{-20 \times 10^{-6}}{9.1 \times 10^3 \times 10^{-9}}} \right)$$

$$= 13.3 \text{ V}$$

### 12.35

$$C = 680 \text{ pF } f = 50 \text{ kHz}$$

$$T = 20 \mu s = T_H + T_L$$

For 75% Duty  $T_H = 15 \mu s$

$$T_L = 5 \mu s$$

From Eq (17.43) we have:

$$T_L = CR_B \ln 2$$

$$\therefore R_B = \frac{5 \times 10^{-6}}{680 \times 10^{-12} \ln 2} = 10.6 \text{ k}\Omega$$

From Eq (17.41)

$$T_H = C(R_A + R_B) \ln(2)$$

$$\begin{aligned} R_A &= \frac{15 \times 10^{-6}}{680 \times 10^{-12} \ln(2)} = 10.6 \times 10^3 \\ &= 21.2 \text{ k}\Omega \end{aligned}$$

### 12.36



For the rise:

$$V_C = V_{CC} - (V_{CC} - V_{TL})e^{-t/CR_A + R_B}$$

$$V_{TH} = V_{CC} - (V_{CC} - V_{TL})e^{-T_H/CR_A + R_B}$$

$$\frac{V_{CC} - V_{TH}}{V_{CC} - V_{TL}} = e^{-T_H/CR_A + R_B}$$

$$T_H = C(R_A + R_B) \ln \left( \frac{V_{CC} - V_{TH}}{V_{CC} - V_{TL}} \right)$$

For exponential fall:

$$V_C = V_{TH} e^{-t/CR_B}$$

$$\therefore V_{TL} = V_{TH} e^{-T_L/CR_B}$$

$$T_L = CR_B \ln \left( \frac{V_{TH}}{V_{TL}} \right)$$

for  $V_{TH} = 2 V_{TL} \Rightarrow T_L = CR_B \ln(2)$

(b)  $C = \ln F$ ,  $R_A = 7.2 \text{ k}\Omega$ ,  $R_B = 3.6 \text{ k}\Omega$

$$V_{CC} = 6 \text{ V } V_{TH \text{ crit}} = 0$$

$$\therefore T_H + T_L = T = \ln 2 (R_A + 2R_B) C$$

$$T = 9.98 \mu s \rightarrow f = 100 \text{ kHz}$$

$$\begin{aligned} \text{Duty cycle} &= \frac{T_H}{T_H + T_L} = \frac{R_A + R_B}{R_A + 2R_B} = 0.75 \\ &\Rightarrow 75\% \end{aligned}$$

(c)  $V_{CC} = 5 \text{ V}$ ,

$$V_{TH} = \frac{2}{3} \times 5 = \frac{10}{3} = 3.33 \text{ V}$$

for IV input  $V_{TH}^I = 4.33 \text{ V}$

$$V_{TL}^I = \frac{1}{2} V_{TH}^I = 2.17 \text{ V}$$

$$T_H^I = 10^{-9} (3.6 + 7.2) \times 10^3 \ln \left( \frac{5 - 2.17}{5 - 4.33} \right)$$

$$= 15.6 \mu s$$

$$T_L^I = 10^{-9} \times 3.6 \times 10^3 \ln 2 = 2.5 \mu s$$

$$\therefore f = \frac{1}{(15.6 + 2.5)10^{-6}} = 55.2 \text{ kHz}$$

$$\text{duty cycle} = \frac{15.6}{2.5 + 15.6} = 86.2\%$$

for IV input  $V_{TH}^{II} = 2.33$

$$V_{TL}^{II} = 1.17$$

$$T_H^{II} = 10^{-9} (3.6 + 7.2) 10^3 \ln \left( \frac{5 - 1.17}{5 - 2.33} \right)$$



$$= 3.92 \mu s$$

$$T_L^{II} + T_L^I = 2.5 \mu s$$

$$\therefore f = \frac{10^6}{(3.92 + 2.5)} = 156 \text{ kHz}$$

$$\text{duty cycle} = \frac{3.92}{2.5 + 3.92} = 61\%$$

12.37

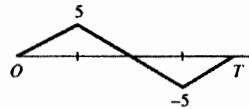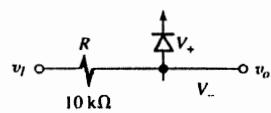

$$v_o = A \sin \frac{2\pi}{T} t$$

Slope of  $v_o$  at  $t=0$ :

$$\begin{aligned} \frac{\partial v_o}{\partial t} &= A \frac{2\pi}{T} \cos\left(\frac{2\pi}{T} t\right)|_{t=0} = 0 \\ &= \frac{A 2\pi}{T} = \text{SLOPE AT ZERO CROSSING} \end{aligned}$$

$$\text{Slope of } \Delta^- \text{ wave} = \frac{5}{T/4} = \frac{20}{T}$$


$$\therefore \frac{20}{T} = \frac{A 2\pi}{T}$$

$$A = 3.18 \text{ V}$$

$\therefore$  Clamp voltage:

$$\begin{aligned} V_T &= -V_- = 3.18 - 0.7 \\ &= 2.48 = 2.5 \text{ V} \end{aligned}$$

12.38

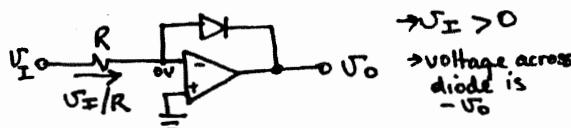


$$i_D = \frac{v_i}{R} = I_s e^{-v_i/2kT}$$

$$-\frac{v_o}{2kT} = \ln\left(\frac{v_i}{R I_s}\right)$$

$$v_o = -n V_T \ln\left(\frac{v_i}{R I_s}\right), \quad v_i > 0$$

Q.E.D.

12.39

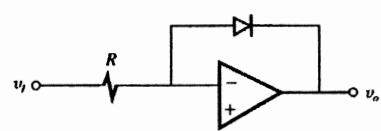

$$= -n V_T \ln\left(\frac{v_i}{R I_s}\right)$$

Now,

$$V_A = -n V_T \ln\frac{V_1}{R I_s} \quad R = 1 \text{ k}\Omega$$

$$V_B = -n V_T \ln\frac{V_2}{R I_s} \quad V_1, V_2 > 0$$

$$V_C = +n V_T \ln\frac{1}{R I_s}$$

$$V_D = -(V_A + V_B + V_C)$$

$$= n V_T \left( \ln \left[ \frac{V_1}{R I_s} \times \frac{V_2}{R I_s} \times \frac{1}{R I_s} \right] \right)$$

$$= n V_T \ln\left(\frac{V_1 V_2}{R^3 I_s^3}\right)$$

$$i_{D4} = I_s e^{V_D/n V_T}$$

$$= I_s \times \frac{V_1 V_2}{R I_s} = \frac{V_1 V_2}{R}$$

$$v_o = -i_{D4} R = -\frac{V_1 V_2}{R} \times R$$

$\therefore v_o = -v_1 v_2$  ANALOG MULTIPLIER

To check  $v_1 = 0.5, v_2 = 2$

$$I_{D1} = 0.5 \text{ mA} \rightarrow V_A = -0.7 + n V_T \ln\left(\frac{0.5}{1}\right)$$

$$= 0.7 + 2(0.025) \ln\left(\frac{1}{2}\right)$$

$$= -0.6653 \text{ V}$$

$$I_{D2} = 2 \text{ mA} \rightarrow V_B = (0.7 + 0.05 \ln(2))(-1) \\ = -0.7347 \text{ V}$$

$$I_{D3} = 1 \text{ mA} \rightarrow V_C = 0.700 \text{ V}$$

$$V_D = -(-0.6653 - 0.7347 + 0.7) = 0.7 \text{ V}$$

$$V_D = V_{D4} = 0.7 \text{ V} \Rightarrow I_{D4} = 1 \text{ mA}$$

$$\therefore v_O = -1 \text{ V i.e. } 2 \times 0.5 = 1$$

For  $v_1 = 3, v_2 = 2$ :

$$I_{D1} = 3 \text{ mA} \rightarrow V_A = -(0.7 + 0.05 \ln 3) \\ = -0.7549 \text{ V}$$

$$I_{D2} = 2 \text{ mA} \rightarrow V_A = -(0.7 + 0.05 \ln 2) \\ = -0.7347 \text{ V}$$

$$I_{D3} = 1 \text{ mA} \rightarrow V_C = 0.7 \text{ V}$$

$$\therefore V_D = V_{D4} = -(V_A + V_B + V_C) = +0.7896 \text{ V}$$

$$\therefore \frac{I_{D4}}{1 \text{ mA}} = \frac{I_S e^{V_D/0.05}}{I_S e^{0.7/0.05}}$$

$$I_{D4} = e^{\frac{0.7896 - 0.7}{0.05}} = 6 \text{ mA}$$

$$\therefore v_O = -6 \text{ V i.e. } 2 \times 3 = 6.$$

For square:  $v_1 = 2$  through  $\frac{1}{2} \text{ k}\Omega$  resistor

$$I_{D1} = 4 \text{ mA} \rightarrow V_A = -(0.7 + 0.05 \ln 4) \\ = -0.7693$$

$$V_D = -(-0.7693) = 0.7693 \text{ V}$$

$$I_{D4} = e^{\frac{0.7693 - 0.7}{0.05}} = 3.999 \text{ mA}$$

$$\therefore V_D = -3.999 \text{ V i.e. } 2^2 = 4.$$

## 12.40


$$\text{Say } V_{BE} = \tilde{V}_D @ I_R = 1$$

for  $v_O = 0.25v_T$ :

$$I_R = \frac{0.25V_T}{R} = \frac{0.25V_T}{2.5V_T} = \frac{I}{10}$$

$$V_{BE1} = \tilde{V}_D + nV_T \ln\left(\frac{I + I/10}{I}\right)$$

$$\cong \tilde{V}_D + V_T \ln(1.1)$$

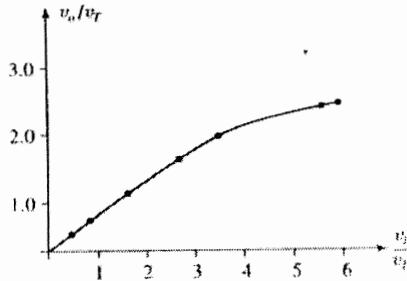

$$V_{BE2} = \tilde{V}_D + nV_T \ln\left(\frac{I + I/10}{I}\right)$$

$$\cong \tilde{V}_D + V_T \ln(0.9)$$

$$V_I = -V_{BE2} + V_D + V_{BE1}$$

$$= V_T [\ln(1.1) + 0.25 - \ln(0.9)]$$

$$= 0.451V_T$$

For  $v_O = 0.5V_T$

$$I_R = \frac{0.5I}{2.5} = 0.2I$$

$$V_I = V_T [\ln(1.2) + 0.5 - \ln(0.8)]$$

$$= 0.905V_T$$

$$V_O = V_T, I_R = 0.4I$$

$$V_I = V_T [\ln 1.4 + 1 - \ln 0.6]$$

$$= 1.847V_T$$

$$V_O = 1.5V_T, I_R = 0.6I$$

$$V_I = V_T (\ln 1.6 + 1.5 - \ln 0.4)$$

$$= 2.886V_T$$

$$V_O = 2V_T, I_R = 0.8I$$

$$V_I = V_T (\ln 1.8 + 2 - \ln 0.2) = 4.197V_T$$

$$V_O = 2.4V_T, I_R = 0.96I$$

$$V_I = V_T (\ln 1.96 + 2.4 - \ln 0.04) = 6.292V_T$$

$$V_O = 2.42V_T, I_R = 0.968I$$

$$V_I = V_T (\ln 1.968 + 2.42 - \ln 0.032)$$

$$= 6.519V_T$$


Ideal curve given by

$$v_O = 2.42V_T \sin\left(\frac{v_I}{6.6V_T} \times 90^\circ\right)$$

$$\frac{v_I}{v_T} = \frac{6.6}{90} \sin^{-1}\left(\frac{v_O}{2.42V_T}\right)$$

$v_O/v_T$	0.25	0.50	1.00	1.50	2.00	2.40	2.42
$v_I/v_T$	0.451	0.905	1.85	2.89	4.20	6.29	6.52
$v_I/v_T$ (ideal)	0.435	0.874	1.79	2.81	4.09	6.06	6.60

12.41

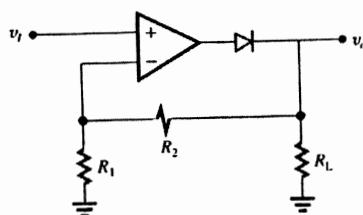


for  $v_i \geq 0$

$$v_o = \left(1 + \frac{R_2}{R_1}\right)v_i$$

for a gain of 2  $R_1 = R_2 = 10 \text{ k}\Omega$

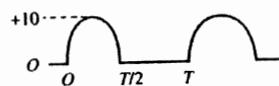for  $v_i = 10V_{rr}$  sine wave  $v_o \Rightarrow$




$$\text{Avg} = \frac{1}{T} \int_0^{T/2} 10 \sin \frac{2\pi t}{T} dt$$

$$= \frac{1}{T} \frac{T}{2\pi} \cos \frac{2\pi t}{T} \Big|_0^{T/2}$$

$$= \frac{-10}{2\pi} (\cos \pi - \cos 0)$$

$$= 10/\pi = 3.18 \text{ V}$$

12.42

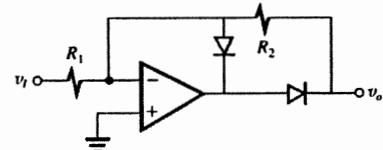

for  $v_i < 0 \Rightarrow v_o = -R_2/R_1 v_i$

$$R_{in} = R_1 = 100 \text{ k}\Omega \therefore R_2 = 200 \text{ k}\Omega$$

12.43

for high  $R_{out}$ , use  $R_1 = 1 \text{ M}\Omega$

Ac gain is given by  $R_2/R_1$

$$\Rightarrow R_2 = 1 \text{ M}\Omega$$

Now for 1 Vrms sine, peak is 1.414 V. The value

$$\text{of } V_i \text{ is then } \frac{1.414}{\pi} = 0.450 \text{ V}$$

For 10 V out at second stage gain (dc)

$$= \frac{10}{0.450} = 22.2$$

$$\therefore R_4/R_3 = 22.2$$

& Choose  $\frac{1}{2\pi R_4 C} = 10 \text{ Hz}$  (i.e. corner frequency)

To make  $C$  small, make  $R_4 = 1 \text{ M}\Omega$

$$\therefore C = 15.9 \text{ nF}$$

$$R_3 = \frac{1 \text{ M}\Omega}{22.2} = 45 \text{ k}\Omega$$

12.44

At the +ve terminal  $V_+ = -5 \text{ V}$

for  $v_i > -5$   $D_1$  is "ON" and faces virtual short.


$\therefore V_- = -5$ , and no current will flow in feedback  $R$ .

$$\therefore v_o = -5 \text{ V}$$

for  $v_i < -5$   $D_1$  is "off" and

$$\frac{v_o}{v_i} = \frac{-5 - v_i}{R} = \frac{v_o + 5}{R}$$

$$\Rightarrow v_o = -v_i$$

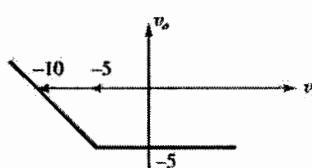

12.45

for  $v_i < 0$

$D_2$  "off"

$$\frac{v_{o1}}{v_i} = -1$$


$$\frac{v_{o2}}{v_i} = 0$$

for  $v_i > 0$


$D_1$  "off"

$$\frac{v_{o1}}{v_i} \approx 0$$

$$\frac{v_{o2}}{v_i} = -1$$

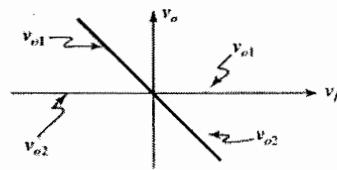

12.46

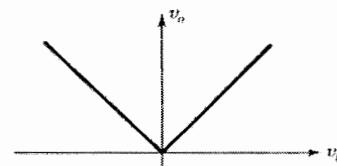

For  $v_i < 0$  ~ Diode is on, and cathode is forced to  $\approx 0$  V.


$$\therefore (v_o / v_i) = -1$$

For  $v_i > 0$  ~ Diode is off, and the cathode now follows  $v_i$  since no current flows in resistor. So  $v_o$  must follow  $v_i$  so that no current flows in feedback resistor.

$$\therefore \frac{v_o}{v_i} = +1$$

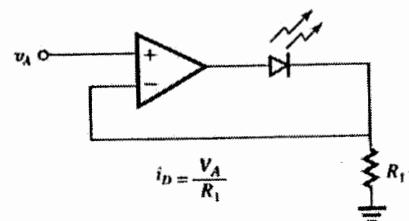
12.47

Simply place the LED in the feedback path.



$$i_D = \frac{V_A}{R_f}$$

12.48

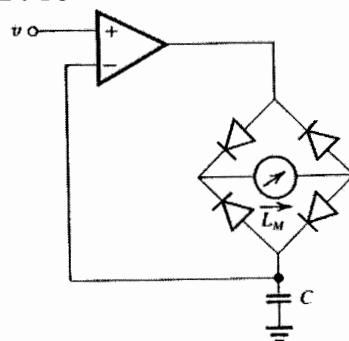

$$i_m = |i_d| = C \frac{dv}{dt} \text{ using } R = 1 \text{ k}\Omega$$

$$i_m = |i_R| = \frac{|v|}{R} = \frac{|v|}{1 \text{ k}\Omega} \Rightarrow i_m = |v| \text{ mA}$$

$$\text{Now } v = V \sin 2\pi 60t$$

$$\Rightarrow i_m = C \times 2\pi 60 |\cos(2\pi 60t)|$$

for equivalence:

$$\frac{V}{10^3} |\sin 2\pi 60t| = 2\pi 60 V C |\cos 2\pi 60t|$$


$$\therefore C = \frac{1}{2\pi 60 10^3} = 2.65 \mu F$$

$$\text{At } 120 \text{ Hz: } i_m = 2\pi 120 V C |\cos 2\pi 60t|$$

$$i_{m120} = 2i_{m60}$$

$$\text{At } 180 \text{ Hz: } i_{m180} = 3i_{m60}$$

For  $\Delta$ -wave

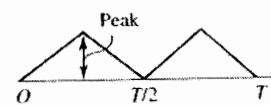

with  $R$ .

$$i_m = 1 \text{ mA}, R = 1 \text{ k}\Omega$$

∴ Full wave rectified wave has average voltage =  $N$ .

$$\therefore V_{\text{peak}} = 2 \text{ V}$$

with  $C$ :

$$\text{slope} = \frac{V_{\text{peak}}}{T/4} = 4V_{\text{peak}}f$$

$$= 4 \times 2 \times 60 = 480$$

Now: current through the capacitor will be a square wave (50% duty cycle)

$$\text{Peak current} = 2.65 \times 10^{-6} \times 480$$

$$= 1.27 \text{ mA.}$$

$$\therefore i_m = i_{\text{avg}} = 1.27 \text{ mA}$$

### 12.49

10 V pulses of  $10 \mu\text{s}$ , and large  $C_{\text{load}}$ , will cause the op amp to current limit.

Charge transferred in one pulse:

$$Q = (10 \text{ mA})(10 \mu\text{s})$$

$$= 10^{-7} \text{ C}$$

Voltage change per pulse:

$$\Delta V = Q/C = \frac{10^{-7}}{10 \times 10^{-6}} = 10 \text{ mV}$$

$$\text{after: 1 pulse} \quad V_c = 10 \text{ mV}$$

$$2 \text{ pulses} \quad 20 \text{ mV}$$

$$10 \text{ pulses} \quad 100 \text{ mV}$$

to reach 0.5 V require 50 pulses

$$1.0 \text{ V} \quad 100 \text{ pulses}$$

$$2.0 \text{ V} \quad 200 \text{ pulses}$$

### 12.50

For  $IV_{rr}$ , peak detector output  $V_o = 0.5 \text{ V}$ .

Ripple voltage = (1%)  $0.5 = 5 \text{ mV}$


Total leakage =  $10 + 1 = 11 \text{ nA}$

∴ total charge lost:

$$\Delta Q = 11 \text{ nA} \times 1 \text{ ms} = 11 \text{ pC}$$


∴ Required capacitance:
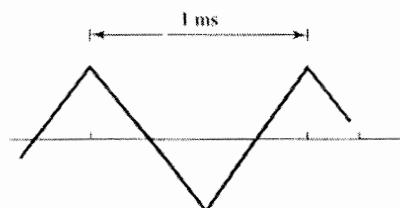
$$C = \frac{\Delta Q}{\Delta V} = \frac{11 \times 10^{-12}}{5 \times 10^{-3}} = 2.2 \text{ nF}$$


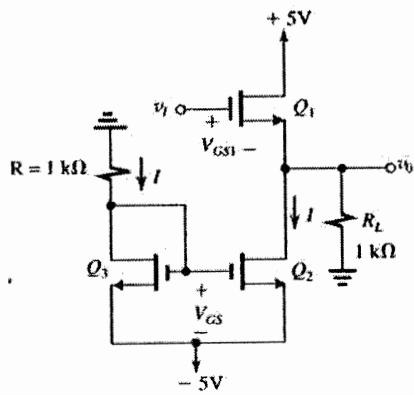
### 13.1

First we determine the bias current  $I$  as follows:



$$I = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$\begin{aligned} \text{But } V_{GS} &= 5 - IR \\ &= 5 - I \end{aligned}$$

Thus

$$I = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (5 - I - V_t)^2$$

$$I = 10(5 - I - 1)^2$$

$$\Rightarrow I^2 - 8.1I + 16 = 0$$

$$I = 3.416 \text{ mA and } V_{GS} = 1.584 \text{ V}$$

The upper limit on  $v_o$  is determined by  $Q_1$  leaving the saturation region (and entering the triode region). This occurs when  $v_t$  exceeds  $V_{DI}$  by  $V_t$  volts,

$$v_{t\max} = 5 + 1 = +6 \text{ V}$$

To obtain the corresponding value of  $v_o$  we must find the corresponding value of  $V_{GS1}$ , as follows:

$$v_o = v_t - V_{GS1}$$

$$\begin{aligned} i_L &= \frac{v_o}{R_L} = \frac{v_t - V_{GS1}}{1} \\ &\approx v_t - V_{GS1} = 6 - V_{GS1} \end{aligned}$$

$$\begin{aligned} i_1 &= I + i_L \\ &= 3.416 + 6 - V_{GS1} \\ &= 9.416 - V_{GS1} \end{aligned}$$

$$\text{But } i_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_t)^2$$

$$\text{Thus, } 9.416 - V_{GS1} = 10(V_{GS1} - 1)^2$$

$$\Rightarrow V_{GS1}^2 - 1.9 V_{GS1} + 0.0584 = 0$$

$$V_{GS1} = 1.869 \text{ V}$$

$$v_{o\max} = 6 - 1.869$$

$$= +4.131 \text{ V}$$

The lower limit of  $v_o$  is determined either by  $Q_1$  cutting off,

$$v_o = -IR_L = -3.416 \times 1 = -3.416 \text{ V}$$

or by  $Q_2$  leaving saturation,

$$\begin{aligned} v_o &= V_{GS} - V_t \\ &= -5 + 1.584 - 1 = -4.416 \text{ V} \end{aligned}$$

$$\text{Thus, } v_{o\min} = -4.416 \text{ V}$$

The corresponding value of  $v_t$  is determined by moving that since  $Q_1$  is on the verge of cut-off,

$$V_{GS1} = V_t = 1 \text{ V and}$$

$$v_t = -3.416 + 1 = -2.416 \text{ V}$$

### 13.2

For a load resistance of  $100 \Omega$  and  $v_o$  ranging between  $-5 \text{ V}$  and  $+5 \text{ V}$ , the maximum current through  $Q_1$  is

$$I + \frac{5}{0.1} = I + 50 \text{ mA and the minimum current is } I - \frac{5}{0.1} = I - 50 \text{ mA.}$$

For a current ratio of 10,

$$\begin{aligned} \frac{I + 50}{I - 50} &= 10 \\ \Rightarrow I &= 61.1 \text{ mA} \end{aligned}$$

$$R = \frac{9.3 \text{ V}}{61.1 \text{ mA}} = 152 \Omega$$

The incremental voltage gain is  $A_v = \frac{R_L}{R_L + r_{e1}}$

For  $R_L = 100 \Omega$ :

At  $v_o = +5 \text{ V}$ ,  $I_{E1} = 61.1 + 50 = 111.1 \text{ mA}$

$$r_{e1} = \frac{25}{111.1} = 0.225 \Omega$$

$$A_v = \frac{100}{100 + 0.225} = 0.998 \text{ V/V}$$

At  $v_o = 0 \text{ V}$ ,  $I_{E1} = 61.1 \text{ mA}$

$$r_{e1} = \frac{25}{61.1} = 0.409 \Omega$$

$$A_v = \frac{100}{100.409} = 0.996 \text{ V/V}$$

At  $v_o = -5 \text{ V}$ ,  $I_{E1} = 61.1 - 50 = 11.1 \text{ mA}$


$$r_{e1} = \frac{25}{11.1} = 2.25 \Omega$$

$$A_v = \frac{100}{102.25} = 0.978 \text{ V/V}$$

Thus the incremental gain changes by  $0.998 - 0.978 = 0.02$  or about 2% over the range of  $v_o$ .
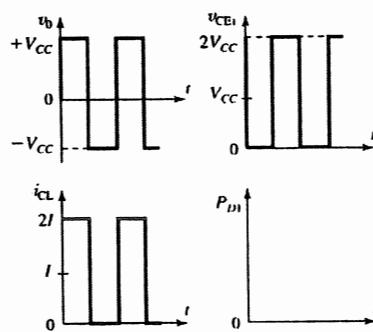
### 13 . 3


For  $v_o$  being a square wave of  $\pm V_{CC}$  levels:



$P_{DI}|_{\text{average}} = 0$  For the corresponding sine wave

$$\text{curve } P_{DI}|_{\text{avg}} = \frac{1}{2} V_{CC} I$$

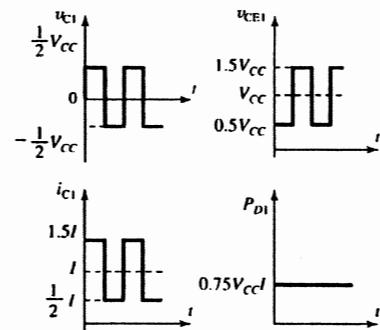For  $v_o$  a square wave of  $\pm V_{CC}/Z$  levels :



$$P_{DI}|_{\text{average}} = 0.75 V_{CC} I$$

For a sine-wave output of  $V_{CC}/2$  peak amplitude,

$$v_{C1} = \frac{1}{2} V_{CC} \sin \theta$$

$$i_{C1} = I + \frac{1}{2} \frac{V_{CC}}{R_L} \sin \theta = I + \frac{1}{2} I \sin \theta$$

$$v_{CE1} = V_{CC} - \frac{1}{2} V_{CC} \sin \theta$$

$$\begin{aligned} P_{DI} &= \left( V_{CC} - \frac{1}{2} V_{CC} \sin \theta \right) \left( I + \frac{1}{2} I \sin \theta \right) \\ &= V_{CC} I - \frac{1}{4} V_{CC} I \sin^2 \theta \\ &= V_{CC} I - \frac{1}{4} V_{CC} I \times \frac{1}{2} (1 - \cos 2\theta) \\ &= \frac{7}{8} V_{CC} I + \frac{1}{8} V_{CC} I \cos 2\theta \end{aligned}$$

$$P_{DI}|_{\text{average}} = \frac{7}{8} V_{CC} I$$

### 13 . 4

In all cases, the average voltage across  $Q_2$  is equal to  $V_{CC}$ . Thus, since  $Q_2$  conducts a constant current  $I$ , its angle power dissipation is  $V_{CC} I$ .

### 13 . 5

$$V_{CC} = 16, 12, 10 \text{ and } 8 \text{ V}$$


$$I = 100 \text{ mA } R_L = 100 \Omega$$

$$\hat{V}_o = 8 \text{ V}$$

$$\begin{aligned} \eta &= \frac{1}{4} \left( \frac{\hat{V}_o}{IR_L} \right) \left( \frac{\hat{V}_o}{V_{CC}} \right) \\ &= \frac{1}{4} \left( \frac{8}{10} \right) \left( \frac{8}{V_{CC}} \right) = \frac{1.6}{V_{CC}} \end{aligned}$$

$V_{CC}$	16	12	10	8
$\eta$	10%	13.3%	16%	20%

13.6

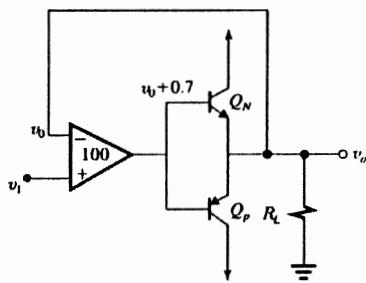

With  $v_i$  sufficiently positive so that  $Q_N$  is conducting the situation shown obtains. Then,  $(v_i - v_o) \times 100 = v_o + 0.7$

$$\Rightarrow v_o = \frac{1}{1.01}(v_i - 0.007)$$

This relationship applies for  $v_i \geq 0.007$ . Similarly, for  $v_i$  sufficiently negative so that  $Q_P$  conducts, the voltage at the output of the amplifier becomes  $v_o - 0.7$ .


thus

$$(v_i - v_o) \times 100 = v_o - 0.7$$

$$\Rightarrow v_o = \frac{1}{1.01}(v_i + 0.007)$$

This relationship applies for  $v_i \leq -0.007$ .

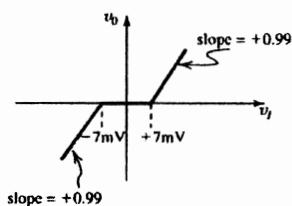The result is the transfer characteristic



Without the feedback arrangement, the deadband becomes  $\pm 700$  mV and the slope change a little (to nearly  $\pm 1$  V/V).

13.7


With  $R_L = \infty$  and  $V_T = +5$  V,  $v_o$  will be  $V_I - V_{GS} = V_I - V_t = 4$  V (since the current is virtually zero and thus  $V_{GS} \approx V_t$ ). Thus the resulting peak output voltage will be 4 V.

$$\sin \theta = \frac{1}{3}$$

$$\Rightarrow \theta = 11.54^\circ$$

$$\text{Cross-over interval} = 4\theta$$
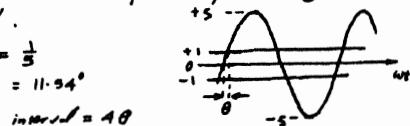
$$\text{Fraction of Cycle} = \frac{4\theta}{360^\circ} = 12.8\%$$



For  $V_I = +5$  V and


$$V_o = +2.5$$
 V,

$$V_{GS} = 2.5$$
 V, thus

$$i_D = \frac{1}{2} \mu C_s (\bar{V}_{GS} - V_t)^2$$

$$= 0.1 (2.5 - 1)^2 = 0.225 \text{ mA}$$
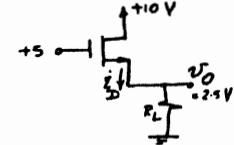
$$\text{Thus, } R_L = \frac{2.5}{0.225} = 11.1 \text{ k}\Omega$$



13.8

For  $V_{CC} = 10$  V and  $R_L = 100 \Omega$ , the maximum sine-wave output power occurs when  $\hat{v}_o = V_{CC}$

$$\text{and is } P_{L\max} = \frac{1}{2} \frac{V_{CC}^2}{R_L}$$

$$= \frac{1}{2} \times \frac{100}{100} = 0.5 \text{ W}$$

Correspondingly,

$$P_{S+} = P_{S-} = \frac{1}{\pi} \frac{\hat{v}_o}{R_L} V_{CC}$$

$$= \frac{1}{\pi} \times \frac{10}{100} \times 10 = 0.318 \text{ W}$$

For a total supply power of

$$P_s = 2 \times 0.318 = 0.637 \text{ W}$$

The power conversion efficiency  $\eta$  is

$$\eta = \frac{P_L}{P_s} \times 100 = \frac{0.5}{0.637} \times 100 = 78.5 \%$$

For  $\hat{v}_o = 5$  V,

$$P_L = \frac{1}{2} \frac{\hat{v}_o^2}{R_L} = \frac{1}{2} \times \frac{25}{100} = \frac{1}{8} \text{ W}$$

$$P_{S+} = P_{S-} = \frac{1}{\pi} \frac{\hat{v}_o}{R_L} V_{CC}$$

$$= \frac{1}{\pi} \times \frac{5}{100} \times 10 = \frac{1}{2\pi} \text{ W}$$

$$P_{S+} = \frac{1}{\pi} \text{ W} = 0.318 \text{ W}$$

$$\eta = \frac{1/8}{1/\pi} \times 100 = \frac{\pi}{8} \times 100 = 39.3 \%$$

### 13.9

$$V_{CC} = 5 \text{ V}$$

For maximum  $\eta$ ,

$$\hat{V}_o = V_{CC} = 5 \text{ V}$$

The output voltage that results in maximum device dissipation is given by Eq. (12.20),

$$\hat{V}_o = \frac{2}{\pi} V_{CC}$$

$$= \frac{2}{\pi} \times 5 = 3.18 \text{ V}$$

If operation is always at full output voltage,

$\eta = 78.5\%$  and thus

$$P_{\text{dissipation}} = (1 - \eta) P_L$$

$$= (1 - \eta) \frac{P_L}{\eta} = \frac{1 - 0.785}{0.785} P_L = 0.274 P_L$$

$$P_{\text{dissipation/device}} = \frac{1}{2} \times 0.274 P_L = 0.137 P_L$$

For a rated device dissipation of 1 W, and using a factor of 2 safety margin,

$$P_{\text{dissipation/device}} = 0.5 \text{ W}$$

$$= 0.137 P_L$$

$$\Rightarrow P_L = 3.65 \text{ W}$$

$$3.65 = \frac{1}{2} \times \frac{25}{R_L}$$

$$\Rightarrow R_L = 3.425 \Omega \text{ (i.e., } R_L \geq 3.425 \Omega)$$

The corresponding output power (i.e., greatest possible output power) is 3.65W.

If operation is allowed at  $\hat{V}_o = \frac{1}{2} V_{CC} = 2.5 \text{ V}$ ,

$$\eta = \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}} \text{ (Eq. 12.15)}$$

$$= \frac{\pi}{4} \times \frac{1}{2} = 0.393$$

$$P_{\text{dissipation/device}} = \frac{1}{2} \frac{1 - \eta}{\eta} P_L = 0.772 P_L$$

$$0.5 = 0.772 P_L$$

$$\Rightarrow P_L = 0.647 \text{ W}$$

$$= \frac{1}{2} \frac{2.5^2}{R_L}$$

$$\Rightarrow R_L = 4.83 \Omega \text{ (i.e., } R_L \geq 4.83 \Omega)$$

### 13.10

$$P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

$$100 = \frac{1}{2} \frac{\hat{V}_o^2}{16}$$

$$\hat{V}_o = 56.6 \text{ V}$$

$$V_{CC} = 56.6 + 4 = 60.6 \rightarrow 61 \text{ V}$$

$$\text{Peak current from each supply} = \frac{\hat{V}_o}{R_L} = \frac{56.6}{16} = 3.54 \text{ A}$$

$$P_{ss} = P_{s-} = \frac{1}{\pi} \times 3.54 \times 61$$

$$\text{Thus, } P_s = \frac{2}{\pi} \times 3.54 \times 61 \\ = 137.4 \text{ W}$$

$$\eta = \frac{P_L}{P_s} = \frac{100}{137.4} = 73\%$$

Using Eq. (12.22),

$$P_{DN\max} = P_{DP\max} = \frac{V_{CC}^2}{\pi^2 R_L} = \frac{61^2}{\pi^2 \times 16} \\ = 23.6 \text{ W}$$

### 13.11

$$P_L = \frac{\hat{V}_o^2}{R_L}$$

$$P_{ss} = P_{s-} = \frac{1}{2} \left( \frac{\hat{V}_o}{R_L} \right) V_{SS}$$

$$P_s = \frac{\hat{V}_o}{R_L} V_{SS}$$

$$\eta = \frac{P_L}{P_s} = \frac{V_{SS}^2 / R_L}{\hat{V}_o V_{SS} R_L} = \frac{\hat{V}_o}{V_{SS}}$$

$\eta_{\max} = 1(100\%)$ , obtained for  $\hat{V}_o = V_{SS}$

$$P_{L\max} = \frac{V_{SS}^2}{R_L}$$

$$P_{\text{dissipation}} = P_s - P_L \\ = \frac{\hat{V}_o}{R_L} V_{SS} - \frac{\hat{V}_o^2}{R_L}$$

$$\frac{\partial P_{\text{dissipation}}}{\partial \hat{V}_o} = \frac{V_{SS}}{R_L} - \frac{2\hat{V}_o}{R_L}$$

$$= 0 \text{ for } \hat{V}_o = \frac{V_{SS}}{2}$$

$$\text{Correspondingly, } \eta = \frac{V_{SS}/2}{V_{SS}} = \frac{1}{2} \text{ or } 50\%$$

13.12

$$A_{\sigma} = \frac{R_L}{R_L + R_{out}}$$

$$\text{where, } R_{out} = \frac{V_T}{2} = \frac{V_T}{2 I_Q}$$

For  $A_{\sigma} \geq 0.99$  with  $R_L \geq 100 \Omega$ ,

$$0.99 = \frac{100}{100 + R_{out}} \Rightarrow R_{out} = 1 \Omega$$

$$\frac{V_T}{2 I_Q} = 1 \Rightarrow I_Q = 12.5 \text{ mA}$$

$$V_{BB} = 2 V_{BE}$$

$$= 2 \left[ 0.7 + V_T \ln \frac{12.5}{100} \right]$$

$$= 1.296 \text{ V}$$

This table is for 13.13

$v_i$ (V)	$i_L$ (mA)	$i_N$ (mA)	$i_p$ (mA)	$V_{BE}$ (V)	$V_{FB}$ (V)	$V_o$ (V)	$V_o/V$	$R_{out}$ ( $\Omega$ )	$V_o/V$	$i_i$	$R_{in}$ ( $\Omega$ )
+10.0	100	100.04	0.04	0.691	0.495	10.1	0.99	0.25	1.00	2	5050
+5.0	50	50.08	0.08	0.673	0.513	5.08	0.98	0.50	1.00	1	5080
+1.0	10	10.39	0.39	0.634	0.552	1.041	0.96	2.32	0.98	0.2	5205
+0.5	5	5.70	0.70	0.619	0.567	0.526	0.95	4.03	0.96	0.1	5260
+0.2	2	3.24	1.24	0.605	0.581	0.212	0.94	5.58	0.95	0.04	5300
+0.1	1	2.56	1.56	0.599	0.587	0.106	0.94	6.07	0.94	0.02	5300
0	0	2	2	0.593	0.593	0	-	6.25	0.94		
-0.1	-1	1.56	2.56	0.587	0.599	-0.106	0.94	6.07	0.94	-0.02	5300
-0.2	-2	1.24	3.24	0.581	0.605	-0.212	0.94	5.58	0.95	-0.04	5300
-0.5	-5	0.70	5.70	0.567	0.619	-0.526	0.95	4.03	0.96	-0.1	5260
-1.0	-10	0.39	10.39	0.552	0.634	-1.041	0.96	2.32	0.98	-0.2	5205
-5.0	-50	0.08	50.08	0.513	0.673	-5.08	0.98	0.50	1.00	-1	5080
-10.0	-100	0.04	100.04	0.495	0.691	-10.1	0.99	0.25	1.00	-2	5050

$$I_Q = \frac{V_T}{4} = \frac{25 \times 10^{-3}}{4} = 6.25 \text{ mA}$$

$$V_{BB} = 2V_{BE} = 2[0.7 + V_T \ln\left(\frac{6.25}{100}\right)] \\ = 1.26 \text{ V}$$

### 13.13

The current  $i_i$  can be obtained as

$$i_i = \frac{i_N}{\beta_N + 1} - \frac{i_p}{\beta_p + 1} = \frac{i_L}{\beta + 1}$$

$$\therefore \beta_N = \beta_p = \beta = 49$$

Using values of  $i_i$  from the table one can evaluate  $R_{in}$

$$\therefore R_{in} = \frac{v_i}{i_i}$$

Using resistance reflection rule

$$R_{in} \cong \beta R_L = 49 \times 100 \\ = 4900 \Omega$$

For large input signal the two values of  $R_{in}$  are somewhat same. For the small values of  $v_i$ , the calculated value in the table is larger.

### 13.14

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{out}} \text{ and}$$

$$R_{out} = \frac{V_T}{i_p + i_N} = \frac{V_T}{I_Q + I_Q} \text{ at } v_i = 0$$

$$\text{a. } \epsilon = 1 - \left. \frac{v_o}{v_i} \right|_{v_i=0}$$

$$= 1 - \frac{R_L}{R_L + R_{out}} = 1 - \frac{R_L}{R_L + \frac{V_T}{2I_Q}} = \frac{V_T/2I_Q}{R_L + (V_T/2I_Q)}$$

$$\epsilon = \frac{V_T/2I_Q}{R_L + (V_T/2I_Q)} = \frac{V_T}{2R_L I_Q + V_T}$$

If  $2I_Q R_L \gg V_T$ ,

$$\epsilon = \frac{V_T}{2I_Q R_L}$$

b. Quiescent Power Dissipation =  $2V_{CC} I_Q = P_D$

c.  $\epsilon \times$  Quiescent Power Dissipation =

$$\frac{V_T}{2I_Q R_L} \times 2V_{CC} I_Q = V_T \times \left( \frac{V_{CC}}{R_L} \right)$$

$$\therefore \epsilon P_D = V_T \left( \frac{V_{CC}}{R_L} \right)$$

$$\text{d. } \epsilon P_D = V_T \frac{V_{CC}}{R_L} = 25 \times 10^{-3} \times \frac{15}{100}$$

$$= 3.75 \text{ mW}$$

$$P_D = \frac{3.75 \times 10^{-3}}{\epsilon}$$

$\epsilon$	$P_D$ in mW
0.05	75
0.02	187.5
0.01	375

### 13.15

$I_Q = I_{bias} = 0.5 \text{ mA}$ , neglecting the base current of  $Q_N$ . More precisely,

$$I_Q = I_{bias} - \frac{I_Q}{\beta + 1}$$

$$\Rightarrow I_Q = \frac{I_{bias}}{1 + \frac{1}{\beta + 1}} \approx 0.98 \times 0.5 = 0.49 \text{ mA}$$

The largest positive output is obtained when all of  $I_{bias}$  flows into the base of  $Q_N$ , resulting in

$$v_o = (\beta_N + 1)I_{bias}R_L$$

$$= 51 \times 0.5 \times 100 \Omega = 2.55 \text{ V}$$

The largest possible negative output voltage is limited by the saturation of

$$Q_P \text{ to } -10 + V_{ECSat} = -10 \text{ V}$$

To achieve a maximum positive output of 10 V without changing  $I_{bias}$ ,  $\beta_N$  must be

$$10 = (\beta_N + 1) \times 0.5 \times 100 \Omega$$

$$\Rightarrow \beta_N = 199$$

Alternatively, if  $\beta_N$  is held at 50,  $I_{bias}$  must be increased so that

$$10 = 51 \times I_{bias} \times 100 \Omega$$

$$\Rightarrow I_{bias} = 1.96 \text{ mA}$$

for which,

$$I_Q = \frac{I_{bias}}{1 + \frac{1}{\beta + 1}} = 1.92 \text{ mA}$$

### 13.16

$$\text{At } 20^\circ\text{C}, I_Q = 1 \text{ mA} = I_S e^{(0.6/0.025)}$$

$$\Rightarrow I_S \text{ (at } 20^\circ\text{C)} = 3.78 \times 10^{-11} \text{ mA}$$

$$\text{At } 70^\circ\text{C}, I_S = 3.78 \times 10^{-11} (1.14)^{50}$$

$$= 2.64 \times 10^{-8} \text{ mA}$$

$$\text{At } 70^\circ\text{C}, V_T = 25 \frac{273 + 70}{273 + 20} = 29.3 \text{ mV}$$

$$\text{Thus, } I_Q \text{ (at } 70^\circ\text{C)} = 2.64 \times 10^{-8} e^{(0.6/0.0293)}$$

$$= 20.7 \text{ mA}$$

$$\text{Additional current} = 20.7 - 1 = 19.7 \text{ mA}$$

$$\text{Additional power} = 2 \times 20 \times 19.7 = 788 \text{ mW}$$

$$\text{Additional temperature rise} = 10 \times 0.788 = 7.9^\circ\text{C}.$$

At  $77.9^\circ\text{C}$ :

$$V_T = \frac{25}{293} (273 + 77.9) = 29.9 \text{ mV}$$

$$I_Q = 3.78 \times 10^{-11} \times (1.14)^{57.9} e^{(0.6/0.0299)}$$

$$= 37.6 \text{ mA}$$

etc., etc.

### 13.17

Since the peak positive output current is 200 mA, the base current of  $Q_N$  can be as high as

$$\frac{200}{\beta_N + 1} = \frac{200}{51} \approx 4 \text{ mA. We select}$$

$I_{bias} = 5 \text{ mA}$ , thus providing the multiplier with a minimum current of 1 mA.

Under quiescent conditions ( $v_o = 0$  and  $i_L = 0$ ) the base current of  $Q_N$  can be neglected.

Selecting  $I_R = 0.5 \text{ mA}$  leaves  $I_{C1} = 4.5 \text{ mA}$ . To obtain a quiescent current of 2 mA in the output transistors,  $V_{BB}$  should be

$$V_{BB} = 2V_T \ln \frac{2 \times 10^{-3}}{10^{-15}} = 1.19 \text{ V}$$

Thus

$$R_1 + R_2 = \frac{V_{BB}}{I_R} = \frac{1.19}{0.5} = 2.38 \text{ k}\Omega$$

At a collector current of 4.5 mA,  $Q_1$  has

$$V_{BE1} = V_T \ln \frac{4.5 \times 10^{-3}}{10^{-14}} = 0.671 \text{ V}$$

The value of  $R_1$  can now be determined as

$$R_1 = \frac{0.671}{0.5} = 1.34 \text{ k}\Omega \text{ and}$$

$$R_2 = 2.58 - 1.34 = 1.04 \text{ k}\Omega$$

### 13.18

(a)  $V_{BE} = 0.7 \text{ V}$  at 1 mA

At 0.5 mA,

$$V_{BE} = 0.7 + 0.025 \ln \frac{0.5}{1} = 0.683 \text{ V}$$

13.19

$$\text{Thus } R_1 = \frac{0.683}{0.5} = 1.365 \text{ k}\Omega$$

and  $R_2 = 1.365 \text{ k}\Omega$

(b) For  $I_{\text{bias}} = 2 \text{ mA}$ ,  $I_C$  increases to nearly 1.5 mA for which

$$V_{BE} = 0.7 + 0.025 \ln \frac{1.3}{I} = 0.710 \text{ V}$$

Note that  $I_R = \frac{0.710}{1.365} = 0.52 \text{ mA}$  is very nearly

equal to the assumed value of 0.50 mA. Thus no further iterations are required.

$$V_{BB} = 2V_{BE} = 1.420 \text{ V}$$

(c) For  $I_{\text{bias}} = 10 \text{ mA}$ , assume that  $I_R$  remains constant at 0.5 mA, thus  $I_{C1} = 9.5 \text{ mA}$

$$\text{and } V_{BE} = 0.7 + 0.025 \ln \frac{9.5}{1} = 0.756 \text{ V}$$

at which

$$I_R = \frac{0.756}{1.365} = 0.554 \text{ mA}$$

Thus,

$$I_{C1} = 10 - 0.554 = 9.45 \text{ mA}$$

$$\text{and } V_{BE} = 0.7 + 0.025 \ln \frac{9.45}{1} = 0.756 \text{ V}$$

Thus  $V_{BB} = 2 \times 0.756 = 1.512 \text{ V}$

(d) Now for  $\beta=100$ ,

$$I_{R1} = \frac{0.756}{1.365} = 0.554 \text{ mA}$$

$$I_{R2} = 0.554 + \frac{9.45}{100} = 0.648 \text{ mA}$$


$$I_C = 10 - 0.648 = 9.352 \text{ mA}$$

$$\text{Thus, } V_{BB} = 0.7 + 0.025 \ln \frac{9.352}{1} = 0.756 \text{ V}$$

$$V_{BB} = 0.756 + I_{R2} R_2$$

$$= 0.756 + 0.648 \times 1.365$$

$$= 1.641 \text{ V}$$

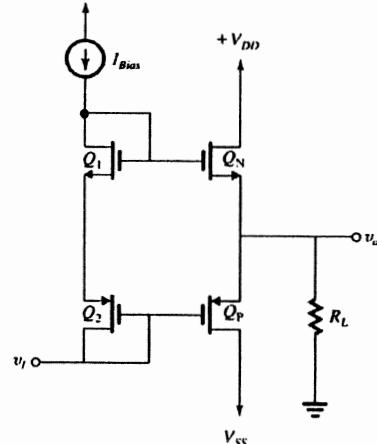

a. under quiescent condition

$$\text{Voltage gain} = \frac{v_o}{v_i} = \frac{R_L}{R_L + R_{out}}$$

As shown in problem 11.24, for matched transistors

$$R_{out} = \frac{1}{2g_m}$$

Substitute for  $R_{out}$  above for  $\frac{v_o}{v_i}$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + \frac{1}{2g_m}}$$

$$\text{b. Voltage gain} = 0.98 = \frac{R_L}{R_L + \frac{1}{2g_m}}$$

$$0.98 = \frac{1000}{1000 + \frac{1}{2g_m}}$$

$$\Rightarrow g_m = 24.5 \text{ mA/V}$$

For  $Q_1$ ,  $I_{\text{bias}} = I_D$

$$\therefore 0.1 = \frac{1}{2} k_T V_{ov}^2$$

$$0.1 = \frac{1}{2} \times 20 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = 0.1 \text{ V}$$

For  $Q_N$

$$g_m = k_n V_{ov}$$

$$24.5 = k_n \times 0.1$$

$$k_n = 245 \text{ mA/V}^2$$

$$n = \frac{k_n}{k_t} = \frac{245}{20}$$


$$= 12.25$$

and  $I_Q = nI_{bias}$

$$= 12.25 \times 0.1$$

$$= 1.225 \text{ mA}$$

### 13.20

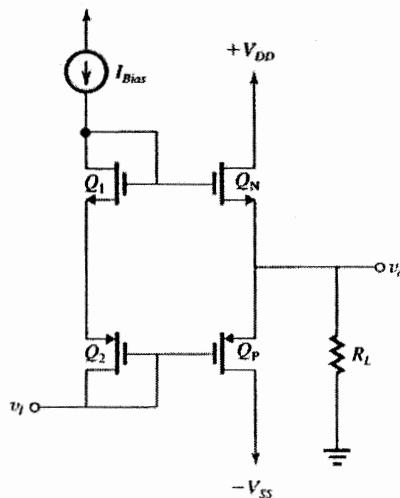

$$I_Q = I_{bias} \frac{(W/L)_n}{(W/L)_t}$$

$$1 = 0.1 \frac{(W/L)_n}{(W/L)_t}$$

$$\frac{(W/L)_n}{(W/L)_t} = 10$$

$$Q_N: I_{bias} = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_t V_{ov}^2$$

$$0.1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_t \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_t = 20$$

$$Q_N: 0.1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_t \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_t = 50$$

$$Q_N: 1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_N \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_N = 200$$

$$Q_P: 1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_P \times (0.2)^2$$

$$\left(\frac{W}{L}\right)_P = 500$$

b. From the circuit we get  $-v_t + V_{GSN} + v_o = 0$

Since  $v_o = 0$

$$v_t = V_{GSN}$$

$$V_{SGP} = |V_{ov}| + |V_t| \\ = 0.2 + 0.45 \\ = -0.65 \text{ V}$$

$$\therefore v_t = V_{GSN} = -0.65 \text{ V}$$

c. Using equation 11.4

$$v_{omax} = V_{DD} - V_{ov}|_{Bias} - V_{GSN}$$

To find  $V_{GSN}$ ,

$$i_{DNmax} = \frac{1}{2} k_n' \frac{W}{L} (V_{GSN} - V_t)^2$$

$$10 = \frac{1}{2} \times 0.250 \times 200 (V_{GSN} - V_t)^2$$

$$\Rightarrow V_{GSN} - V_t = 0.63 \text{ V}$$

$$V_{GSN} = V_t + 0.63 = 0.45 + 0.63 \approx 1.1 \text{ V}$$

$$\therefore v_{omax} = 2.5 - 0.2 - 1.1 = 1.2 \text{ V}$$

### 13.21

$$I_Q = 3 \text{ mA}, |V_{ov}| = 0.15 \text{ V}$$

$$g_{mn} = g_{mp} = \frac{2I_D}{V_{ov}} = \frac{2 \times 3}{0.15} = 0.04 \text{ A/V} \\ = 40 \text{ mA/V}$$

Using equation 11.57

$$R_{out} = \frac{1}{\mu(g_{mp} + g_{mn})} = \frac{1}{5(0.04 + 0.04)} \\ = 2.5 \Omega$$

### 13.22

$$|\text{Gain Error}| = \frac{1}{2\mu g_m R_L}$$

From equation 11.57

$$R_{mn} = \frac{1}{\mu(g_{mp} + g_{mn})} \\ = \frac{1}{2\mu g_m} \text{ when } g_{mp} = g_{mn} = g_m$$

$$\therefore |\text{Gain Error}| = \frac{1}{2\mu g_m} \times \frac{1}{R_L} \\ = \frac{R_{out}}{R_L}$$

$$|\text{Gain Error}| = \frac{1}{2\mu g_m R_L}$$

$$0.05 = \frac{1}{2 \times 10 \times g_m \times 100}$$

$$g_m = 0.01 \text{ A/V} = 10 \text{ mA/V}$$

$$g_m = \frac{2I_Q}{V_{ov}}$$

$$V_{ov} = \frac{2I_Q}{g_m} = \frac{2 \times 1}{10}$$

$$V_{ov} = 0.2 \text{ V}$$

13.23

$$\text{a. } I_Q = \frac{1}{2} k_n \frac{W}{L} V_{ov}^2$$

$$1.5 \times 10^{-3} = \frac{1}{2} \times 100 \times 10^{-6} \left( \frac{W}{L} \right)_p (0.15)^2$$

$$\Rightarrow \left( \frac{W}{L} \right)_p \geq 1333.3$$

$$\left( \frac{W}{L} \right)_N = \frac{(W/L)_P}{(k_n' / k_{Q_p})} = \frac{1333.3}{(250/100)} = 533.3$$

$$\text{b. } g_m = \frac{2I_Q}{V_{ov}} = \frac{2 \times 1.5}{0.15} = 20 \text{ mA/V}$$

$$= 0.02 \text{ A/V}$$

$$R_{\text{out}} = \frac{1}{2\mu g_m} \quad g_{op} = g_{av} = g_m$$

$$2.5 = \frac{1}{2\mu \times 0.02}$$

$$\mu = \frac{1}{2.5 \times 2 \times 0.02}$$

$$\mu = 10$$

$$\text{c. Gain Error} = -\frac{V_{ov}}{4\mu I_Q R_L}$$

$$= -\frac{0.15}{4 \times 10 \times 1.5 \times 10^{-3} \times 50}$$

$$= -0.05$$

Gain Error = 5%

d. In the quiescent state  $v_o = 0$

The voltage at the output of each amplifier will be

$$= \mu(v_i - v_t) = -\mu v_i$$

e.  $Q_1$  turn off when the voltage at its gate drops from quiescent value of  $-1.85 \text{ V}$  to  $-2 \text{ V}$ , at which point  $V_{GS1} = V_{th}$ , and an equal change of  $-0.15 \text{ V}$  appear at the output of the top amplifier.

$$i_P = \frac{1}{2} k_P \left( \frac{W}{L} \right)_p (0.3)^2$$

$$= \frac{1}{2} \times 0.100 \times 1333.3 \times 0.3^2$$

$$i_P = 6 \text{ mA}$$

$$v_o = 6 \times 10^{-3} \times 50 \Omega = 0.3 \text{ V}$$

So for  $v_o > 0.3 \text{ V}$ ,  $Q_1$  conducts all the current.

f. the situation at  $v_o = v_{max}$  will occur when  $Q_1$  will go from saturation to triode region and it will be approximately  $2 \text{ V}$ .

Linear range of  $v_o$  from 2 to  $-2 \text{ V}$

13.24

$$\theta_{JA} = \frac{150 - 25}{0.2} = 625^\circ \text{C/W} = 0.625^\circ \text{C/mW}$$

At  $70^\circ \text{C}$ , Power rating

$$= \frac{150 - 70}{0.625} = 128 \text{ mW}$$

$$T_J = 50 + 0.625 \times 100 = 112.5^\circ \text{C}$$

13.25

$$\text{(a) } \theta_{JA} = \frac{T_{Jmax} - T_{A0}}{P_{D0}}$$

$$= \frac{100 - 25}{2} = 37.5^\circ \text{C/W}$$

(b) At  $T_A = 50^\circ \text{C}$

$$P_{Dmax} = \frac{T_{Jmax} - T_A}{\theta_{JA}}$$

$$= \frac{100 - 50}{37.5} = 1.33 \text{ W}$$

$$\text{(c) } T_J = 25^\circ + 37.5 \times 1 = 62.5^\circ \text{C}$$

13.26

$$T_C - T_A = \theta_{CA} P_D$$

$$= (\theta_{CS} + \theta_{SA}) P_D$$

$$\Rightarrow P_D = \frac{T_C - T_A}{\theta_{CS} + \theta_{SA}} = \frac{90 - 30}{0.5 + 0.1} = 100 \text{ W}$$

$$T_J - T_C = \theta_{JC} P_D$$

$$130 - 90 = \theta_{JC} \times 100$$

$$\Rightarrow \theta_{JC} = 0.4^\circ \text{C/W}$$

13.27

$$\theta_{JC} = \frac{T_J - T_C}{P_D} = \frac{180^\circ - 50^\circ}{50} = 2.6^\circ \text{C/W}$$

$$T_J - T_S = \theta_{JS} P_D$$

$$180^\circ - T_S = (\theta_{JC} + \theta_{CS}) P_D$$

$$\Rightarrow T_S = 180 - (2.6 + 0.6) \times 30 = 84^\circ$$

$$T_S - T_A = \theta_{SA} P_D$$

$$84 - 39 = \theta_{SA} \times 30$$


$$\Rightarrow \theta_{SA} = 1.5^\circ \text{C/W}$$

$$\text{Required heat-sink length} = \frac{4.5^\circ \text{C/W/Cm}}{1.5^\circ \text{C/W}}$$

$$= 3 \text{ cm}$$

13.28

(a) For  $R_L = \infty$ :

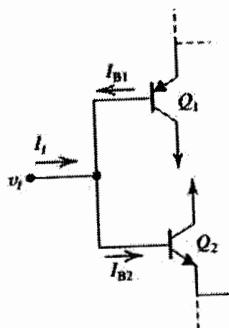

At  $v_i = 0$  V,

$$I_{B1} = I_{B2} = \frac{2.87}{200}$$

$$I_f = I_{B2} - I_{B1} = 0$$

At  $v_i = +10$  V,

$$I_{B1} = \frac{0.88}{200} \text{ mA} = 4.4 \mu\text{A}$$

$$I_{B2} = \frac{4.87}{200} \text{ mA} = 24.4 \mu\text{A}$$

$$I_f = I_{B2} - I_{B1} = 20 \mu\text{A}$$

At  $v_i = -10$  V,

$$I_{B1} = \frac{4.87}{200} \text{ mA} = 24.4 \mu\text{A}$$

$$I_{B2} = \frac{0.88}{200} \text{ mA} = 4.4 \mu\text{A}$$

$$I_f = I_{B2} - I_{B1} = -20 \mu\text{A}$$

(b) For  $R_L = 100 \Omega$ :

At  $v_i = 0$  V,  $I_f = 0$

At  $v_i = +10$  V,

$$I_{B1} = \frac{0.38}{200} = 1.9 \mu\text{A}$$

$$I_{B2} = \frac{4.87}{200} = 24.4 \mu\text{A}$$

$$I_f = I_{B2} - I_{B1} = 22.5 \mu\text{A}$$

$$\text{At } v_i = -10 \text{ V}, I_f = -22.5 \mu\text{A}$$

13.29

Circuit operating near  $v_i = 0$  and is fed with a signal source having zero resistance.


The resistance looking as shown by the arrow X is  $= R_1 \parallel r_{e1}$

This resistance is reflected from base to the emitter of  $Q_3$  is  $= (\beta_3 + 1)/(R_1 \parallel r_{e1})$


This resistance seen as shown by arrow Y, from the upper half of the circuit =  $R_3 + r_{e3} + (\beta_3 + 1)/(R_1 \parallel r_{e1})$

A similar resistance is as shown by the arrow Z and both of these resistances (seen arrow Y and arrow Z) are parallel, therefore
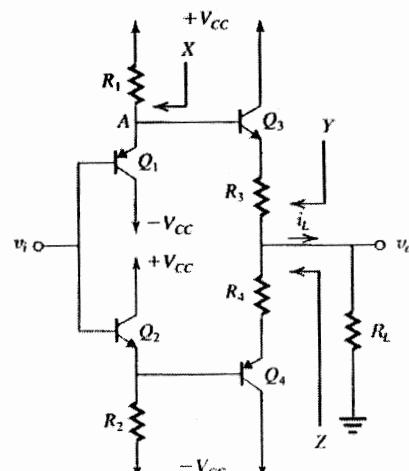
$$R_{\text{out}} = \frac{1}{2} [R_3 + r_{e3} + (R_1 \parallel r_{e1}) / (\beta_3 + 1)]$$



13.30

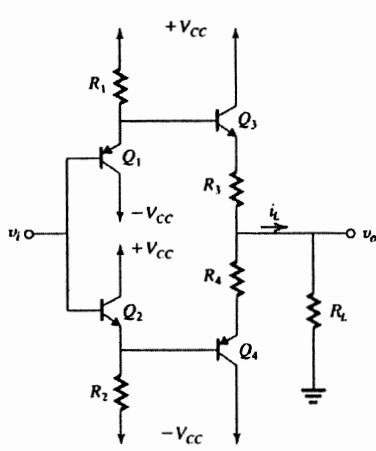

At  $v_i = 5V$ , the voltage  $V_{ce}$  across the resistor  $R_1$  is  
 $v_{ce} = V_{cc} - 0.7 - 5 = 4.3V$

$$i_{c1} = 2 \times 10 \text{ mA}$$

The current  $i_{c1}$  should be enough to allow for  $i_{c3}$ , as much as 10 mA and only a 2 to 1 variation in  $i_c$ ,

$$\therefore R_1 = \frac{V_{ce}}{i_{c1}} = \frac{4.3}{20 \text{ mA}} = 215 \Omega = 0.215 \text{ k}\Omega$$

Similarly  $R_2 = 215 \Omega = 0.215 \text{ k}\Omega$

Now solve for  $R_3$  and  $R_4$

For  $v_i = 0$  and  $V_{ce1} \approx 0.7V$

$$i_{c1} = \frac{10 - 0.7 - 0}{215} = 43.3 \text{ mA}$$

$$v_{E1} = 0.7 + 25 \times 10^{-3} \ln \left( \frac{43.3}{10} \right) = 0.7366 \text{ V}$$

$$\approx 0.74 \text{ V}$$

In  $Q_1$ ,  $I_q = 40 \text{ mA}$  and  $I_{c1} = 3I_q = 30 \text{ mA}$

$$v_{BE1} = 0.7 + 25 \times 10^{-3} \ln \left( \frac{40}{30} \right) = 0.7072 \text{ V}$$

$$R_3 = \frac{V_{E1} - V_{BE1}}{I_{c3}} = \frac{0.7366 - 0.7072}{40 \times 10^{-3}} \approx 0.74 \Omega$$

Similarly  $R_4 = 0.74 \Omega$

Output Resistance at  $v_i = 0$

$$R_{out} = \frac{1}{2} \left( R_3 + r_{e1} + \frac{r_{e1}}{\beta_3 + 1} \parallel R_1 \right)$$

$$\approx \frac{1}{2} \left( R_3 + r_{e1} + \frac{r_{e1}}{\beta_3 + 1} \right) \text{ Since } r_{e1} \parallel R_1 \approx r_{e1}$$

This  $\frac{1}{2}$  is there because of two paths to output.

$$r_{e1} \approx r_{e1} = \frac{25 \text{ mV}}{40 \text{ mA}} = 0.625 \Omega$$

$$R_{out} = \frac{1}{2} \left( 0.735 + 0.625 + \frac{0.625}{50 + 1} \right)$$

$$\approx 0.69 \Omega$$

Output voltage for  $v_i = 1 \text{ V}$  and  $R_L = 2 \Omega$

Let  $v_i = 1 \text{ V}$

$$i_L = \frac{1 \text{ V}}{2 \Omega} = 500 \text{ mA}$$

$$i_{c3} = \frac{500}{50} = 10 \text{ mA}$$

$$I_{c1} = \frac{10 - 0.7 - 1}{0.215 \text{ k}\Omega} = 10 = 28.6 \text{ mA}$$

So

$$V_{E1} = 0.7 + 25 \times 10^{-3} \ln \left( \frac{28.6}{10} \right) = 0.726 \text{ V}$$

$$V_{ce} = v_i + V_{ce1} = 1 + 0.726 = 1.726 \text{ V}$$

Assuming  $i_{c2} \approx 0$

$$V_{BE3} = 0.7 + 0.025 \ln \left( \frac{500}{30} \right)$$

$$\therefore i_{c3} = i_L = 500 \text{ mA}$$

$$= 0.770 \text{ V}$$

$$\therefore i_L = \frac{1.726 - 0.770}{0.74 + 2} = 0.349 \text{ A} \approx 0.35 \text{ A}$$

This value of  $i_L$  gives

$$v_i = 2 \Omega \times 0.349 \text{ A} = 0.698 \text{ V}$$

The voltage drop across the series combination of  $R_4$  and the emitter base junction of  $Q_3$  can be determined as follows

$$V_{ce} = V_{i2} = V_i - V_{ce2} = 1 - 0.74 \\ = 0.26 \text{ V}$$

$V_{ce} = 0.26 \text{ V}$ , leaves a drop across  $V_{ce2}$  and  $R_4$  of  $v_o - V_{ce}$ , that is  $0.698 - 0.26 = 0.438$  and this will give  $i_{c2} \approx 0$  as assumed earlier.

Do one more iteration

$$i_L \approx 0.35 \text{ A}$$

$$i_{c3} \approx \frac{0.35}{51} \approx 7 \text{ mA}$$

$$i_{c1} = \frac{10 - 1 - 0.73}{0.215 \text{ k}\Omega} = 31.5 \text{ mA}$$

$$V_{E1} = 0.7 + 0.025 \ln \left( \frac{31.5}{10} \right) = 0.729 \text{ V}$$

$$V_{ce1} = 1 + 0.729 = 1.729 \text{ V}$$

$$V_{BE3} = 0.7 + 0.025 \ln \left( \frac{31.5}{10} \right) = 0.729 \text{ V}$$

$$= 0.761 \text{ V}$$

Here  $i_{c3} = i_L = 0.35 \text{ A} = 350 \text{ mA}$

$$i_L = \frac{1.729 - 0.761}{2 + 0.74} = 0.353 \text{ A}$$

$$v_o = 2 \Omega \times 0.353 \text{ A}$$

$$= 0.706 \text{ V}$$

13.31

a.  $v_i = 0$  and transistors have  $\beta = 100$

$$I_Q \equiv I_{E3} = I_{E4} = I_{E1} = I_{E2} \approx 1 \text{ mA}$$

$$\text{More precisely } I_Q = \frac{\beta}{\beta + 1} \times 1 = 0.99 \text{ mA}$$

Input bias current in zero because  $I_{B1} = I_{B2}$


output voltage = 0 V

$$2R_{out} = r_{e1} + \frac{r_{e2}}{\beta + 1}$$

$$= 25 + \frac{25}{101}$$

$$R_{out} = 12.6 \Omega$$

13.32

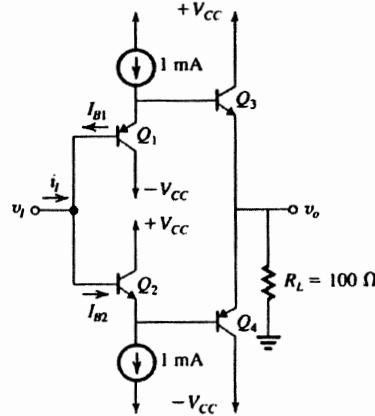


b. From the equivalent half circuit

$$2R_i = (\beta_1 + 1)[r_{e1} + (\beta_3 + 1)(r_{e3} + 2R_2)]$$

$$r_{e1} = r_{e3} = \frac{V_T}{I_E} = \frac{25}{1} = 25 \Omega$$

$$2R_i = (100 + 1)[25 + (100 + 1)(25 + 2 \times 100)]$$

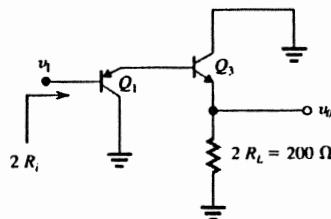
$$\Rightarrow R_i = 1.15 \text{ M}\Omega$$



$$A_v = \frac{v_o}{v_i} = \frac{2R_L}{2R_L + r_{e1} + \frac{r_{e1}}{\beta_1 + 1}}$$

$$= \frac{200}{200 + 25 + \frac{25}{101}}$$

$$\approx 0.89 \text{ V/V}$$

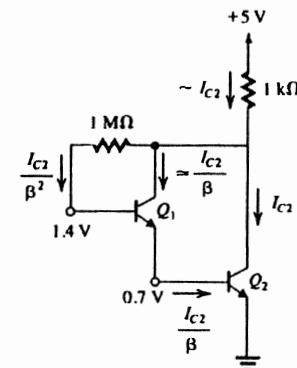

a. DC Analysis

Current through 1 kΩ ≈  $I_{C2}$

$$5 = 1k \times I_{C2} + 1M \times \frac{I_{C2}}{\beta^2} + 1.4$$

$$I_{C2} = \frac{3.6}{1 + \frac{1000}{\beta^2}} \text{ in mA}$$

$$= 3.3 \text{ mA}$$


$$I_{C1} = \frac{I_{C2}}{\beta} = \frac{3.3}{100} = 0.033 \text{ mA}$$

$$\begin{aligned} b. i_C &= g_m v_{be2} \\ &= g_m \frac{(\beta_2 + 1)r_{e2}}{r_{e1} + (\beta_2 + 1)r_{e2}} \times v_i \end{aligned}$$

$$\text{But } r_{e1} = \frac{V_T}{I_{E1}} = \frac{V_T}{I_{C2}} \approx r_{e2}(\beta_2 + 1)$$

$$i_C = g_m \frac{r_{e2}}{\beta_2 + 1} \cdot v_i$$

13.33

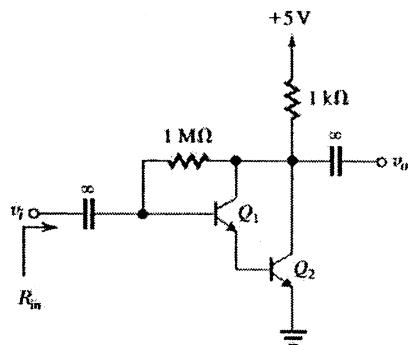

$$i_C = \frac{g_m r_{e2}}{r_{e2} + r_{e2}} \cdot v_i$$

But  $g_m r_{e2} \approx 1$

$$i_C \approx \frac{v_i}{2r_{e2}}$$

For this circuit  $g_m$  equi. is

$$g_m \text{ equi.} \approx \frac{i_C}{v_i} = \frac{1}{2r_{e2}} = \frac{1}{2 \times \frac{V_T}{I_{C2}}} = 66 \text{ mA/V}$$

Now  $v_o \approx -i_C \times 1 \text{ k}$

$$= -g_m \text{ equi.} \times v_i \times 1 \text{ k}$$

$$\frac{v_o}{v_i} = -66 \frac{\text{mA}}{\text{V}} \times 1 \text{ k} = -66 \text{ V/V}$$

c.  $i_i = i_{b1} + i_{1\text{MD resistor}}$

$$\approx \frac{i_C}{\beta^2} + \frac{v_i - v_o}{1 \text{ M}\Omega}$$

$$= \frac{1}{\beta^2} \times \frac{v_i}{2r_{e2}} + \frac{v_i - (-66 v_i)}{1 \text{ M}\Omega}$$

$$i_i = \frac{v_i}{2\beta^2 r_{e2}} + \frac{67 v_i}{1 \text{ M}\Omega}$$

$$= v_i \left[ \frac{1}{2 \times 100^2 \times \frac{25}{3.3}} + \frac{67}{1 \text{ M}} \right]$$

$$= v_i (6.6 + 67) \times 10^{-6}$$

$$R_{in} = \frac{v_i}{i_i} = 13.6 \text{ k}\Omega$$

The quiescent current through  $Q_2$  and  $Q_1$  is to be 2 mA. Then

$$V_{BE2} = V_{BE1} = 0.7 + 0.025 \ln \left( \frac{2}{10} \right) = 0.660 \text{ V}$$

For  $Q_1$  and  $Q_2$ ,  $I_C \approx \frac{2}{100} = 0.02 \text{ mA}$ , thus

$$V_{BE1} = V_{EB3} = 0.7 + 0.025 \ln \frac{0.02}{1} = 0.602 \text{ V}$$

$$I_{BL} = \frac{20 \mu\text{A}}{100} = 0.2 \mu\text{A}$$

$$I_{bias} = 100 \times 0.2 = 20 \mu\text{A}$$

$$I_{R_1 R_2} = \frac{1}{10} \times 20 \mu\text{A} = 2 \mu\text{A}$$

$$I_{CS} = 20 - 2 = 18 \mu\text{A}$$

$$V_{BES} = 0.7 + 0.025 \ln \frac{0.018}{1} = 0.600 \text{ V}$$

$$V_{BB} = V_{BE1} + V_{BE2} + V_{EB3} = \underline{1.864 \text{ V}}$$

$$R_1 + R_2 = \frac{1.864}{2 \mu\text{A}} = 932 \text{ k}\Omega$$

$$R_1 = \frac{0.600}{2 \mu\text{A}} = \underline{300 \text{ k}\Omega}$$

$$R_2 = 932 - 300 = \underline{632 \text{ k}\Omega}$$

For  $V_O = -10 \text{ V}$  and  $R_L = 1 \text{ k}\Omega$ :

$$i_L = \frac{-10}{1} = -10 \text{ mA}$$

Assume that the current through  $Q_2$  becomes almost zero, thus

$$I_{CA} = 10 \text{ mA}$$

i.e. the current through  $Q_1$  increases by a factor of 5. It follows that the current through  $Q_3$  must increase by the same factor, thus  $V_{EB3}$  becomes

$$V_{EB3} = 0.602 + 0.025 \ln 5$$

$$= 0.642 \text{ V} \quad (\text{an increase of } 0.04 \text{ V})$$

Let us check the current through  $Q_2$ . Since we assumed  $Q_1$  and  $Q_2$  to be almost cut off, all of  $I_{bias}$  now flows through the  $V_{BE}$  voltage, an increase of  $0.2 \mu\text{A}$ . Assuming that most of this increase occurs in  $I_{CS}$ ,  $V_{BES}$  becomes

$$V_{BES} = 0.7 + 0.025 \ln \frac{0.018}{1} = 0.608 \text{ V}$$

Thus the voltage across the  $V_{BE}$ -multiplier remains approximately constant and the voltage ( $V_{BE1} + V_{BE2}$ ) decreases by the same value that  $V_{EB3}$  increases by. That is

$$V_{BE1} + V_{BE2} = 0.660 + 0.602 - 0.04$$

Since the current through each of  $Q_1$  and  $Q_2$  decreases by the same factor (call it  $m$ ),

$$0.025 \ln m + 0.025 \ln m = -0.04 \text{ V}$$

$$\Rightarrow m = 0.45$$

$$\text{Thus } I_{C2} = 0.45 \times 2 = 0.9 \text{ mA}$$

New iteration:  $I_{C1} = 10.9 \text{ mA}$  (an increase by a factor  $\approx 5.5$ ).

$$V_{EB3} = 0.602 + 0.025 \ln 5.5$$

$$= 0.645 \text{ V}$$

$$V_I \approx -10.645 \text{ V}$$

For  $V_D = +10 \text{ V}$  and  $R_L = 1k\Omega$ :

Assume that  $Q_3$  is now conducting a negligible current. Then,  $I_{C2} \approx I_L = 10 \text{ mA}$ . i.e. the currents through each of  $Q_1$  and  $Q_2$

increase by a factor of 5. Thus

$$V_{BE2} = 0.66 + 0.025 \ln 5$$

$$= 0.700 \text{ V}$$

$$V_{BE1} = 0.602 + 0.025 \ln 5 = 0.642 \text{ V}$$

$$I_{B1} = 5 \times 0.2 = 1 \mu\text{A}$$

Thus the current through the multiplier becomes  $19 \mu\text{A}$ , and assuming that most of the decrease occurs in  $I_{C3}$ ,

$$V_{BES} = 0.7 + 0.025 \ln \frac{0.017}{1}$$

$$= 0.598 \text{ V}$$

Thus the voltage across the multiplier becomes

$$V_{BB} = 0.598 \times \frac{932}{300} = 1.858 \text{ V}$$

It follows that  $V_{EB3}$  becomes

$$V_{EB3} = 1.858 - 0.700 - 0.642 = 0.516 \text{ V}$$

i.e.  $V_{EB3}$  decreases by  $0.600 - 0.516 = 0.084 \text{ V}$

and corresponding  $I_{C3}$  decreases by a factor of  $e^{-0.084/0.025} = 0.035$ . Thus  $I_{C3}$  becomes  $0.035 \times 2 = 0.07 \text{ mA}$ , close to the zero value assumed. Thus no further iteration are required and

$$V_I \approx 10 + 0.7 + 0.642 - 1.858$$

$$= \underline{\underline{+9.484 \text{ V}}}$$

### 13.34

Now  $Q_3$  has  $I_S = 10^{-13} \text{ A}$ . Thus,

$$2 \times 10^{-3} = 10^{-13} e^{\frac{V_{BE}}{V_T}}$$

$$V_{BE} = 0.025 \ln \frac{2 \times 10^{-3}}{10^{-13}}$$

$$= 0.593 \text{ V}$$

$$R_{E1} = \frac{0.593}{150 \text{ mA}} \approx 4 \Omega$$

For a normal peak current of  $100 \text{ mA}$ , the voltage drop across  $R_{E1}$  is  $400 \text{ mV}$  and its collector current is  $10^{-13} e^{400/25} = 0.89 \mu\text{A}$

13 . 35

$$2 \times 10^{-3} = 10^{-14} e^{V_{BE}/V_T}$$

$$\Rightarrow V_{BE} = 0.650 \text{ V}$$

$$R_{E1} = \frac{0.650 \text{ V}}{50 \text{ mA}} = 13 \Omega$$

For a peak output current of 33.3 mA,

$$V_{RE} = 13 \times 33.3 = 433 \text{ mV}$$

$$I_{CS} = 10^{-14} e^{433/25} = 0.33 \mu\text{A}$$

13 . 36

$$2 \times 10^{-3} = 10^{-14} e^{V_{EB5}/V_T}$$

$$V_{EB5} = 0.025 \ln(2 \times 10^{-11})$$

$$= 0.650 \text{ V}$$

$$R = \frac{0.650 \text{ V}}{150 \text{ mA}} = 4.3 \Omega$$

For a peak output current of 100 mA,  
 $V_{EB5} = 430 \text{ mV}$

$$I_{CS} = 10^{-14} e^{430/25} = 0.3 \mu\text{A}$$

13 . 37

At 125°C.

$$V_Z = 6.8 + (125 - 25) \times 2 = 7.0 \text{ V}$$

$$V_{E1} = 7.0 - (0.7 - 100 \times 0.002)$$

$$= 6.5 \text{ V}$$

$$V_{BE2} = 0.5 \text{ V}$$

$$R_2 = \frac{0.5 \text{ V}}{100 \mu\text{A}} = 5 \text{ k}\Omega$$

$$R_1 = \frac{6.5 - 0.5}{100 \mu\text{A}} = 60 \text{ k}\Omega$$

At 25°C,  $V_Z = 6.8 \text{ V}$ ,

$$V_{E1} = 6.8 - 0.7 = 6.1 \text{ V}$$

$$V_{B2} = 6.1 \times \frac{5}{60 + 5} = 0.469 \text{ V}$$

$$I_{C2} = 100 e^{(469 - 700)/25} = 0.01 \mu\text{A}$$

13 . 38

$$V_{B1} = 0$$

$$V_{E1} = +0.7 \text{ V}$$

$$V_{E3} = +1.4 \text{ V}$$

$$V_{C10} = 20 - 0.7 = 19.3 \text{ V}$$

$$I_{E3} = \frac{19.3 - 1.4}{50} = 0.358 \text{ mA}$$

$$I_{BS} = I_{E1} = \frac{0.358}{21} = 17.05 \mu\text{A}$$

$$I_{B1} = \frac{17.05}{21} = 0.81 \mu\text{A}$$

$$V_{B1} = 0.81 \mu\text{A} \times 150 \text{ k}\Omega = 0.122 \text{ V} \geq 0$$

$$\text{i.e. } I_{E1} = I_{E2} = 17 \mu\text{A}$$

$$I_{E3} = I_{E4} = 358 \mu\text{A}$$

$$I_{E5} = I_{E6} = \frac{20}{21} \times 358 = 341 \mu\text{A}$$

$$I_{R1} = I_{R2} = 358 \mu\text{A}$$

$$V_o = 0.12 + 1.4 + 25 \text{ k}\Omega \times 0.358 \text{ mA} = 10.5 \text{ V}$$

13 . 39 for 8Ω load, we see that  $V_S = 16 \text{ V}$

allows more than 1.5 W power dissipation for some input signals. Thus we use

$$V_S = 14 \text{ V}$$

For THD = 3%,  $P_{Lmax} = 1.9 \text{ W}$

$$1.9 = V_o^2 / R_L = V_o^2 / 8$$

$$V_o = \sqrt{8 \times 1.9}$$

Peak-to-Peak output sinusoid

$$= 2\sqrt{2} \sqrt{8 \times 1.9} = 11 \text{ V}$$

### 13.40

For  $i_L = 1\text{A}$ ,  $i_{C3} \approx 1\text{A}$  and  $i_{B3} = \frac{1\text{A}}{50} = 20\text{ mA}$

$$i_{E3} = 0.9 \times 20 = 18\text{ mA}$$

↑ 10%

For  $i_L = 20\text{ mA}$ ,

$$i_{C3} = 2\text{ mA} - i_{B3} = \frac{2}{50} = 0.04\text{ mA}$$

$$i_{C3} = \frac{50}{51} \times 18 = 17.65\text{ mA}$$

$$i_{B3} = i_{C3} - i_{B3} = 17.61\text{ mA}$$

$$\text{Thus, } R_3 = \frac{0.7}{17.61} = 39.8 \approx 40\Omega$$

Similarly,  $R_4 = 40\Omega$

$$\text{Since } i_{B3} \leq 20\text{ mA}, i_{C3} \leq \frac{0.7}{40} \text{ V} + 20\text{ mA}$$

i.e.  $i_{C3} \leq 37.5\text{ mA}$

$$i_{B3} \leq \frac{37.5}{50} = 0.75\text{ mA}$$

Allowing for a factor of safety of 2, we select  $R_1$  so that the current through it is 1.5 mA. Now, for  $V_o = 11\text{ V}$ ,  $V_{E1} = 11.7\text{ V}$ ,

$$R_1 = \frac{15 - 11.7}{1.5} = 2.2\text{ k}\Omega$$

Similarly,

$$R_2 = 2.2\text{ k}\Omega$$

### 13.41


$$\frac{v_o}{v_i} = 2K = 2\left(1 + \frac{R_2}{R_1}\right) = 10$$

$$\Rightarrow \frac{R_2}{R_1} = 4 \quad R_2 = 40\text{ k}\Omega$$

$$\text{Also, } K = \frac{R_4}{R_3} = 5$$

$$\Rightarrow R_4 = 50\text{ k}\Omega$$

### 13.42

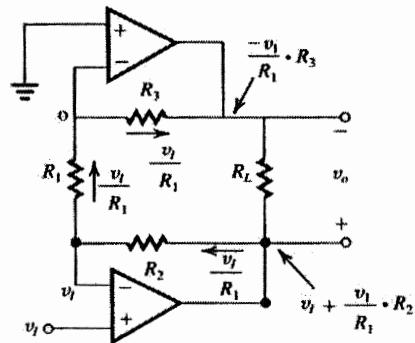

As shown on the diagram

$$\begin{aligned} v_o &= \left(v_i + \frac{V_I}{R_1} \cdot R_2\right) - \left(\frac{v_i}{R_1} \cdot R_3\right) \\ &= v_i \left(1 + \frac{R_2}{R_1} + \frac{R_3}{R_1}\right) = v_i \left(1 + \frac{R_2 + R_3}{R_1}\right) \end{aligned}$$

The largest sine wave output is obtained when the output voltage of one op amp is +13 V and the output voltage of the other op amp is -13 V, which results in A 26 V peak output

$$\text{For } \frac{v_o}{v_i} = 10 = 1 + \frac{R_2 + R_3}{R_1} \text{ choose}$$

$$R_1 = 1\text{ k}\Omega \text{ and } (R_2 + R_3) = 9\text{ k}\Omega$$

To keep the output complementary

$$\frac{R_3}{R_1} = 1 + \frac{R_2}{R_1} \text{ here } R_1 = 1\text{ k}\Omega$$

$$\Rightarrow R_3 = 1 + R_2$$

$$\text{So } R_2 = 4\text{ k}\Omega, R_3 = 5\text{ k}\Omega$$

### 13.43

For

$$I_{Q8} = I_{Dp} = 10 \text{ mA} = \mu C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$10 = 100(V_{GS} - 2)^2$$

$$\Rightarrow V_{GS} = 2.32 \text{ V}$$

$$V_R = 2|V_{GS}| = 4.63 \text{ V}$$

For  $I_R = 10 \text{ mA}$ ,

$$R = \frac{4.63 \text{ V}}{10 \text{ mA}} = 463 \Omega$$

$$V_{BB} = 4.63 + 4 \times 0.7 = 7.43 \text{ V}$$

$$I_{R2} = I_{R4} = \frac{100}{2} = 50 \mu\text{A}$$

$$R_2 = R_4 = \frac{700 \text{ mV}}{50 \mu\text{A}} = 14 \text{ k}\Omega$$

Now, since  $V_{GS}$  changes by

$2 \times -3 \text{ mV}/{}^\circ\text{C} = -6 \text{ mV}/{}^\circ\text{C}$  while  $V_{BE1}$ ,

$V_{BE2}$ ,  $V_{BE3}$  and  $V_{BE4}$  remain constant,  $V_{BB}$  changes by  $-6 \text{ mV}/{}^\circ\text{C}$ . But the voltage across the  $Q_5$  multiplier remains constant. Thus the voltage across the  $Q_6$  multiplier should be made to change by  $-6 \text{ mV}/{}^\circ\text{C}$  which can be achieved by making

$$1 + \frac{R_3}{R_4} = 3$$

$$\Rightarrow R_3 = 2R_4 = 28 \text{ k}\Omega$$

The voltage across the  $Q_5$  multiplier is

$$V_{BB} - 3V_{BE6} = 7.43 - 2.1 = 5.33 \text{ V}$$

$$\text{Thus, } 5.33 = \left(1 + \frac{R_1}{R_2}\right) \times 0.7$$

$$\Rightarrow \frac{R_1}{R_2} = 6.61$$

But  $R_2 = 14 \text{ k}\Omega$ , thus


$$R_1 = 92.6 \text{ k}\Omega$$

14.1

$$NM_H = V_{OH} - V_{IH} = 3.3 - 1.7 = 1.6 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 1.3 - 0 = 1.3 \text{ V}$$

14.2

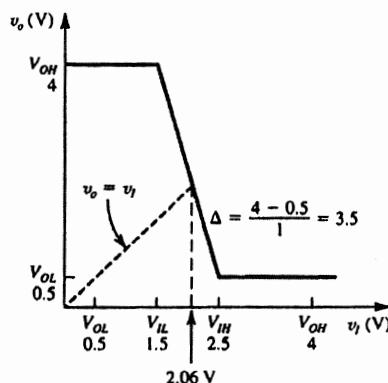

$$(a) NM_H = V_{OH} - V_{IH} = 4 - 2.5 = 1.5 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 1.5 - 0.5 = 1 \text{ V}$$

(b) In the transition region

$$\begin{aligned} V_o &= 4 - 3.5(V_i - 1.5) \\ &= 9.25 - 3.5V_i \end{aligned}$$

If

$$V_o = V_i \Rightarrow 4.5V_o = 9.25$$

$$V_o = V_i = 2.06 \text{ V}$$

(c) Slope =  $-3.5 \text{ V/V}$

14.3

$$NM_H = V_{OH} - V_{IH} = 0.8V_{DD} - 0.6V_{DD} = 0.2V_{DD}$$

$$NM_L = V_{IL} - V_{OL} = (0.4 - 0.1)V_{DD} = 0.3V_{DD}$$


width of transition region

$$= V_{IH} - V_{IL} = 0.2V_{DD} \text{ for a minimum NM of}$$

$$1 \text{ V} \Rightarrow 0.2V_{DD} = 1$$

$$V_{DD} = 5 \text{ V}$$

14.4

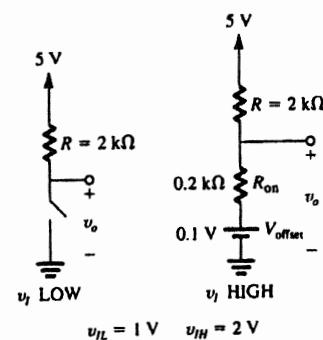

$$(a) V_{OL} = \frac{5 - 0.1}{2.2} = 0.2 + 0.1 = 0.545 \text{ V}$$

$$V_{OH} = 5 \text{ V}$$

$$NM_H = V_{OH} - V_{IH} = 3 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 0.455 \text{ V}$$

$$(b) V_{OH} = 5 - N(0.2 \times 10^{-3})R = 5 - 0.4N$$

$$NM_H = 5 - 0.4N - 2 = 3 - 0.4N = 0.455 \quad \therefore N = 6$$

$$(c) (i) P_{D_{v_o, \text{Low}}} = (5 - 0.1)^2 / 2.2 \text{ k}\Omega = 10.9 \text{ mW}$$

$$(ii) P_{D_{v_o, \text{HIGH}}} = 5 \times (0.2 \times 6) = 6 \text{ mW}$$

14.5

Ideal 3V logic implies :

$$V_{OH} = V_{DD} = \underline{\underline{3.0V}} ; V_{OL} = \underline{\underline{0.0V}}$$

$$V_{th} = V_{DD}/2 = 3.0/2 = \underline{\underline{1.5V}}$$

$$V_{IL} = V_{DD}/2 = \underline{\underline{1.5V}} ; V_{IH} = V_{DD}/2 = \underline{\underline{1.5V}}$$


$$NM_H = V_{OH} - V_{IH} = 3.0 - 1.5 = \underline{\underline{1.5V}}$$

$$NM_L = V_{IL} - V_{OL} = 1.5 - 0.0 = \underline{\underline{1.5V}}$$

The gain in the transition region is :

$$(V_{OH} - V_{OL}) / (V_{IH} - V_{IL}) =$$
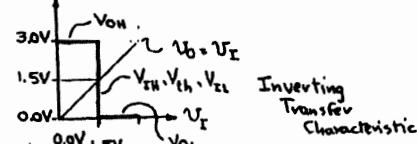
$$\infty \quad (3.0 - 0.0) / (1.5 - 1.5) = 3/0 = \underline{\underline{\infty}}$$



### 14.6

Nearly ideal 3.3V logic, assumed ideal:

$$\rightarrow V_{OH} = 3.3V \quad V_{OL} = 0.0V \quad V_{IH} = 0.4(3.3) = 1.32V$$

Now, at  $V_{th}$ ,  $V_o = V_i$ , so to reach  $V_o = 1.32V$

the required input is  $1.32/(-50) = -26.4mV$

$$\text{Thus, } V_{IL} = 1.32 - 26.4 \times 10^{-3} = 1.294V$$

$$\text{Likewise, } V_{IH} = 1.32 + (3.3 - 1.32)/50 = 1.360V$$

Best possible noise margins are:

$$NM_H = V_{OH} - V_{IH} = 3.30 - 1.360 = 1.940V$$

$$NM_L = V_{IL} - V_{OL} = 1.294 - 0.0 = 1.294V$$

For noise margins only 7/10 of these, and


$V_{OH}, V_{OL}$  still ideal:

$$V_{IH} = 3.3 - 0.7(1.940) = 1.942V, \text{ and}$$

$$V_{IL} = 0.0 + 0.7(1.294) = 0.906V$$

Correspondingly, the large-signal voltage gain is:  
 $G = (3.3 - 0.0)/(0.906 - 1.942) = -3.18V/V$

### 14.7

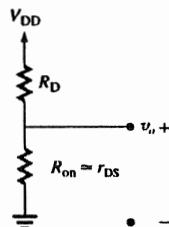

Equivalent circuit for output-low state

The output high level for the simple inverter circuit shown in Fig 13.2 of the Text is

$$V_{OH} = V_{DD} \Rightarrow V_{DD} = 2V.$$

When the output is low, the current drawn from the supply can be calculated as:

$$I = \frac{V_{DD}}{R_D + R_{DS}} = 20 \mu A$$

$$\text{Therefore: } R_D + r_{DS} = \frac{2}{20 \times 10^{-6}} = 100 k\Omega$$

Also:

$$V_{OL} = 0.1V = \frac{r_{DS}}{R_D + r_{DS}} \times V_{DD}$$

$$\Rightarrow r_{DS} = 100 k\Omega \times \frac{0.1}{2} = 5 k\Omega$$

$$\text{Hence: } R_D = 100 k\Omega - 5 k\Omega = 95 k\Omega$$

$$r_{DS} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)} = \frac{1}{100 \times 10^{-6} \times \frac{W}{L} (2 - 0.5)}$$

$$= 5 k\Omega$$

$$\frac{W}{L} = \frac{10}{1.5 \times 5} = 1.3$$

when the output is low:

$$P_D = V_{DD} I_{DD} = 2 \times 20 \mu A = 40 \mu W$$

when the output is high, the transistor is off:

$$P_D = 0W$$

### 14.8

$$V_{OH} = V_{DD} = 2.5V$$

The power drawn from the supply during the low-output state is:

$$P_{DD} = V_{DD} \Rightarrow 125 \mu A = 2.5 \times I_{DD}$$

$$\Rightarrow I_{DD} = 50 \mu A$$

In this stage:

$$I_{DD} = \frac{V_{DD} - V_{OL}}{R_D} \Rightarrow 50 \mu A = \frac{2.5 - 0.1}{R_D}$$

$$\Rightarrow R_D = 48 k\Omega$$

In order to determine  $\frac{W}{L}$ , we note that

$$k_n R_D = 1/V_x \text{ or } k' n \frac{W}{L} R_D = \frac{1}{V_x}$$

Therefore, we need to first calculate  $V_x$ .

$$V_{OL} = \frac{V_{DD}}{1 + \frac{V_{DD} - V_t}{V_x}} \text{ or equivalently:}$$

$$0.1V = \frac{2.5}{1 + \frac{2.5 - 0.5}{V_x}} \Rightarrow V_x = \frac{2}{24} = 0.083V$$

$$\text{Hence, } k' n \frac{W}{L} R_D = \frac{1}{V_x} \text{ gives:}$$

$$100 \times 10^{-6} \times \frac{W}{L} \times 48 \times 10^3 = \frac{1}{0.083} \Rightarrow \frac{W}{L} = 2.5$$

$$V_{IL} = V_i + V_x = 0.5 + 0.083 = 0.583V$$

$$V_M = V_i + \sqrt{2(V_{DD} - V_i)V_x + V_x^2} - V_x$$

$$= 0.5 + \sqrt{2(2.5 - 0.5)0.083 + 0.083^2} - 0.083$$

$$V_M = 1V$$

$$V_{IH} = V_i + 1.63\sqrt{V_{DD}V_x} - V_x$$

$$= 0.5 + 1.63\sqrt{2.5 \times 0.083} - 0.083 = 1.16V$$

$$NM_H = V_{OH} - V_{IH} = 2.5 - 1.16 = 1.34V$$

$$NM_L = V_{IL} - V_{OL} = 0.583 - 0.1 = 0.483V$$

### 14.9

$$V_{i2} = V_{io} + r[\sqrt{V_{OH} + 2\varphi_F} - \sqrt{2\varphi_F}],$$

$$V_{OH} = V_{DD} - V_{i2}$$

$$\text{Iteration 1: } V_{i2} = 0.5 \text{V}$$

$$V_{OH} = 1.8 - 0.5 = 1.3 \text{V}$$

Iteration 2:

$$V_{i2} = 0.5 + 0.3[\sqrt{1.3 + 0.8} - \sqrt{0.8}] = 0.67 \text{V}$$

$$V_{OH} = 1.8 - 0.67 = 1.13 \text{V}$$

Iteration 3:

$$V_{i2} = 0.5 + 0.3[\sqrt{1.13 + 0.8} - \sqrt{0.8}] = 0.65 \text{V}$$

$$V_{OH} = 1.8 - 0.65 = 1.15 \text{V}$$

Iteration 4:

$$V_{i2} = 0.5 + 0.3[\sqrt{1.15 + 0.8} - \sqrt{0.8}] = 0.65 \text{V}$$

$$V_{OH} = 1.8 - 0.65 = 1.15 \text{V}$$

$$\therefore V_{i2} = 0.65 \text{V} \text{ and } V_{OH} = 1.15 \text{V}$$

$\Delta V_{OH} = 1.3 - 1.15 = 0.15 \text{V}$   $V_{OH}$  is reduced by 0.15V due to the body effect on  $Q_2$

### 14.10

$$V_{IH} \approx V_M + \frac{V_M}{K_r} = 0.63 + \frac{0.63}{5} = 0.756 \text{V}$$

The value calculated the long way in Example 13.2 is:  $V_{IH} = 0.75 \text{V}$  and is very close to the above approximation.

### 14.11

Given:  $V_{OL} \approx 0.05 \text{V}$

$$V_{OH} = V_{DD} - V_i = 2.5 - 0.5 = 2 \text{V}$$

$$V_{IL} = V_i = 0.5 \text{V}$$

$$V_{OL} = \frac{(V_{DD} - V_i)^2}{2k_r^2(V_{DD} - 2V_i)} = \frac{(2.5 - 0.5)^2}{2k_r^2(2.5 - 2 \times 0.5)} = \frac{4}{3k_r^2} \approx 0.05 \text{V} \Rightarrow K_r = 5.2$$

$$V_M = \frac{V_{DD} + (K_r - 1)V_i}{(K_r + 1)} = \frac{2.5 + (5.2 - 1) \times 0.5}{5.2 + 1} = 0.74 \text{V}$$

$$V_{IH} \approx V_M + \frac{V_M}{K_r} = 0.74 \text{V} + \frac{0.74 \text{V}}{5.2} = 0.88 \text{V}$$

$$NM_H = V_{OH} - V_{IH} = 2 - 0.88 = 1.12 \text{V}$$

$$NM_L = V_{IL} - V_{OL} = 0.5 - 0.05 = 0.45 \text{V}$$

To obtain  $\frac{W}{L}$ .

$$K_r = \sqrt{\frac{W/L_1}{W/L_2}} \Rightarrow K_r = \sqrt{\frac{1}{\frac{W/L_1}{W/L_2}}} = \left(\frac{W}{L}\right)$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = 5.2 \left(\frac{W}{L}\right)_2 = \frac{1}{5.2} = 0.19$$

$$\begin{aligned} I_{DD} &= i_{D2} = \frac{1}{2} K_{n1} (V_{DD} - V_{OL} - V_i)^2 \\ &= \frac{1}{2} \times 100 \times 10^{-6} \times 0.19 \times (2.5 - 0.05 - 0.5)^2 \\ &= 36.1 \mu\text{A} \\ P_D &= V_{DD} I_{DD} = 2.5 \times 36.1 \mu = 90.2 \mu\text{W} \end{aligned}$$

### 14.12

$$E_{dissipated/cycle} = CV_{DD}^2 = 10 \times 10^{-15} \times 2.5^2$$

$$E_{dissipated/cycle} = 62.5 \text{fJ}$$

$$\begin{aligned} P_{dyn} &= fCV_{DD}^2 = 1 \times 10^9 \times 10 \times 10^{-15} \times 2.5^2 \\ &= 62.5 \mu\text{W} \end{aligned}$$

This is the power consumption for one inverter. For a chip with 1 million inverters, the power consumption is:

$$P_{dyn(chip)} = 62.5 \times 10^{-6} \times 10^6 = 62.5 \text{W}$$

To determine the average current drawn from the supply, we note that

$$P_{dyn} = I_{DDavg} V_{DD} \Rightarrow I_{DD-avg} = \frac{62.5}{2.5} = 25 \text{A}$$

### 14.13

$$P_{dynamic} = fCV_{DD}^2 = 100 \times 10^6 \times 10 \times 10^{-12} \times 25 = 25 \text{mW}$$

$$P = V_{DD} I_{avg} = 5I_{avg} = 25 \text{mW}$$

$$I_{avg} = 5 \text{mA}$$


14.14

(a)  $V_{OL} = 0$

$V_{OH} = 5$

$NM_L = V_{IL} - V_{OL} = 2.5 - 0 = 2.5V$

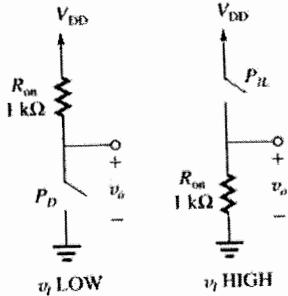$NM_H = V_{OH} - V_{IH} = 5 - 2.5 = 2.5V$



(b)

$$V_o(t) = 0 - (0 - 5)e^{-t/R_{on}C} = 5e^{-t/R_{on}C}$$

For  $t_{PLH} \Rightarrow V_o(t) = 5e^{-t/R_{on}C} = \frac{1}{2}(5) = 2.5$


$$t_{PLH} = -(10^3)(10^{-12})\ln\frac{2.5}{5} = 0.69ns$$

$$\text{For } t_{PHL} V_o(t) = 5e^{-t_H/R_{on}C} = 4.5V$$

$$t_1 = 0.1 ns \quad V_o(t) = 5e^{-t_1/R_{on}C} = 0.5V$$

$$t_2 = 2.3 ns$$

$$t_{THL} = t_2 - t_1 = 2.2 ns$$

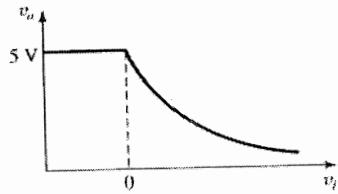

(c)

$$V_o(t) = 5 - (5 - 0)e^{-t/R_{on}C} = 5 - 5e^{-t/R_{on}C}$$

$$V_O = 5 - 5e^{-t_{PLH}/R_{on}C} = 2.5$$


$$t_{PLH} = 0.69 ns$$

For  $t_{PLH}$ ,

$$V_o(t) = 5 - 5e^{-t_1/R_{on}C} = 0.5 \Rightarrow t_1 = 0.10 ns$$

$$V_o(t) = 5 - 5e^{-t_2/R_{on}C} = 4.5 \Rightarrow t_2 = 2.3 ns$$

$$t_{PLH} = 2.3 - 0.1 = 2.2 ns$$

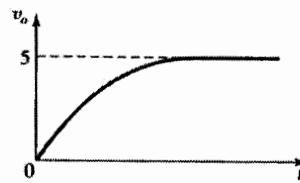

14.15

(a) Generally,  $t_p = (t_{PHL} + t_{PLH})/2$ , but due to current ratio,  $t_{PHL} = 0.5t_{PLH}$ .

Thus  $1.5t_{PHL} = 2(1.2ns)$ , whence

$$t_{PLH} = 2.4/1.5 = 1.6 ns, \text{ and } t_{PHL} = 0.8 ns$$

Check:

$$t_p = (1.6 + 0.8)/2 = 1.2ns$$

(b) Generally,  $t_p = CV/I = kC$

$$\text{Originally, } 1.2n = kC \quad (1)$$

$$\text{Then, } 1.7(1.2)n = k(C + 1p) \quad (2)$$

$$\text{Dividing } \left(\frac{2}{1}\right) : 1.7 = (C + 1p)/C$$

Thus,  $1.7C = C + 1$ ,  $0.7C = 1$ ,

$$C = 1.43pF$$

(the combined load and output capacitances)

(c) With the load inverter removed:

$$0.6(1.2n) = k(1.43 - C_{in}) \quad (3)$$

$$\text{Dividing } \left(\frac{3}{1}\right) : 0.6 = (1.43p - C_{in})/1.43$$

Thus,


$$C_{in} = 1.43(1 - 0.6) = 0.57pF;$$

$$C_{out} = 1.43 - 0.57 = 0.86pF$$
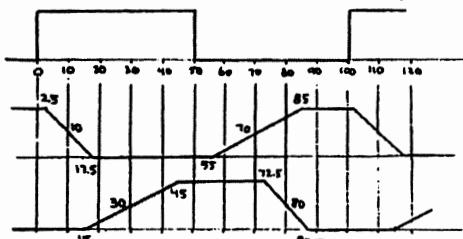
### 14.16

The results depend on whether the gates are inverting or non-inverting.

For inverting gates, the timing diagram is:



Note: For simplicity, 0% to 100% (rather than 10% to 90%) both in the diagram above and calculation to follow:

For inverting gates (as shown, above):

- For a rising input, time to 90% change of output of second gate is  $10 + 20 + \frac{30}{2} = 45\text{ns}$
- For a falling input, time to 90% change of output of 2nd gate is  $20 + 10 + \frac{15}{2} = 37.5\text{ns}$

For non-inverting gates:

- Time to 90% rise is  $10 + 10 + \frac{15}{2} = 27.5\text{ns}$
- Time to 90% fall is  $20 + 20 + \frac{30}{2} = 55\text{ns}$

The propagation delay for these gates is

$$t_p = (t_{PLH} + t_{PHL})/2 = (10 + 20)/2 = 15\text{ns}$$

### 14.17

Note that this question ignores the possibility of dynamic power dissipation: Average propagation delay is  $t_p = (50 + 70)/2 = 60\text{ ns}$

Average power loss at 50% duty cycle


$$= (1 + 0.5)/2 = 0.75\text{ mW}$$

Delay-Power product is

$$DP = 60 \times 10^{-9} \times 0.75 \times 10^{-3} \text{ or}$$

$$DP = 45 \times 10^{-12} \text{ J} = 45\text{ pJ}$$

### 14.18

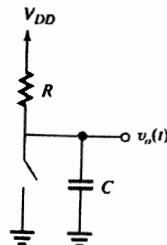

$v_o(t)$  begins at  $V_{OL}$  and rises toward  $V_{OH}$  (in this case  $V_{OH} = V_{DD}$ ) according to

$$v_o(t) = v_s - (v_s - v_{OL})e^{-t/CR}$$

$$= V_{OH} - (V_{OH} - V_{OL})e^{-t/CR}$$

$$= V_{OH} - (V_{OH} - V_{OL})e^{-t/\tau_1}, \quad \tau_1 = CR \quad \text{Q.E.D.}$$


$v_o(t)$  reaches  $\frac{1}{2}(V_{OH} + V_{OL})$  at  $t = t_{PLH}$ ,

$$\frac{1}{2}(V_{OH} + V_{OL}) = V_{OH} - (V_{OH} - V_{OL})e^{-t_{PLH}/\tau_1}$$

$$\Rightarrow t_{PLH} = \tau_1 \ln 2 = 0.69CR \quad \text{Q.E.D.}$$

(b)
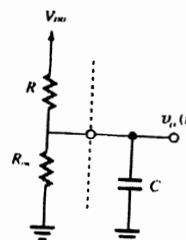
$$v_o(t) = v_s - (v_s - v_{OL})e^{-t/\tau_2}, \\ \tau_2 = C(R//R_{on})$$



### 14 . 19

$$V_M = \frac{r(V_{DD} - |V_{ip}|)}{1+r} \text{ where}$$

$$r = \sqrt{\frac{k_p}{k_n}} = \sqrt{\frac{\mu_p w_p}{\mu_n w_n}}$$

a) For  $w_p = 3.5w_n$  or matched case:

$$\frac{w_p}{w_n} = \frac{\mu_n}{\mu_p} \text{ we have } r = 1 \text{ and:}$$

$$V_M = \frac{1(2.5 - 0.5) + 0.5}{1+1} = \frac{V_{DD}}{2} = 1.25V,$$

$$A = (w_p + w_n)L = 4.5w_nL$$

$$b) \text{ For } w_p = w_n; r = \sqrt{\frac{1}{3.5} \times 1} = 0.53$$

$$V_M = \frac{0.53(2.5 - 0.5) + 0.5}{1+0.53} = 1.02V$$

The shift in  $NM_L$  is approximately equal to the shift in  $V_M$ , that is:

$$\Delta V_M = 1.25 - 1.02 = 0.23V, \text{ hence } NM_L \text{ is reduced by } 0.23V.$$

$$A = (w_p + w_n)L = (w_n + w_n)L = 2w_nL, \text{ therefore the area is reduced by}$$

$$(4.5 - 2)w_nL = 2.5w_nL = 2.5 \times 1.5 \times 0.25 \times 0.25 = 0.23\mu m^2 \text{ or by } \frac{25}{4.5} = 0.56, 56\%$$

$$c) \text{ For } w_p = 2w_n; r = \sqrt{\frac{1 \times 2}{3.5}} = 0.76.$$

$$V_M = \frac{0.76(2.5 - 0.5) + 0.5}{1+0.76} = 1.15V$$

The shift in  $V_M$  is  $1.25 - 1.15 = 0.1V$ , hence, the  $NM_L$  is approximately reduced by  $0.1V$  or comparing to  $NM_L$  in P13.26 above, it is reduced by 9.4%.

$$A = (w_p + w_n)L = (2w_n + w_n)L = 3w_nL, \text{ therefore the area is reduced by } 1.5w_nL \text{ or}$$

$$1.5 \times 1.5 \times 0.25 \times 0.25 = 0.14\mu m^2 \text{ or by}$$

$$\frac{1.5}{4.5} = 0.33 \text{ or } 33\%.$$

### 14 . 20

In the low-output state,  $V_m$  is high and  $V_{om}$  is low and therefore NMos operates in triode region:

$$I_D = \mu_n C_{ox} \left( \frac{W}{L} \right)_n \left[ (V_{GS} - V_{to})V_{DS} - \frac{1}{2}V_{DS}^2 \right]$$

$$= k_n \left( \frac{W}{L} \right)_n \left[ (V_{DD} - 0.2V_{DD}) \times 0.1V_{DD} - \frac{1}{2}(0.1V_{DD})^2 \right]$$

$$I_D = k_n' \left( \frac{W}{L} \right)_n (0.08V_{DD}^2 - 0.005V_{DD}^2)$$

$$= 0.075k_n' \left( \frac{W}{L} \right)_n V_{DD}^2$$

For  $I = 0.5mA$ ,

$$V_{DD} = 2.5V, k_n' = 115\mu A/V^2, \text{ we'll have:}$$

$$0.5 \times 10^{-3} = 0.075 \times 115 \times 10^{-6} \left( \frac{W}{L} \right)_n \times 2.5^2$$

$$\Rightarrow \left( \frac{W}{L} \right)_n = 9.3$$

### 14 . 21

For  $v_t = 1.5V$ , the NMOS operates in triode mode while the PMOS is cut off.

$$r_{DSN} = [k_n(v_t - V_t)]^{-1} = [100 \times 10^{-6}(1.5 - 0.5)]^{-1} = 10k\Omega$$

Thus,

$$v_a = 100 \times 10^{-3} \times 10^4 / (10^4 + 10^5) = 9.09mV$$

For  $v_t = -1.5V$ , the PMOS operates with

$$r_{DSP} = [k_p(|v_t|) - V_t]^{-1} = [(100 \times 10^{-6})(1.5 - 0.5)]^{-1} = 10^5\Omega$$

Thus

$$v_a = 100 \times 10^{-3} \times 10^5 / (10^5 + 10^5) = 50mV$$

### 14 . 22

Since at M, both  $Q_N$  and  $Q_P$  operate in saturation, their currents are given

Substituting  $V_1 = V_o = V_M$  and equating the two currents results in:

$$i_{DN} = i_{DP} \Rightarrow \frac{1}{2}k_n' \left( \frac{W}{L} \right)_n (V_1 - V_{in})^2$$

$$= \frac{1}{2}k_p \left( \frac{W}{L} \right)_p (V_{DD} - V_M - |V_{ip}|)^2$$

$$\frac{K_p}{k_n'} = \frac{(V_M - V_{in})^2}{(V_{DD} - V_M - |V_{ip}|)^2}, \text{ Considering}$$

$$r = \sqrt{\frac{K_p}{k_n'}}, \text{ we have: } r = \frac{V_M - V_{in}}{V_{DD} - |V_{ip}| - V_M}$$

Now, for

$$V_M = 0.6V_{DD} = 0.6 \times 1.8 = 1.08V$$

$$r = \frac{1.08 - 0.5}{1.8 - 0.5 - 1.08} = 2.64$$

$$r = \sqrt{\frac{\mu_p w_p}{\mu_n w_n}} = r \frac{w_p}{w_n} = \frac{(2.64)^2}{V_A} = 27.9$$

### 14.23

The peak current happens when  $V_I = V_M$  and since  $Q_p$  and  $Q_N$  are matched

$$V_M = \frac{V_{DD}}{2} - \frac{1.8}{2} = 0.9V$$

Noting that both transistors are in saturation region, Find the current.

$$\begin{aligned} I &= \frac{1}{2} k_n \left( \frac{W}{L} \right)_n (V_M - V_{in})^2 \\ &= \frac{1}{2} K_n \left( \frac{W}{L} \right)_n \left( \frac{V_{DD}}{2} - V_{in} \right)^2 \end{aligned}$$

For  $k_n = 300 \mu A/V^2$ ,

$$\left( \frac{W}{L} \right)_n = 1.5 V_{DD} = 1.8V \quad V_{in} = 0.5V$$

$$\begin{aligned} I_{peak} &= \frac{1}{2} \times 300 \times 10^{-6} \times 1.5 \times \left( \frac{1.8}{2} - 0.5 \right)^2 \\ &= 36 \mu A \end{aligned}$$

### 14.24

since  $V_{in} = |V_{ip}|$ , then  $\alpha_n = \alpha_p$ , then

$\alpha_n = \alpha_p$ . From above, we have

$$\alpha_n = \alpha_p = 2.32.$$

$$\begin{aligned} t_p &= \frac{1}{2} (t_{PLH} + t_{PHL}) \\ &= \frac{1}{2} \left( \frac{\alpha_n C}{k_n V_{DD}} + \frac{\alpha_p C}{k_p V_{DD}} \right) \end{aligned}$$

Since QN and QP are matched, then  $k_p = k_n$  and

$$t_p = \frac{\alpha_p C}{k_n V_{DD}} = \frac{2.32 \times 20 \times 10^{-15}}{K_n \times 1.2V}$$

$$t_p \leq 20ps \Rightarrow \frac{38.7 \times 10^{-15}}{k_n} \leq 2.0 \times 10^{-12} \Rightarrow k_n \approx 1.9m$$

Now if we substitute in

$$\begin{aligned} k_n &= (k_n) \left( \frac{W}{L} \right)_n = 430 \times 10^{-6} \times \left( \frac{W}{L} \right)_n = 1.9m \\ \Rightarrow \left( \frac{W}{L} \right)_n &= 4.4 \end{aligned}$$

Since  $Q_P$  and  $Q_N$  are matched and  $k_n = k_p$ , then

$$\left( \frac{W}{L} \right)_p = \left( \frac{W}{L} \right)_n \times \frac{k_n}{k_p} 4.4 \times 4 = 17.6$$

### 14.25

Using the equivalent resistance approach, we first find  $R_N$

$$R_N = \frac{12.5}{\left( \frac{W}{L} \right)_n} = \frac{12.5}{1.5} = 8.33k\Omega$$

to determine  $t_{PHL}$

$$\begin{aligned} t_{PHL} &= 0.69 R_N C = 0.69 \times 8.33 \times 10^3 \times 10 \times 10^{-15} \\ &= 57.5 ps. \end{aligned}$$

to determine  $R_p$

$$R_p = \frac{30}{\left( \frac{W}{L} \right)_p} = \frac{30}{3} = 10k\Omega$$

to determine  $t_{PLH}$

$$\begin{aligned} t_{PLH} &= 0.69 R_p C = 0.69 \times 10 \times 10^3 \times 10 \times 10^{-15} \\ &= 69 ps \\ t_p &= \frac{1}{2} (57.5 + 69) = 63.2 ps \end{aligned}$$

Note that while the value obtained for  $t_{PHL}$  is higher than that found using the average currents method, the value for  $t_{PLH}$  is about the same.

### 14.26

$$t_{PHL} = 0.69 R_N C, t_{PLH} = 0.69 R_p C$$

Since  $t_{PHL} = t_{PLH}$ , then  $R_N = R_p = R$

For  $t_p \leq 40ps$ , we have to have:

$$\frac{1}{2} (t_{PHL} + t_{PLH}) \leq 40 ps \text{ or}$$

$$\frac{1}{2} (0.69 \times 2R \times C) \leq 40ps$$

$$\therefore R \leq \frac{40 \times 10^{-12} \times 2}{0.69 \times 2 \times 10^{-15} \times 10} \Rightarrow R \leq 5.8k\Omega$$

To determine the transistor widths in  $0.18 \mu m$  technology,

$$L_n = L_p = .18 \mu m$$

$$R_N = \frac{12.5}{\left( \frac{W}{L} \right)_n} k\Omega \text{ or}$$

$$\frac{12.5}{\left( \frac{W}{L} \right)_n} K \leq 5.8k\Omega \Rightarrow \left( \frac{W}{L} \right)_n \geq 2.2$$

$$\Rightarrow w_n \geq 0.4 \mu m$$

$$R_p = \frac{30}{\left( \frac{W}{L} \right)_p} k\Omega \text{ or}$$

$$\frac{30}{\left( \frac{W}{L} \right)_p} K \leq 5.8k\Omega \Rightarrow \left( \frac{W}{L} \right)_p \geq 5.2$$

$$\Rightarrow w_p \geq .94 \mu m$$

### 14.27

$$\begin{aligned}\alpha_n &= 2 / \left[ \frac{7}{4} - \frac{3V_{in}}{V_{DD}} + \left( \frac{V_{in}}{V_{DD}} \right)^2 \right] \\ &= 2 / \left[ \frac{7}{4} - \frac{3 \times 0.7}{3.3} + \left( \frac{0.7}{3.3} \right)^2 \right] = 1.73 \\ t_{PLH} &= \frac{\alpha_n C}{k_n' \left( \frac{W}{L} \right)_n V_{DD}} = \frac{1.73 \times (2fF \times 0.75 + 1fF)}{180 \times 10^{-6} \times \frac{0.75}{0.5} \times 3.3} \\ &= 4.85 \text{ ps}\end{aligned}$$

Since,  $V_{in} = |V_{tp}|$ , then  $\alpha_n = \alpha_p = 1.73$ . We

also have  $\left( \frac{W}{L} \right)_n = \left( \frac{W}{L} \right)_p$ , hence:

$$t_{PLH} = t_{PHL} \times \frac{k'_p}{k'_n} = 4.85 \times 3 = 14.55 \text{ ps}$$

$$t_p = \frac{1}{2}(t_{PHL} + t_{PLH}) = \frac{1}{2}(4.85 + 14.55) = 9.7 \text{ ps}$$

If both devices are matched, then  $k'_p = k'_n$ .

$t_{PLH} \approx t_{PHL}$  and

$$t_p = \frac{1}{2}(t_{PLH} + t_{PHL}) = t_{PHL} = 4.85 \text{ ps}$$

### 14.28

In order to determine the propagation delay, we first need to calculate the total value for  $C$ , using

$$C = 2C_{gd1} + 2C_{gd2} + C_{db1} + C_{db2} + C_{g3} + C_{g4} + C_w$$

where  $C_{gd1} = 0.4w_n = 0.4 \times 0.75 = 0.3 \text{ fF}$

Since transistors are matched

$$k'_p \left( \frac{W}{L} \right)_p = k'_n \left( \frac{W}{L} \right)_n \Rightarrow w_p = \frac{180}{45} \times 0.75 = 3 \mu\text{m}$$

$$C_{gd2} = 0.4 \times w_p = 0.4 \times 3 = 1.2 \text{ fF}$$

$$C_{db1} = 1.0 \times w_n = 1 \times 0.75 = 0.75 \text{ fF}$$

$$C_{db2} = 1.0 \times w_p = 1.0 \times 3 = 3.0 \text{ fF}$$

$$C_{g3} = (WL)_s C_{ox} + C_{gdov3} + C_{gsor3}$$

$$= (0.75 \times 0.5) \times 3.7 + 0.4 \times 0.75 + 0.4 \times 0.75$$

$$= 1.99 \text{ fF}$$

$$C_{g4} = 3 \times 0.5 \times 3.7 + 2 \times 0.4 \times 3 = 7.95 \text{ fF}$$

$$C = 2 \times 0.3 + 2 \times 1.2 + 0.75 + 3 + 1.99 + 7.95 + 2$$

$$= 18.7 \text{ fF}$$

to deter-

mine  $t_{PHL}$ :

$$\alpha_n = 2 / \left[ \frac{7}{4} - \frac{3 \times 0.7}{3.3} + \left( \frac{0.7}{3.3} \right)^2 \right] = 1.74$$

then,  $t_{PHL}$

$$= \frac{1.74 \times 18.7 \times 10^{-15}}{180 \times 10^{-6} \times \frac{0.75}{0.5} \times 3.3} = 36.5 \text{ ps}$$

Since  $|V_{tp}| = V_{in}$  and transistors are matched,

$$t_{PHL} = t_{PLH} = t_p \Rightarrow t_p = 36.5 \text{ ps}$$

Considering that  $t_{PHL}$  and  $t_{PLH}$  both are proportional to  $C$ , then for an increase of 50% in  $t_p$ ,  $C$  also has to be increased by 50%. Hence,

$$\Delta C = 18.7 \times 0.5 = 9.4 \text{ fF}$$

### 14.29

$$\begin{aligned}\frac{t_{new}}{t_{old}} &= \frac{C_{int} + C_{ext}/s}{C_{int} + C_{ext}} \Rightarrow \frac{30}{60} = \frac{10 + 20/s}{10 + 20} \\ &\Rightarrow 15 = 10 + \frac{20}{s} \Rightarrow s = 4\end{aligned}$$

Note that  $S = \frac{R_{eq}}{R_{eq}}$  and hence  $R_{eq}$  has to be

reduced by a factor of 4 or equivalently  $\left( \frac{W}{L} \right)_n$

and  $\left( \frac{W}{L} \right)_p$  have to be increased by a factor of 4.

### 14.30

Dynamic power is  $P_D = fCV^2_{DD}$ ; Static Power is  $P_s$ .

Now,  $9.0 = P_s + 120 \times 10^6 C^2 5$  and

$$4.7 = P_s + 50 \times 10^6 C^2 5$$

$$\text{Subtracting, } 4.3 = 70 \times 10^6 C(25)$$

Whence

$$C = 4.3 / (25 \times 70 \times 10^6) = 2457 \text{ pF}$$

$$\text{and } P_s = 9.0 - 120 \times 10^6 (25) 2457 \times 10^{-12}$$

$$= 9.0 - 7.37 = 1.63 \text{ W}$$

For 70% of the gates active, total gates

$$= 0.7 \times 10^6$$

Capacitance per gate is

$$2457 \times 10^{-12} / (0.7 \times 10^6) = 3.5 \text{ fF}$$

### 14.31

$$C = 2C_{sd1} + C_{sd2} + C_{db1} + C_{db2} + C_{s3} + C_{s4} + C_n$$

$$W = W_n = W_p = 0.75 \mu\text{m}$$

$$C_{sd1} = \frac{4f}{\mu\text{m}} \cdot W_n = \frac{4f}{\mu\text{m}} \times 0.75 \mu\text{m} = 0.3f\text{F}$$

$$C_{sd2} = \frac{0.4f}{\mu\text{m}} \cdot W_p = \frac{0.4f}{\mu\text{m}} \times 0.75 \mu\text{m} = 0.3f\text{F}$$

$$C_{db1} = C_{db2} = \frac{1f}{\mu\text{m}} \cdot W = \frac{1f}{\mu\text{m}} \times 0.75 \mu\text{m}$$

$$= 0.75f\text{F}$$

$$C_{s3} = C_{s4} = (WL)C_{ov} + C_{sdov} + C_{sinv}$$

$$= (0.75 \mu\text{m} \times 0.5 \mu\text{m}) \frac{3.7f}{\mu\text{m}^2} + 2 \times \frac{0.4f}{\mu\text{m}} \times 0.75 \mu\text{m}$$

$$C_{s3} = C_{s4} = 1.99f\text{F}$$

$$C = 2 \times 0.3f + 2 \times 0.3f + 2 \times 0.75f$$

$$+ 2 \times 1.99f + 2f = 8.7 f\text{F}$$

$$\alpha_n = 2 / \left[ \frac{7}{4} - \frac{3 \times 0.7}{3.3} + \left( \frac{0.7}{3.3} \right)^2 \right] = 1.74$$

$$t_{PHL} = \frac{1.74 \times 8.7 \times 10^{-15}}{180 \times 10^{-6} \times \frac{0.75}{0.5} \times 3.3} = 17 \text{ ps}$$

$$\alpha_p = 2 \left[ \frac{7}{4} - \frac{3 \times 0.7}{3.3} + \left( \frac{0.7}{3.3} \right)^2 \right] = 1.74$$


$$t_{PLH} = \frac{1.74 \times 8.7 \times 10^{-15}}{45 \times 10^{-6} \times \frac{0.75}{0.5} \times 3.3} = 68 \text{ ps}$$

$$t_p = \frac{1}{2}(t_{PHL} + t_{PLH}) = \frac{1}{2}(17p + 68p) = 42.5 \text{ ps}$$

$$P_D = fCV_{DD}^2 = 250 \times 10^6 \times 8.7 \times 10^{-15} \times (3.3)^2$$

$$= 23.7 \mu\text{W}$$

### 14.32

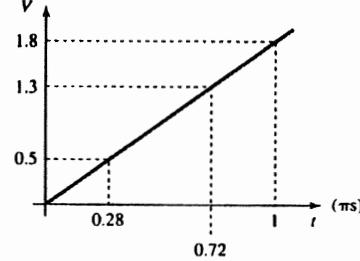

$$I_{peak} = \frac{1}{2} \mu_n C_{ov} \left( \frac{W}{L} \right)_n \left( \frac{V_{DD}}{2} - V_{in} \right)^2$$

$$I_{peak} = \frac{1}{2} \times 450 \frac{\mu\text{A}}{\text{V}^2} \left( \frac{1.8}{2} - 0.5 \right)^2 = 36 \mu\text{A}$$

The time when the input reaches  $V_i$  is:

$$\frac{0.5}{1.8} \times 1 \text{ ns} = 0.28 \text{ ns}$$

The time when the input reaches  $V_{DD} - V_i$  is

$$\frac{1.8 - 0.5}{1.8} \times 1 \text{ ns} = 0.72 \text{ ns}$$


So the base of the triangle is

$$\Delta t = 0.72 - 0.28 = 0.44 \text{ ns wide}$$

$$E = \frac{1}{2} I_{peak} \times V_{DD} \times \Delta t = \frac{1}{2} \times 36 \mu\text{A} \times 1.8 \times 0.44 \text{ ns}$$

$$= 14.3 \text{ fJ}$$
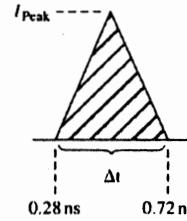
$$P = f \times E = 100 \times 10^6 \times 14.3 \times 10^{-15} = 1.43 \mu\text{W}$$




14 . 33


$$Y = AB + \bar{A}B \rightarrow \bar{Y} = \overline{AB + \bar{A}B} = \overline{AB} \cdot \overline{\bar{A}B}$$

$$\text{or } Y = (\bar{A} + B)(A + \bar{B}) = AB + \bar{A}\bar{B}$$

PUN for  $Y = AB + \bar{A}\bar{B}$ :

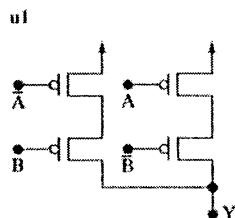


PDN dual to u1

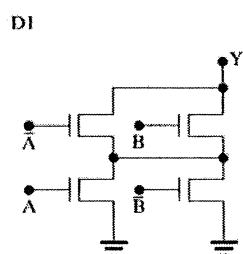


\*Note, however that D1 can be redrawn as shown, then its columns (series links) converted to rows (parallel links of a PUN):

PDN for  $Y = AB + \bar{A}B$ :

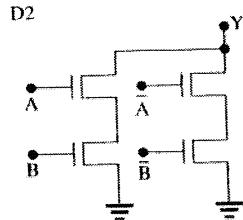


PUN dual to D2:

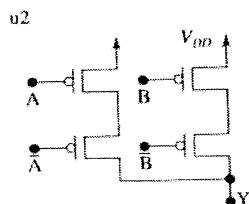

The two circuits required are  $U_1$  with D1 and  $U_2$  with D2.

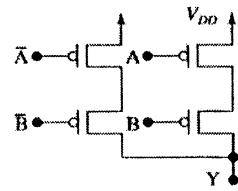14 . 34

$Y = AB + \bar{A}\bar{B}$ . Directly, the PUN is as follows: u1




Now,

$$\bar{Y} = \overline{AB + \bar{A}\bar{B}} = \overline{AB} \cdot \overline{\bar{A}\bar{B}} = (\bar{A} + \bar{B}) / (A + B)$$


$$\text{or } \bar{Y} = \bar{A}\bar{B} + A\bar{B}$$

Directly, the PDN is:

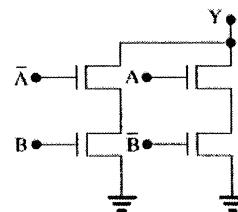


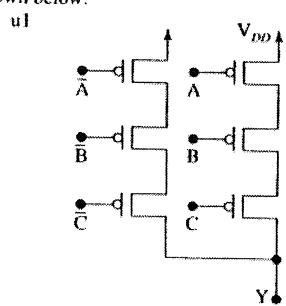14 . 35

$Y = ABC + \bar{A}\bar{B}\bar{C}$ . Directly, the PUN is as shown below:



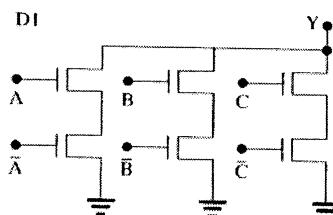The corresponding dual PDN is shown above below.




### 14 . 36

a) Even-parity circuit:

$$\bar{Y} = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + A\bar{B}\bar{C},$$


b) PDN directly is:

D1

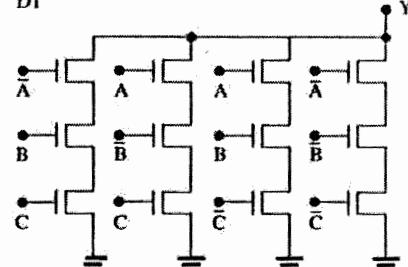


It uses 12 transistors.

(c) PDN reduced to 10 transistors:

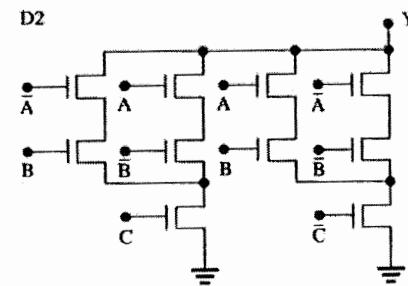

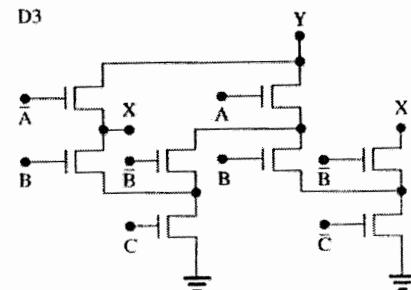PDN reduced to 8 transistors: (X and X are joined)




[Think circuit is not "planar", but has one "cross-over" (x-x); it has no convenient dual]

PUN as the dual of D2:

[Think of the structure of the dual of D1 when constructing this]

The complete circuit, using  $u_2$  and D2 has 20 transistors.

u2

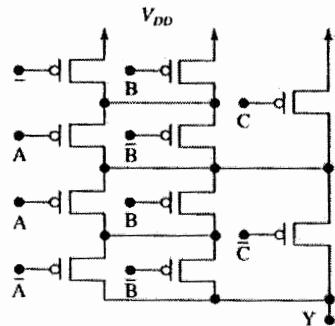

### 14 . 37

$$\text{Sum, } S = A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC$$


$$\text{Carry } C_o = AB\bar{C} + A\bar{B}\bar{C} + \bar{A}BC + ABC$$

$$= AB + AC + BC = A(B + C) + BC$$

Create the PUN, directly, simplifying that for S as in P13.50 above as

$$S = \bar{A}(B\bar{C} + \bar{B}C) + A(\bar{B}\bar{C} + BC)$$

This figure is for 14.37

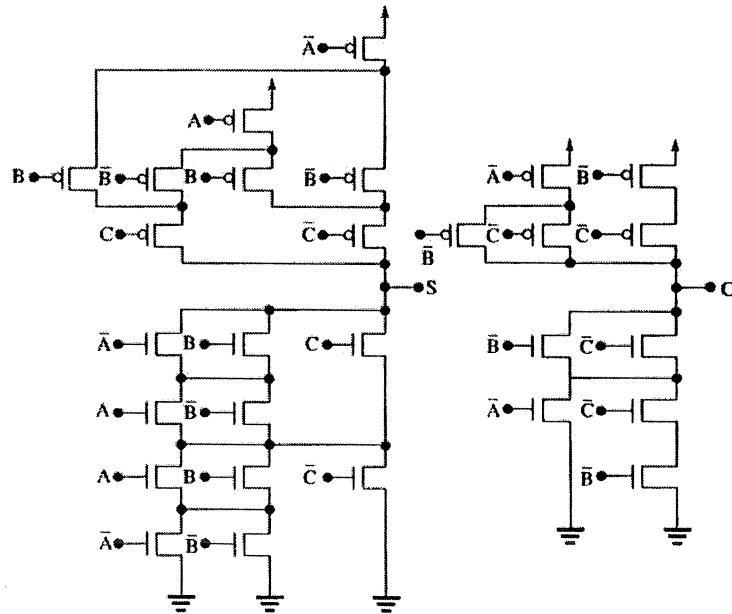

#### 14.38

For matched-inverter equivalence of the circuit

$$p_A = p_B = p_C = p_D = 2p$$

and

$$n_A = n_B = 2n; n_C = n_D = 2(2n) = 4n.$$

14.39 blank

#### 14.40

Ignore the capacitances of the transistors themselves; For the matched NAND.

$t_{PLH} = t_{PHL} = t_p$ . For the "uncompensated NAND,  $t_{PLH} = t_p$ ,  $t_{PHL} = t_p/4$ . Thus,  $t_{PLH}$  are the same, but  $t_{PHL}$  is 4 times greater with no matching.

#### 14.41

For design a), there are  $2(6) + 2 = 14$  transistors;

All 7 NMOS use  $(W/L)_n = n$

1 PMOS uses  $(W/L)_p = p$

6 PMOS use  $(W/L)_p = 6p$

$$\text{Total Area} = 7(1.2)0.8 + 1(3.6)0.8 + 6(6)(3.6)0.8 = 113.3 \mu\text{m}^2$$

For design b), there are  $2(3)2 + 1(2)2 = 16$  transistors;

6 NMOS use  $(W/L)_n = n$

6 PMOS use  $(W/L)_p = 3p$

2 PMOS use  $(W/L)_p = p$

2 NMOS use  $(W/L)_n = 2n$

$$\text{Total equivalent devices is } 6n + 18p + 2p + 2n = 10n + 20p$$

$$\text{Total equivalent area is } [10 + 3(20)]n = 70n, \text{ and}$$

$$\text{Total Area} = 70(1.2)0.8 = 67.2 \mu\text{m}^2, \text{ or } 59\% \text{ of a)}$$

### 14.42

Corresponding to a matched inverter characterized by n and p where  $k_p = k_n = k$ , the two-input NOR uses transistors n and 2p where

$$k_p = 2k_n$$

a) For A grounded,  $V_{thB}$  occurs near  $V_{DD}/2$ , with  $Q_{PB}$  and  $Q_{NB}$  in saturation and  $Q_{PA}$  in trade. Let  $V_{th} = v$  and the voltage across  $Q_{PA}$  be x.

$$\text{Thus } i_D = k_p[(5 - 1)x - x^2/2]$$

$$\text{and } i_D = \frac{1}{2}k_p(5 - x - v - 1)^2$$

$$\text{and } i_D = \frac{1}{2}k_n(v - 1)^2$$

$$\text{For } k_p = 2k_n$$

$$i_p = 2k_n(4x - x^2/2) = k_n(8x - x^2) \quad (1)$$

$$\text{and } i_D = k_n(4x - x - v)V^2 \quad (2)$$

$$\text{and } i_D = \frac{1}{2}k_n(v - 1)^2 \quad (3)$$

$$\text{From 2) 3): } \pm(v - 1)(0.707) = 4 - x - v$$

Thus,

$$1.707v = 4.707 - x \quad \text{or}$$

$$x = 4.707v - 1.707v$$

$$0.293v = 3.293 - x$$

$$x = 3.293 - 0.293v$$

Now x = 0, in which case

$$v = 4.707 / 1.707 = 2.38 \text{ or}$$

$$v = 3.293 / 0.293 = 11.2 \text{ (clearly too large)}$$

Thus

$$x = 4.707 - 1.707v \quad (4)$$

$$\text{Now, from 1), 3): } (v - 1)^2 = 2(8x - x^2)$$

with 4)

$$v^2 - 2v + 1 = 16(4.707 - 1.707v) - 2$$

$$(4.707 - 1.707v)^2 \text{ or}$$

$$v^2 - 2v + 1 = 75.32 - 27.32v - 44.31 + 32.13v$$

$$-5.83v^2$$

or

$$6.83v^2 + v(-2 + 27.32 - 32.13)$$

$$+ (1 - 75.32 + 44.31) = 0$$

or

$$6.833v^2 - 6.81v - 30.01 = 0$$

whence

$$v = (-6.81 \pm (6.81^2 - 4(6.83)30.01)^{\frac{1}{2}}) / 2(6.83)$$

$$= (6.81 \pm 29.43) / 13.66 = 2.65V$$

Check: [ $>2.5V$  probably OK since one PMOS is full on]

$$\text{Thus } V_{th} = 2.65V$$

b) For A and B joined, the PMOS can be approximated as a single device with twice the length for which the width is twice that in a matched inverter. Thus, for the equivalent PMOS device  $(W/L)_{peq} = P$  and  $k_p = k$ . For each of the two NMOS  $(W/L)_n = n$  and  $k_n = k$ .

Thus at  $v_{th} = v$  with all devices in saturation:

$$i_D = 2k / 2(v - 1)^2 = (k/2)(5 - v - 1)^2$$

$$2(v - 1)^2 = (4 - v)^2, \text{ and}$$

$$\pm\sqrt{2}(v - 1) = (4 - v)$$

$$\text{Thus, } 1.414v - 1.414 = 4 - v,$$

$$2.414v = 5.414,$$

$$\text{whence } V_{th} = v = 2.24V$$

See this is reduced from the single-input value (of 2.65V)!

Note that this fact can be used to control the relative threshold of multiple gates connected to a single fanout node in order to guarantee operation sequence for slowly changing signals.

### 14.43

a)  $t_p \alpha \frac{\alpha C}{k' V_{DD}}$ , and  $k'$  is scaled by S, and C and

$V_{DD}$  are scaled by  $\frac{1}{S}$  thus  $t_p$  is scaled by

$$\frac{\frac{1}{S}}{S \times \frac{1}{S}} = \frac{1}{S}$$

$$S = 4 \Rightarrow t_p \text{ is scaled by } \frac{1}{4} \text{ (} t_p \text{ decreases)}$$

The maximum operating speed is  $\frac{1}{2t_p}$  and therefore is scaled by 4.

$$P_{dyn} = f_{max} CV^2_{DD}$$
 and thus is scaled by

$$S \times \frac{1}{S} \times \frac{1}{S^2} = \frac{1}{S^2} = \frac{1}{16} \text{ (P}_{\text{dyn}} \text{ decreases) power}$$

$$\text{density} = \frac{P_{\text{dyn}}}{\text{area}} \text{ and thus is scaled by } \frac{\frac{1}{S^2}}{\frac{1}{S^2}} = 1$$

i.e., remains unchanged.

PDP is scaled by  $\frac{1}{S^3}$  (power is scaled by  $\frac{1}{S^2}$  and

delay by  $\frac{1}{S}$  and thus it is scaled by  $\frac{1}{64}$  (PDP decreases)

b) If  $V_{DD}$  and  $V_{in}$  only scaled by  $\frac{1}{2}$  while  $S=4$  we have:

$$t_p = \frac{\alpha C}{k' V_{DD}} \text{ and } \alpha = \frac{2}{\frac{7}{4} - \frac{3V_{in}}{V_{DD}} + \left(\frac{V_{in}}{V_{DD}}\right)^2} \text{ so}$$

$\alpha$  remains unchanged and  $t_p$  is scaled by

$$\frac{\frac{1}{S}}{S \times \frac{1}{2}} = \frac{\frac{1}{4}}{4 \times \frac{1}{2}} = \frac{1}{8}$$

The maximum operating speed is  $\frac{1}{2t_p}$  and therefore is scaled by 8.

$P_{\text{dyn}} = f_{\text{max}} CV_{DD}^2$  and thus is scaled by

$$8 \times \frac{1}{5} \times \frac{1}{2^2} = 8 \times \frac{1}{4} \times \frac{1}{2} = 1$$

Power density =  $\frac{P_{\text{dyn}}}{\text{area}}$  is thus scaled by

$$\frac{\frac{1}{S}}{\frac{1}{S^2}} = \frac{1}{16}$$

PDP is scaled by  $1 \times \frac{1}{8} = \frac{1}{8}$

#### 14.44

$$V_{DSSat} = \left(\frac{L}{\mu_n}\right)v_{sat} \Rightarrow \mu_n = \frac{L}{V_{DSSat}} v_{sat}$$

$$v_{sat} \geq 10^7 \text{ cm/s} = 10^5 \text{ m/s}, L = 0.18 \text{ } \mu\text{m}$$

$$\text{and } V_{DSSat} = 0.6 \text{ V}$$

$$\begin{aligned} \mu_n &= \frac{0.18 \times 10^{-6} \text{ m}}{0.6 \text{ V}} \times 10^5 \text{ m/s} = 0.03 \frac{\text{m}^2}{\text{V} \cdot \text{s}} \\ &= 300 \frac{\text{cm}^2}{\text{V} \cdot \text{s}} \end{aligned}$$

For PMOS we have  $V_{DSSat} = 1 \text{ V}$ , thus

$$\mu_p = \frac{0.18 \times 10^{-6} \text{ m}}{1 \text{ V}} \times 10^5 \text{ m/s} = 0.018 \frac{\text{m}^2}{\text{V} \cdot \text{s}}$$

$$= 180 \frac{\text{cm}^2}{\text{V} \cdot \text{s}}$$

From equation (13.92) of the Text, we have:

$$E_{cr} = \frac{V_{DSSat}}{L}$$

$$\begin{aligned} \text{For NMOS: } E_{cr} &= \frac{0.6 \text{ V}}{0.18 \mu\text{m}} = 3.33 \times 10^6 \frac{\text{V}}{\text{m}}; \\ &= 3.33 \times 10^{-4} \frac{\text{V}}{\text{cm}} \end{aligned}$$

$$\begin{aligned} \text{For PMOS: } E_{cr} &= \frac{1 \text{ V}}{0.18 \mu\text{m}} = 5.56 \times 10^6 \frac{\text{V}}{\text{m}} \\ &= 5.56 \times 10^3 \frac{\text{V}}{\text{cm}} \end{aligned}$$

#### 14.45

assuming  $g_{sat} = 10^7 \text{ cm/s}$ ,

then:

$$V_{DSSat_n} = \frac{L}{\mu_n} \times g_{sat} = \frac{0.13 \times 10^{-6}}{325 \times 10^{-4}} \times 10^7 \times 10^{-2}$$

$$= 0.4 \text{ V}$$

$$V_{DSSat_p} = \frac{L}{\mu_p} \times g_{sat} = \frac{0.13 \times 10^{-6}}{200 \times 10^{-4}} \times 10^7 \times 10^{-2}$$

$$= 0.65 \text{ V}$$

#### 14.46

$$t_{PHL} = \frac{CV_{DD}}{2I_{av}}$$

Since based on the assumption in this problem,  $Q_N$  turns on immediately ( $V_t$  rises instantaneously to  $V_{DD}$ ) and it operates in the velocity-saturation

$$\text{region then } I_{av} = I_{Dsat} \text{ thus, } t_{PHL} = \frac{CV_{DD}}{2I_{Dsat}}$$

b) From equations (13.68) and (13.70) of the Text we have:

$$t_{PHL} = 0.69R_N C \text{ and}$$

$$R_N = \frac{12.5 \text{ k}\Omega}{(W/L)_n} \Rightarrow t_{PHL} = 0.69C \frac{12.5 \times 10^3}{(W/L)_n}$$

c) If the formula in (a) and (b) yield the same result we have:

$$\frac{CV_{DD}}{2I_{Dsat}} = 0.69C \frac{12.5 \times 10^3}{(W/L)_n} \text{ and from equation}$$

(13.94) of the Text we have:

$$I_{Dsat} = \mu_n C_{ox} \left(\frac{W}{L}\right)_n V_{DSSat} \left(V_{GS} - V_t - \frac{1}{2}V_{DSSat}\right)$$

where in this case  $V_{GS} = V_{DD}$  thus:

$$\begin{aligned} & \frac{V_{DD}}{2 \times 0.69 \times 12.5 \times 10^3} \\ &= \frac{\mu_n C_{ox} \left( \frac{W}{L} \right)_n V_{DSsat} \left( V_{DD} - V_t - \frac{1}{2} V_{DSsat} \right)}{\left( \frac{W}{L} \right)_n} \\ &\Rightarrow \frac{1.2}{17250} = 325 \times 10^{-6} \left( 1.2 - 0.4 - \frac{V_{DSsat}}{2} \right) \\ &\frac{1.2}{17250} = 325 \times 10^{-6} V_{DSsat} \left( 1.2 - 0.4 - \frac{V_{DSsat}}{2} \right) \\ &1.2 = 5.61 V_{DSsat} \left( 0.8 - \frac{V_{DSsat}}{2} \right) \\ &\Rightarrow 2.805 V_{DSsat}^2 - 4.488 V_{DSsat} + 1.2 = 0 \end{aligned}$$

$$V_{DSsat} = 1.261 \text{ V or } V_{DSsat} = 0.339 \text{ V}$$

The answer  $V_{DSsat} = 1.261 \text{ V}$  is not acceptable

as it is above  $V_{DD}$ . Thus,  $V_{DSsat} = 0.339 \text{ V}$

#### 14.48

- a)  $R = 27 \text{ m}\Omega/\square \times \frac{10 \text{ mm}}{0.5 \mu\text{m}} = 540 \Omega$
- b)  $C = 0.1 \text{ fF}/\mu\text{m} \times 10 \text{ mm}$   
 $= 0.1 \text{ fF}/\mu\text{m} \times 10000 \mu\text{m} = 1000 \text{ fF} = 1 \text{ pF}$
- c)  $t_{delay} = 0.69RC = 372.6 \text{ ps}$

#### 14.47

$$I_{DSsatn} = \mu_n C_{ox} \left( \frac{W}{L} \right)_n V_{DSsatn} \left( V_{GS} - V_{tn} - \frac{1}{2} V_{DSsatn} \right)$$

and

$$I_{DSsatp} = \mu_p C_{ox} \left( \frac{W}{L} \right)_p |V_{DSsatp}| |V_{GS}| - |V_{tp}| - \left( -\frac{1}{2} |V_{DSsatp}| \right)$$

Since  $|V_{GS}| = V_{DD}$  (i.e., for NMOS

$V_{GS} = V_{DD}$  and for PMOS  $|V_{GS}| = V_{DD}$  and

$I_{DSsatn} = I_{DSsatp}$  we have:

$$\begin{aligned} & \mu_n C_{ox} \left( \frac{W}{L} \right)_n V_{DSsatn} \left( V_{DD} - V_{tn} - \frac{1}{2} V_{DSsatn} \right) \\ &= \mu_p C_{ox} \left( \frac{W}{L} \right)_p |V_{DSsatp}| \left( V_{DD} - |V_{tp}| - \frac{1}{2} |V_{DSsatp}| \right) \end{aligned}$$

$L_n = L_p \Rightarrow$  Thus,

$$\frac{w_p}{w_n} = \frac{\mu_n V_{DSsatn}}{\mu_p |V_{DSsatp}|} \frac{V_{DD} - V_{tn} - \frac{1}{2} V_{DSsatn}}{V_{DD} - |V_{tp}| \left| \frac{1}{2} V_{DSsatp} \right|}$$

$$\text{b) } \frac{w_p}{w_n} = \frac{\mu_n V_{DSsatn}}{\mu_p |V_{DSsatp}|} \frac{V_{DD} - V_{tn} - \frac{1}{2} V_{DSsatn}}{V_{DD} - |V_{tp}| \frac{1}{2} V_{DSsatp}}$$

$$= 4 \times \frac{0.34}{0.6} \frac{1.2 - 0.4 - \frac{0.34}{2}}{1.2 - 0.4 - \frac{0.6}{2}} = 2.86$$

### 15.1

$$\text{Here } V_{DD}/4 = 5/4 = 1.25V$$

Now, for  $V_D$  rising, the NMOS is cutoff, and

the PMOS is in triode mode with:

$$i_{Dp} = k_p [(V_{SS} - V_t) V_{SD} - V_{SD}^2/2], \text{ and here}$$

$$i_D = k_p [(5 - 0.8)(5 - 1.25) - (5 - 1.25)^2/2]$$

$$= k_p (18.75 - 7.03) = 8.72 k_p$$

Now, for  $V_D$  falling, the net current extracted

$$\text{from the load is } i_{Dn} - i_{Dp} \text{ which should be } i_{Dp}$$

$$\text{Thus } i_{Dn} = 2i_{Dp} = 2(8.72)k_p, \text{ for triode}$$

$$\text{operation where } i_{Dn} = k_n [(5 - 0.8)1.25 - 1.25^2/2]$$

$$\text{Overall, } i_{Dn} = 2(8.72)k_p = k_n (5.25 - 0.78) = 4.47 k_n$$

$$\text{Thus } k_n = (4.47)/(2(8.72)) k_p = 0.255 k_p$$

Check using Eq 10.39, where  $r = k_n/k_p = 3.91$ :

$$V_{OL} = (V_{DD} - V_t) [1 - (1 - r)r]^{1/2}$$

$$= (5 - 0.8) [1 - (1 - 1/3.91)]^{1/2} = 0.577V$$

$$\text{From Eq 13.35, } V_{IL} = V_t + (V_{DD} - V_t)/(r(r+1))^{1/2}$$

$$= 0.8 + 4.2/(3.91 \times 4.91)^{1/2} = 1.76V$$

$$\text{From Eq 13.38, } V_{ZH} = V_t + (2/\sqrt{3r})(V_{DD} - V_t)$$

$$= 0.8 + (2/\sqrt{3(3.91)})4.2 = 3.25V$$

$$\text{From Eq 13.36, } V_M = V_t + (V_{DD} - V_t)/(r+1)^{1/2}$$

$$= 0.8 + 4.2/(4.91)^{1/2} = 2.70V$$

$$\text{Now, } NM_H = V_{OH} - V_{ZH} = 5.00 - 3.25 = 1.75V$$

$$\text{and } NM_L = V_{IL} - V_{OL} = 1.76 - 0.58 = 1.18V$$

### 15.2

$$\alpha_p = 2/\left[\frac{7}{4} - 3\left(\frac{0.4}{1.2}\right) + \left(\frac{0.4}{1.2}\right)^2\right] = 2.3$$

$$t_{PLH} = \frac{\alpha_p C}{k_p V_{DD}} = \frac{2.3(10f)}{\left(\frac{430 \mu}{4}\right) \cdot \left(\frac{W}{L}\right)_p \cdot 1.2}$$

$$r = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}{\mu_p C_{ox} \left(\frac{W}{L}\right)_p} = 4$$

$$\frac{430 \mu(1)}{\frac{430 \mu}{4} \left(\frac{W}{L}\right)_p} = 4 \Rightarrow \left(\frac{W}{L}\right)_p = \frac{4}{4} = 1$$

$$t_{PLH} = 0.18 \text{ nsec or } 180 \text{ psec}$$

using eq. (14.17) and (14.18)

$$\alpha_n = 2/\left[1 + \frac{3}{4}\left(1 - \frac{1}{r}\right) - \left(3 - \frac{1}{r}\right)\left(\frac{V_+}{V_{DD}}\right)^2\right] = 2.6$$

$$t_{PHL} \cong \frac{\alpha_n C}{k_n V_{DD}} = \frac{2.6(10f)}{(430 \mu)(1)(1.2)} = 50 \text{ psec}$$

$$t_p = \frac{1}{2}(t_{PLH} + t_{PHL}) = \frac{1}{2}(180p + 50p) = 115 \text{ psec}$$

### 15.3

$$NM_L = V_t - (V_{DD} - V_t) [1 - (1 - \frac{1}{r})^{\frac{1}{2}} - (r(r+1))^{\frac{1}{2}}]$$

$$\text{Now, } \Delta NM_L / \Delta r = -(V_{DD} - V_t) [-\frac{1}{2}(1 - \frac{1}{r})^{\frac{1}{2}}(-\frac{1}{r}) - (-\frac{1}{2}(r(r+1))^{\frac{1}{2}})]$$

Maximum occurs where:

$$-\frac{1}{2}(1 - \frac{1}{r})^{\frac{1}{2}}(-\frac{1}{r}) = -\frac{1}{2}(r(r+1))^{\frac{1}{2}}(2r+1)$$

$$\text{Square both sides: } (1 - \frac{1}{r})^{\frac{1}{2}} \frac{1}{r} = r^{-2}(r(r+1))^{\frac{1}{2}}(2r+1)^2$$

$$\text{or } \frac{1 - \frac{1}{r}}{r} = \frac{1}{(r+1)^2} (2r+1)^2 = \frac{r}{r+1}$$

### 15.4 blank

$$NM_H = (V_{DD} - V_t)(1 - z/\sqrt{3r})$$

This is zero, when  $1 - z/\sqrt{3r} = 0$ ,  
 $\text{or } \sqrt{3r} = z, \text{ or } 3r = z^2, \text{ or } r = \frac{z^2}{3}$

$$\text{For } r=1, NM_H = 4.2(1 - z/\sqrt{3}) = -0.65V$$

$$\text{For } r=2, NM_H = 4.2(1 - z/\sqrt{6}) = 0.77V$$

$$\text{For } r=4, NM_H = 4.2(1 - z/\sqrt{12}) = 1.78V$$

$$\text{For } r=8, NM_H = 4.2(1 - z/\sqrt{24}) = 2.48V$$

$$\text{For } r=16, NM_H = 4.2(1 - z/\sqrt{48}) = 2.99V$$

But, what about  $NM_L$ ? (For  $r=16$ , it is 0.92V)

### 15.6

Noise margins are equal

when

$$V_t - (V_{DD} - V_t) \left[ 1 - \left(1 - \frac{1}{r}\right)^{\frac{1}{2}} \right] / \left( r(V_{DD})^{\frac{1}{2}} \right) = (V_{DD} - V_t) \left[ 1 - 2/(3r)^{\frac{1}{2}} \right]$$

$$\text{or } V_t / (V_{DD} - V_t) = 2 - 2/(3r)^{\frac{1}{2}} = (1 - V_t)^{\frac{1}{2}} - 1 / (r(V_{DD}))^{\frac{1}{2}} - 1$$

$$\text{Here } V_t / (V_{DD} - V_t) = 0.8 / (5.0 - 0.8) = 0.1904$$

Try various values of  $r$  to solve (1) :

$$\text{For } r=2, f(r) = 2 - 2/6^{\frac{1}{2}} - (1 - \frac{1}{2})^{\frac{1}{2}} - 1 / (2(2))^{\frac{1}{2}} \\ = 2 - 0.86 - 0.707 - 0.408 = 0.069$$

$$\text{For } r=3, f(r) = 2 - 2/9^{\frac{1}{2}} - (1 - \frac{1}{3})^{\frac{1}{2}} - 1 / (3(3))^{\frac{1}{2}} \\ = 2 - 0.667 - 0.816 - 0.289 = 0.228$$

$$\text{Try } r=2.8, f(r) = 2 - 2/(3(2.8))^{\frac{1}{2}} - (1 - \frac{1}{2.8})^{\frac{1}{2}} - 1 / (2(2.8))^{\frac{1}{2}} \\ = 2 - 0.690 - 0.802 - 0.307 = 0.209$$

$$\text{Try } r=2.7, f(r) = 2 - 2/(3(2.7))^{\frac{1}{2}} - (1 - \frac{1}{2.7})^{\frac{1}{2}} - 1 / (2(2.7))^{\frac{1}{2}} \\ = 2 - 0.703 - 0.793 - 0.316 = 0.189$$

Conclude  $r \approx 2.72$ , for which the margins are:

$$NM_H = NM_L = (V_{DD} - V_t)(1 - 2/(3r)^{\frac{1}{2}}) \\ = 4.2(1 - 2/(3(2.72))^{\frac{1}{2}}) = 1.26V$$


### 15.7 blank

### 15.8

$$Y = \overline{A + B(C + D)}$$

$$\text{whence } \bar{Y} = A + B(C + D)$$

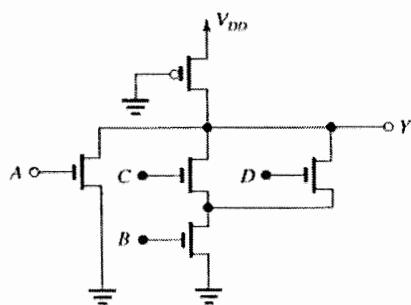Thus the PDN can be formed directly as shown :



$$\text{Now, } t_{PLH}/t_{PHL} = (k_n/k_p)(1 - 0.46/r)$$

$$= r(1 - 0.46/r) = 2.72 - 0.46 = 2.26$$

Now,

$$t_{PLH} = 1.7(1 \times 10^{-12}) / (25 \times 10^{-6}(1.33/0.8)(5)) \\ = 8.24\text{ns}$$

$$\text{and } t_{PHL} = 8.24 / 2.26 = 3.65\text{ns}$$

$$\text{and } t_p = (8.24 + 3.65) / 2 = 5.95\text{ns}$$

Now, dynamic power is approximately  $fC V^2 DD$   
since the output swing is not quite  $V_{DD}$ .

For equal static and dynamic power

$$f \times 1 \times 10^{-12} \times 5^2 = 1.82 \times 10^{-3}$$

whence

$$f = 1.82 \times 10^{-3} / (25 \times 10^{-12}) = 72.8\text{MHz}$$

for which the period is

$$1 / (72.8 \times 10^6) = 13.7\text{ ns}$$

Now, for transition times in the same proportion  
as propagation delays

$$t_{TLH}/t_{TTHL} = 8.24 / 3.65 = 2.26$$

Now, for full output swing, there must be time for  
2 full transitions in each cycle :

Thus

$$t_{THL} = 13.7 / (1 + 2.26) \approx 4.19\text{ns and}$$

$$t_{TLH} = 4.19(2.26) = 9.47\text{ns}$$

Since these values are of the same order as the  
propagation delays. Full swing operation is likely  
not possible at 72.8MHz.


### 15.9

For an Exclusive OR,  $Y = A\bar{B} + \bar{A}B$ , and

$$\bar{Y} = \overline{A\bar{B} + \bar{A}B} = \overline{A\bar{B}} \cdot \overline{\bar{A}B} = (\bar{A} + B)(A + \bar{B})$$

$$\text{or } \bar{Y} = \bar{A}\bar{B} + AB$$

The PDN results directly :

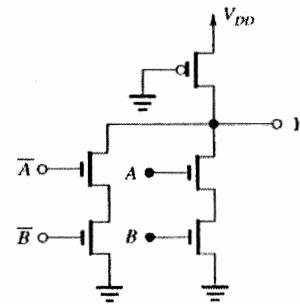

### 15.10


For a pseudo-NMOS NOR gate, independent of the number of inputs, the worst-case value of  $V_{OL}$  occurs for one input high (and a single NMOS conducting)

From Eq. 10.39,  $V_{OL} = (V_{DD} - V_t)[1 - (1 - V_r)^{1/2}]$ ,  
for which  $0.2 = (5.0 - 0.4)[1 - (1 - V_r)^{1/2}]$ ,  
and  $(1 - V_r)^{1/2} = 1 - 0.2/4.2 = 0.952$

Thus  $1 - V_r = 0.907$   
 $V_r = 0.093$ , and  $V_r = 10.76$

Thus  $k_n/k_p = 10.76 = 75(1.8/1.2)/(25(W/L)_p)$   
Thus  $(W/L)_p = (75/25)(1.8/1.2)/10.76 = 0.418$   
Thus for  $W_p = 1.8\mu m$ ,  $L_p = 1.8/0.418 = 4.31\mu m$   
and  $(W/L)_p = (1.8/4.31)$

### 15.11

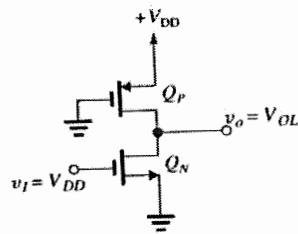

$$V_{DSat} = 0.6V$$

$$V_{DO} = 1.2V$$

$$V_t = 0.4V$$

$$\mu_n C_{ox} = 4 \mu_p C_{ox} = 430 \mu A/V^2$$

$$L = 0.13\mu m$$

In the case of  $Q_p$ ,

$$V_{SG} - V_t = 1.2V - 0.4V = 0.8V, \text{ which is}$$

$$> V_{DSat}$$

For reliable logic levels and noise margins,  
 $V_{SD} > V_{DSat}$  so that  $Q_p$  is operating in the velocity saturation region.

Ignoring channel-length modulation,

$$I_{DSat} = \mu_p C_{ox} \left(\frac{W}{L}\right) |V_{DSat}| \cdot \left[ V_{SG} - |V_t| - \frac{1}{2}|V_{DSat}| \right]$$

$$= \frac{1}{4}(430 \mu A/V^2) \left(\frac{W}{L}\right) (0.6V) \cdot$$

$$\left[ 1.2V - 0.4V - \frac{1}{2}(0.6V) \right]$$

$$I_{DSat} = 32.25 \left(\frac{W}{L}\right) \mu A$$

For  $Q_N$ ,

$$V_{GS} - V_t = 1.2V - 0.4V = 0.8V$$

$$\text{and } V_{DSat} = 0.6V$$

$$V_{GS} - V_t > V_{DSat}, \text{ but } V_{DS} < V_{DSat}$$

This defines the triode region.

$$i_{DN} = \mu_n C_{ox} \left(\frac{W}{L}\right) V_{DS} \left[ (V_{GS} - V_t) - \frac{1}{2}V_{DS} \right]$$

$$i_{DN} = (430 \mu A/V^2) \left(\frac{W}{L}\right) \left[ (0.8V) V_{DS} - \frac{1}{2}V_{DS}^2 \right]$$

$$\text{The unknowns in this problem are } \left(\frac{W}{L}\right)_n, \left(\frac{W}{L}\right)_p$$

and  $V_{DS}$ . One possibility would be to match the source and sink currents for charging the output capacitance.

Without further information, let us assume as in Exercise 13.26

$$\text{that } \left(\frac{W}{L}\right)_n = \left(\frac{W}{L}\right)_p = 1.5$$

In this case,

$$I_{DSat} = 32.25(1.5)\mu A = 48.4\mu A$$

In the static state,

$$i_{DN} = i_{DP} \text{ so that}$$

$$(430 \mu A/V^2)(1.5) \left[ (0.8V) V_{DS} - \frac{1}{2}V_{DS}^2 \right]$$

$$= 48.4\mu A$$

$$0.8V_{DS} - \frac{1}{2}V_{DS}^2 = \frac{48.4\mu A}{430 \mu A(1.5)} = 0.075$$

$$V_{DS}^2 - 1.6V_{DS} + 0.15 = 0$$

$$V_{DS} = \frac{1.6 \pm \sqrt{(1.6)^2 - 4(1)(0.15)}}{2} = 0.8 \pm 0.7 V$$

$$V_{OL} = V_{DS} = 0.1V$$

### 15.12

$$(a) V_{OH} = V_{DD} - V_t$$

$$\text{and } V_t = V_{in} + \gamma(\sqrt{V_{OH} + 2\phi_f} - \sqrt{2\phi_f})$$

$$\text{so, } V_t = V_{in} + \gamma(\sqrt{V_{DD} - V_t + 2\phi_f} - \sqrt{2\phi_f})$$

Substituting values, we have

$$V_t = 0.5V + 0.3V^{1/2} \times$$

$$(\sqrt{1.8V - V_t + 0.85V} - \sqrt{0.85V})$$

$$V_t = 0.22V = (0.3V^{1/2})(\sqrt{2.65V - V_t})$$

Squaring both sides,

$$V_i^2 - 0.44V_i + 0.048 = 0.09(2.65 - V_i)$$

$$\text{or } V_i^2 - 0.35V_i - 0.191 = 0$$

Solving this quadratic, we obtain

$$V_i = 0.646 \text{ V}$$

So that,


$$V_{OH} = V_{DD} - V_i = 1.8 \text{ V} - 0.646 \text{ V} = 1.15 \text{ V}$$

$$\begin{aligned} \text{(b)} i_{DP} &= \frac{1}{2}\mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{DD} - V_{OH} - V_{to})^2 \\ &= \frac{1}{2}75\mu\text{A/V}^2 \left(\frac{0.54}{0.18}\right) (1.8 \text{ V} - 1.15 \text{ V} - 0.5 \text{ V})^2 \end{aligned}$$

$$i_{DP} = 2.53 \mu\text{A}$$

$$P_D = V_{DD} i_{DP} = 1.8 \text{ V} (2.53 \mu\text{A}) = 4.6 \mu\text{W}$$

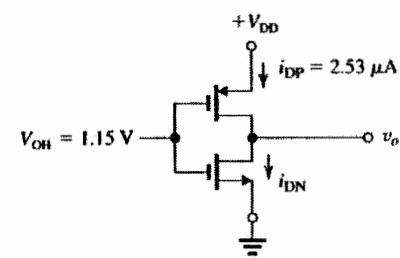To find the inverter's output voltage, we note that  
 $i_{DN} = i_{DP} = 2.53 \mu\text{A}$



Since  $V_{DS} < V_{GS} - V_t$  (triode region), we can  
 to find  $v_o$ :

$$i_{DN} = k_n \left[ (V_t - V_o) v_o - \frac{1}{2} v_o^2 \right]$$

where  $V_t = V_{to}$

$$2.53 \mu\text{A} = 300 \mu\text{A/V}^2 \left(\frac{0.54}{0.18}\right) \times$$

$$\left[ (1.15 \text{ V} - 0.5 \text{ V}) v_o - \frac{1}{2} v_o^2 \right]$$

$$\frac{2.53 \mu\text{A}}{300 \mu\text{A/V}^2 (1.5)} = 0.65 \text{ V } v_o - \frac{1}{2} v_o^2$$

or,

$$v_o^2 - 1.3 v_o + 0.0112 = 0$$

solving for  $v_o$ , we get

$$v_o = 0.01 \text{ V}$$

(c) To find  $t_{PLH}$ , we can follow the procedure of

$$\begin{aligned} i_{D00} &= \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - V_{to})^2 \\ &= \frac{1}{2}300 \mu\text{A/V}^2 1.5 (1.8 - 0.5)^2 \text{ V}^2 = 380.3 \mu\text{A} \end{aligned}$$

$$V_t (\text{at } v_o = 0.9 \text{ V}) = V_{to} + \gamma (\sqrt{v_o + 2\phi_f} - \sqrt{2\phi_f})$$

$$= 0.5 \text{ V} + 0.3 \text{ V}^{1/2} (\sqrt{0.9 \text{ V} + 0.85 \text{ V}} - \sqrt{0.85 \text{ V}})$$

$$V_t = 0.62 \text{ V}$$

$$i_D(t_{PLH}) = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - V_{to} - V_t)^2$$

$$= \frac{1}{2}(300 \mu\text{A/V}^2)(1.5)(1.8 \text{ V} - 0.9 \text{ V} - 0.62 \text{ V})^2$$

$$= 17.6 \mu\text{A}$$

$$i_D|_{av} = \frac{380.3 \mu\text{A} + 17.6 \mu\text{A}}{2} = 199 \mu\text{A}$$

$$t_{PLH} = \frac{C \left(\frac{V_{DD}}{2}\right)}{i_D|_{av}} = \frac{10(10^{-15})F \left(\frac{1.8 \text{ V}}{2}\right)}{199(10^{-6})\text{A}}$$

$$= 0.045 \text{ ns}$$

(d) For  $V_t$  going LOW

$$i_{D(o)} = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - V_{to})^2$$

$$= \frac{1}{2}(300 \mu\text{A/V}^2)(1.5)(1.8 \text{ V} - 0.5 \text{ V})^2 = 380.3 \mu\text{A}$$

$$\text{At } t = t_{PHL}$$

$$i_D(t_{PHL}) = k_n \left[ (V_{DD} - V_{to}) v_o - \frac{1}{2} v_o^2 \right]$$

$$= 300 \mu\text{A/V}^2 \left(\frac{1}{2}\right) \times$$

$$\left[ (1.8 \text{ V} - 0.5 \text{ V})(0.9 \text{ V}) - \frac{1}{2}(0.9 \text{ V})^2 \right]$$

$$i_D(t_{PHL}) = 114.8 \mu\text{A}$$

$$i_D|_{av} = \frac{1}{2}(380.3 \mu\text{A} + 114.8 \mu\text{A}) = 247.6 \mu\text{A}$$

so that,

$$t_{PHL} = \frac{C \left(\frac{V_{DD}}{2}\right)}{i_D|_{av}} = \frac{10(10^{-15})F \left(\frac{1.8 \text{ V}}{2}\right)}{247.6(10^{-6})\text{A}}$$

$$= 0.036 \text{ ns}$$

(e)  $t_p$

$$\frac{1}{2}(t_{PLH} + t_{PHL}) = \frac{1}{2}(0.045 \text{ ns} + 0.036 \text{ ns})$$

$$= 0.04 \text{ ns}$$

### 15 . 13

For a) see directly that  $X = 1 \cdot \bar{A} = \bar{A}$

and  $Y = X \cdot \bar{B} = \bar{A} \cdot \bar{B}$

For b) see directly that  $Y = \bar{A} \cdot \bar{B}$

For each circuit node Y nominally satisfies both conditions. However in a) with A high and B low, Y is not pulled down completely to ground, but remains at  $V_{th}$ , due to the PMOS threshold. Circuit b) does not have this problem, but node X is floating for A,B both high. However, X is not an output node. The body effect makes this worse! Notice that b) is exactly a complementary CMOS

NOR gate for which  $Y = \bar{A} \cdot \bar{B} = \overline{A + B}$

For  $V_{DD}$  replaced by an inverter driven by C,

$$Y = \bar{C}(\bar{A} \cdot \bar{B}) = \bar{A} \cdot \bar{B} \cdot \bar{C} = \overline{A + B + C}$$

a 3-input NOR for both a) and b).

Practically speaking, however, there is a problem because as noted above, the series PMOS do not operate well with a low input. In fact Y is pulled down only to one threshold drop below ground, when C is high.

### 15 . 14

For the switch gate and input both at

$V_{DD} = 3.3V$ , the switch output is

$$V_{OH} = V_{DD} - V_t$$

$$\text{where } V_t = V_{th} + \gamma[\sqrt{V_{DD} + 2\phi_F} - \sqrt{2\phi_F}]$$

Substituting for  $V_{OH}$ , we get :

$$\begin{aligned} V_t &= V_{th} + \gamma[\sqrt{V_{DD} - V_t + 2\phi_F} - \sqrt{2\phi_F}] \\ &= 0.8V + 0.5V^{1/2}[\sqrt{3.3V - V_t + 0.6V} - \sqrt{0.6V}] \end{aligned}$$

So that,

$$V_t = 0.413V + 0.5V^{1/2}\sqrt{3.9V - V_t}$$

$$V_t - 0.413V = 0.5V^{1/2}\sqrt{3.9V - V_t}$$

Squaring both sides, we get

$$V_t^2 - 0.826V_t + 0.171 = 0.975 - 0.25V_t$$

$$\text{or, } V_t^2 - 0.576V_t - 0.804 = 0$$

Solving this quadratic, we find that

$$V_t = 1.23V$$

$$V_{OH} = V_{DD} - V_t = 3.3V - 1.23V = 2.07V$$

with the input Low and the gate switch H1GH,

$$V_{OL} \rightarrow 0V$$

If  $V_{OH} = 2.07V$ , the PMOS transistor of the inverter is in the saturation region. Since the inverter transistors are matched,

$$\left(\frac{W}{L}\right)_P = \frac{k_n}{k_p} \left(\frac{W}{L}\right)_n \text{ so that}$$

$$i_{DP} = \frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L}\right)_P (V_{DD} - V_{OH} - V_{th})^2$$

$$i_{DP} = \frac{1}{2} (25\mu\text{A/V}^2) \left(\frac{1.2}{0.8}\right) (3) \times$$

$$(3.3V - 2.07V - 0.8V)^2 = 10.4\mu\text{A}$$

For  $t_{PLH}$ , at  $t = 0$ ,

$$i_D(0) = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - V_{th})^2$$

$$= \frac{1}{2} (75\mu\text{A/V}^2) \left(\frac{1.2}{0.8}\right) (3.3V - 0.8V)^2 = 352\mu\text{A}$$

$$\text{At } v_O = \frac{V_{DD}}{2},$$

$$V_t = V_{th} + \gamma \left[ \sqrt{\frac{V_{DD}}{2} + 2\phi_F} - \sqrt{2\phi_F} \right]$$

$$= 0.8V + 0.5V^{1/2} \left[ \sqrt{\frac{3.3V}{2} + 0.6V} - \sqrt{0.6V} \right]$$

$$= 1.16V$$

$$i_D(t_{PLH}) = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - v_o - v_t)^2$$

$$= \frac{1}{2} (75\mu\text{A/V}^2) \left(\frac{1.2}{0.8}\right) (3.3V - \frac{3.3V}{2} - 1.16V)^2$$

$$= 13.5\mu\text{A}$$

$$i_D|_{av} = \frac{(352\mu\text{A} + 13.5\mu\text{A})}{2} = 183\mu\text{A}$$

$$t_{PLH} = \frac{C \left(\frac{V_{DD}}{2}\right)}{i_D|_{av}} = \frac{100(10^{-15})F(1.65V)}{183\mu\text{A}}$$

$$= 0.9\text{ ns}$$

For  $t_{PHL}$ ,  $V_t = V_{th}$  and

$$i_{D(O)} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - V_{th})^2$$

$$= \frac{1}{2} (75\mu\text{A/V}^2) \left(\frac{1.2}{0.8}\right) (3.3V - 0.8V)^2 = 352\mu\text{A}$$

$$i_D(t_{PHL}) = \mu_n C_{ox} \left(\frac{W}{L}\right)_n \left[ (V_{DD} - V_{th})v_o - \frac{1}{2}v_o^2 \right]$$


$$= 75\mu\text{A/V}^2 \left(\frac{1.2}{0.8}\right)$$

$$\left[ (3.3V - 0.8V) \left(\frac{3.3V}{2}\right) - \frac{1}{2} \left(\frac{3.3V}{2}\right)^2 \right] = 311\mu\text{A}$$

$$i_D|_{av} = \frac{1}{2} (352\mu\text{A} + 311\mu\text{A}) = 332\mu\text{A}$$

$$t_{PHL} = \frac{C \left(\frac{V_{DD}}{2}\right)}{i_D|_{av}} = \frac{100(10^{-15})F(1.65V)}{332\mu\text{A}} = 0.5\text{ ns}$$

15.15

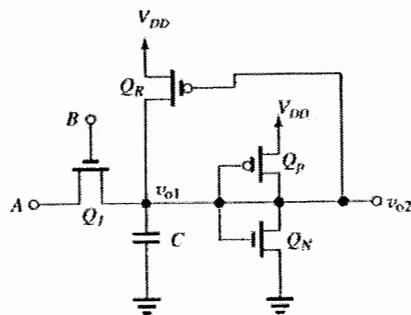

For the inverter, with

$$v_{o2} = V_{DD} - |V_{to}| = 3.3 \text{ V} - 0.8 \text{ V} = 2.5 \text{ V}$$

$Q_N$  is in the saturation region, so that

$$\begin{aligned} i_{DN} &= \frac{1}{2} k_n \left( \frac{W}{L} \right)_n (v_{o1} - v_{to})^2 \\ &= \frac{1}{2} (75 \mu\text{A/V}^2) \left( \frac{1.2}{0.8} \right) (v_{o1} - 0.8 \text{ V})^2 \\ &= 56.25 (v_{o1} - 0.8 \text{ V})^2 \mu\text{A} \\ Q_P &\text{ is operating in the triode region so} \\ i_{DP} &= k_p \left( \frac{W}{L} \right)_p [(V_{DD} - v_{o1} - V_m)(v_{DS}) \\ &\quad - \frac{1}{2}(v_{DS})^2] \\ &= (25 \mu\text{A/V}^2) \left( \frac{3.6}{0.8} \right) \times \\ &\quad [(3.3 \text{ V} - v_{o1} - 0.8 \text{ V})(0.8 \text{ V}) - \frac{1}{2}(0.8 \text{ V})^2] \\ &= 112.5 [1.68 - 0.8 v_{o1}] \mu\text{A} \end{aligned}$$

Since  $i_{DP} = i_{DN}$ , we set these equal:

$$\begin{aligned} 56.25(v_{o1} - 0.8 \text{ V})^2 &= 189 - 90v_{o1} \\ 56.25(v_{o1}^2 - 1.6v_{o1} + 0.64) &= 189 - 90v_{o1} \end{aligned}$$

Simplifying, we get

$$v_{o1}^2 - 2.72 = 0$$

$$v_{o1} = \sqrt{2.72} = 1.65 \text{ V}$$

for  $Q_1$ ,

$$\begin{aligned} v_i &= v_{to} + \gamma [\sqrt{v_{o1} + 2\phi_f} - \sqrt{2\phi_f}] \\ V_t &= 0.8 \text{ V} + 0.5 \text{ V}^{1/2} [\sqrt{1.65 \text{ V}} + 0.6 \text{ V} - \sqrt{0.6 \text{ V}}] \\ &= 1.16 \text{ V} \end{aligned}$$

Capacitor charging current before  $Q_R$  turns on is due to the current supplied by  $Q_r$ .

$$\text{At } v_{o1} : i_D = \frac{1}{2} k_n \left( \frac{W}{L} \right)_n (V_{DD} - v_{o1} - v_i)^2$$

$$= \frac{1}{2} (75 \mu\text{A/V}^2) \left( \frac{1.2}{0.8} \right) (3.3 \text{ V} - 1.65 \text{ V} - 1.16 \text{ V})^2$$

$$= 13.5 \mu\text{A}$$

At  $v_{o1} = 0 \text{ V}$ ,

$$i_D = \frac{1}{2} k_n \left( \frac{W}{L} \right)_n (V_{DD} - v_{to})^2$$

$$= \frac{1}{2} (75 \mu\text{A/V}^2) \left( \frac{1.2}{0.8} \right) (3.3 \text{ V} - 0.8 \text{ V})^2 = 351.6 \mu\text{A}$$

$$i_D|_{av} = \frac{1}{2} (13.5 \mu\text{A} + 351.6 \mu\text{A}) = 182.6 \mu\text{A}$$

$$t_{PLH} = \frac{Cv_{o1}}{i_D|_{av}} = \frac{20(10^{-15})F(1.65 \text{ V})}{182.6(10^{-6}) \text{ A}} = 0.18 \text{ ns}$$

(b) For the inverter,

$$V_{IH} = \frac{1}{8}(5V_{DD} - 2V_i)$$

$$= \frac{1}{8}[5(3.3 \text{ V}) - 2(0.8 \text{ V})] = 1.86 \text{ V}$$

For this value,

$$i_{D1} = k_n \left( \frac{W}{L} \right)_n [(V_{DD} - v_{to})(v_{DS1}) - \frac{1}{2}(v_{DS1})^2]$$

$$i_{D1} = (75 \mu\text{A/V}^2) \left( \frac{1.2}{0.8} \right) \times$$

$$[(3.3 \text{ V} - 0.8 \text{ V})(1.86 \text{ V}) - \frac{1}{2}(1.86 \text{ V})^2]$$

$$i_{D1} = 328.5 \mu\text{A}$$

The current in

$$Q_R = k_p \left( \frac{W}{L} \right)_R (V_{DD} - v_{to})^2 = \frac{i_{D1}}{2}$$

So,

$$(25 \mu\text{A/V}^2) \left( \frac{W}{L} \right)_R (3.3 \text{ V} - 0.8 \text{ V})^2 = \frac{328.5 \mu\text{A}}{2}$$

$$\left( \frac{W}{L} \right)_R = \frac{328.5 \mu\text{A}}{2} = \frac{1}{(25 \mu\text{A/V}^2)(2.5 \text{ V})^2} = 1.05$$

OR,

$$\left( \frac{W}{L} \right)_R = \frac{W}{0.8 \mu\text{m}} \Rightarrow W = 0.84 \mu\text{m}, \text{ and}$$

$$\left( \frac{W}{L} \right)_R = \frac{0.84 \mu\text{m}}{0.8 \mu\text{m}}$$

Initially, at  $v_{o1} = V_{DD}$ ,  $i_{DR} = 0$ , since

$$V_{DSR} = 0, \text{ and } i_{D1} = \frac{1}{2} k_n \left( \frac{W}{L} \right)_n (V_{DD} - v_{to})^2$$

$$= \frac{1}{2} (75 \mu\text{A/V}^2) \left( \frac{1.2}{0.8} \right) (3.3 \text{ V} - 0.8 \text{ V})^2 = 352 \mu\text{A}$$

At  $v_{o1} = V_{IH} = 1.86 \text{ V}$ ,

$$i_{DR} = k_p \left( \frac{W}{L} \right)_R [(V_{SG} - v_{to}) \times$$

$$(V_{DD} - V_{IH}) - \frac{1}{2}(V_{DD} - V_{IH})^2]$$

$$= (25\mu A/V^2)(1.05)((3.3V - 0.8V)(3.3V - 1.86V) \\ - \frac{1}{2}(3.3V - 1.86V)^2]$$

$$= 67.3\mu A$$

$$i_{D1} = k_n \left( \frac{W}{L} \right)_n [(V_{GS} - v_{to})(V_{DS}) - \frac{1}{2}(V_{DS})^2]$$

$$= (75\mu A/V^2) \left( \frac{1.2}{0.8} \right) ((3.3V - 0.8V)(1.86V)$$

$$- \frac{1}{2}(1.86V)^2] = 328.5\mu A$$

$$i_C|_{av} = \frac{1}{2}(328.5 + 352 - 67.3 - 0)\mu A = 306.6\mu A$$

$$t_{PHL} \approx$$

$$\frac{C \Delta v_{OL}}{i_C|_{av}} = \frac{20(10^{-15})F(3.3V - 1.86V)}{306.6\mu A} = 94 \text{ ps}$$

### 15.16

(a) When the input goes HIGH,  $Q$  is ON and  $V_{OH}$  will approach  $+V_{DD}$

(b) when the input goes Low and  $Q$  is ON,

$$V_{OL} \rightarrow |V_{to}|$$

$$(c) i_D(o) = \frac{1}{2}k_p(V_{DD} - |V_{to}|)^2$$

$$i_D(o) = \frac{1}{2}(225\mu A/V^2)(1.8 V - 0.5 V)^2 = 190\mu A$$

$$\text{when } v_o = \frac{V_{DD}}{2} = 0.9 \text{ V},$$

$$i_D(t_{PLH}) = k_p[(V_{DD} - |V_{to}|) \left( \frac{V_{DD}}{2} \right)$$

$$- \frac{1}{2} \left( \frac{V_{DD}}{2} \right)^2]$$

$$i_D(t_{PLH}) = 225\mu A/V^2[(1.8 V - 0.5 V)(0.9 V)$$

$$- \frac{1}{2}(0.9 V)^2]$$

$$= 172\mu A$$

$$i_D|_{av} = \frac{1}{2}(190\mu A + 172\mu A) = 181\mu A$$

$$t_{PLH} = \frac{C \left( \frac{V_{DD}}{2} \right)}{i_D|_{av}} = \frac{C(0.9V)}{181\mu A} = 5000C$$

### 15.17

$$V_{OH} = V_{DD} = 1.8 \text{ V}$$

$$V_{OL} = 0 \text{ V}$$

$$(b) i_{DN}(o) = \frac{1}{2}k_n \left( \frac{W}{L} \right)_n (V_{DD} - V_{in})^2$$

$$= \frac{1}{2}(300\mu A/V^2)(1.5)(1.8V - 0.5V)^2 = 380.3\mu A$$

$$i_{DP}(o) = \frac{1}{2}k_p \left( \frac{W}{L} \right)_p (V_{DD} - V_{in})^2$$

$$= \frac{1}{2}(75\mu A/V^2)(1.5)(1.8 - 0.5)^2 V^2$$

$$= 95.1\mu A$$

$i_{DN}(t_{PLH})$  can be found by finding  $V_t$

$$\text{when } v_o = \frac{V_{DD}}{2} :$$

$$V_t = V_{to} + \gamma(\sqrt{v_o + 2\phi_f} - \sqrt{2\phi_f})$$

$$V_t = 0.5 \text{ V} + 0.3 \text{ V}^{1/2}(\sqrt{0.9 \text{ V} + 0.85 \text{ V}} - \sqrt{0.85 \text{ V}})$$

$$V_t = 0.62 \text{ V}$$

$$i_{DN}(t_{PLH}) = \frac{1}{2} k_n \left( \frac{W}{L} \right)_n \left( V_{DD} - \frac{V_{DD}}{2} - V_t \right)^2$$

$$= \frac{1}{2} (300 \mu\text{A/V}^2) (1.5) (1.8 - 0.9 - 0.62)^2$$

$$= 17.64 \mu\text{A}$$

$$i_{DP}(t_{PLH}) = k_p \left( \frac{W}{L} \right)_p [(V_{DD} - V_{to}) \left( \frac{V_{DD}}{2} \right)]$$

$$- \frac{1}{2} \left( \frac{V_{DD}}{2} \right)^2]$$

$$= (75 \mu\text{A/V}^2) (1.5) [(1.8 \text{ V} - 0.5 \text{ V})(0.9 \text{ V})$$

$$- \frac{1}{2} (0.9 \text{ V})^2]$$

$$= 86.1 \mu\text{A}$$

$$i_D|_{av} \approx$$

$$\frac{1}{2} [i_{DN}(0) + i_{DP}(0) + i_{DN}(t_{PLH}) + i_{DP}(t_{PLH})]$$

$$i_D|_{av} \approx$$

$$\frac{1}{2} [380.3 + 95.1 + 17.6 + 86.1] \mu\text{A} = 290 \mu\text{A}$$

$$t_{PLH} = \frac{C \frac{V_{DD}}{2}}{i_D|_{av}} = \frac{15(10^{-15})F\left(\frac{1.8\text{V}}{2}\right)}{290 \mu\text{A}} = 0.047 \text{ ns}$$

(c) For the situation in Fig. 14.12(b),

$$i_{DN}(o) = \frac{1}{2} k_n \left( \frac{W}{L} \right)_n (V_{DD} - V_{to})^2$$

$$= \frac{1}{2} (300 \mu\text{A/V}^2) (1.5) (1.8 \text{ V} - 0.5 \text{ V})^2 = 380.3 \mu\text{A}$$

$$i_{DP}(o) = \frac{1}{2} k_p \left( \frac{W}{L} \right)_p (V_{DD} - |V_{to}|)^2$$

$$= \frac{1}{2} (75 \mu\text{A/V}^2) (1.5) (1.8 \text{ V} - 0.5 \text{ V})^2 = 95.1 \mu\text{A}$$

$$\text{At } V_o = \frac{V_{DD}}{2} = 0.9 \text{ V},$$

$$i_{DN}(t_{PLH}) = k_n \left( \frac{W}{L} \right)_n \left[ (V_{DD} - V_{to}) v_o - \frac{1}{2} v_o^2 \right]$$

$$= (300 \mu\text{A/V}^2) (1.5) [(1.8 \text{ V} - 0.5 \text{ V})(0.9 \text{ V})$$

$$- \frac{1}{2} (0.9 \text{ V})^2]$$

$$= 344.3 \mu\text{A}$$

To estimate  $i_{DP}(t_{PLH})$ , we find  $|V_{tp}|$  at

$$v_o = \frac{V_{DD}}{2};$$

$$|V_{tp}| (\text{at } V_o = 0.9 \text{ V}) = |V_{to}| + \gamma \times$$

$$[\sqrt{V_{DD} - v_o + 2\phi_f} - \sqrt{2\phi_f}]$$

$$= 0.5 \text{ V} + 0.3 \text{ V}^{1/2} [\sqrt{1.8 \text{ V} - 0.9 \text{ V}} + 0.85 \text{ V}$$

$$- \sqrt{0.85 \text{ V}}]$$

$$= 0.62 \text{ V}$$

$$i_{DP}(t_{PLH}) = \frac{1}{2} k_p \left( \frac{W}{L} \right)_p (V_{DD} - v_o - V_t)^2$$

$$= \frac{1}{2} (75 \mu\text{A/V}^2) (1.5) (1.8 \text{ V} - 0.9 \text{ V} - 0.62 \text{ V})^2$$

$$= 4.41 \mu\text{A}$$

$$i_D|_{av} \approx$$

$$\frac{1}{2} [i_{DN}(0) + i_{DP}(0) + i_{DN}(t_{PLH}) + i_{DP}(t_{PLH})]$$

$$= \frac{1}{2} [380.3 + 95.1 + 344.3 + 4.41] \mu\text{A} = 412 \mu\text{A}$$

$$t_{PLH} = \frac{C \left( \frac{V_{DD}}{2} \right)}{i_D|_{av}} = \frac{15(10^{-15})F(0.9 \text{ V})}{412 \mu\text{A}}$$


$$= 0.033 \text{ ns}$$

$Q_P$  will turn off when  $v_o = |V_{tp}| = 0.5 \text{ V}$

$$(d) t_p = \frac{1}{2} (t_{PLH} + t_{PLL}) = \frac{1}{2} (0.047 + 0.033) \text{ ns}$$

$$= 0.04 \text{ ns}$$

## 15.18

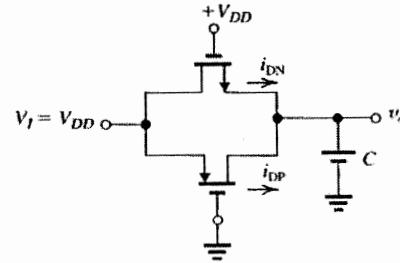

With  $V_I$  going to  $V_{DD}$  and  $v_o(o) = 0 \text{ V}$ ,

$$R_{N_{eq}} = \frac{V_{DD} - v_o}{\frac{1}{2} k_n \left( \frac{W}{L} \right)_n (V_{DD} - V_{to} - v_o)^2}$$

$$= \frac{1.8 \text{ V} - 0 \text{ V}}{\frac{1}{2} (300 \mu\text{A/V}^2) (1.5) (1.8 \text{ V} - 0.5 \text{ V} - 0 \text{ V})^2}$$

$$= 4.7 \text{ k}\Omega$$

$$R_{P_{eq}} = \frac{V_{DD} - 0}{\frac{1}{2} k_p \left( \frac{W}{L} \right)_p (V_{DD} - |V_{tp}|)^2}$$

$$= \frac{1.8 \text{ V} - 0}{\frac{1}{2} (75 \mu\text{A/V}^2) (1.5) (1.8 \text{ V} - 0.5 \text{ V})^2}$$

$$R_{P_{eq}} = 18.9 \text{ k}\Omega$$

$$R_{TG}(V_o = 0) = R_{N_{eq}} \parallel R_{P_{eq}} = 4.7 \text{ k}\Omega \parallel 18.9 \text{ k}\Omega$$

$$= 3.76 \text{ k}\Omega$$

when  $V_o = 0.9 \text{ V}$ ,  $Q_N$  is still considered in the saturation region.

So,  $R_{N_{eq}}$  ( $V_o = 0.9$  V)

$$= \frac{V_{DD} - v_o}{\frac{1}{2}k_n(W/L)(V_{DD} - V_{in} - v_o)^2}$$

$$\text{Where } V_{in} = V_{to} + \gamma(\sqrt{V_o + 2\phi_f} - \sqrt{2\phi_f}) \\ = 0.5 + 0.3 \text{ V}^{1/2} (\sqrt{0.9 \text{ V} + 0.85 \text{ V}} - \sqrt{0.85 \text{ V}}) \\ = 0.62 \text{ V}$$

$$R_{N_{eq}} = \frac{1.8 \text{ V} - 0.9 \text{ V}}{\frac{1}{2}(300 \mu\text{A/V}^2)(1.5)(1.8 \text{ V} - 0.62 \text{ V} - 0.9 \text{ V})^2} = \frac{1}{k_n[(V_{DD} - V_{in}) - \frac{1}{2}v_o]}$$

$$= 51 \text{ k}\Omega$$

$$R_{P_{eq}} = \frac{1}{k_p \left( \frac{W}{L} \right)_p [V_{DD} - |V_{ip}| - \frac{1}{2}(V_{DD} - V_o)]}$$

$$R_{P_{eq}} = \frac{1}{(75 \mu\text{A/V}^2)(1.5)[1.8 \text{ V} - 0.5 \text{ V} - \frac{1}{2}(1.8 \text{ V} - 0.9 \text{ V})]} \quad \text{where}$$


$$= 10 \text{ k}\Omega$$

$$R_{TG}(V_o = 0.9 \text{ V}) = R_{N_{eq}} \parallel R_{P_{eq}} = 51 \text{ k}\Omega \parallel 10 \text{ k}\Omega \\ = 8.36 \text{ k}\Omega$$

$$R_{TG}|_{av} = \frac{1}{2}(3.76 \text{ k}\Omega + 8.36 \text{ k}\Omega) = 6.06 \text{ k}\Omega$$

$$t_{PLH} \approx 0.69 R_{TG} C = 0.69(6.06 \text{ k}\Omega)(1.5)(10^{-15})F \\ = 62.7 \text{ ps}$$

### 15.19

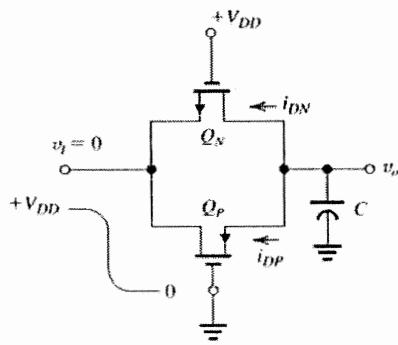

C is charged so that  $v_o = V_{DD}$

When  $v_i$  goes Low to OV,  $Q_N$  is initially in the saturation region w.th

$$i_{DN} = \frac{1}{2}k_n(V_{DD} - V_{in})^2$$

until  $V_{DSN} = V_{GS} - V_{in} = V_{DD} - V_{in}$

$$R_{N_{eq}} = \frac{v_o - 0}{\frac{1}{2}k_n(V_{DD} - V_{in})^2} = \frac{2v_o}{k_n(V_{DD} - V_{in})^2}$$

for  $v_o \geq V_{DD} - V_{in}$

When  $Q_N$  enters the triode region,

$$i_{DN} = k_n[(V_{DD} - V_{in})v_o - \frac{1}{2}v_o^2]$$

for  $v_o \leq V_{DD} - V_{in}$

$$\text{Then, } R_{N_{eq}} = \frac{v_o}{k_n[(V_{DD} - V_{in})v_o - \frac{1}{2}v_o^2]}$$

For  $Q_P$  initially,

$$i_{DP} = \frac{1}{2}k_p(v_o - |V_{ip}|)^2 \text{ so that}$$

$$R_{P_{eq}} = \frac{2v_o}{k_p(v_o - |V_{ip}|)^2}$$

$$|V_{ip}| = |V_{to}| + \gamma(\sqrt{V_{DD} - v_o + 2\phi_f} - \sqrt{2\phi_f})$$

until  $v_o = |V_{ip}|$

For  $v_o = V_{DD}$

$$R_{N_{eq}}(v_o = V_{DD}) = \frac{2V_{DD}}{k_n \left( \frac{W}{L} \right)_n (V_{DD} - V_{in})^2}$$

$$= \frac{2(1.8 \text{ V})}{(300 \mu\text{A/V}^2)(1.5)(1.8 \text{ V} - 0.5 \text{ V})^2} = 4.7 \text{ k}\Omega$$

$$R_{N_{eq}}(v_o = V_{DD}) = \frac{2V_{DD}}{k_p \left( \frac{W}{L} \right)_p (V_{DD} - |V_{ip}|)^2}$$

$$= \frac{2(1.8 \text{ V})}{(75 \mu\text{A/V}^2)(1.5)(1.8 \text{ V} - 0.5 \text{ V})^2} = 18.9 \text{ k}\Omega$$

$$R_{TG}(v_o = V_{DD}) = R_{N_{eq}} \parallel R_{P_{eq}} = 4.7 \text{ k}\Omega \parallel 18.9 \text{ k}\Omega$$

$$= 3.76 \text{ k}\Omega$$

$$\text{At } v_o = \frac{V_{DD}}{2} = 0.9 \text{ V}$$

$$V_{DD} - V_{in} = 1.8 \text{ V} - 0.5 = 1.3 \text{ V}$$

$$\text{since } V_{DS} = v_o - 0 = 0.90$$

$Q_N$  is in the triode region.

$$R_{N_{eq}} = \frac{1}{k_n \left( \frac{W}{L} \right)_n [(V_{DD} - V_{in}) - \frac{1}{2}v_o]}$$

$$= \frac{1}{(300 \mu\text{A/V}^2)(1.5)\left(1.8 \text{ V} - 0.5 \text{ V} - \frac{0.9 \text{ V}}{2}\right)}$$

$$R_{N_{eq}}(0.9 \text{ V}) = 2.6 \text{ k}\Omega$$

$$\text{At } v_o = 0.9 \text{ V},$$

$$|V_{ip}| = |V_{to}| + \gamma(\sqrt{V_{DD} - v_o + 2\phi_f} - \sqrt{2\phi_f})$$

$$= 0.5 \text{ V} + 0.3 \text{ V}^{1/2} \sqrt{1.8 \text{ V} - 0.9 \text{ V} + 0.85 \text{ V}}$$

$$= \sqrt{0.85 \text{ V}}$$

$$= 0.62 \text{ V}$$

$$\begin{aligned}
 R_{req} &= \frac{2v_o}{k_p \left(\frac{W}{L}\right)_p (v_o - |V_{tp}|)^2} \\
 &= \frac{2(0.9 \text{ V})}{(75 \mu\text{A/V}^2)(1.5)(0.9\text{V} - 0.62\text{V})^2} \\
 &= 204 \text{ k}\Omega \\
 R_{TG}(v_o = 0.9\text{V}) &= 2.6 \text{ k}\Omega \parallel 204 \text{ k}\Omega = 2.57 \text{ k}\Omega \\
 R_{TG}|_{av} &= \frac{1}{2}(3.76 \text{ k}\Omega + 2.57 \text{ k}\Omega) = 3.17 \text{ k}\Omega \\
 t_{PLH} &= 0.69 R_{TG} C = 0.69(3.17 \text{ k}\Omega)(15)(10^{-15})F \\
 &= 32.8 \text{ ps} \\
 (\text{This is close to the answer of Problem 14.19})
 \end{aligned}$$

### 15.20

$$R_{TG} = \frac{12.5}{\left(\frac{W}{L}\right)_n} \text{ k}\Omega = \frac{12.5}{1.5} \text{ k}\Omega = 8.3 \text{ k}\Omega$$


$$t_P = t_{PLH} = t_{PLH} = 0.69 R_{TG} C = 0.69(8.3 \text{ k}\Omega) \times (10)(10^{-15})F = 57.3 \text{ ps}$$

### 15.21


$$\begin{aligned}
 t_p &= 0.69 C R_{TG} \cdot \frac{n(n+1)}{2} \\
 &= 0.69(10)(10^{-15})F(10 \text{ k}\Omega) \frac{16(16+1)}{2} = 9.38 \text{ ns}
 \end{aligned}$$
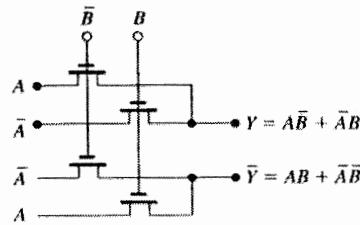
### 15.22

Need a CPL circuit for  $Y = A\bar{B} + \bar{A}B$  and  $\bar{Y} = AB + \bar{A}\bar{B}$  (See Exercise 14.8b)



### 15.23

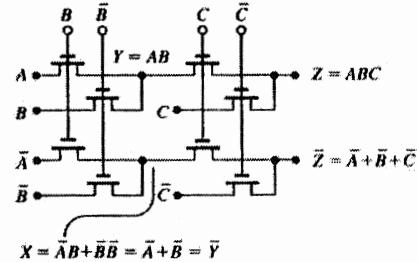

$$X = \bar{A}B + \bar{B}\bar{B} = \bar{A} + \bar{B} = \bar{Y}$$

Require a CPL for  $Z = ABC$  and


$$\bar{Z} = \overline{ABC} = \bar{A} + \bar{B} + \bar{C}$$

Extend Fig 14.18 to 3 variables by dealing in pairs, creating  $Y = AB$ , then  $Z = YC$  with

$$\bar{Y} = \bar{A} + \bar{B}$$

$$\bar{Z} = \bar{Y} + \bar{C}$$

### 15.24

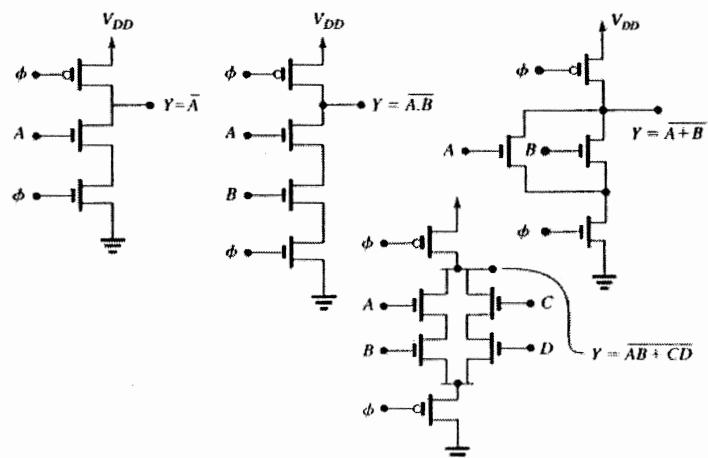

15.25

$$\text{At } V_Y = 0.3V, i_{Dp} = k_2 \left( \frac{75}{2} \right) \left( 2.4 / 0.8 \right) \left( 3.0 - 0.8 \right) = \underline{181.5A}$$

$$\text{At } V_Y = 2.7V, i_{Dp} = \left( \frac{75}{2} \right) \left( 2.4 / 0.8 \right) \left[ \left( 3.0 - 0.8 \right) 0.3 - 0.3^2 \right] = \underline{46.1A}$$

$$\text{Thus } i_{Dav} = (181.5 + 46.1) / 2 = \underline{114.4A}$$

$$\text{and } t_{RLH} = t_p = 15 \times 10^{-9} (2.7 - 0.3) / (114 \times 10^{-6}) = \underline{316 \mu s}$$

15.26

$$\text{For a } 0.5V \text{ change, } t = \frac{C_{av} V}{I_L} = 30 \times 10^{-9} \times 0.5 / 10^{-6} = \underline{15ms}$$

Since the precharge interval is much shorter than the evaluate, the period of the minimum clocking frequency can be as great as 15ms, for which  $f_{min} = 1 / (15 \times 10^{-3}) = \underline{67Hz}$

15.27

a)  $C_1 = 5FF$ :

Now, for  $V_{C1}$  rising to  $V_{DD} - V_t = 5.1 + 4V$ , and assuming  $Q_1$  continues to conduct,  $V_Y$  will fall by an amount  $(C_1/C_s)(\Delta V_{C1}) = 5/30(4) = \underline{0.67V}$  to  $5.0 - 0.67 = 4.33V$ . Since this exceeds 4.0, the assumption that  $Q_1$  continues to conduct is verified. Thus  $V_Y$  drops by 0.67V

Note that if the body effect is included, it will likely to be impossible to raise  $V_{C1}$  to 4V. Thus 0.67V is the largest possible change.

b)  $C_1 = 10FF$ :

In view of the previous analysis, assume that ultimately  $V_Y = V_{C1} = V$ . Now, the charge change in each capacitor is the same:  
 $Q = CV \rightarrow 10(V - 0) = 30(5 - V)$   
 and  $10V = 150 - 30V$ ,  $40V = 150$ , and  $V = \underline{3.75V}$

Thus  $V_Y$  drops by  $5 - 3.75 = \underline{1.25V}$  to 3.75V

15.28

(a) Since  $Q_1$  and  $Q_{c1}$  are in series,  $W$  remains the same, but the effective length doubles. So,

$$\left( \frac{W}{L} \right)_{eq1} = \left( \frac{W}{2L} \right) = \frac{1}{2} \left( \frac{W}{L} \right)_n$$

Similarly,

$$\left( \frac{W}{L} \right)_{eq1} = \left( \frac{W}{2L} \right) = \frac{1}{2} \left( \frac{W}{L} \right)_n$$

(b)

$$\begin{aligned} i_{D1} (V_{Y1} = V_{DD}) &= \frac{1}{2} k_n \left( \frac{W}{L} \right)_{eq1} (V_{DD} - 0.2V_{DD})^2 \\ &= \frac{1}{2} k_n \left( \frac{W}{L} \right)_{eq1} (0.64 V_{DD}^2) \\ &= 0.32 k_n \left( \frac{W}{L} \right)_{eq1} V_{DD}^2 \\ &= 0.16 k_n \left( \frac{W}{L} \right)_n V_{DD}^2 = 0.16 k_n V_{DD}^2 \end{aligned}$$

At  $V_{Y1} = V_i$ :

$$\begin{aligned} i_{D1} (V_{Y1} = V_i) &= k_n \left( \frac{W}{L} \right)_{eq1} \times \\ &\quad [(V_{DD} - 0.2V_{DD})(0.2V_{DD}) - \frac{1}{2}(0.2V_{DD})^2] \\ &= k_n \left( \frac{W}{L} \right)_{eq1} [0.16V_{DD}^2 - 0.02V_{DD}^2] \end{aligned}$$

$$\begin{aligned}
 &= k_n \left( \frac{W}{L} \right)_{eq1} V_{DD}^2 = 0.07 k_n \left( \frac{W}{L} \right)_n V_{DD}^2 \\
 &= 0.07 k_n V_{DD}^2 \\
 i_{D1} \Big|_{av} &= \\
 &= \frac{1}{2} \left[ 0.16 k_n \left( \frac{W}{L} \right)_n V_{DD}^2 + 0.07 k_n \left( \frac{W}{L} \right)_n V_{DD}^2 \right] \\
 &= 0.115 k_n \left( \frac{W}{L} \right)_n V_{DD}^2 = 0.115 k_n V_{DD}^2 \\
 (c) \Delta t &= \frac{C_{L1}(V_{DD} - V_t)}{i_{D1} \Big|_{av}} = \frac{C_{L1}(0.8V_{DD})}{0.115 k_n V_{DD}^2} \\
 &= \frac{6.96 C_{L1}}{k_n V_{DD}}
 \end{aligned}$$

(d)  $Q_{eq2}$  will conduct during the time that  $v_{y1}$  drops from  $V_{DD}$  to  $V_t$ . The transition half point is

$$\text{when } v_{y1} \Big|_{av} = \frac{V_{DD} - 0.2V_{DD} + 0.2V_{DD}}{2}$$

$$v_{y1} \Big|_{av} = 0.6V_{DD}$$

$$\begin{aligned}
 i_{D2} \Big|_{av} &= \frac{1}{2} k_n \left( \frac{W}{L} \right)_{eq2} (0.6V_{DD} - 0.2V_{DD})^2 \\
 &= 0.08 k_n \left( \frac{W}{L} \right)_{eq2} V_{DD}^2 = 0.04 k_n V_{DD}^2
 \end{aligned}$$

$$(e) \Delta v_{y2} = -\frac{i_{D2} \Big|_{av} \Delta t}{C_{L2}}$$

Since  $C_{L1} = C_{L2}$

$$\Delta v_{y2} = -\frac{0.04 k_n V_{DD}^2 (6.96 C_{L1})}{C_{L1} k_n V_{DD}} = -0.278 V_{DD}$$

So that  $v_{y2}$  is  $V_{DD} - 0.278 V_{DD} = 0.72 V_{DD}$

## 15.29

The precharge time can be approximated as the rise time of the output voltage. In Example 14.3,  $t_r \approx 0.19$  ns. Assuming that the evaluation time is relatively short, the total cycle time can be estimated as being slightly longer than  $t_r + t_{PHL}$ .

With  $t_{PHL} \approx 0.25$  ns, the maximum clocking frequency is  $f \leq \frac{1}{T} = \frac{1}{(t_r + t_{PHL})}$

$$= \frac{1}{(0.19 + 0.25)(10^{-9})} = 2.27 \text{ GHz}$$

## 15.30

$$(a) V_{OH} = 0 - 0.75 = -0.75 \text{ V}$$

$$V_{OL} = 0 - 0.75 - IR = -(0.75 + IR)$$

(b)

$$V_{th} = -(IR/2 + 0.75) = -(0.75 + IR/2)$$

(c) For  $i = 0.99 I$ ,

$$v_{gt} \approx 750 + 25 \ln(0.99) = 750 \text{ mV}$$

$$i = 0.01 I, \\ v_{BE} = 750 + 25 \ln(0.01) = 635 \text{ mV}$$

For

$$0.99I \text{ in } Q_R,$$

$$\begin{aligned}
 v_I &= -\left(0.75 + \frac{IR}{2}\right) = (0.750 - 0.635) \\
 &= -(0.875 + IR/2)
 \end{aligned}$$

(d) For  $0.01I$  in  $Q_R$ ,

$$\begin{aligned}
 v_I &= -(0.75 + IR/2) + 0.115 \\
 &= -(0.635 + IR/2)
 \end{aligned}$$

$$(e) V_{IH} = -(0.635 + IR/2)$$

$$V_{IL} = -(0.875 + IR/2)$$

$$\begin{aligned}
 (f) NM_H &= -0.75 - [-(0.635 + IR/2)] \\
 &= IR/2 - 0.115
 \end{aligned}$$

$$\begin{aligned}
 NM_L &= -(0.875 + IR/2) - [-(0.75 + IR)] \\
 &= IR/2 - 0.115
 \end{aligned}$$

$$\begin{aligned}
 (g) V_{IH} - V_{IL} &= -(0.635 + IR/2) - [-(0.875 + IR/2)] \\
 \text{That is: } IR/2 - 0.115 &= 0.230
 \end{aligned}$$

and  $IR = 2(0.345) = 0.690 \text{ V}$

$$(h) V_{OH} = -0.75 \text{ V};$$

$$V_{OL} = -0.75 - 0.69 = -1.44 \text{ V};$$

$$V_{IH} = -(0.875 + 0.345) = -1.22 \text{ V};$$

$$V_{IL} = -(0.635 + 0.345) = -0.98 \text{ V};$$

$$V_R = -(0.750 + 0.345) = -1.095 \text{ V}.$$

## 15.31

See that once started the process continues; that is we have an oscillation. In each cycle, each gate output rises and falls.


Thus the period is  $3(3+7) = 30 \text{ ns}$

Frequency is  $1/30 = 33.3 \text{ MHz}$ .

Any output is high for  $3+7+3 = 13 \text{ ns}$

and low for  $7+3+7 = 17 \text{ ns}$

Check: 30 ns.

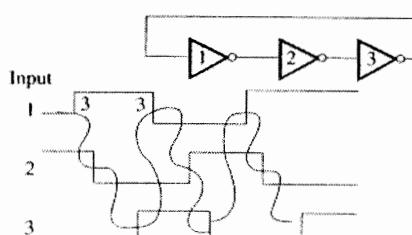



$$\frac{v_{OR}}{v_i} = \frac{50 \Omega}{5.4 \Omega + 50 \Omega} \cdot \left(\frac{100}{101}\right) \cdot \frac{(245 \Omega \parallel 5.6 \text{ k}\Omega)}{630 \Omega + 6.4 \Omega} \\ = 0.33 \text{ V/V}$$

At point m,

$$I_{EA} = I_{EB} = \frac{I_E}{2} = \frac{4 \text{ mA}}{2} = 2 \text{ mA}$$

$$r_{eA} = r_{eB} = \frac{V_T}{I_{EA}} = \frac{25 \text{ mV}}{2 \text{ mA}} = 12.5 \Omega$$

$$I_{E2} = \frac{v_{OR} - V_{BE}}{R_T} = \frac{-1.31 - (-2 \text{ V})}{50 \Omega} = 13.8 \text{ mA}$$

$$r_{e2} = \frac{V_T}{I_{E2}} = \frac{25 \text{ mV}}{13.8 \text{ mA}} = 1.81 \Omega$$

$$R_{in2} = (\beta + 1)(R_T + r_{e2}) = (101)(50 + 1.81) \\ = 5.23 \text{ k}\Omega$$

$$\text{Gain} = \frac{V_{OR}}{V_i} = \frac{50 \Omega}{50 \Omega + 1.81 \Omega} \cdot \left(\frac{100}{101}\right) \\ \cdot \frac{(245 \Omega \parallel 5.23 \text{ k}\Omega)}{12.5 \Omega + 1.81 \Omega} = 8.95 \text{ V/V}$$

At point Y,

$$I_{EA} = 0.99(4.12 \text{ mA}) = 4.08 \text{ mA}$$

$$r_{eA} = \frac{V_T}{I_{EA}} = \frac{25 \text{ mV}}{4.08 \text{ mA}} = 6.13 \Omega$$

$$I_{EB} = (0.01)(4.12 \text{ mA}) = 41.2 \mu\text{A}$$

$$r_{eB} = \frac{V_T}{I_{EB}} = \frac{25 \text{ mV}}{41.2 \mu\text{A}} = 607 \Omega$$

$$I_{E2} = \frac{v_{OR} - V_{BE}}{R_T} = \frac{-0.88 \text{ V} - (-2 \text{ V})}{50 \Omega} \\ = 22.4 \text{ mA}$$

$$r_{e2} = \frac{25 \text{ mV}}{22.4 \text{ mA}} = 1.1 \Omega$$

$$R_{in2} = (101)(50 \Omega + 1.1 \Omega) = 5.16 \text{ k}\Omega$$

$$\text{Gain} = \frac{V_{OR}}{V_i} = \frac{50 \Omega}{50 \Omega + 1.1 \Omega} \cdot \left(\frac{100}{101}\right)$$

$$\cdot \frac{(245 \Omega \parallel 5.16 \text{ k}\Omega)}{607 \Omega + 6.13 \Omega} = 0.37 \text{ V/V}$$

### 15.35

Assume  $I_E$  is constant at 4 mA.

(a) Currents are: 3.6 mA and 0.4 mA

$$\therefore \text{Emitter-Base voltage difference} = V_T \ln \frac{3.6}{0.4}$$

or  $25 \ln 9 = 54.9 \text{ mV}$ .

$$\text{Thus } V_{IL} = -1.32 - .055 = -1.375 \text{ V}$$

$$V_m = -1.32 + .055 = -1.265 \text{ V}$$

(b) Currents are:  $4(0.999) = 3.996 \text{ mA}$  and

$$.001 \times 4 = 0.004 \text{ mA}$$

$\therefore$  Emitter-Base voltage difference =

$$V_T \ln \left( \frac{3.996}{0.004} \right)$$

### 15.36

$NM_H = 0.325 \text{ V}$ , of which 50% is 162 mV, for  $\beta=100$ , and  $V_{BE2} = 0.83 \text{ V}$ ,  $I_{E2} = 22.4 \text{ mA}$ .

Approximately:

$$-2 + \frac{50}{50 + \frac{245}{\beta + 1}} \cdot (2 - 0.83) = -0.88 - 0.162$$

$$\text{or } \frac{50(1.17)}{50 + \frac{245}{\beta + 1}} = 0.958$$

$$50 + \frac{245}{\beta + 1} = 61.06$$


$$\text{Hence } \beta = \frac{245}{11.06} - 1 = 21.2$$

Check: For  $V_o = -0.88 - .162 = -1.042 \text{ V}$

$$I_{E2} = \frac{2 - 1.042}{50} = 19.2 \text{ mA}$$

and  $V_T \ln \left( \frac{22.4}{19.2} \right) = 3.85 \text{ mV}$  – OK, Since small, can ignore.

### 15.37

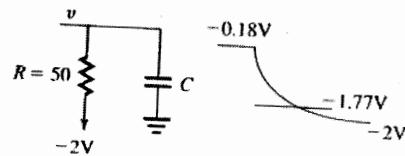

$$v = -0.88 + (.88 - 2)(1 - e^{-t/RC})$$

$$\text{or } v = -2 + 1.12 e^{-t/50 \text{ s}}$$

After 1ns,  $v = -1.77 \text{ V}$

$$\text{i.e., } -1.77 = -2 + 1.12 e^{-1/50 \text{ s}}$$

$$\text{or } e^{-1/50 \text{ C}} = \frac{2 - 1.77}{1.12} \text{ and}$$

$$-1/50 \text{ C} = -1.583$$

Thus

$$C = \frac{10^{-9}}{50(1.583)} = 12.6 \times 10^{-12} \text{ F} = 12.6 \text{ pF}$$

### 15.38

$$v = 2/3 \times 30 \text{ cm/ns} \times 20 \text{ cm/ns}$$


$$\text{Rate} = \frac{\text{Rise Time}}{\text{Return Time}} = 5/1 = \frac{3.5}{2L/20}$$

$$L = \frac{3.5 \text{ ns} \times 20 \text{ cm/ns}}{5 \times 2} = 7 \text{ cm}$$

### 15.39

$$V_{OL} = 0.7 \text{ V}; V_{OH} = +5.0 \text{ V}$$

More precisely, for  $V_{OL} = v$

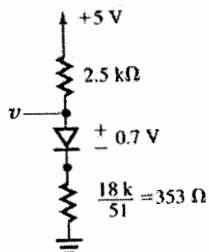

$$v = \frac{0.353}{2.5 + 0.353}(5 - 0.7) + 0.7 = 1.23 \text{ V}$$

$$\text{i.e., } V_{OL} = 1.23 \text{ V}$$

Logically: A is high if one of A or B and one of C or D are high.

That is A = (A + B) · (C + D)

### 15.40

$$\text{For } V_1 = V_o = V_{DD/2} = 5/2 = 2.5 \text{ V.}$$

$$\begin{aligned} i_{DN} &= (1/2) k_n (W/L)_n (V_{GS} - V_t)^2 \\ &= (1/2)(100)10^{-6}(2/1)(2.5 - 0.7 - 1)^2 \\ &= 64 \mu\text{A} \end{aligned}$$

Now, the collector current of

$$\begin{aligned} Q_2 &= \beta i_B = \beta i_{DN} \\ &= 100(64 \times 10^{-6}) = 6.4 \text{ mA} \end{aligned}$$

Corresponding, the totem-pole current is

$$i_{EQ2} = (6400 + 64)10^{-6} = 6.46 \text{ mA}$$

Now, for  $i_{EQ1} = i_{EQ2}$ ,  $i_{DP} = i_{DN} = 64 \mu\text{A}$

Thus

$$64 = 1/2(100/2.5)(W/L)_p(5 - 2.5 - 0.7 - 1)^2$$

$$\text{where } (W/L)_p = 2.5(2/1) = (5\mu\text{m}/1\mu\text{m})$$

### 15.41

At the threshold  $V_{th}$ ,  $v_o = v_t = V_{th} = v$ , and the two MOS operate in saturation with equal currents. Thus

$$1/2(100)(2/1)(5 - y - 0.7 - 1)^2$$

$$\text{Thus, } (3.3 - v)^2 = 2.5(v - 1.7)^2$$

$$\text{and } (3.3 - v) = \pm \sqrt{2.5} (v - 1.7).$$

$$\text{Usefully, } (3.3 - v) = (1.58v - 2.69), \text{ hence } 2.58v = 5.99, \text{ and } v = V_{th} = 2.32 \text{ V}$$

For this value,

$$\begin{aligned} i_{DN} &= 1/2(100)(2/1)(2.32 - 0.7 - 1) \\ &= 38.4 \mu\text{A} \end{aligned}$$

and the totem-pole current is  $(\beta + 1)i_{DN}$

$$\text{or } 101(38.4)10^{-6} = 3.88 \text{ mA}$$

### 15.42

The problem as stated is very general, and correspondingly, its solution can be long and complex. the specifications of matched MOS having

$$(W/L)_p = 2.5(W/L)_n$$

$$\text{For } R_2: \text{With } v_{DS} = V_{DD/2} = 1/3 = 0.333 \text{ V}$$

$$i_{DN} = 100(10^{-6})(2/1) \times$$

$$[(5 - 0.7 - 1)0.33 - 0.33^2/2] = 209 \mu\text{A}$$

Now, if 50% of this is lost in  $R_2$ ,

$$R_2 = 0.7 / (0.50 \times 209) = 6.70 \text{ k}\Omega$$

Now if 20% is lost in  $R_2$ ,

$$R_2 = 0.7 / (0.20 \times 209) = 16.7 \text{ k}\Omega$$

$$\text{For } R_1: i_{DP} = (100/2.5)10^{-6}(2.5(2/1)) \times$$

$$[(5 - 0 - 1)0.33 - 0.33^2/2] = 256 \mu\text{A}$$

Now, if 50% of this is lost in  $R_1$ ,

$$R_1 = (5 - 0.333) / (0.5 \times 256) = 36.5 \text{ k}\Omega$$

Now, if 20% is lost in  $R_1$ ,

$$R_1 = 2.5(36.5) = 91.1 \text{ k}\Omega$$

In comparison:

For the 50% case,

$$R_1 / R_2 = 36.5 / 6.70 = 5.45$$

For the 20% case,

$$R_1 / R_2 = 91.1 / 16.7 = 5.45$$

(why should their equality be obvious?)

Thus, in general  $R_1 / R_2 = 5.45$

### 15.43

For  $t_{PLH}$ :

At  $V_O = 0 \text{ V}$ ,

$$i_{D_P} = \frac{1}{2}(100/2.5)(2/1)(5.0 - 1)^2 = 640 \mu\text{A}$$

At

$V_O = 2.5 \text{ V}$ ,

$$i_{D_P} = (100/2.5)(2/1)[(5 - 1)2.5 - 2.5^2 / 2] = 550 \mu\text{A}$$

Thus  $i_{D_{Pav}} = (640 + 550)/2 = 595 \mu\text{A}$

and  $i_{D_{av}} = (100 + 1)595 = 60.1 \text{ mA}$

Thus

$$t_{PLH} = CV/I = 2 \times 10^{-12} \times 2.5 / (60.1 \times 10^{-3}) = 83.2 \text{ ps}$$

For  $t_{PHL}$ :

At

$v_O = 5.0 \text{ V}$ ,

$$i_{DN} = \frac{1}{2}(100)(2/1)(5 - 0.7 - 1)^2 = 1.09 \text{ mA}$$

At

$v_O = 2.5 \text{ V}$ ,  $i_{DN} = 100(2/1)$

$$[(5 - 0.7 - 1)(2.5 - 0.7) - (2.5 - 0.7)^2 / 2] = 864 \mu\text{A}$$

Thus

$$i_{D_{Nav}} = (1089 + 864)/2 = 977 \mu\text{A}$$

and  $i_{D_{av}} = 101(977 \times 10^{-6}) = 98.6 \text{ mA}$

Thus

$$t_{PHL} = CV/I = 2 \times 10^{-12}(2.5) / (98.6 \times 10^{-3}) = 50.7 \text{ ps}$$

Thus  $t_p = (83.2 + 50.7)/2 = 67.0 \text{ ps}$

Note that this solution embodies two assumptions

- 1) Internal capacitances can be neglected.
- 2) Transitions are from ideal 0 V and 5 V output-signal level.

If outputs of  $(5 - 0.7) = 4.3 \text{ V}$  and  $(0 + 0.7) = 0.7 \text{ V}$  apply,  $t_p$  becomes about  $67 \times (2.5 - 0.7) / 2.5 = 48 \text{ ps}$

### 15.44

$$R_1 = R_2 = 5 \text{ k}\Omega$$

robs the base of some of its drive current, namely  $0.7/5 \times 10^3 = 140 \mu\text{A}$ . Using results from the solution of P 14.46 above :

For  $t_{PLH}$

$$i_{R_{av}} = 595 - 140 = 455 \mu\text{A} \text{ and}$$

$$i_{R_{av}} = 101(455 \times 10^{-6}) = 46.0 \text{ mA}$$

Thus

$$t_{PLH} = 2 \times 10^{-12} \times 2.5 / 4.6 \times 10^{-3} = 108.7 \text{ ps}$$

For  $t_{PLH}$ :

$$i_{D_{av}} = 977 - 140 = 837 \mu\text{A}$$

$$\text{and } i_{B_{av}} = 101(837 \times 10^{-6}) = 84.5 \text{ mA}$$

Thus

$$t_{PLH} = 2 \times 10^{-12} \times 2.5 / 84.5 \times 10^{-3} = 59.2 \text{ ps}$$

$$\text{Thus } t_p = (59.2 + 108.7)/2 = 84 \text{ ps}$$

### 15.45


For the BiCMOS NAND of Fig 14.39 to have a dynamic response somewhat like that of the inverter of Fig. 14.37e :

$$(W/L)_{PA} = (W/L)_{PB} = (W/L)_P$$

$$\text{and } (W/L)_{NA} = (W/L)_{NB} = 2(W/L)_N$$

### 15.46

A BiCMOS 2-input NOR is as shown:

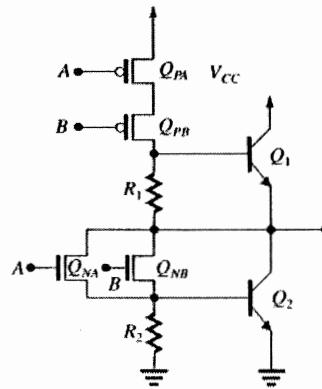


In terms of the basic matched inverter :

$$(W/L)_{PA} = (W/L)_{PB} = 2(W/L)_P$$

$$(W/L)_{NA} = (W/L)_{NB} = (W/L)_N$$

where  $(W/L)_P$  and  $(W/L)_N$  characterize the inverter.

16.1

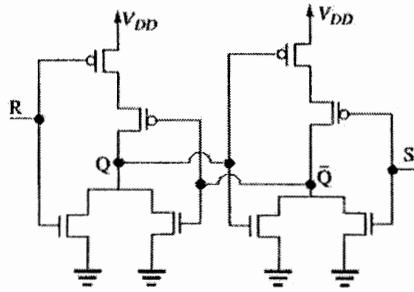

16.2

$$\begin{aligned} \mu_n \frac{1}{2} \left( \frac{W}{L} \right)_5 & \left[ (V_{DD} - V_{tp}) \frac{V_{DD}}{2} - \frac{1}{2} \left( \frac{V_{DD}}{2} \right)^2 \right] \\ & = \mu_p \left( \frac{\mu_n}{\mu_p} \right) \left( \frac{W}{L} \right)_5 \left[ (V_{DD} - V_{tp}) \left( \frac{V_{DD}}{2} \right) - \frac{1}{2} \left( \frac{V_{DD}}{2} \right)^2 \right] \end{aligned}$$

Assuming  $V_m = V_{tp}$  we have:

$$\begin{aligned} \mu_n \frac{1}{2} \left( \frac{W}{L} \right)_5 & = \mu_p \left( \frac{\mu_n}{\mu_p} \right) \left( \frac{W}{L} \right)_5 \Rightarrow \frac{1}{2} \left( \frac{W}{L} \right)_5 = \left( \frac{W}{L} \right)_5 \\ & \Rightarrow \left( \frac{W}{L} \right)_5 = 2 \left( \frac{W}{L} \right)_5 \end{aligned}$$

If the flip-flop is fabricated in a 0.13- $\mu\text{m}$  process, we have:

$$\begin{aligned} \left( \frac{W}{L} \right)_1 & = \left( \frac{W}{L} \right)_3 = 1 \Rightarrow W_1 = W_3 = 1 \times L_{\min} \\ & = 0.13 \mu\text{m} \\ \left( \frac{W}{L} \right)_2 & = \left( \frac{W}{L} \right)_4 = \left( \frac{\mu_n}{\mu_p} \right) \left( \frac{W}{L} \right)_5 = 4 \times 1 = 4 \\ & \Rightarrow W_2 = W_4 = 4 \times 0.13 = 0.52 \mu\text{m} \\ \left( \frac{W}{L} \right)_5 & = \left( \frac{W}{L} \right)_6 = \left( \frac{W}{L} \right)_7 = \left( \frac{W}{L} \right)_8 = 2 \left( \frac{W}{L} \right)_5 \\ & = 2 \Rightarrow W_5 = W_6 = W_7 = W_8 = 2 \mu\text{m} \end{aligned}$$

16.3 output  $v_Q = \frac{V_{DD}}{2}$ , and

assuming a single equivalent transistor for  $Q_5$  and  $Q_6$  where  $\left( \frac{W}{L} \right)_{eq} = \frac{1}{2} \left( \frac{W}{L} \right)_5 = \frac{1}{2} \left( \frac{W}{L} \right)_6$

Use eq. 13.100.

For equivalent  $n$  transistor

$$\begin{aligned} \Rightarrow V_{GS} - V_t & = 1.8 - 0.5 = 1.3 > V_{DS_{satn}} \\ & = 0.6\text{V} \end{aligned}$$

For  $P_{transistor}$

$$\begin{aligned} \Rightarrow |V_{GS}| - |V_t| & = 1.8 - 0.5 = 1.3 > V_{DS_{satp}} \\ & = 1\text{V} \end{aligned}$$

Both operating in velocity saturation :

$$\begin{aligned} & \mu_n C_{ox} \left( \frac{W}{L} \right)_{eq} V_{DS_{satn}} \left( V_{GS} - V_m - \frac{1}{2} V_{DS_{satn}} \right) \\ & \times (1 + \lambda_n V_{DS}) = \mu_p C_{ox} \left( \frac{W}{L} \right)_2 |V_{DS_{satp}}| \\ & \times \left( |V_{GS}| - |V_{tp}| - \frac{1}{2} |V_{DS_{satp}}| \right) (1 + |\lambda_p| V_{DS}) \\ & 300 \times 10^{-6} \times \left( \frac{W}{L} \right)_{eq} \times 0.6 \left( 1.8 - 0.5 - \frac{1}{2} \times 0.6 \right) \\ & \times \left( 1 + .1 \times \frac{1.8}{2} \right) = 75 \times 10^{-6} \left( \frac{1.08}{0.18} \right) \\ & \times 1 \left( 1.8 - 0.5 - \frac{1}{2} \times 1 \right) \left( 1 + .1 \times \left( \frac{1.8}{2} \right) \right) \\ & \left( \frac{W}{L} \right)_{eq} = 2 \\ & \left( \frac{W}{L} \right)_{eq} = \frac{1}{2} \left( \frac{W}{L} \right)_5 = 2 \\ & \therefore \left( \frac{W}{L} \right)_5 = 4, \\ & \left( \frac{W}{L} \right)_6 = \left( \frac{W}{L} \right)_5 = 4 = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}} \end{aligned}$$

This value is greater thus requiring 33% more width area of both  $n$  transistors as a minimum.

16.4

$$V_m = \frac{r(V_{DD} - |V_{tp}|) + V_m}{r + 1} \text{ where}$$

$$r = \sqrt{\frac{\mu_p W_p}{\mu_n W_n}}$$

$$W_p = W_n = 0.27 \mu\text{m} \text{ and } \mu_n = 4\mu_p$$

$$\therefore r = \sqrt{\frac{1}{4}} = 0.5$$

$$V_m = \frac{0.5(1.8 - 0.5) + 1}{0.5 + 1} = 1.1\text{V}$$

(threshold voltage)

Assuming

$$\left( \frac{W}{L} \right)_5 = \left( \frac{W}{L} \right)_6 = \left( \frac{W}{L} \right)_7 = \left( \frac{W}{L} \right)_8 \text{ and } Q_5, Q_6$$

have an equivalent single transistor

$$\left( \frac{W}{L} \right)_{eq} = \frac{1}{2} \left( \frac{W}{L} \right)_5 = \frac{1}{2} \left( \frac{W}{L} \right)_6 \text{, the equivalent } n$$

transistor and  $Q_2$  are in triode region with the same current flowing through them.

$$300\mu_m \times \left(\frac{W}{L}\right)_5 \left[ (1.8 - 0.5) \frac{1.8}{2} - \frac{1}{2} \left(\frac{1.8}{2}\right)^2 \right] \\ = 75 \times 10^{-6} \times \left(\frac{0.27}{0.18}\right) \left[ (1.8 - 0.5) \frac{1.8}{2} - \frac{1}{2} \left(\frac{1.8}{2}\right)^2 \right]$$

$$\left(\frac{W}{L}\right)_5 = 0.375 \Rightarrow \left(\frac{W}{L}\right)_5 = 1$$


(cannot have less than minimum)

$$\left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_8 = \frac{0.18 \text{ } \mu\text{m}}{0.18 \text{ } \mu\text{m}}$$

## 16.5

$Q_2$  is conducting and  $Q_5$  is conducting and operating in triode region:

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_5 \left[ (V_{DD} - V_{in}) \frac{V_{DD}}{2} - \frac{1}{2} \left(\frac{V_{DD}}{2}\right)^2 \right] \\ = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ (V_{DD} - |V_{tp}|) \frac{V_{DD}}{2} - \frac{1}{2} \left(\frac{V_{DD}}{2}\right)^2 \right]$$

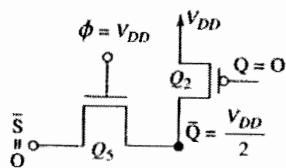

$$\mu_n \left(\frac{W}{L}\right)_5 = \mu_p \left(\frac{W}{L}\right)_2,$$

$$\therefore \left(\frac{W}{L}\right)_5 = \frac{\mu_p}{\mu_n} \left(\frac{W}{L}\right)_2$$

## 16.6

Note that the devices are matched, with

a)  $K_n = K_p = 20(12/6) = 40 \text{ } \mu\text{A/V}^2$ , and

$|V_t| = 1 \text{ V}$ .

For  $V_I = 2.5 \text{ V}$

$$V_o = 2.5 \text{ V}$$

For  $V_I = 0 \text{ V}, 5 \text{ V}$ : one device is on, one off;

$$V_o = 5 \text{ V}, 0 \text{ V}$$

For  $V_I = 1 \text{ V}, 4 \text{ V}$ : one on, one off;

$$V_o = 5 \text{ V}, 0 \text{ V}$$

For  $V_I = 1.5 \text{ V}, 3.5 \text{ V}$ : one in saturation, one in triode mode.

$$i_D = \frac{1}{2}(40)(1.5 - 1)^2 = 40[(5 - 1.5 - 1)v_o - v_o^2/2]$$

$$\text{Thus } 0.125 = 2.5v_o - v_o^2/2$$

$$\text{or } v_o^2 - 5v_o + 0.25 = 0$$

$$\text{and } V_o = -5 \pm \sqrt{5^2 - 4(0.25)} / 2$$

$$= (5 \pm 4.8484) / 2 = 0.05 \text{ V}$$

$$\text{Thus } v_o = 0.05 \text{ V or } 4.95 \text{ V}$$

$$\text{For } v_I = 2.0 \text{ V, } 3.0 \text{ V:}$$

$$1/2(2-1)^2 = (5-2-1)v_o - v_o^2/2$$

$$\text{or } (2-1)^2 = 2 \times 2v_o - v_o^2$$

$$\text{and } v_o^2 - 4v_o + 1 = 0$$

$$\text{Whence } v_o = (- -4 \pm \sqrt{4^2 - 41.1}) / 2$$

$$= (4 \pm 3.464) / 2 = 0.27 \text{ V}$$

$$\text{Thus } v_o = 0.27 \text{ V or } 4.73 \text{ V}$$


$$\text{For } v_I = 2.25 \text{ V or } 2.75 \text{ V:}$$

$$(2.25 - 1)^2 = 2(5 - 2.25 - 1)v_o - v_o^2$$

$$1.5625 = 3.5 - v_o - v_o^2$$

$$v_o^2 - 3.5v_o + 1.5625 = 0$$

b)

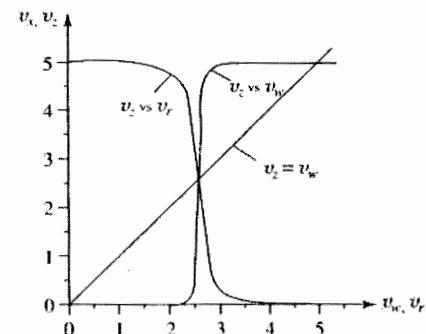

## 16.7

Whence

$$\begin{aligned} v_o &= (-3.5 \pm \sqrt{3.5^2 - 4(1.5625)})/2 \\ &= (3.5 \pm 2.45)/2 = 0.525 \end{aligned}$$

Thus  $v_o = 0.525$  V or 4.475 V

For  $v_i = 2.5$  V,  $v_o = 3.5$  V by symmetry

Now, having plotted  $v_z$  versus  $v_i$  (or  $v_i$  versus  $v_w$ ) use the graph to find  $v_z$  versus  $v_w$ .

Work backwards: first  $v_z$ , then  $v_y = v_x$  than  $v_w$ .

For  $v_z = 2.5$  V,  $v_y = v_x = v_w = 2.5$  V

For  $v_z = 4.4$  V,  $v_y = 2.25$  V;

For  $v_z = 4.5$  V  $v_y = 1.50$  V; for

$v_x = 1.50$  V  $v_w = 2.65$  V

(c)  $v_z = v_w$  line at:

point A: (0, 0)

point B: (2.5, 2.5)

point C: (5, 5)

At point B, the current flow in each inverter is:

$$i_D = \frac{1}{2}(40)(2.5 - 1)^3 = 45 \mu\text{A/V}$$

where for each transistor,  $r_o = 100/(45 \times 10^{-6})$

$$= 2.22 \text{ M}\Omega$$

$$\text{and } g_m = 2\left(\frac{1}{2}\right)40(2.5 - 1) = 60 \mu\text{A/V}$$

Thus for each inverter operating at (2.5, 2.5), the voltage gain is  $-(g_m + g_m)(r_o \parallel r_o)$

$$= -g_m V_o = -60 \times 10^{-6} \times 2.22 \times 10^6 = 133 \text{ V/V}$$

Thus an estimate of the slope of the  $v_z$

versus  $v_w$  curve at B is  $(13.3) = 17.7 \times 10^3 \text{ V/V}$

Correspondingly a lower bound on the width of the transition region is  $(5 - 0)/(17.7 \times 10^3)$ , or 0.28 mV, that is  $\pm 0.14$  mV around 2.5 V.

The approximate transfer characteristic of each inverter passes through points: (0.5), (2.0, 4.4), (2.42, 0.4), (5, 0).

For the linear centre segment between (2.0, 4.4), (2.42, 0.4)

an equation is  $v_o = a - b v_i$

Here:  $4.4 = a - 2.0b$ , and

$$0.4 = a - 2.42b$$

$$\text{Subtract: } 4.4 = a - 2.0b \rightarrow b = \frac{10}{12} = \frac{5}{6}$$

$$\text{Now, } 4.4 = a - 2(10/6) \rightarrow a = 4.4 + 20/6 = 24.6$$

Check:  $0.4 = 24.6 - 2(10/6) \checkmark$

Thus the middle part of the characteristic is

$$v_o = 24.6 - 10v_i$$

For each device,  $v_{o1} = v_{z1} = v$ , when

$$v = 24.6 - 10v \text{ or } 11v = 24.6, \text{ or } v = \frac{24.6}{11} \text{ V}$$

where the gain is  $\Delta v_o / \Delta v_z = -b = -10 \text{ V/V}$

Thus point B on the open-loop characteristic is


$$v_{z1} = v_{z2} = \frac{24.6}{11} = 2.236 \text{ V}, \text{ where the loop gain can be approximated to be at least } (-10)^2 = 100 \text{ V/V}$$

The open-loop characteristic reaches  $v_o = 5$  V,

$$\text{where } v_{z1} = 2.236 + (5 - 2.236)/100 = 2.264 \text{ V}$$

and it reaches 0 V where
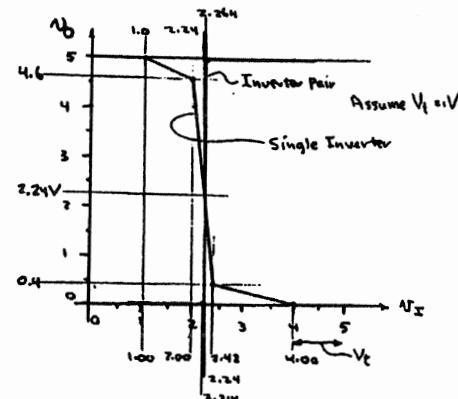
$$v_{z1} = 2.236 - 2.236/100 = 2.244 \text{ V}$$



### 16.8

(a)  $Q_5, Q_6$  are conducting for  $D = 1$  or 0

$$\bar{Q} = \bar{D} \text{ and } Q = D$$

If  $D = 1$  then  $\bar{Q} = 0$  and  $Q = 1$

$Q_1$  conducts

If  $D = 0$  then  $\bar{Q} = 1$  and  $Q = 0$

$Q_4$  conducts

(b) If  $D = 1$  then  $\bar{Q} = 0$  and  $Q = 1$

when  $\phi$  goes low,  $(Q_1, Q_2)$  conduct ( $Q_3$  also conducts)

The value at the gate of  $G_2$  stays high (through  $Q_1, Q_2$ )  $\bar{Q} = 0$  and  $Q = 1$  (value is "latched")

(c) If  $D = 0$  then  $\bar{Q} = 1$  and  $Q = 0$

when  $\phi$  goes low,  $(Q_3, Q_4)$  conduct so gate value at  $G_2$  is low (through  $Q_3, Q_4$ ) to keep  $\bar{Q} = 1$  and  $Q = 0$

(d) No. The operation connects either  $V_{DD}$  or ground directly to gate of  $G_2$  which maintains values at  $\bar{Q}$  and  $Q$ .

### 16.9

A 1 Mb array requires  $n$  address bits where  $2^n = 10^6$ , or  $n \log_{10} 2 = 6$ ,  $n = 6/\log_{10} 2 = 19.93$ . Thus 20 bits are needed to address every cell.

For 16-bit words,  $2^4 = 16$  and 4 bits are not needed. Thus  $20 - 4 = 16$  bits of address are sufficient.

Check:  $m = \log_{10}(10^6/16)/\log_{10}(2) = 4.79/0.301 = 15.93$

Use 16V

Note: A "1 Mb array" actually holds  $2^{10} = 1024^2 = 1048576$  cells.

### 16.10

The cell area is  $10^3 \times 0.38 \times 10^{-6} \times 0.76 \times 10^{-6}$   
 $= 0.289 \times 10^{-12} \text{ m}^2$

The chip area is  $19 \times 10^{-3} \times 38 \times 10^{-3}$   
 $= 0.722 \times 10^{-5} \text{ m}^2$

Thus the peripheral circuits and interconnect occupy  $(0.722 - 0.289)10^{-3} = 0.433 \text{ mm}^2$   
or  $(\frac{433}{722}) \times 100 = 60\%$  of the chip area.

### 16.11

$$\left(\frac{W}{L}\right)_5 \leq \frac{1}{\left(1 - \frac{0.5}{1.8 - 0.5}\right)^2} - 1 = 1.64$$

minimum area when  $\left(\frac{W}{L}\right)_5 = 1$  so

$W_5 = 0.18 \mu\text{m}$   $Q_5$  is saturated and  $Q_1$  is in triode. Currents are equal:

$$\frac{1}{2} \mu_n C_{ox} (1)(1.8 - 0.5 - 0.2)^2 = \mu_n C_{ox} \left(\frac{W_1}{0.18 \mu}\right)$$

$$\left[ (1.8 - 0.5)0.2 - \frac{1}{2}(0.2)^2 \right]$$

Solving for  $W_1 = 0.45 \mu\text{m}$

Check condition above :

$$\left(\frac{1}{\frac{0.45}{0.18} \mu}\right) = 0.4 < 1.64$$

### 16.12

$$\left(\frac{W}{L}\right)_a \leq \frac{1}{\left(1 - \frac{V_m}{V_{DD} - V_m}\right)^2} - 1$$

$$= \frac{1}{\left(1 - \frac{0.5}{2.5 - 0.5}\right)^2} - 1 = 0.78$$

$$\left(\frac{W}{L}\right)_a \leq 0.78 \times 1.5 \text{ or } \left(\frac{W}{L}\right)_a \leq 1.17$$

### 16.13

(a) 0.25  $\mu\text{m}$ :  $V_{DD} = 2.5 \text{ V}$  and  $V_t = 0.5 \text{ V}$

$$A: \left(\frac{V_Q = V_t}{V_{DD} - V_m}\right) = \frac{0.5}{2.5 - 0.5} = \frac{0.5}{2} = 0.25$$

$$\Rightarrow \left(\frac{W}{L}\right)_5 \approx 0.8$$

$$\left(\frac{W}{L}\right)_1$$

$$\Rightarrow \frac{(W/L)_5}{(W/L)_1} \approx 0.8$$


(b) 0.18  $\mu\text{m}$ :  $V_{DD} = 1.8 \text{ V}$  and  $V_t = 0.5 \text{ V}$

$$B: \left(\frac{0.5}{1.8 - 0.5}\right) = 0.385 \Rightarrow \left(\frac{W}{L}\right)_5 \approx 1.7$$

$$\Rightarrow \frac{(W/L)_5}{(W/L)_1} = 1.64$$

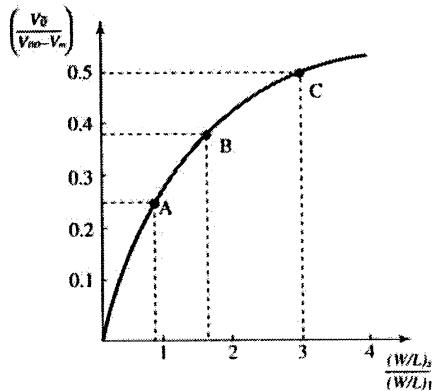(c)  $0.13 \mu\text{m}$ :  $V_{DD} = 1.2 \text{ V}$  and  $V_t = 0.4 \text{ V}$

$$\text{C: } \left( \frac{W}{L} \right)_5 = 0.5$$



$$\begin{aligned} \left( \frac{W}{L} \right)_5 &= 3 \\ \left( \frac{W}{L} \right)_1 & \end{aligned}$$

$$\left( \frac{W}{L} \right)_5 / \left( \frac{W}{L} \right)_1 = 3$$

#### 16.14

When  $V_Q \leq V_t = 0.5 \text{ V}$ :

$Q_5$ :  $V_{GS} - V_t = 1.8 - 0.5 = 1.3 > 0.6 \text{ V}$  and  
 $V_{DS} = 1.8 - 0.5 > V_{DS_{sat}} = 0.6$

$Q_1$ :  $V_{GS} - V_t = 1.8 - 0.5 = 1.3 > 0.6 \text{ V}$  and  
 $V_{DS} = 0.5 - 0 < V_{DS_{sat}} = 0.6$

(not in velocity saturation)

Only  $Q_5$  is in velocity saturation.

using Eq. 13.100:

$$\begin{aligned} i_D &= \mu_n C_{ov} \left( \frac{W}{L} \right)_5 V_{DS_{sat}} \left( V_{GS} - V_t - \frac{1}{2} V_{DS_{sat}} \right) \\ &\times (1 + \lambda V_{DS}) \end{aligned}$$

Neglecting  $\lambda$  ( $\lambda = 0$ )

$$\begin{aligned} \mu_n C_{ov} \left( \frac{W}{L} \right)_5 0.6 &\left( 1.8 - 0.5 - 0.5 - \frac{1}{2}(0.6) \right) \\ &= \mu_n C_{ov} \left( \frac{W}{L} \right)_1 0.6 \left[ (1.8 - 0.5)0.5 - \frac{1}{2}(0.5)^2 \right] \end{aligned}$$

$$\begin{aligned} \left( \frac{W}{L} \right)_5 &= 1.75 \\ \left( \frac{W}{L} \right)_1 & \end{aligned}$$

without velocity saturation: (Eq. 15.4)

$$\begin{aligned} \left( \frac{W}{L} \right)_5 &\approx \frac{1}{\left( 1 - \frac{0.5}{1.8 - 0.5} \right)^2} - 1 \approx 1.64 \\ \left( \frac{W}{L} \right)_1 & \end{aligned}$$

#### 16.15

With body effect considerations:

$$V_t = V_{in} + r[\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}]$$

$$V_t = 0.5 + 0.3[\sqrt{0.8 + 0.5} - \sqrt{0.8}] = 0.574 \text{ V}$$

$$\left( \frac{W}{L} \right)_5 \leq \left[ \frac{1}{\left( 1 - \frac{0.574}{1.8 - 0.574} \right)^2} - 1 \right] = 2.54$$

without body effect:  $V_{in} = V_{io}$

$$\left( \frac{W}{L} \right)_5 \leq \left[ \frac{1}{\left( 1 - \frac{0.5}{1.8 - 0.5} \right)^2} - 1 \right] = 1.64$$

#### 16.16

$\left( \frac{W}{L} \right)_5$  for body effect can have a large maximum ratio.

$$\left( \frac{W}{L} \right)_5 \leq \left[ \frac{1}{\left( 1 - \frac{0.4}{1.2 - 0.4} \right)^2} - 1 \right] = 3$$

For  $V_Q$  kept below  $V_{in}$ , Eq. 15.10 becomes

$$\left( 1 - \frac{V_{in}}{V_{DD} - V_{in}} \right)^2 = 1 - \left( \frac{\mu_p}{\mu_n} \right) \left( \frac{W}{L} \right)_4 \left( \frac{W}{L} \right)_6$$

$$\left( \frac{W}{L} \right)_4 = \frac{\left( 1 - \frac{V_{in}}{V_{DD} - V_{in}} \right)^2}{(\mu_p / \mu_n)}$$

$$\text{Assuming } \frac{\mu_n}{\mu_p} = 4$$

$$\left( \frac{W}{L} \right)_4 = 3$$

$$\Rightarrow \Delta t = \frac{C_B \Delta V}{I_5} \text{ where } I_5 \text{ is obtained from}$$

$$\begin{aligned} I_5 &= \frac{1}{2} \times 430 \times 10^{-6} \times 1 \times (1.2 - 0.4 - 0.4)^2 \\ &= 34.4 \mu\text{A} \end{aligned}$$

$$\Delta t = \frac{C_B \Delta V}{I_5} = \frac{2 \times 10^{-12} \times 0.2}{34.4 \times 10^{-6}} = 11.6 \text{ ns.}$$

$$(c) \left( \frac{W}{L} \right) = 3$$

(Eq. 15.1):

$$I_5 = \frac{1}{2} \times 430 \times 10^{-6} \times 3(1.2 - 0.4 - 0.4)^2$$


$$= 103 \mu\text{A}$$

$$\Delta t = \frac{C_B \Delta V}{I_5} = \frac{(2 \times 10^{-12} \times 0.2)}{103 \times 10^{-6}} = 3.9 \text{ ns.}$$
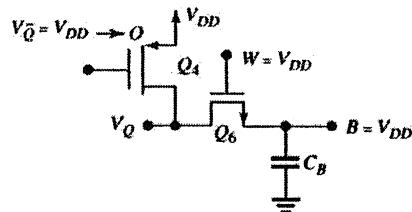
### 16.17

Storing a 0:  $V_Q = 0$ ,  $V_{\bar{Q}} = V_{DD}$

To write a 1  $\rightarrow$  B line raised to  $V_{DD}$ ,  $\bar{B}$  line lowered, and word line raised to  $V_{DD}$ .  $V_Q$  changes to  $V_{DD}$  and  $V_{\bar{Q}} = 0$ . Relevant transistors:



$Q_4$  in saturation and  $Q_6$  in triode, which is the same as the text for writing a 0.

### 16.18

$$\left(\frac{W}{L}\right)_p \leq \left(\frac{W}{L}\right)_n \times 4 \times \left[1 - \left(1 - \frac{0.5}{2.5 - 0.5}\right)^2\right]$$

$$\left(\frac{W}{L}\right)_p \leq 1.75 \left(\frac{W}{L}\right)_n$$

### 16.19

For a 1Mb square array, there are 1024 rows and 1024 columns.

Thus the bit-line capacitance is  $10^{15} (1024 \times 1 + 12)$  or 1.036 pF

When storing a '1', the voltage on  $C_S$  is  $(V_{DD} - V_t)$  or  $(5 - 1.5) = 3.5V$ . With precharge to  $V_{DD} = 2.5V$ , the change in voltage on  $C_S = 3.5 - 2.5 = 1.0V$ ,

For  $C_S = 25 fF$ , the bit-line voltage resulting is  $25 / (25 + 1024) \times 1 = \underline{23.6 mV}$

When storing a '0', the voltage on  $C_S$  is 0V and the change is  $2.5 - 0 = 2.5V$  with a resulting bit-line signal of  $25 / (25 + 1024) \times 2.5 = \underline{50.9 mV}$

### 16.20

$$\text{Let } \left(\frac{W}{L}\right)_S = \frac{0.13 \mu\text{m}}{0.13 \mu\text{m}}$$

$$\text{Let } V_{\bar{Q}} = V_m = 0.4V.$$

$$I_2 = I_1$$

$$\frac{1}{2} \mu_n C_{ox} \times 1 \times (1.2 - 0.4 - 0.4)^2$$

$$= \mu_n C_{ox} \times \left(\frac{W}{L}\right)_1 \times \left[(1.2 - 0.4)0.4 - \frac{1}{2}(0.4)^2\right]$$

Solving for  $\left(\frac{W}{L}\right)_1 = .33$  so choose

$$\left(\frac{W}{L}\right)_1 = \frac{0.13 \mu\text{m}}{0.13 \mu\text{m}} = 1$$

Checking

$$1 \leq \left[ \frac{1}{\left(1 - \frac{0.4}{1.2 - 0.4}\right)^2} - 1 \right] = 3$$

$$\text{Let } \left(\frac{W}{L}\right)_4 = \frac{0.13 \mu\text{m}}{0.13 \mu\text{m}}$$

$$\text{Let } V_Q = V_m = 0.4V. \\ : I_4 = I_6$$

$$\frac{1}{2} \mu_p C_{ox} \times 1 \times (1.2 - 0.4)^2 = \mu_p C_{ox} \times \left(\frac{W}{L}\right)_6 \\ \times \left[(1.2 - 0.4)0.4 - \frac{1}{2}(0.4)^2\right]$$

$$\left(\frac{W}{L}\right)_6 = 1.33 \therefore \left(\frac{W}{L}\right)_6 = 2 = \frac{0.26 \mu\text{m}}{0.13 \mu\text{m}}.$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \frac{0.13 \mu\text{m}}{0.13 \mu\text{m}}$$

Checking

$$\frac{\left(\frac{W}{L}\right)_p}{\left(\frac{W}{L}\right)_n} \leq \left(\frac{\mu_n}{\mu_p}\right) \left[ 1 \left(1 - \frac{V_m}{V_{DD} - V_m}\right)^2 \right]$$

$$\text{(Assume } \left(\frac{\mu_n}{\mu_p}\right) \approx 4 \text{)}$$

$$\frac{1}{2} \leq 4 \left[ 1 - \left(1 - \frac{0.4}{1.2 - 0.4}\right)^2 \right] = 3$$

### 16.21

If the memory array has  $n$  columns, it has  $2n$  rows and  $2n^2$  cells

Refresh time is

$$2n (30) 10^{-9} \text{ s} = (1.00 - 0.98) \text{ s} \times 10^{-3} \text{ s}$$

Whence

$$n = 0.02 \times 8 \times 10^{-3} / 40 \times 10^{-9} = 4000$$

The corresponding memory capacity is

$$2n^2 = 2(4000)^2 \text{ or } 32 \text{ M bits}$$

### 16.22

For leakage current  $I$ , the voltage change on C in time  $T$  is  $V = IT/C$

Correspondingly,  $I = I \times 10^{-3} / 20 \times 10^{-15}$ , and the maximum leakage is  $I = 20 \times 10^{15} / 10 \times 10^{-3} = 2 \mu\text{A}$

### 16.23

For leakage current  $I$ , the voltage change on c in time  $T$  is  $V = \frac{IT}{C}$

Hence,

$$0.2 \text{ V} = \frac{I \times 10^{-3} \times 10}{20 \times 10^{-15}} \Rightarrow I = 0.4 \times 10^{-12}$$

= 0.4 pA is the maximum leakage current.

### 16.24

For the bit-line output to reach  $0.9 V_{dd} = 2.7 \text{ V}$  from  $V_{dd}/2 = 1.5 \text{ V}$  in 2ns for an initial bit-line signal at  $0.1/2 = 0.05 \text{ V}$ :

signal of  $0.1/2 = 0.05 \text{ V}$ :

$$2.7 = 1.5 + 0.05e^{2j}$$

whence  $2j = \ln [(2.7 - 1.5)/0.05] = 3.178$

and  $j = 2/3.178 = 0.629 \text{ ns}$

Thus  $C/G_n = 0.629 \times 10^{-9}$ , and  $G_n = 1 \times 10^{-12} / (0.629 \times 10)$

= 1.589 mA/V

For matched inverters  $g_m = g_{op} = G_n/2 = 1.589/2 = 0.795 \text{ mA/V}$

Now  $g_n = k'(WL)(v_{dd} - V_i)$

and  $0.795 \times 10^{-3} = 100 \times 10^{-6} (W/L)_n (3.0/2 - 0.8)$

$$\begin{aligned} \text{Thus } (W/L)_n &= 0.795 \times 10^{-3} / (100 \times 10^{-6}) / 0.7 \\ &= 11.36 \end{aligned}$$

Now, for devices assumed to have length  $L \mu\text{m}$

(or, alternatively, for each micron of device length)  $W_v = 11.36 \mu\text{m}$  and  $W_p = 3(11.36) = 34.1 \mu\text{m}$

Now, for a differential input signal of 0.2V (and

0.1V on each bit-line), the response time is  $t_r$ ,

where  $2.7 = 1.5 + 0.1 e^{2j \Delta v}$  whence  $\Delta v = 0.629 \text{ ln}(2.7 - 1.5) / 0.1 = 1.56 \text{ ns}$

### 16.25

Note that for the inverters

$$k_s = k_n (W/L)_n = 100(6/1.5) = 400 \mu\text{A/V}^2$$

$$k_p = k_p (W/L)_p = (100/2.5)(15/1.5) = 400 \mu\text{A/V}^2$$

Thus we see that the inverters are matched.

$$\text{Generally, } i_o = 1/2 k_s (v_{dd} - V_i)^2 \text{ and } g_m = 2i_o / 3V_{dd} = k_s(v_{dd} - V_i)$$

$$\text{Now, at } v_{dd} = v_i = V_{dd}/2 = 3.3/2 = 1.65 \text{ V.}$$

$$g_m = 400 (1.65 - 0.8) = 340 \mu\text{A/V}$$

$$\text{Thus } G_n = g_m + g_{op} = (340) = 680 \mu\text{A/V}$$

For a bit-line capacitance of 0.8 pF  $j = C/G_n$

$$\text{or } j = 0.8 \times 10^{-12} / 680 \times 10^{-6} = 1.176 \text{ ns}$$

Now, for 0.9  $V_{dd}$  reached in 2ns, for a signal  $\Delta v$ ,

$$0.9(3.3) = 1.65 + \Delta v e^{2j \Delta v}$$

$$\text{or } \Delta v = (2.97 - 1.65) / 5.478 = 0.241 \text{ V}$$

Thus the initial voltage between B lines must be

$$2(0.241) = 0.482 \text{ V}$$

If an additional 1ns is allowed :  $t = 2+1 = 3 \text{ ns}$  and  $\Delta v = (2.97 - 1.65) / e^{0.116} = 0.103 \text{ V}$  allowing a signal to be used of  $2(0.103) = 0.206 \text{ V}$

Now, with the original bit-line signal of 0.241 V, and a delay of 3 ns:

$$2.97 = 1.65 + 0.241 e^{2j}$$

$$\text{and } e^{2j} = (2.97 - 1.65) / 0.241 = 5.477$$

$$3j = \ln(5.477) = 1.7006$$

$$\text{whence } j = 3/1.7006 = 1.764 \text{ ns}$$

$$\text{Thus } C = G_n j = 680 \times 10^{-6} \times 1.764 \times 10^{-9} = 1.20 \text{ pF}$$

This is an increase (from 0.8 pF) of  $\left(\frac{1.2 - 0.8}{0.8}\right)$

$100 \times 50\%$

For the longer line, the initial delay to establish a suitable signal becomes 150% of 5ns = 7.5ns

### 16.26

(a) For an initial difference between bit lines of  $\Delta V$ , each bit-line signal is  $\Delta V/2$ .

for the rising line:  $v_B = \frac{V_{DD}}{2} + \frac{\Delta V}{2} e^{\frac{t}{(C_B/G_m)}}$

$$e^{\frac{t}{(C_B/G_m)}} = \frac{2}{\Delta V} \cdot (0.9 - 0.5)V_{DD} = \frac{0.8V_{DD}}{\Delta V}$$

Taking the natural log of both sides

$$\ln e^{\frac{t}{(C_B/G_m)}} = \ln\left(\frac{0.8V_{DD}}{\Delta V}\right)$$

$$t_d = \left(\frac{C_B}{G_m}\right) \ln\left(\frac{0.8V_{DD}}{\Delta V}\right) \text{ as stated}$$

(b) For reduction of one half the original,  $G_m$  has to be doubled.  $G_m \propto (W/L)$

$G_m$  is doubled by doubling the width of all transistors

(c)  $V_{DD} = 1.8 \text{ V}$ ,  $\Delta V = 0.2 \text{ V}$

original design:

$$t_d = \left(\frac{C_B}{G_m}\right) \ln\left(\frac{0.8(1.8)}{0.2}\right) = 0.9 \left(\frac{C_B}{G_m}\right)$$

Reducing  $\Delta V$  by 4:  $\Delta V = \frac{0.2}{4} = 0.05 \text{ V}$

$$t_d = \left(\frac{C_B}{G_{m2}}\right) \ln\left(\frac{0.8(1.2)}{0.05}\right) = 1.5 \left(\frac{C_B}{G_{m2}}\right)$$

for these to be equal:

$$\frac{0.9}{G_m} = \frac{1.5}{G_{m2}} \text{ and } G_{m2} = \frac{1.5}{0.9} G_m = 1.7 G_m$$

Thus the transistors must be made 70% wider (or increased by a factor of 1.7x)

### 16.27

For the DRAM arrangement, the signal is applied to only one side; Thus in comparison to the SRAM treatment, the applied signal is only half as large.

Now, the specification must be met for either a '0' or a '1' stored. The worst case is a differential signal of 40 mV (corresponding to a single-side signal of 70 mV)

Thus  $2.0 = 20 \times 10^{-3} e^{5/\hat{j}}$ , and  $5 = \hat{j} \ln(2)$

$20 \times 10^{-3}$ , or  $5 = \hat{j} \ln(100) \times 4.605 \hat{j}$ , whence  $\hat{j} = 1.086 \text{ ns}$  (next)

For a 1 pF bit-line capacitance,  $G_n C \hat{j}$  or  $G_n = 1 \times 10^{-12} / 1.086 \times 10^{-9} = 0.921 \text{ mA/V}$ , with  $0.921 = 0.46 \text{ mA/V}$  from each transistor.

Now, for the n-channel device,  $g_n = k'_n (W/L)_n (V_{DS} - V_t)$  or  $0.46 \times 10^{-3} = 100 \times 10^{-4} (W/L)_n (2.5 - 1)$

Thus  $(W/L)_n = (0.46/0.1)/1.5 = 3.07$

For matched inverters,  $(W/L)_p = 2.5(3.07) = 7.68$

When a '1' is read, the response time will be  $t = \hat{j} \ln(2/20 \times 10^{-3}) = 1.086 \ln 100 = 5 \text{ ns}$

(note: this is as designed!)

When a '0' is read,  $t = 1.086 \times 10^{-9} \ln(2/(100/2) \times 10^{-3}) = 4.01 \text{ ns}$

### 16.28

$$\Delta t = \frac{CV_{DD}}{I}$$

$$I = \frac{CV_{DD}}{\Delta t} = \frac{60 \times 10^{-15} \times 1.2}{0.3 \times 10^{-9}} = 240 \mu\text{A}$$

$$P = V_{DD} I = 1.2 \times 240 \mu\text{A} = 288 \mu\text{W}$$

## 16 . 29

Here  $2^x = 512$ ,  $n \log_{10} 512 = \log_{10} 512$ ,  $n = 2.709 / 0.301 = 9.00$

Thus the number of bits is 9

The decoder has 512 output line, one of which is active (high). The NOR away requires true and complement input lines for each bit:  $2 \times 9 = 18$ . Each row uses 9 NMOS for a total of  $9 \times 512 = 4608$  NMOS and 512 PMOS, for a total of 5120 transistors.

## 16 . 30

For a 256 K bit square array, there are  $(256 \times 1024)^n = 512$  rows and columns

Number of column-address bits is  $\log_2 512 = 9$

Two multiplexors are needed, since both true and complement bit lines are required. For each multiplexor, there are 512 output lines.

For each (half) multiplexor, 512 NMOS needed for a total of 1024 NMOS pass gates.

For the 512 output NOR decoder itself,  $512 \times 9 = 4608$  NMOS and 512 PMOS are needed.

The address-bit inverters need 9 NMOS and 9 PMOS. Overall, the need is for  $1024 + 4608 + 9 = 5641$  NMOS and 512 + 9 = 521 PMOS, for a total of 6162 transistors.

## 16 . 31

From the solution above, a square 256 K-bit array has 512 rows and 512 columns for which 9 row and 9 column address bits are needed. Check:  $2^{9+9} = 2^{18} = 262144$

For the tree 9 levels of pass gates are needed.



The total number of pass gates is  $N = 2 + 4 + 8 + 16 + 32 + 64 + 128 + 256 + 512$

See that  $N = 2 + 2(N - 512)$ , or  $N = 2 + 2N - 1024$ , whence  $N = 1022$

Thus a tree column decoder for 9 bits needs 1022 pass transistors

For true and complement bit lines, a total of  $2(1022) = 2044$  pass transistors are needed. Compare this with the number required beyond the input inverters namely  $6162 - 18 = 6144$

## 16 . 32

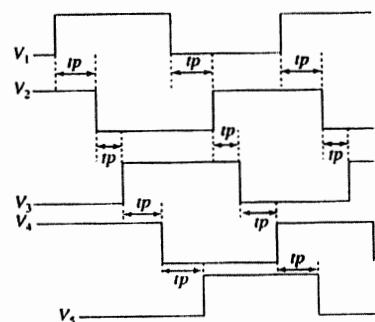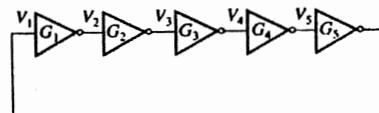

$$t_p = \frac{1}{2}(t_{PLH} + t_{PHL}) = \frac{1}{2}(6n + 4n) = 5 \text{ ns.}$$

$$f = \frac{1}{10t_p} = 20 \text{ MHz}$$

## 16 . 33

$$N = 11$$

$$f = 20 \mu\text{Hz} = \frac{1}{2Nt_p} = \frac{1}{2(11)t_p}$$

$$\therefore t_p = 2.3 \text{ nsec}$$

### 16.34


Note that the output is high if no word is selected. Thus, logically, high must correspond to logic 0 (and no transistor, as noted in the text).

Correspondingly, the words stored in are 0100, 0000, 1000, 1001, 0101, 0001, 0110, and 0010.

### 16.35

Need  $z = x + y$

X	Y	Z
00	00	0000
00	01	0000
00	10	0000
00	11	0000
01	00	0000
01	01	0001
01	10	0010
01	11	0011
10	00	0000
10	01	0010
10	10	0100
10	11	0110
11	00	0000
11	01	0011
11	10	0110
11	11	1001

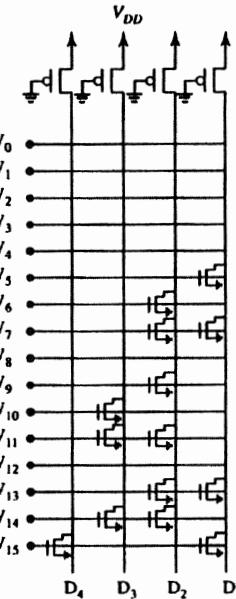

Note that a total of 14NMOS and 4PMOS are used.



### 16.36

(a) For the PMOS, with  $V_B = 2.5 \text{ V}$

$$L_D = (90/3)10^{-6}(12/1.2)[(5-1)2.5 - 2.5^2/2] \\ = 30 \times 10^{-6}(10)(4(2.5) - 2.5^2/2) \\ = 2.0625 \text{ mA}$$

Thus the average charging current is 2.06 mA  
Time for precharge  $t = CV/I$   
whence

$$t = 1 \times 10^{-12}(5-0)/(2.06 \times 10^{-3}) = 2.42 \text{ ns}$$

(b) For the word-line rise,

$$T = RC = 5 \times 10^4 \times 2 \times 10^{-12} = 10 \text{ ns}$$

Here,  $v_w = 5(1 - e^{-t/10})$

Thus the rise time (10% to 90%) is essentially the time  $t$  to 90%, where

$$0.9(5) = 5(1 - e^{-t/10})$$

$$e^{-t/10} = 0.1$$

and  $t = -10 \ln(0.1) = 23 \text{ ns}$

At the end of one time constant,  $T = 1 = 10 \text{ ns}$   
and  $v_s = 5(1 - e^{-10/10}) = 3.16 \text{ V}$

For discharge,

$$\begin{aligned} i_{D_{av}} &= 1/2 k_n' (W/L)_n (v_{ds} - V_t)^2 \\ &= 1/2(90)(3/1.2)(3.16 - 1)^2 = 525 \mu\text{A} \end{aligned}$$

Thus, the bit-line voltage will lower by 1V in  
about  $\Delta t = C \Delta V / i_{D_{av}} = 1 \times 10^{-12}, (\times \dots$   
 $\dots) \times 1 / (525 \times 10^{-6}) = 1.90 \text{ ns}$