




Computer Architecture

Hossein Asadi
Department of Computer Engineering
Sharif University of Technology
asadi@sharif.edu

Today's Topics

- Data Path Design

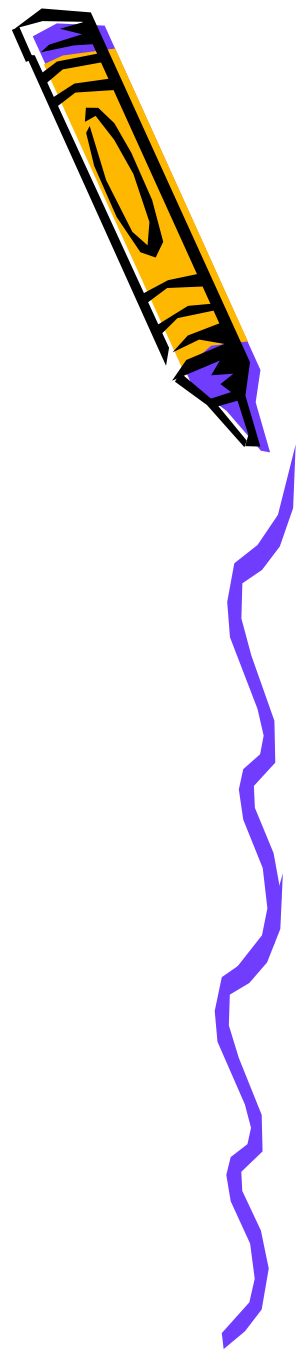

Copyright Notice



- Parts (text & figures) of this lecture adopted from:
 - Computer Organization & Design, The Hardware/Software Interface, 3rd Edition, by D. Patterson and J. Hennessey, MK publishing, 2005.
 - "Intro to Computer Architecture" handouts, by Prof. Hoe, CMU, Spring 2009.
 - "Computer Architecture & Engineering" handouts, by Prof. Kubiawicz, UC Berkeley, Spring 2004.
 - "Intro to Computer Architecture" handouts, by Prof. Hoe, UWisc, Fall 2009.
 - "Computer Arch I" handouts, by Prof. Garzarán, UIUC, Spring 2009.




Datapath






- Datapath?
 - A functional unit used to **operate** on or **hold** data within a processors
- Datapath Elements in MIPS
 - Instruction memory
 - Data memory
 - Register file
 - ALU
 - Adders
- Control Unit
 - Schedule data movements in datapath



Datapath (cont.)

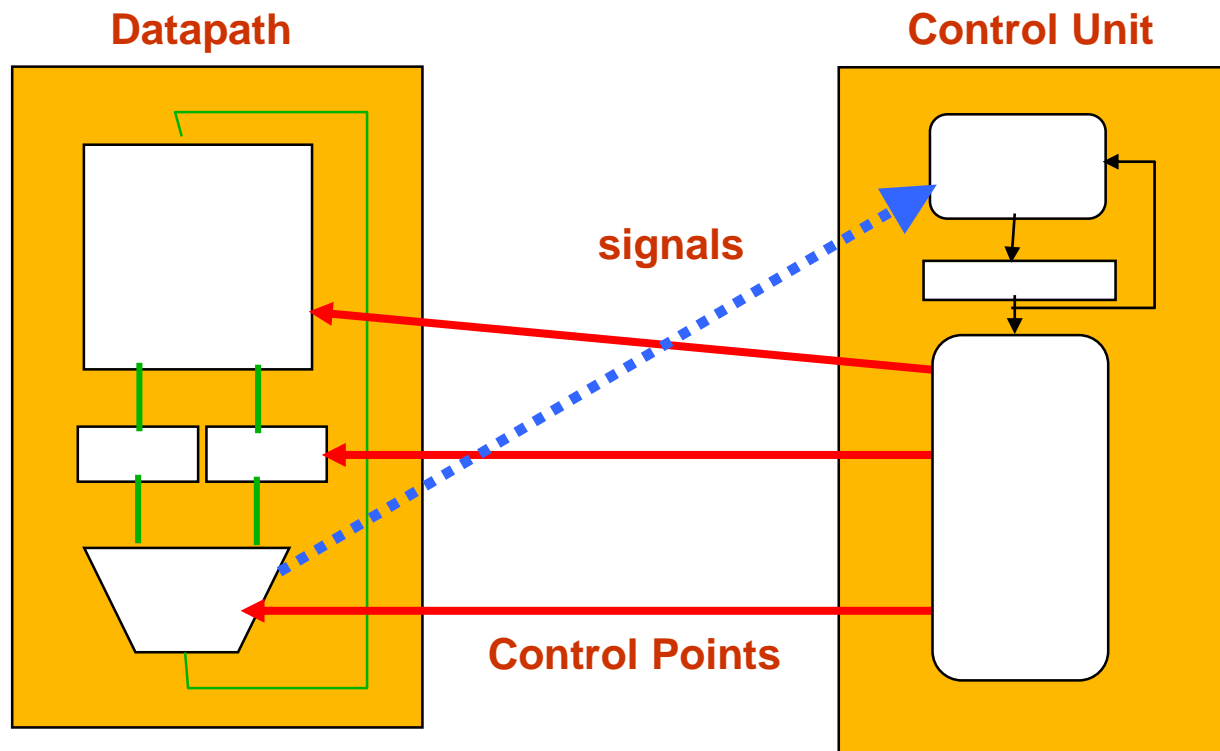


Abstract View of MIPS Implementation

 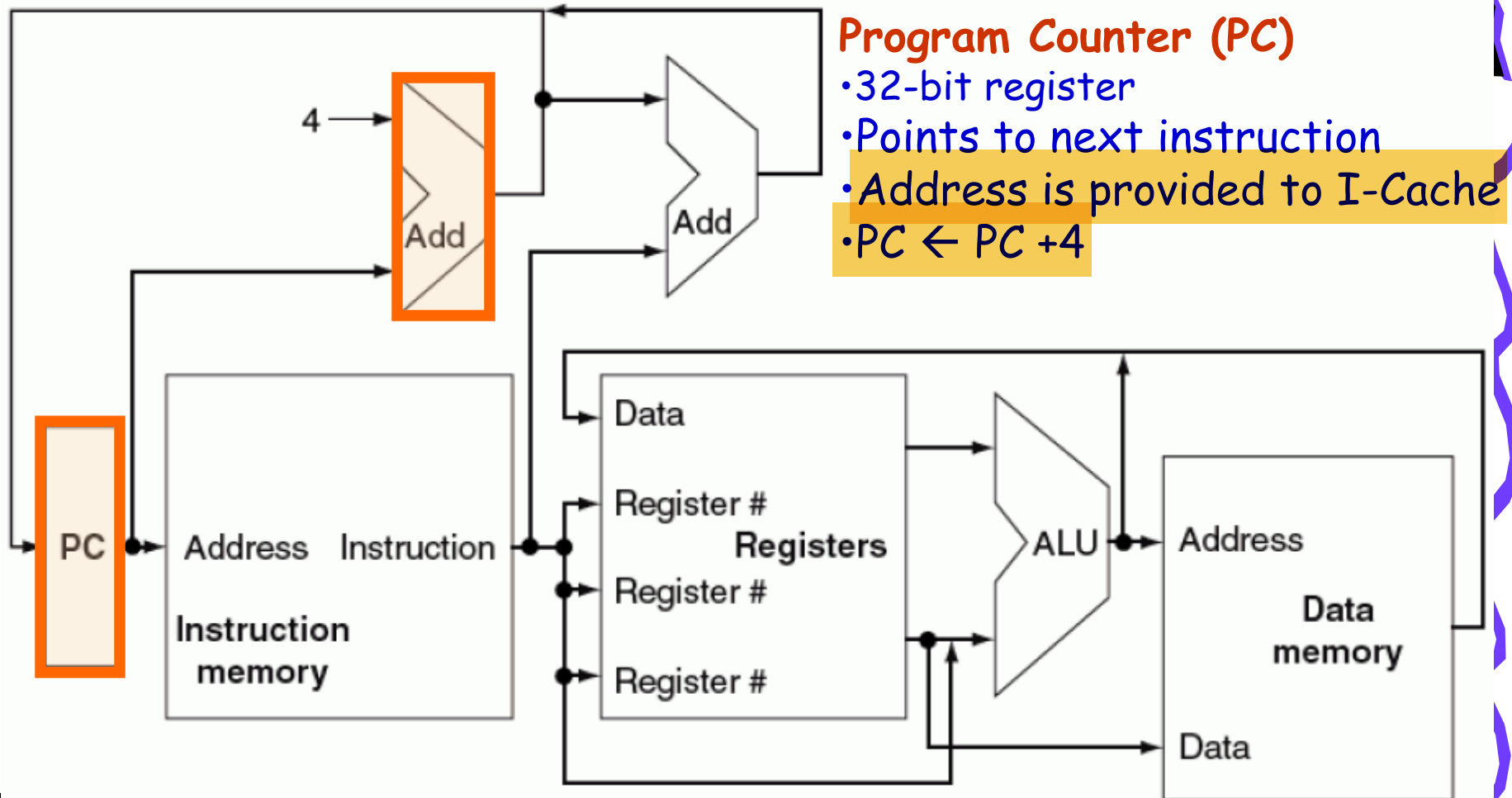 


Instruction Fetch

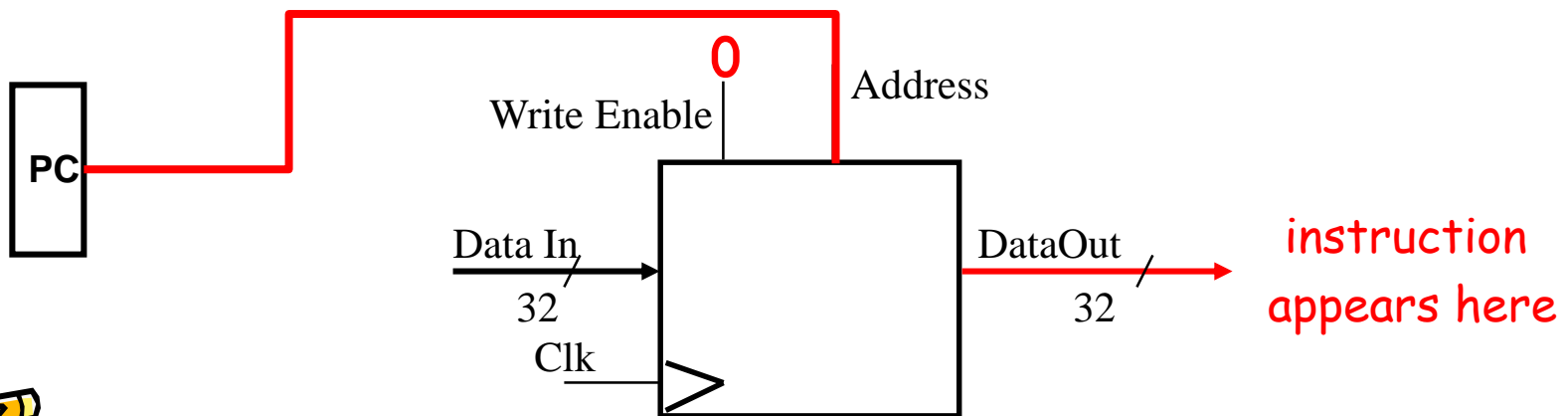- Program Counter (PC)
 - Supplies instruction address
 - Get instructions from memory



Instruction Memory (I-Cache)

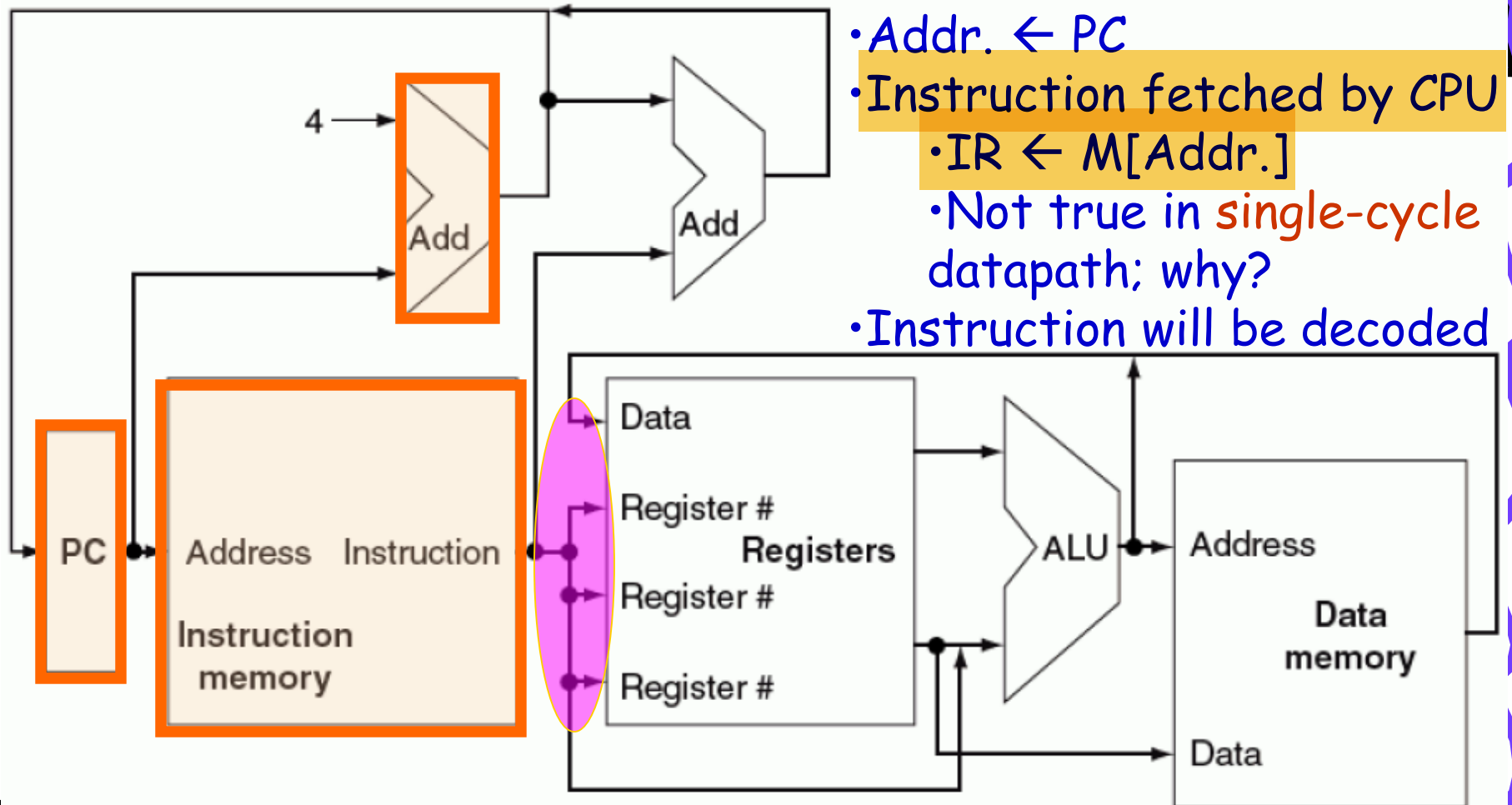
چون داخل طراحی single cycle چیزی به عنوان IR نداریم



Instruction Fetch Unit



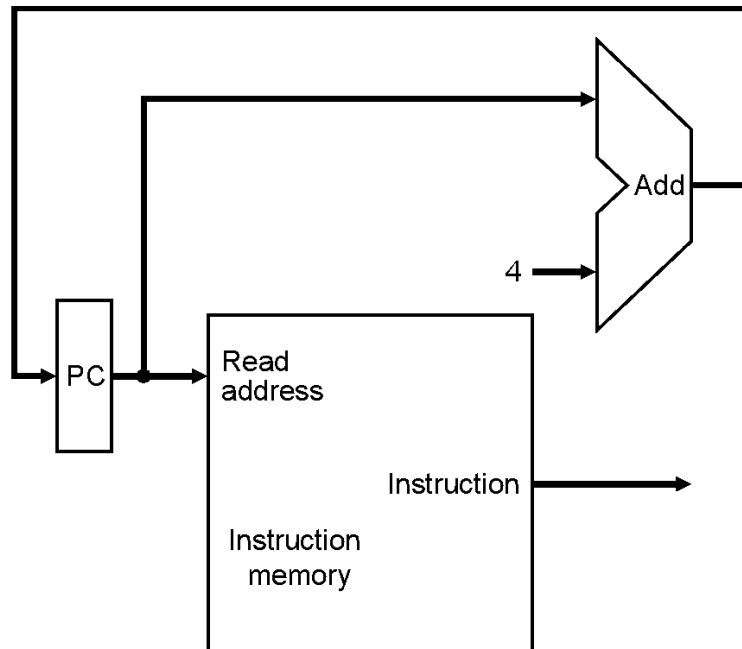- Updating PC for Next Instruction
 - Sequential Code: $PC \leftarrow PC + 4$
 - Branch and Jump: $PC \leftarrow \text{New Address}$
 - we'll worry about this later



Instruction Encoding



- MIPS Instruction Format

	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
r format	OP	rs	rt	rd	sa	funct
i format	OP	rs	rt	immediate		
j format	OP	target				

- OP: opcode
- rs: first register source operand
- rt: second register source operand
- rd: register destination operand
- sa: shift amount
- funct: function code




Instruction Encoding (cont.)




- R-TYPE

- *add rd, rs, rt*
- *sub, and, or, slt*

 


- LOAD / STORE

- *lw rt, rs, imm*
- *sw rt, rs, imm*

 


- BRANCH

- *beq rs, rt, imm*

 

R-Type Encoding

 


add \$4, \$3, \$2

rd

rt


rs

 

0 0 0 0 0 0 0 0 0 1 1 0 0 0 1 0 0 0 1 0 0 0 0 0 0 0 1 0 0 0 0 0

Encoding = 0x00622020

Register File

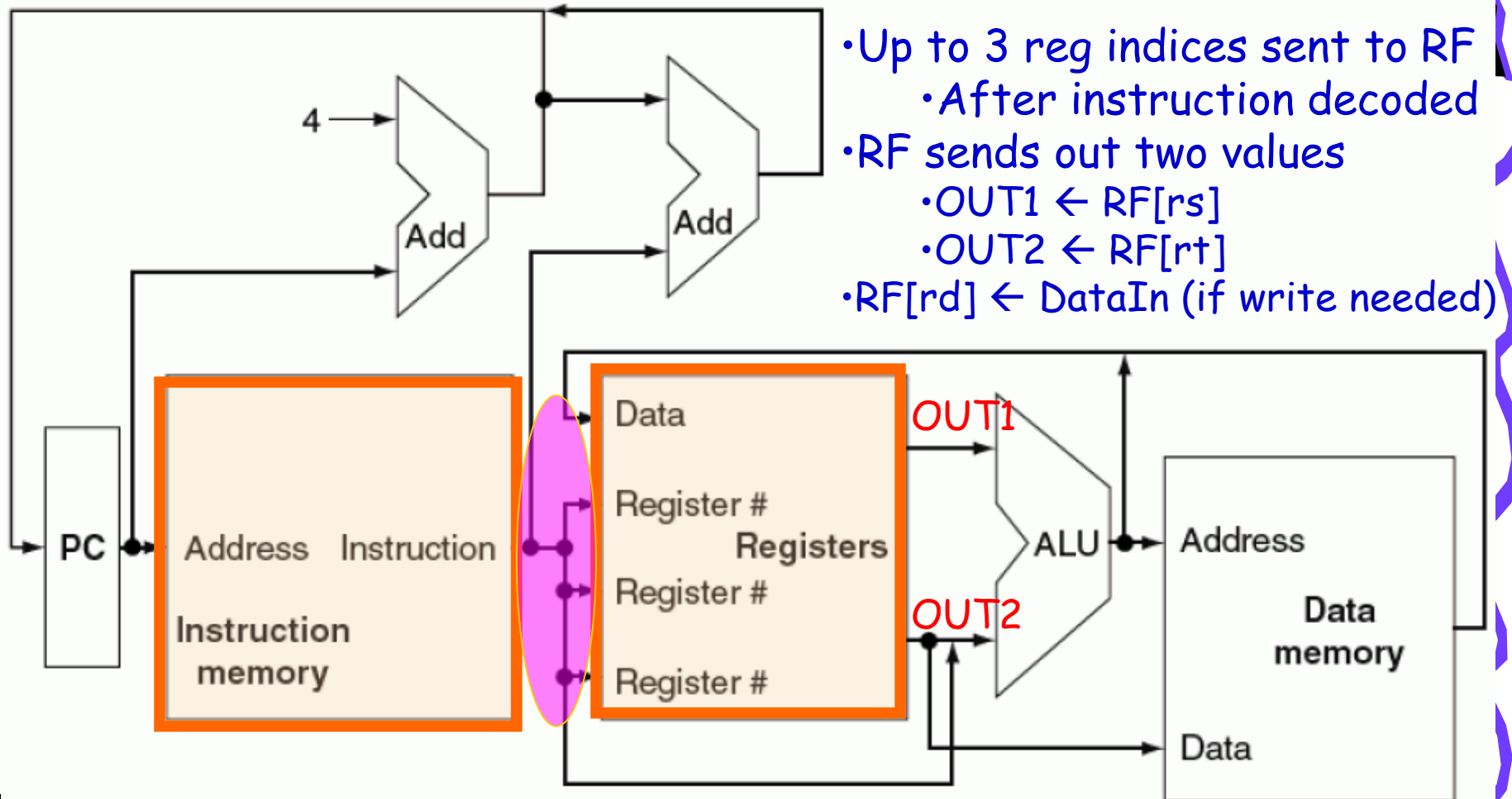


- Up to 3 reg indices sent to RF
 - After instruction decoded
- RF sends out two values
 - $OUT1 \leftarrow RF[rs]$
 - $OUT2 \leftarrow RF[rt]$
- $RF[rd] \leftarrow DataIn$ (if write needed)

Datapath Elements



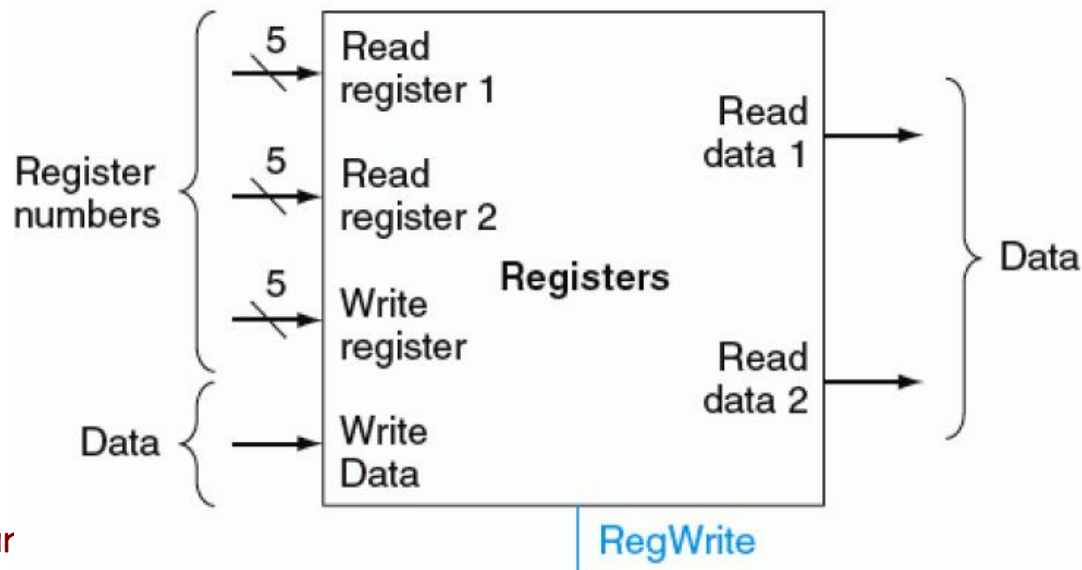
- Register File (RF)
 - Also called, General Purpose Registers (GPR)
 - Up to three indices as inputs
 - 32-bit write input data
 - Two 32-bit outputs



Datapath Elements (cont.)



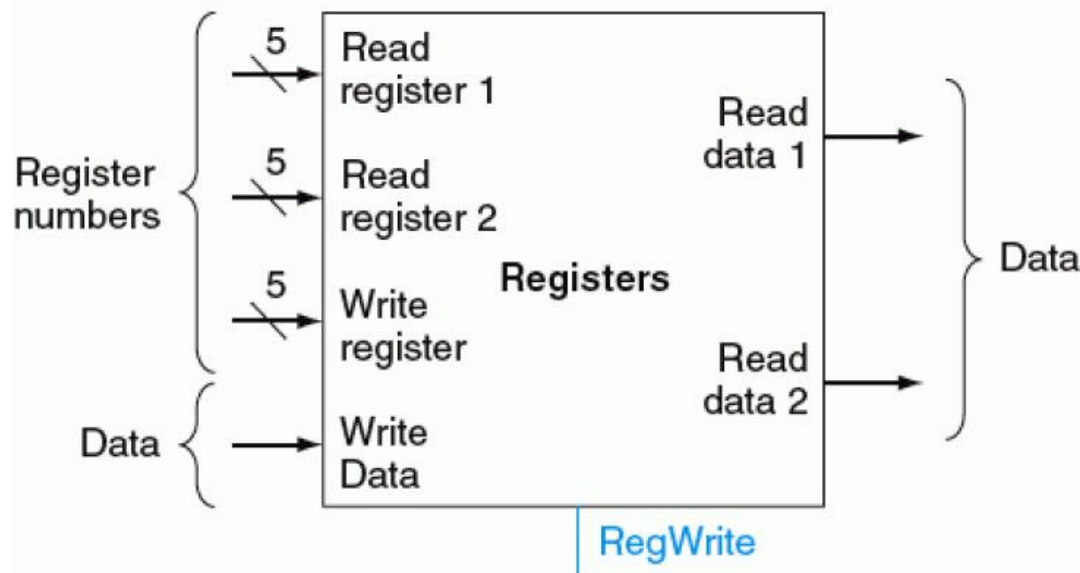- Question 1:
 - How read & write can be accomplished in one clock cycle without data contention?




اولین راه: در لبه
بالارونده بخوانیم و در
لبه پایین رونده بنویسیم
دومین راه: تاخیر
read را جوری در
نظر بگیریم که write
قبلش انجام شده باشد




Datapath Elements (cont.)



 - Question 2:
 - How two simultaneous read operations possible?



ALU

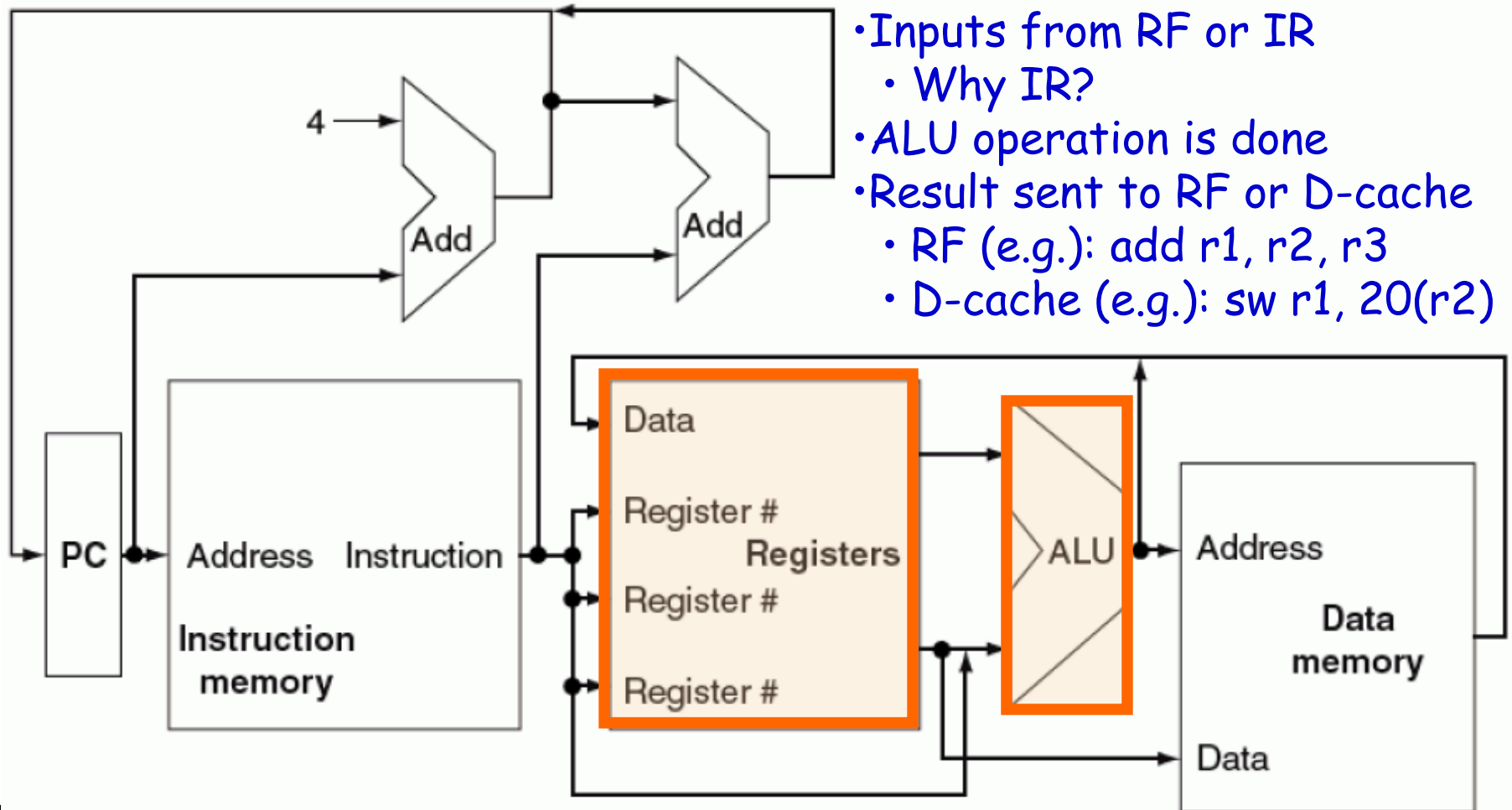


Reminder: Addressing Modes





Operand is constant

1. Immediate addressing



 


Operand is in register

2. Register addressing

 
 


3. Base addressing

   




lb \$t0, 48(\$s0)

4. PC-relative addressing

  

bne \$4, \$5, Label
(label will be assembled into
a distance)

5. Pseudodirect addressing

   


j Label





Datapath Elements (cont.)



 - ALU
 - Two 32-bit inputs
 - One 32-bit output
 - 4-bit operation selector
 - Zero?



Data Memory (D-Cache)

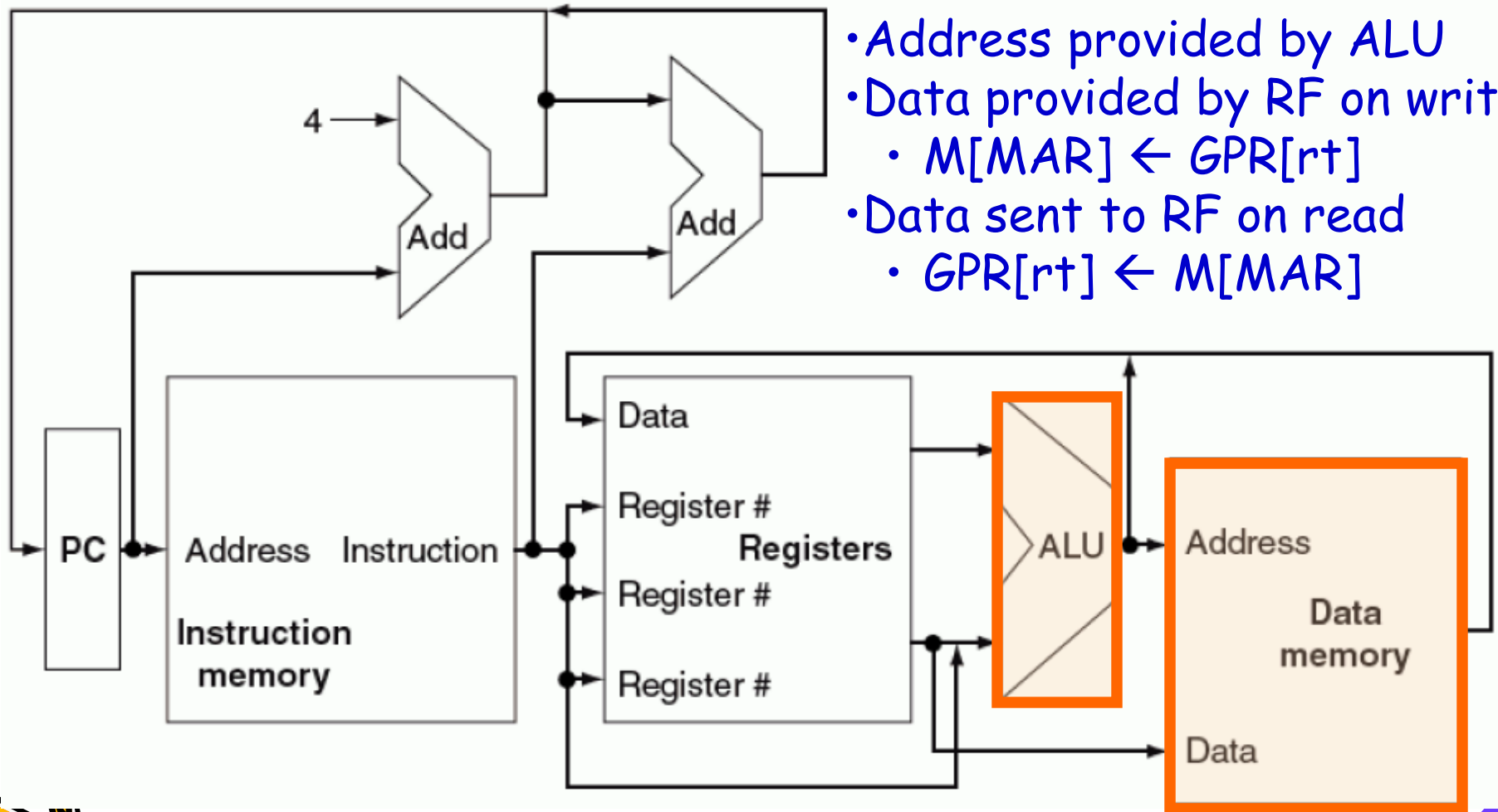 


- Address provided by ALU
- Data provided by RF on write
 - $M[MAR] \leftarrow GPR[rt]$
- Data sent to RF on read
 - $GPR[rt] \leftarrow M[MAR]$



Datapath Elements (cont.)



 - Data Memory Unit
 - Address
 - Loads/store: $MAR = GPR[rs] + imm16$
 - 32-bit write data
 - Write data $\leftarrow GPR[rt]$
 - 32-bit read data
 - $GPR[rt] \leftarrow \text{Read data}$
 - MemRead signal
 - MemWrite signal





Discussion



- Compare **MemRead** and **MemWrite** Activation Process in Following Cases
 - Case A: separate I-cache & D-cache with separate data bus
 - Case B: separate I-cache & D-cache with common data bus
 - Case C: unified I-cache & D-cache



Abstract View of MIPS Implementation

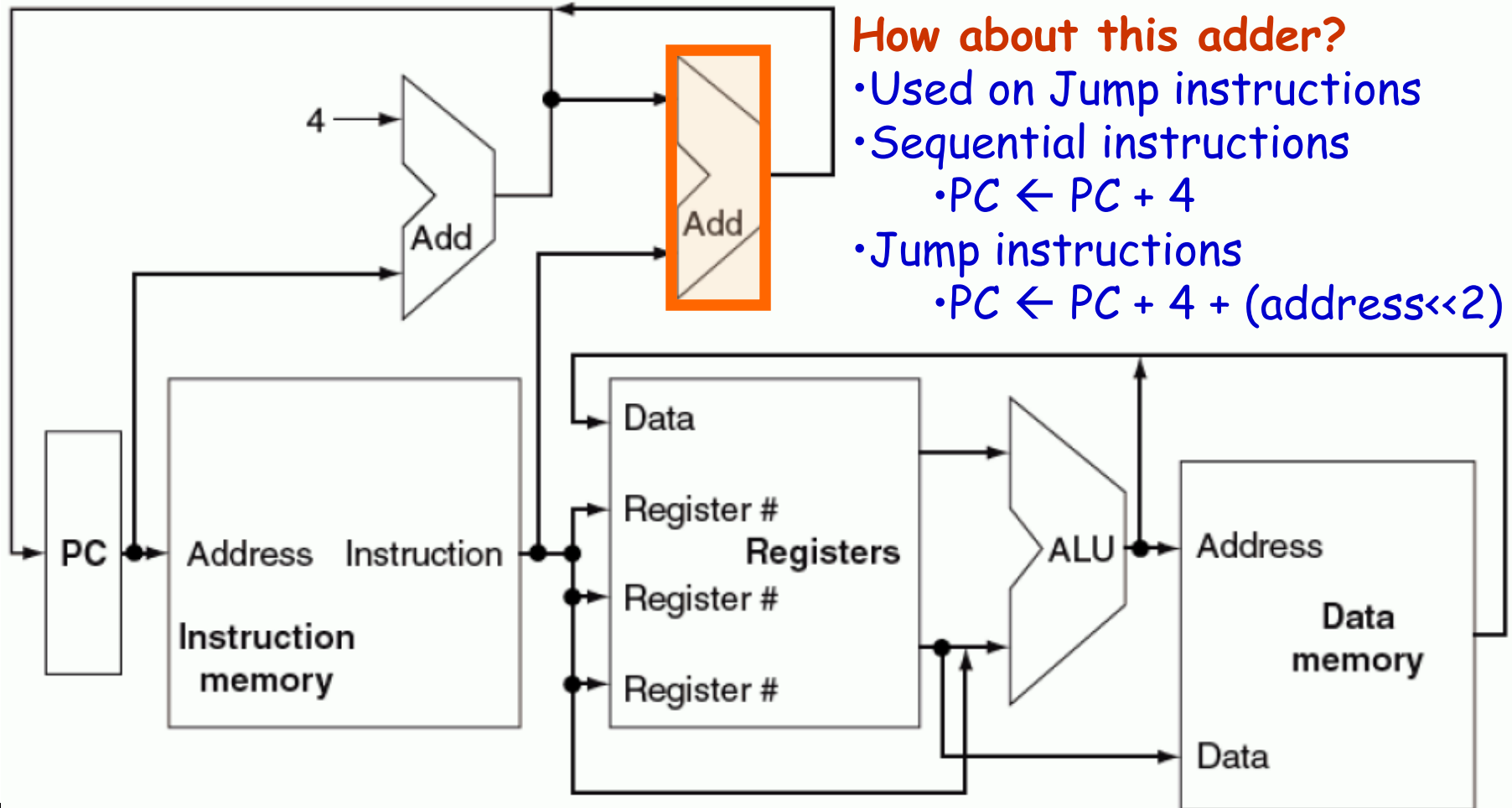 


Datapath Elements (cont.)




- Branch Unit
 - Sign extend unit
 - Adder
 - Shifter
 - Do we need a shifter here?

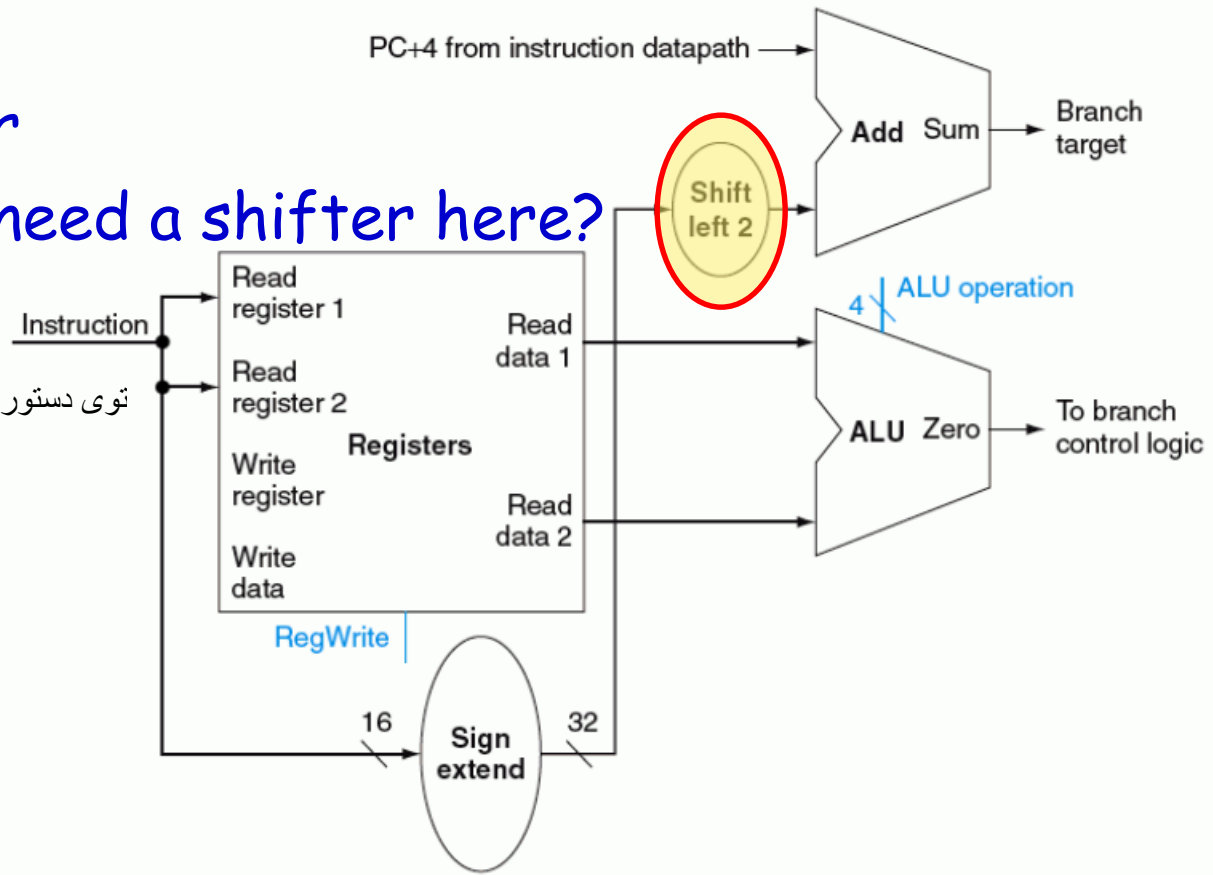توی دستور branch برای پیدا کردن خط دستور بعدی




Practice

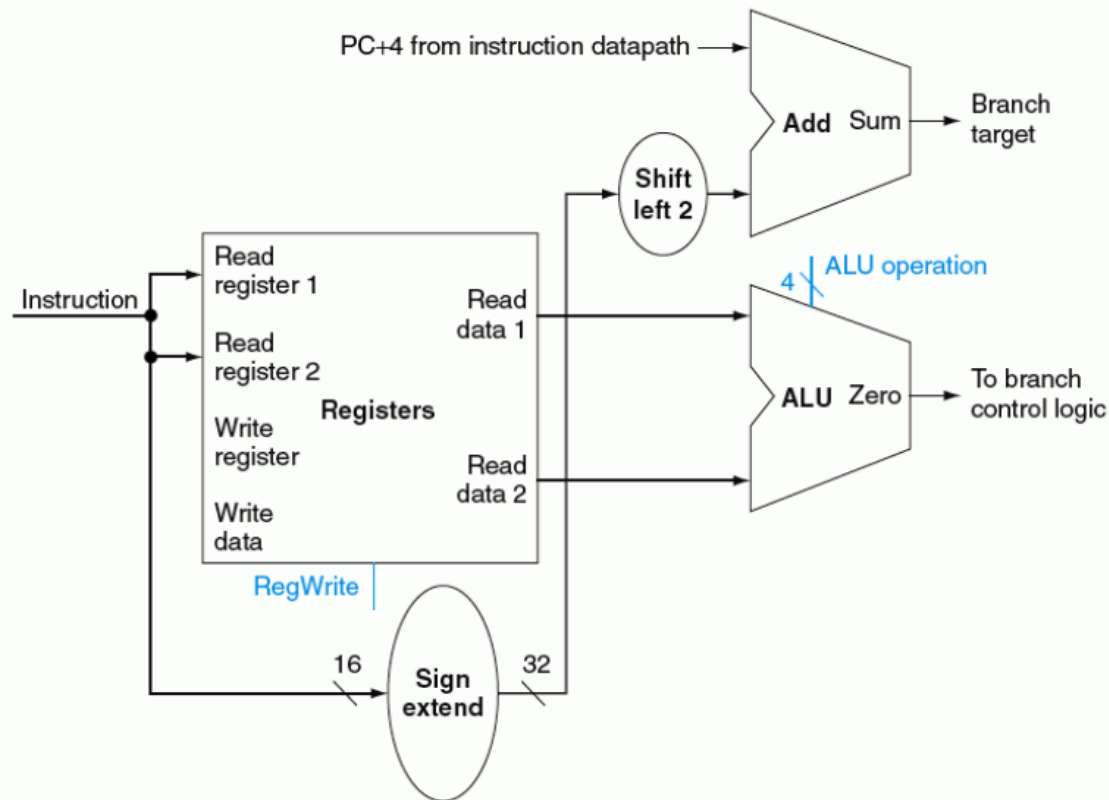- In Following Circuit:
 - Draw sign-extend & shift logic




Address Bus & Data Bus

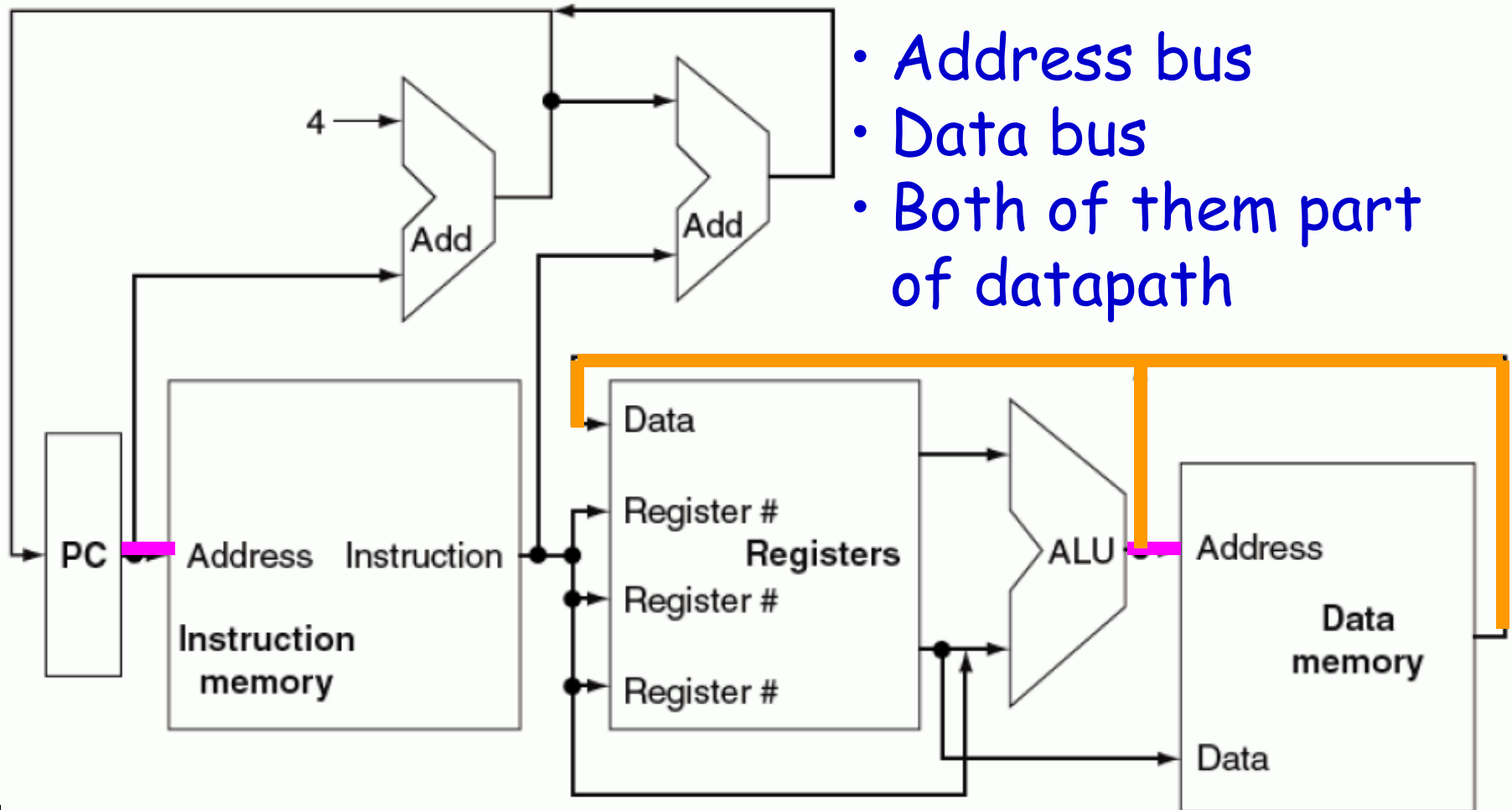

- Address bus
- Data bus
- Both of them part of datapath


Combining Datapaths

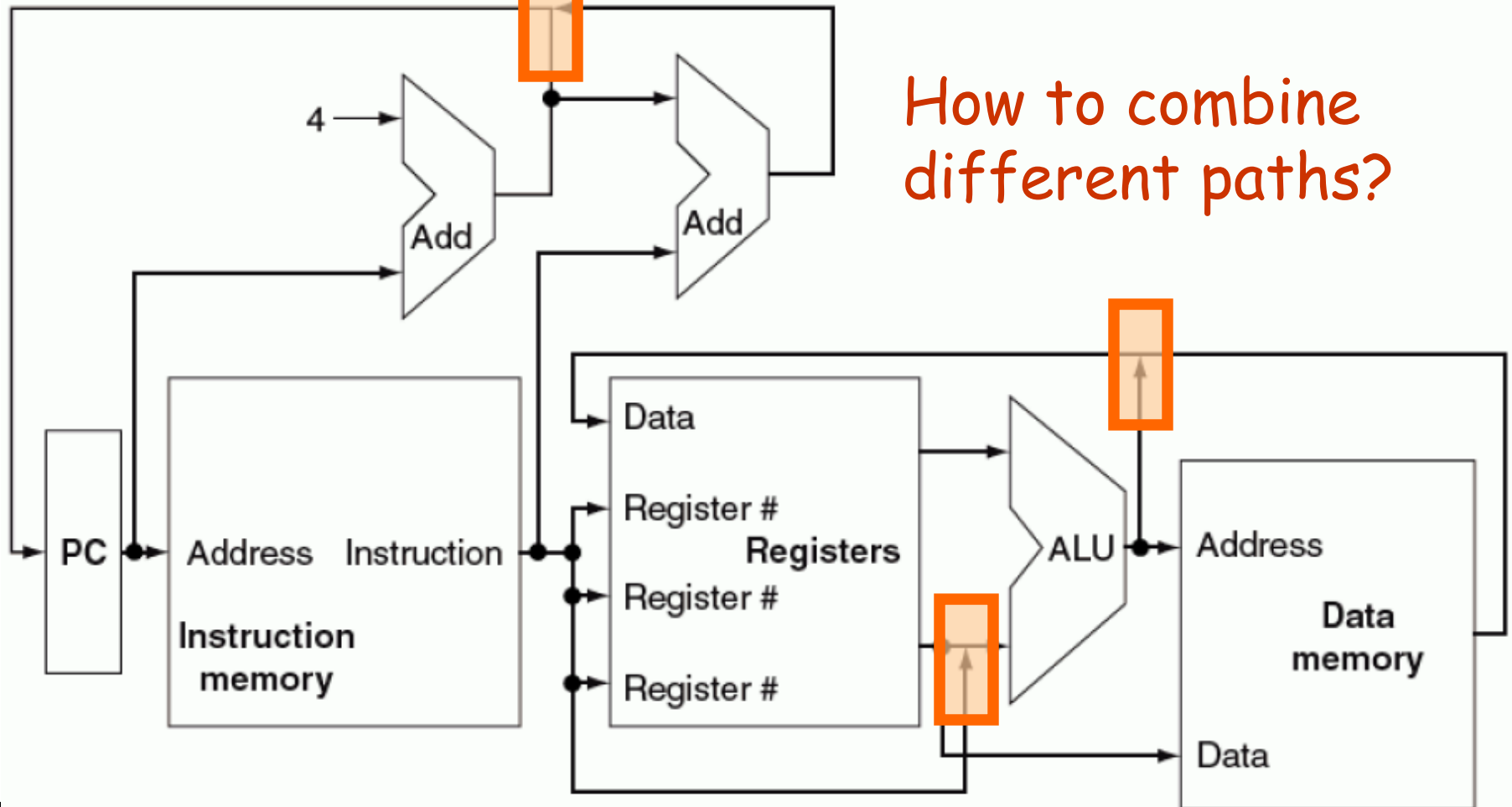


Combining Datapaths (cont.)



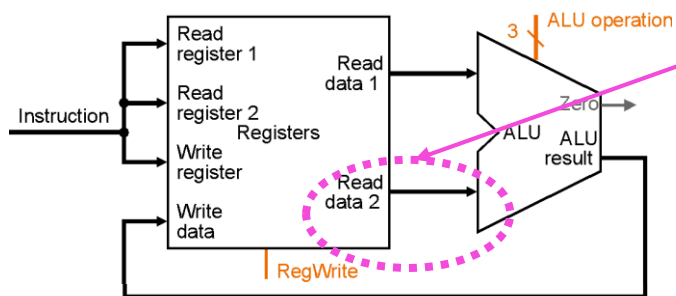- How to have different datapaths for different instruction?



R-type

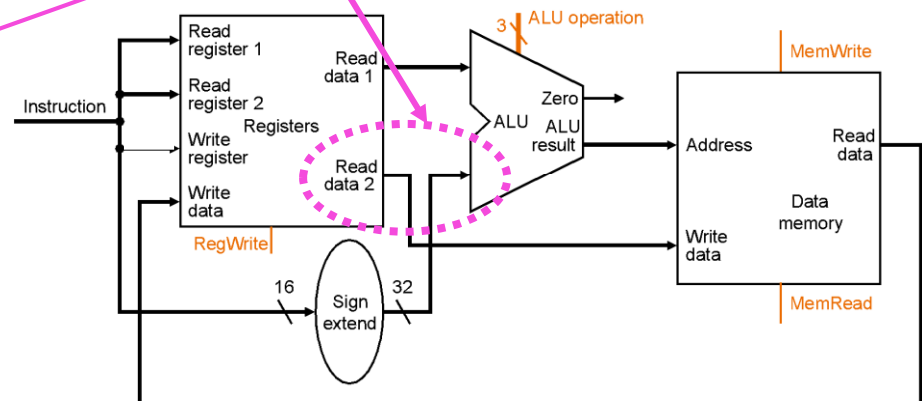



Store




Combining Datapaths (cont.)



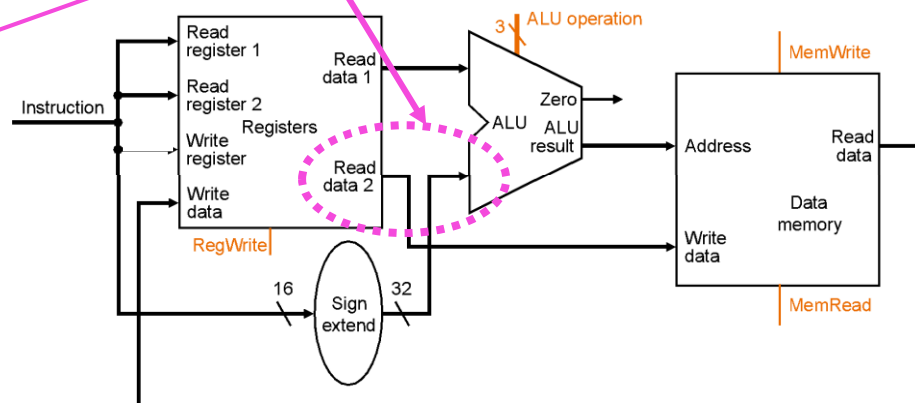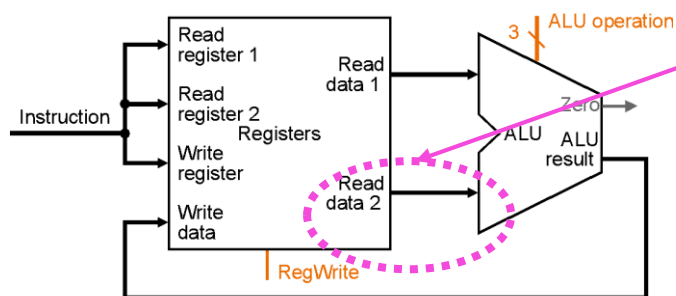- How to have different datapaths for different instruction?




- Use a multiplexer

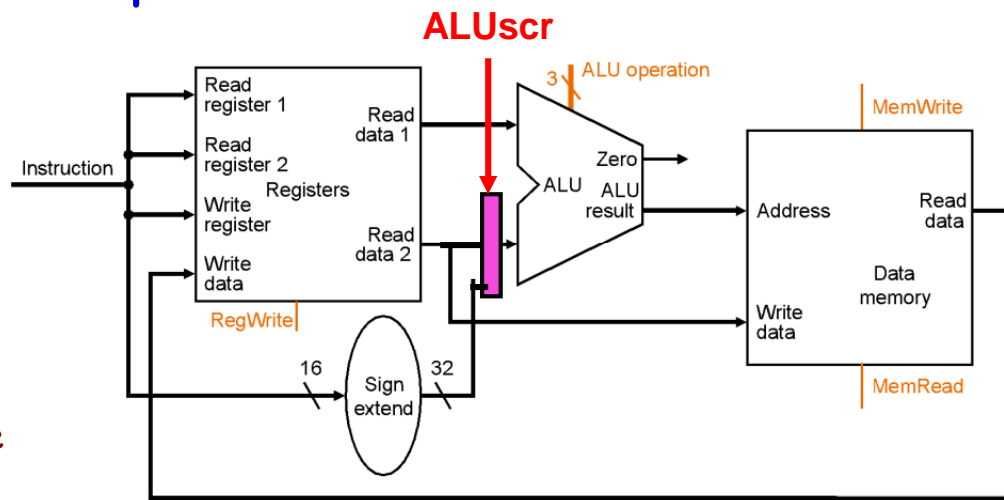


Combining Datapaths (cont.)



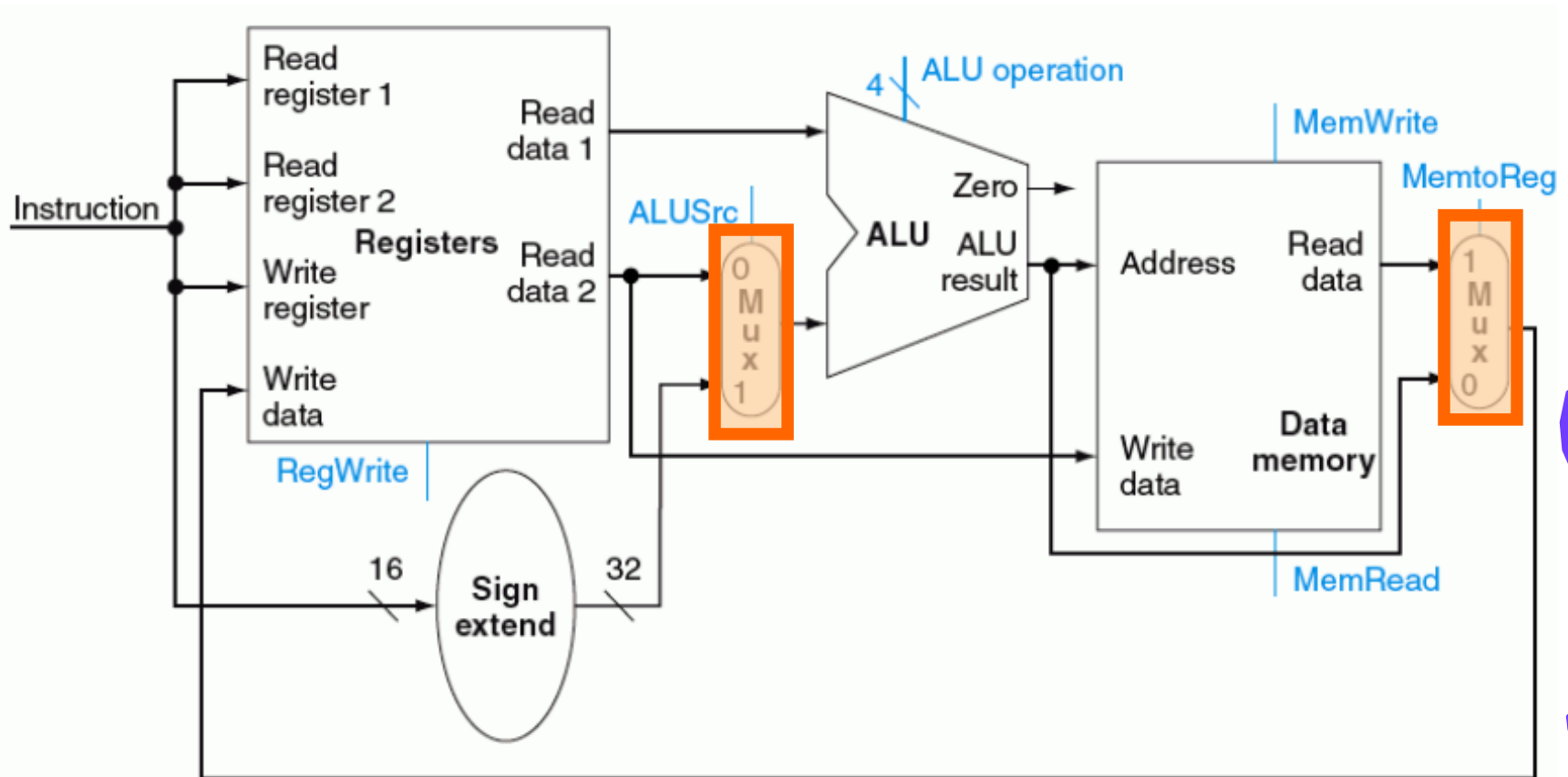- Merging R-type datapath with load/store datapath using multiplexer



All Together: Single Cycle Datapath

 


Practice



- Question:
 - Could we swap rs, rt, & rd bits to have easier datapath design?
 - In other words, can we remove RegDst MUX?



Practice: Answer

 

- R-type
 - rs & rt: read index bits
 - rd: write index bits
- lw:
 - rs: read index bits
 - rt: write index bits
- sw:
 - rs & rt: read index bits




Reminder: Instruction Encoding




- R-TYPE

- *add rd, rs, rt*
- *sub, and, or, slt*

 


- LOAD / STORE

- *lw rt, rs, imm*
- *sw rt, rs, imm*

 


- BRANCH

- *beq rs, rt, imm*

 


All Together: Single Cycle Datapath

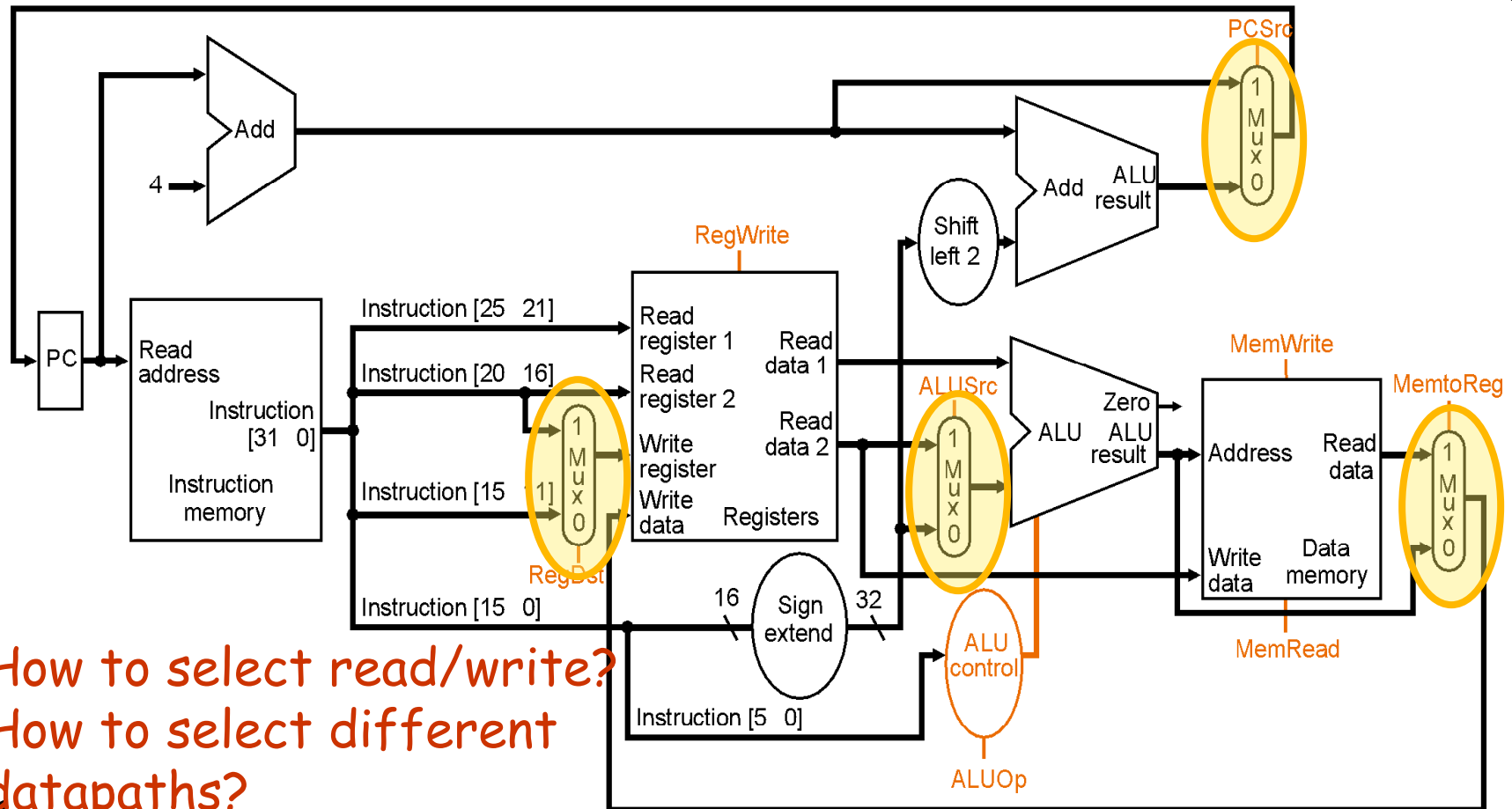

How to select read/write?
How to select different
datapaths?



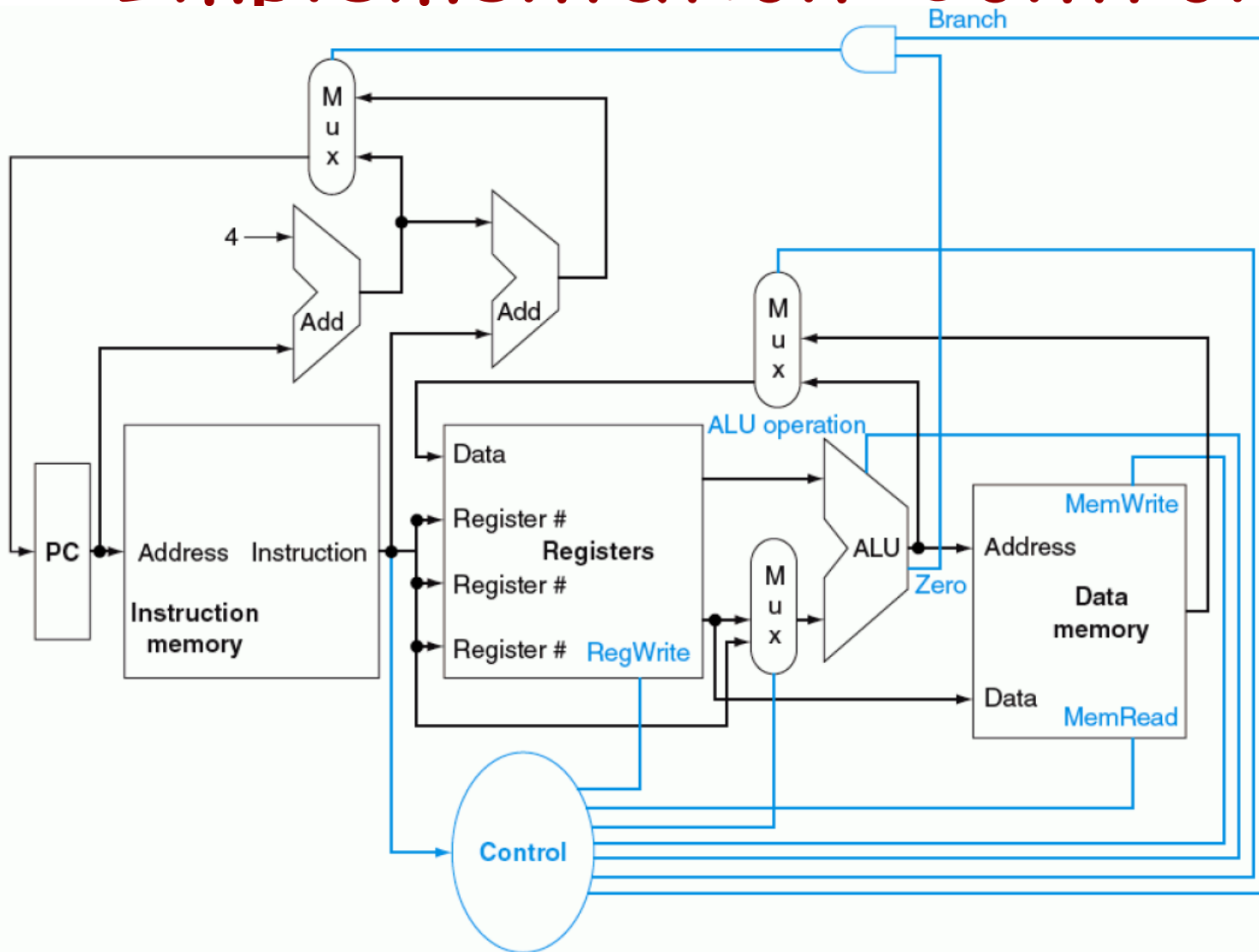
Abstract View of MIPS Implementation: Control



Datapath for Reg-Reg Operations



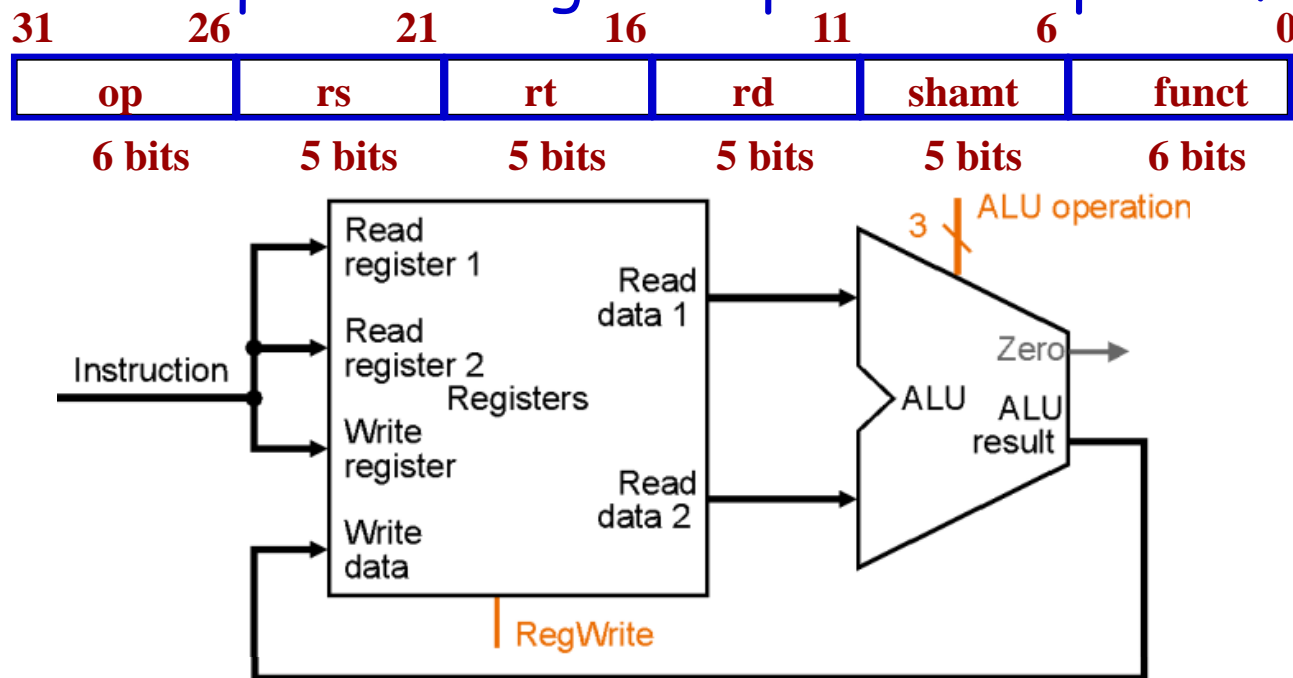- $GPR[rd] \leftarrow GPR[rs] \text{ op } GPR[rt]$
 - Example: *add rd, rs, rt*
 - ALU operation signal depends on op and funct




ALU operation and **RegWrite**: control logic after decoding instruction



Datapath for Load Operations



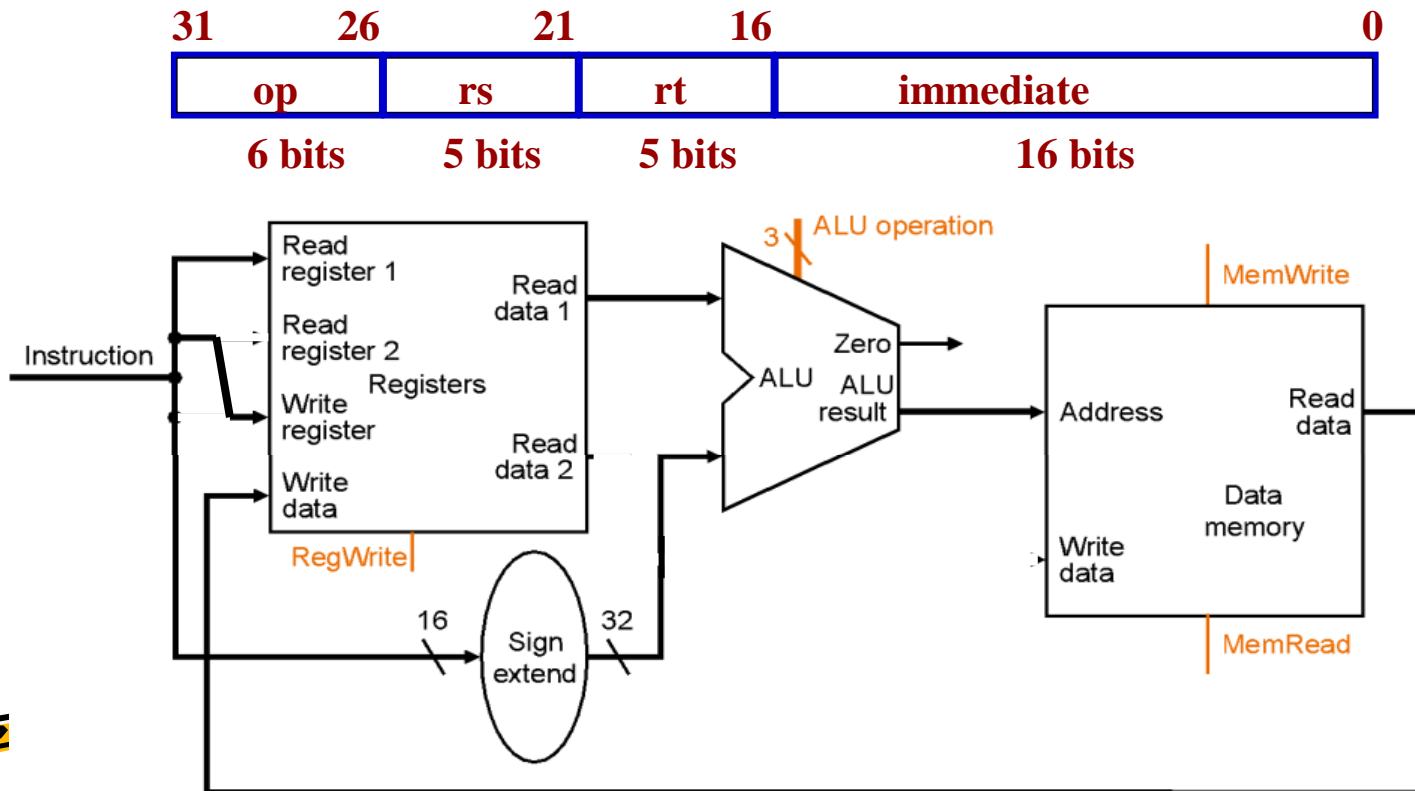
- $GPR[rt] \leftarrow Mem[GPR[rs] + SignExt[imm16]]$
 - Example: *lw rt, rs, imm16*



Datapath for Store Operations




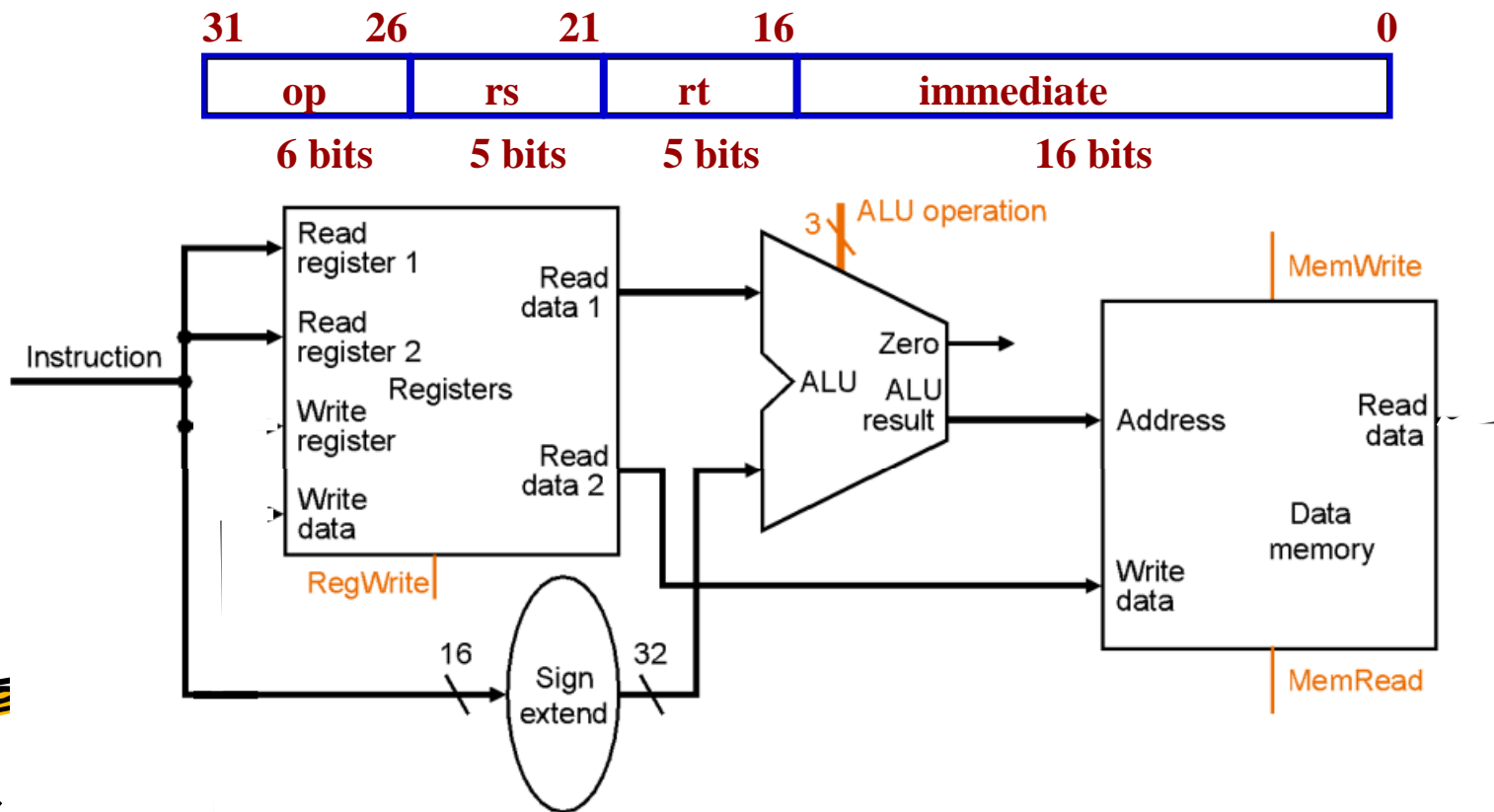
- $\text{Mem}[\text{GPR}[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow \text{GPR}[\text{rt}]$
 - Example: *sw rt, rs, imm16*



Datapath for Branch Operations



- beq rs, rt, imm16*

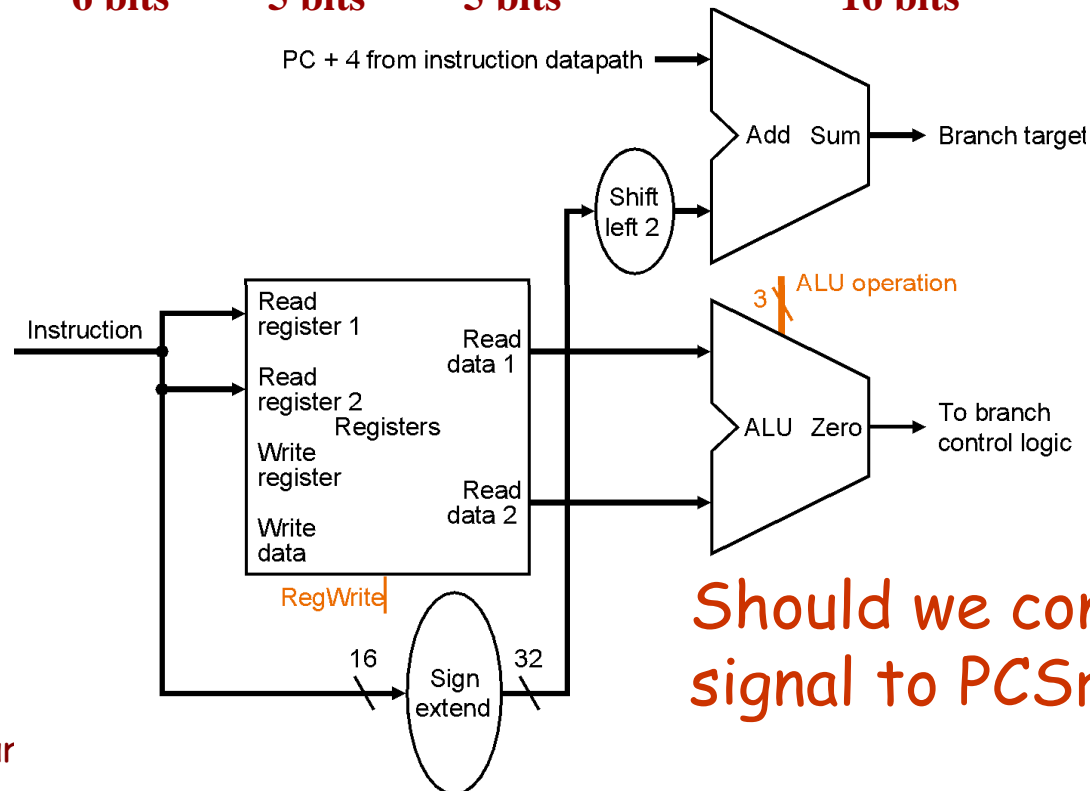 


Should we connect "Zero" signal to PCSrc selector?



A stylized illustration of a yellow pencil with a purple eraser and a purple sharpened lead tip. The pencil is oriented diagonally from the top-left towards the bottom-right. It features black outlines and decorative black lines along its length.




Load Datapath

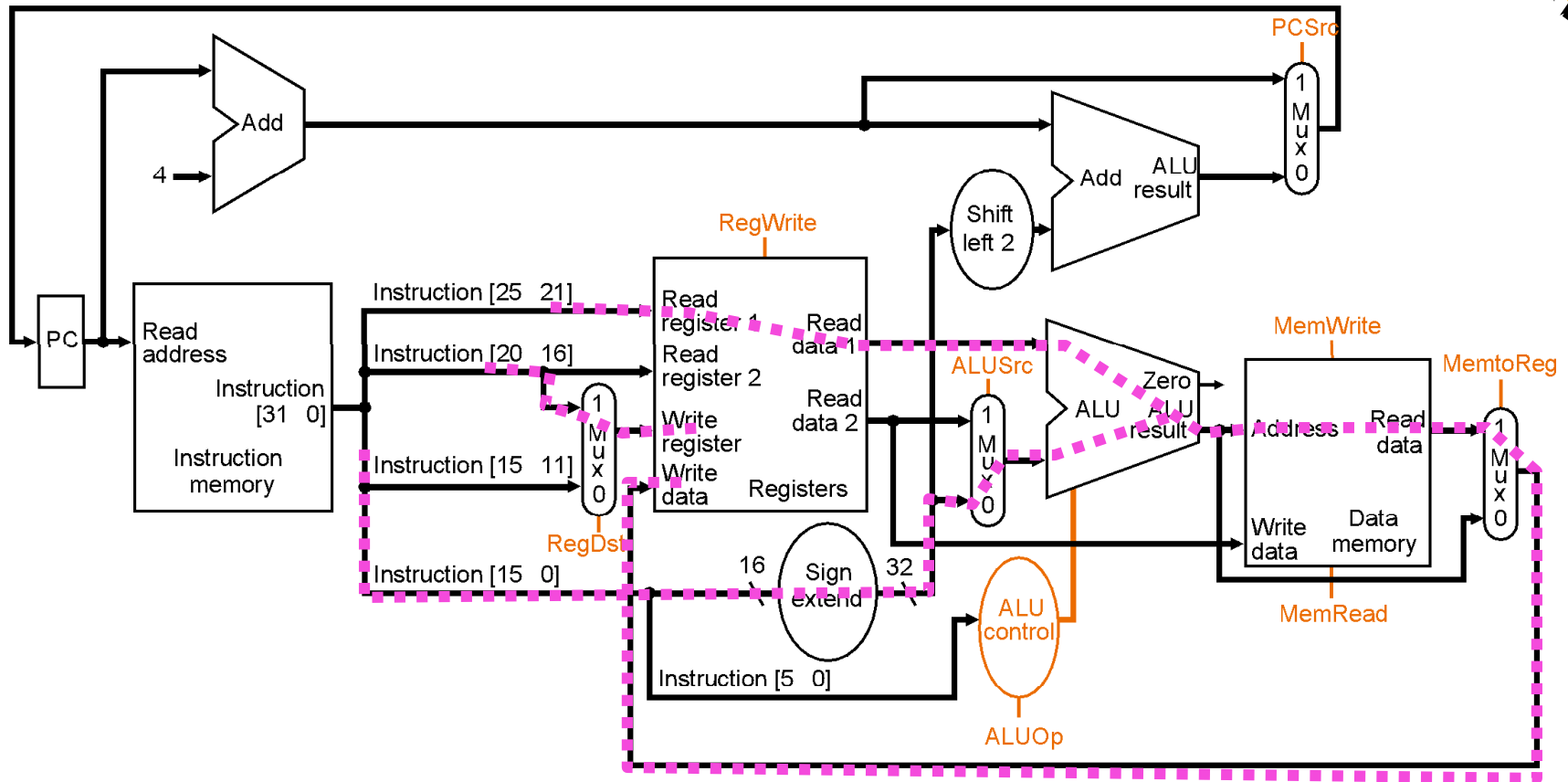


What control signals do we need for load??


Store Datapath

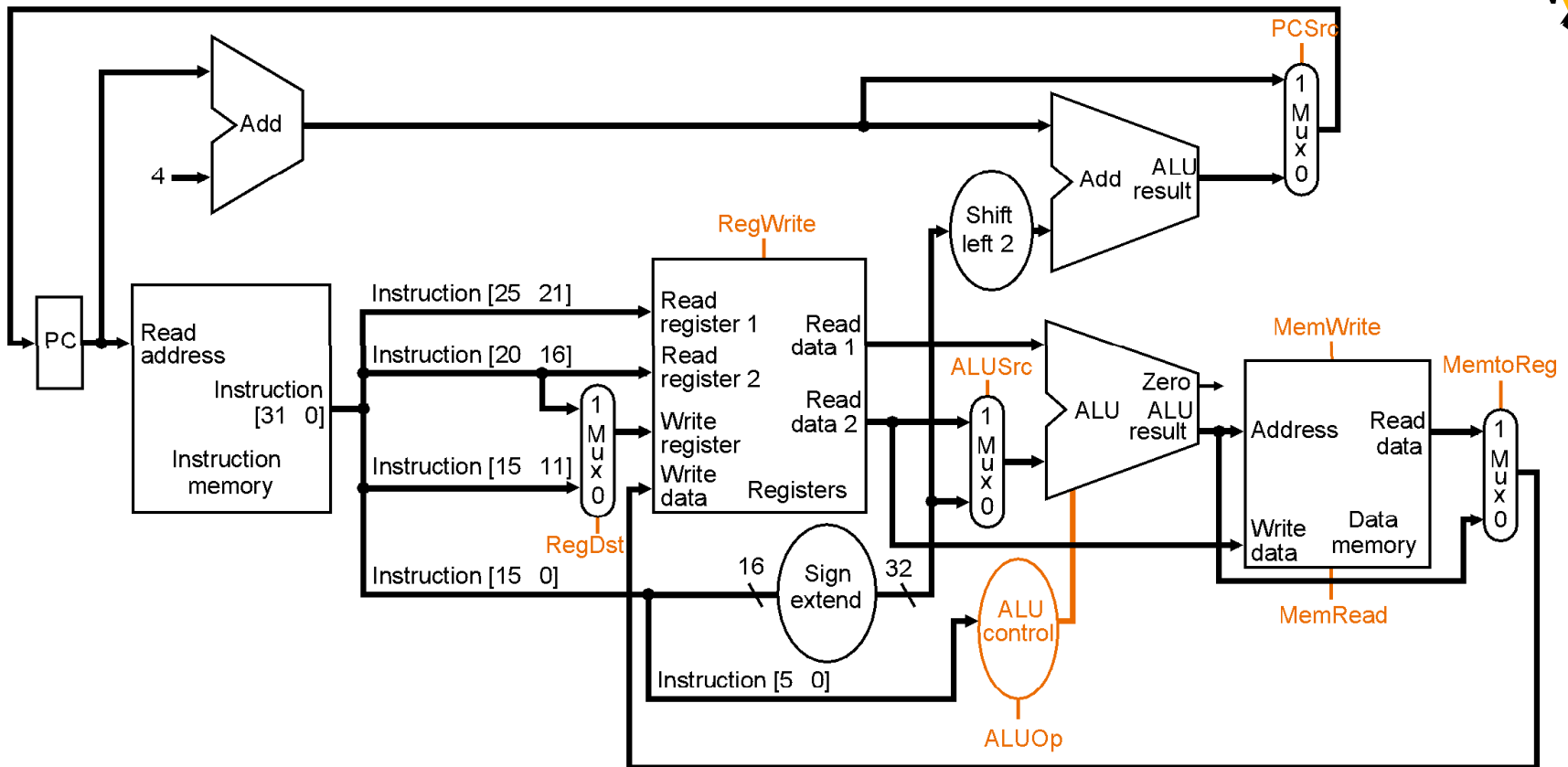

beq Datapath

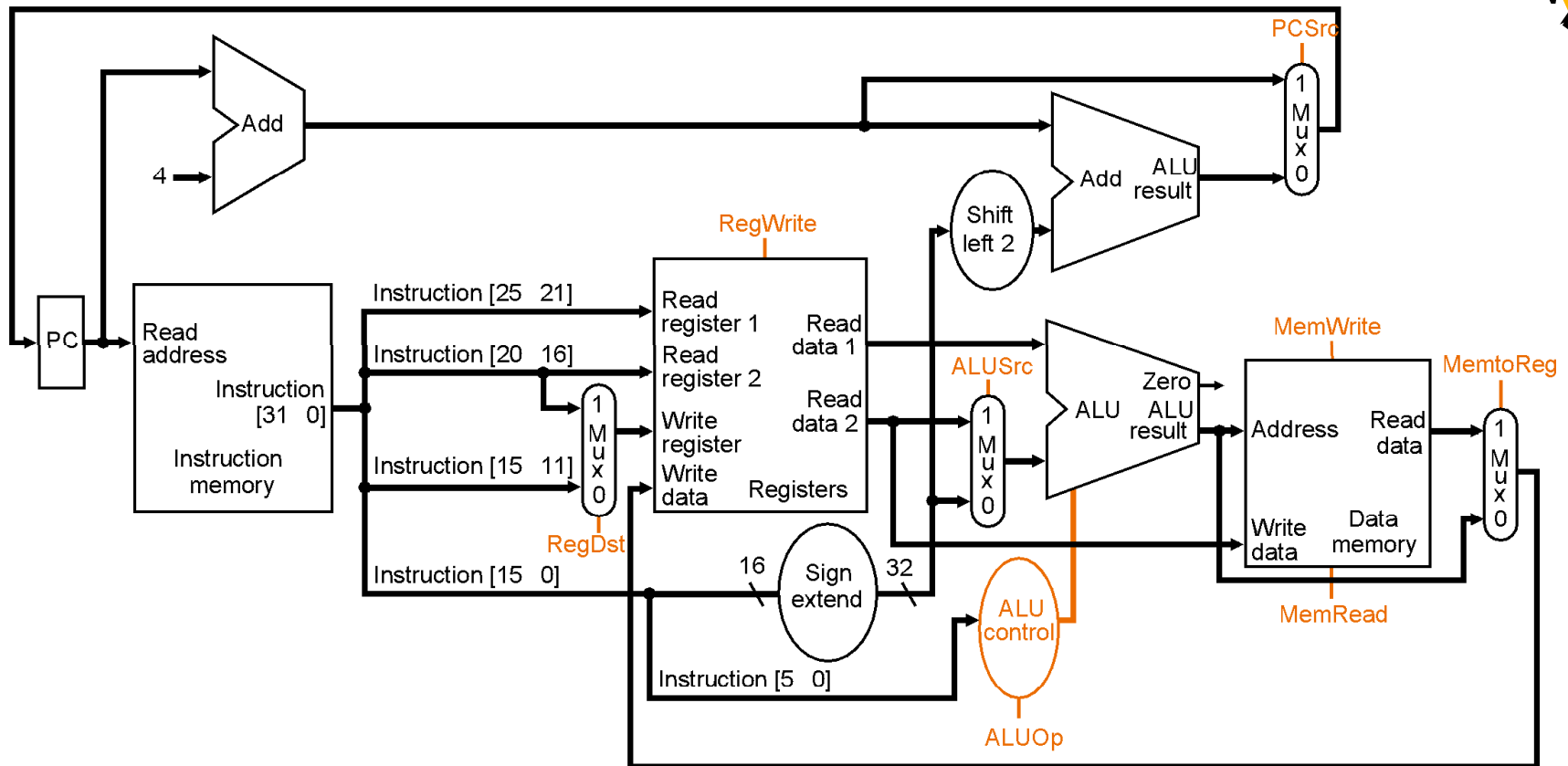

Putting it All Together

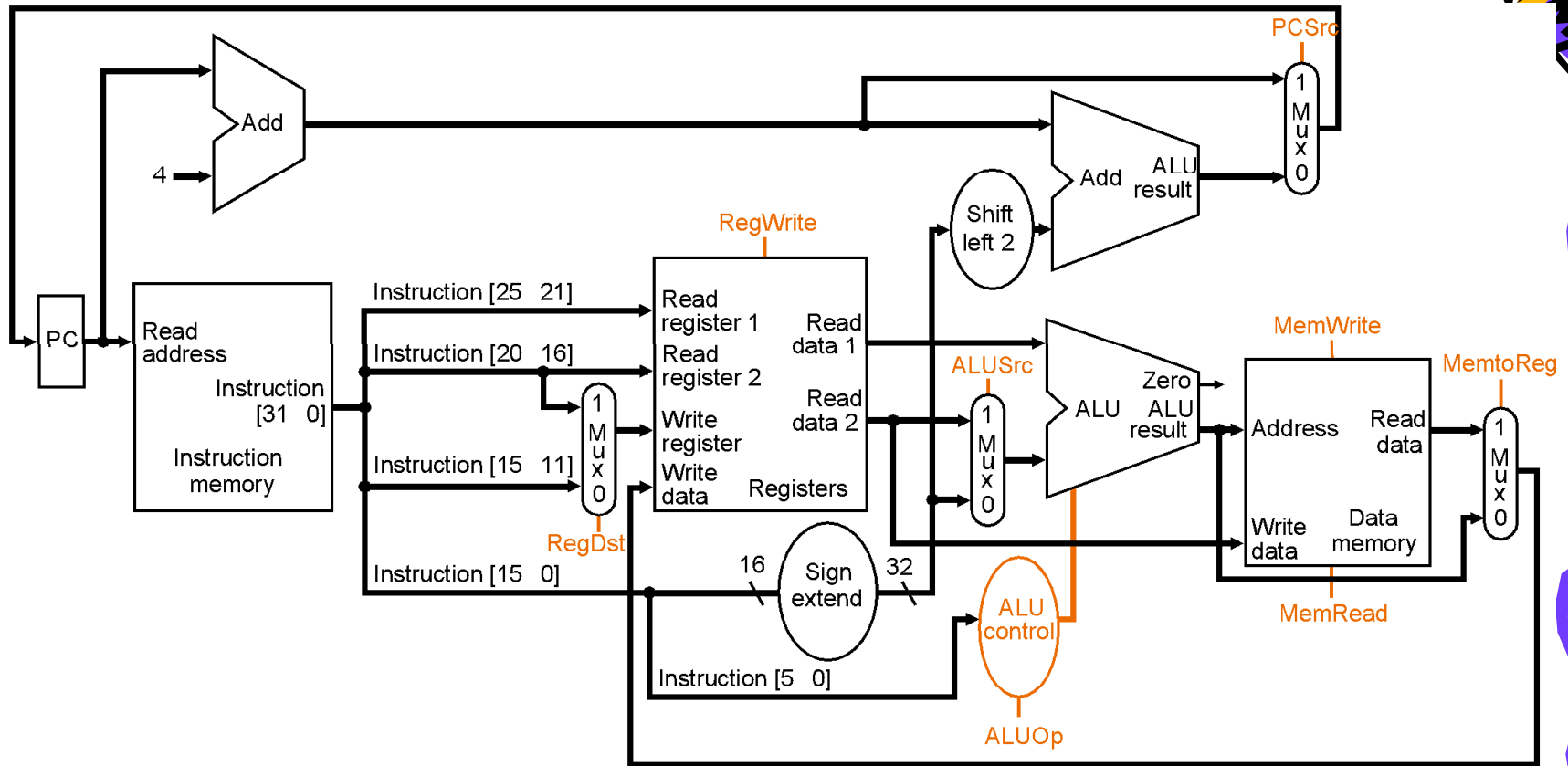

We have everything except details for generating control signals

Backup

