




Computer Architecture

Hossein Asadi
Department of Computer Engineering
Sharif University of Technology
asadi@sharif.edu

Today's Topics

- Data Path Design

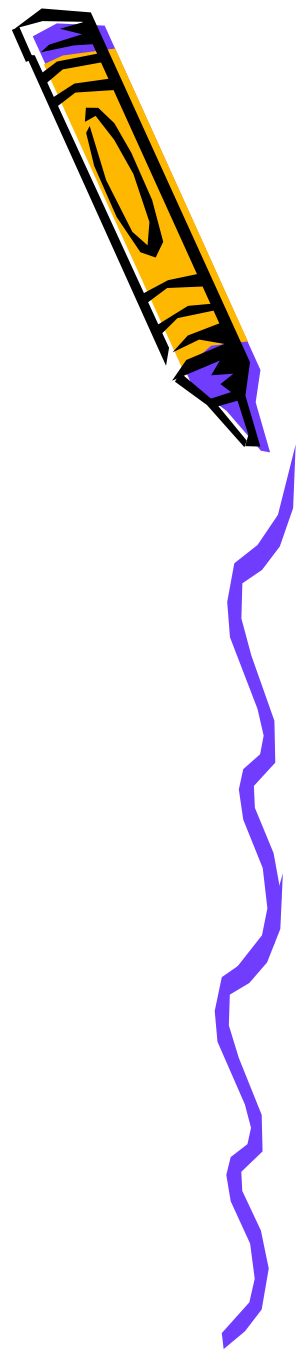

Copyright Notice



- Parts (text & figures) of this lecture adopted from:
 - Computer Organization & Design, The Hardware/Software Interface, 3rd Edition, by D. Patterson and J. Hennessey, MK publishing, 2005.
 - "Intro to Computer Architecture" handouts, by Prof. Hoe, CMU, Spring 2009.
 - "Computer Architecture & Engineering" handouts, by Prof. Kubiawicz, UC Berkeley, Spring 2004.
 - "Intro to Computer Architecture" handouts, by Prof. Hoe, UWisc, Fall 2009.
 - "Computer Arch I" handouts, by Prof. Garzarán, UIUC, Spring 2009.




Datapath





- Datapath?
 - A functional unit used to **operate** on or **hold** data within a processors
- Datapath Elements in MIPS
 - Instruction memory
 - Data memory
 - Register file
 - ALU
 - Adders
- Control Unit
 - Schedule data movements in datapath



Datapath (cont.)

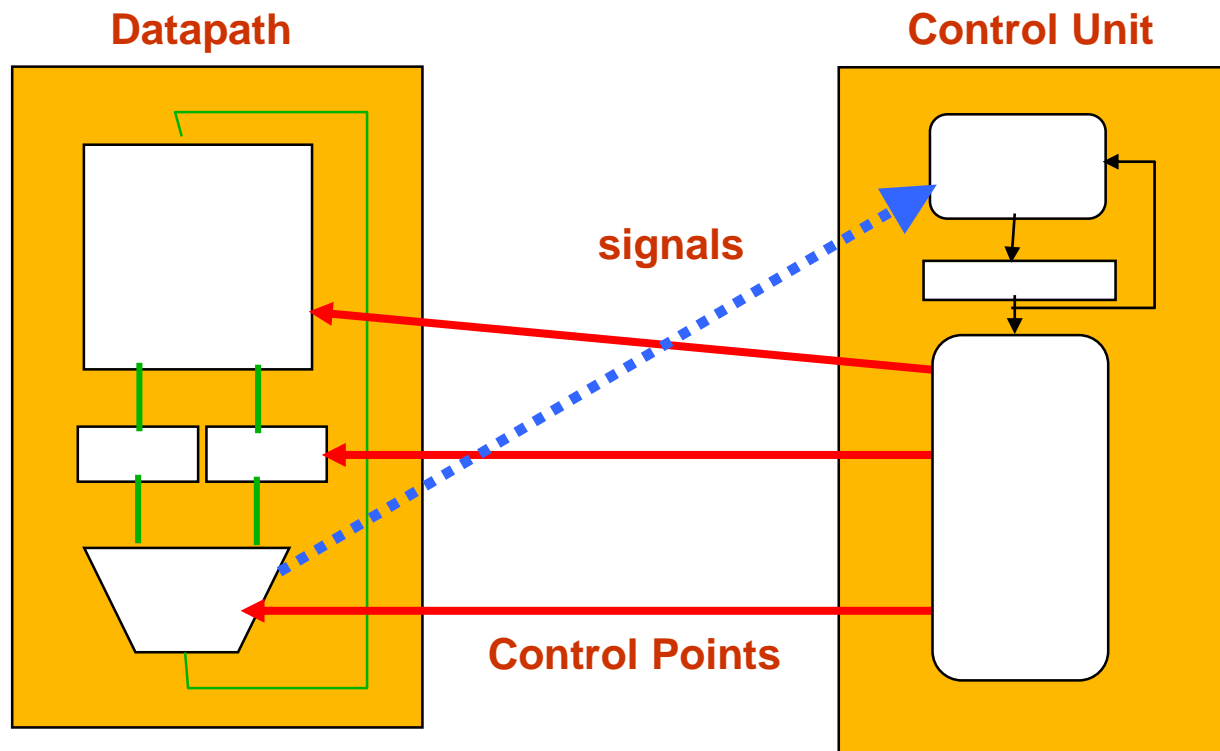

Abstract View of MIPS Implementation

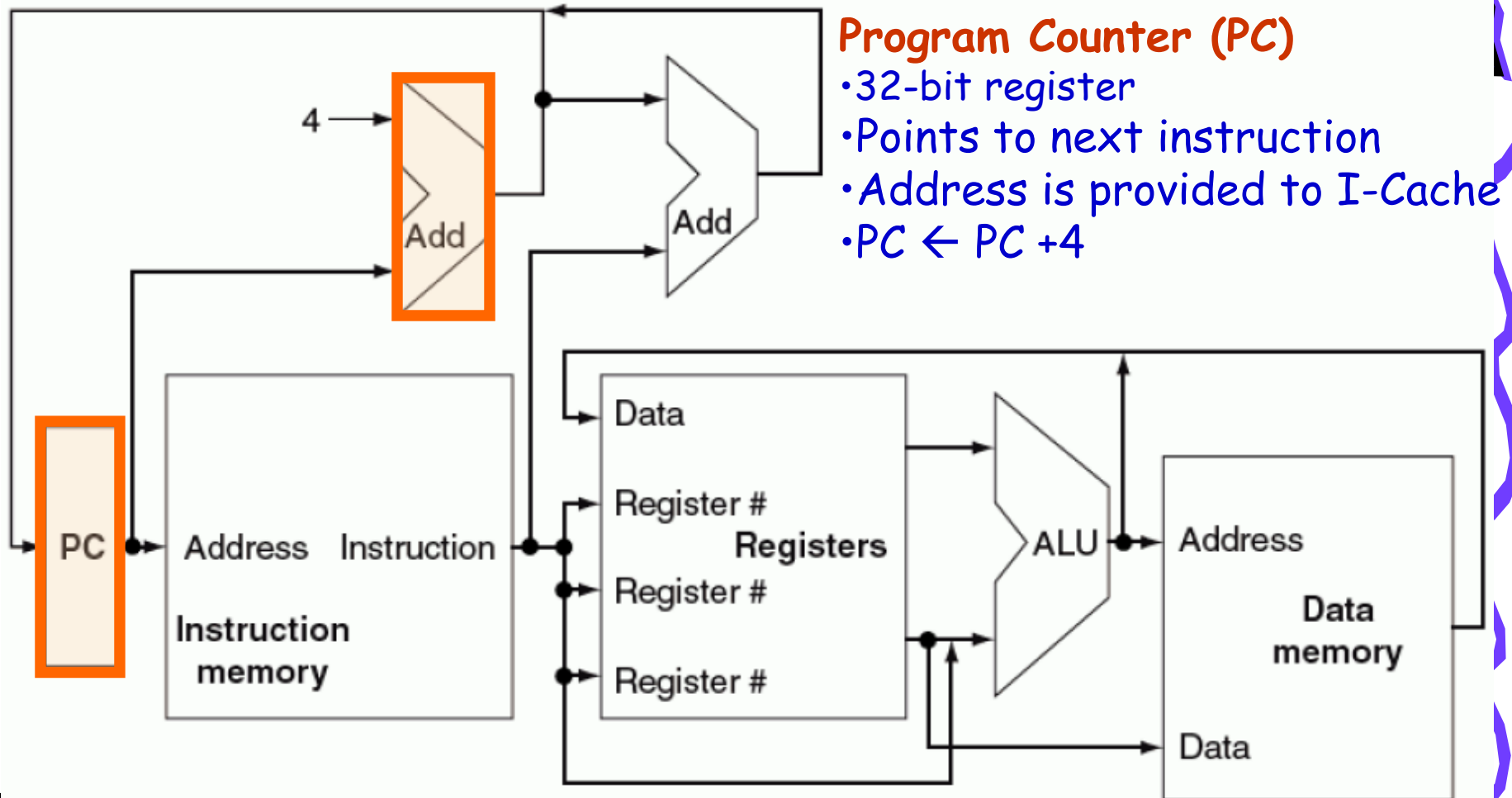 

Program Counter (PC)


- 32-bit register
- Points to next instruction
- Address is provided to I-Cache
- $PC \leftarrow PC + 4$





Instruction Fetch



 - Program Counter (PC)
 - Supplies instruction address
 - Get instructions from memory




Instruction Memory (I-Cache)

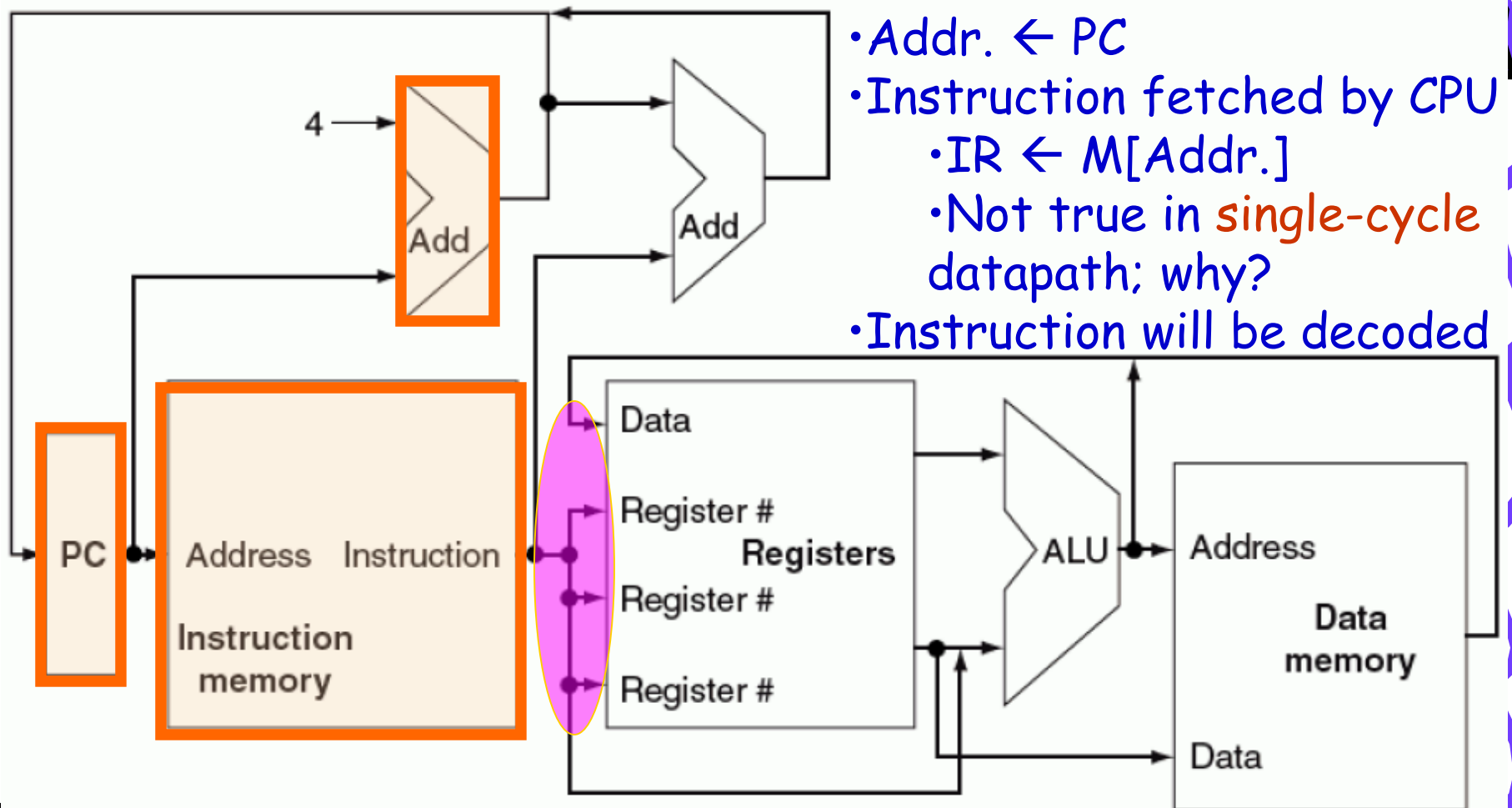 

Instruction Fetch Unit



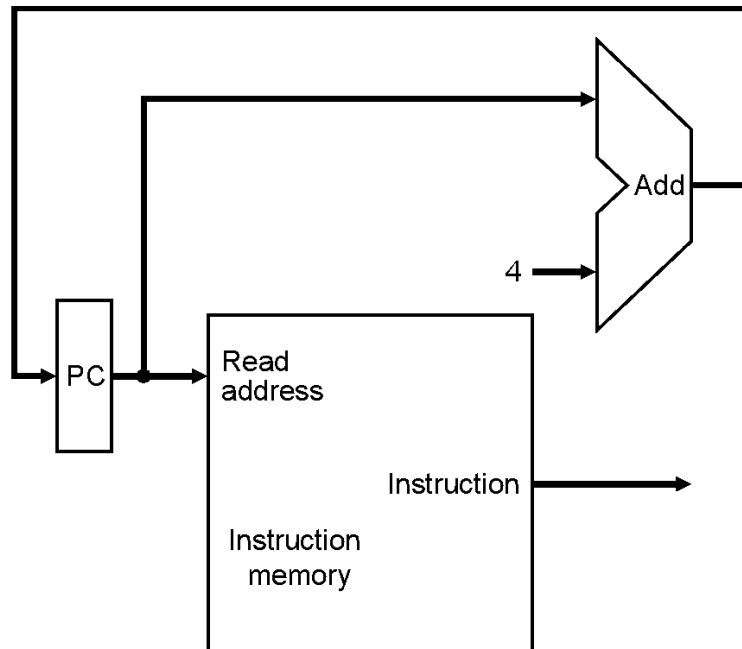- Updating PC for Next Instruction
 - Sequential Code: $PC \leftarrow PC + 4$
 - Branch and Jump: $PC \leftarrow \text{New Address}$
 - we'll worry about this later



Instruction Encoding



- MIPS Instruction Format

	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
r format	OP	rs	rt	rd	sa	funct
i format	OP	rs	rt	immediate		
j format	OP	target				

- OP: opcode
- rs: first register source operand
- rt: second register source operand
- rd: register destination operand
- sa: shift amount
- funct: function code




Instruction Encoding (cont.)




- R-TYPE

- *add rd, rs, rt*
- *sub, and, or, slt*

 


- LOAD / STORE

- *lw rt, rs, imm*
- *sw rt, rs, imm*

 


- BRANCH

- *beq rs, rt, imm*

 

R-Type Encoding

 


add \$4, \$3, \$2

rd

rt


rs

 

0 0 0 0 0 0 0 0 0 1 1 0 0 0 1 0 0 0 1 0 0 0 0 0 0 0 1 0 0 0 0 0

Encoding = 0x00622020

Register File

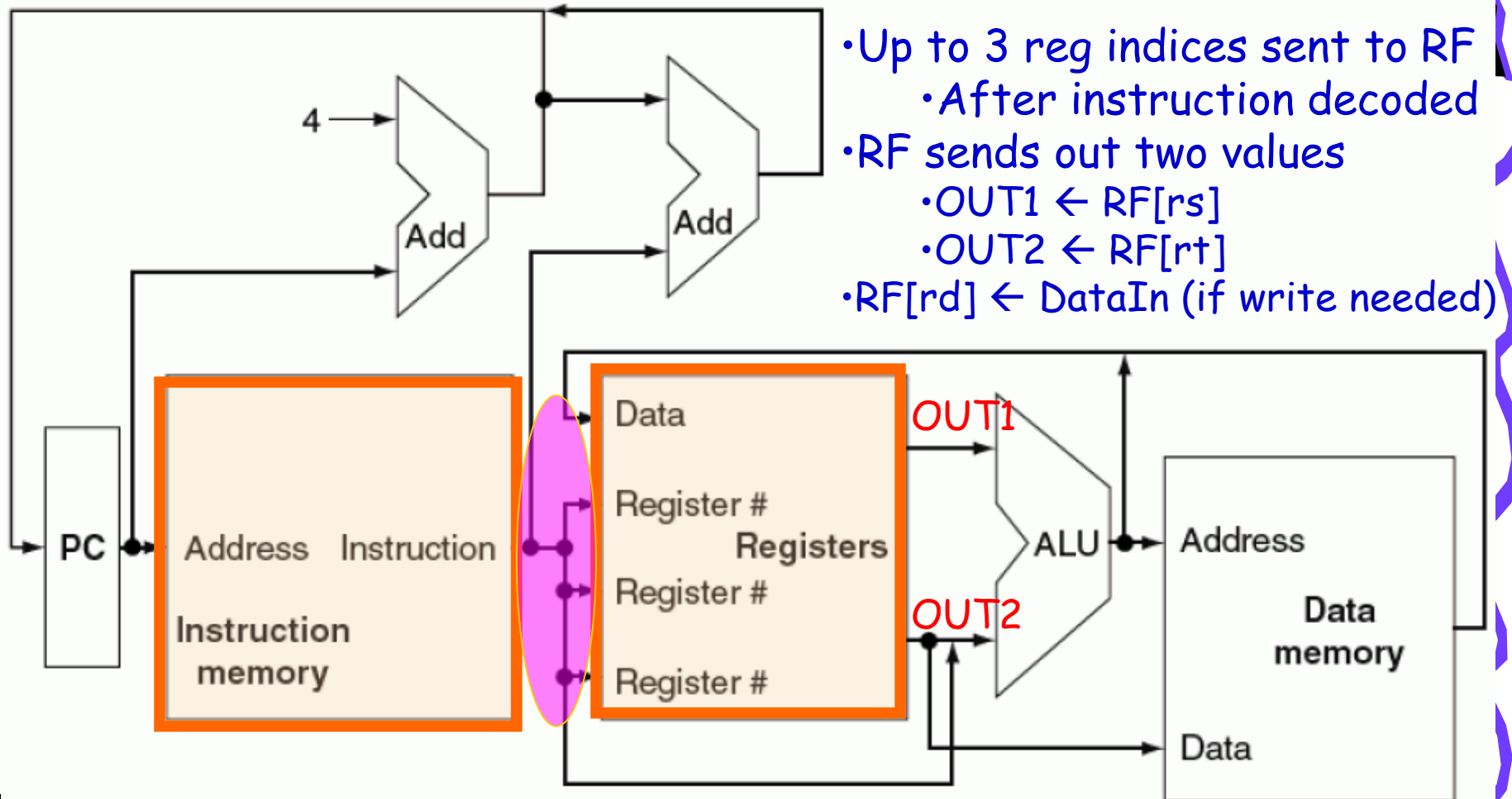


- Up to 3 reg indices sent to RF
 - After instruction decoded
- RF sends out two values
 - $OUT1 \leftarrow RF[rs]$
 - $OUT2 \leftarrow RF[rt]$
- $RF[rd] \leftarrow DataIn$ (if write needed)

Datapath Elements



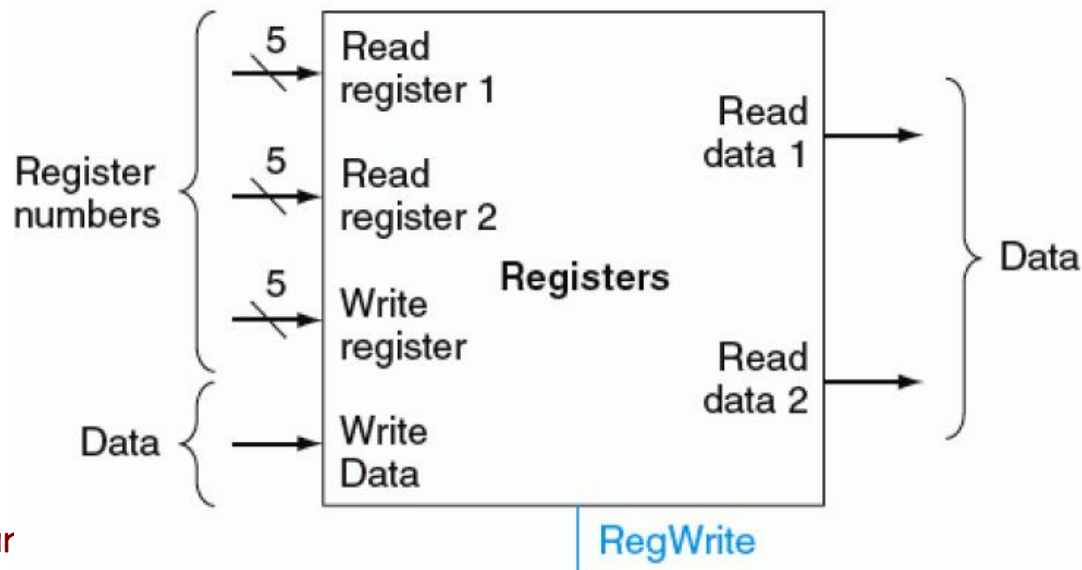
- Register File (RF)
 - Also called, General Purpose Registers (GPR)
 - Up to three indices as inputs
 - 32-bit write input data
 - Two 32-bit outputs



Datapath Elements (cont.)



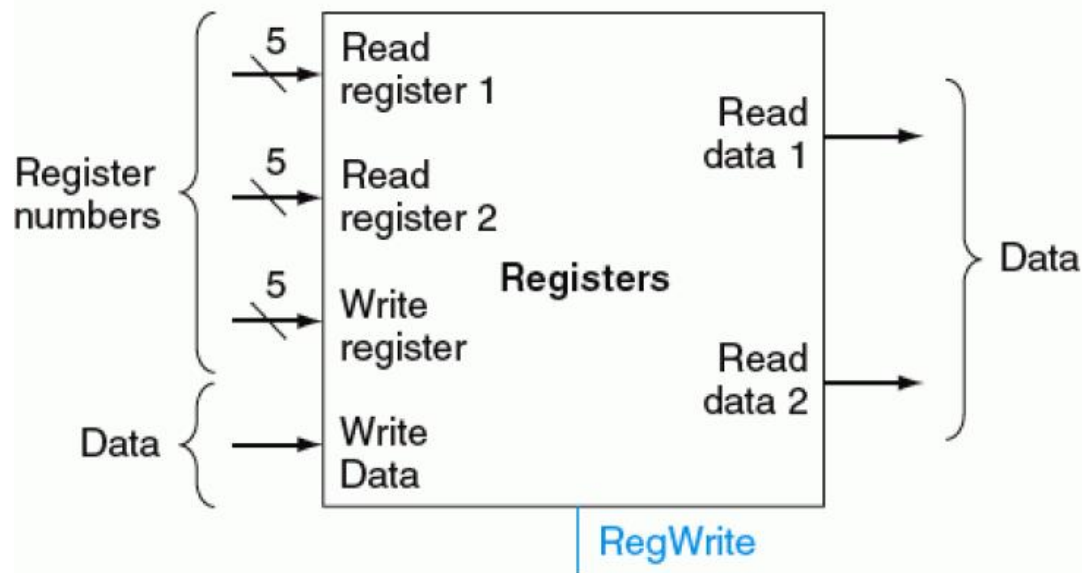
- Question 1:
 - How read & write can be accomplished in one clock cycle without data contention?




Datapath Elements (cont.)



 - Question 2:
 - How two simultaneous read operations possible?



ALU

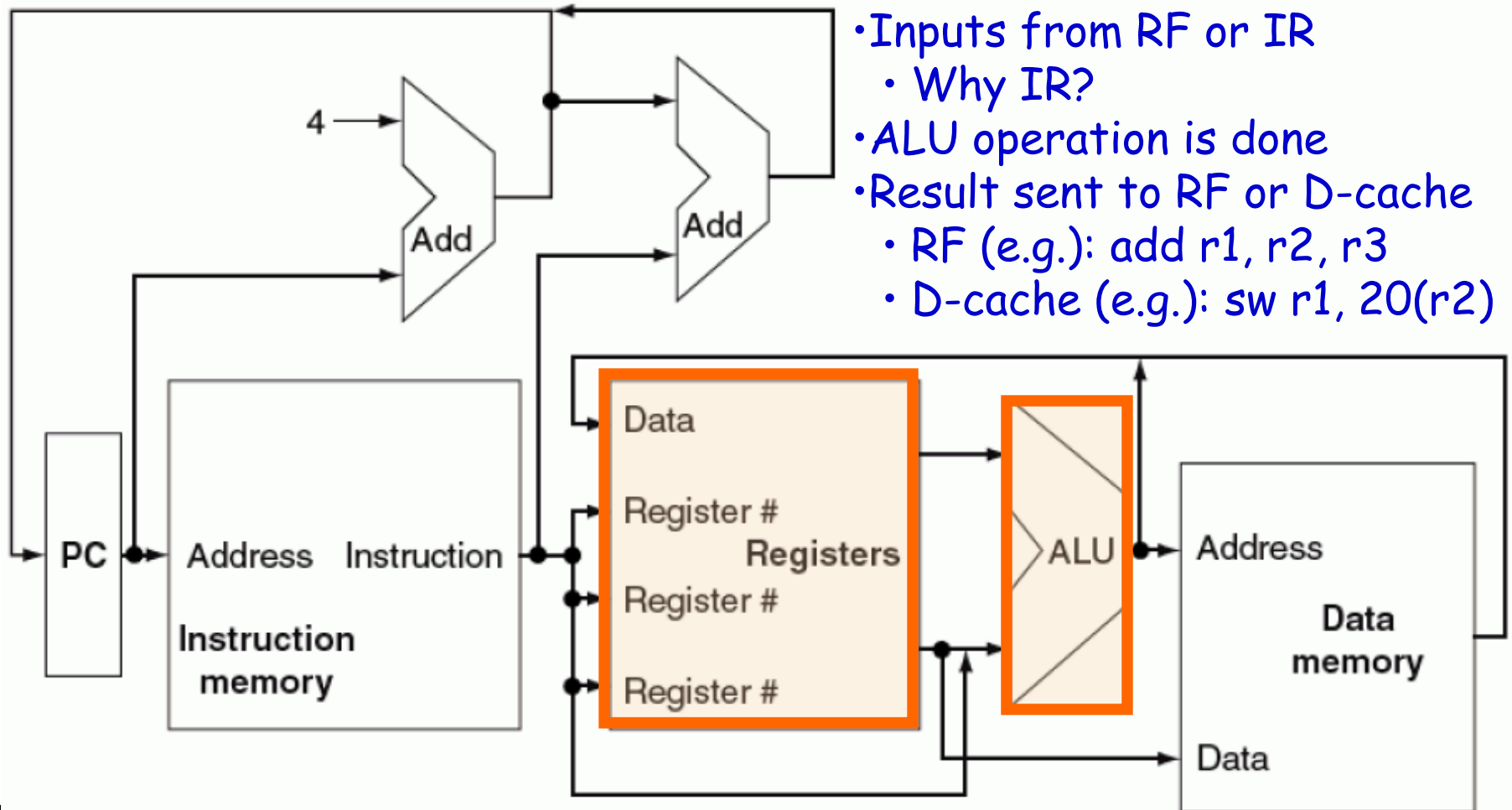


- Inputs from RF or IR
 - Why IR?
- ALU operation is done
- Result sent to RF or D-cache
 - RF (e.g.): `add r1, r2, r3`
 - D-cache (e.g.): `sw r1, 20(r2)`

Reminder: Addressing Modes





Operand is constant

1. Immediate addressing



 


Operand is in register

2. Register addressing

 
 


3. Base addressing

   




lb \$t0, 48(\$s0)

4. PC-relative addressing

  

bne \$4, \$5, Label
(label will be assembled into
a distance)

5. Pseudodirect addressing

   


j Label





Datapath Elements (cont.)



 - ALU
 - Two 32-bit inputs
 - One 32-bit output
 - 4-bit operation selector
 - Zero?



Data Memory (D-Cache)

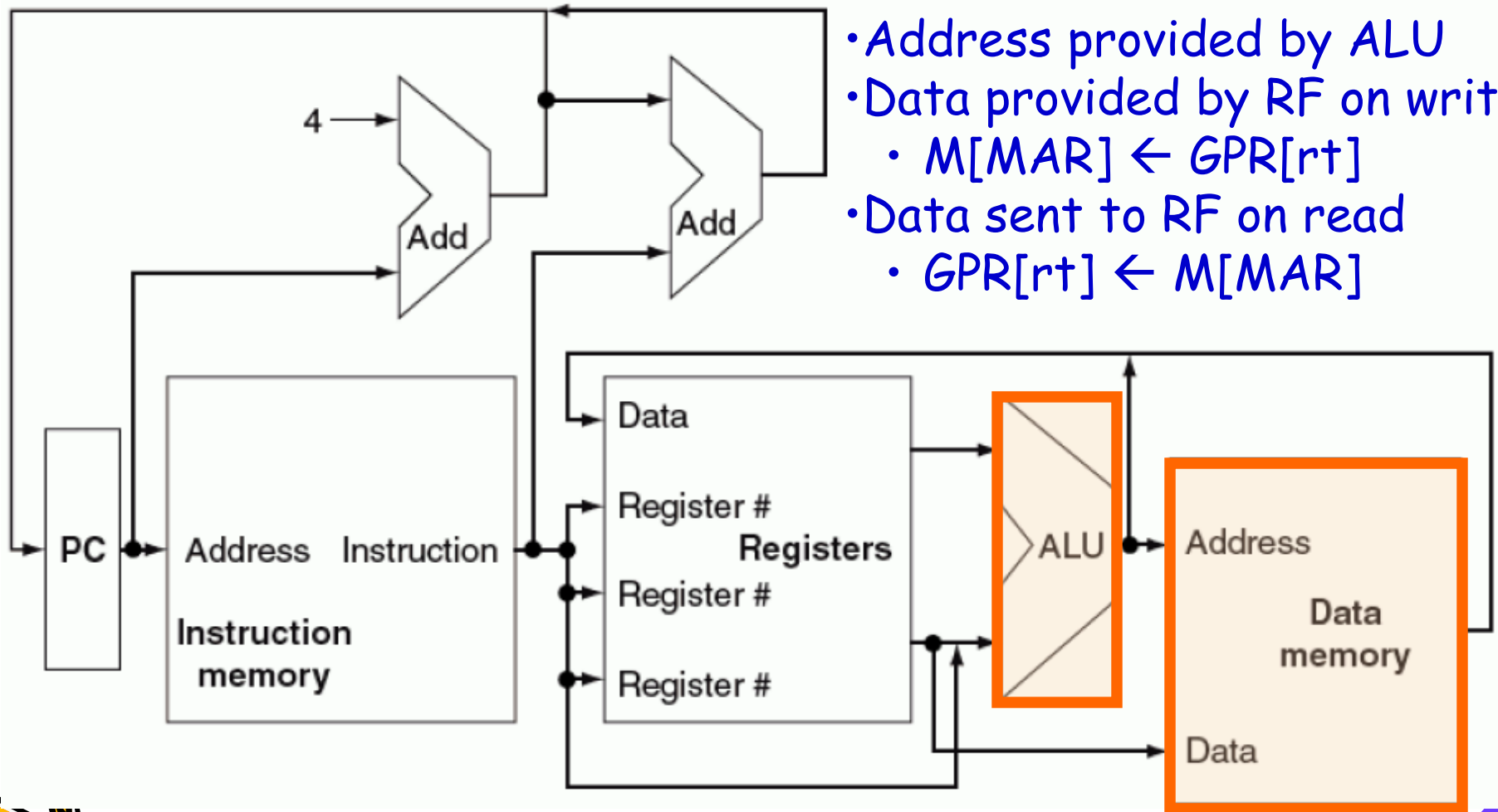 


- Address provided by ALU
- Data provided by RF on write
 - $M[MAR] \leftarrow GPR[rt]$
- Data sent to RF on read
 - $GPR[rt] \leftarrow M[MAR]$



Datapath Elements (cont.)



 - Data Memory Unit
 - Address
 - Loads/store: $MAR = GPR[rs] + imm16$
 - 32-bit write data
 - Write data $\leftarrow GPR[rt]$
 - 32-bit read data
 - $GPR[rt] \leftarrow \text{Read data}$
 - MemRead signal
 - MemWrite signal





Discussion



- Compare **MemRead** and **MemWrite** Activation Process in Following Cases
 - Case A: separate I-cache & D-cache with separate data bus
 - Case B: separate I-cache & D-cache with common data bus
 - Case C: unified I-cache & D-cache




Abstract View of MIPS Implementation

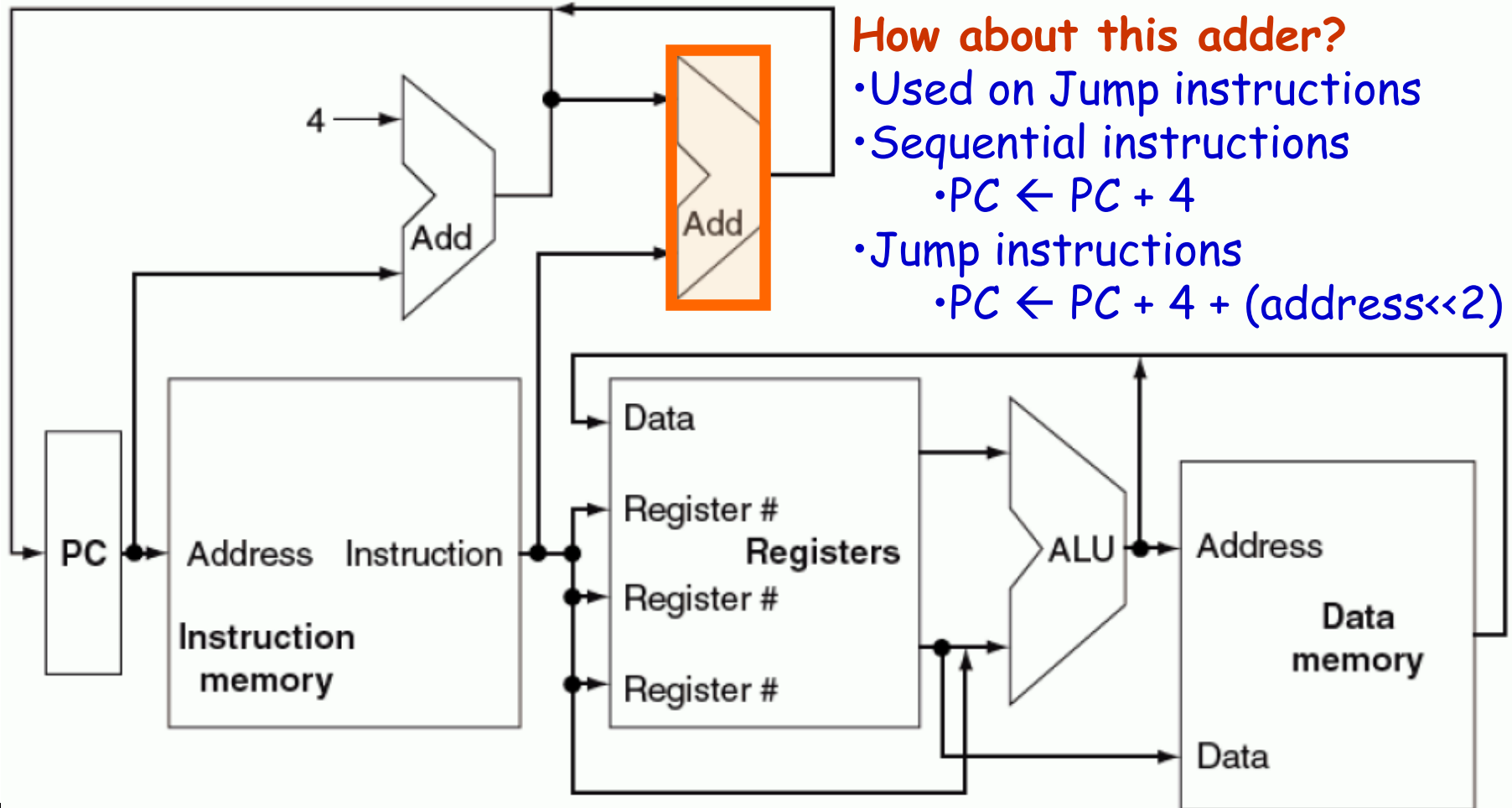 

Datapath Elements (cont.)




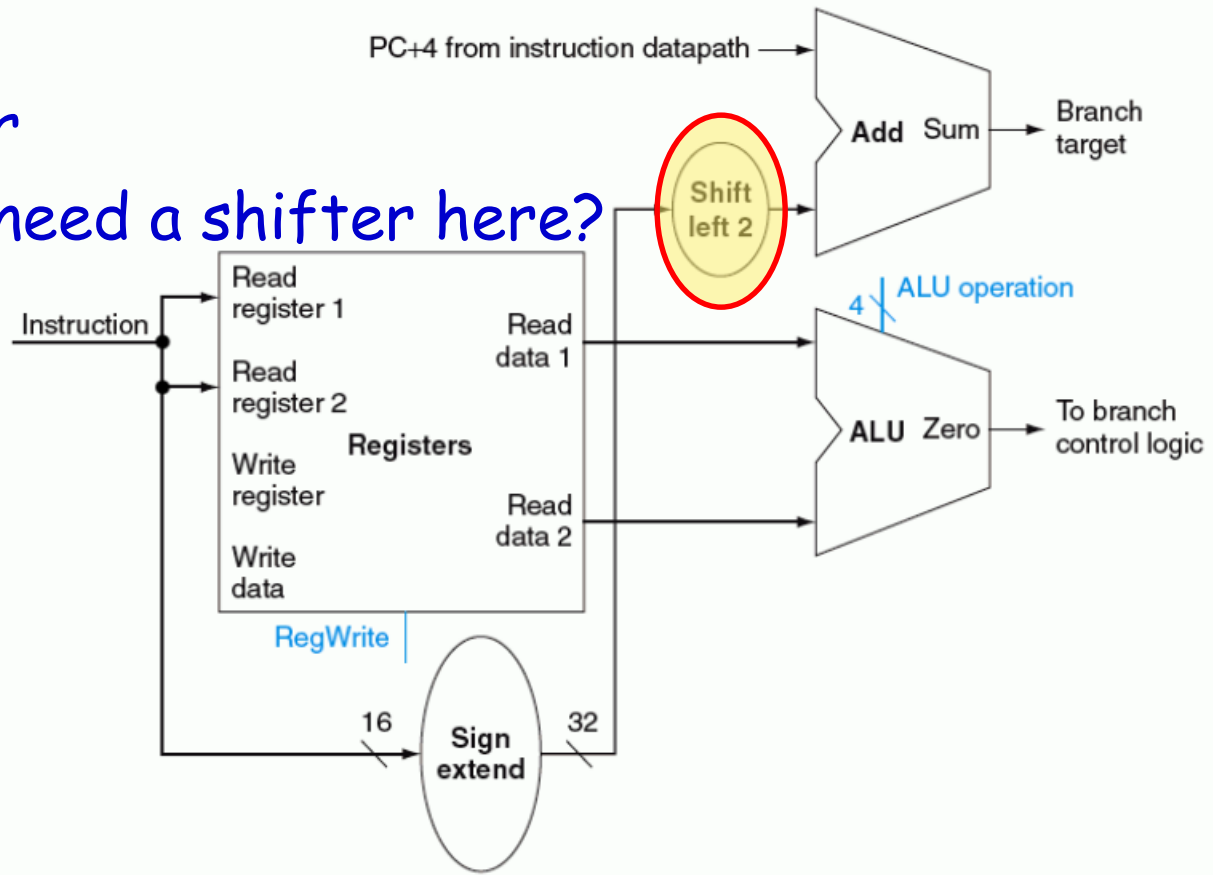- Branch Unit
 - Sign extend unit
 - Adder
 - Shifter
 - Do we need a shifter here?




Practice

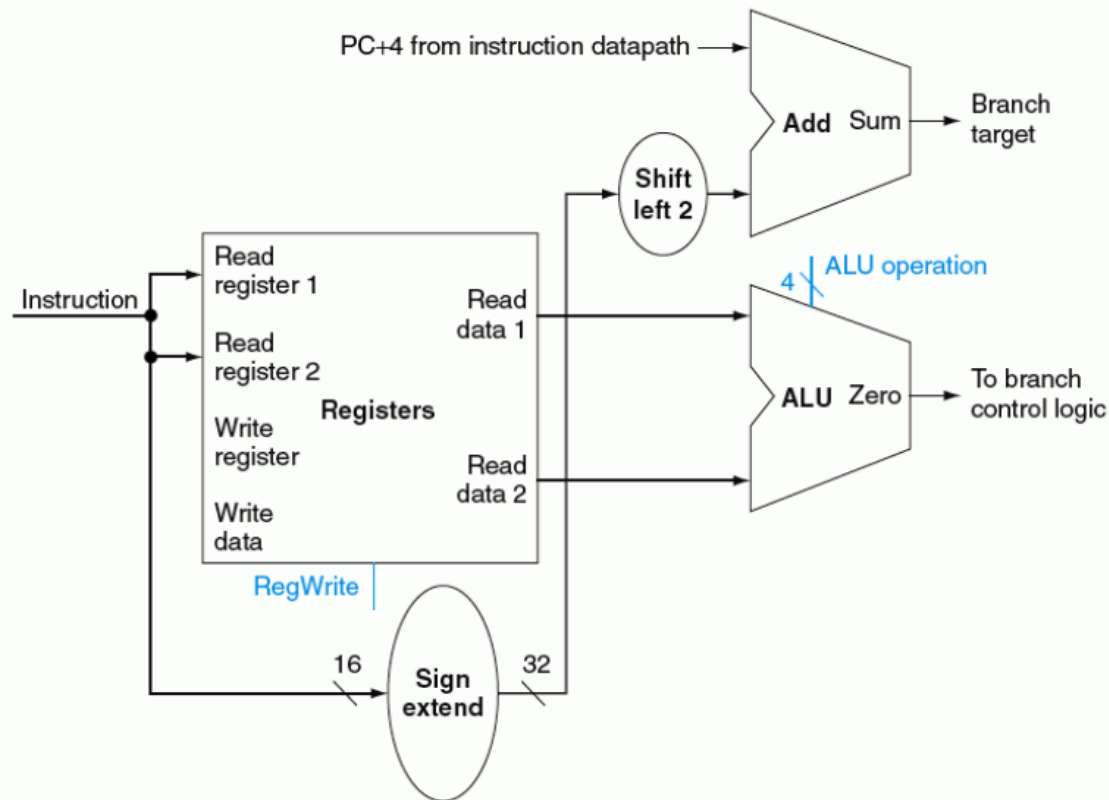
- In Following Circuit:
 - Draw sign-extend & shift logic



Address Bus & Data Bus

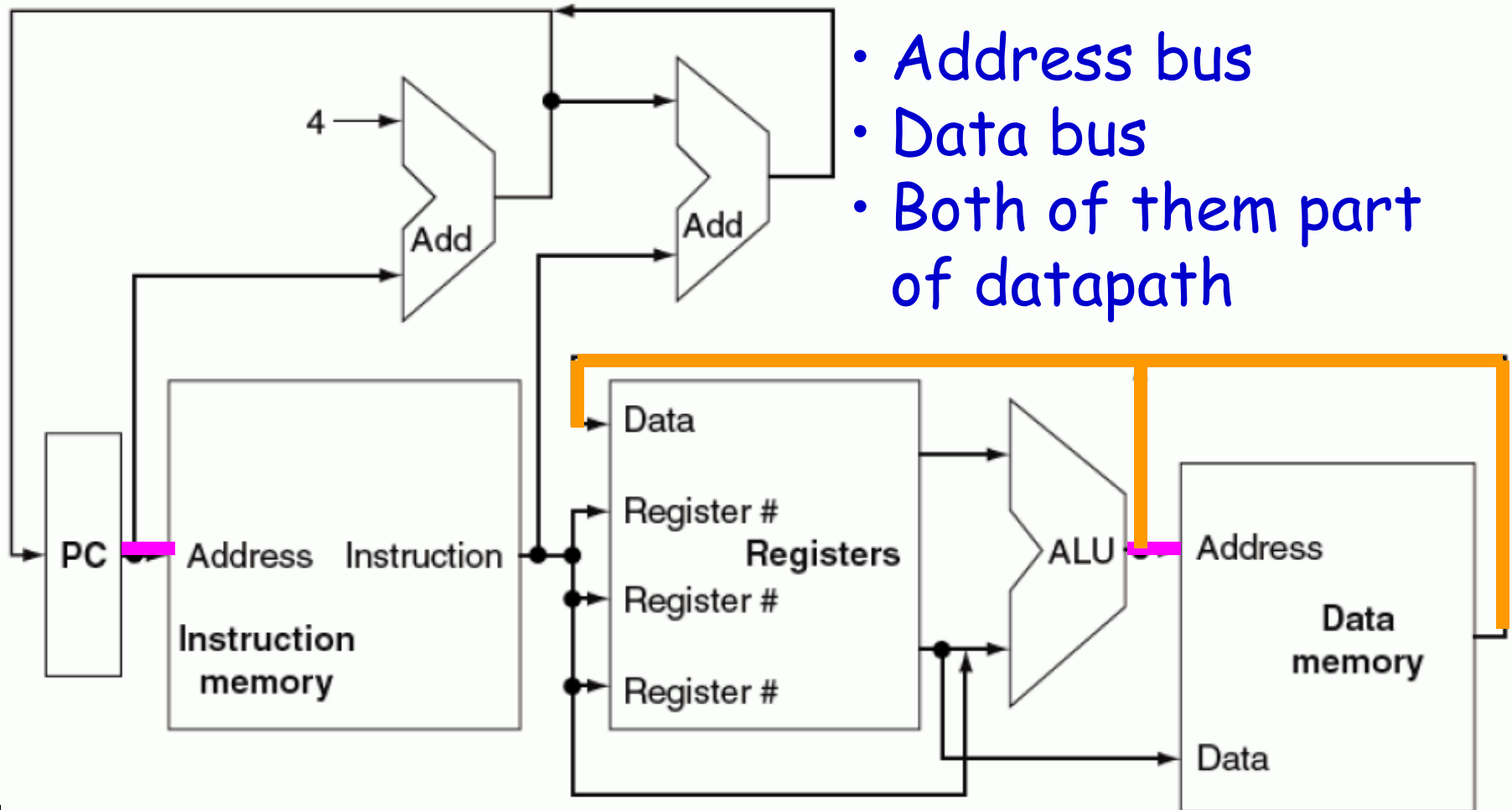


Combining Datapaths

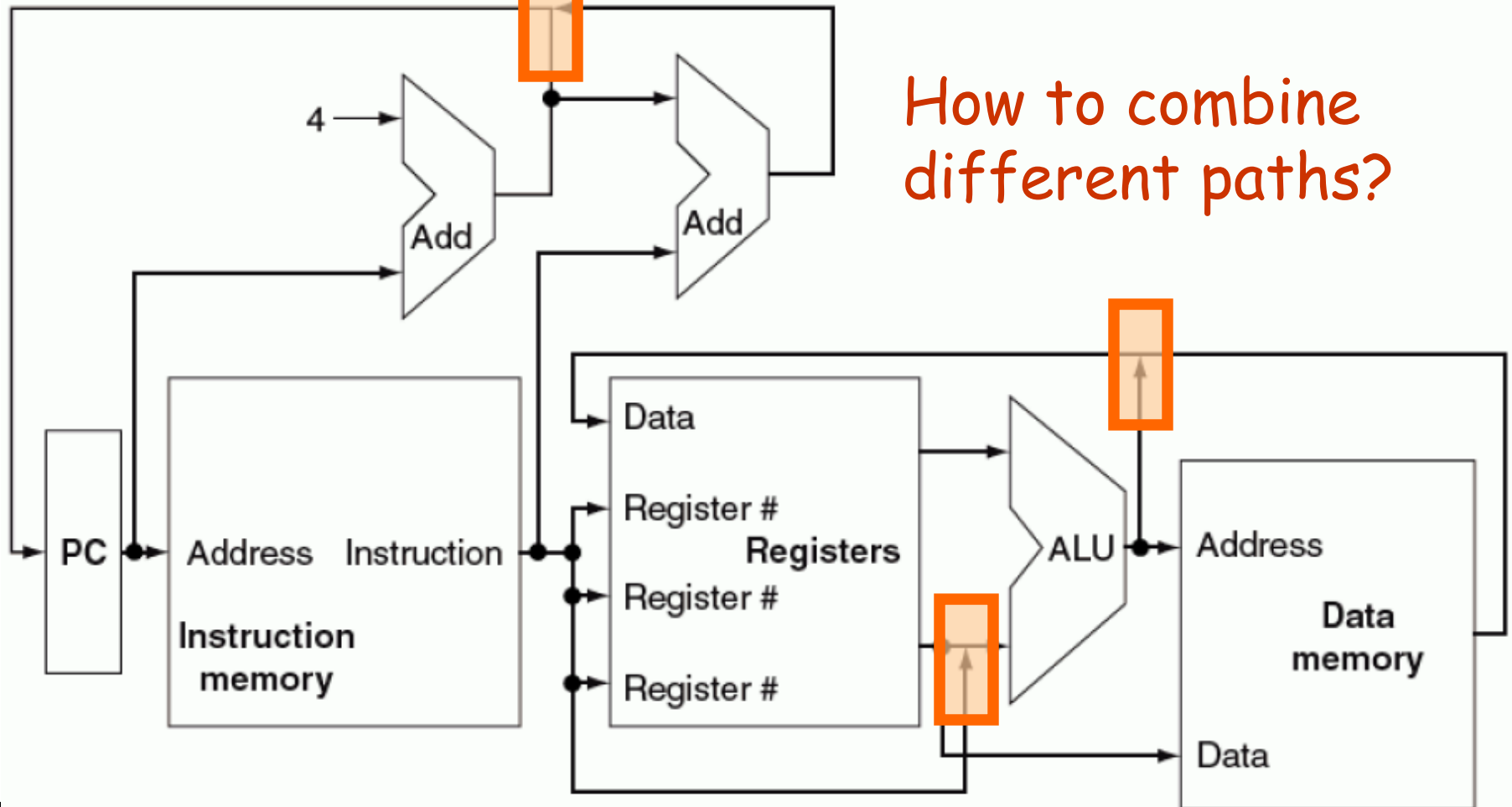


Combining Datapaths (cont.)



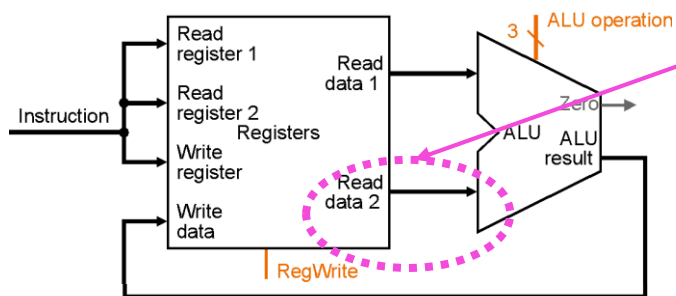- How to have different datapaths for different instruction?



R-type

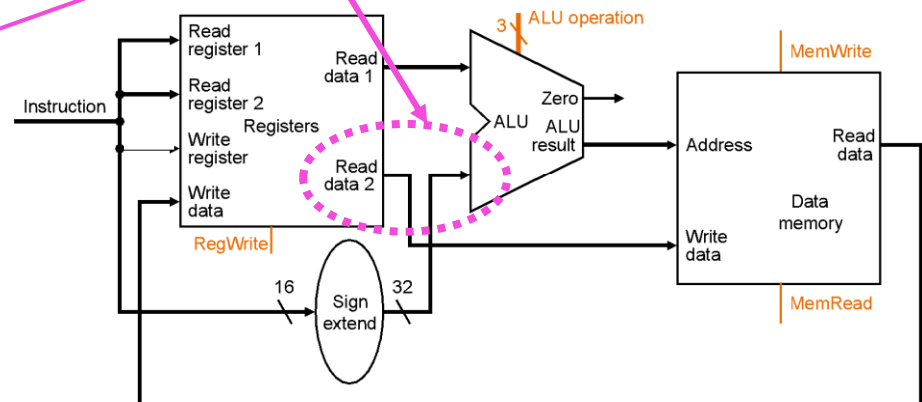



Store




Combining Datapaths (cont.)



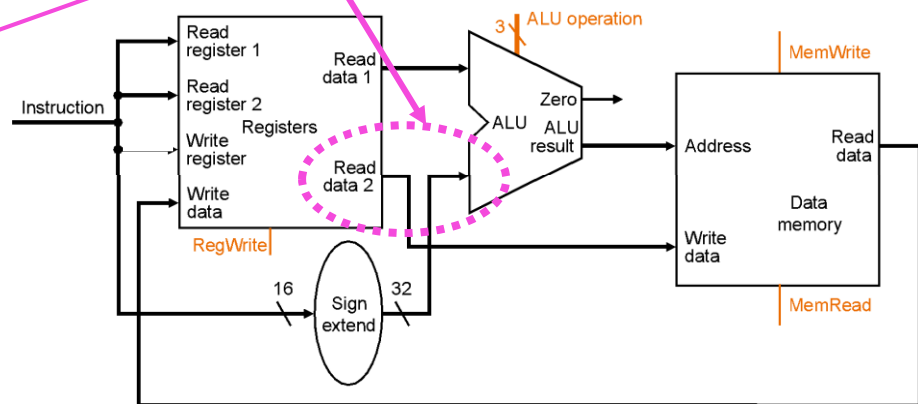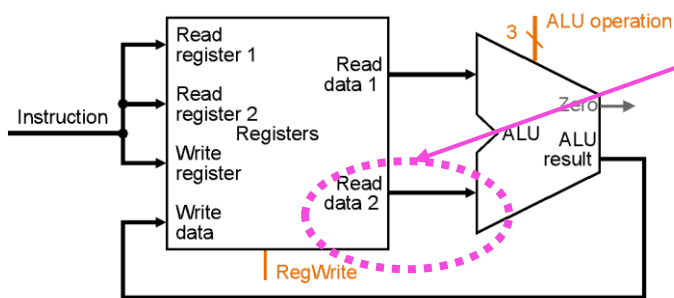- How to have different datapaths for different instruction?




- Use a multiplexer

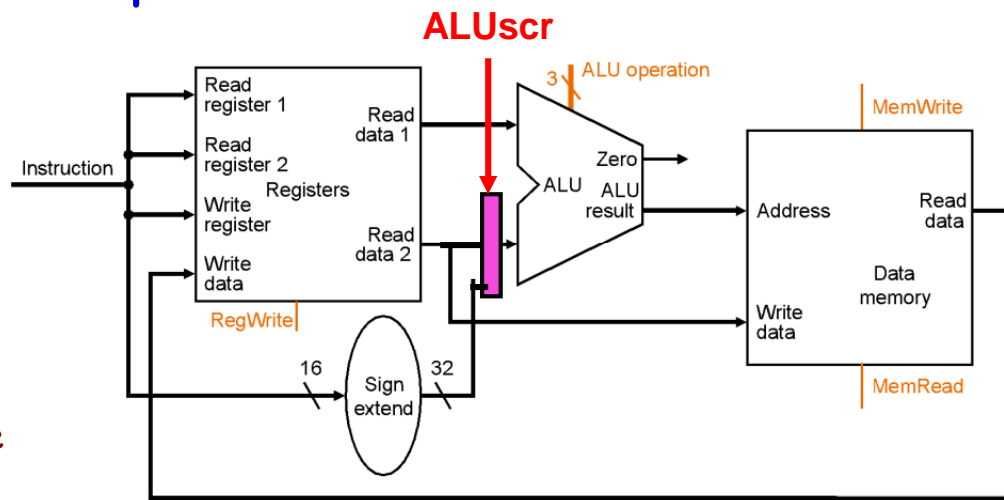



Combining Datapaths (cont.)



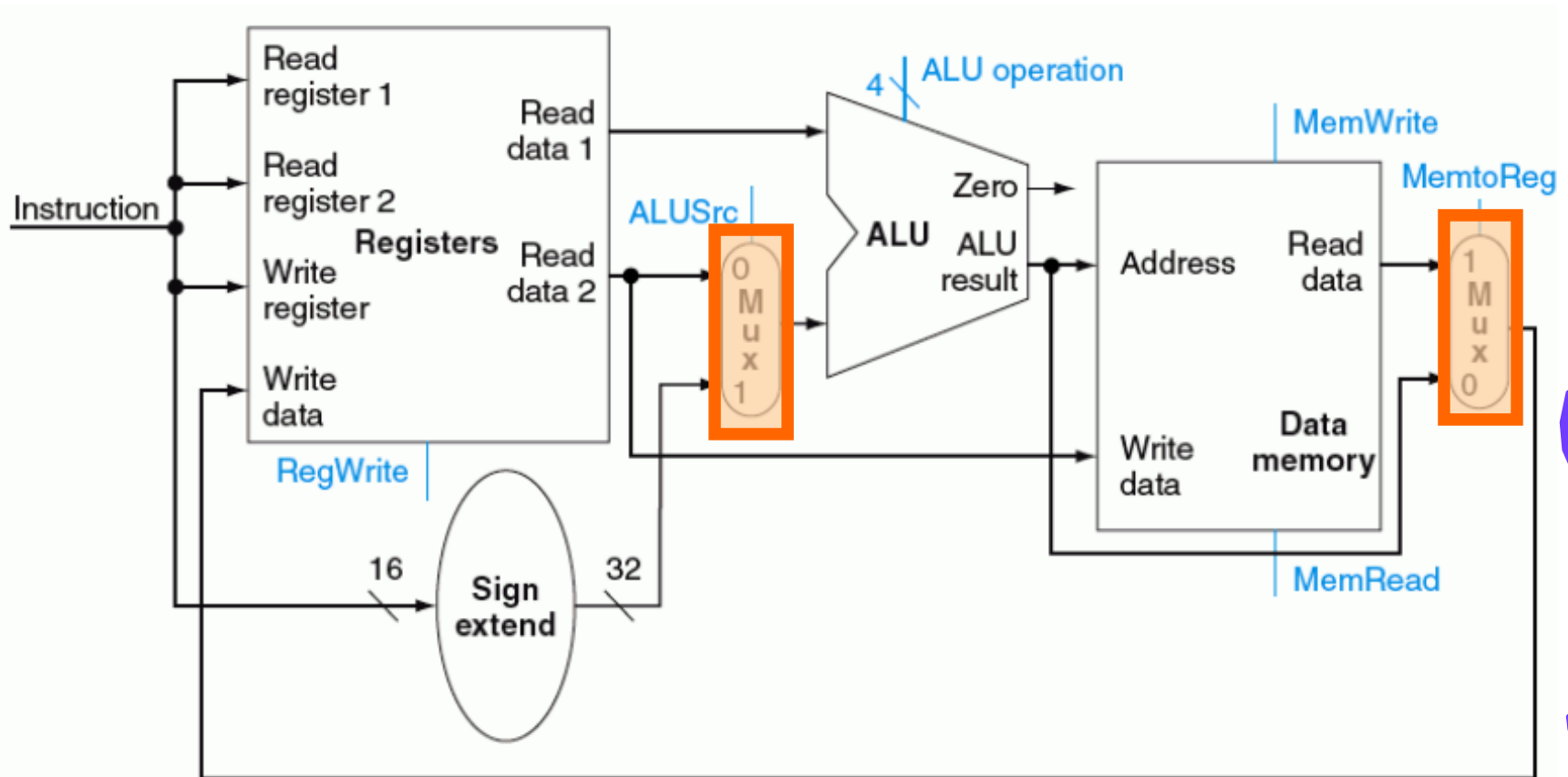- Merging R-type datapath with load/store datapath using multiplexer



All Together: Single Cycle Datapath

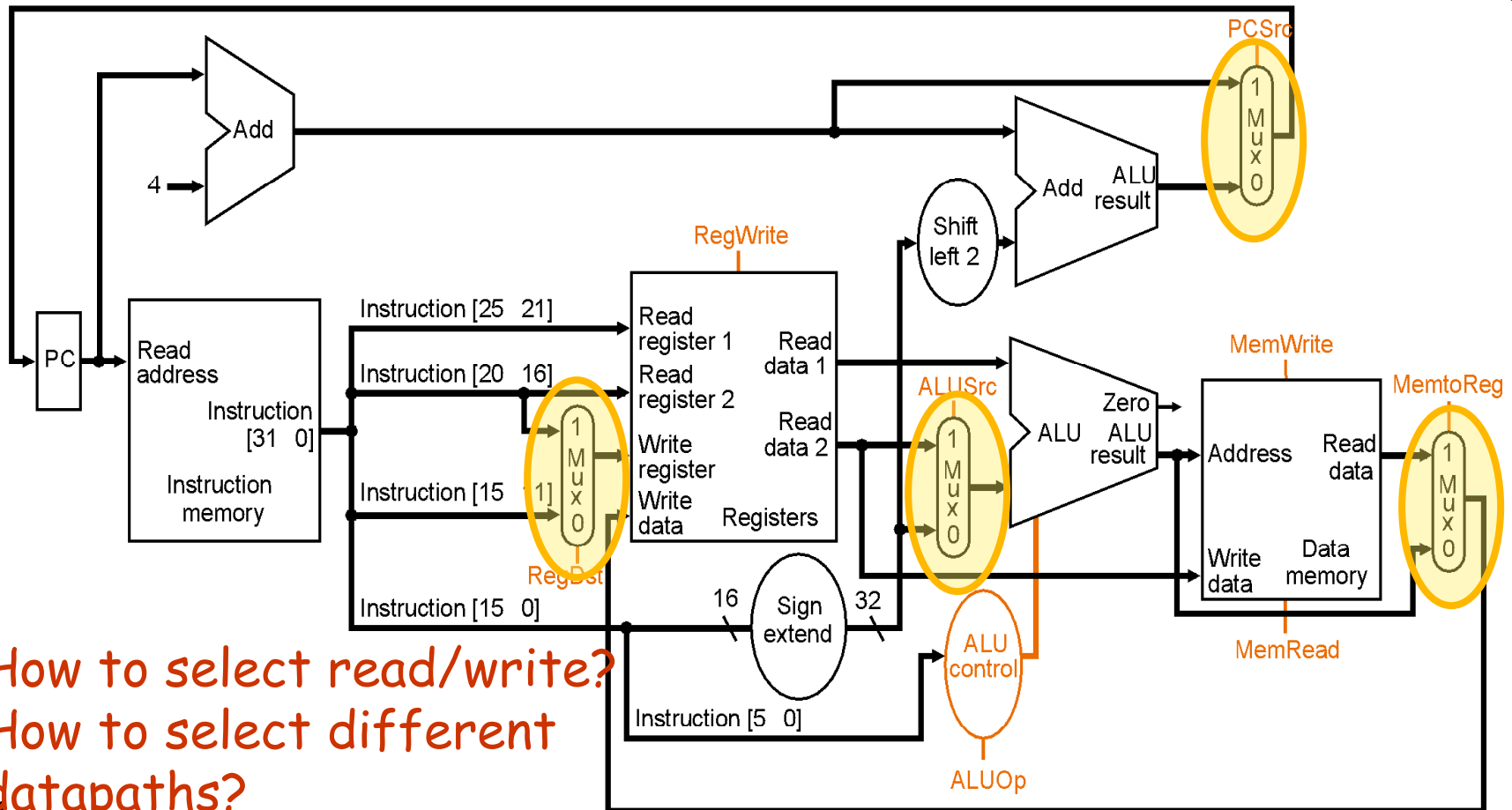 

How to select read/write?
How to select different
datapaths?




Practice



- Question:
 - Could we swap rs, rt, & rd bits to have easier datapath design?
 - In other words, can we remove RegDst MUX?



Practice: Answer

 

- R-type
 - rs & rt: read index bits
 - rd: write index bits
- lw:
 - rs: read index bits
 - rt: write index bits
- sw:
 - rs & rt: read index bits




Reminder: Instruction Encoding




- R-TYPE

- *add rd, rs, rt*
- *sub, and, or, slt*

 


- LOAD / STORE

- *lw rt, rs, imm*
- *sw rt, rs, imm*

 


- BRANCH

- *beq rs, rt, imm*

 



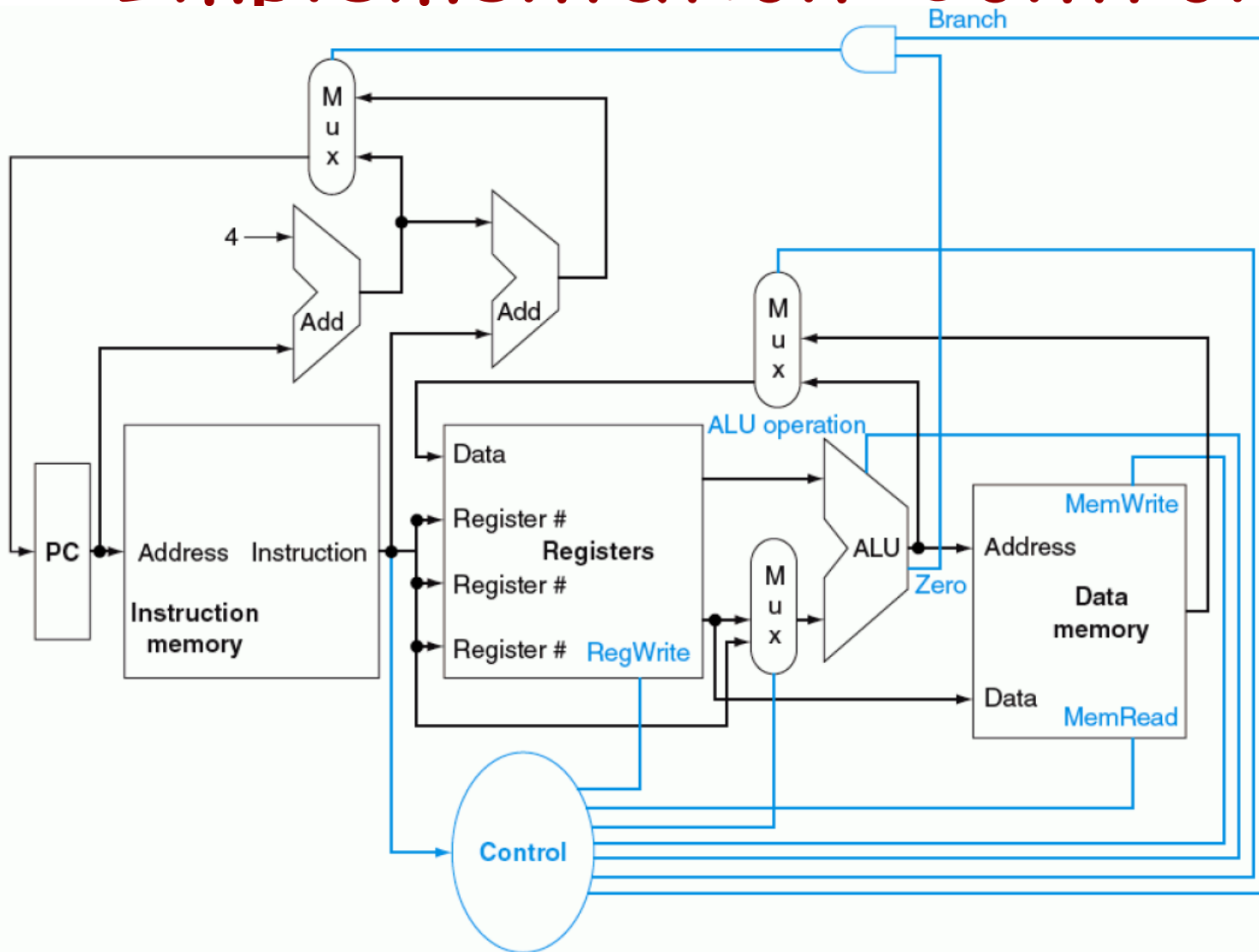
Abstract View of MIPS Implementation: Control



Datapath for Reg-Reg Operations



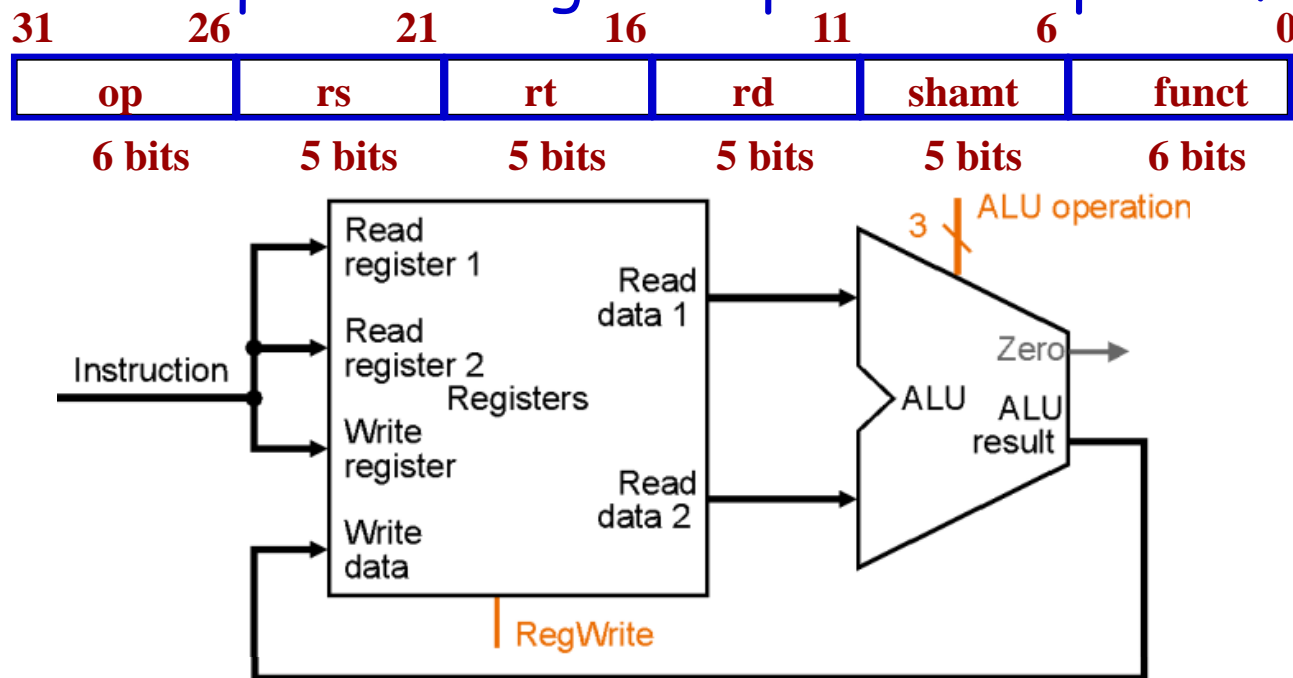- $GPR[rd] \leftarrow GPR[rs] \text{ op } GPR[rt]$
 - Example: *add rd, rs, rt*
 - ALU operation signal depends on op and funct




ALU operation and **RegWrite**: control logic after decoding instruction



Datapath for Load Operations



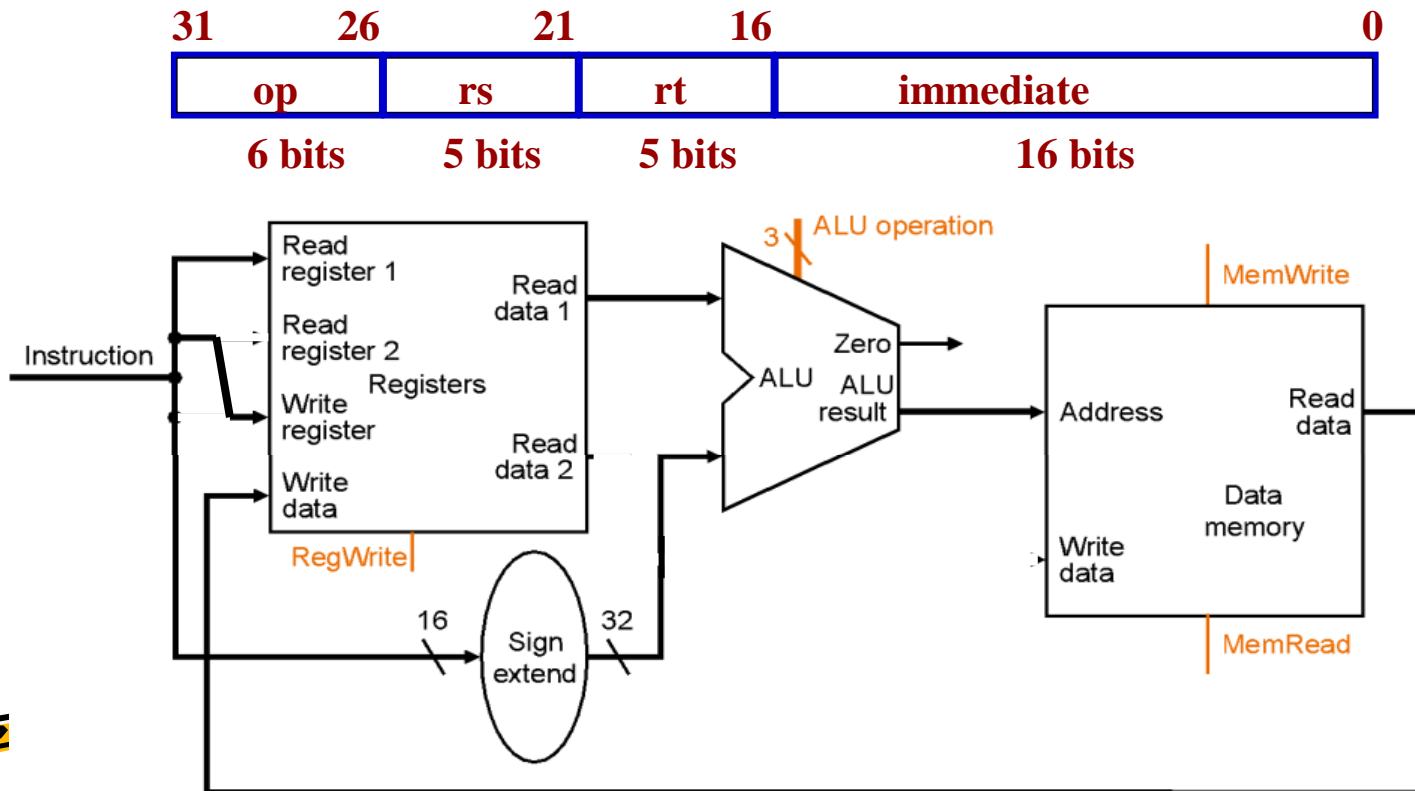
- $GPR[rt] \leftarrow Mem[GPR[rs] + SignExt[imm16]]$
 - Example: *lw rt, rs, imm16*



Datapath for Store Operations




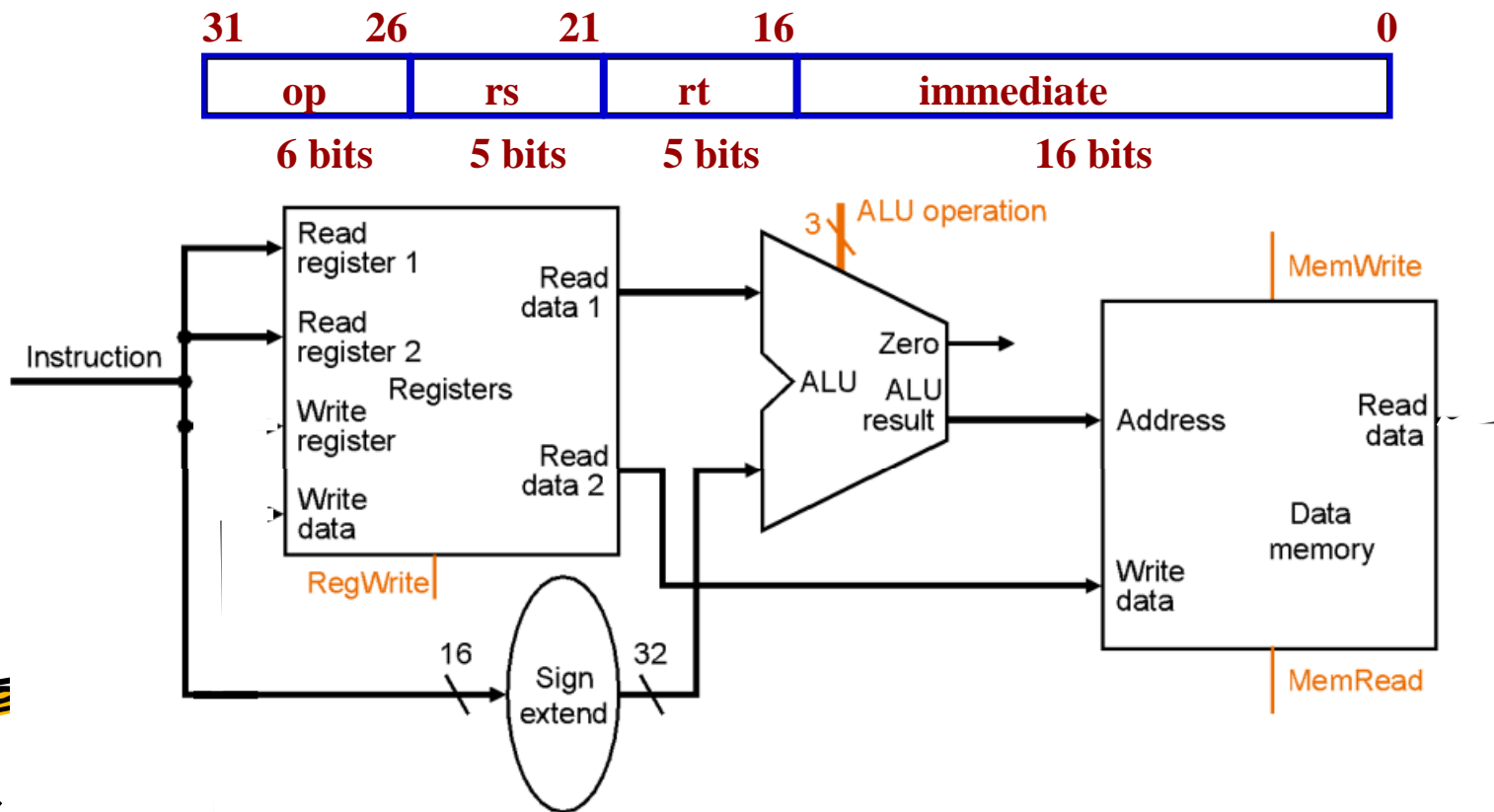
- $\text{Mem}[\text{GPR}[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow \text{GPR}[\text{rt}]$
 - Example: *sw rt, rs, imm16*



Datapath for Branch Operations



- beq rs, rt, imm16*

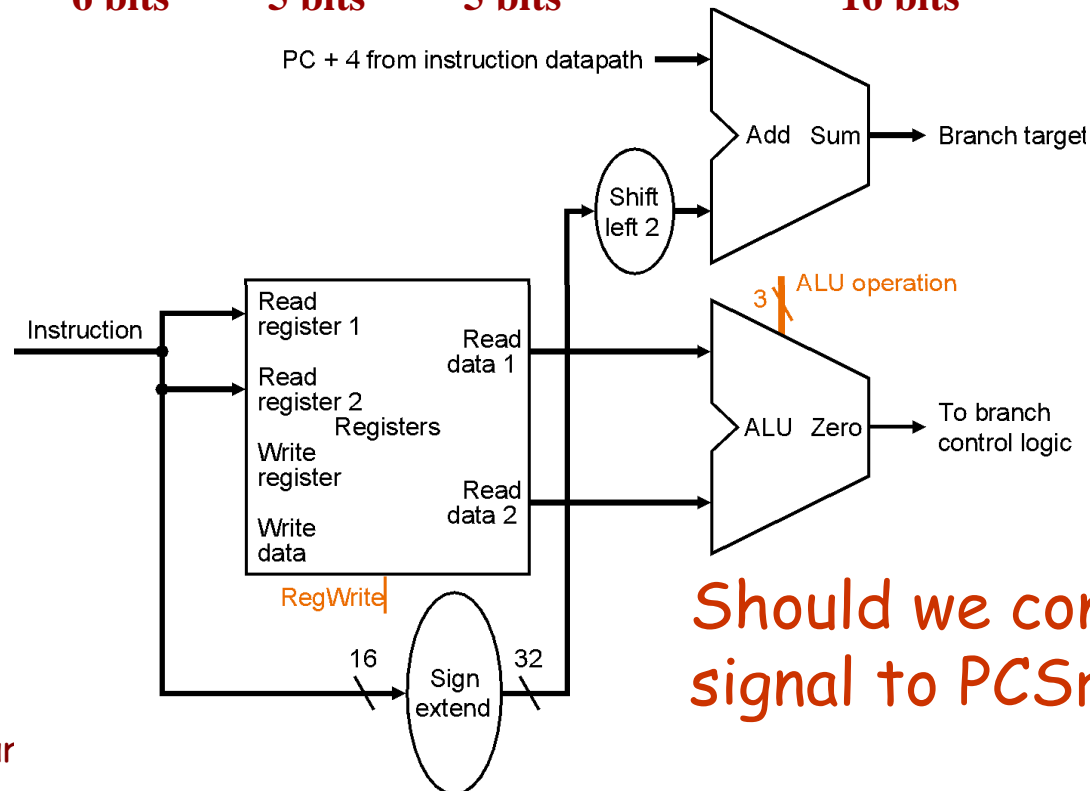 


Should we connect "Zero" signal to PCSrc selector?



A stylized illustration of a yellow pencil with a purple eraser and a purple band near the tip. The pencil is oriented vertically, pointing downwards. It has a black outline and a black oval in the center of the yellow body. The eraser is purple with a black outline, and there is a purple band near the tip. The pencil is set against a white background.




Load Datapath

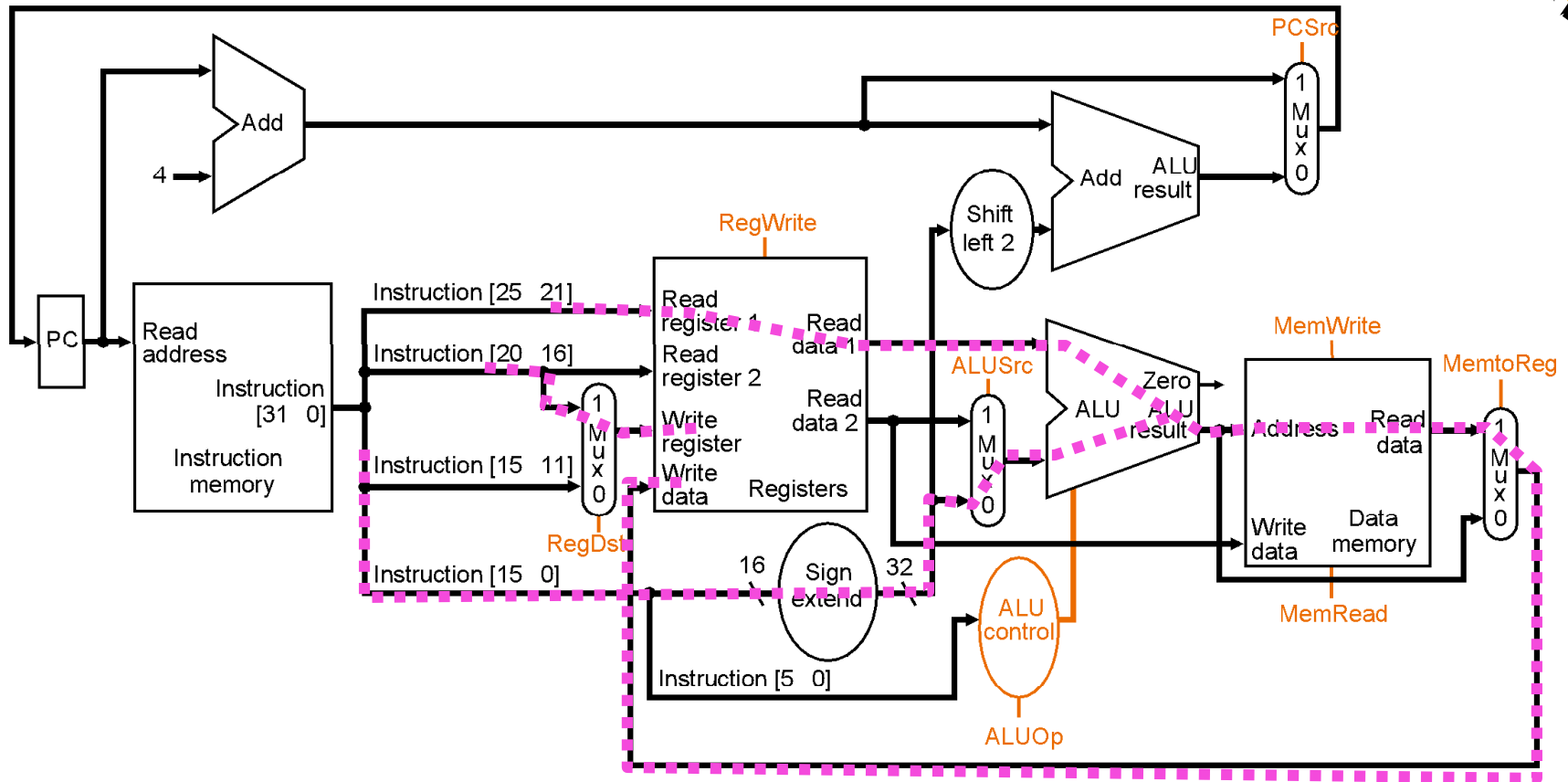


What control signals do we need for load??


Store Datapath

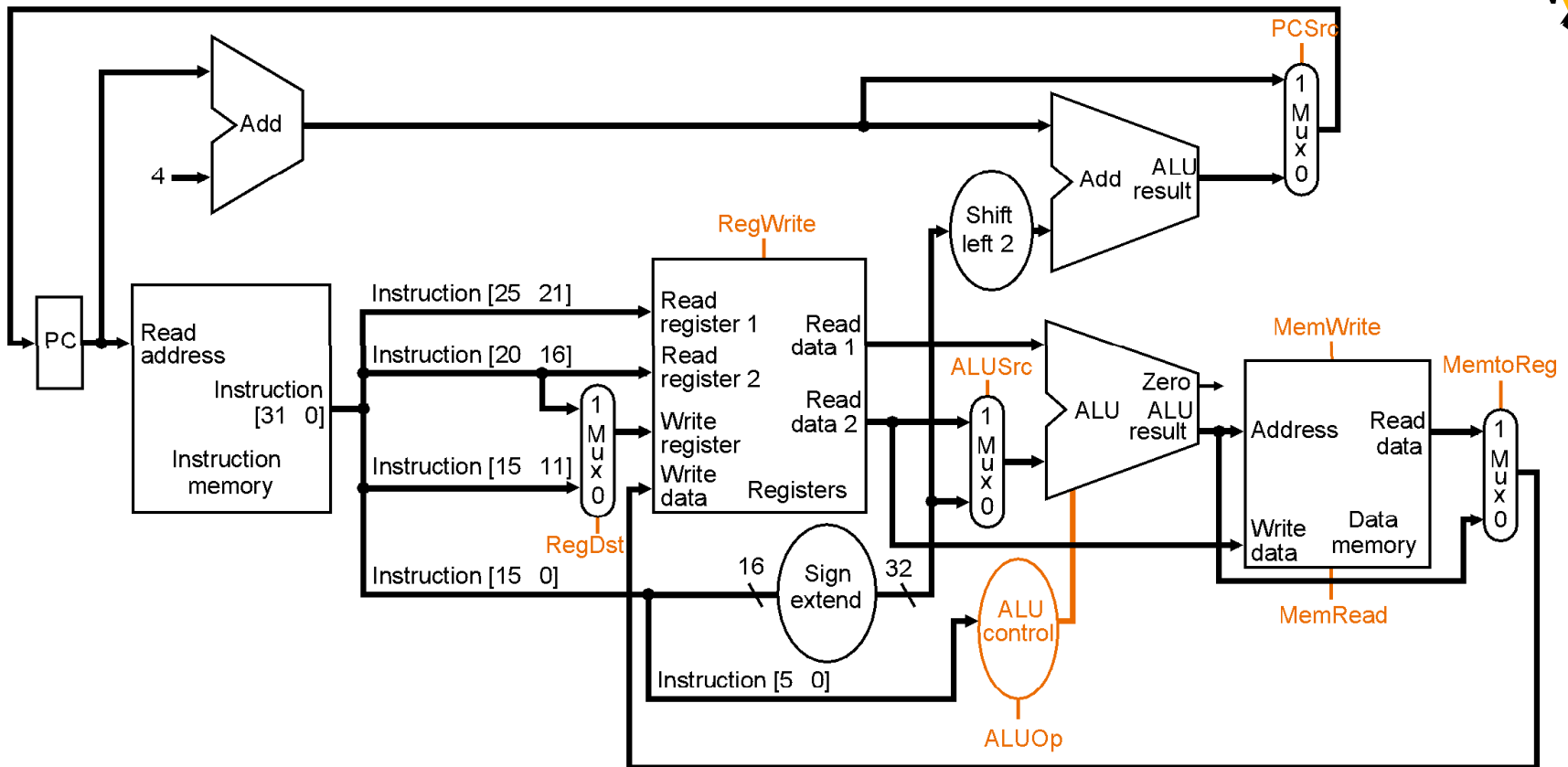

beq Datapath

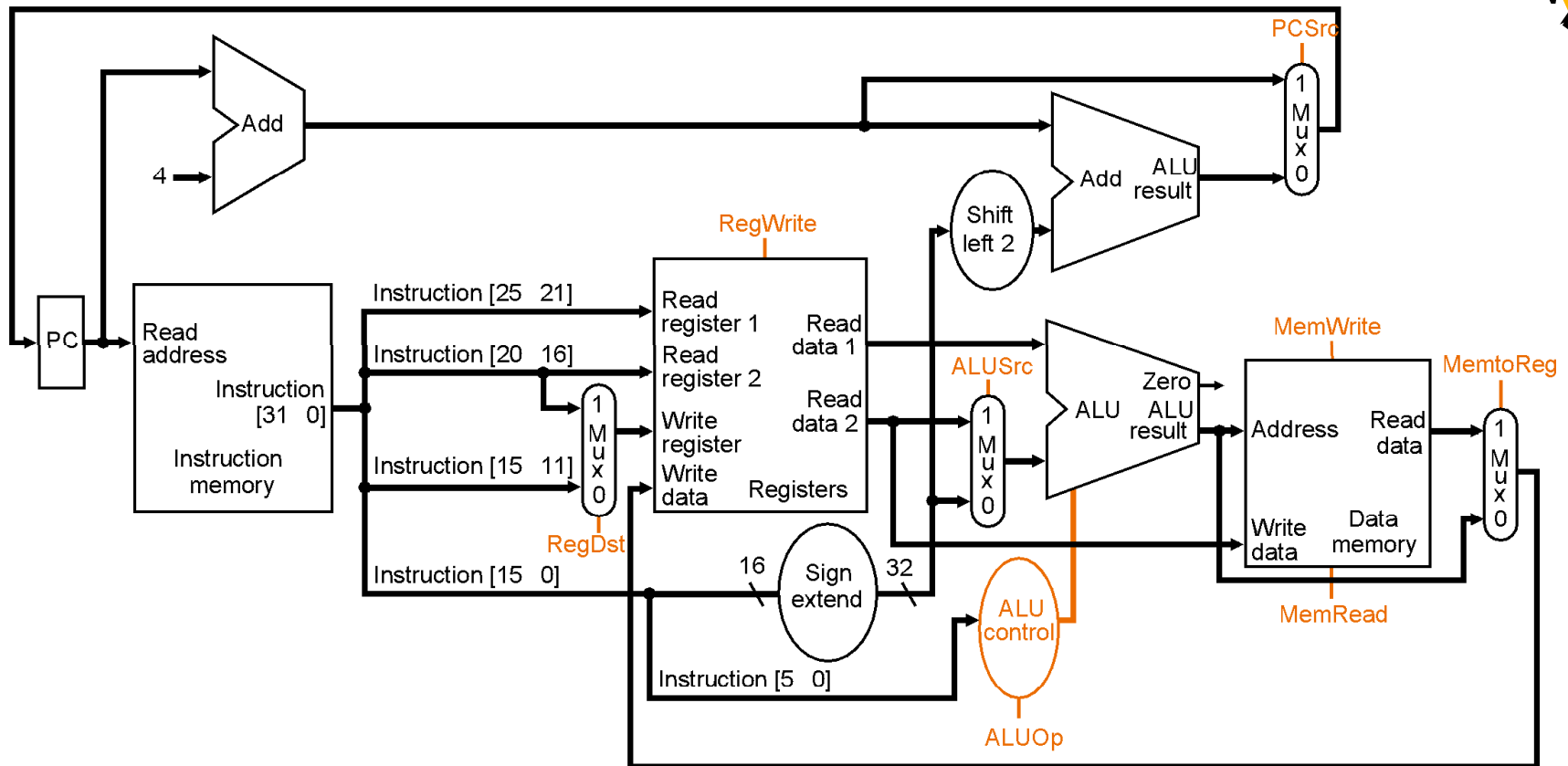

Putting it All Together

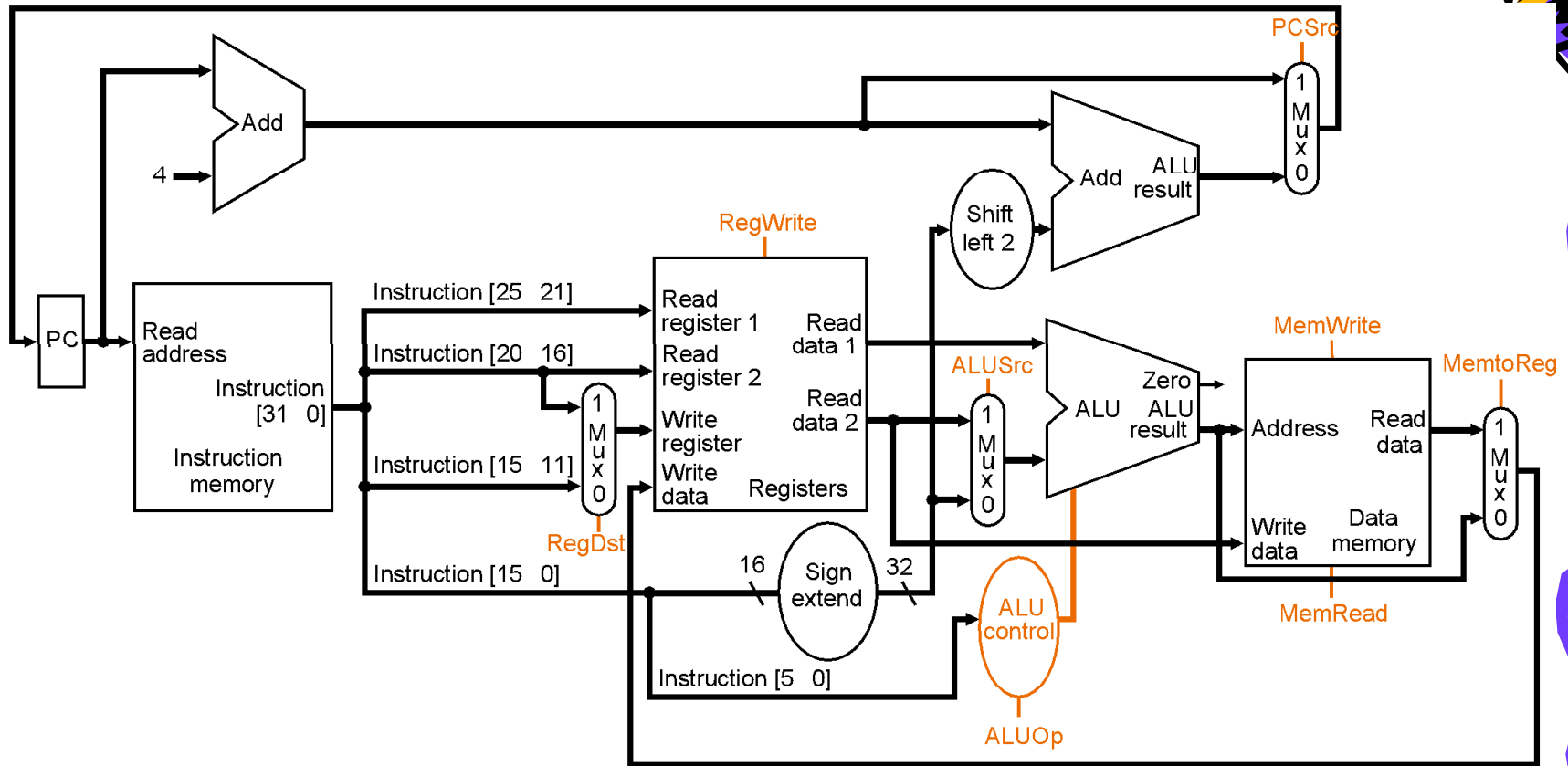

We have everything except details for generating control signals

Backup

